

Electrical Science

Rose-Hulman Institute of Technology

R.J. Marks II Class Notes

(1969-1970)



E. SCL
I

ENCYCLOPEDIA OF ELECTRICITY

WEEK-CLASS	CH.	PAGES	TOPIC	PROBLEMS
Oct. 1	1-1 1-2 1-3	1 1-17 17-21	Voltage Current	5, 8 12, 19
Oct. 7	2-1 2-2 2-3	2 29-43 43-55	V-I Curves Sources-Connections	1, 3, 4, 6 7, 9, 10 15, 16, 19, 21
Oct. 14	3-1 3-2 3-3	3 61-67 67-73	Hank Kirchoff's Laws Node-Datum	2, 4, 5 6, 7, 9 9, 11, 12
MIDWINTER				
Oct. 21	4-1 4-2 4-3	74-79 79-85	Mesh Currents Non-Linear Elements	13, 14, 15, 16 17, 19, 20 22, 24, 25
Oct. 28	5-1 5-2 5-3	86-91	Dep. Sources-Superpos.	26, 28, 29 32, 33, 34 35, 36, 38
Nov. 4	6-1 6-2	105-116 116-133	Equivalence Thevenins-Norton	1, 2, 3, 5 6, 7
Mid-Terms	6-3			10, 11, 12, 14
Nov. 11	7-1 7-2 7-3	133-142	3-Node Equiv. Slush Day	15, 18 19, 21, 22, 24
Nov. 18	8-1 8-2 8-3	195-203 203-223 205-208	Capacitance Inductance Impulse	1, 2, 3, 4 7, 8, 10, 11 12, 14, 15
THANKSGIVING				
Dec. 2	9-1 9-2 9-3	224-225 233-247	Impulse Equivalence R-C, R-L	16 1, 3, 4, 5
Dec. 9	10-1 10-2 10-3	247-256		8, 9, 12, 13 15, 17, 20 21, 22, 25, 27
NEXT QUARTER?	11-1 11-2 11-3	8 265-274 275-287	Slush Day	1, 2, 4, 5 6, 7, 8, 10

today - 13, 14, 15, 16

FRIDAY

ELECTRICAL SCIENCE I

FORMULAS

I. CHAPT I CIRCUIT THEORIES & VARIABLES

A) DEFINITIONS

- 1) Voltage - measure of energy necessary to move charge from one terminal to the other
- 2) Current - Measure of rate charge is moving
- 3) Power = Voltage (Current)

B) Coulomb's law & such

$$1) F = \frac{Q_1 Q_2}{4\pi\epsilon_0 r^2}$$

$$2) E = \frac{dF}{dQ} = \frac{Q_1}{4\pi\epsilon_0 r^2} = \text{electric field intensity (Pt. Charge) in } \frac{Nt}{COUL} = \frac{V}{M}$$

$$a) \epsilon_0 = 8.85 \times 10^{-12} \frac{COUL^2}{Nt \cdot m^2}$$

$$b) \frac{1}{4\pi\epsilon_0} = 9.0 \times 10^9 \frac{Nt \cdot m^2}{COUL^2}$$

$$C) E \text{ between 2 plates} = \frac{Q}{\epsilon_0 A}$$

$$D) F_{FIELD} = QE$$

$$E) \Delta W = \frac{1}{2} mU^2 = QEL \text{ (Independent of path in cons. field)}$$

$$1) \text{ Voltage (DEF)} = V_{21} = \frac{W_{P2} - W_{P1}}{Q} = -\int_1^2 E_L dL = \text{potential difference}$$

$$2) V_{21} = -E_L L_{12}$$

F) Current (DEF)

$$i = \frac{dq}{dt} \text{ in Amps} = \frac{Coul}{sec}$$

G) Current density J in $\frac{A}{m^2}$

$$1) J = \frac{di}{dA}$$

$$2) i = \iint J_n dA$$

H) Charge density ρ (rho) in $\frac{COUL}{m^3}$

$$1) \rho = \frac{dq}{dV}$$

$$2) J_L = \rho U_L$$

J) Cathode Ray Tube

$$1) \frac{1}{2} mU^2 = eV_0 \text{ (EMISION } V=0)$$

$$2) E_L = \frac{V_{01}}{d_p}$$

II. CHAPT II - VOLTAGE - CURRENT RELATIONSHIPS

A) Energy of a Photon - $W = \frac{hc}{\lambda}$

$$1) h = \text{Planck's constant} = 6.63 \times 10^{-34} \text{ J} \cdot \text{sec}$$

$$2) \lambda = \text{wavelength}$$

$$3) c = \text{speed of light}$$

$$B) j(T) = aAT^2 e^{-\frac{b}{T}} \text{ (T = } ^\circ\text{K, A = surface area, a \& b material constants)}$$


$$C) \text{ Child - Langmuir Law - } j(V) = 2.33 \times 10^{-6} \frac{A}{d^2} V^{\frac{3}{2}} \text{ (d = + and - spacing)}$$

(OVER)

0) SOURCES & CIRCUITS

1) Voltage source

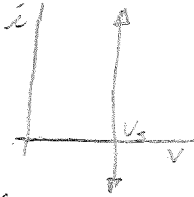- a) A lumped, 2 terminal circuit, with constant V or
- b) $V = V_S$ for all i



2) Current source

- a) A lumped, two terminal circuit, with constant i_s or
- b) $i = i_s$ for all V




- 3) May be dependent or independent \diamond
- 4) Open circuit $\Rightarrow i = 0$ for all V (special current source)
- 5) Short circuit $\Rightarrow V = 0$ for all i ("voltage")

E) OHM'S LAW

- 1) $V = R i$
- 2) $R = \frac{dV}{di}$ (reciprocal of $V-i$ slope)
- 3) R has same sign as P (power)

F) An ideal DIODE

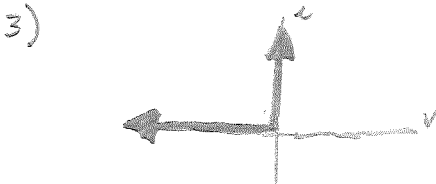- 1) allows no (+) voltage or (-) current
- 2) i.e) $V = 0, i > 0$
 $i = 0, V < 0$
 $V i = 0$ for all $V-i$



G) Parallel & Series Connections

- 1) Series $\Rightarrow i = i_1 = i_2$



- 2) Parallel $\Rightarrow V = V_1 = V_2$



III. CHAPT. III - NETWORK SOLUTIONS

A) DEFINITIONS

- 1) NODE - A point at which 2 or more circuit elements have a common connection
- 2) BRANCH - A part of a network extending from one node to another \cong circuit element
- 3) LOOP - A sequence of circuit elements forming a closed path that doesn't pass thru any node \rightarrow !
- 4) MESH - A loop with no circuit elements
- 5) PLANAR NETWORK - A network with no crossing wires
- 6) ONE PORT NETWORK - Only 2 terminals available for connection

B) KIRCHHOFF'S LAW

1) VOLTAGE LAW

$\sum E$ around a closed path $= 0$

$\therefore \sum_{i=1}^N V_i = 0$ around any closed path

2) CURRENT LAW

$\sum i$ entering any node $= 0$

$\therefore \sum_{j=1}^M i_j = 0$

CLASS

Measure indirectly

$$\vec{F} = k \frac{m_1 m_2}{r^2} \vec{a}$$

Coulomb's Law

$$\vec{F} = \frac{q_1 q_2}{(4\pi\epsilon_0) r^2} \vec{a}_r$$

q = elec. charge

$$\epsilon_0 = \frac{\text{permittivity of free space}}{\text{gravitational field}} = \frac{10^{-9} \text{ FARAD}}{36\pi \text{ M}}$$




$$\vec{E} = \lim_{q \rightarrow 0} \frac{\vec{F}_e}{q}$$

$$\vec{a} = \lim_{m \rightarrow 0} \frac{\vec{F}_g}{m}$$

CHAPT. J
5, 8, 12, 19

Can't measure field directly; must be force

EX

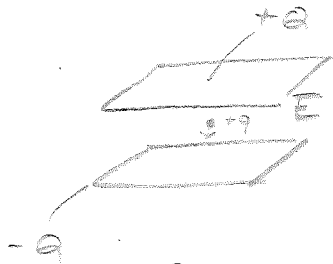

must take into account charge (+q)

BOOK

VOLTAGE - Energy to transmit electric charge from one terminal to another

CURRENT - Measure of rate at which an electric charge is moving thru an element

$$(VOLTAGE)(CURRENT) = POWER$$

COULOMB'S LAW:

$$F = \frac{Q_1 Q_2}{4\pi\epsilon_0 R^2} ; \epsilon_0 = 8.85 \times 10^{-12} \frac{\text{FARAD}}{\text{METER}}$$

FIELD - Region of influence or source of influence
ELECTRIC FIELD INTENSITY:

$$E = \lim_{\Delta Q \rightarrow 0} \frac{\Delta F}{\Delta Q} = \frac{dF}{dQ}$$

MAGNITUDE

OF THE FIELD OF A PT. CHARGE Q,

$$E = \frac{Q_1}{4\pi\epsilon_0 R^2}$$

$$E = \frac{\text{NEWT}}{\text{COUL}} = \frac{\text{VOLT}}{\text{M}}$$

~~1.02 x 10^-12 = 1.02~~

$$\frac{\text{V}}{\text{m}} \text{ C} = \text{N}$$

CHARGE = Q
AREA = A



CHARGE = -Q

$$F = 9.65 \times 10^4 \text{ C}$$

$$\epsilon_0 = 8.54 \times 10^{-12} \frac{\text{C}}{\text{m}}$$


$$E = \frac{Q}{\epsilon_0 A}$$

$$\frac{C}{F} = V$$

Q in COLOMBS

TAIVIA
↓ ↓

~~EX~~ XI-1

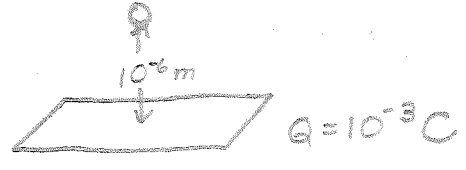

$$E = \frac{Q_1}{4\pi\epsilon_0 R^2}$$

$$= \frac{10^{-3} \text{ COUL}}{4\pi(8.85 \times 10^{-12} \text{ FAR}) 10^{-12} \text{ m}^2}$$


$$= 8.98 \times 10^{19} \frac{\text{COUL}}{\text{FARAD}}$$

$$= 8.98 \times 10^{19} \frac{\text{COUL}}{\text{FARAD}} \frac{\text{FAR}}{\text{COUL } 9.65 \times 10^4}$$

$$E = 9.41 \times 10^{14} = F \times d$$

$$F = \frac{9.41 \times 10^{14}}{10^{-6} \text{ m}} =$$


~~EX~~ XI-1

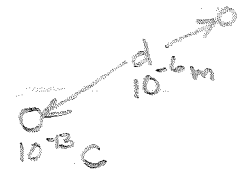

$$a) F = \frac{Q_1 Q_2}{4\pi\epsilon_0 d^2}$$

$$F = \frac{(10^{-13} \text{ C})(-1.6 \times 10^{-19} \text{ C})}{4\pi(8.85 \times 10^{-12} \text{ FAR}) 10^{-12} \text{ m}^2 9.65 \times 10^4 \text{ C}}$$
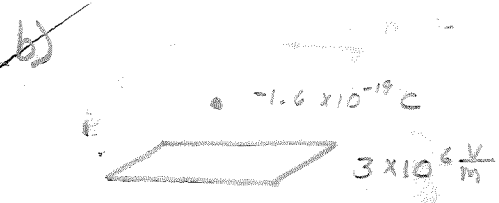
$$F = 1.490 \times 10^{14} \frac{\text{C}}{\text{m}}$$



$$F = \frac{Q_1 Q_2}{4\pi\epsilon_0 R^2}$$

$$E = \frac{Q}{\epsilon_0 A}$$

$$=$$

a) $Q_1 = -1.6 \times 10^{-19} \text{ C}$
 $r = 10^{-5} \text{ m}$
 $Q_2 = 10^{-19} \text{ C}$


$$F = \frac{Q_1 Q_2}{4\pi \epsilon_0 R^2}$$

$$= \frac{-1.6 \times 10^{-22}}{4\pi (8.85 \times 10^{-12}) (10^{-5})^2}$$

$$= 1.44 \times 10^{-24} \text{ N}$$

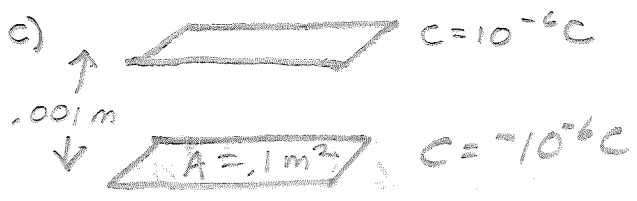b) $E = 3 \times 10^6 \frac{\text{V}}{\text{M}}$
 $\frac{\text{V}}{\text{M}} \text{ C} = \text{N}$

$$(3 \times 10^6 \frac{\text{V}}{\text{M}}) (-1.6 \times 10^{-19}) = 4.8 \times 10^{-13}$$



$$E = \frac{Q}{\epsilon_0 A}$$

$$= \frac{10^{-6} \text{ C}}{8.85 \times 10^{-12} \text{ FAR} \cdot \text{M}^2}$$

$$= .113 \frac{\text{C}}{\text{FAR} \cdot \text{M}} = .113 \frac{\text{V}}{\text{M}}$$

$$(.113 \frac{\text{V}}{\text{M}}) (-1.6 \times 10^{-19} \text{ C}) =$$

$$.181 \times 10^{-20} \text{ NT} =$$

$$1.81 \times 10^{-20} \text{ NT}$$



$$E_0 = \frac{Q_0}{\epsilon_0 A_0}$$

$$E_e = E_0 \cdot Q_e$$

$$F_e = m_e a_e$$

$$d = \frac{(8.85 \times 10^{-12}) (2.5 \times 10^{-14} \text{ m}) (9.11 \times 10^{-31} \text{ kg})}{(5 \text{ M}) (10^{-6} \text{ C}) (-1.6 \times 10^{-19})} = v_0 t \quad v_0 = d/t$$

$$= 1.25 \times 10^{-5} \text{ m}$$


$$\frac{Q}{V_0} = \frac{V_0}{d_0}$$

$$d_0 = \frac{V_0^2}{Q}$$

$$= \frac{V_0^2 m_e}{F_e}$$

$$= \frac{V_0^2 m_e \epsilon_0 A}{Q_0 Q_e}$$

1-X-2) ✗

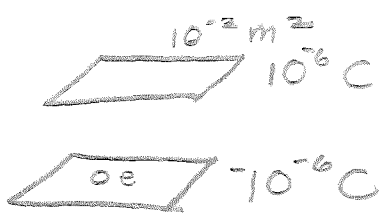

$$E = \frac{Q}{\epsilon_0 A}$$

$$= \frac{10^{-6} \text{ C}}{8.85 \times 10^{-12} \text{ F m}^{-1} \times 10^{-2} \text{ m}^2}$$

$$= 1.13 \times 10^6 \text{ V m}^{-1} = 1.13 \text{ MV m}^{-1}$$

$$F = 1.13 \text{ MV m}^{-1} (-1.6 \times 10^{-19} \text{ C}) = 1.81 \times 10^{-19} \text{ N}$$

$$a = \frac{1.81 \times 10^{-19} \text{ N}}{9.11 \times 10^{-31} \text{ kg}} = 1.99 \times 10^{11} \frac{\text{m}}{\text{s}^2}$$

$$\frac{v^2}{a} = d$$

$$d = \frac{2.5 \times 10^{14} \text{ m}^2}{1.99 \times 10^{11} \text{ m/s}^2} = 12.6 \times 10^3 \text{ m}$$

b) $E = 10^{-15} \text{ J} = 10^{-5} \text{ V C}^{-1}$

$E = \uparrow \uparrow$
TRIVIA

BOOK

$$F_{\text{field}} = QE$$

$$\frac{1}{2}mv^2 = W = QE_L L_{12} \text{ (IN JOULES)} \quad E_L = \text{COMPONENT OF } E \text{ IN } L_{12} \text{ DIRECTION}$$

Work is independent of the path in a conservative field

$$V_{21} = \frac{W_{F2} - W_{F1}}{Q}$$

$$= E_L L_{12}$$

Voltage = Potential difference

$$V = \frac{W}{Q}$$

of $E_L = 0$, (locus of pts = equipotential surface)

MORE TRIVIA

x1-3)



$$20 \text{ cm}^2 = \frac{1 \text{ m}^2}{100 \text{ cm}^2} = 20 \text{ m}^2$$

$$2 \times 10^{-3} \text{ m}$$



v a) $Q_A = 10^{-8} \text{ C}$
 $Q_B = -10^{-8} \text{ C}$

$$E = \frac{Q}{\epsilon_0 A}$$

$$= \frac{10^{-8} \text{ C}}{8.85 \text{ F} \cdot 20 \text{ m} \times 10^{-5}}$$

$$= 5.65 \times 10^{-3} \frac{\text{V}}{\text{m}} = 565 \frac{\text{V}}{\text{m}}$$

$$V_{AB} = E_L L_{BA}$$

$$= (565 \times 10^{-3} \frac{\text{V}}{\text{m}}) (2 \times 10^{-3} \text{ m})$$

$$= 1.13 \times 10^{-6} \text{ V}$$

v b) $V = \frac{J}{C}$

$$= \frac{8 \times 10^{-18} \text{ J}}{-1.6 \times 10^{-19} \text{ C}} = -50 \text{ V}$$

v c) $E_{AB} = 2 \times 10^6 \frac{\text{V}}{\text{m}}$ B A

$$V_{AB} = E_L L_{BA}$$

$$= 2 \times 10^6 \frac{\text{V}}{\text{m}} (2 \times 10^{-3} \text{ m})$$

$$= 400 \text{ V}$$

x1-4)



a) $V = \frac{J}{C}$

$$= \frac{3 \text{ J}}{2 \text{ C}} = 1.5 \text{ V}$$

b) $\Delta P_{12} = 9.6 \times 10^{-19}$

$$V = \frac{9.6 \times 10^{-19}}{-1.6 \times 10^{-19}} = -6 \text{ V}$$

c) (\vec{z})

BOOK

AMPERE = UNIT OF CURRENT = A

$$A = \frac{C}{S}$$

Current is represented by j

CURRENT DENSITY = J

$$j = \frac{dq}{dt}$$

$$J = \frac{A}{m^2} = \frac{dj}{dA}$$

FOR UNIFORM CURRENT DENSITY,

$$j = JA$$

CHARGE DENSITY = ρ

$$\rho = \frac{dq}{dV} \quad (V = \text{VOLUME})$$

$$J_L = \rho u_L$$

$u = \text{VELOCITY}$

POWER

$$P = Vj$$


LAB

OCT. 2 1969

$$\vec{E} = \lim_{q \rightarrow 0} \frac{\vec{F}}{q}$$

OCT. 3 1969
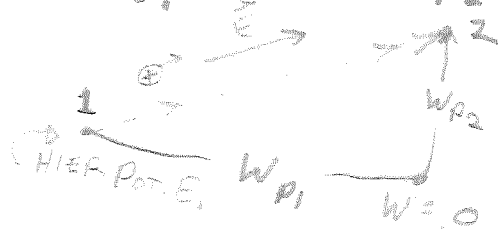
$$W = -\int_1^2 \vec{F} \cdot d\vec{l} = -\int_1^2 q \vec{E} \cdot d\vec{l} = W_{p2} - W_{p1}$$




$$q \left[-\int_1^2 \vec{E} \cdot d\vec{l} \right] = q V_{21}$$

Must memorize:

- Fundamental laws (No derivation)
- And Definitions (Mathematical)

PROB B)

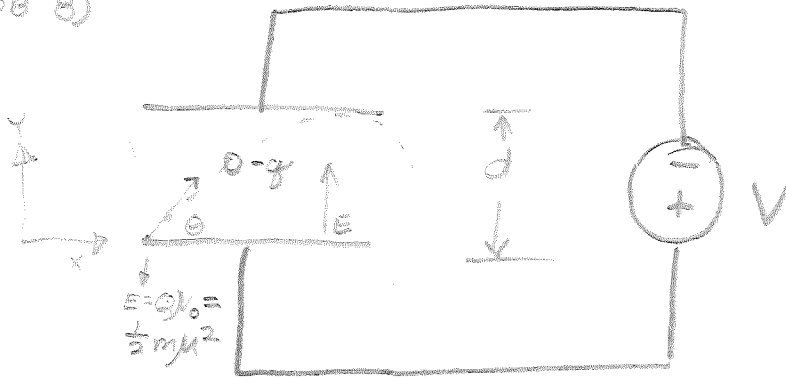

$$W = qV_0 = -eV_0 \quad e = +1.6 \times 10^{-19} \text{ C}$$

$$\mu_y = \mu \sin \theta \quad F_y = q \frac{V}{d} = m \frac{d\mu_y}{dt}$$

$$\mu_x = \mu \cos \theta \quad E_{\text{TOTAL}} = qV_0$$

$$V = V_{z1} = - \int_1^2 E \cdot dl = -(-Ed) \Rightarrow V = ED$$


$$\int_0^t q \frac{V}{d} dt = m \int_{v_0}^0 d\mu_y$$

$$\Delta K_y = \left(\frac{1}{2} m v_{y0}^2 - 0 \right) = qV = eV$$

5/2/7

OCT. 4 1969

TRIVIA

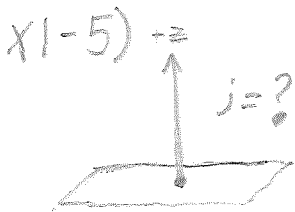

$$J = JA = 5000 \frac{\text{A}}{\text{m}^2} \pi 10^{-6} = 15,700 \times 10^{-6} \text{ A} = 1.57 \times 10^{-2} \text{ A}$$

b) $v_e = 10^7 \frac{\text{m}}{\text{s}}$
 $D = \frac{10^8 \text{ e}}{\text{m}}$

$$J = \rho v$$

$$= \left(\frac{10^8 \text{ e}}{\text{m}^3} \right) \left(\frac{-1.6 \times 10^{-18} \text{ C}}{\text{e}} \right) 10^7 \frac{\text{m}}{\text{s}}$$


$$= -1.6 \times 10^5 \frac{\text{C}}{\text{SEC}}$$

9)

$$J = \frac{0.2}{r} e^{-10,000 r} \frac{A}{m^2}$$

CLASS


5 a)

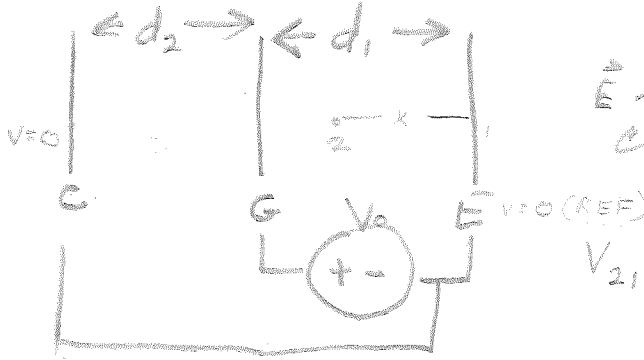

\vec{E} is uniform in closely parallel plates

$$V_{21} = - \int_1^2 \vec{E} \cdot d\vec{l}$$

$$= -E \int_1^2 dl = -EX$$

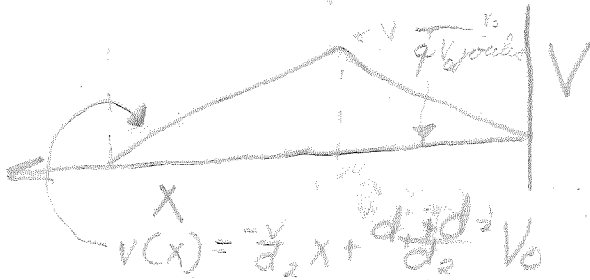

a) $V_0 = 0$

(The difference of the voltage is the same)

$$qV_0 = \frac{1}{2} m \mu^2$$

$$\mu = \sqrt{\frac{2qV_0}{me}}$$

b) $V_G = ?$

$$U = \frac{dx}{dt}$$

$$dx = v dt$$

$$\int_0^{d_1} dx = \int_0^{t_1} v dt$$

$$d_1 = \int_0^{t_1} \frac{qE}{m} t dt$$

$$= \frac{qE}{2m} t_1^2$$

$$t_1 = \sqrt{\frac{2md_1}{qE}}$$

$$F = qE = m \frac{dv}{dt}$$

$$qE \int_0^t dt = \int_0^{v(t)} m dv$$

$$U(t) = \frac{qE}{m} t$$


$$|V| = \left| \int E dx \right|$$

$$\left| \frac{dV}{dx} \right| = |E|$$


Sole Marks

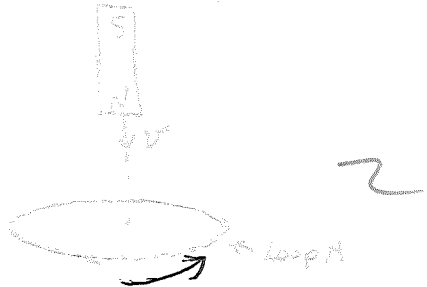(6)


OF FOLLOWING SKETCHES INDICATE THE DIRECTION IN WHICH CURRENT WILL FLOW IN LOOP A




magnet moving toward coil

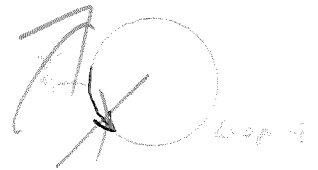

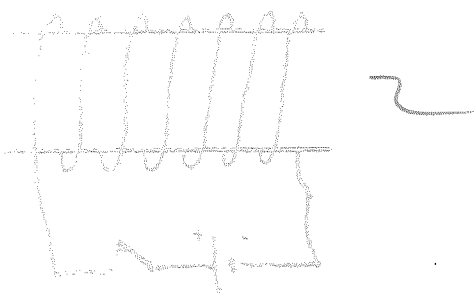2) both coils in same plane, first loop carrying current & 2nd loop moving toward 1st loop.




when switch is closed

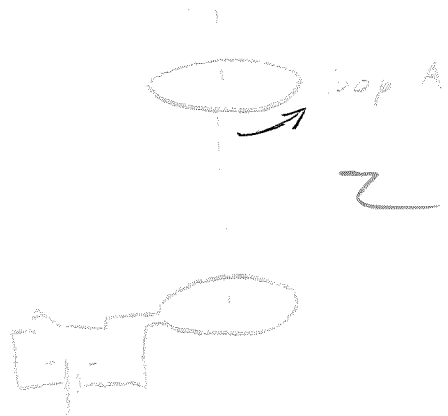

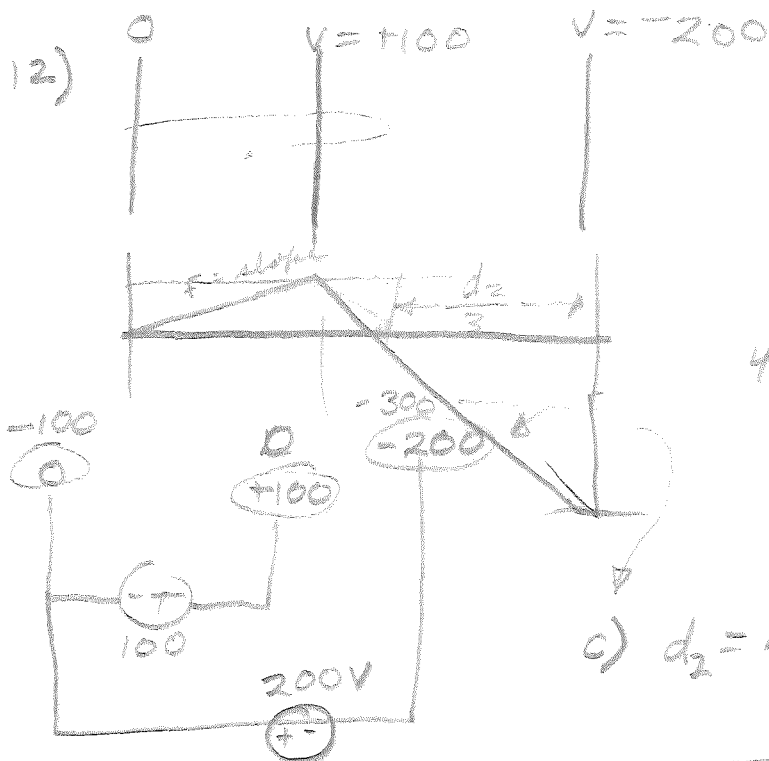4) when switch is closed

WHICH END (A) OR (B) IS AT THE HIGHER POTENTIAL IF METAL ROD AB IS MOVING TO RIGHT IN THE MAGNETIC field produced by current i in a long wire





$$y = \left(\frac{-300}{d_2}\right)x + 100$$

$$\text{if } y=0 \Rightarrow x = \frac{d_2}{3}$$

c) $d_2 = 4d_1$

(15, 13)

CLASS
CURRENT

$$j = \frac{dQ}{dt} \text{ - def.}$$

$$= -jA$$

$$= \rho \mu A$$

$$= (\rho A) \mu \frac{\text{coul}}{\text{m}} \frac{\text{m}}{\text{sec}}$$

$$\text{amp} = \frac{\text{coul}}{\text{sec}}$$

$\rho = \text{charge density, in } \frac{c}{m^3}$

BOOK

POWER (WATT)

$$W = \frac{J}{S}$$

$$F = \frac{qV}{d}$$

$$E = \frac{V}{d}$$

(13)

$$dA = dy dx$$

$$j = 8 \int_0^{\frac{10^{-3}}{2}} \int_{y=x}^{\frac{10^{-3}}{2}} [2 \times 10^5 x] dy dx$$

$$j = 2 \times 10^8$$

$$j = 8 \int_0^{\frac{10^{-3}}{2}} \left[10^5 \frac{x}{\frac{10^{-3}}{2}} \right] \left[\frac{10^{-3}}{2} - x \right] dx$$

$$= 8 \left[10^5 \frac{x^2}{2} - \frac{10^5}{\frac{10^{-3}}{2}} \frac{x^3}{3} \right]_0^{\frac{10^{-3}}{2}}$$

$$= .2 \left(\frac{1}{6} \right) = 33 \text{ mA} = .033 \text{ A}$$

$W = - \int \vec{F} \cdot d\vec{e} = -q \int \vec{E} \cdot d\vec{e}$
 joules = volt meter = coul meter
 = amp volt
 = watt sec

$$qV = \frac{1}{2} m \mu^2 \frac{j}{e} \times \frac{10^{11} e}{m}$$



(61)

$$i = \oint \mathbf{J} \cdot d\mathbf{l} = -\frac{d\theta}{dt} = \frac{d}{dt} \int \rho dv$$

\oint means integrate over a closed surface


Kirchoff's Current Law

CLASS

2 terminal device



i always enters + terminal


PROB 1, 3, 4, 5
CHPT. 2

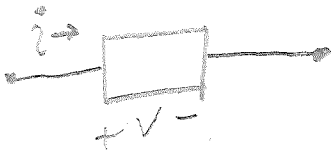

Most electronic circuits don't have handy mathematical equations

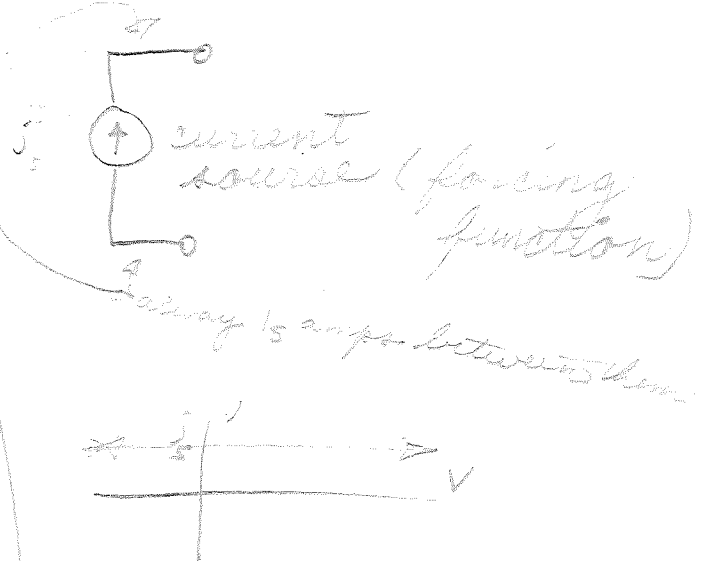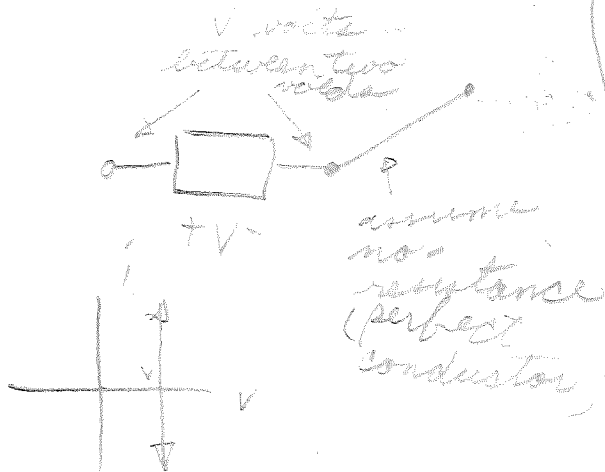Restrictions:
2 terminal device
 $v-i$ are time independent





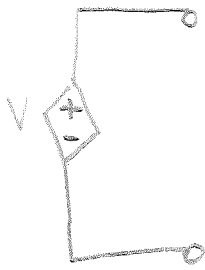



$V = k V_x$, where V_x is some other V in circuit
 $V = k_j i_x$

∴ V is dependant on some other measurement (V, i , etc.) in the circuit


CHAPT 2, PROB. 2

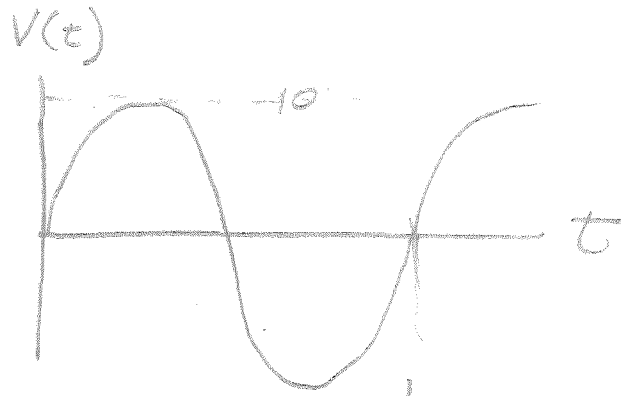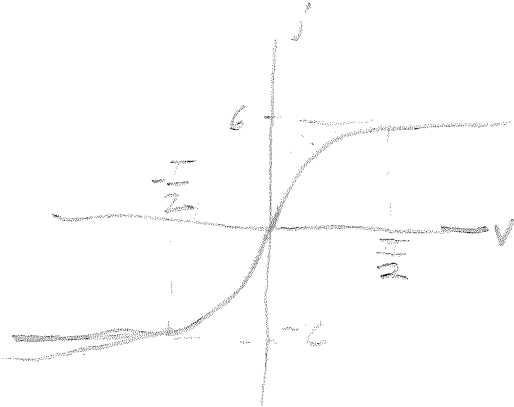

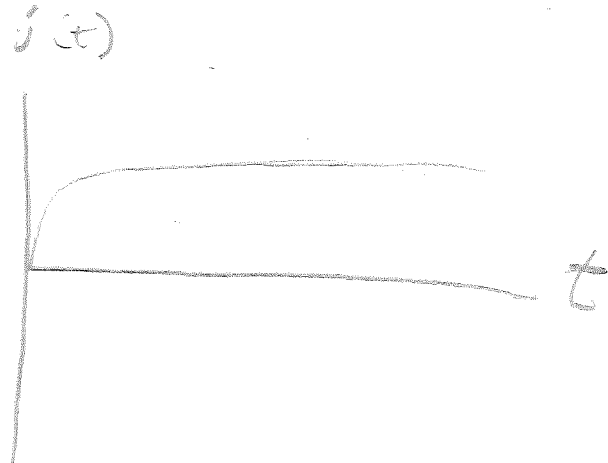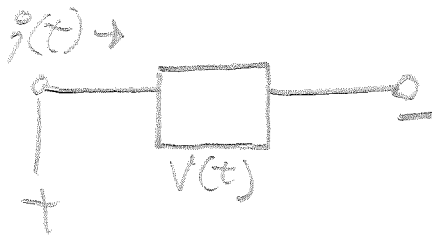
$$V(t) = 10 \left[\sin 60 \left(2\pi \frac{1}{60} t \right) \right]$$



can coincide axes & use projections


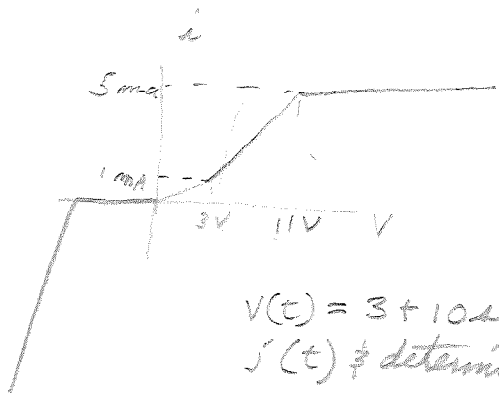


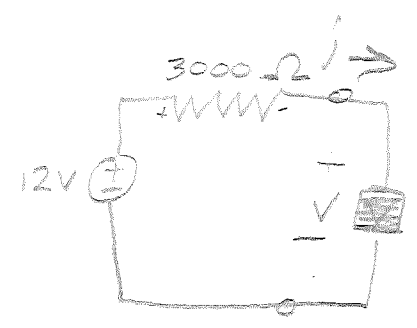$V(t) = 3 + 10 \sin \omega t$
 $i(t)$ determine max & min -



$V = ?$
 $i = ?$

$V = 12 - 3000i$

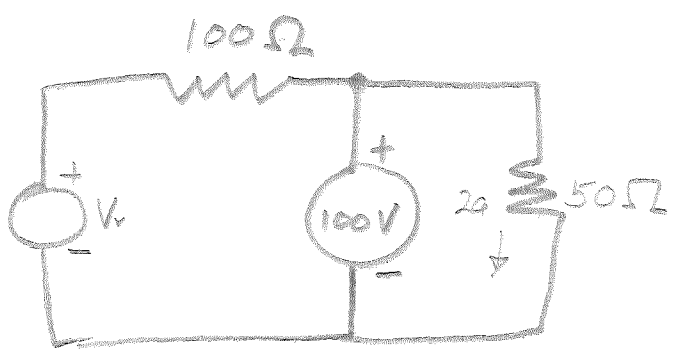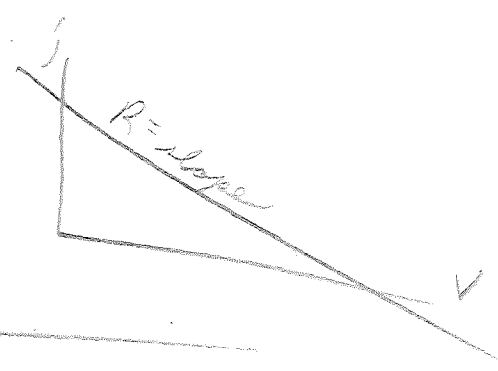

$\oint \mathbf{J} \cdot d\mathbf{A} = \frac{dq}{dt}$

$W = -\int \mathbf{F} \cdot d\mathbf{l} = -q \int \mathbf{E} \cdot d\mathbf{l} = qV$

$P = \frac{dW}{dt} = V \frac{dq}{dt} + q \frac{dV}{dt} = V\dot{q}$

$V = iR$ $P = V\dot{q} = i^2 R = \frac{V^2}{R}$

- 1) Isolate each part of the system
- 2) Observe if the voltage across a line is the Voltage across the same line, but connected through a different source
- 3) Compare both sources by simultaneous equations or intersections of graphs to see common pt.

Diode




- ① When current is flowing with arrow, there's a direct short.
- ② If current flows in opposite direction, got an open circuit

a diode is sensitive to what is going on ⁱⁿ the circuit, like an electric switch

Pp. 259-60

10)

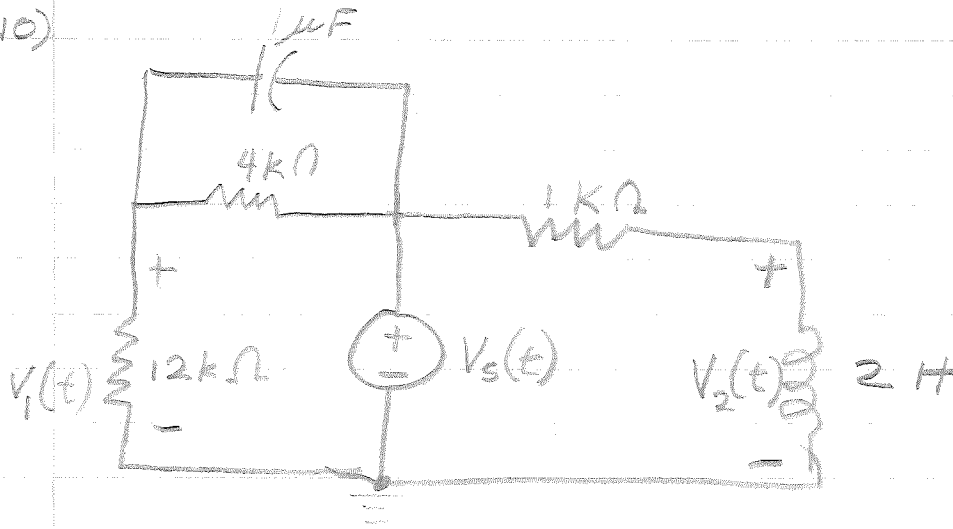

$$V_s(t) = 100 + 200\mu(t)$$

N.T.O

$$\frac{V_1}{12,000} + \frac{V_1 - V_s}{4,000} + 10^{-6} \left(\frac{d}{dt} (V_1 - V_s) \right) = 0$$

$$\frac{1}{2} \int V_2 dt + \frac{V_2 - V_s}{1000} = 10$$

$$\frac{V_1}{12} + \frac{V_1}{4} + 10^{-3} \frac{dV_1}{dt} = \frac{V_s}{4} + 10^{-3} \frac{dV_s}{dt} = 25 + 50\mu(t) + 0.2\delta(t)$$

TO FIND DIFF EQ

$$\frac{V_1}{3} + 10^{-3} \frac{dV_1}{dt} = 0$$

$$V_1 = A e^{-\frac{t}{3 \times 10^{-3}}}$$

$$V_A = V_{11} + V_{12} + V_{13}$$

$$\frac{V_{11}}{3} + 10^{-3} \frac{dV_{11}}{dt} = 25$$

$$V_{11} = 75$$

$$\frac{V_{12}}{3} + 10^{-3} \frac{dV_{12}}{dt} = 50 \quad t \geq 0$$

$$V_{12} = 150$$

$$\frac{V_{13}}{3} + 10^{-3} \frac{dV_{13}}{dt} = 0 \quad t < 0$$


$$V_{13} = 0$$

$$V_{12} = 150\mu(t) + ??$$

$$V_{13} = 0 \text{ at } t \neq 0$$

SOLUTION
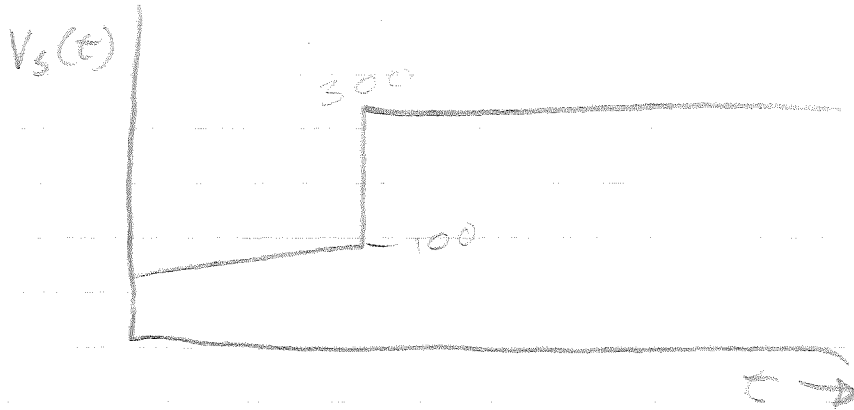
$$V = q \left(\frac{-t}{3 \times 10^{-3}} + 75 + 150 \mu(t) \right) \quad \begin{matrix} = 0 \text{ at } t < 0 \\ t > 0 \\ t < 0 \end{matrix}$$



(X1-3)

$.2 m^2$



$20 cm^2 \frac{1 m^2}{100 cm^2} = .2 m^2$

a) $q_1 = -q_2 = 10^{-8} C$

$E = \frac{q}{\epsilon_0 A} = \frac{10^{-8}}{(8.85 \times 10^{-12})(.2 m^2)} = .565 \times 10^4 \frac{N}{m}$

$V = Ed$

$= (.5650) \frac{N}{m} (.2) = 1.13 V$

b) $W = Fd$

$\frac{NE}{m} = \frac{NE}{Coul}$

$NE m = V Coul$

$Joule = V Coul$

$W = Vq$

$\frac{8 \times 10^{-18}}{1.6 \times 10^{-19}} = V$

$V = 50$

c) $E = 2 \times 10^6 \frac{N}{m}$

$V = Ed$

$= (2 \times 10^6)(2 \times 10^{-4})$

$= 400 V$

(X1-4)



a) $W = Vq$

$V = \frac{W}{q}$

$= \frac{3 J}{2} = 1.5 V$

b) $E = V/d$

$V = \frac{9.6 \times 10^{-19}}{1.6 \times 10^{-19}} = 6 V$

c) $\Sigma V = 4$

X1-5) a) $J = 5000 \frac{A}{m^2}$

$J = jA$

$= (5 \times 10^3) \pi (10^{-8})$

$= 15.7 \times 10^{-5} A$

b) $J = \rho U$

$j = \rho U A$

$= \frac{5}{10^8} \frac{A}{m^2} \pi^2$

$\frac{q}{L} = \frac{10^8 A}{m} \frac{1.6 \times 10^{-19} C}{L} = 1.6 \times 10^{-11} \frac{C}{m}$

$\frac{q}{L} = i = 1.6 \times 10^{-11} 10^7 = 1.6 \times 10^{-4} \frac{C}{m}$

~~$J = \frac{i^2}{r} e^{-10,000r}$~~

$\int J dr = U = \frac{i^2}{r} dr = e^{-10,000r}$

$du = \frac{-2i^2}{r^2} dr = \frac{e^{-10,000r}}{-10,000}$

=

11-6) a) $q = .02 \cos(100t - 1.5\pi)$

$i = \frac{dq}{dt} = -2 \sin(100t - 1.5\pi)$
 $= -2 A$

b) $q = 4 \times 10^{-20} e^{-.2t} \text{ C} \quad (1.6 \times 10^{-19} \frac{C}{e})$
 $q = 6.4 \times 10^{-20} e^{-.2t}$

$i = \frac{dq}{dt} = 1.28 \times 10^{-19} e^{-.2t}$

$i = 12.8 A$ at $t=0$

c) $V = 10(t-3)$ $P = Vi$
 $i = \frac{P}{V}$

$= \frac{4}{10(t-3)}$

at $t=0, i = -1.33 A$

CHAPT. II Pg 34

X2-3) $V = [3.93 \times 10^{-2} T - 1.5] i$

$\frac{\partial V}{\partial i} = 3.93 \times 10^{-2} T - 1.5$

a) at $T=200, \frac{\partial V}{\partial i} = 6.4 \frac{V}{A}$


b) at $T=300, \frac{\partial V}{\partial i} = 10.3 \frac{V}{A}$

c) " " " 400 " " 14.2 $\frac{V}{A}$

X2-3) Pf 40-1

$i = 0.4 T^2 e^{-.12t}$
 $= (0.00)(2.5 \times 10^{-5}) \pi (10^6) e^{-.12t}$

X2-4) Pg 51

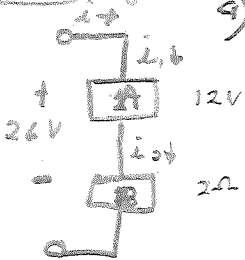

a) $B = \text{Voltage source} = 12V$
 $B = 2\Omega$

$i = i_1 = i_2$

$V_{AB} = 13V$

$V = iR$

$i = \frac{V}{R} = \frac{13}{2} = 6.5 A$

b) $i_1 = i = i_2$


$\Sigma R = 13\Omega$

$V = Ri$

$i = \frac{V}{R} = \frac{26}{13} = 2 A$

c) $i = \frac{26}{8} = 3.25 A$

X2-5)

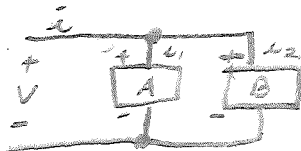

$-i = i_1 + i_2$ $i_1 = 3A$

a) $A = V_{s1} = 10V$

$B = i_{s2} = 5A$

$i = 8A$

b) $A = V_s = 10V$

$B = R = 5\Omega$

$-i = i_1 + i_2$

$i_2 = 2A$

$i = 5A$

c) $\frac{1}{R} = \frac{1}{6} + \frac{2}{6} = \frac{3}{6}$

$R = 2$

$V_1 = 18V$

$i_2 = \frac{18}{3} = 6$

$i = 9$

P8 55
x2-6)


$$a) i_s = .02 \cos 1000\pi t$$

$$.25 \text{ ms} = \frac{1}{1000} = 2.25 \times 10^{-3} \text{ s}$$

$$i_s = .02 \cos .25\pi$$

$$= .02 \frac{1}{\sqrt{2}}$$

$$14.1 \times 10^{-3} \text{ A}$$

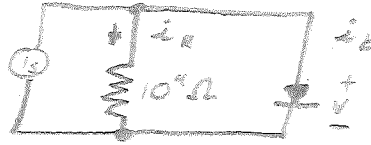

$$b) i_s = i_R + i_b$$

$$i_b = 0$$

$$i_s = i_R = .02 \cos \frac{1}{3}\pi = \frac{.02}{2} = 10^{-2} \text{ A}$$

CHAPT 3 P867

x3-2)

$$60V - V_2 - V_7 = 0 \quad c) V_7 + 40 - 15 - 12 = 0$$

$$V_7 = 13V$$

$$a) 60 - V_2 = -13$$

$$V_2 = 73$$

$$d) V_6 - 12 - 15 = 0$$

$$V_6 = 27V$$

$$b) i_1 + i_2 - 12 = 0$$

$$i_1 - 2 - i_2 = 0$$

$$4 + i_2 + 12$$



$$\oint \vec{D} \cdot d\vec{A} = q$$

$$\vec{D} = \epsilon \vec{E}$$

$$V = -\int \vec{E} \cdot d\vec{L}$$

$$q = CV$$

FAR. LAW.


$$\oint \vec{E} \cdot d\vec{L} = -\frac{d}{dt} \int \vec{B} \cdot d\vec{A} = -\frac{d\Phi}{dt}$$

$$\vec{B} = \mu \vec{H}$$

AMPERES LAW

$$\oint \vec{H} \cdot d\vec{L} = I$$
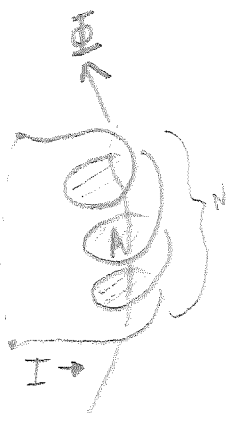
$$L = \frac{N\Phi}{I} = \text{inductance}$$






$\vec{E} = 0$ IN PERFECT CONDUCTOR

$$\therefore V = -\int \vec{E} \cdot d\vec{L} = \frac{d\Phi}{dt}$$

INDUCED EMF = LAW

$$V = N \frac{d\Phi}{dt} = L \frac{di}{dt} \quad i = C \frac{dV}{dt}$$

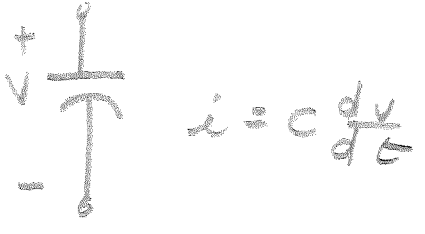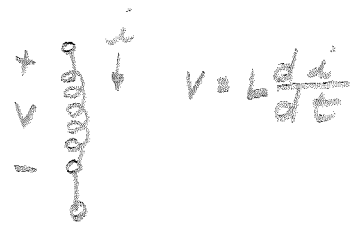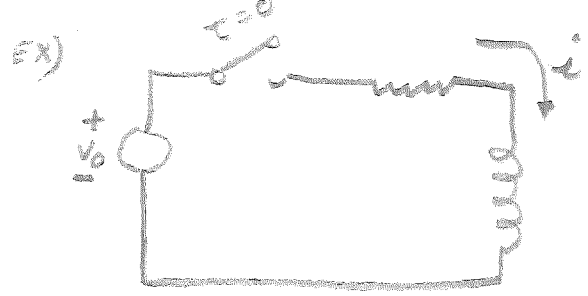for inductor, talk about Φ , i relationship



$$V_0 = Ri + L \frac{di}{dt}$$

$$dt = \frac{L di}{V_0 - i}$$

$$i = \frac{V_0}{R} + I e^{-\frac{R}{L}t}$$

$$I = \frac{V_0}{R}$$

1) a) $(V, j) = (1, 2), (-6, -1)$

$$m = \frac{3}{7}$$

$$j - 2 = \frac{3}{7}(V - 1)$$

$$j - 2 = \frac{3}{7}V - \frac{3}{7}$$


$$j = \frac{3}{7}V + \frac{11}{7}$$

$$j \text{ inter.} = \frac{11}{7}$$

$$\frac{3}{7}V = -\frac{11}{7}$$

$$V = -\frac{11}{3}$$

$$V \text{ inter.} = -\frac{11}{3}$$

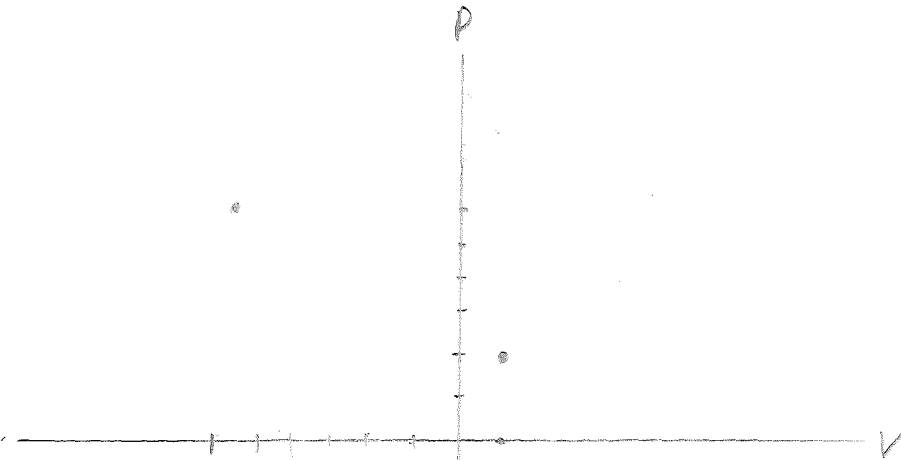

b) one

$$0 = a(0)^2 + b(0) + c$$

$$2 = a(1)^2 + b(1) + c$$

$$-1 = a(36) - 6b + c$$

$$c = 0$$

$$72 = 36a + 36b$$

$$51 = 36a - 6b$$

$$73 = 9b$$

$$b = \frac{73}{9}$$


$$-1 = 36a - 6b$$

$$12 = 6a + 6b$$

$$11 = 42a$$

$$a = \frac{11}{42}$$

$$j = \frac{11}{42}V^2 + \frac{73}{9}V$$

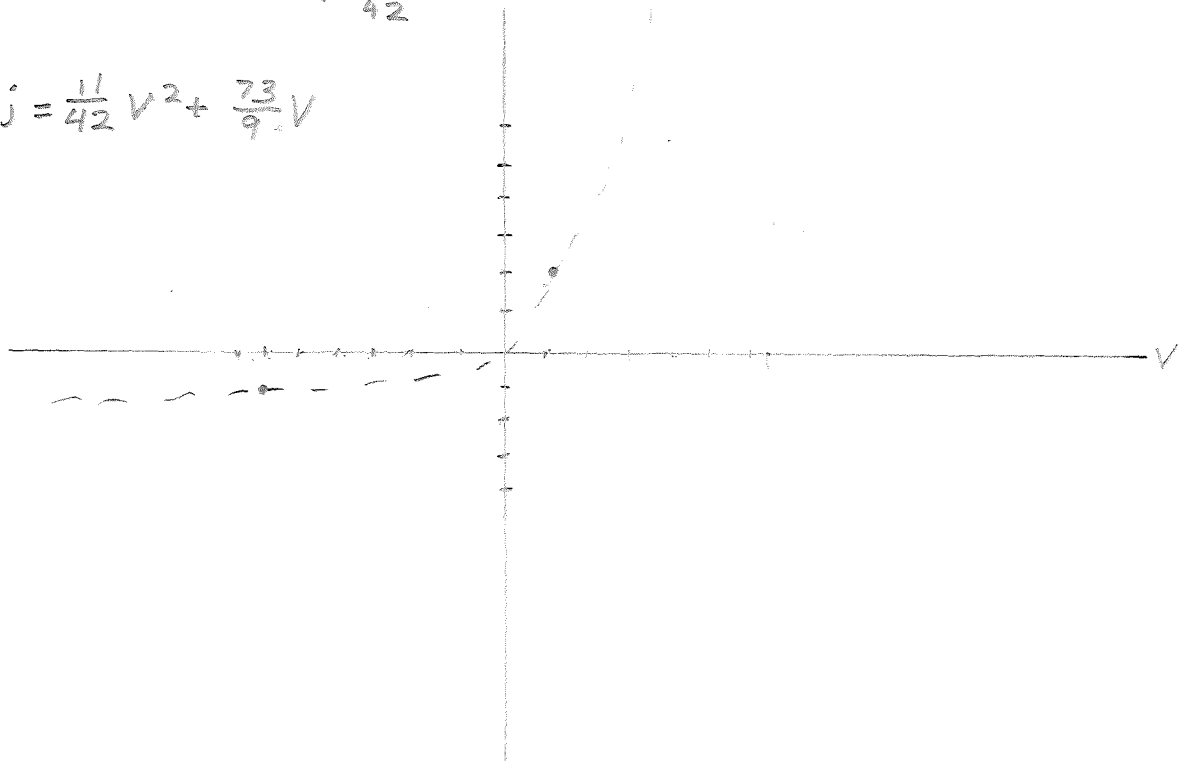

$$3) (2, 3), (4, 5), (0, 0), (8, 8) \quad (v, j)$$

$$3 = 8a + 4b + 2c$$

$$5 = 64a + 16b + 4c$$

$$8 = 512a + 64b + 8c$$

$$6 = 16a + 8b + 4c$$

$$5 = 64a + 16b + 4c$$

$$-1 = 48a + 8b$$

$$-4 = 192a + 32b$$

$$-2 = 384a + 32b$$

$$2 = 192a$$

$$a = \frac{1}{81}$$

$$-2 = 31,304 + 32b$$

$$b = 78.3$$

$$c = -185.6$$

$$8 = 512a + 64b + 8c$$

$$10 = 128a + 32b + 8c$$

$$-2 = 384a + 32b$$

$$8a + 4b + 2c = 3$$

$$64a + 16b + 4c = 5$$

$$512a + 64b + 8c = 8$$

$$a = \begin{array}{|ccc|} \hline 3 & 4 & 2 \\ \hline 5 & 16 & 4 \\ \hline 8 & 64 & 8 \\ \hline 8 & 4 & 2 \\ \hline 64 & 16 & 4 \\ \hline 512 & 64 & 8 \\ \hline \end{array}$$

Chapt. 2

pg 56)

$$4) j = av^3 + bv^2 + cv + d$$

$$(90) (2,3) (4,5) (8,8)$$

$$d = 0$$

$$3 = 8a + 4b + 2c$$

$$5 = 64a + 16b + 4c$$

$$1 = 64a + 8c + c$$

$$D = \begin{vmatrix} 8 & 4 & 2 \\ 64 & 16 & 4 \\ 64 & 8 & 1 \end{vmatrix} = 8 \begin{vmatrix} 16 & 4 \\ 8 & 1 \end{vmatrix} - 4 \begin{vmatrix} 64 & 4 \\ 64 & 1 \end{vmatrix} + 2 \begin{vmatrix} 64 & 16 \\ 64 & 8 \end{vmatrix}$$

$$= -128 + 768 - 1024 = -384$$

$$D_1 = \begin{vmatrix} 3 & 4 & 2 \\ 5 & 16 & 4 \\ 1 & 8 & 1 \end{vmatrix} = 48 + 16 + 80 - 96 - 20 - 32 = -4$$

$$a = \frac{4}{-384} = -\frac{1}{96}$$

$$D_2 = \begin{vmatrix} 8 & 4 & 2 \\ 64 & 16 & 4 \\ 64 & 8 & 1 \end{vmatrix} = 8 \begin{vmatrix} 16 & 4 \\ 8 & 1 \end{vmatrix} - 4 \begin{vmatrix} 64 & 4 \\ 64 & 1 \end{vmatrix} + 2 \begin{vmatrix} 64 & 16 \\ 64 & 8 \end{vmatrix}$$

$$= 8 + 576 - 492 = 92$$

$$b = \frac{-92}{-384} = \frac{23}{96}$$

$$D_3 = \begin{vmatrix} 8 & 4 & 2 \\ 64 & 16 & 4 \\ 64 & 8 & 1 \end{vmatrix} = 8 \begin{vmatrix} 16 & 5 \\ 8 & 1 \end{vmatrix} - 4 \begin{vmatrix} 64 & 5 \\ 64 & 1 \end{vmatrix} + 3 \begin{vmatrix} 64 & 16 \\ 64 & 8 \end{vmatrix}$$

$$= -192 + 1024 - 1536 = -704$$

$$c = \frac{-704}{-384} = \frac{11}{6}$$

$$j = \frac{v^3}{96} - \frac{23v^2}{96} + \frac{11v}{6} = .0104v^3 - .230v^2 + 1.83v$$

$$b) \quad v=1 \Rightarrow j=1.61$$

$$\frac{1.61 - 1.75}{1.75} \times 100\% = 8.0\%$$

$$v=3 \Rightarrow j=3.70$$

$$\frac{4.1 - 3.7}{3.10} = 12.9\%$$

$$v=5 \Rightarrow j=5.20$$

$$\frac{5.2 - 5.8}{5.2} \times 100\% = 11.5\%$$

$$v=7 \Rightarrow j=5.1$$

$$\frac{7.3 - 5.1}{7.3} = 30\%$$

$$4) j = aAT^2 e^{-\frac{b}{T}}$$

$$(.2) = 100(.01)T^2 e^{-\frac{11,600}{T}}$$


$$.2 = T^2 e^{-\frac{11,600}{T}}$$

$$\ln(.2) = 2 \ln T - \frac{11,600}{T}$$

$$-1.6$$

T	2 ln T	$-\frac{11,600}{T}$	$2 \ln T - \frac{11,600}{T}$
300	11.4	-38.7	-27.3
500	12.4	-23.2	-10.8
750	13.3	-15.5	-2.1
775	13.2	-15.0	-1.8

$$T \approx 775 \text{ K}$$

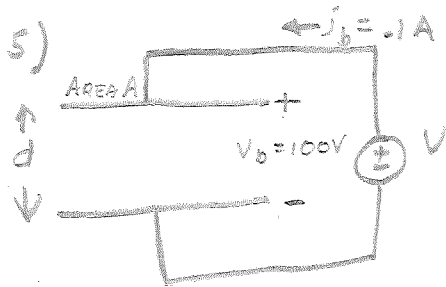

$$j(V) = 2.33 \times 10^{-6} \frac{\text{A}}{\text{d}^2} V^{\frac{3}{2}}$$

$$.01 = 2.33 \times 10^{-6} \frac{\text{A}}{\text{d}^2} 100^{\frac{3}{2}}$$

$$\frac{\text{A}}{\text{d}^2} = \frac{10 \times 10^{-3}}{(2.33 \times 10^{-6}) (1.0 \times 10^3)}$$

$$= 4.39$$



$$j(V) = (2.33 \times 10^{-6}) (4.39) (80 \times 10^3) \text{ A/m}^2$$

$$j(V) = 8.15 \times 10^{-3} \text{ A} = \frac{\Delta q}{\Delta t}$$


$$\Delta q = 8.15 \times 10^{-2} \Delta t$$

$$\Delta q = 8.15 \times 10^{-2} \text{ C}$$

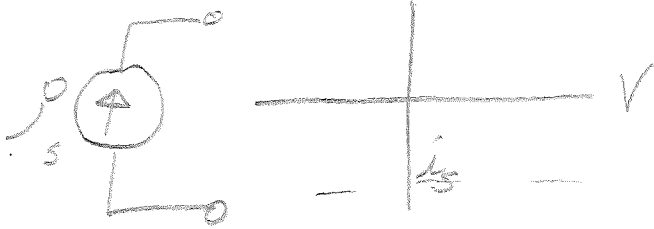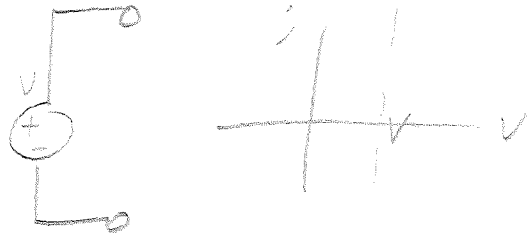
$$8.15 \times 10^{-2} \text{ C} \frac{1 e}{1.6 \times 10^{-19} \text{ C}} = 5.1 \times 10^{17} e$$



shrt. circuit forces V to 0

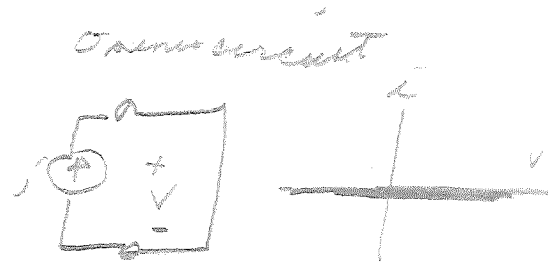

Linear, $v-i$

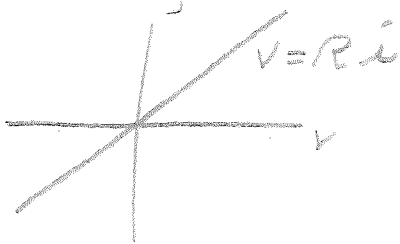

$R = \text{resistance}$




$i = \frac{V}{R} = 0$ open cir

$V = 0$ or $i = 0$ short circuit

$$R \Rightarrow \frac{\text{Volt}}{\text{amp}} \Rightarrow \text{Ohm}$$

$$\frac{1}{R} \Rightarrow \frac{\text{amp}}{\text{Volt}} \Rightarrow \text{mho}$$

x2-4)

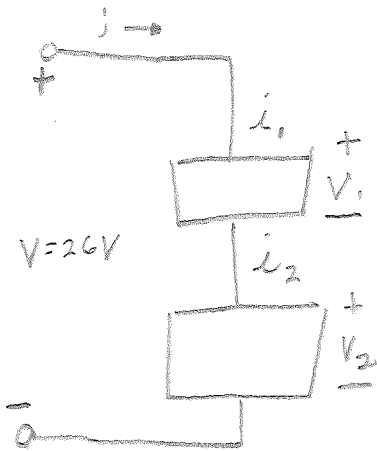

a) $V_1 = 12V$
 $V_2 = 2\Omega$

$i = i_1 = i_2$

$38V$

$R = \frac{V}{I}$

$2 = \frac{38}{I}$

$\frac{1}{2} + \frac{1}{12} = \frac{1}{V}$

a) $\frac{(26-12)V}{2} = 7$

$i = 7A$


b) $13\Omega = \frac{26V}{I}$

$I = 2A$

c) $8\Omega = \frac{26V}{I}$

$I = 3.25A$

x2-5)

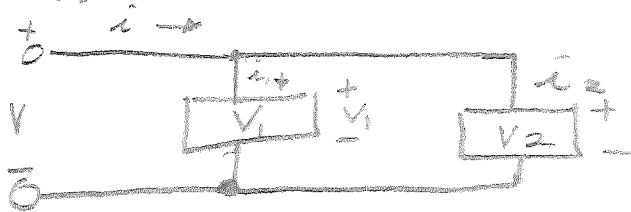

$i_1 = 3A$

$V_{S1} = 10V$


$i_{S2} = 5A$

a) 5A



b) 8A

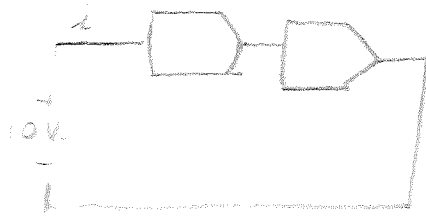c) ~~$\frac{1}{6} + \frac{2}{6} = \frac{3}{6} = \frac{1}{2}$~~







$i = 4A$

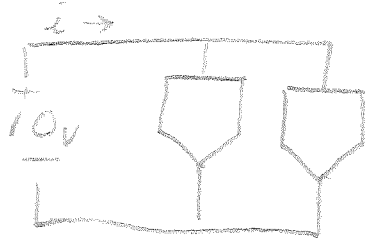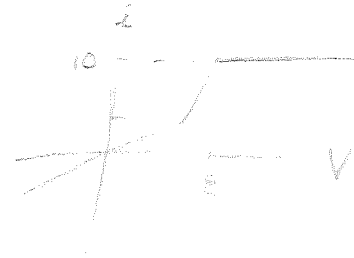


$i = 20A$

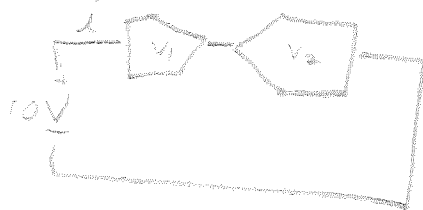


$i = 2.8A$

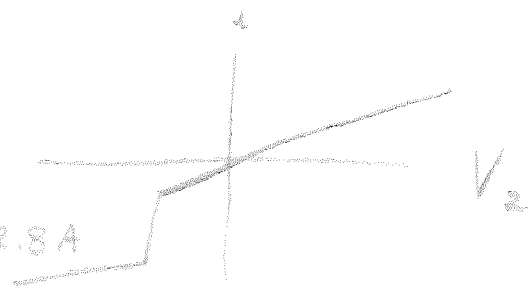


COMPOSITE OF 2 GRAPHS
(BY ADDITION)

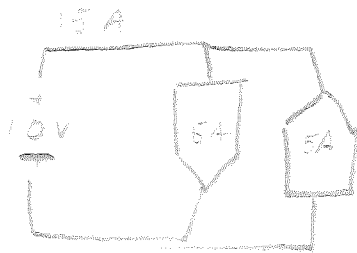

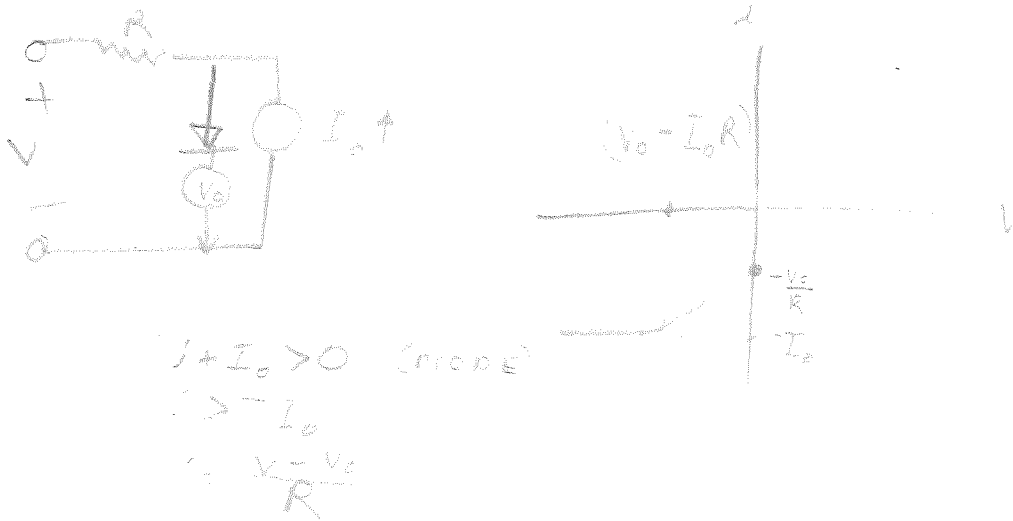

LAB Mesh currents

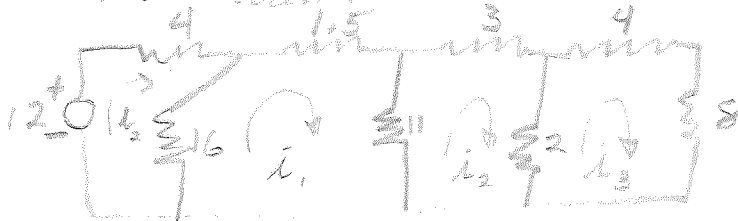


$$\begin{bmatrix} 12 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 20 & -16 & 0 & 0 \\ -16 & 28.5 & -11 & 0 \\ 0 & -11 & 16 & -2 \\ 0 & 0 & -2 & 14 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}$$

Mesh current matrix is symmetrical about the diagonal. All off diagonal are ≤ 0


circuits from equations
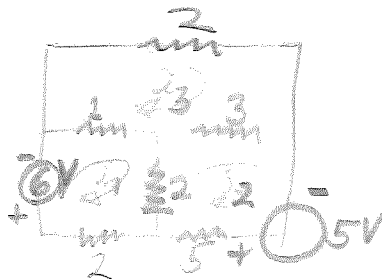
$$\begin{bmatrix} -6 \\ 5 \\ 0 \end{bmatrix} \begin{bmatrix} 5 & -2 & -1 \\ -2 & 10 & -3 \\ -1 & -3 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}$$



diagonal is sum of resistances in around loop

7)

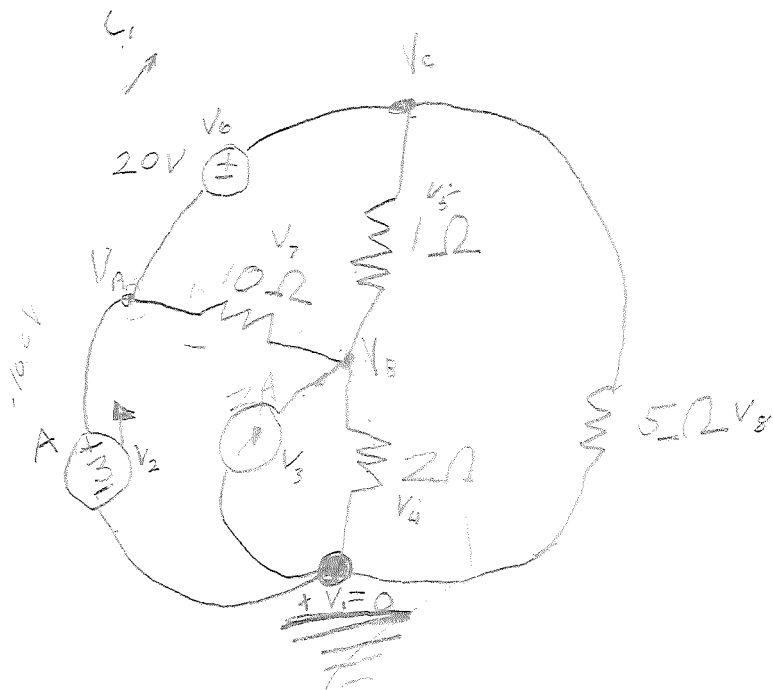

$$3A + 2A = (i_4 + i_5)$$

$$V_C - V_A = 20$$

V_A

$$i_1 + \frac{V_A - V_B}{10} - 3 = 0$$


V_B

$$-2 = \frac{V_B - V_A}{10} + \frac{V_B - V_C}{1} \rightarrow \frac{V_B}{2} = 0$$

V_C

$$-i_1 + \frac{V_C}{5} + \frac{V_C - V_B}{1} = 0$$
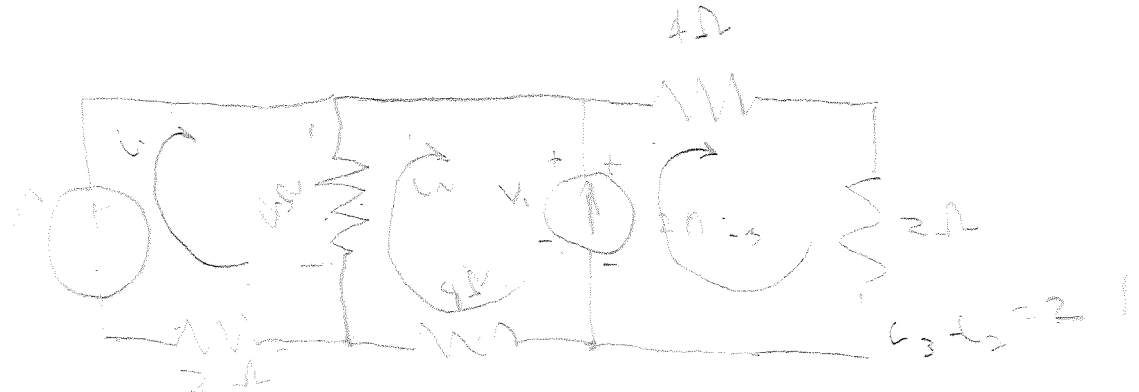
$$-\frac{V_A - V_B}{10} - 3 + \frac{V_C}{5} + V_C - V_B = 0$$




$$-10 + 4(i_1 - i_2) + 2i_3 = 0$$

$$4(i_2 - i_1) + V_1 + 2i_2 = 0$$

$$-V_1 + 4i_2 - 2i_3 = 0$$

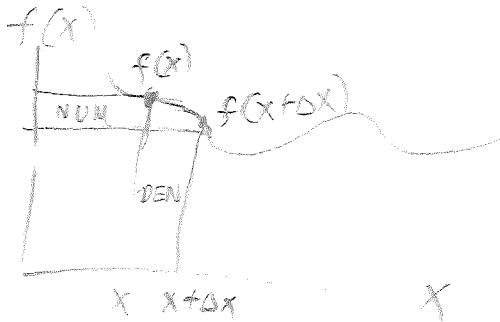
$$\frac{df(x)}{dx} = \lim_{\Delta x \rightarrow 0} \frac{f(x+\Delta x) - f(x)}{\Delta x}$$



TEST ON TEST

Integrals & derivative definitions combining not linear curves
Chapt. 3 as far as we've gone

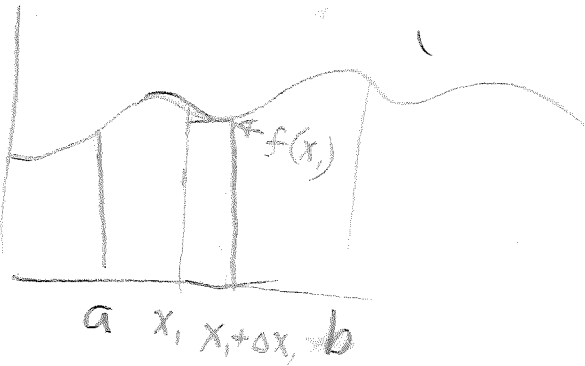
$$\int_a^b f(x) dx = \lim_{\Delta x \rightarrow 0} \sum_{j=1}^N f(x_j) \Delta x; \quad \left(\frac{b-a}{\Delta x}\right) = N \rightarrow \infty$$






Chapt. 3, #12

$$\begin{aligned} 6V_1 - 2V_2 &= 2 \\ -2V_1 + 8V_2 - 4V_3 &= 3 \\ -4V_2 + 5V_3 &= 0 \end{aligned}$$
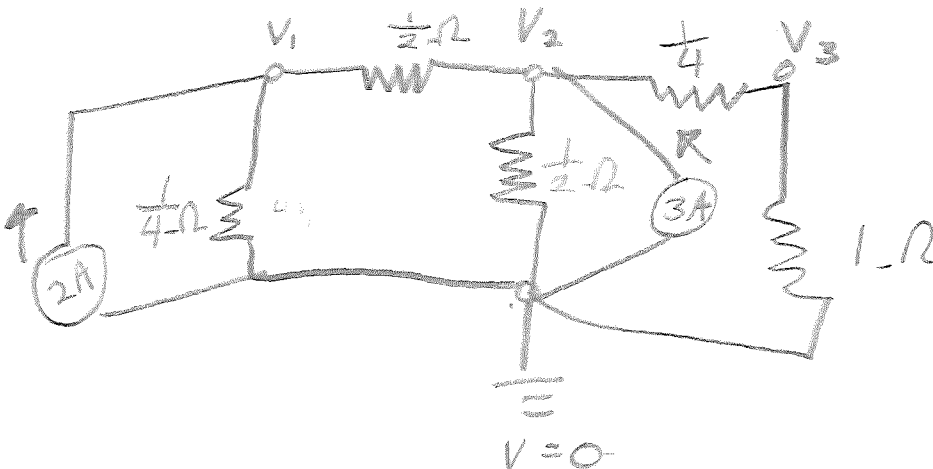
$$\begin{bmatrix} 6 & -2 & 0 \\ -2 & 8 & -4 \\ 0 & -4 & 5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 2 \\ 3 \\ 0 \end{bmatrix}$$




9)

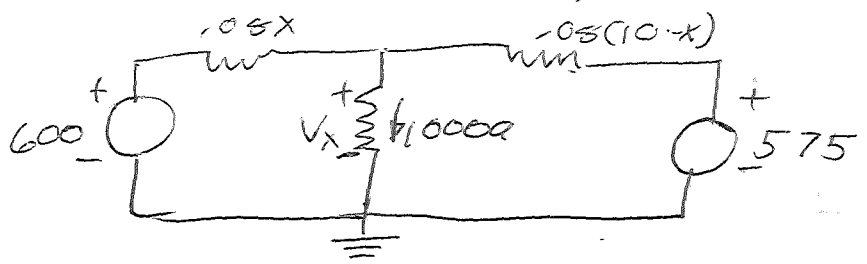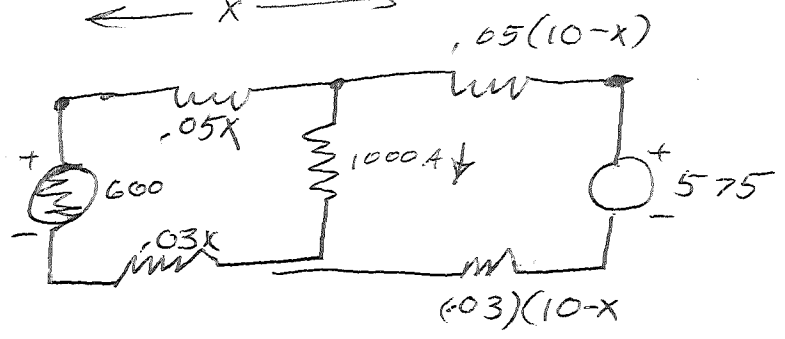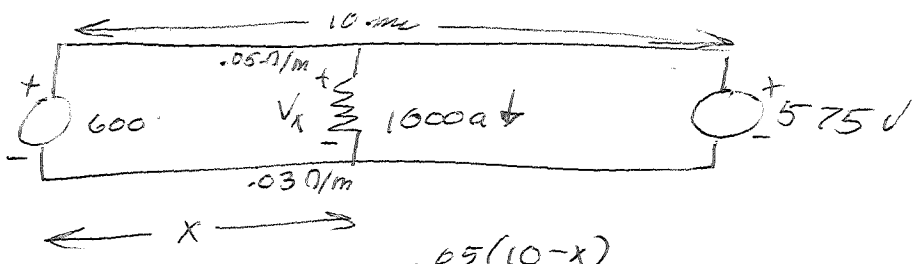


Current at a node: $\frac{600 - V_x}{0.08x} + \frac{575 - V_x}{0.03(10-x)} = 1000$

$V_x = 8x^2 + 82.5x + 600$
 $\frac{dV_x}{dx} = 0 \Rightarrow x = 5.16 \text{ m}$

Diode problems

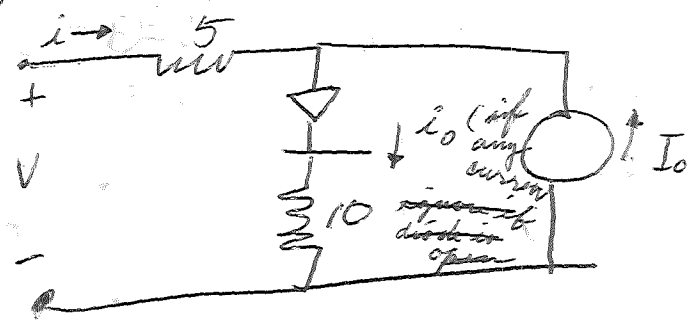


$i_0 = I_0 + i > 0$


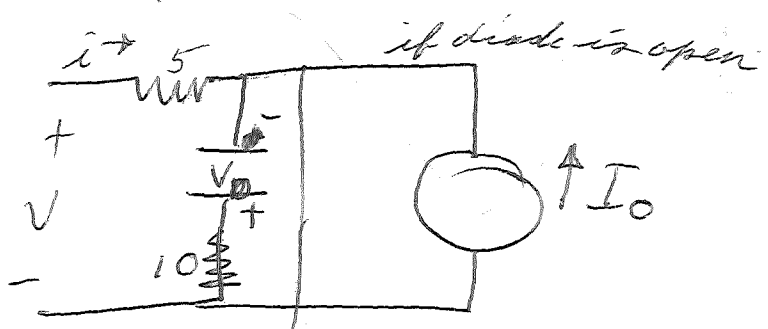


$V_D = 5i - V > 0$
 $V < 5i = -5I_0$
 $i = -I_0$



$i = \frac{1}{15}V - \frac{2}{3}I_0$

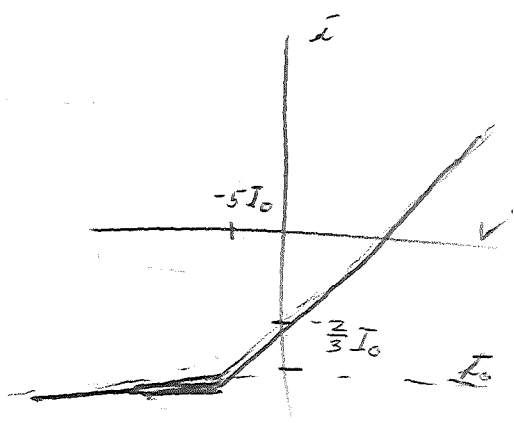

3-24) a)

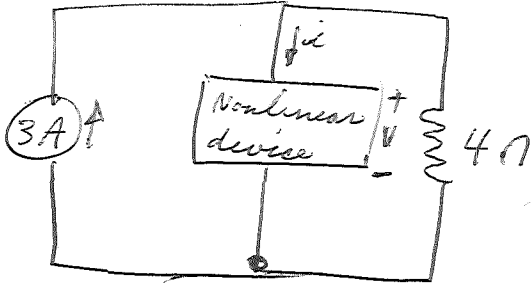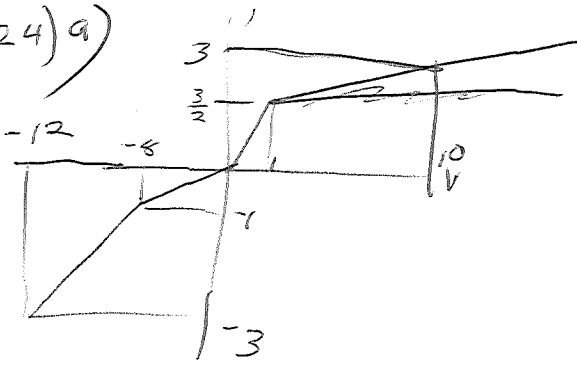



take it out

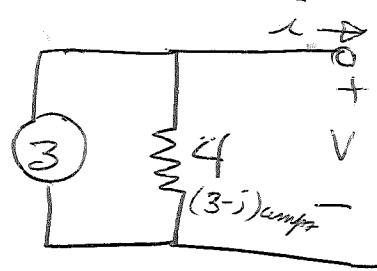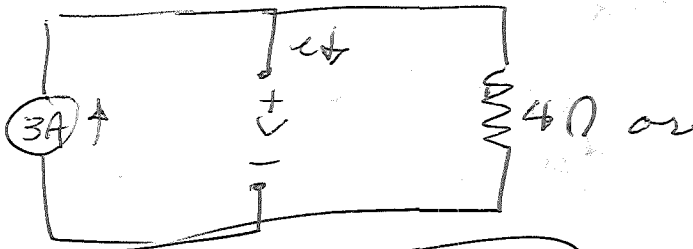

$$V = (3 - j) 4$$

$$j = 3 - \frac{V}{4} = -\frac{V}{4} + 3$$






b)

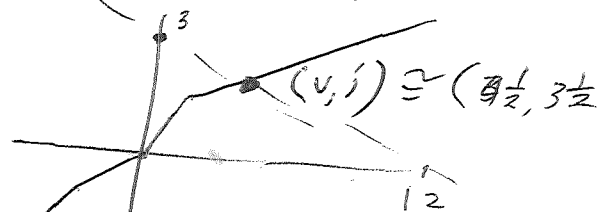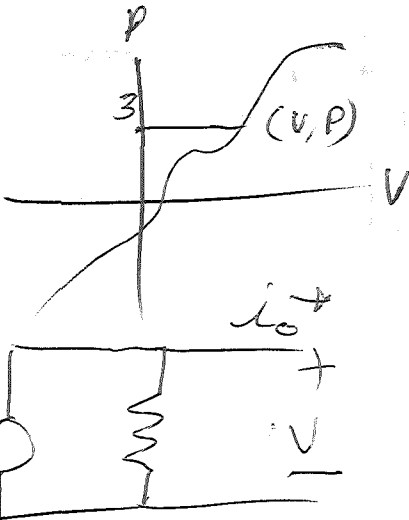

$$i = -\frac{V}{4} + 3$$


~~65 < i < 20~~

$i = 2 \text{ AMPS}$

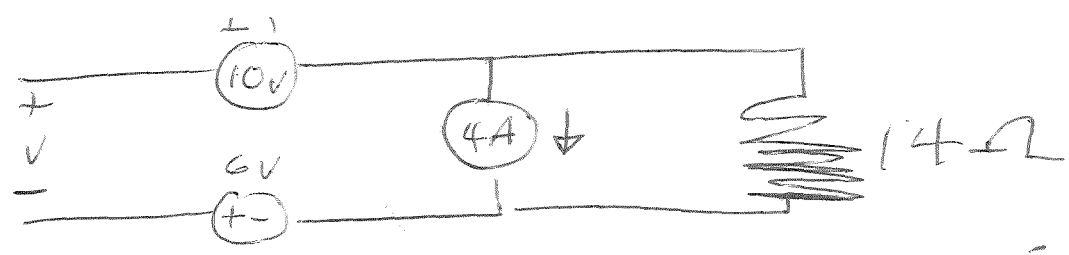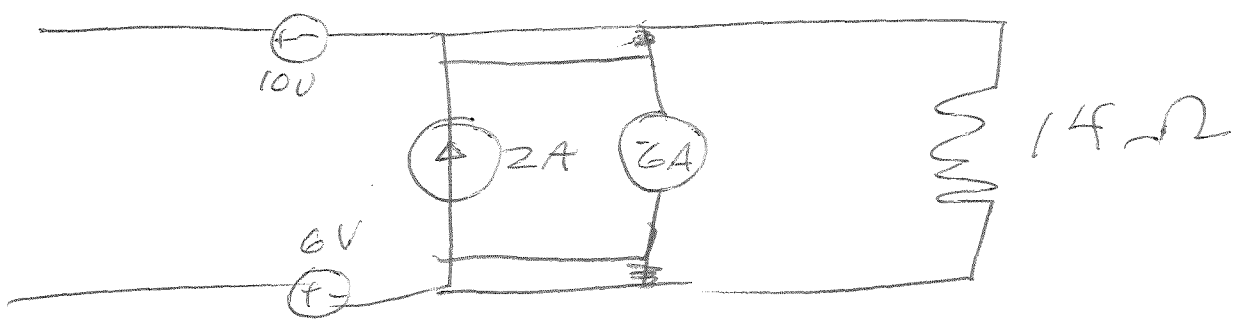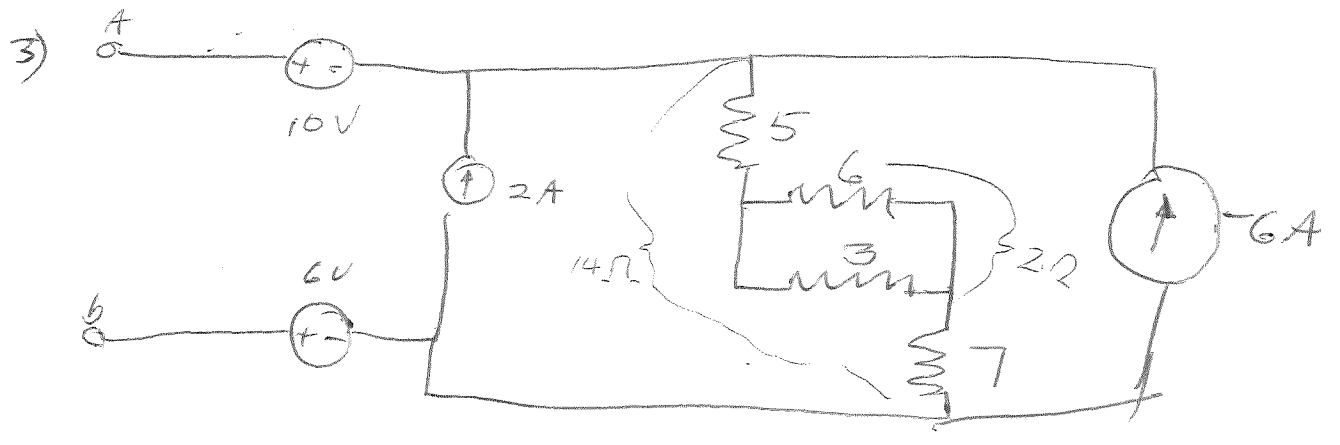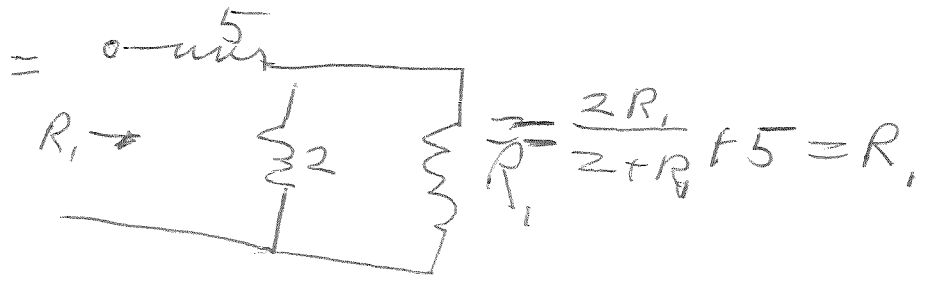
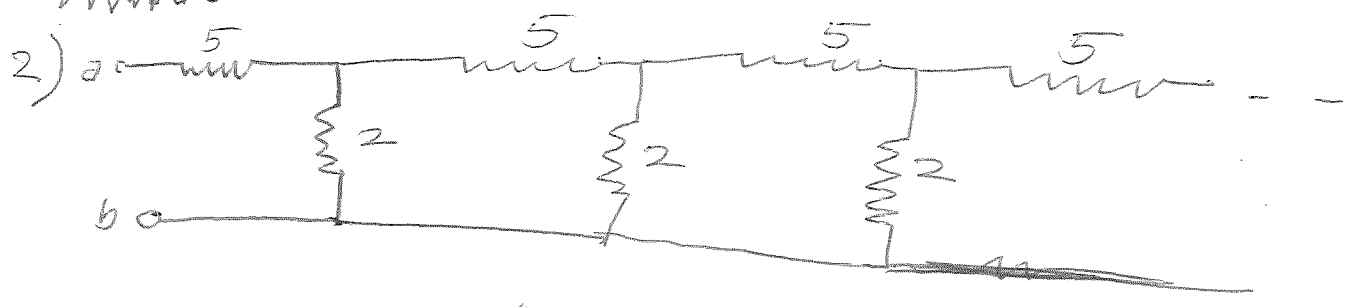


$$V = -6 + (\hat{i} - 4)14 + 10 = -52 + 14\hat{i}$$

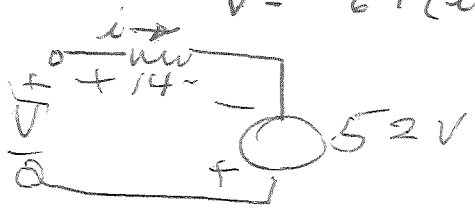
$$\hat{i} = \frac{1}{14}V + \frac{52}{14}$$



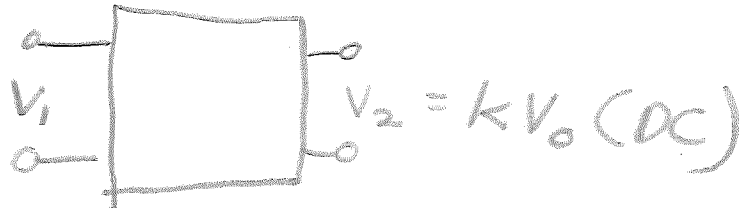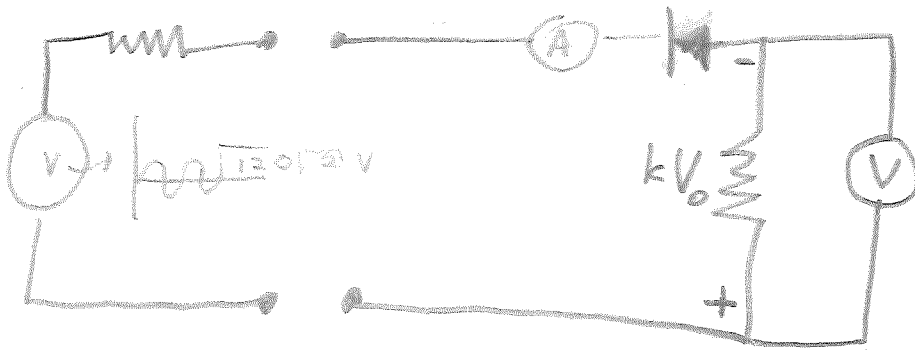
~~Handwritten scribbles and a signature-like mark.~~



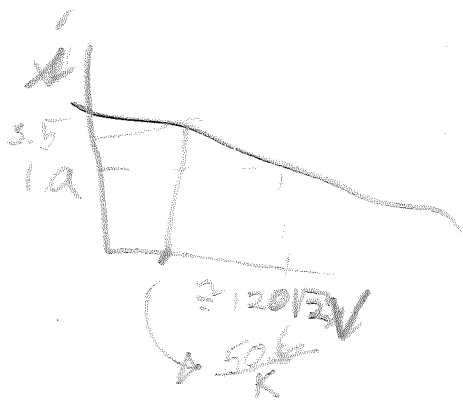But wave ~~shape~~ can't be changed in shape



$$k = \frac{51.2}{12\sqrt{2}}$$

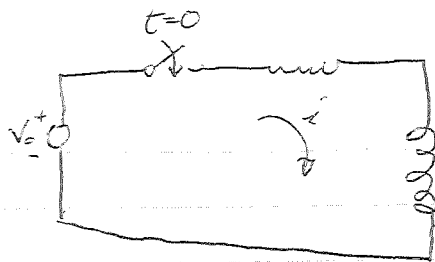

$$V_0 = Ri + L \frac{di}{dt}$$

$$\hat{i}_p = \frac{V_0}{R}$$

$$0 = Ri + L \frac{di}{dt}$$

$$i = I_0 e^{\alpha t}$$

$$0 = R I_0 e^{\alpha t} + L \alpha I_0 e^{\alpha t}$$


$$0 = R + \alpha L$$

$$\alpha = -R/L$$

$$i_c = I_0 e^{-\frac{R}{L}t}$$



$$i(t) = \hat{i}_p + i_c = \frac{V_0}{R} + I_0 e^{-\frac{R}{L}t}$$
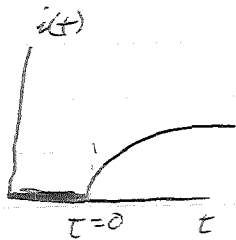
$$i(0^+) = 0 = \frac{V_0}{R} + I_0 \Rightarrow I_0 = -\frac{V_0}{R}$$



$$i(t) = \left(\frac{V_0}{R}\right) \left(1 - e^{-\frac{R}{L}t}\right)$$

$$T = \frac{L}{R}$$

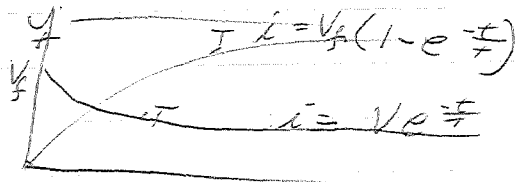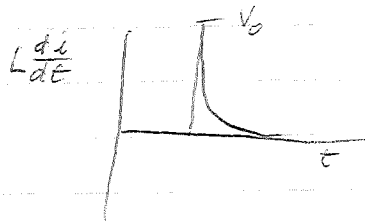

CHAPT 6, #7

Bol Marbas

Electrical Science I



EE-RP1
Oct 69
CCR

Brain Tickler #1

20

HIGH 110
AV 54
LOW 4
FLUNK 35

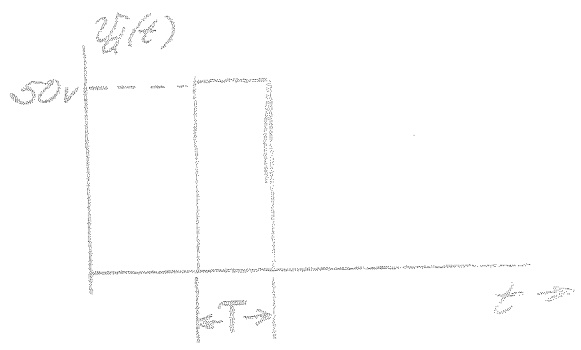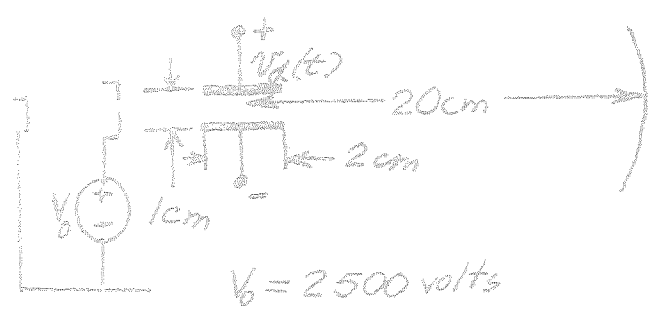Do all work in the space provided. Place your answers in the spaces indicated.



1. For the cathode ray tube sketched above, a "pulse" of voltage $v_d(t)$ of duration T seconds is applied to the deflection plates. (If you wish, you may leave your answers to this problem in algebraic form or numerical form.)
 (a) What is the minimum value of T which will cause a maximum deflection of the beam?

$$\frac{2 \text{ cm}}{V_0}$$

$U_0 = \text{beam's initial velocity}$





$$T = \frac{2 \text{ cm}}{U_0} \text{ seconds}$$




- (b) What will the deflection at the screen in part (a) be?

$U_x = U_0$
 $U_y = \frac{1}{2} a t^2$
 $y = \frac{e E}{2 m V_0^2} x^2$
 $\text{Defl.} = \left[\frac{(20 \text{ cm})^2 e E}{2 m V_0^2} \right]^{1/2}$
 $\frac{dy}{dx} = \frac{e E}{2 m V_0^2} x$
 $\text{at } x = 20 \text{ cm}$
 $P = \tan \theta$
 $D = 20 \text{ cm} \tan \theta$
 $V_0 = 2500 \text{ V}$
 $m = \text{mass of el.}$
 $e = \text{charge on e}$
 $E = \text{electric field between plates} = \frac{V_0}{d}$

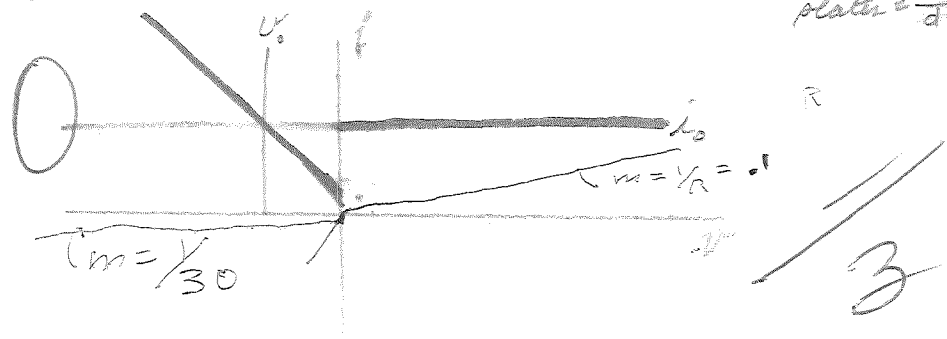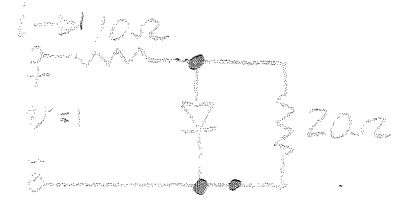2. Determine and accurately sketch the v-i characteristic of the circuit shown.




3

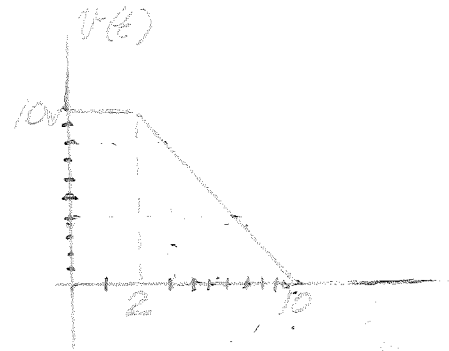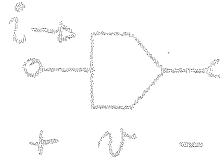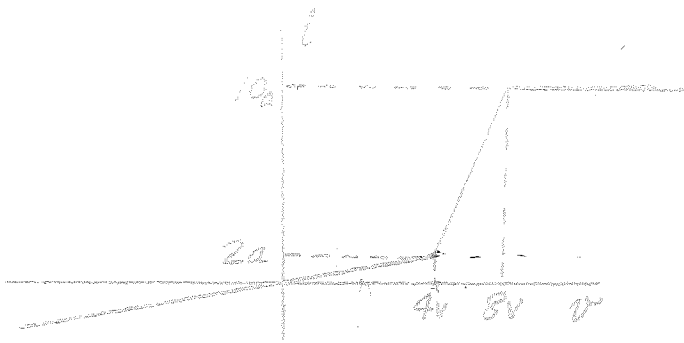


3. The voltage $v(t)$ is applied to the two-terminal device which has the $v-i$ characteristic indicated.

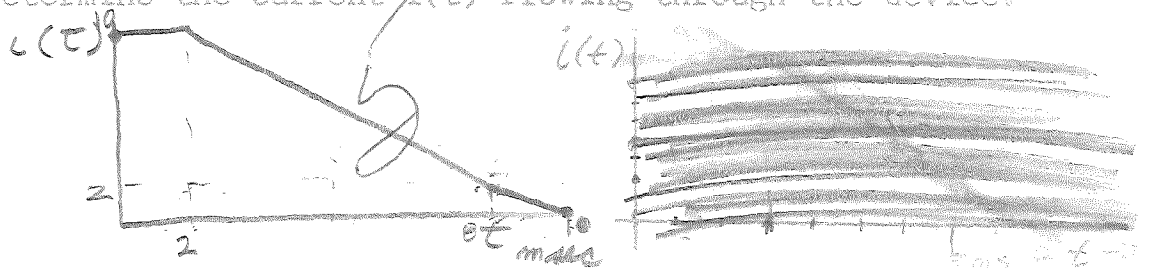(a) Determine the current $i(t)$ flowing through the device.




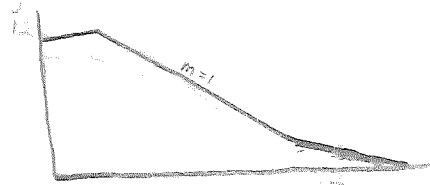(b) Determine the average value of $i(t)$.



Area = 47 amp·ms
 $i(t) = A / 10 \text{ ms}$
 $\bar{i}(t) \approx 4.7 \text{ amp}$

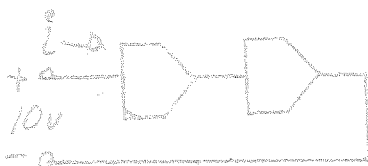
(c) Two identical devices are connected as shown. Determine i , the current flowing through them.



0

$\approx -4.7 \text{ amper}$
 $i = (\text{ANS. TO b}) \times 2$
 (- $i(t)$ amper)

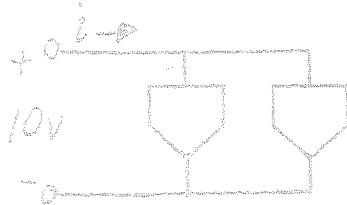(d) Two identical devices are connected as shown. Determine i , the current indicated.



$\approx -8.4 \text{ amper}$
 $i = 2(\text{ANS. TO b})$
 $[2 i(t) \text{ amper}]$

12

4. In problem #1, a pulse of voltage of amplitude 50 volts and duration $2T/3$ (T = time determined in problem 1-(a)) is applied to the deflection plates. What will the deflection of the beam at the screen be?



~~40 cm~~
~~40 cm~~

$$d_N = \frac{2}{3}(2) = \frac{4}{3} = 40 \text{ cm} \approx \frac{2e}{3m_e V_0}$$

$$40 \text{ cm}^2 \left(\frac{e E^3}{2(m_e) V_0^2} \right) = 40 \text{ cm}^2 \frac{e^2}{3m_e V_0} = \frac{40e}{3m_e V_0} = \frac{1.6 \times 10^{-19}}{(9.1 \times 10^{-31})(50)^2} \text{ cm}$$

$\Rightarrow V = Ed$ Deflection = cm

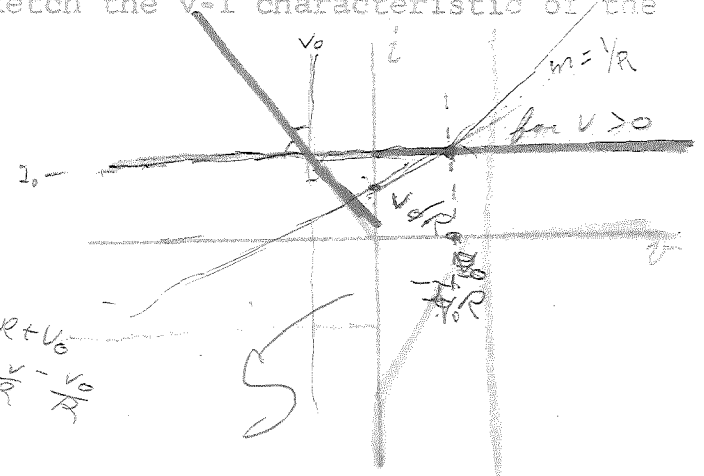
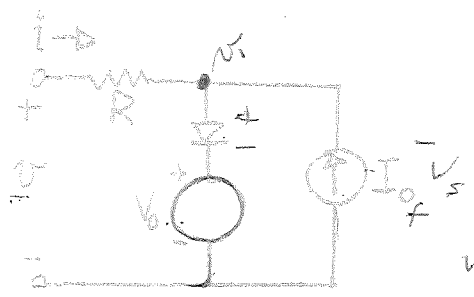
5. Determine and accurately sketch the v-i characteristic of the circuit shown.



$$V = iR + V_0$$

$$i = \frac{V}{R} - \frac{V_0}{R}$$

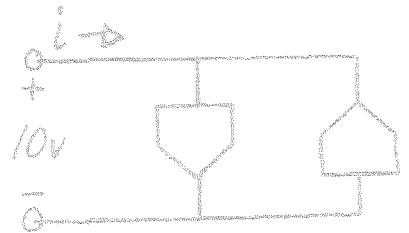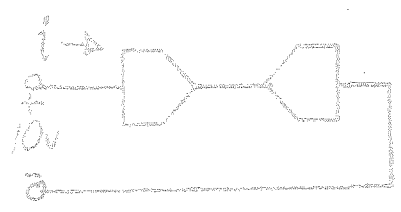6. The devices of problem #3 are connected as shown. Determine the current in each case.



(ans to 3b)

$$i = \underline{4.77 \text{ mA}}$$

$$i = \underline{0} \text{ amps}$$



you have not been into see me yet - Jim expecting you -

BOB MARKS

#1-127
#2-AVER.
LOW-80
EE RFI
Oct 69

73

Electrical Science I


Halloween Trick or Treat

NOTE: In the following definitions and statements, you may use equations, mathematical symbols, graphs, and/or circuit diagrams as you see fit. Words, sentences, and/or phrases are NOT permitted. 2 points will be deducted for each word used.


You may use any letters or symbols without defining them if (a) they are utilized in the text in chapters 1, 2, or 3, or (b) they have been used by Dr. Rogers in class. Any other letters or symbols you wish to use you must define:

1. Define:

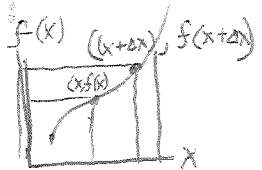(a) $\frac{df(x)}{dx} = \lim_{\Delta x \rightarrow 0} \frac{f(x) - f(x-\Delta x)}{\Delta x} = \lim_{\Delta x \rightarrow 0} \frac{f(x+\Delta x) - f(x)}{\Delta x}$



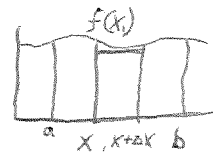(b) $\int_a^b f(x) dx = \lim_{\Delta x \rightarrow 0} \sum_{i=1}^{n} f(x_i) \Delta x$



(c) w(energy or work)



(d) \vec{E} (electric field) $\lim_{\Delta Q \rightarrow 0} \frac{\Delta F}{\Delta Q} = \frac{dF}{dQ}$

(e) $V_{21} = \frac{W_{p2} - W_{p1}}{Q} = - \int \vec{E} \cdot d\vec{l}$

(f) $i = \lim_{\Delta t \rightarrow 0} \frac{\Delta q}{\Delta t}$


25

(g) ~~p (power) = V i~~

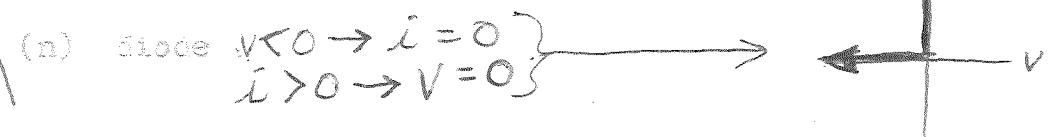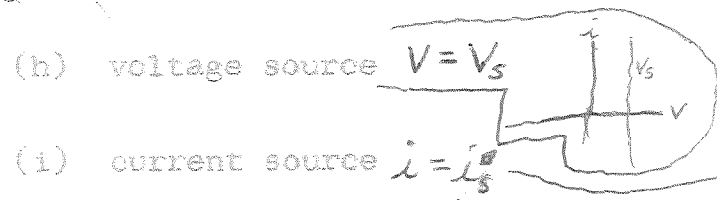

2. State:

(a) Kirchoff's voltage law

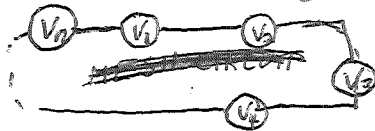

$$\sum V = 0$$

(b) Kirchoff's current law





$$\sum i = 0$$

(c) The law of conservation of charge


} 4

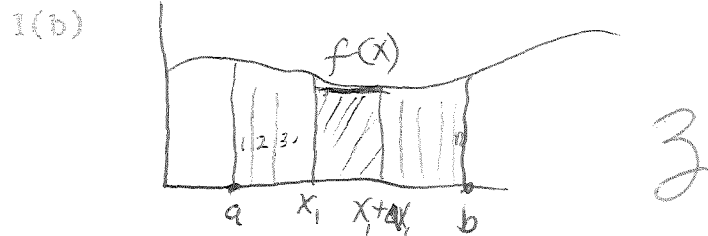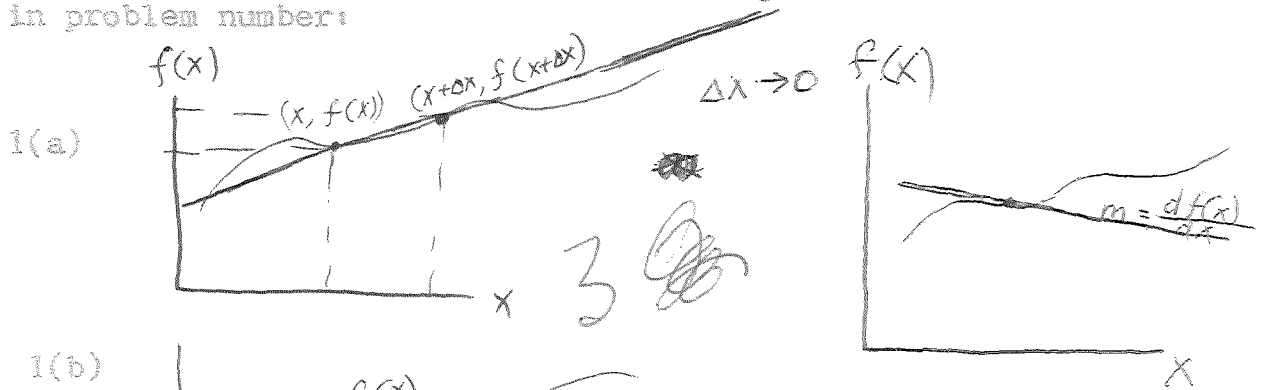
3. Draw a picture to illustrate the meaning of the definitions in problem number:



4. Derive the "plug" for a cathode ray tube and illustrate on the diagram the meaning of each letter which appears in the "plug".

$$d_s = \frac{V_d l_p l_{ps}}{2V_o d}$$

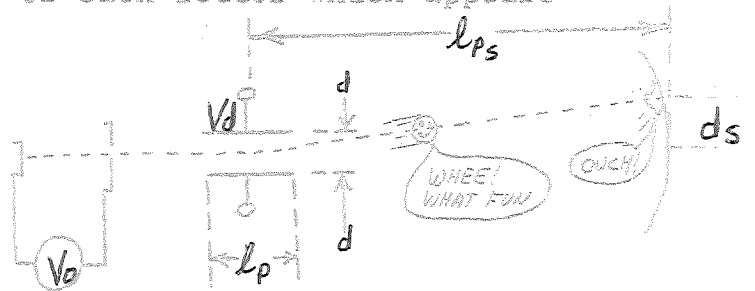

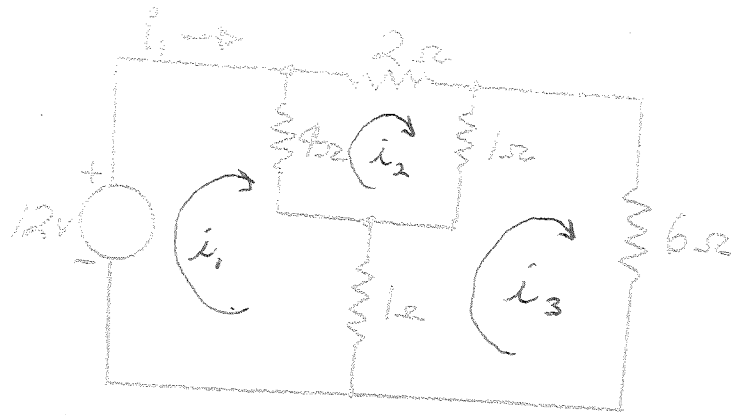

5. Determine i_1 using mesh-current analysis.

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} \begin{bmatrix} 5 & -4 & -1 \\ -4 & 7 & -1 \\ -1 & -1 & 8 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

$$-12 + 4(i_1 - i_2) + 1(i_1 - i_3) = 0$$

$$5i_1 - 4i_2 - i_3 = 12$$

$$4(i_2 - i_1) + 2i_2 + 1(i_2 - i_3) = 0$$

$$-4i_1 + 7i_2 - i_3 = 0$$


$$1(i_3 - i_1) + 1(i_3 - i_2) + 6i_3 = 0$$

$$-1i_1 - i_2 + 8i_3 = 0$$

$$i_1 = \frac{\begin{vmatrix} 12 & -4 & -1 \\ 0 & 7 & -1 \\ 0 & -1 & 8 \end{vmatrix}}{\begin{vmatrix} 5 & -4 & -1 \\ -4 & 7 & -1 \\ -1 & -1 & 8 \end{vmatrix}} = \frac{672 - 120}{280 + 4 + 4 - 5 - 7 - 128}$$

$$= \frac{660}{288 - 140} = \frac{660}{148} = 4.46 \text{ AMPS}$$
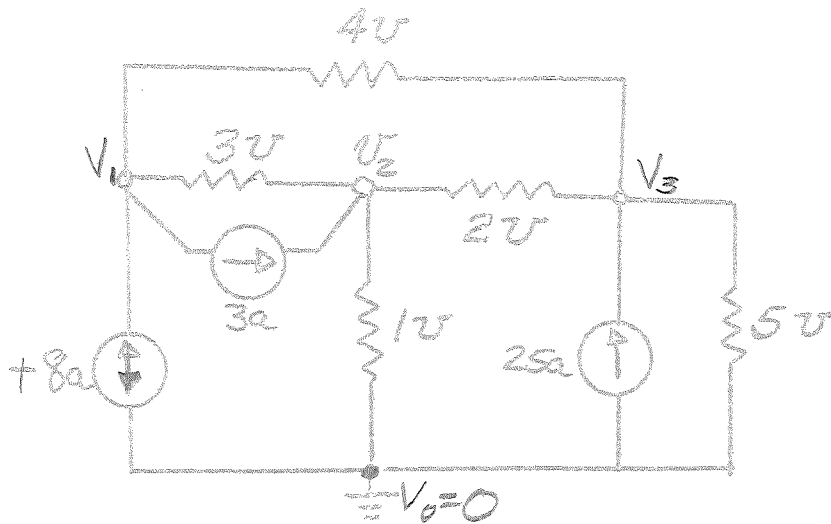
$$\begin{array}{r} 120 \\ 148 \overline{) 1720} \\ \underline{1680} \\ 40 \\ \underline{400} \\ 0 \end{array}$$



6. Determine v_2 using node-voltage analysis.

$$8 + 3 + \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{4} = 0$$

$$\frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{4} = -11$$

$$7V_1 - 4V_2 - 3V_3 = -132$$

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} \begin{bmatrix} 7 & -4 & -3 \\ -2 & 6 & -3 \\ -5 & -10 & 19 \end{bmatrix} = \begin{bmatrix} -132 \\ 18 \\ 500 \end{bmatrix}$$

(NOT SYMMETRICAL
BECAUSE OF SIMPLIFYING
CO-EFFICIENTS)

$$\frac{V_2 - V_1}{3} + \frac{V_2 - V_3}{2} + \frac{V_2}{1} = 3$$

$$-2V_1 + 6V_2 - 3V_3 = 18$$

$$\frac{V_3 - V_2}{2} + \frac{V_3}{5} + \frac{V_3 - V_1}{4} = 25$$

$$10V_3 - 10V_2 + 4V_3 + 5V_3 - 5V_1 = 250$$

$$-5V_1 - 10V_2 + 19V_3 = 250$$


$$V_2 = \frac{\begin{vmatrix} 7 & -132 & -3 \\ -2 & 18 & -3 \\ -5 & 500 & 19 \end{vmatrix}}{\begin{vmatrix} 7 & -4 & -3 \\ -2 & 6 & -3 \\ -5 & -10 & 19 \end{vmatrix}} = \frac{(7)(18)(19) + (132)(3)(5) + (6)(500)}{42(19) - 60 - 30 - 210 - 90 - 8(19)}$$

$$= \frac{2520 + 1980 + 13500 - 270 - 5020}{80 - 54}$$

$$= \frac{1171}{26} = 45 \text{ V}$$

NOTE: This problem, if done properly, takes TIME, but should be straightforward. DO NOT hurry. Use the graph paper provided. You might expect to spend one hour on this problem.

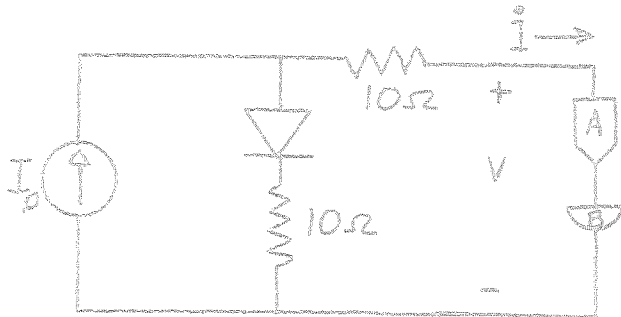The v-i characteristics for devices A and B are shown on the attached sheets and the diode in the circuit is ideal. Determine v and i if (a) $I_0 = +4$ amps, and (b) $I_0 = -2$ amps.



~~$$V = Ri$$

$$i > 0$$


$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \begin{bmatrix} 10 & -10 \\ -10 & 20 \end{bmatrix} = \begin{bmatrix} 24 \\ -2 \end{bmatrix}$$

$$i = \frac{10 \cdot 24 - 10 \cdot (-2)}{10 \cdot 20 - (-10 \cdot 10)}$$

$$i = \frac{10V - 10I_0}{100}$$

$$i = \frac{1}{10}V - \frac{1}{10}I_0$$~~

if $i < 0$

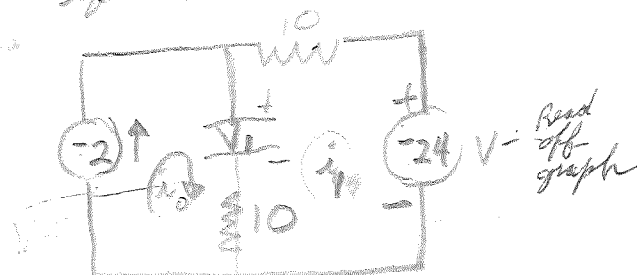

$$\begin{bmatrix} i_0 \\ i_1 \end{bmatrix} \begin{bmatrix} 10 & -10 \\ -10 & 20 \end{bmatrix} = \begin{bmatrix} 24 \\ -2 \end{bmatrix}$$

$$-V_1 + 10(i_0 - i_1) = 0$$

$$-V_1 + 10i_1 = 24 + 10(i_1 - i_0)$$

$$20i_0 - 10i_1 - V_1 = 24$$

$$i_0 = -2$$

$$20i_0 - V_1 = 4$$

$$20(-2) - V_1 = 4$$

$$-40 - V_1 = 4$$

$$V_1 = -44$$

$$10i_1 = 24$$

$$i_1 = 2.4A$$

$$V_1 = 10i = 20$$

$$V_1 = 20 + 10i$$

$$V = 20 + 24$$




$$= 44$$

(a) $V = 16$ volts
 $i =$ amps

(b) $V = 44$ volts
 $i = 2.4$ amps (OVER)

(Take a break. DO NOT work any Electrical Science problems this weekend?)

10

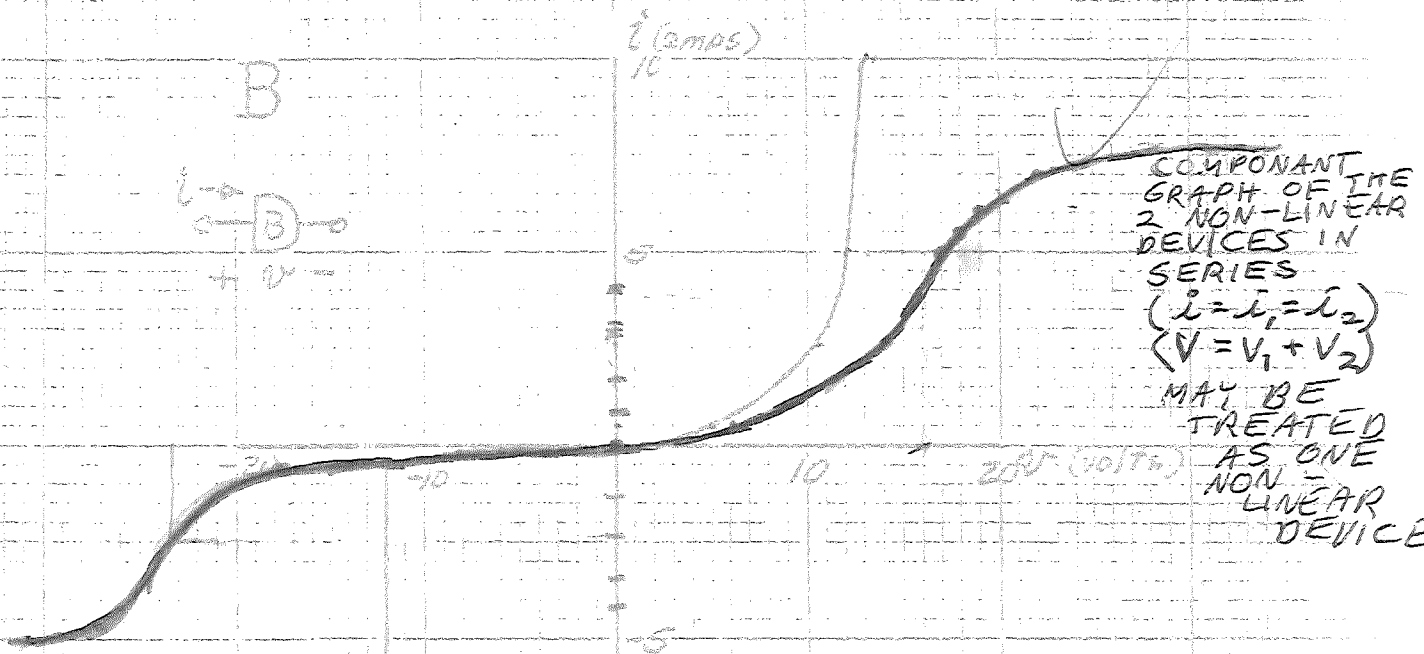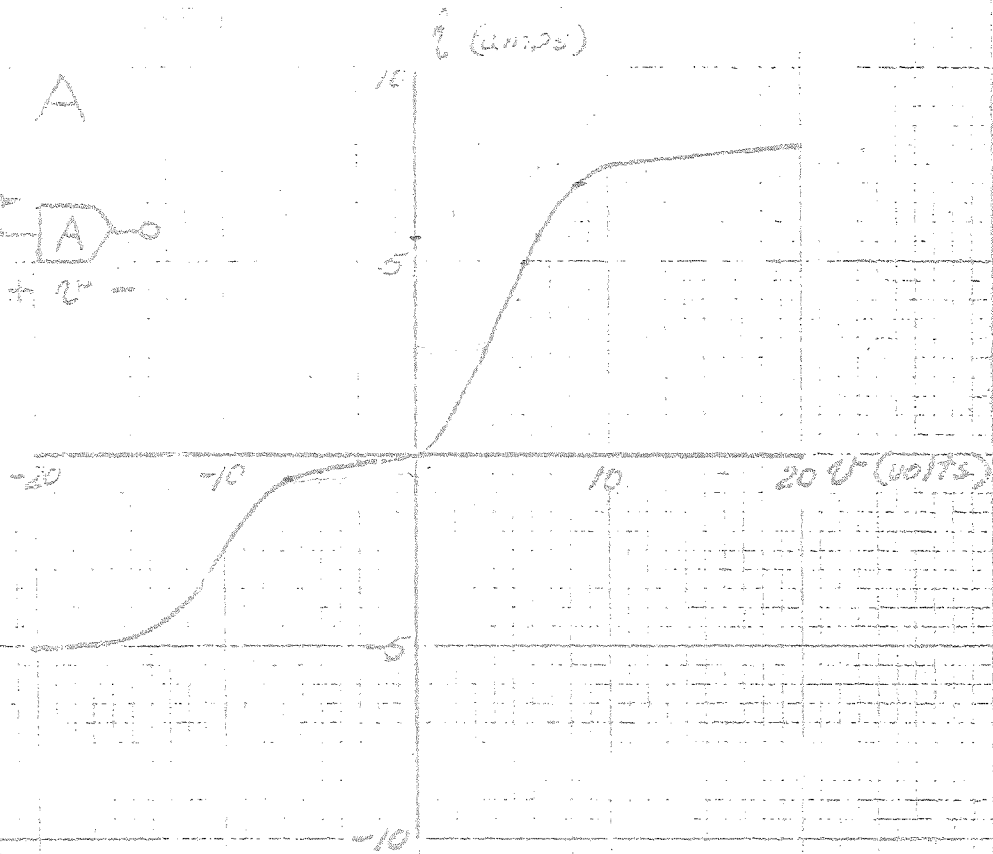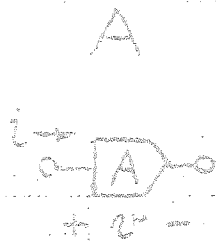

COMPONENT
 GRAPH OF THE
 2 NON-LINEAR
 DEVICES IN
 SERIES
 $(i = i_1 = i_2)$
 $(v = v_1 + v_2)$
 MAY BE
 TREATED
 AS ONE
 NON-
 LINEAR
 DEVICE

i (amps)

10

5

-10

-20

20

40V (volts)

5

-10

$$(a) \frac{df(x)}{dx} = \lim_{\Delta x \rightarrow 0} \frac{f(x+\Delta x) - f(x)}{\Delta x}$$


$$(b) \int_a^b f(t) dt = \lim_{\Delta t_j \rightarrow 0} \sum_{j=1}^n f(t_j) \Delta t_j$$

$$(c) W = \int \vec{F} \cdot d\vec{l}$$



$$(d) \vec{E} = \lim_{q \rightarrow 0} \frac{\vec{F}}{q}$$

$$(e) V_{21} = - \int_1^2 \vec{E} \cdot d\vec{l} \quad (f) i = \frac{dq}{dt}$$


$$(g) P = \frac{dW}{dt}$$

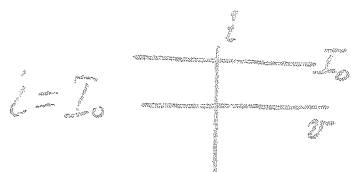

(k)

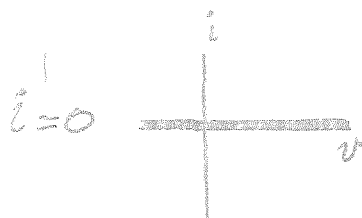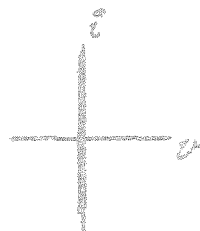

(n)


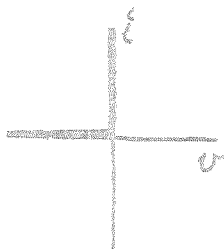


$$2. (a) \sum_{i=1}^N v_i = 0$$


$$(b) \sum_{i=1}^N i_i = 0$$

$$(c) \oint \vec{J} \cdot d\vec{A} = - \frac{dq}{dt} = - \frac{d}{dt} \int \rho dv$$

3. (a)

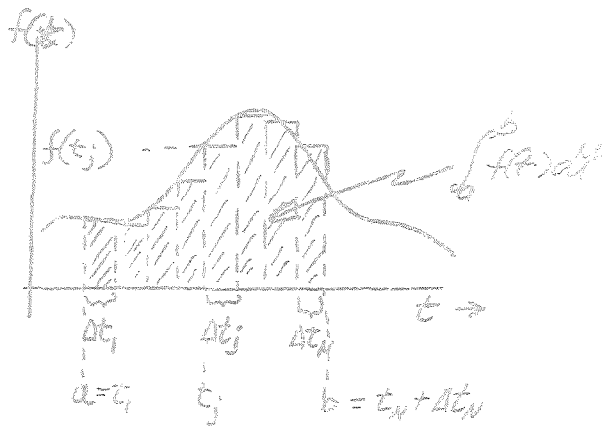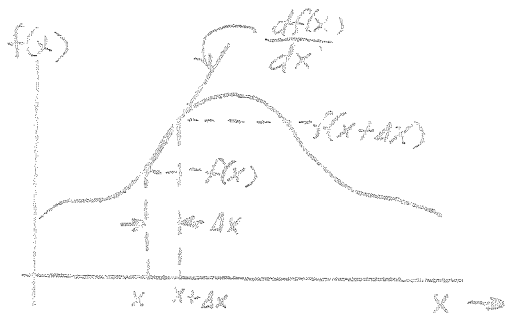


4. QED

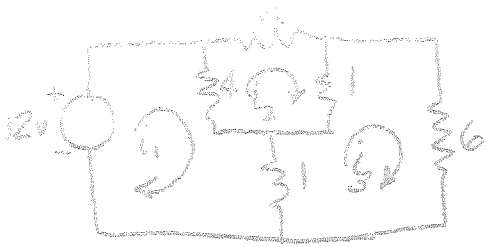

$$\begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 5 & -4 & -1 \\ -4 & 7 & -1 \\ -1 & -1 & 8 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}$$
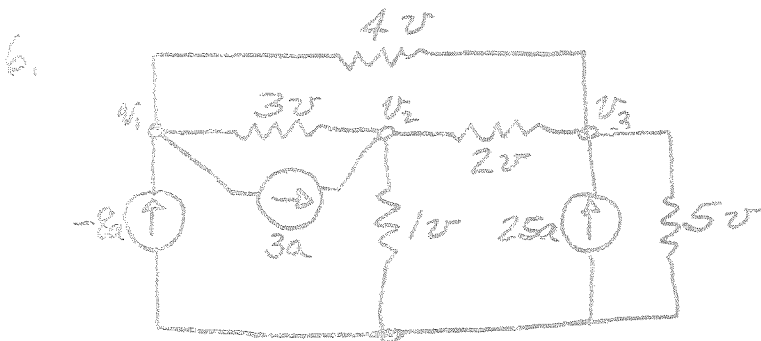
$$i_1 = \frac{\begin{vmatrix} 12 & -4 & -1 \\ 0 & 7 & -1 \\ 0 & -1 & 8 \end{vmatrix}}{\begin{vmatrix} 5 & -4 & -1 \\ -4 & 7 & -1 \\ -1 & -1 & 8 \end{vmatrix}} = \frac{12(56-1)}{5(56-1) + 4(-32-1) - 1(4+7)} = \frac{12(55)}{11(25-12-1)} = 56$$



$$\begin{bmatrix} -11 \\ 3 \\ 25 \end{bmatrix} = \begin{bmatrix} 7 & -3 & -4 \\ -3 & 6 & -2 \\ -4 & -2 & 11 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

$$v_2 = \frac{\begin{vmatrix} 7 & -11 & -4 \\ -3 & 6 & -2 \\ -4 & -2 & 11 \end{vmatrix}}{\begin{vmatrix} 7 & -3 & -4 \\ -3 & 6 & -2 \\ -4 & -2 & 11 \end{vmatrix}} = \frac{7(33+50) + 11(-33-8) - 4(-75+12)}{7(66-4) + 3(-33-8) - 4(6+24)} = \frac{382}{191} = 2 \text{ volts}$$

7. (a) 11 volts
 (b) -22 volts
 -2 amps
 1.5 amps

ELECTRICAL SCIENCE I

Winter Quarter 1970

TEXT: Hayt & Hughes, Introduction to Electrical Engineering,
McGraw-Hill, 1968

<u>Period</u>	<u>Week of</u>	<u>Text Pages</u>	<u>Text Problems</u>	<u>Special Problems</u>
1	Jan. 5			
2		1-17	1-5	
3	12	17-21	1-15, 1-16	
4		29-43	2-5	
5		43-55	2-12, 2-18	
6	19		2-19	
7		61-71	3-6, 3-8	
8		71-82	3-10, 3-12	
9	26	82-91	3-13, 3-14	
10			3-28	1
11				2, 3
12	Feb. 2			4
13		105-116	4-4	
14		116-133	4-9	
15	9	133-142	4-12, 4-20	
16				5
17				6
18	16	195-203	6-5	
19		204-217	6-12	
20		217-226		7, 8
21	23	233-247	7-3	
22		247-257	7-7, 7-17	
23			7-24	
24	March 2			9
25		265-274	8-5, 8-10	
26		275-287	8-12, 8-16	
27	9		8-22	10
28		Review		11
29				
30	16			

VEN

ROSE POLYTECHNIC INSTITUTE
Department of Chemical Engineering

Moore's Rules

Course Grade

Exams, quizzes	60 (1-y)%	
Final	30 (1-y)%	
Problems	10 (1-y)%	
Instructor's Opinion	100 (1-y)%	$0 < y < 0.3$

Problems

Problems will be assigned for nearly every class session. The problems are an essential part of the course and each student is expected to understand the correct solution of each assigned problem. No student in the lower half of the class ranking will be permitted to take the final examination until acceptable solutions to at least 90% of the assigned problems have been turned in.

Until this privilege is abused, it will be permissible for students to work together on homework in groups of two or three. However, each student is expected to contribute significantly toward the solution of the problems, to understand the final solution, and to turn in a solution for grading.

Problems are to be turned in at the beginning of the class session on the due date. The paper should be 8 1/2" x 11", with holes punched so that the returned problems may be kept in a loose-leaf notebook. Only one side of each page is to be used and the margins should be at least 1 1/4" on the left edge and 1" on the right edge. Each problem should be started on a new page. The student's name and the problem number(s) will appear on the reverse side of the last page. In addition, the names of any students who collaborated will be listed.

No numerical grade will be given for problems turned in more than one week after the due date, but such problems will count toward the 90% requirement mentioned above. No late problems will be accepted during the seven days preceding the final exam.

Absences

No make-up exams are anticipated. It is important that the instructor be notified prior to any absence from an exam. If the instructor can not be contacted, leave a message with the secretary at extension 320.

MOORE'S MYSTICAL GRADING SYSTEM

Purpose: Believe it or not, the system is used in an attempt to be fair. It should help account for variation between tests as well as the usual variation between students.

How Standard Scores Are Calculated: The mean and the standard deviation are computed for each test. [Of course, the mean is the average score and the standard deviation is related to the "spread", or distribution, of scores.] Each raw score is then converted to a standard score by using the following equation.

$$Z_i = \frac{x_i - \bar{x}}{\sigma}$$

where Z_i is the standard score

x_i is the raw score

\bar{x} is the mean

and σ is the standard deviation

Thus, a standard score is the number of standard deviations above or below the mean. A positive score is above the mean and a negative score is below the mean. Standard scores are measures of the performance in comparison with all other scores without regard to the numerical value of the average score or the distribution.

Combining Standard Scores: If all tests were of the same difficulty and importance, an individual's standard scores could simply be added to arrive at a total score. However, not all tests are of equal difficulty and importance. To correct for such differences, weighting factors are used. Every standard score will be multiplied by a weighting factor which is determined by the instructor and is based on the difficulty and importance of the test.

An individual's final cumulative score is the algebraic sum of the products of each standard score multiplied by the appropriate weighting factor. The final cumulative scores are used to rank students from top to bottom. No predetermined distribution of grades, such as a "normal" curve, is assumed.

UNIVERSITY OF KENTUCKY
DEPARTMENT OF CHEMICAL ENGINEERING

Problem Grading Standards

<u>Grade</u>	<u>Criteria</u>
5	Correct method, correct answer, clear presentation, neat paper, on time
4	Correct method but with one of the following: a) minor error in calculation b) unclear presentation c) paper not neat
3	Correct method (or minor error in method) plus more than one of the following: a) error in calculation b) unclear presentation c) paper not neat
2	Major error(s)
0	Paper not turned in

Late papers will receive a maximum grade of 3

(E-1X)

ENERGY - ability to do work


WORK - Force times distance (MECHANICAL)

RESISTOR - DISSIPATES ENERGY (CONSUMES)

INDUCTOR - CONVERTS EL. E. INTO MAGNETIC FLD

CAPACITOR - " " " " " ELECTRIC "

DIRECTION OF EL. FLD

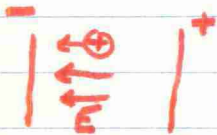

$$E = \frac{F}{q}$$

x1-1)

a) 10^{-13} coul e^-
 \oplus 10^{-6} m \ominus

$$F = \frac{q_1 q_2}{4\pi\epsilon_0 r^2} = \frac{(10^{-13})(1.6 \times 10^{-19})(9 \times 10^9)}{(10 \cdot 10^{-6})^2}$$

$$= 1.44 \times 10^{-12} \text{ N}$$

b) $E = 3 \times 10^6 \frac{\text{V}}{\text{m}}$

$$F = (3 \times 10^6) e_0$$

$$= .481 \times 10^{-12} \text{ N}$$


c) $E = \frac{Q}{\epsilon_0 A}$

$$F = Q_c E = \frac{Q F Q}{\epsilon_0 A}$$

$$= .181 \times 10^{-12} \text{ NT.}$$

X1-3)

a)

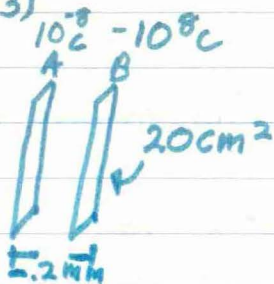

$$E = \frac{Q}{\epsilon_0 A}$$

$$V = Ed$$

$$= \frac{Qd}{\epsilon_0 A}$$

$$= \frac{(10^{-8})(.2 \times 10^{-3})}{(8.85 \times 10^{-12})(20 \times 10^{-4})}$$

$$= 113 \text{ V}$$

b) $W = qV$

$$V = \frac{W}{q}$$

$$= \frac{9(8 \times 10^{-18})}{(1.602 \times 10^{-19})}$$

$$= -50 \text{ V}$$


c) $2 \times 10^6 \frac{\text{V}}{\text{m}} \rightarrow$

$$V = Ed$$

$$= (2 \times 10^6)(.2 \times 10^{-3})$$

$$= 400 \text{ V}$$

X1-4)

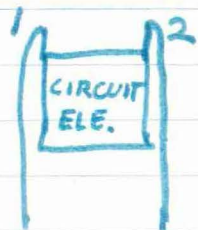


a) 2 COUL_{1,2}

3 JOULES

$$V = \frac{3J}{2C} = -1.5 \text{ VOLTS}$$

b) $V = \frac{+9.6 \times 10^{-19}}{-1.602 \times 10^{-19}}$


$$= -6 \text{ VOLTS}$$

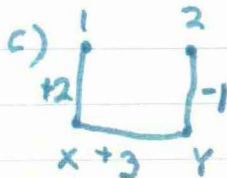

V IS INDEPENDENT OF PATH $\therefore V_{1,2} = 4$


FOR REFERENCE; KEEP CURRENT +
GOING IN POSITIVE TERMINAL

$$P = Vi$$

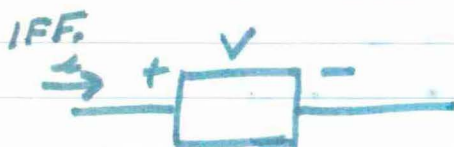

X1-5)

a)

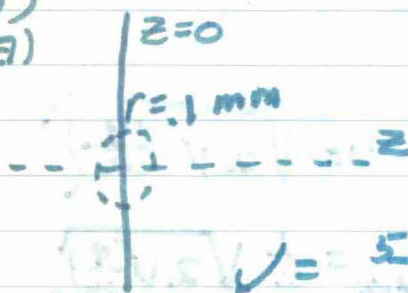

$$i = J \pi r^2$$

$$= -157 \mu A$$

b) $D = 10^8 \text{ e/m}$

$$U = 10^7 \frac{\text{m}}{\text{s}}$$

$$i = \nabla \cdot D U = (10^8) (-1.602 \times 10^{19}) (10^7 \frac{\text{m}}{\text{s}})$$

$$= -160 \mu A$$


c) $i = \int J dA$

$$= \int_0^{\infty} \frac{2}{r} e^{-10,000r} \pi 2R dR$$

$$= -126 \mu A$$

HOMWORK PROBLEMS

1-5)

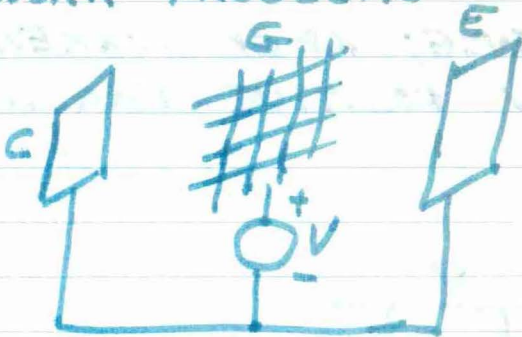


AT GRID, $U=0$, K.E IS MAX

a) ANSWER $U=0$

b) $\frac{1}{2} m v_f^2 = qV$

~~$v = \sqrt{2mU_f}$~~ $U = \sqrt{2V \left(\frac{q}{m}\right)}$

c)

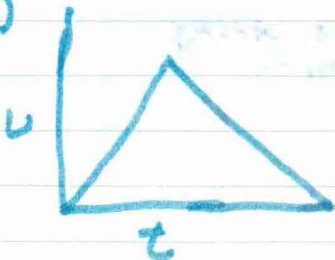

$U_{avg} = \frac{1}{2} \sqrt{2V \left(\frac{q}{m}\right)}$

1-12-70

1-120-70

THE CATHODE RAY TUBE

+ ION SHIELD: COLLECTS + GAS IONS IN TUBE

FILAMENT: HEATS UP & EMITS ELECTRONS


CONTROL GRID: CONTROL'S # E

ANODE - TO ACCELERATE E'S

FOCUSING ANODE - NARROWS BEAM DOWN FOR SHARPER PIC.

SCREEN - COVERED WITH PHOSPHOR

CATHODE RAY OSCIL.

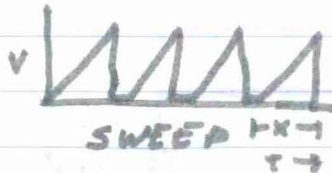

SWEEP CONTROLS AT (HORIZONTAL DEFLECTION PLATES

INPUT CONTROLS VERTICAL D.P.


PROBLEM #16

a) WOULD DOUBLE

b)

1-14-70


07-051-1

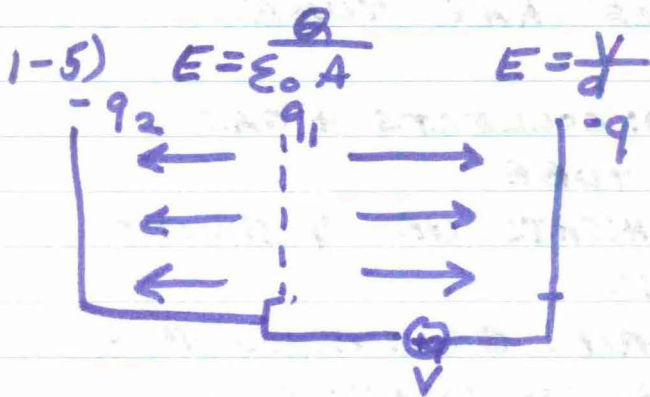

$$E_1 \neq -E_2$$

$\therefore Q$ MUST BE KNOWN
IN THIS CASE.


WOULD USE $E = \frac{V}{d}$

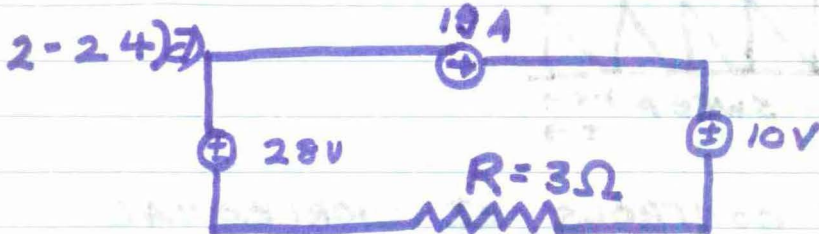

REARRANGE, PLUG & CHUG.

SHOULD HAVE CURRENT
ENTERING POSITIVE IS
CHOOSING TERMINALS
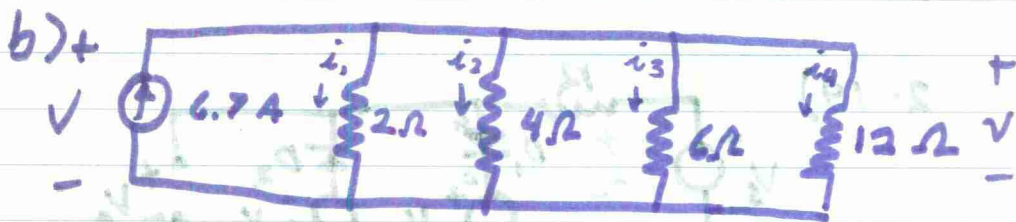
$$P_{CS} = -741 \text{ WATTS (GIVING OFF ENER)}$$



$$V = i Z \quad (Z = \text{IMPEDENCE})$$

$$6.7 \text{ A} = i_1 + i_2 + i_3 + i_4$$

$$V = 2i_1 = 4i_2 = 6i_3 = 12i_4$$

$$i_1 = 6i_4 \text{ ETC.}$$


$$P_{cs} = -Vi \approx 45 \text{ WATTS}$$

(USE $-Vi$ IN THAT THERE IS INCONSISTANCE IN REFERENCES)


IF CURRENT ENTERS A NEGATIVE TERMINAL, $P = -Vi$

1-16-70

2-19)

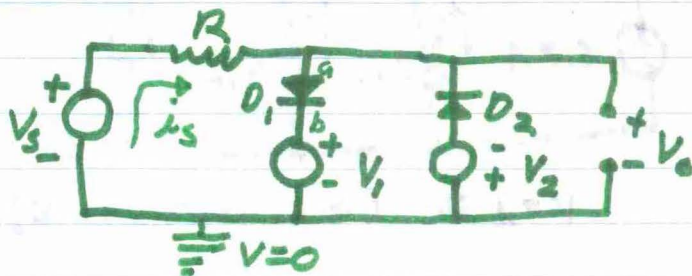
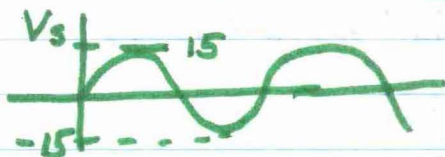
$$V_1 = 5V \quad V_2 = 2V \quad V_s = 15 \sin \omega t$$




V_s IS NOT IN // WITH V_D CAUSE OF RESISTOR


D_1 WILL CONDUCT FOR $V_s > 5$
(NO ∇ DROP OVER $R \Rightarrow i = 0$)

$$V_{D_{MAX}} = 5V$$

\therefore

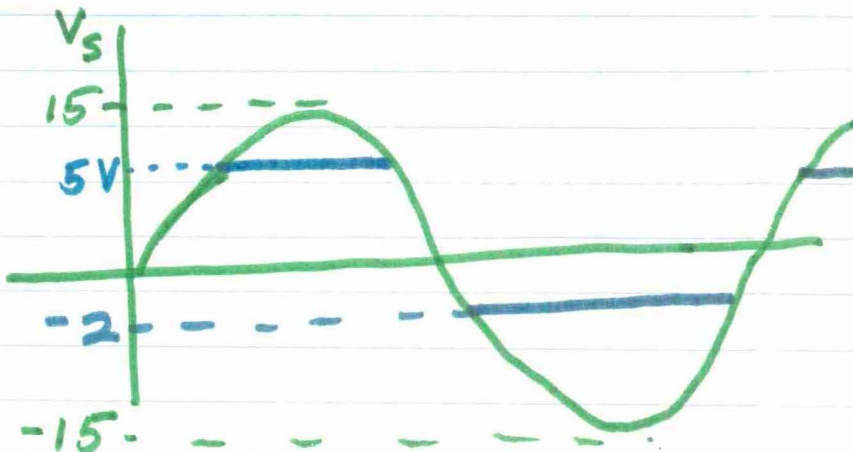

DIODE:

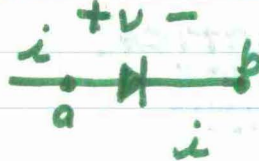


~~$V_b < V_a$~~




FOR IDEAL DIODE

FLUID ANALOGY:

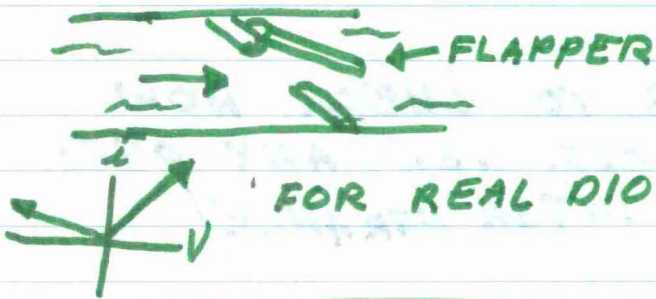

FOR REAL DIODE

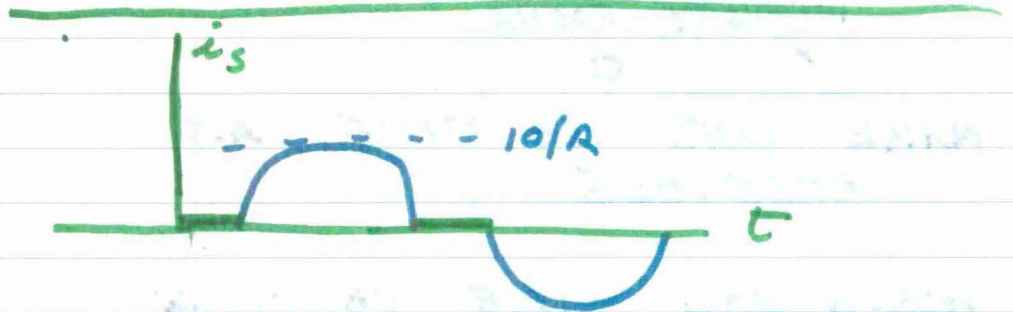


1-16-70 - LAB

THE OSCILLOSCOPE



VERTICLE

CONTROLS VERTICAL DEFLECTION

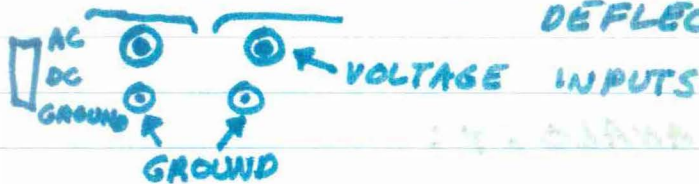

A & B TO CHECK HOW GOOD OSS. IS. ANY OUT-SIDE INTERFERANCE

INTENSITY FOCUS



MAKE LINE AS FINE AS POSSIBLE

HORIZONTAL LIKE VERTICLE BLOCK. WHEN IN USE, PUT TIME SWEEP = 0

○
FREQ

○
TIME SWEEP

□⁺ IF ON PLUSS, OSS. WOULD
START ON FIRST POSITIVE
SLOPE

500 MV 5 MV
0 0 -TO TEST
CALIBRATION


1-19-70

- 1) FIELD EMISSION OF ELECTRON
PULL OF ELECTRONS ✓
- 2) PHOTOELECTRIC EMISSION
(BY MEANS OF RADIATION,
SUCH AS LIGHT)
 - a) PHOTOTUBE - MUCH LIGHT YIELDS
MINIMUM CURRENT
 - b) PHOTOMULTIPLIER - LIGHT EMITS
ELECTRONS, WHOSE NUMBERS
ARE MULTIPLIED BY SEC. EMISSION (Pg. 37)
- 3) SECONDARY EMISSION - LIKE POOL.
ELECTRON
HEAT EMITS ELECTRONS FROM
IT'S KINETIC POTENTIAL ENERGY
- 4) THERMIONIC EMISSION - BY THERMO
ENERGY (BY HEATING CATHODE)
 - a) MOST COMMON TYPE
 - b) USED IN VACUUM TUBES

WHEN ELECTRIC FIELD INTENSITY IS GREAT ENOUGH TO REMOVE ALL THE EMITTED ELECTRONS:

$$i(T) = 0 A T^2 e^{-b/T}$$

FOR A GIVEN VOLTAGE.

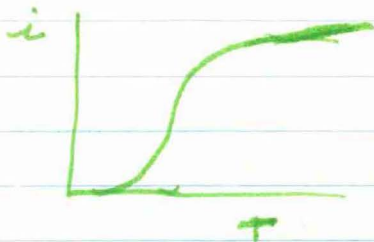

TAPERS OFF BECAUSE TRANSPORTATION CAN'T MEET EMISSION

CHILD-LANGMUIR LAW

$$i(V) = 2.33 \times 10^{-6} \frac{A}{cm^2} V^{3/2}$$

AT A GIVEN TEMP.



HERE, EMISSION CAN'T MEET TRANSPORTATION.

- x 2-3) $i(\pi) = 43.7 \text{ mA}$ - CAPACITY FROM CATH. (MAX.)
 $i(1) = 4.58 \text{ mA}$
 $i(2) = 12.95 \text{ mA}$
 $i(10) = 150 \text{ mA}$


1-21-69

DEFINITIONS:


- 1) VOLTAGE SOURCE HAS SAME POTENTIAL FOR ALL CURRENTS
- 2) CURRENT SOURCE HAS SAME CHARGE DISPLACEMENT FOR ALL VOLTAGE
- 3) OHM'S LAW: $V = iR$
(i MUST GO INTO + TERMINAL)

INCREMENTAL: $r = \frac{dV}{di}$

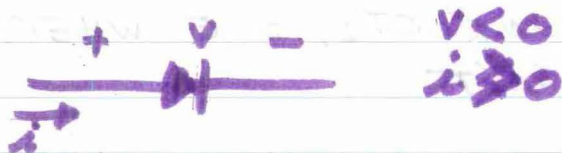
- 4) DIODE - NO REVERSE CURRENT & NO FORWARD VOLTAGE.



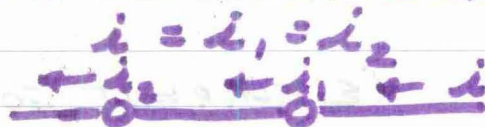- 5) OPEN CIRCUIT: $i = 0$
(A CURRENT SOURCE)
- 6) SHORT CIRCUIT: $V = 0$
(A VOLTAGE SOURCE)
- 7) SERIES CONNECTION



- 8) V/ CONNECTION

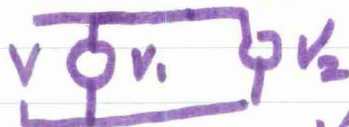


$V = V_1 = V_2$

$$V_{AVE} = \bar{V} = \frac{1}{T} \int_{t_0}^{t_0+T} V dt$$


1-23-70

TEST UP TO PAGE 63

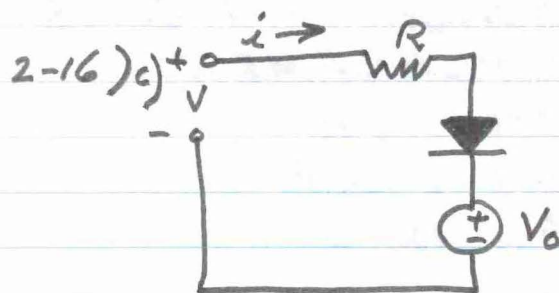

non-conduct
 $i=0$
 conduct

$$V = V_0 + iR$$

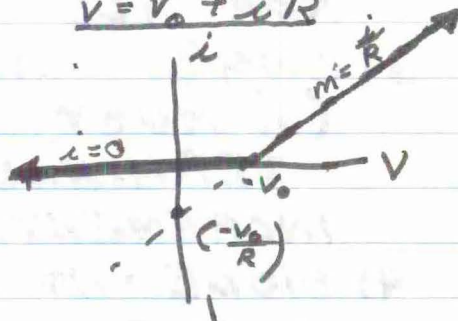

THE DIODE

GRAPH TWO PARTS. ONE PART WHERE IT CONDUCTS, ONE WHERE IT DOESN'T

KIRCHHOFF'S LAWS

1) $\sum_{i=0}^N V_i = 0$ (Σ VOLTAGES AROUND A CLOSED PATH)


A CLOSED PATH! NOT NECESSARILY A MESH!

2) $\sum_{j=1}^M i_j = 0$ (Σ CURRENT GOING IN AND OUT OF NODE)

1-26-70

NTD TO FIND VOLTAGES BY KIRCHHOFF'S LAW

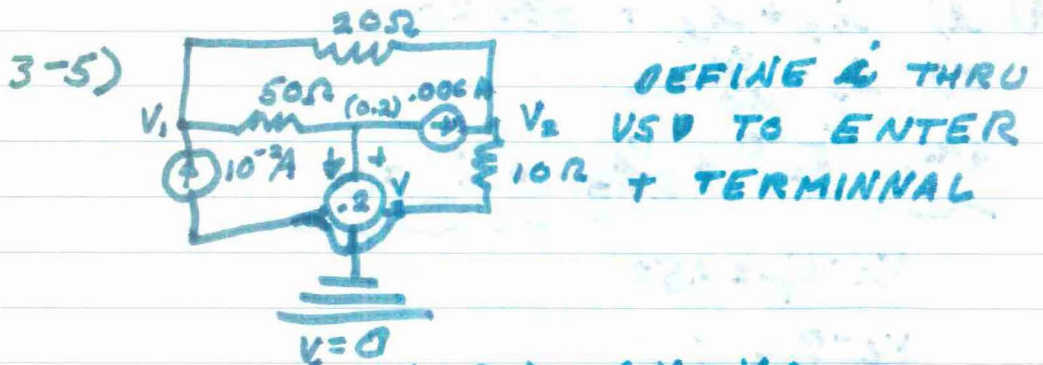
- 1) DEFINE i_s THROUGH V SOURCE
- 2) Σ CURRENTS AT NODE
- 3) Σ NODES $\rightarrow \Sigma - 1$ INDEPENDENT EQUATIONS




$$V = 0$$

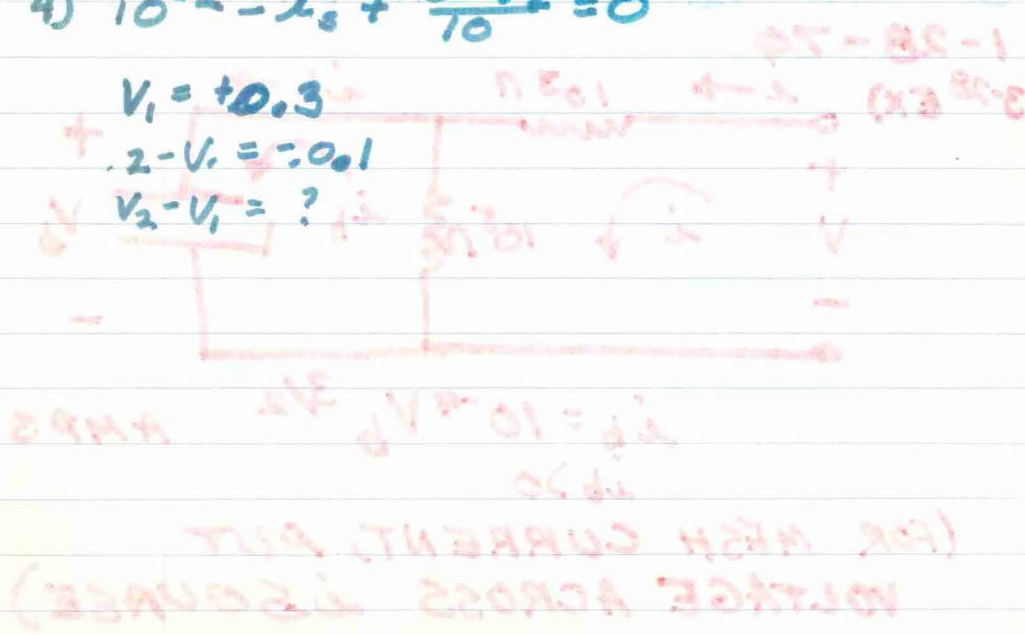- 1) $-10^{-2} + \left(\frac{V_1 - 2}{50}\right) + \left(\frac{V_1 - V_2}{20}\right) = 0$
- 2) $\frac{V_2 - V_1}{20} + (-0.006) + \left(\frac{V_2 - 0}{10}\right) = 0$
- 3) $\frac{V_1 - 3}{50} + (-i_s) - 0.006 = 0$
- 4) $10^{-2} - i_s + \frac{0 - V_2}{10} = 0$

$V_1 = +0.3$
 $2 - V_1 = -0.1$
 $V_2 - V_1 = ?$



3-10)

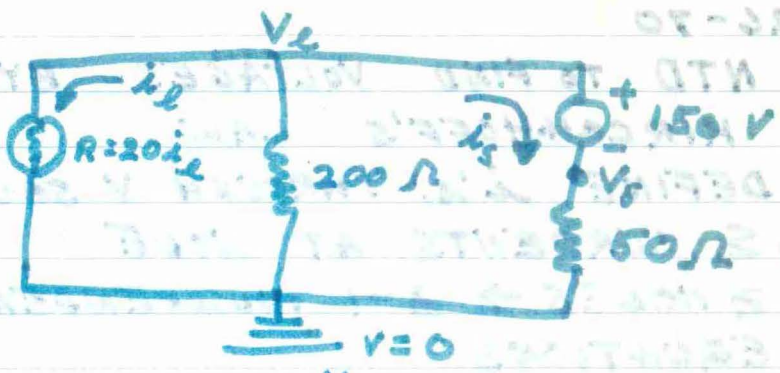

1) $i_s + i_L + \frac{V_S}{200} = 0$

5) $i_s - \frac{V_S}{50} = 0$

(KRO) $\frac{V_S - 0}{50} + \frac{V_L}{200} + i_L = 0$

$V_L - V_S = 150$


$\frac{V_L - 0}{20 \Omega} = i_L$

2 VALUES OF i_L , use $i_L > 0$

B) THEN $V_L - V_S = 300 \Rightarrow R = \frac{8}{3} \Omega$

1-28-79

3-28 EX)

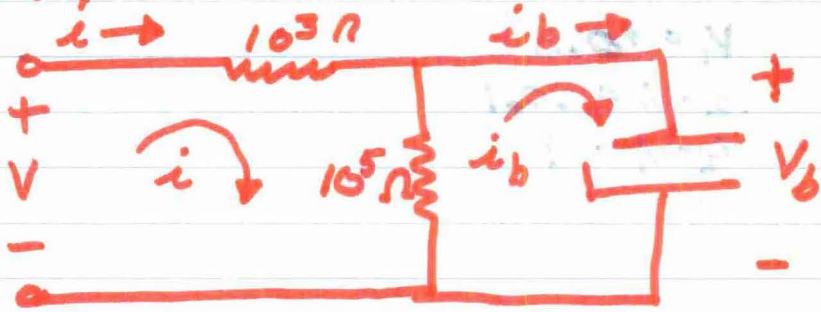


$i_b = 10^{-4} V_b^{3/2}$ AMPS
 $i_b > 0$

(FOR MESH CURRENT, PUT VOLTAGE ACROSS i_b SOURCE)

$$i) -V + 10^3 i + 10^5 (i - i_b) = 0$$

$$ii) 10^5 (i_b - i) + V_b = 0$$
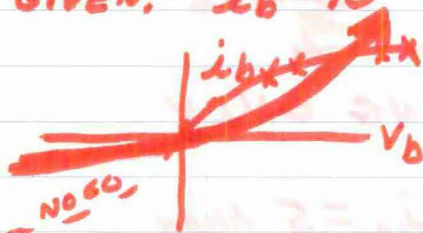
$$\text{GIVEN: } i_b = 10^{-4} V_b^{3/2}$$



MESH CURRENT IS HYPOTHETICAL
DEFINE VOLTAGE ACROSS
CURRENT SOURCES
USE KIRCHHOFF'S V LAW
EQUATIONS = # MESHES


NON-LINEAR ELEMENTS
KIRCHHOFF'S LAW STILL
APPLY.

LOAD LINE - GRAPHICAL
SOLUTION OF NON-LINEAR
DEVICE




SUPERPOSITION CAN ONLY BE
USED ON LINEAR SYSTEM

REPLACE V.S. WITH SHRT. CIRCUIT

" i.S " OPEN "

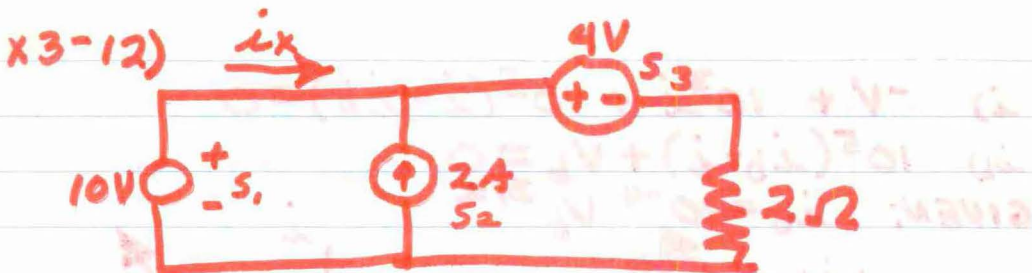

① ASSUME s_1 OPERATING ONLY

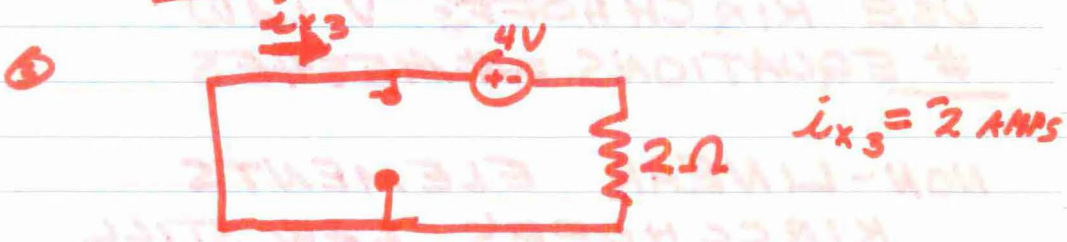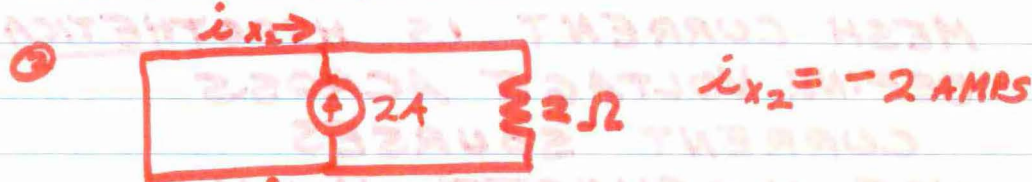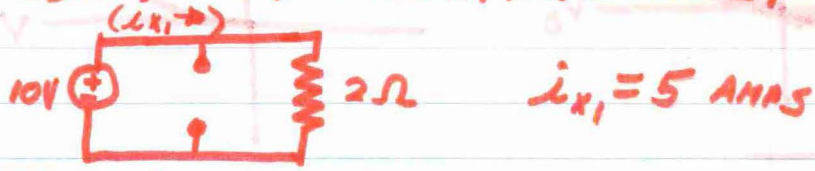


TOTAL

$$i_x = i_{x1} + i_{x2} + i_{x3} = 1 \text{ AMP}$$

1-30-70

SPECIAL PROBLEM # 2

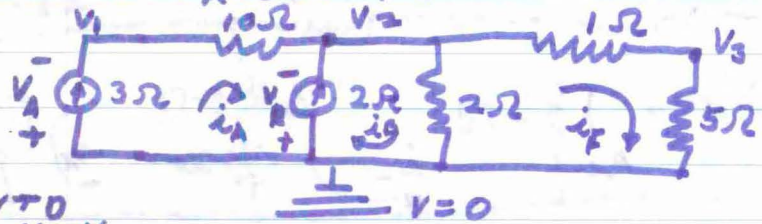

by NTD

$$1) \frac{V_1 - V_2}{10} - 3 = 0$$

$$2) \frac{V_2 - V_1}{10} - 2 + \frac{V_2 - V_3}{1} + \frac{V_2}{2} = 0$$

$$3) \frac{V_3 - V_2}{1} + \frac{V_3}{5} = 0$$

$$GR) 3 + 2 - \frac{V_2}{2} - \frac{V_3}{5} = 0$$

by MESH

$$A) V_A + 10i_a - V_B = 0$$

$$B) 2(i_b - i_f) + V_B = 0$$

$$F) 2(i_f - i_b) + 6i_f = 0$$

$$i_a = 3$$

$$i_b - i_a = 2 \Rightarrow i_b = 5$$

$$V_1 = -V_A$$

$$V_A = V_0 - V_1$$


$$V_2 - V_0 = -V_B = V_1 - 30 = 2(i_b - i_f)$$

$$V_3 - V_0 = 5i_f$$

$$V_3 - V_1 = -10i_a - i_f \quad 1$$

FOR FINDING V BETWEEN 2 PTS.
IN CIRCUIT, EXTEND OPEN CIRCUIT
& SUM UP VOLTAGES AROUND LOOP

SPECIAL PROBLEM # 4 HELPFUL HINTS?

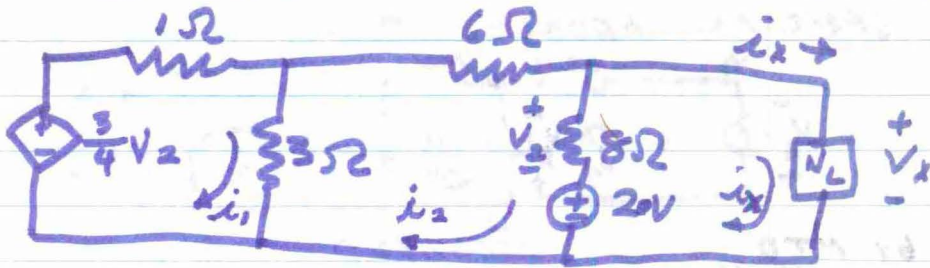

$$-\frac{3}{4}V_2 + i_1 + 3(i_1 - i_2)$$


$$3(i_2 - i_1) + 6i_2 + 8(i_2 - i_x) + 20 = 0$$

$$-20 + 8(i_x - i_2) + V_x = 0$$


$$V_2 = 8(i_2 - i_x)$$

FIFTH RELATION IS GRAPH.

REDUCE ABOVE TO $i_x = f(V_x)$

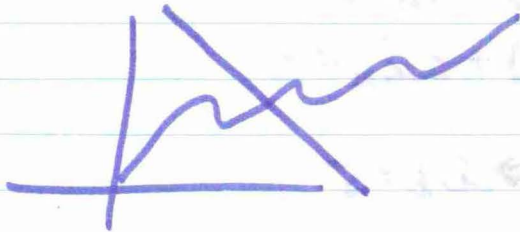


2-2-70
4-4)

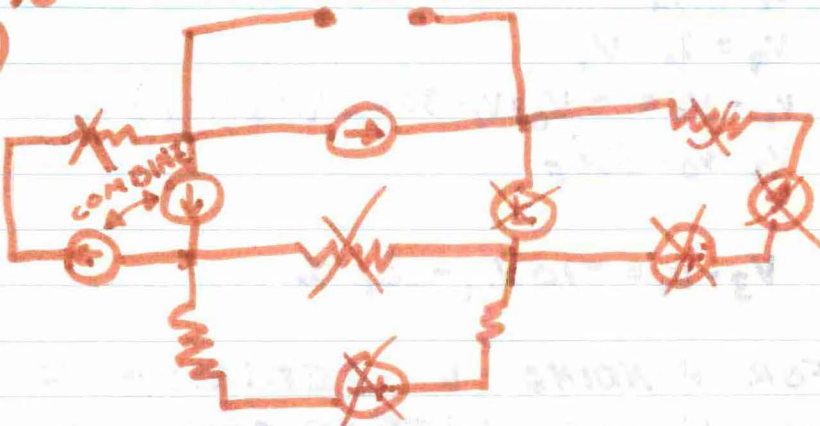

$$i = 0$$

2-6-70



4-9)

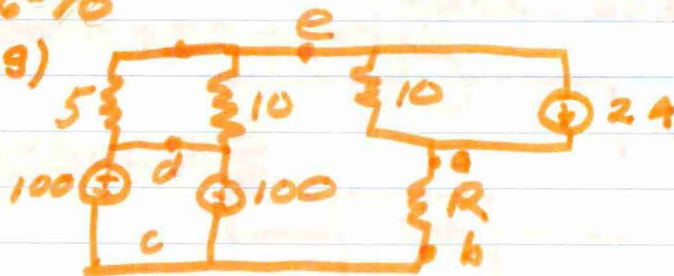

SIMPLIFY:

MAX POWER WHEN $R = R_{eq}$

EQUIVALENT CIRCUIT:

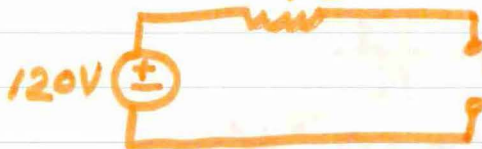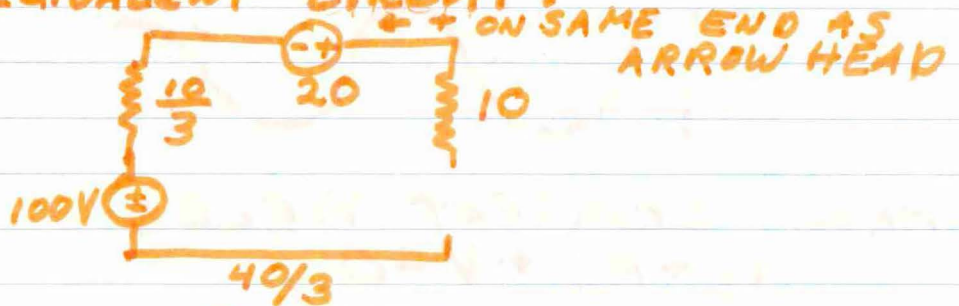

PUT IN R IN CIRCUIT:

$$R = 13\frac{1}{3} \Omega$$

$$P = i^2 R = \left(\frac{-120}{R + 40/3} \right)^2 R$$



$$\frac{dP}{dR} = 0 \Rightarrow R = 13.33$$

NON-LINEAR JUNK:

3-96)

$$v_s(t) = -3 + 2 \cos 22\pi t$$

$i(t) \uparrow$

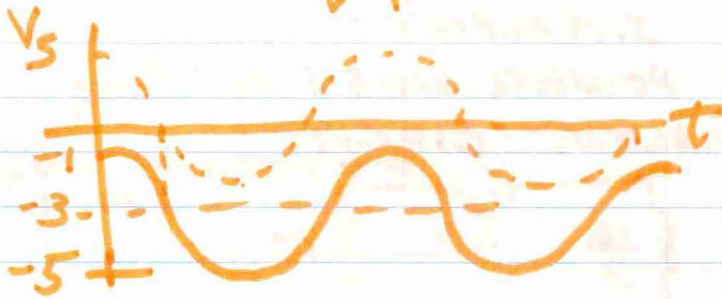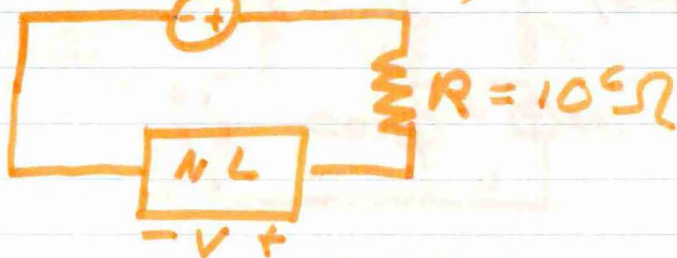

MESH CURRENT YIELDS

$$-V_s + Ri + V = 0$$

$$\Rightarrow i = -\frac{1}{R}V + \frac{V_s}{R}$$

$$= -10^{-6}V + 10^{-6}V_s$$

$$\text{LET } V_s = -1 \Rightarrow i = -10^{-6}V - 10^{-6}$$


$$i \approx -0.8 \mu\text{A}$$

$$\text{LET } V_s = 5$$

$$\Rightarrow i = 10^{-6}V + 10^{-6}$$


$$i \approx 4.2 \mu\text{A}$$



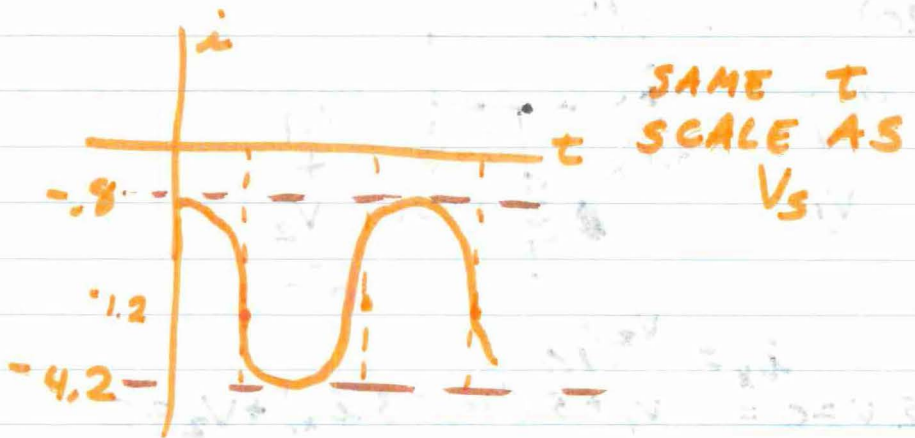

2-9-70

TWO TERMINAL:

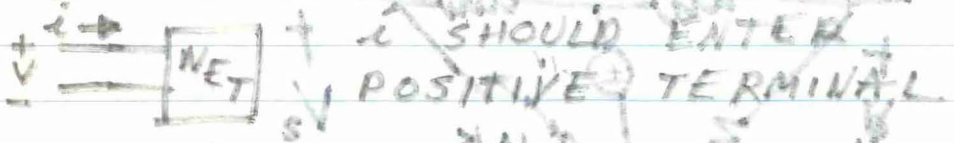

$$i = \frac{1}{R_{eq}} v + I_{eq}$$

$$v = R_{eq} i + V_{eq}$$

THREE TERMINAL:


TFORM

$$\begin{cases} v_1 = A i_1 + B i_2 + C \\ v_2 = D i_1 + E i_2 + F \end{cases}$$

TFORM


$$\begin{cases} i_1 = G v_1 + H v_2 + J \\ i_2 = K v_1 + L v_2 + M \end{cases}$$

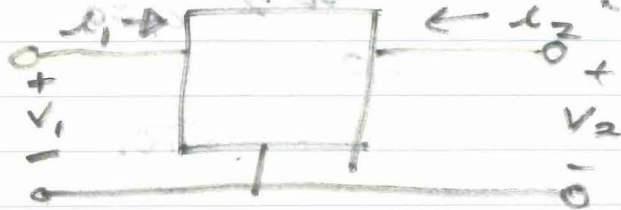CAPITOLS HAVE UNITS OF CONDUCTANCE ($= 1/\Omega$)



MUST SOLVE FOR 6 PARAMETERS

4-20)

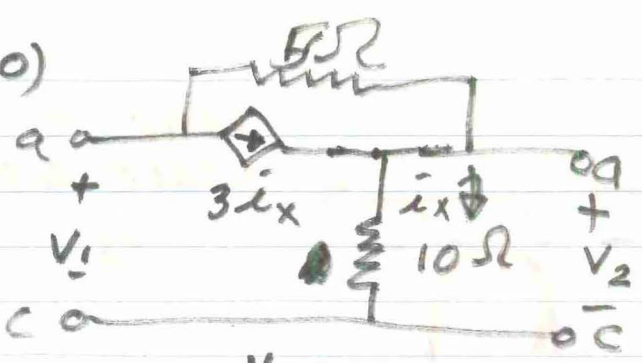


$$i_x = V_2 / 10$$

$$\sum V = 0 = -V_1 + 5(-i_x - 3i_x) + V_2 = 0$$

ETC.

4-21-a)

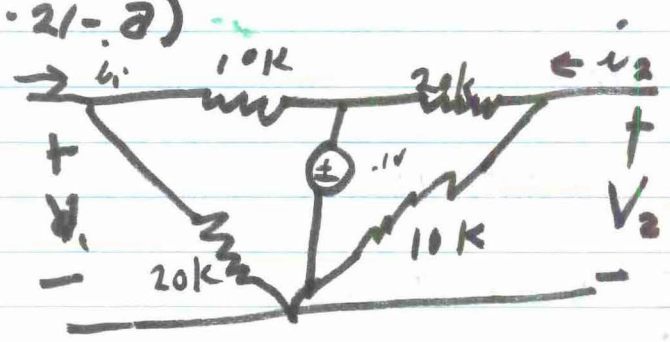

$$C = V_1$$

$$i_1 = i_2 = 0$$


$$= (2/3)(.1) V$$

$$A = \frac{V}{V_1} \quad i_2 = 0, \quad s = 0$$

$$= \frac{(10k)(20k)}{(10 + 20)k}$$


$$D = \frac{V}{V_2} \quad s_1 = 0, \quad c_1 = 0$$

$$= 0$$

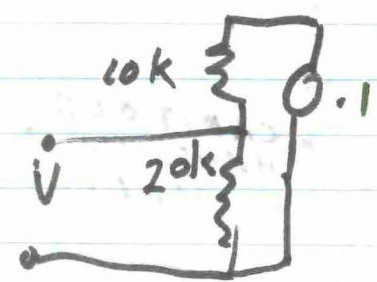

ETC.

2-11-70

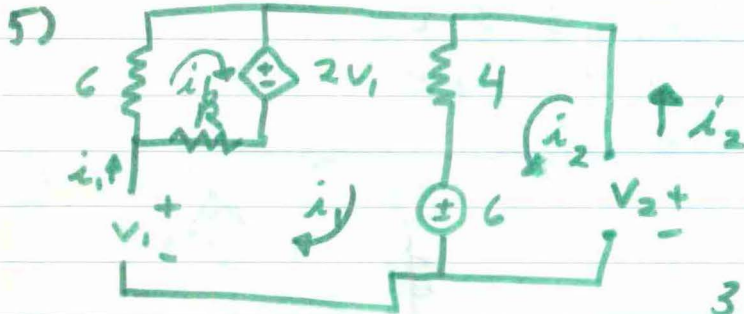

$$3V_1 = V_2$$

WITH $R \neq 0$

WHEN $R = 0$

$$B) \quad C i_b + 2V_1 + R(i_b - i_1) = 0$$

$$1) \quad -V_1 + R(i_1 - i_b) - 2V_1 + 4(i_1 + i_2) + C = 0$$

$$2) \quad -V_2 + 4(i_2 + i_1) + C = 0$$

SOLVE FOR i_1 AND i_2 IN TERMS OF V_1 & V_2

$$i_b = \frac{1}{C+R} (-2V_1 + R i_1)$$

$$0 = -3V_1 + i_1(4+R) + 4i_2 + C - R \left[\frac{1}{C+R} (R i_1 - 2V_1) \right]$$

$$V_1 \left[-3 + \frac{2R}{C+R} \right] + i_1 \left[4+R \right] \frac{R}{C+R} + i_2(4+C) = 0$$

$$i_2 = \frac{V_1}{4} - i_1 - 1.5$$


$$i_1 \left[\frac{CR}{C+R} \right] = V_1 \left[\frac{R+18}{C+R} \right] + V_2 = 0$$

$$\rightarrow i_1 = V_1 \left[\frac{R+18}{CR} \right] + V_2 \left[\frac{C-R}{CR} \right]$$

$$\rightarrow i_2 = V_1 \left[\frac{R+18}{CR} \right] + V_2 \left[\frac{1}{4} + \frac{C+R}{CR} \right] - \frac{3}{2}$$

BY INSPECTION ($R=0$),

IT EQUIVALENT IS

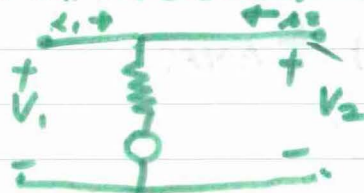


$$V_2 = 3V_1$$

USING T EQ. YIELDS: ($R=0$)


$$V_1 = \frac{4}{3}i_1 + \frac{4}{3}i_2 + 2$$

$$V_2 = 4i_1 + 4i_2 + 6$$

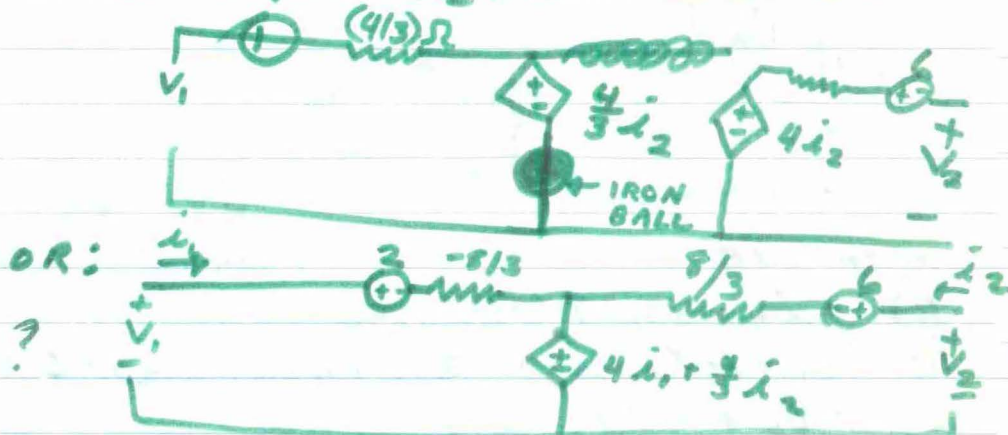

2-13-70

SP, #6)

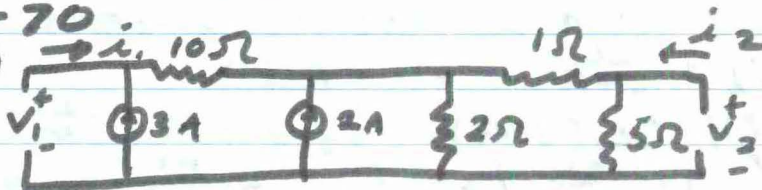

$$V_1 = A i_1 + B i_2 + C$$

$$V_2 = D i_1 + E i_2 + F$$

SOLVING TERM BY TERM

$$C = V_1 | i_1 = i_2 = 0$$

$$= 3(10) + 5 \left(\frac{(2 \times 6)}{2+6} \right)$$

$$= 3(10) + \frac{3}{4} \cdot \frac{2}{3} (5) \quad \text{BY DIVIDING UP CURRENTS}$$

$$= 37 \frac{1}{2}$$

$$F = V_2 | i_1 = i_2 = 0$$

$$= (5 \Omega) \frac{5}{4} \text{ AMPS}$$

$$= 6.25$$

$$A = \frac{V_1}{i_1} \Big|_{\substack{c=0 \\ i_2=0}} \quad (c=0 \text{ WHEN ALL SOURCES ARE IDLE})$$

OPEN CIRCUIT (O.C.) FOR i_2

$$A = \left(\frac{2 \cdot 6}{2+6} \right) + 10 = 11.5$$

$$E = \frac{V_2}{i_2} \Big|_{\substack{i_1=0 \\ F=0}}$$

$$\begin{aligned} &= \frac{5 \left(1 + \frac{2 \cdot 10}{2+10} \right)}{5 + \left(1 + \frac{2 \cdot 10}{2+10} \right)} \\ &= \frac{40}{25} (?) = 1.74 \end{aligned}$$

$$E = \frac{(3)(5)}{8} = 1.875$$

$$B = \frac{V_1}{i_2} \Big|_{\substack{i_1=0 \\ c=0}}$$

ASSUME $i_2 = 1$

$$B = \frac{\left(\frac{5}{8} \right) (2)}{1} = 1.25 \Omega$$


$$D = \frac{V_2}{i_1} \Big|_{\substack{i_2=0 \\ F=0}}$$

let $i_2 = 8$

$$= \frac{8 \left(\frac{2}{8} \right) 5}{8} = 1.25 \Omega$$


IFF $\frac{V_1}{i_2} = \frac{V_2}{i_1}$, CIRCUIT DISPLAYS RECIPROCALITY

BACK TO 2 TERMINAL:

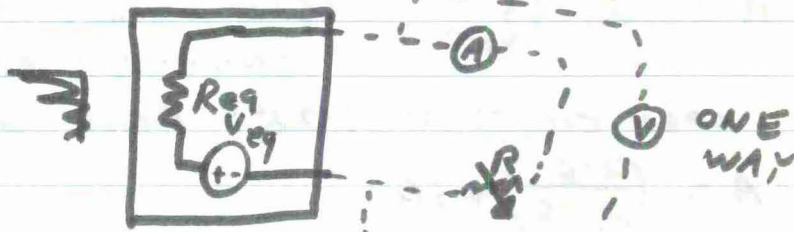


BLACK BOX

①

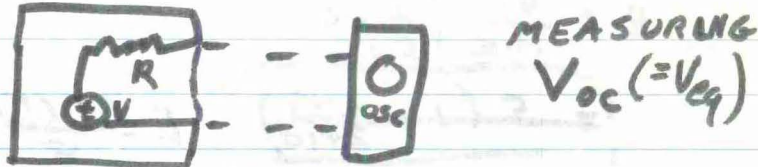

②

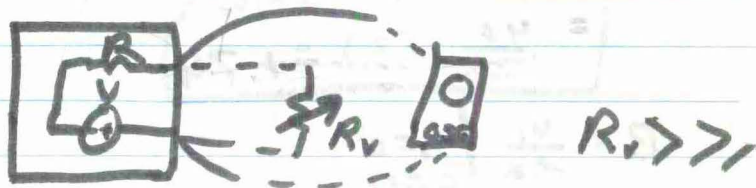

- ③ REDUCE R_{EXT}
IF $V = V_{oc}/2$
THEN $R_{eq} = R_v$

2-12-70 LAB


PULSE GENERATOR

PRE
○
↑
PULSE REPETITION FREQ.

PULSE DURATION
○

RANGE OF P.D
○
AMPLITUDE (V)
○

○
FOR IN BETWEEN VALUES OF PRF

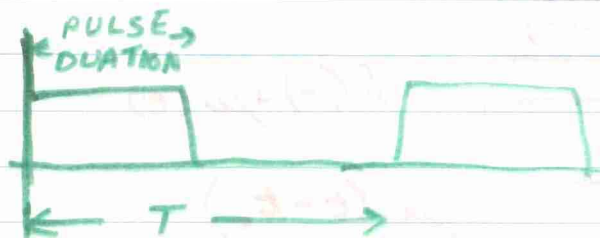

$$\frac{1}{T} = \text{P.R.F.}$$

$$\text{P.D.} < T$$

2-16-70

ENERGY STORAGE THINGS
(ALL TIME DEPENDENT)


CAPACITOR - STORES EL. ENERGY
BY WAY OF
AN ELECTRIC FIELD

CAPACITANCE FUNCTION OF E

$$i = \frac{d(CV)}{dt} = C \frac{dv}{dt} + V \frac{dC}{dt}$$

$$V_c(t) = \frac{1}{C} \int_0^t i_c(x) dt + K$$

$K = V$ AT TIME = 0

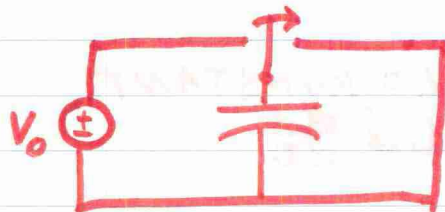

CAPAC. WILL DISCHARGE SPARKWISE

- 1) CAPAC. ACTS LIKE OPEN CIRCUIT IN D.C.
- 2) WILL NOT LET VOLTAGE ACROSS ITSELF CHANGE ABRUPTLY


STEP FUNCTION


$$f(t) = u(t)$$


$$u(t - t_0)$$

$$\mathcal{L}\{u(t)\} = \frac{1}{s}$$

IMPULSE

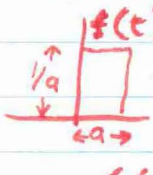
$$\text{IMPULSE} = \int_0^{\infty} \infty \cdot 0 = 1$$

$$\lim_{a \rightarrow 0} f(t) = \delta(t)$$

$$\mathcal{L}\{\delta(t)\} = 1$$

MAGNETISM


$$V = \frac{d(N\Phi)}{dt} = \frac{d(Li)}{dt}$$

INDUC

$$P = \frac{L di}{dt} \quad \text{FOR } L = \text{KONSTANT}$$
$$P = \frac{dL}{dx} i \quad P = L i \frac{di}{dt}$$

2-18-70

EXAM # 2, PROB # 3

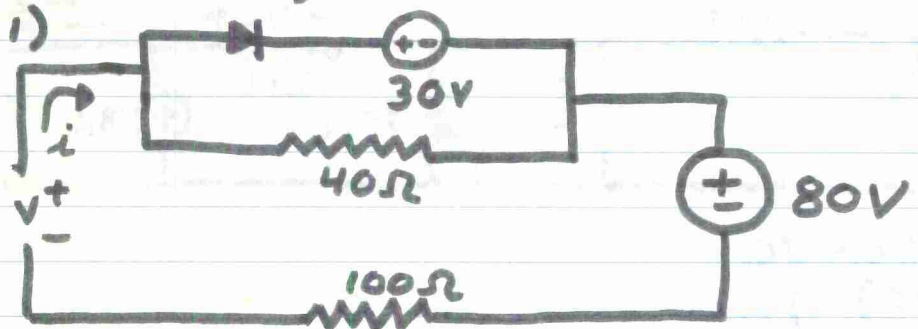

a) CONDUCTS:


$$-V + 30 + 30 + 100i = 0$$

$$i = \frac{1}{100} V - 1.1$$

b) DOESN'T CONDUCT:

$$-V + 140i + 80 + 100i = 0$$

$$i = \frac{1}{240} V - \frac{1}{3}$$

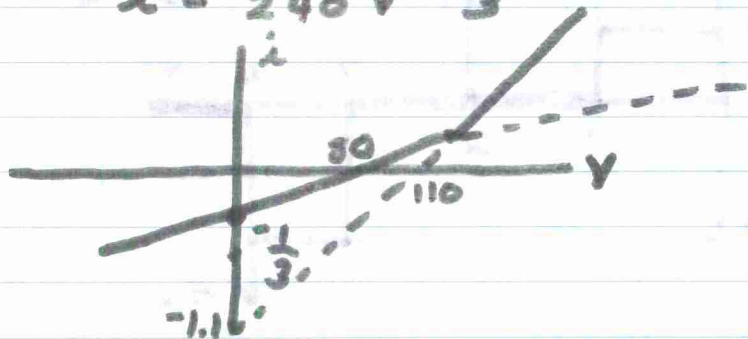

2) REVERSING POLARITY ON 30V SOURCE

a) NON CONDUCTS (SAME AS 1b)


b) CONDUCTS: $i = \frac{V}{100} - \frac{1}{2}$

3) REVERSE POLARITY ON 80V SOURCE

a) CONDUCTS - $i = \frac{V}{120} + \frac{1}{3}$


b) NON-CONDUCTS - $i = \frac{V}{100} + \frac{1}{2}$

EXAM #2, PROB #3
 MAY REDRAW CIRCUIT:

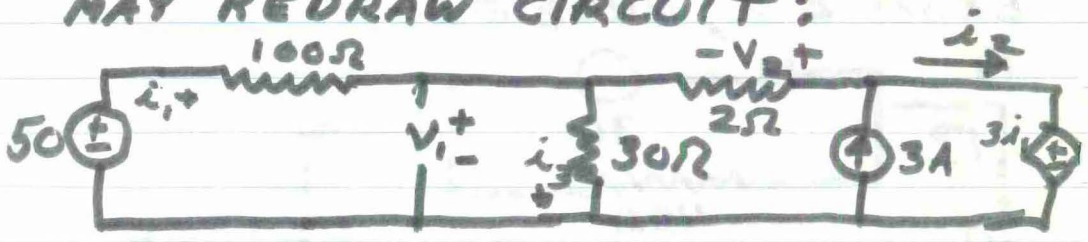


2-20-70

6-12)

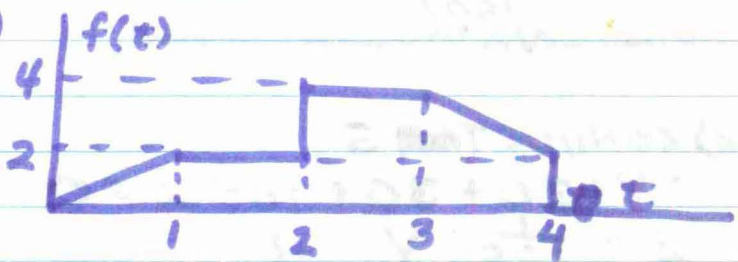

a) $i = C \frac{df}{dt}$

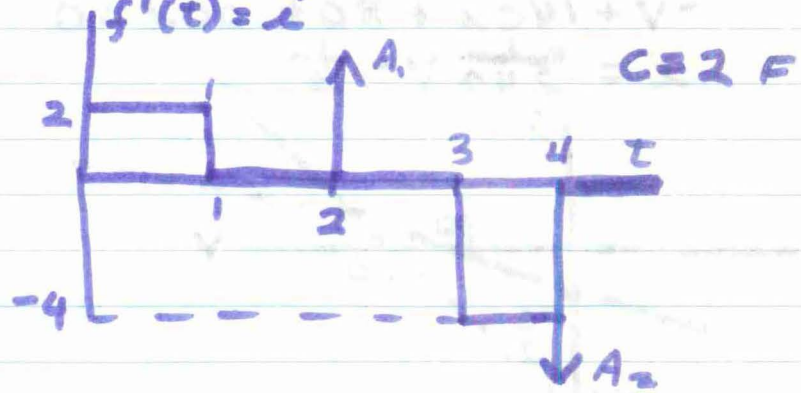

MUST FIND MAGNETUDE
 OF IMPULSE THINGIES



$$v = \frac{1}{c} \int i dt + k$$

SO CHECK BACKWARDS
 TO $f(t)$

$\therefore A_1 = 4$, FOR $f(t)$ JUMPS TO FOUR. $A_2 = -4$


• $i = C \frac{dv}{dt}$
 $v = \frac{1}{C} \int i dt + K$

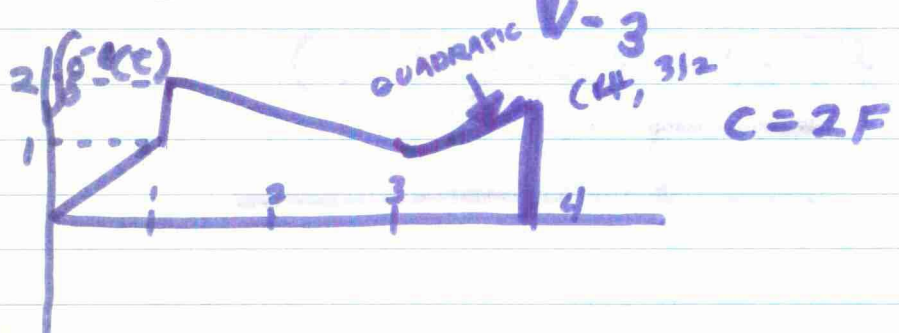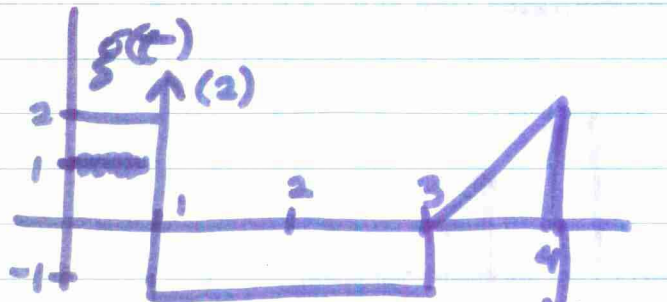$v = L \frac{di}{dt}$
 $i = \frac{1}{L} \int v dt + K$




ON BOTH GRAPHS, MULTIPLYING FUNCTION SCALE BY TWO YIELDS ANSWERS TO INDUCTOR PARTS OF THIS NEAT PROBLEM.

$$6-5) f(t) = 3u(t-1)$$

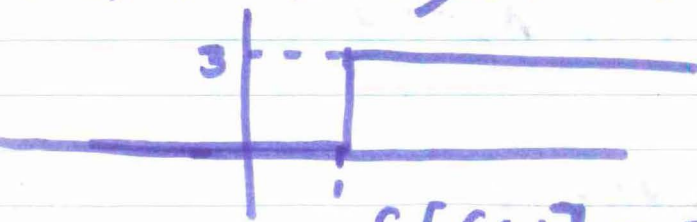


$$\mathcal{L}[f(t)] = \frac{3e^{-s}}{s}$$


$$b) \int_{-\infty}^t f(t) dt$$

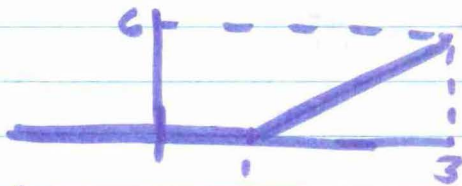

$$c) \frac{d}{dt} f(t)$$

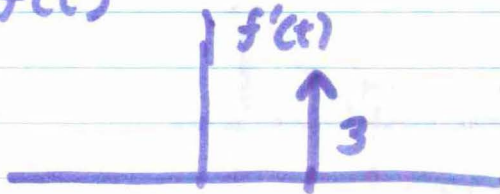

$$d) f(-t) = 3u(-t-1)$$

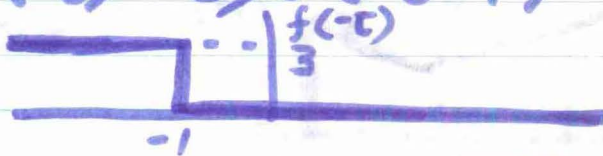

2-20-20

$$d^n y = (0)^n y \Rightarrow y^{(n)} = 0$$

$$d^n y = (0)^n y \Rightarrow y^{(n)} = 0$$

$$d^n y = (0)^n y \Rightarrow y^{(n)} = 0$$

COEFFICIENTS $F(x)$

$$0 = y'' + y' - 2y = (x^2 + 1)y' - 2xy + 2y = 0$$

BACK TO $y'' - y' = 0$

$$dy = (0)^n y \Rightarrow y^{(n)} = 0$$

$$dy = (0)^n y \Rightarrow y^{(n)} = 0$$

$$dy = (0)^n y \Rightarrow y^{(n)} = 0$$

LOOKS A BIT OF A LOT LIKE A TAYLOR SERIES:

$$f(x) = f(0) + x f'(0) + \frac{x^2}{2!} f''(0) + \dots + \frac{x^n}{n!} f^{(n)}(0) + \dots$$

$$f(x) = a + b(x) + \frac{1}{2} x^2 + \frac{1}{6} x^3 + \dots$$

$$\left(\dots + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots \right) d = \dots + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots$$

$$x^2 \text{ term } 2x + \frac{1}{2} x^2 \text{ term } d =$$

$$d + 2d = 2d = 2d = 2d$$

$$(2d - d) = d = 2d$$

$$\frac{d + 2d}{1 - 2d} = 2d$$

$$x^2 \text{ term } \frac{1}{2} + x^2 \text{ term } d = y$$

2-20-70

$$y'' - 4y = 0 \quad y(0) = a \quad y'(0) = b$$

• COEFFICIENTS $F(x)$

$$\text{EX) } (x^2 + 1)y' - 2xy' + 2y = 0$$

→ BACK TO $y'' - 4y = 0$

$$\Rightarrow y'' = 4y \Rightarrow y''(0) = 4a$$

$$y''' = 4y' \Rightarrow y'''(0) = 4b$$

$$y^{(4)} = 4y'' \Rightarrow y^{(4)}(0) = 4^2 a$$

⋮

⋮

⋮

LOOKS A HELL OF A LOT LIKE

A TAYLOR SERIES:

$$f(x) = f(0) + xf'(0) + \frac{x^2}{2}f''(0) + \dots + \frac{x^n}{n!}f^{(n)}(0)$$

$$y(x) = a + b(x) + \frac{1}{2}x^2 4a + \frac{1}{6}x^3 + \frac{1}{24}x^4 16a + \frac{1}{120}x^5 16b + \dots$$

$$= a \left(1 + \frac{4x^2}{2} + \frac{16x^4}{4!} + \dots \right) + b \left(x + \frac{4x^3}{3!} + \frac{16x^5}{5!} + \dots \right)$$

$$= a \cosh 2x + \frac{1}{2}b \sinh 2x$$

BY \mathcal{L}

$$s^2 \bar{y} - as - b - 4\bar{y} = 0$$

$$(s^2 - 4)\bar{y} = as + b$$

$$\bar{y} = \frac{as + b}{s^2 - 4}$$

$$y = a \cosh 2x + \frac{1}{2}b \sinh 2x$$

$$y'' - 4y = 0$$

$$y = a_0 + a_1x + a_2x^2 + a_3x^3 + \dots + a_kx^k + \dots$$

$$= \sum_{n=0}^{\infty} a_n x^n$$

$$y' = a_1 + 2a_2x + 3a_3x^2 + \dots + k a_k x^{k-1}$$

$$= \sum_{n=1}^{\infty} n a_n x^{n-1} = \sum_{n=0}^{\infty} n a_n x^{n-1}$$

$$y'' = \sum_{n=0,1,2}^{\infty} n(n-1) a_n x^{n-2}$$

$$\text{TAKE } (x^2+1)y'' - 2xy' + 2y = 0$$

$$(x^2+1)(2a_2 + 6a_3x + 12a_4x^2) - 2x(a_1 + 2a_2x + 3a_3x^2 + 4a_4x^3) + 2(a_0 + a_1x + a_2x^2 + a_3x^3 + a_4x^4) = 0$$

$$(2a_2 + 2a_0) + (6a_3 + 2a_1) x + (12a_4 + 2a_2 - 4a_2 + 2a_2) x^2 + (\text{HOFFY DIDN'T DO IT}) = 0$$

$$\text{THEREFORE: } 2a_2 + 2a_0 = 0$$

$$6a_3 = 0$$

$$12a_4 = 0$$

IF CONTINUED, ALL $a_k = 0$

$$\therefore y = a_0 + a_1x + a_2x^2 + a_3x^3 + \dots$$

$$\text{EVERY TERM } (n < 3) = 0$$

FURTHERMORE, $a_2 = -a_2$

OR... $x_2 D^2 + x_1 D + a_0 = Y$

$$Y = a_0(1-x^2) + a_1 x$$

GOING BACK TO $Y, Y',$ ETC.

AS INFINITE SERIES;

$Y(0) = a_0$; $Y'(0) = a_1$


COEFFICIENTS MAY BE EXPRESSED
IN TERMS OF OTHER COEFFICIENTS,
AND MADE INTO FINITE FORMULA

A) THE GENERAL SOLUTION OF
 $PY'' + QY' + RY = 0$
OBTAINS TWO ARBITRARY
CONSTANTS; $Y = AY_1 + BY_2$
WHERE $X_0 \neq Y_0$ ARE BOTH
SOLUTIONS.


B) A PARTICULAR SOLUTION MAY
BE OBTAINED BY PRESCRIPTION
OF TWO CONDITIONS

e.g. $Y(0) = a$; $Y'(0) = b$
OR $Y(0) = a$; $Y'(2) = b$

2-23-70

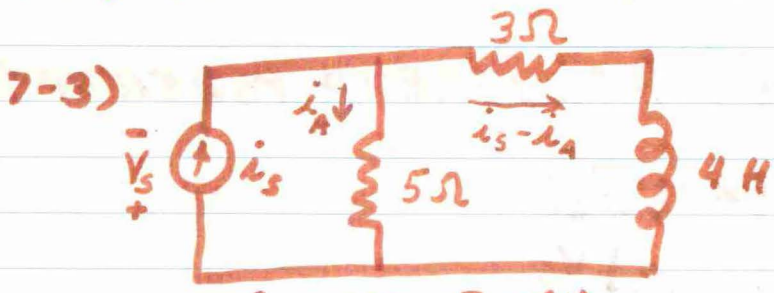


$$i_s = -8 + 3U(t)$$

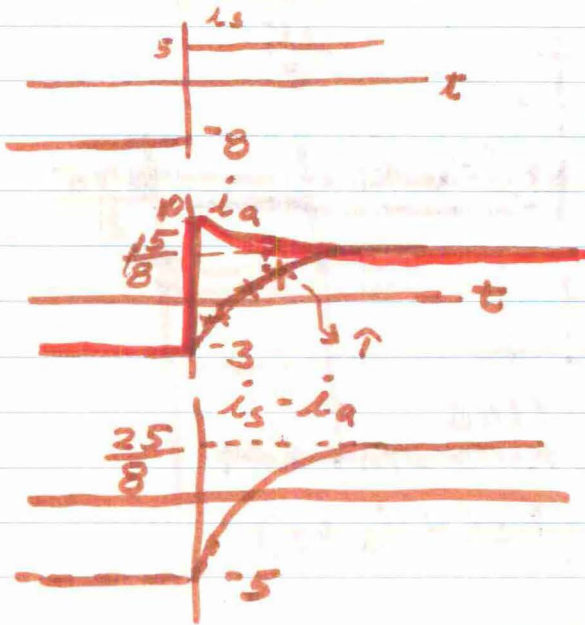

$\tau = \text{TIME CONSTANT} = \frac{L}{R} = \frac{4}{8} = \frac{1}{2}$
 (R IS REQ FROM INDUCTOR'S TERMINALS)


$$V_s = -5 i_A$$

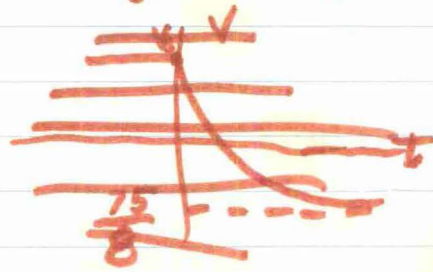


$$P_s = V_s i_s$$

(POWER DELIVERED = POWER OF SCE)


$$V_s (= -5 i_s)$$

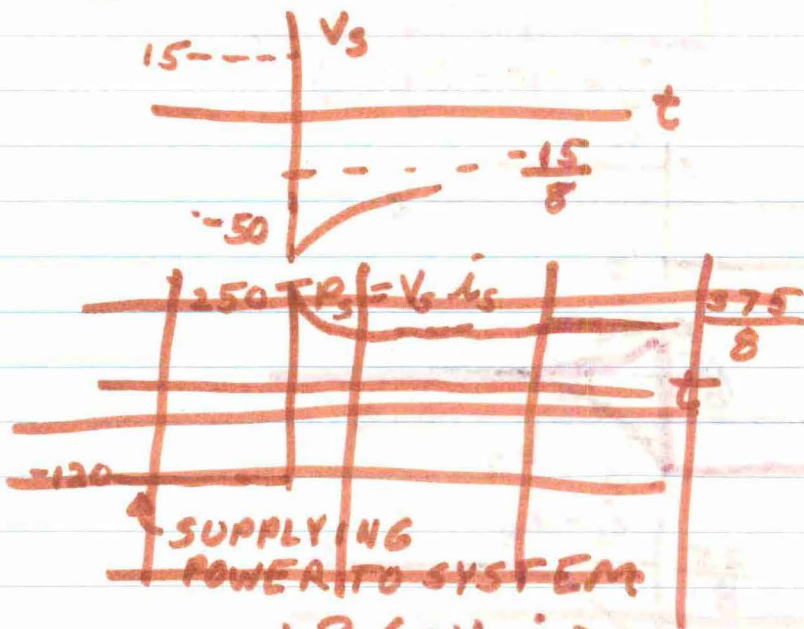

$$P_s (= V_s i_s)$$

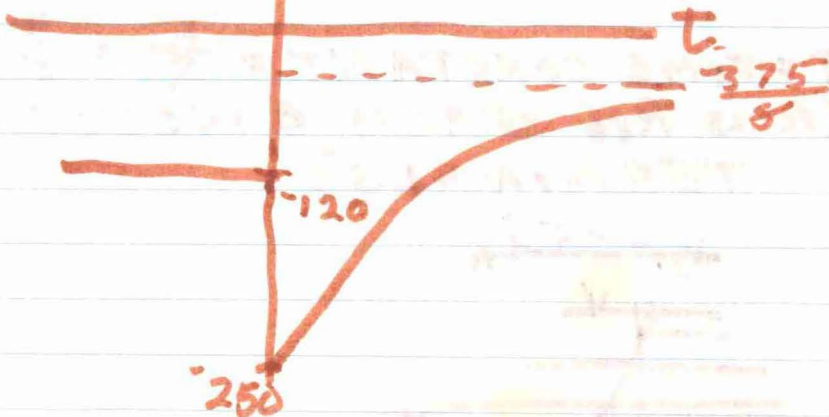


$\therefore P_{SYS}$

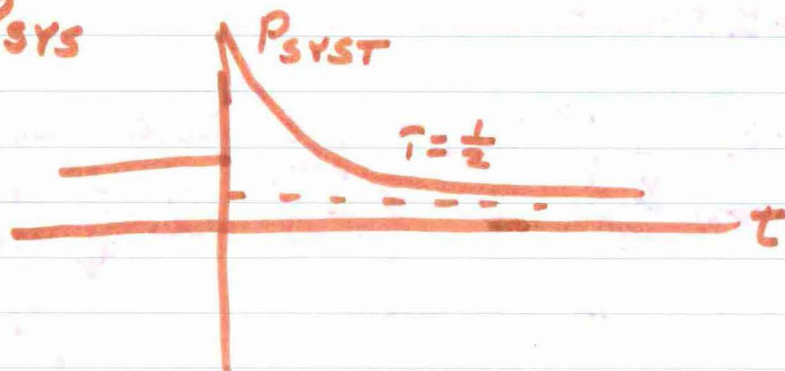

- 1) MUST HAVE $t=0^-$
- 2) $t=0^+$
- 3) $t=\infty$
- 4) $\tau = ?$

IN SYSTEM WITH ONE TIME INDEPENDENT ~~THE~~ THINGIE, THESE FOUR CONDITIONS DEFINE A CURVE.

7-3) BY ALGEBRA

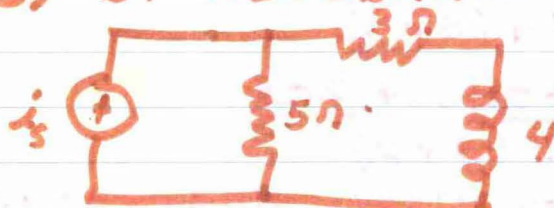

$$-5i_a + 5(i_s - i_a) + 4 \frac{d(i_s - i_a)}{dt} = 0$$


$$5(-I_A(s)) + 3[I_S(s) - I_A(s)] + 4s[I_S(s) - i(0^+) - I_A(s)] = 0$$

$$t > 0; i_s = 15 \Rightarrow I_S = \frac{15}{s}$$

$$I_A(s) \{-4s - 8\} = \frac{15}{s} - 20 + 20s$$

AT THIS POINT, MOORE BLEW IT, SO NOTES AT THIS POINT SHALL BE TERMINATED.

2-25-70

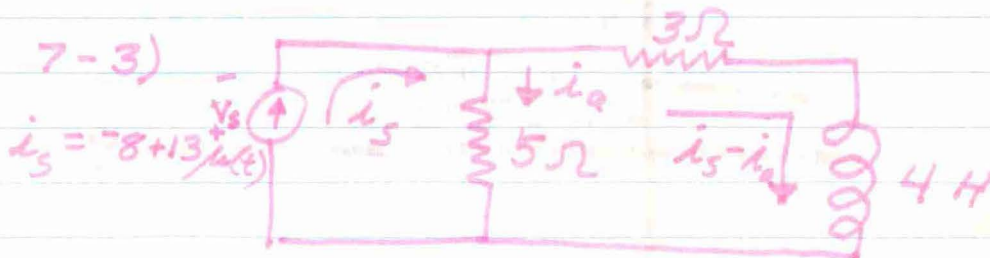

$$0 = 5(-i_a) + 3(i_s - i_a) + 4 \frac{d(i_s - i_a)}{dt}$$
$$-5I_A + 3I_S - 3I_A + 4[5I_S - 5]$$
$$-4[5I_A - 10] = 0$$

$$I_A(-8 - 45) + I_S(3 + 45) + 20 = 0$$

$$I_A = \frac{I_S[3 + 45] + 20}{45 + 8}$$

$$I_S = \frac{5}{s} \quad (\text{L OF STEP})$$


$$I_A = \frac{\frac{5}{s}[3 + 45] + 20}{45 + 8}$$

$$= \frac{15 + 20s + 20s}{45(s + 2)}$$


EXPAND BY PARTIAL FRACTIONS

$$\frac{15 + 40s}{45(s + 2)} = \frac{15}{85} + \frac{65}{8(s + 2)}$$
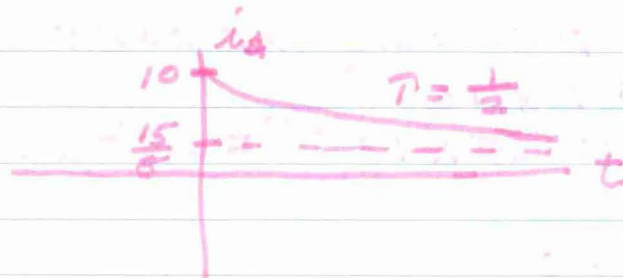
$$\therefore i_a = \frac{15}{8} + (e^{-2t}) \frac{65}{8}$$




$$P = i_s V_s = (5)(-5i_A) = -25i_A$$

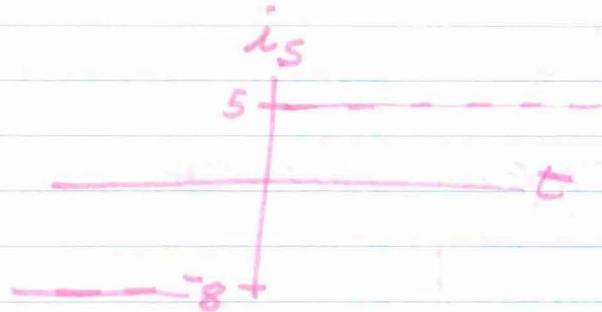


$$P(t) = -25 \left(\frac{15}{8} + \frac{65}{8} e^{-2t} \right)$$

7-17)

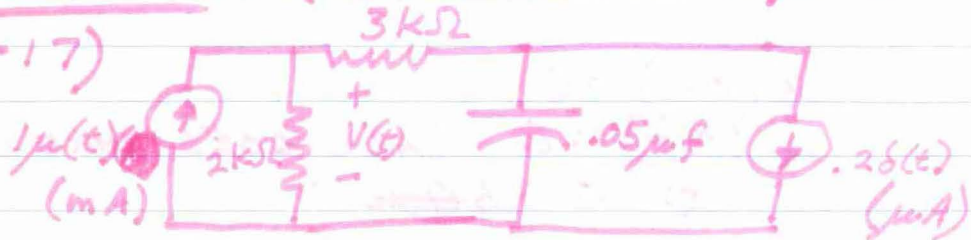

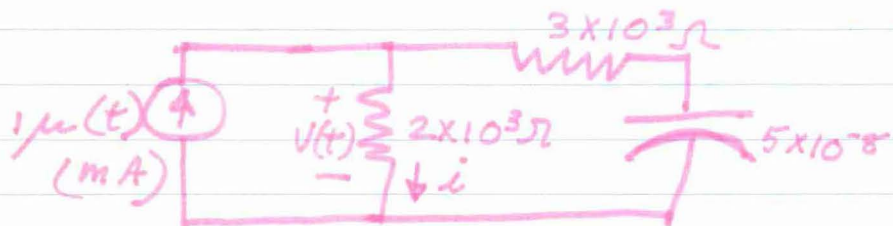MAY DO BY SUPERPOSITION:
CONSIDER LEFT SOURCE ONLY:



$$i(0^-) = 0$$

$$i(0^+) = 0.6 \times 10^{-3} \text{ CONT.} \rightarrow$$

$$= \left(\frac{3000}{5000} \right) (1 \times 10^{-3})$$

CAP. ON D.C. ACTS AS OPEN CIRCUIT

$$i(\infty) = 1 \times 10^{-3}$$

$$\tau = RC = 25 \times 10^{-5} = 250 \mu\text{SEC}$$


$$V(0-) = 0$$

$$V(0+) = 1.2$$

$$V(\infty) = 2$$

$$\tau = 250 \mu\text{SEC}$$

CONSIDER OTHER SOURCE

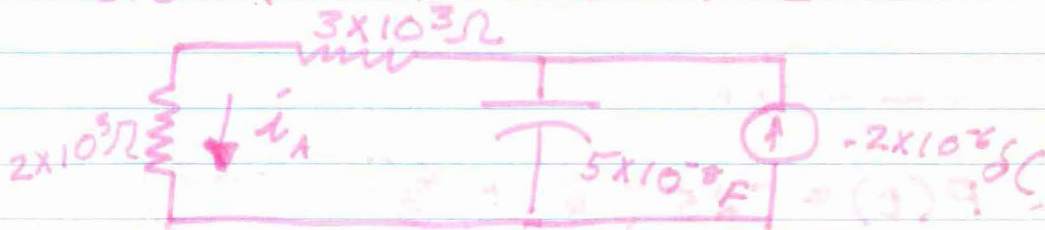


$$i(0-) = 0$$

$$i(0+) = 0 \text{ (ALL GOES THRU C)}$$

$$i(\infty) = 250 \mu\text{O}$$
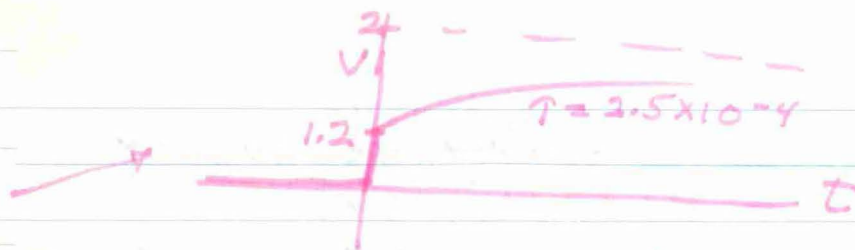
$$\tau = 250 \mu\text{SEC (CHARACTERISTIC OF SYSTEM)}$$




$$V(t) = \left[2 - .8 e^{-\frac{t}{250 \times 10^{-6}}} \right] U(t)$$

3-2-70

Pg. 252-3

X 7-8

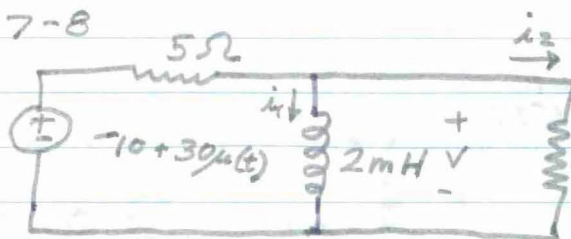

- 1) LAPLACE TRANSFORMS (MESH CURR.)
- 2) 4 NUGGETS OF KNOWLEDGE IF ONE TIME DEPEND.

4 NUGGETS OF KNOWLEDGE

1) $V(0^-)$

INDUCTOR ACTS AS SHORT CIRCUIT

$$\therefore V_1(0^-) = 0 \quad (i_1(0^-) = 2 \text{ AMPS})$$

2) $V(0^+)$

$$(i_1(0^+) = -2 \text{ AMPS})$$

summing \downarrow $20 + 5(i_1 + i_2) + 20i_2 = 0 \quad i_1 = -2$

$$\therefore i_2 = \frac{30}{25} = \frac{6}{5}$$

$$\Rightarrow V(0^+) = 20i_2 = 24 \text{ V}$$


3) $V(\infty) = 0$

(IND. ACTS AS SH. CIR.)

4) $\tau = \frac{1}{R} = \frac{2 \times 10^{-3}}{R}$

$$R \text{'S ARE IN } \parallel \Rightarrow R = 4$$

$$\tau = \frac{2 \times 10^{-3}}{4}$$

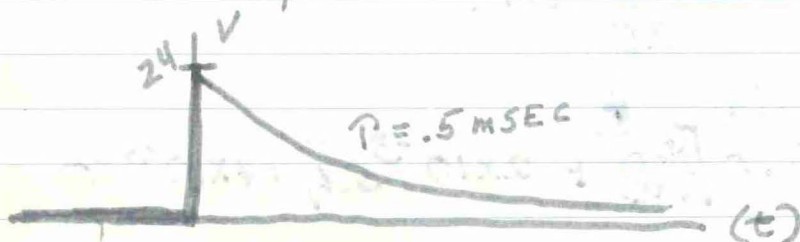


(CONT.)

AT 0^+ , I IS ^{SUPPLYING} CONSUMING ENERGY

$$P_I(0^+) = V(0^+) \cdot i_1(0^+) \\ = (24)(-2) = -48 \text{ WATTS}$$

MINUS SIGN IMPLIES THE INDUCTOR IS SUPPLYING ENERGY (OPPOSED TO $i^2R (>0)$ WHICH ALWAYS CONSUMES ENERGY)

USING LAPLACE

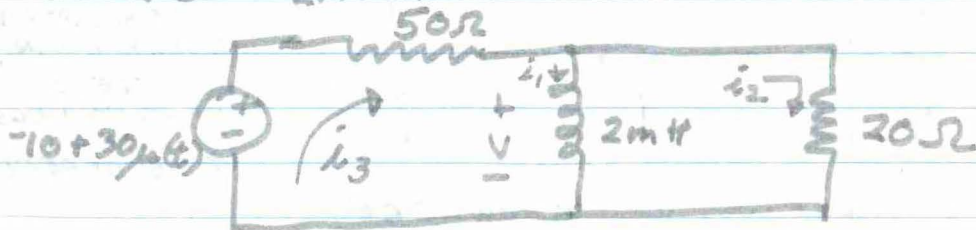

$t > 0$; MESH CURRENTS

$$\textcircled{1} -20\mu(t) + 5i_3 + 2 \times 10^{-3} \frac{di_1}{dt} = 0$$

$$\textcircled{2} -20\mu(t) + 5i_3 + 20(i_3 - i_1) = 0$$

$$\textcircled{3} V = 2 \times 10^{-3} \frac{di_1}{dt} = 20(i_3 - i_1)$$

$$1a) \frac{-20}{s} + 5\bar{i}_3 + 2 \times 10^{-3} [s\bar{i}_1 + 2] = 0$$

$$2a) \frac{-20}{s} + 5\bar{i}_3 + 20\bar{i}_3 - 20\bar{i}_1 = 0$$

$$3a) \bar{V} = 2 \times 10^{-3} (s\bar{i}_1 + 2) = 20\bar{i}_3 - 20\bar{i}_1$$

SOLVING:

$$(2a) \bar{i}_3 = \frac{\frac{20}{s} + 20\bar{i}_1}{25}$$

SUBING INTO (1a)

$$\frac{-20}{s} + 5 \left[\frac{\frac{20}{s} + 20\bar{i}_1}{25} \right] + 2 \times 10^{-3} s\bar{i}_1 + 4 \times 10^{-3} = 0$$

$$\bar{I}_1 [4 + 2 \times 10^{-3} s] = \frac{20}{s} - \frac{4}{s} - 4 \times 10^{-3}$$

$$\bar{I}_1 = \frac{\frac{16}{s} - 4 \times 10^{-3}}{(2 \times 10^{-3} s + 4)} = \frac{16 - 4 \times 10^{-3} s}{s(s + 2000)(2 \times 10^{-3})}$$

$$= \frac{16}{s} + \frac{\frac{16+8}{-4}}{s+2000}$$

$$\therefore \bar{I}_1 = \frac{4}{s} - 6 \frac{1}{s+2000}$$


$$\underline{i(t)} = [4 - 6e^{-2000t}] \mu(t)$$

$$\bar{V} = 2 \times 10^{-3} [sI_1 + 2]$$


$$= 2 \times 10^{-3} \left[2 \frac{16 - 4 \times 10^{-3} s}{(s+2000)(2 \times 10^{-3})} + 2 \right]$$

$$= \frac{16 - 4 \times 10^{-3} s + 4 \times 10^{-3} s + 8}{s+2000}$$
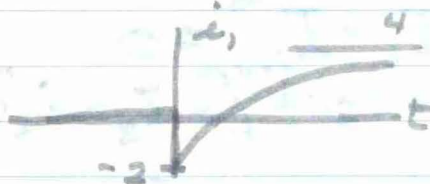
$$= \frac{24}{s+2000} \Rightarrow v(t) = 24 e^{-2000t} \mu(t)$$



3-5-70

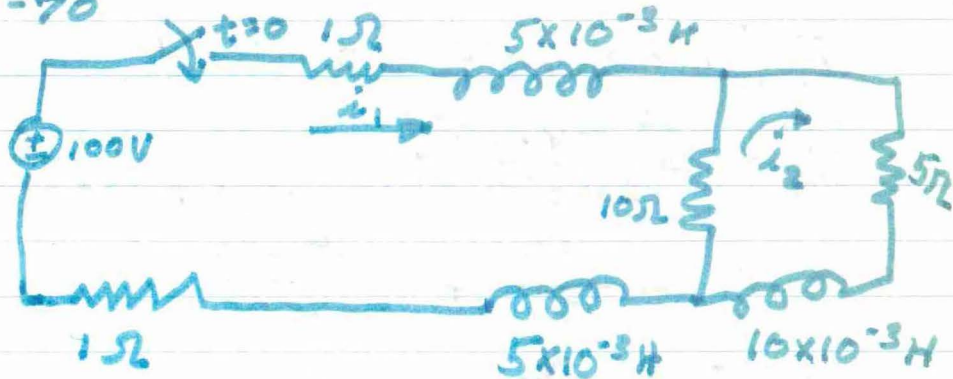

FIND $i_2(t)$

$t > 0$

$$\textcircled{1} -100 + i_1 + 5 \times 10^{-3} \frac{di_1}{dt} + 10i_1 - 10i_2 + 5 \times 10^{-3} \frac{di_1}{dt} + i_1 = 0$$

$$\textcircled{2} 10i_2 - 10i_1 + 5i_2 + 10^{-2} \frac{di_2}{dt} = 0$$

$$\textcircled{1} \frac{-100}{s} + 2I_1 + 10^{-2} [sI_1 - i_1(0^+)]$$

$$+ 10[I_1 - I_2] = 0$$

$$\textcircled{2} 10I_2 - 10I_1 + 5I_2 + 10^{-2} [sI_2 - i_2(0^+)] = 0$$

SOLVING FOR I_2

$$\textcircled{1} I_1(2 + 10^{-2}s + 10) = \frac{100}{s} + 10I_2$$

$$I_1 = \frac{\frac{100}{s} + 10I_2}{10^{-2}s + 12} = \frac{10^4 + 10^3 s I_2}{s(s + 1200)}$$

SUBSTITUTE INTO 2

$$I_2(15 + 10^{-2}s) - 10 \left\{ \frac{10^4 + 10^3 s I_2}{s(s + 1200)} \right\}$$


$$I_2 \left\{ 15 + 10^{-2}s - \frac{10^4 s}{s(s+1200)} \right\} = \frac{10^5}{s+1200}$$

$$I_2 = \frac{10^5}{s(s+1200)(15+10^{-2}s)} - \frac{10^4 s}{10^5}$$

$$= \frac{5 \{ 10^{-2}s^2 + 275s + 8000 \}}{10^5}$$

$$= \frac{12.5}{s} + \frac{2.09}{s+2360} + \frac{-14.59}{s+339}$$
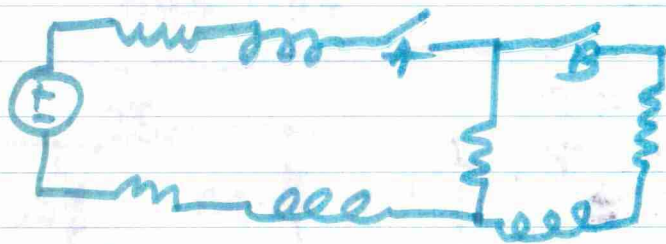
$$i_2(t) = (12.5 + 2.09e^{-2360t} - 14.59e^{-339t})$$



A CLOSED
B OPEN


$$\tau_1 = \frac{1}{1200}$$

A OPEN

B CLOSED $\tau_2 = \frac{1}{1500}$


∴ UNRELATED TO INITIAL PROBLEM

FOR CIRCUIT WITH 1 E.S.C

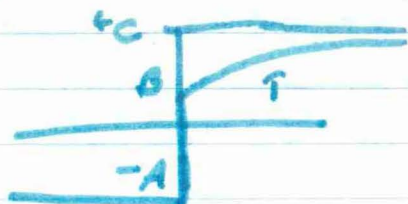

$$Y(t) = -A e^{-t/\tau} + \left\{ (C-B) [1 - e^{-t/\tau}] + B \right\} u(t)$$

3-7-70

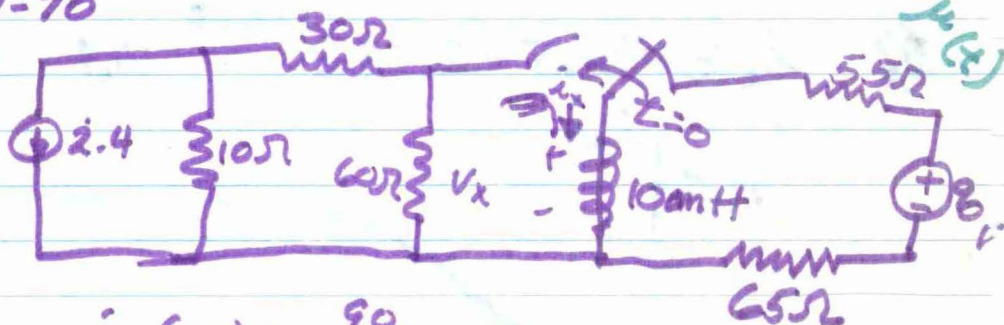

$$i_x(0^-) = \frac{90}{55+65} = .75 \text{ A}$$

$$i_x(0^+) = -.75 \text{ A}$$

$$i_x(\infty) = \left(\frac{10}{10+30} \right) \cdot 2.4 = -.6 \text{ A}$$


$$\tau = \frac{1}{s} = \frac{10 \times 10^{-3}}{24} = \frac{1}{240}$$



1) $V_x(0^-) = 0$

2) $V_x(0^+) = 0$
 $V_x(0^+) = -32.5 \text{ V}$

3) $V_x(\infty) = 0$

4) τ

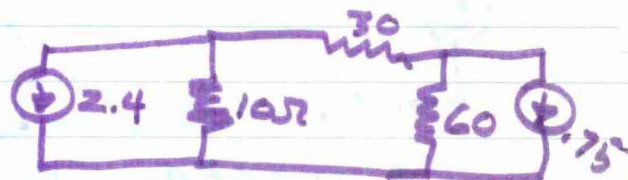

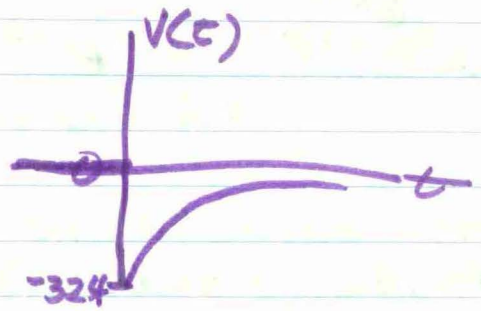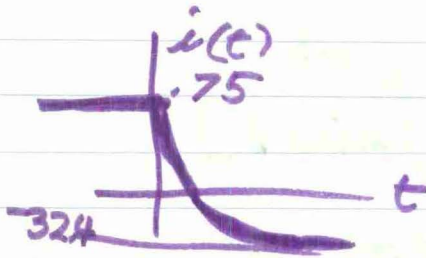

3-15-70

CH 7



CH 8



DIFFERS IN AMPLI.
 & PHASE \angle

INPUT:

$$A_1 \cos(\omega t + \phi_1) ; A_2 \cos(\omega t + \phi_2)$$

$\cos \omega t$ APPEARS


IN BOTH EXPRESSIONS.

REDUCED TO

POLAR: $A_1 \angle \phi_1$

PHASOR: $A_2 \angle \phi_2$

RECTANGULAR:

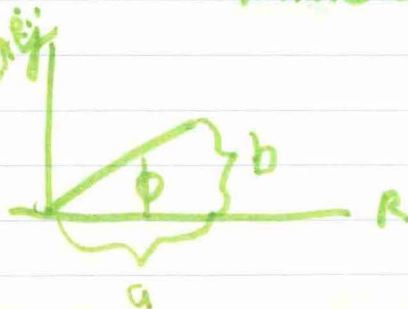

$$a + jb$$

EULER (EXP)

$$e^{a+jb} = e^a e^{jP} = A_1 e^{jb}$$

$$= A_1 [\cos b + j \sin b]$$

MAY EXPRESS IN TERMS OF
POLAR, COORDINATE (RECTANGULAR),
OR EULER (EXPONENTIAL)

PHASOR

$A_1 \angle \phi_1 \leftrightarrow A_1 \cos(\omega t + \phi_1)$
(MUST BE FUNCTION OF TIME)
WILL REPRESENT VOLTAGE
AND CURRENTS.


$$\omega = 2\pi f$$

$$T = 1/f$$

SHOULD KNOW EULER'S EQUA.

$$Z_R = R \angle 0^\circ = R + j0$$

$$\frac{V}{I} = Z$$

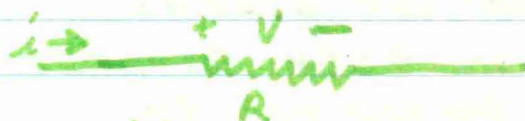

$$R = \frac{V(s)}{I(s)}$$

$$V = RI \Rightarrow R = \frac{V(s)}{I(s)}$$

$$Z_C \quad i \rightarrow \overset{+}{V} \overset{-}{|} \text{---}$$

$$V = \frac{1}{C} \int i dt$$

$$\frac{V_s}{I_s} = \frac{1}{C} \frac{1}{s}$$

$$\frac{V_s}{I_s} \Rightarrow \frac{V_s}{I_s} = \frac{1}{Cs}$$

$$Z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$

$$= 0 - j \left(\frac{1}{\omega C} \right)$$



$$= \frac{1}{\omega C} \angle -90^\circ$$

$$Z_L = j\omega L$$

EX



CONVERT

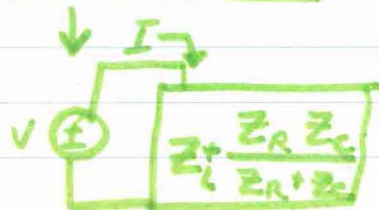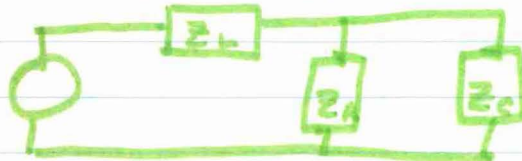


(CONT →)

$$I = \frac{V}{Z_{eq}} = \frac{V}{Z_L + \frac{Z_R Z_C}{Z_R + Z_C}}$$

$$I \angle \phi_3 = \frac{V \angle \phi_1}{|Z_{eq}| \angle \phi_2} \quad \text{IF } \phi_2 = 0$$

(SUBTRACT \angle 'S WHEN DIVIDING)

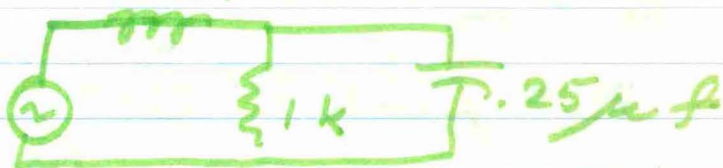

$$Z_{eq} = Z_L + \frac{Z_R Z_C}{Z_C + Z_R}$$

$$= j\omega(.2) + \frac{(1000)(-j(25 \times 10^{-6}\omega))}{(25 \times 10^{-6}\omega) + 1000}$$


$$= j\omega(.2) + \frac{16 \times 10^8}{1000 + \frac{16 \times 10^8}{\omega^2}} - \frac{45 \times 10^4}{\omega} j$$

IF PHASE $\angle = 0$, UNREAL
 PART OF EQ. = 0
 $\omega = 2000$

3-13-70

8-10)

$$V_s = 100 \angle 0^\circ$$

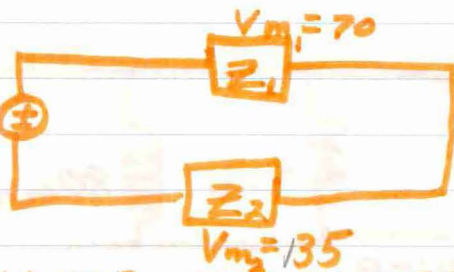

FIND 2 PHASOR VOLTAGES

$$V_1 = 70 (\cos \phi_1 + j \sin \phi_1)$$

$$V_2 = 135 (\cos \phi_2 + j \sin \phi_2)$$


$$V_s = V_1 + V_2$$

$$100 + j0 = 70 \cos \phi_1 + j70 \sin \phi_1 + 135 \cos \phi_2 + j135 \sin \phi_2$$


$$100 = 70 \cos \phi_1 + 135 \cos \phi_2$$

$$0 = 70 \sin \phi_1 + 135 \sin \phi_2$$


ϕ_1	ϕ_2
-76°	$+30.3^\circ$
76°	-30.3°

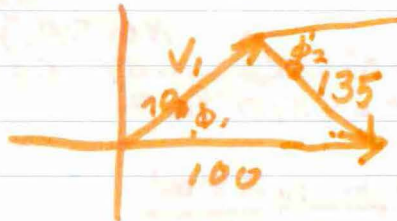

8-16)

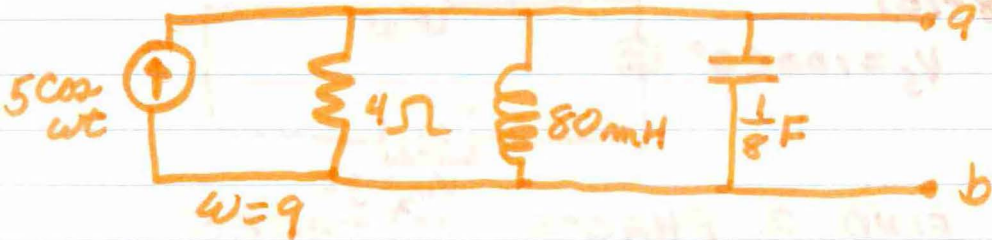

FIND THEV. EQ. IN PHASOR FORM

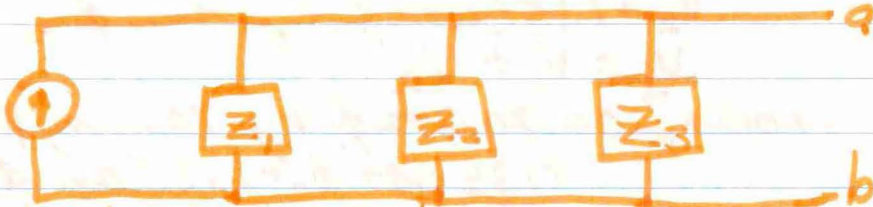

$$Z_1 = 4 \angle 0^\circ$$

$$Z_2 = (80 \times 10^{-3}) \bullet j \omega$$

$$Z_3 = -\frac{8j}{\omega}$$

$$\text{LET } Z_4 = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{4 (.08) j \omega}{4 + .08 j \omega}$$

$$Z_4 = \frac{j .32 \omega (4 - j .08 \omega)}{16 + 64 \times 10^{-4} \omega^2} \quad \begin{array}{l} \text{MULTIPLY} \\ \text{BY CONJUGATE} \end{array}$$

$$= \frac{.0256 \omega^2 + j 1.28 \omega}{16 + .0064 \omega^2}$$

$$Z_{eq} = \frac{10.24 \omega - j (2.048) \omega^2}{.0256 \omega^2 + j 1.28 \omega^2 - 128j - .0512 \omega^2 j}$$

ETC

CONT \longrightarrow

$$\frac{a+jb}{c+jd} = \frac{N \angle \phi_1}{D \angle \phi_2}$$

IF $\phi_1 = \phi_2$, THEN $Z = R$


$$a) Z = 2.75 \angle 46.6^\circ \quad \omega = 9$$

$$V_{eq} = 13.75 \angle 46.6^\circ$$

$$b) Z_{eq} = 2.89 \angle -43.7^\circ \quad \omega = 11$$

$$V_{eq} = 14.45 \angle -43.7^\circ$$

$$c) \omega = 10$$

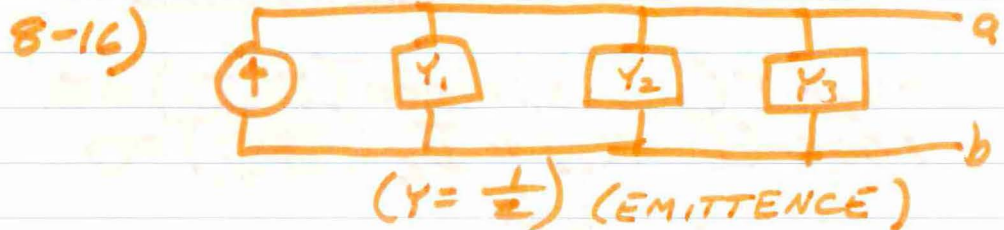

$$Y_1 = .25$$

$$Y_2 = \frac{1}{j \cdot .080 \omega} = -\frac{j}{.080 \omega}$$

$$Y_3 = j \cdot \omega / 8$$

$$Y_{eq} = Y_1 + Y_2 + Y_3$$

$$= (.25) + j \cdot 8 \omega - \frac{j}{.080 \omega}$$

$$= .25 + j \left(\frac{\omega}{8} - \frac{1}{.080 \omega} \right)$$


$$Z_{eq} = \frac{1}{Y_{eq}}$$

$$= \frac{1}{.25 + j \left(\frac{\omega}{8} - \frac{1}{.080 \omega} \right)}$$


$$\frac{\omega}{8} - \frac{1}{.080 \omega} = 0 \Rightarrow \omega = 10$$

FOR $Z = 0$

8-22)

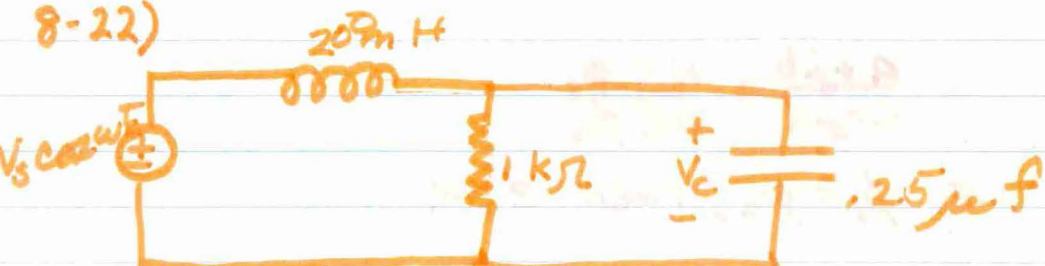

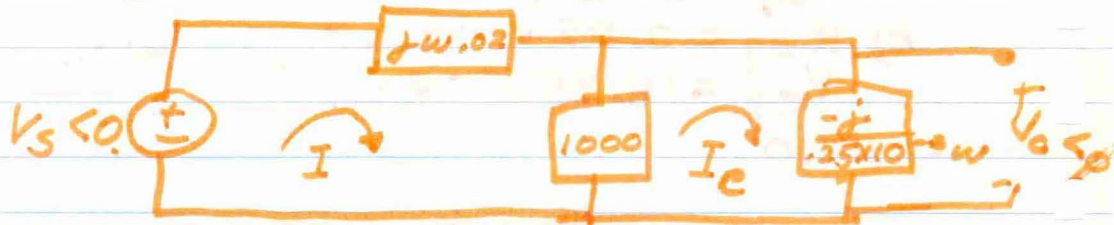b) FIND ω FOR WHICH AMPLITUDE IS A MAXIMUM



$$-V_s + I(j\omega \cdot 2) + 1000(I - I_c) = 0$$

$$1000(I_c - I) + I_c \left(\frac{-j}{.25 \times 10^{-6} \omega} \right) = 0$$

$$V_c = I_c \frac{4j}{10^{-6}}$$

$$\frac{dV_c}{d\omega} = 0$$

$$\frac{dV_c}{d\omega} = 0 = 2(4 \times 10^{-9} - 200\omega^2)(-400\omega)$$

$$+ .64 \times 10^{12}(2\omega) = 0$$

$$\omega = 3460$$




3-16-70

ANSWERS TO LAST TEST


① $A = -30 ; B = 40$

② $T = \frac{L}{R} = \frac{100 \times 10^{-3}}{\frac{(20 \times 80)}{20+80}} = 6.25 \text{ mSEC}$

③

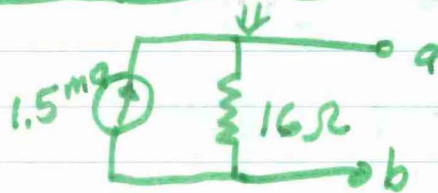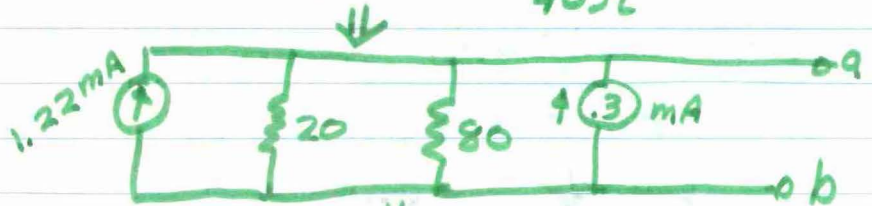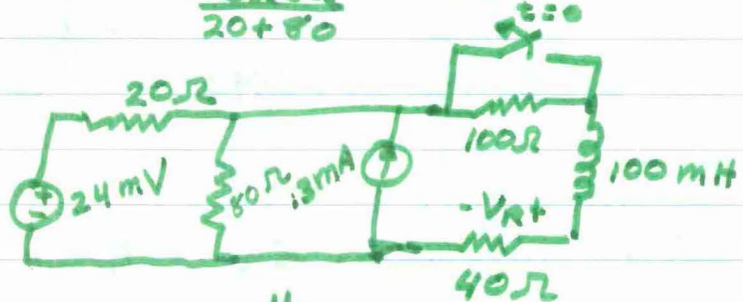

CONNECTING ON REST OF CIRCUIT

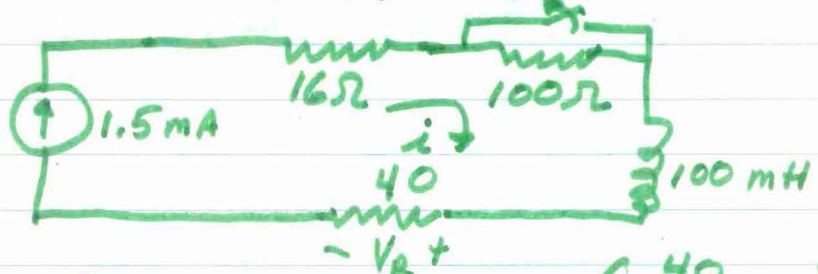


$t(0^-) \Rightarrow V_R = 24 \text{ mV} \left(\frac{40}{40+16} \right) = 17.1 \text{ mV}$

$t(0^+) \Rightarrow V_R(0^+) = 17.1 \text{ mV} \quad i = \frac{24 \times 10^{-3}}{56}$

$t(\infty) \Rightarrow V_R(\infty)$


$= 24 \left(\frac{40}{156} \right) = 6.15 \text{ mV}$

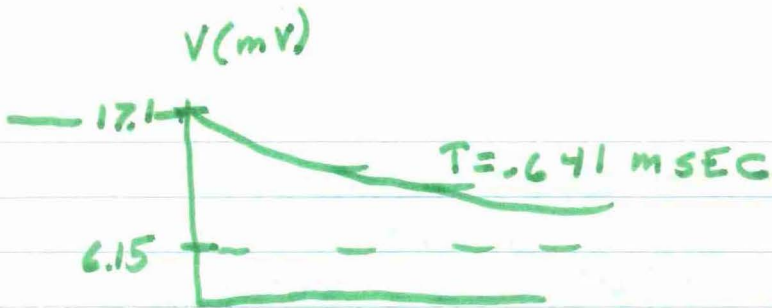$T = \frac{L}{R} = \frac{1}{156} = 0.641 \text{ mSEC} \quad \text{CONT} \rightarrow$




$$V_R(t) = 17.1 \mu(t) + [6.15 + 10.95 e^{-\frac{t}{T}}] \mu(t)$$

(mV)

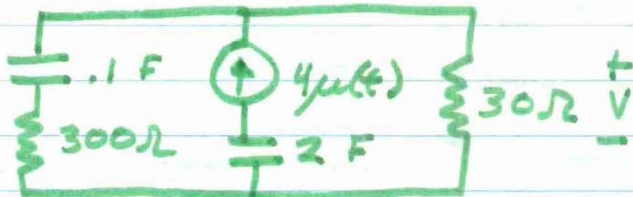


FIND $V(0^+)$

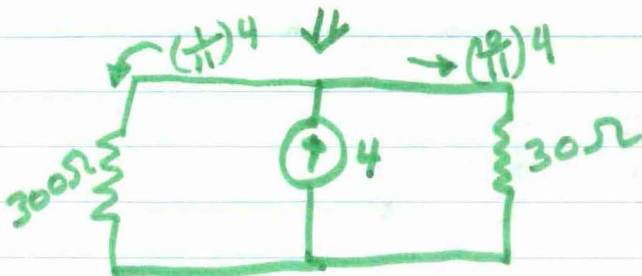

$$\therefore V = \frac{10}{11} (4) (36) = 109 \text{ V}$$

X8-6)

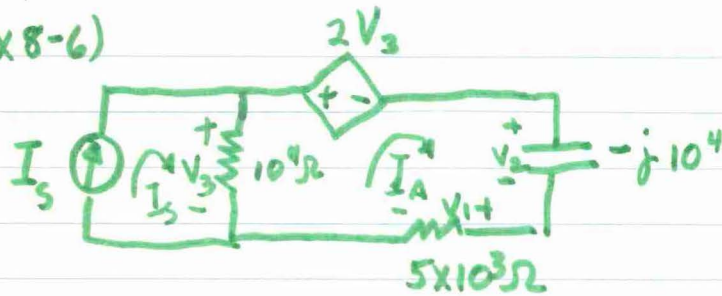

$$I_s = 2 \times 10^{-3} \angle 90^\circ$$

$$10^4 I_A = 2 \times 10^{-3} \angle -90^\circ$$

$$10^4 (I_A + j 2 \times 10^{-3}) + 2V_3 - I_A 10^4 j + 5 \times 10^3 I_A = 0$$

$$V_3 = 10^4 [-j 2 \times 10^{-3} - I_A]$$

$$10^4 (-j 2 \times 10^{-3} - I_A) + I_A (-j 10^4) + I_A (5 \times 10^3) = 0$$

$$I_A = \frac{j 20}{-10^4 - j 10^4 + 5 \times 10^3}$$

$$= \frac{20j}{-5 \times 10^3 - j 10^4} = \frac{j 2 \times 10^{-2} (5 + j 10)}{-5 + j 10 (5 + j 10)}$$

$$= \frac{-0.2 - 0.1j}{125} = \frac{-2}{1250} - j \frac{1}{1250}$$

$$\Rightarrow I_A = \frac{2(1.118)}{1250} \angle -153^\circ$$

$$V_1 = \frac{10,000(1.118)}{1250} \angle -153^\circ$$

$$= 8.94 \angle -153^\circ$$

$$|V_2| = 2|V_1|$$

I) INTRODUCTION TO VOLTAGE AND CURRENT

A) DEFINITION (WORD) - 3-4

- 1) VOLTAGE - MEASURE OF ENERGY NECESSARY TO MOVE AN ELECTRIC CHARGE FROM ONE TERMINAL TO ANOTHER
- 2) CURRENT - RATE AT WHICH CHARGE MOVES THROUGH ELEMENT
- 3) POWER = (CURRENT)(VOLTAGE)
WATT = (AMP)(VOLT)

B) THE ELECTRIC FIELD - 4

1) COULOMB'S LAW - $F = \frac{q_1 q_2}{4\pi\epsilon_0 r^2}$

a) $\epsilon_0 = 8.85 \times 10^{-12} \frac{\text{FARADAY}}{\text{METER}}$

b) F IS IN NEWTONS

2) ELECTRON

a) MASS = $9.109 \times 10^{-31} \text{ kg}$

b) $q = -1.602 \times 10^{-19} \text{ COUL}$


3) ELECTRIC FIELD INTENSITY

a) $E = \frac{dF}{dQ}$

b) MAGNITUDE OF A FIELD: $E = \frac{Q}{4\pi\epsilon_0 r^2}$ (POINT)

c) $E = \frac{N}{C} = \frac{V}{m}$

4) f) FOR 2 // PLATES

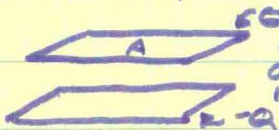1)  $E = \frac{Q}{\epsilon_0 A}$

2) ACCEL OF AN ELECTRON

a) $E = Fd$

b) $F = ma$ ETC

C) VOLTAGE - POTENTIAL DIFFERENCE

1) PLACE TEST CHARGE Q IN A FIELD E . Q DOESN'T EFFECT E

a) $F_{\text{FIELD}} = QE$

b) MOVE CHARGE AGAINST FIELD $-L$ (RIGHT)

1) $W = QEL$ (W IN JOULES)

2) $W_f - W_o = QEL$

c) TAKE AWAY FORCE THAT MOVED Q

1) WOULD GO TO THE RIGHT

2) $W = \text{K.E.} = \frac{1}{2} m v^2 = QEL$

d) W INDEPENDENT OF PATH

e) $W = W_f - W_o = -Q \int_1^2 E_L dL$

FOR NON-UNIFORM FIELDS

2) $V = \frac{\text{JOULE}}{\text{COULOMB}}$

3) $V = Ed$

D) CURRENT (i)

1) a) LINEAR, $i = \frac{q}{t}$

b) NON-LINEAR, $i = \frac{dq}{dt}$

2) AMP = $\frac{\text{COULOMB}}{\text{SEC}}$

3) CURRENT DENSITY a) $J = \frac{d i}{d A}$

b) UNITS OF $\frac{\text{AMP}}{\text{METER}^2}$

c) CURRENT \perp AREA

4) a) LINEARLY, $i = JA$

b) NON-LINEAR, $i = \iint J dA$


5) CHARGE DENSITY (ρ)

a) $\rho = \frac{dq}{dV}$

b) UNITS - $\frac{\text{COULOMBS}}{\text{m}^3}$

6) $J_L = \rho \cdot U$ ($U = \text{VELOCITY}$)

E) THE CATHODE RAY TUBE

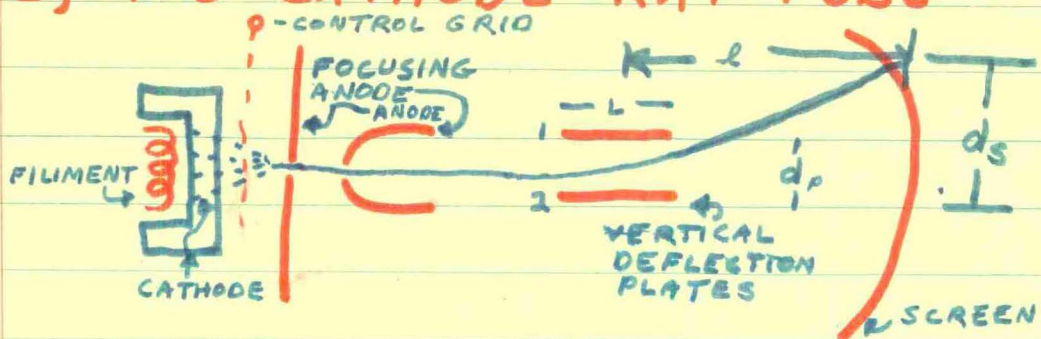

(OF AN ELECTRON)

$$1) \frac{1}{2} m_e u_{fa}^2 = eV_0$$

$$\therefore u_{fa} = \sqrt{\frac{2eV_0}{m_e}} = 5.93 \times 10^5 \sqrt{V_0}$$

2) PASSING THRU V.D.P.

$$a) V_{V.D.P.} = EL_{21}$$

$$b) E_L = \frac{V_d}{d_p}$$

3) AFTER V.D.P.

$$a) \text{UPWARD } a = \frac{eE_L}{m_e} \quad (\text{DURING V.D.P.})$$

(TAKES $\frac{L}{u_{fa}} = t$) TO GO THRU V.D.P.

b) ~~HITS SCREEN~~

$$b) u_y = \frac{eE_L L}{m_e u_{fa}}$$

$$c) d_s = u_y \frac{l}{u_{fa}} = \frac{V_{d1} L l}{2V_0 d_p}$$

4) OTHER INTERESTING JUNK

a) AT CATHODE

$$1) i = ne \quad (n = \# \text{ELECTRONS/SEC})$$

2) i IS FROM R TO L

b) CURRENT DENSITY

$$J = \frac{i}{A} = \frac{ne}{\pi r^2} \quad (r = \text{RADIUS OF e BEAM})$$

c) CHARGE DENSITY

$$\rho = \frac{J}{u_0} = \frac{i}{\pi r^2} \sqrt{\frac{m}{2eV_0}}$$

II) VOLTAGE-CURRENT RELATIONSHIPS - 29

A) TIME-INDEPENDENT V-I RELATIONSHIPS (LINEAR & NONLINEAR)

B) FAMILY OF V-I CURVES

1) OCCURS WHEN OTHER VARIABLE IS PRESENT.

2) EX) $i = 10^{-6}V + 10^{-3}L$

3) SET 3RD VARIABLE TO CONVENIENT CONSTANTS TO PLOT FAMILY OF CURVES

4) A CURVE IN WHICH $i = 0$ FOR $V < 0$ AND LINEAR FOR $V > 0$ IS CALLED "PIECEWISE LINEAR"

C) THE V-I CHARACTERISTIC OF A PHYSICAL DEVICE

1) ELECTRON EMISSION OCCURS AT CATHODE

b) ENERGY NEEDED FOR EMISSION IS CALLED "POTENTIAL BARRIER"

2) PHOTOEMISSION (LIGHT ENERGY WHICH CAUSES EMISSION)

$$W(\text{ENERGY OF A PHOTON}) = \frac{hc}{\lambda}$$

a) $h =$ PLANCK'S CONSTANT

b) $c =$ VEL. OF LIGHT

c) $\lambda =$ WAVELENGTH OF LIGHT

$$d) \therefore W = \frac{1.242 \times 10^{-6}}{\lambda} \text{ eV}$$

3) TYPES OF EMISSION

a) PHOTOEMISSION - BY LIGHT

b) SECONDARY EMISSION - BY E. OF OTHER e^- 'S

c) FIELD EMISSION - BY ELECTRIC FIELD

d) THERMIONIC EMISSION - BY HEAT

4) CURRENT AS FUNCTION OF TEMP

$$i(T) = aAT^2 e^{-b/T}$$

a) $T = 0K$ b) $a, b =$ CONSTANT CHARAC. OF MATERIAL

c) $A =$ SURFACE AREA OF MATERIAL

d) ELECTRIC FIELD STRENGTH AT CATH.

MUST BE GREAT ENOUGH TO REMOVE ALL THE EMITTED ELEC.

ie, IFF ANODE-CATHODE V IS SUFFICIENTLY HIGH, i VARIES WITH T

5) CHILD-LANGMUIR LAW

$$i(V) = 2.33 \times 10^{-6} \frac{A}{d^2} V^{3/2}$$

FOR || PLANE CAPACITOR

a) $d =$ DISTANCE BETWEEN THE TWO

b) $A =$ AREA (SURFACE)

c) HOLD TO POINT WHERE EVERY ELECTRON HAS BEEN USED

D) METHODS OF REPRESENTING $V-i$

RELATIONSHIPS - RARELY DO TRUE

$V-i$ RELATION. HAVE SIMPLE FUNCTIONS

E) DEFINITIONS - IDEAL

1) LUMPED CIRCUIT ELEMENT - REGION OF SPACE, WITH AT LEAST 2 TERMINALS


2) LUMPED CIRCUIT - A COLLECTION OF CONNECTED LUMPED CIRCUIT ELE.


3) CIRCUIT ANALYSIS - STUDY OF $V-i$ RELATIONSHIP IN LUMPED CIRCUIT

4) VOLTAGE SOURCE

a) A LUMPED 2 TERMINAL CIR. ELE.

b) $V = \text{CONSTANT} = V_s$ FOR ALL i

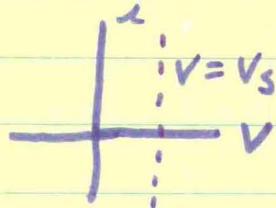


c) INDEPENDENT:  V_s

d) DEPENDENT:  V_s

5) CURRENT SOURCE

a) A LUMPED 2 TERMINAL CIR. ELE.

b) $i = \text{CONSTANT} = i_s$

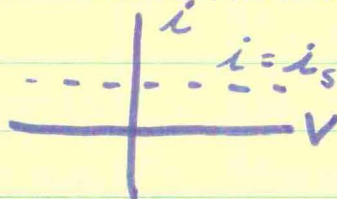



c)  i_s - INDEP.

d)  i_s - DEPEND.

6) LINEAR RESISTOR

a) A LUMPED 2 TERMINAL CIR. ELE

b) $V = iR$ (OHM'S LAW)

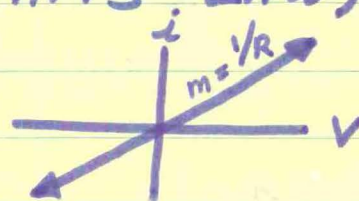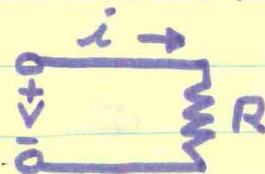

c) MEASURED IN OHMS (Ω) ($\frac{\text{VOLT}}{\text{AMP}} = \Omega$)

d) POWER INTO A RESISTOR ALWAYS HAS THE SAME SIGN AS R

e) FOR NONLINEAR RESISTORS:

1) $R = \frac{dV}{di}$

2) R IS RECIPROCAL OF $V-i$ SLOPE



7) IDEAL DIODE - 2 TERMINAL L.C.E.

a) CONDITIONS

1) $V = 0 \quad i > 0$

2) $i = 0 \quad V < 0$

3) $V i = 0$

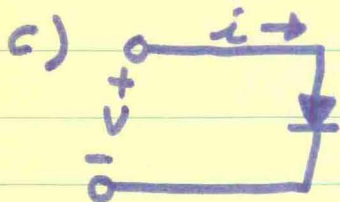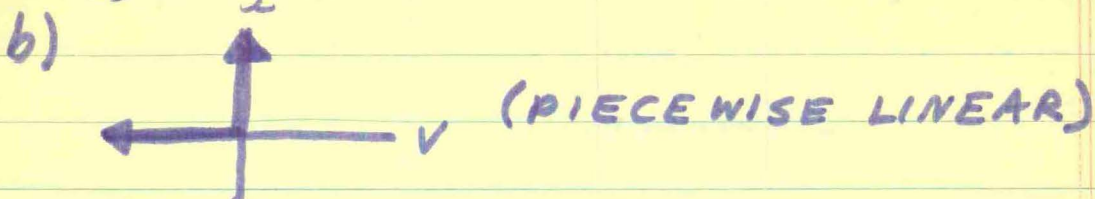


8) OPEN CIRCUIT - ~~V=0~~ $i = 0$ FOR ALL V



b) SPECIAL CASE OF CURRENT SOURCE

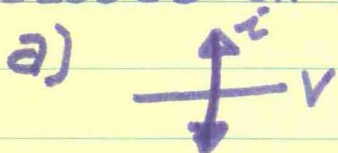
9) CLOSED OR SHORT CIRCUIT - $V = 0$ FOR ALL i



b) SPECIAL CASE OF VOLTAGE SOURCE


10) SERIES CONNECTION

a) TWO ELEMENT, $V \quad i = i_1 = i_2$

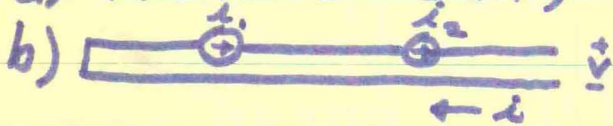

11) PARALLEL CONNECTION

a) TWO ELEMENTS $V \quad V = V_1 = V_2$

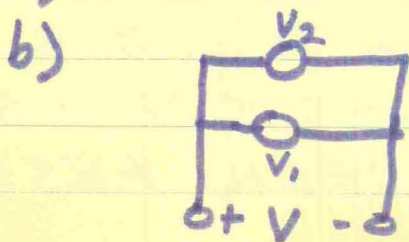

III) NETWORK SOLUTIONS

A) USEFUL DEFINITIONS

- 1) NODE - POINT AT WHICH 2 OR MORE CIRCUIT ELEMENTS MEET
- 2) BRANCH - PART OF NETWORK FROM ONE NODE TO ANOTHER (LUMPED CIR. ELE.)
- 3) LOOP - A SEQUENCE OF CIRCUIT ELEMENTS FORMING A CLOSED PATH
- 4) MESH - A LOOP WITH NO CIR. ELE. INSIDE
- 5) PLANAR NETWORK - ANY NETWORK THAT CAN BE DRAWN ON PAPER WITHOUT CROSSING LINES
- 6) ONE PORT NETWORK - 2 TERMINALS

B) KIRCHHOFF'S LAWS & SUCH

1) IN A CIRCUIT, ONE NEEDS 2 EQUATIONS FOR EACH ELEMENT TO SOLVE FOR V & i

2) SUM OF V AROUND CLOSED PATH = 0

$$\sum_{i=1}^N V_i = 0$$

3) SUM OF CURRENT ENTERING NODE = 0

$$\sum_{j=1}^M i_j = 0$$

4) MAY APPLY TOWARD SOLVING V & i

C) MESH & NODE TO DATUM

1) MESH

a) SOLVE FOR V USING CURRENT LAW ($V = iR$)

b) MUST DEFINE VOLTAGES ACROSS ALL CURRENT SOURCES

2) NODE TO DATUM

a) DEFINE DATUM ($V=0$)

b) PUT CURRENTS THRU ALL VOL. SOURCES

c) USE ~~VOL~~ CURRENT LAW TO FIND VOLTAGES ($i = V/R$)

D) NON-LINEAR ELEMENTS

1) KIRCHHOFF'S LAWS DON'T ARE EFFECTIVE.

2) SOLVE GRAPHICALLY, INSTEAD OF ALGEBRAICALLY.

E) CIRCUITS CONTAINING 2 OR MORE NON-LINEAR ELEMENTS MAY BE ADDED GRAPHICALLY AS ONE

F) LINEARITY AND SUPERPOSITION

1) LINEARITY - PROPERTY OF HAVING A

$V-i$ RELATIONSHIP IN FORM $i = aV + b$

OR $V = ci + d$. \Rightarrow GRAPHICALLY, A STRAIT LINE

(IF EVERY SOURCE IN CIRCUIT IS

DOUBLED, $V \nmid i$ ACROSS EVERY

BRANCH WILL DOUBLE

2) SUPERPOSITION PRINCIPLE - THE RESPONSE

OF ANY LINEAR NETWORK TO MORE

THAN ONE INDEPENDENT EXCITATION

IS GIVEN BY THE SUM OF THE

RESPONSES TO EACH EXICATION ACTING ALONE

IV) NETWORK EQUIVALENCE

A) DEFINITION - 2 NETWORKS ARE EQUIVALENT IFF THEY HAVE SAME $V-i$ RELATIONSHIP


B) TABLE OF EQUIVALENCE OF LUMPED CIRCUIT ELEMENTS

ELEMENTS	SERIES	PARALLEL
V_{s1}, V_{s2}	$V_s = V_{s1} + V_{s2}$	IMPOSSIBLE
I_{s1}, I_{s2}	IMPOSSIBLE	$I_s = I_{s1} + I_{s2}$
R_1, R_2	$R_{eq} = R_1 + R_2$	$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$
V_{s1}, R_2	UNCHANGED	$V_s = V_{s1}$
V_{s1}, I_{s2}	$I_s = I_{s2}$	$V_s = V_{s1}$
I_{s1}, R_2	$I_s = I_{s2}$	UNCHANGED


C) THE ULTIMATE REDUCTION:

THEVENIN & NORTON EQUIVALENTS

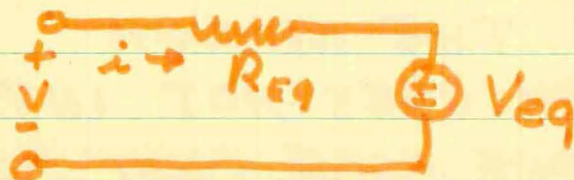
- 1) ANY LINEAR NETWORK MAY BE REDUCED TO THESE EQUIVALENTS
- 2) THEVENIN EQUIVALENT:



3) NORTON EQUIVALENT:

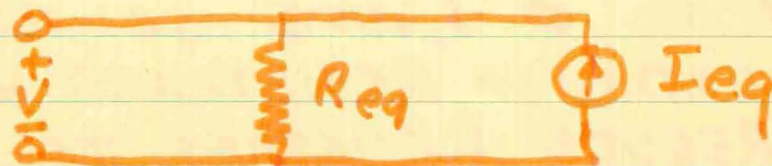

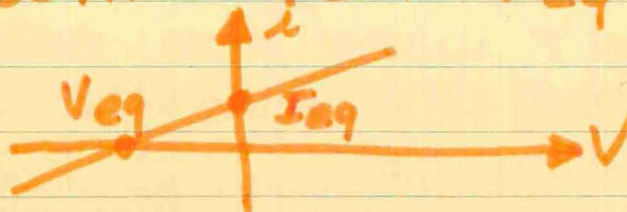4) IN BOTH CASES: $V_{eq} = R_{eq} I_{eq}$



D) METHODS OF REDUCTION TO EQUIVALENTS

1) USING DIRECT DETERMINATION OF A V-I EQUATION

a) THEVENIN EQ $\rightarrow V = a i + b$

NORTON EQ $\rightarrow i = k V + d$

b) $R_{eq} = a = 1/k$

c) $V_{eq} = b$

d) $I_{eq} = -d$

2) DETERMINATION OF V-I CURVE BY 2 PTS.

a) $R_{eq} = (V_2 - V_1) / (i_2 - i_1)$

b) $V_{eq} = V_1 - R_{eq} i_1 = V_2 - R_{eq} i_2$

c) $I_{eq} = V_1 / R_{eq} - i_1 = V_2 / R_{eq} - i_2$

3) USE OF OPEN CIRCUIT V & SH. CIR. CURRENT

a) ~~YIELD INTERCEPTS OF V-I GRAPH~~

b) USING $(V_{oc}, 0)$ AND $(0, i_{sc})$

1) $R_{eq} = -V_{oc} / i_{sc}$

2) $V_{eq} = V_{oc}$

3) $I_{eq} = -i_{sc}$

c) DOESN'T WORK IF INDEPENDENT SOURCE IS IN THE CIRCUIT

d) IF GRAPH DOES NOT INTERSECT

ORIGIN, ONE MORE POINT MUST BE DETERMIND.

MAY, IF CONVENIENT, SET i OR

V TO 0, AND SOLVE

4) REDUCTION OF RESISTANCE WITH V_{oc} OR i_{sc}

a) REDUCE RESISTORS TO $R_{eq} = 1/\text{slope}$

b) USE V_{oc} OR i_{sc} TO DETERMINE POINT

c) DOESN'T WORK FOR DEP. SOURCES



5) USE TABLE TO REDUCE SUPERFLUOUS COMBINATIONS

E) NETWORKS WITH THREE NODE SPECIFIED


1) IN T FORM

$$a) V_1 = Ai_1 + Bi_2 + C$$

$$V_2 = Di_1 + Ei_2 + F$$

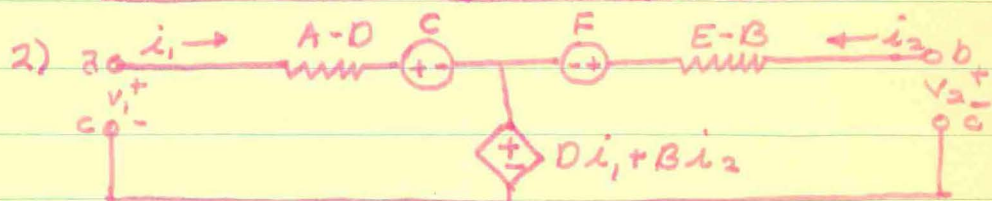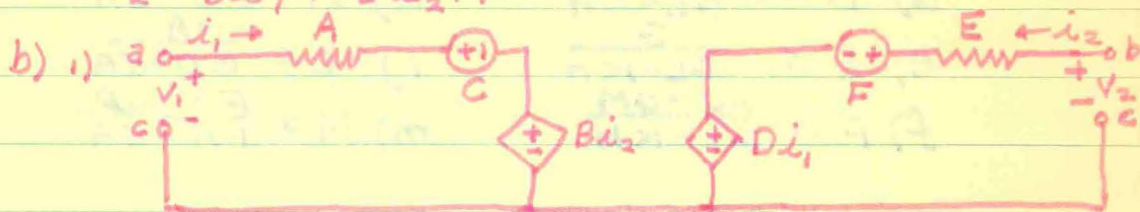

c) IF $B=D$ (KNOWN AS RECIPROCY)


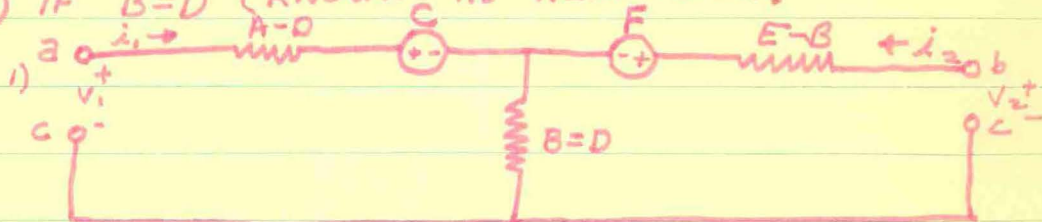


2) OCCURS WHEN INITIAL CIRCUIT IS COMPOSED OF LINEAR AND INDEPENDENT CIRCUIT ELEMENTS.


2) IN π FORM

$$a) i_1 = GV_1 + HV_2 + J$$

$$i_2 = KV_1 + LV_2 + M$$

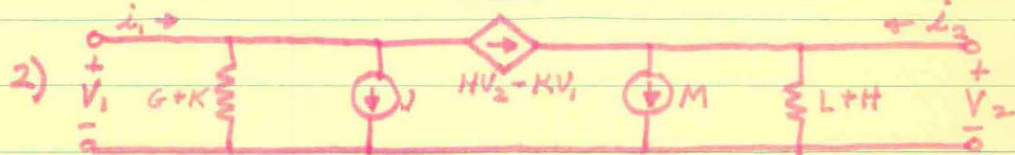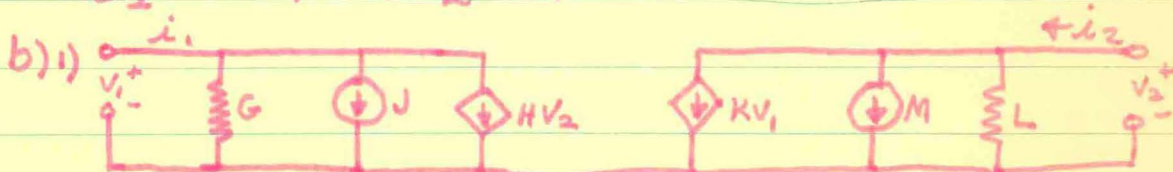

c) UNDER RECIPROCY ($H=K$)

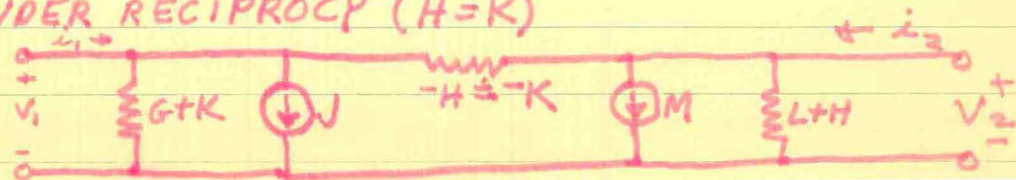

3) SOLVING ALGEBRICALLY FOR COEFF. OF T AND π EQUIVALENTS

$$a) A = \frac{L}{LG - KH}$$

$$b) B = \frac{-H}{LG - KH}$$

$$c) C = \frac{MH - JL}{LG - KH}$$

$$d) D = \frac{-K}{GL - KH}$$

$$e) E = \frac{G}{GL - KH}$$

$$f) F = \frac{KJ - GM}{GL - KH}$$

$$g) G = \frac{E}{EA - BD}$$

$$h) H = \frac{-B}{EA - BD}$$

$$j) J = \frac{BF - CE}{EA - BD}$$

$$k) K = \frac{D}{BD - EA}$$

$$l) L = \frac{-A}{BD - EA}$$

$$m) M = \frac{FA - CD}{BD - EA}$$

V) ENERGY STORAGE ELEMENTS

A) THE CAPACITOR

1) GAUSS' LAW $\nabla \cdot \mathbf{D} = \rho$

$$\oint_S \mathbf{D}_n \cdot d\mathbf{S} = \int_V \rho \, dV = q$$

\mathbf{D}_n = COMPONENT OF THE ELECTRICAL DISPLACEMENT NORMAL TO THE ENCLOSING SURFACE

b) IF SYSTEM IS LINEAR;

$$\mathbf{D} = \epsilon \mathbf{E}$$

(ϵ = PERMITTIVITY OF THE MEDIUM)

c) $q = CV$ (C = CAPACITANCE)

MKS FOR C IS FARAD = $\frac{\text{COUL}}{\text{VOLT}}$

d) CAPACITANCE

1) IN LINEAR SYSTEM, ϵ WILL APPEAR IN THE EXPRESSION ON C

2) C DEPENDS OF SYSTEM'S GEOM.

3) IN A LINEAR MEDIUM, C IS

INDEPENDENT OF q , V , AND i

4) IF NON-LINEAR, $C = dq/dV$

e) PERMITTIVITY CONSTANT $\nabla \cdot \mathbf{E} = \rho/\epsilon_0$


$$\mathbf{E} = \epsilon_r \mathbf{E}_0$$

1) ϵ = PERMITTIVITY OF MATERIAL

2) ϵ_0 = " CONSTANT ($= 8.85 \times 10^{-12} \frac{\text{F}}{\text{m}}$)

3) ϵ_r = RELATIVE PERMITTIVITY OF MATERIAL (> 1)

2) FOR A // PLATE CAPACITOR

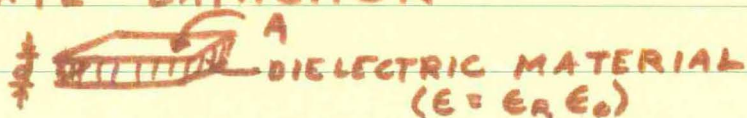


$$a) E = \frac{q}{\epsilon A}$$

$$b) V = Ed = \frac{qd}{\epsilon A}$$

$$c) C = \frac{q}{V} = \frac{\epsilon A}{d}$$

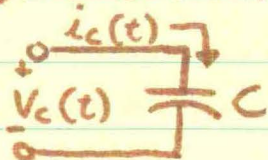3) CAPACITOR - DEFINITION & SUCH

$$a) V-i \text{ RELATIONSHIP} \rightarrow i_c(t) = C \frac{dV_c(t)}{dt}$$



$$\text{OR } V_c(t) = \frac{1}{C} q(t)$$

$$\rightarrow b) V_c(t) = \frac{1}{C} \int i_c(t) dt + k$$

(k SUMMERIZES EFFECT OF V_c BEFORE $i_c(t)$ WAS KNOWN)

c) POWER IN A CAPACITOR

$$P(t) = V_c(t) i_c(t) = V_c(t) C \frac{dV_c(t)}{dt}$$

d) WORK (ENERGY STORED)

$$W_c = \int_0^{V_c(t)} C V_c(t) dV_c(t)$$

$$= \frac{1}{2} C V_c^2(t) = \frac{1}{2} q V_c(t) = \frac{1}{2} \frac{q^2(t)}{C}$$

e) WHEN $V=0$, CAP. ACTS AS OPEN CIRCUIT

f) THERE ARE NO DISCONTINUITIES IN A CAPAC UNLESS $i = \infty$

B) THE UNIT STEP FUNCTION

$$1) u(t-t_0) = 0 \quad -\infty < t < t_0$$

$$= 1 \quad t_0 < t < \infty$$


$$2) u(t-t_0)$$



c) UNIT IMPULSE FUNCTION δ

1) $u(t-t_0) = \int_{-\infty}^t \delta(t-t_0) dt$

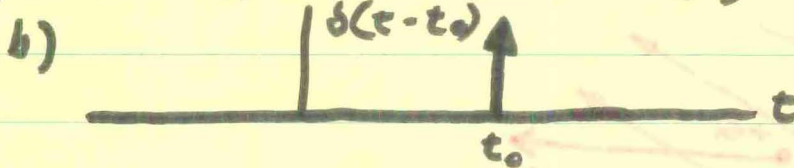
2) a) $\delta(t-t_0) = 0$ FOR $t < t_0$; $t > t_0$



3) $\int_{-\infty}^{\infty} \delta(t-t_0) dt = 1 \Rightarrow$ AREA OF UNIT IMPULSE ($0 \cdot \infty$) IS UNITY

4) BY APPROXIMATION

a)

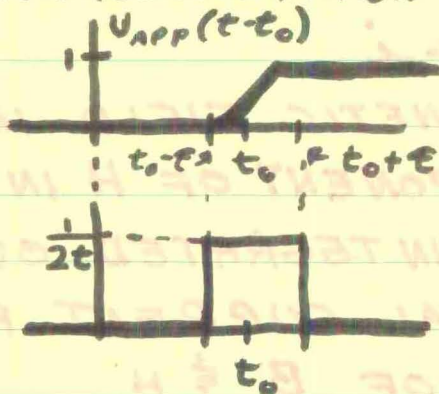

b) $u(t_0+t) = \lim_{\epsilon \rightarrow 0} U_{APP}(t-t_0)$

c) $\delta(t-t_0) = \lim_{\epsilon \rightarrow 0} \frac{d}{dt} [U_{APP}(t-t_0)]$

d) THE MAGNETIC FLUX FIELD

1) THE MAGNETUDE OF FORCE ON A POINT CHARGE MOVING IN A MAGNETIC AT A VELOCITY

$$F = QUB \sin \theta (= Q \vec{U} \times \vec{B})$$

a) $B =$ MAGNETIC FLUX DENSITY ($\frac{\text{WEBER}}{\text{M}^2} = \text{TESLA}$)

b) $Q =$ POINT CHARGE

c) $U =$ VELOCITY OF PARTICLE

d) $\theta =$ ANGLE BETWEEN U AND B

e) DIRECTION OF F DETERMINED BY RIGHT HAND SCREW RULE.


2) IF MAGNETIC FLUX DENSITY (\vec{B}) IS PRESENT:

a) $\Phi = \int_S B_n dS$ (= FLUX)

1) B_n = COMPONENT OF B NORMAL TO SURFACE ELEMENT

2) S = SURFACE

3) θ

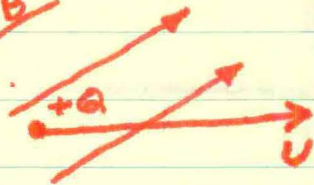

b) WHEN COMPUTED AROUND A CLOSED SURFACE, $\Phi = 0$

3) AMPERE'S LAW:

$$\oint H_\ell d\ell = i$$

a) H = MAGNETIC FIELD INTENSITY ($\frac{\text{AMP}}{\text{m}}$)

b) H_ℓ = COMPONENT OF H IN THE DIRECTION OF $d\ell$, INTEGRATED OVER A CLOSED PATH

c) i = TOTAL CURRENT PASSING THRU

4) RELATION OF B & H

a) IN FREE SPACE; $B = \mu_0 H$

$$(\mu_0 = 4\pi \times 10^{-7} \frac{\text{HENRIES}}{\text{METER}})$$

b) IF THE MATERIAL IS LINEAR, HOMOGENEOUS, AND ISOTROPIC:

1) $B = \mu H$

2) $\mu = \mu_r \mu_0$

(μ_r = DIMENSIONLESS RELATIVE PERMEABILITY)

E) FARADAY'S LAW

$$1) \oint E_e dl = -\frac{d}{dt} \int_S B_n ds = -\frac{d\Phi}{dt}$$

2) FOR A LOOP OF WIRE:

$$a) \oint E_e dl = \frac{2\pi r_0^2 B_0}{r_0}$$

$$b) \text{OR } E_{\text{AVE}} = \frac{r_0 B_0}{T}$$

$$3) \int B_n ds = N\Phi$$

F) THE INDUCTOR

$$1) \text{ IN A COIL: } a) L = \frac{N\Phi}{I}$$

$$b) \text{ NON-LINEAR: } L = \frac{d(N\Phi)}{di}$$

2) FOR A SOLENOID: 

$$L = \mu_0 n^2 d \pi a^2$$

$$3) V = \frac{d(Li)}{dt} = i \frac{dL}{dt} + L \frac{di}{dt}$$

4) DEFINITION: $N\Phi = Li$; A LUMPED TWO TERMINAL CIRCUIT ELEMENT.

$$V-i \text{ RELATIONSHIP } V_L(t) = L \frac{di(t)}{dt}$$

$$5) i(t) = \frac{1}{L} \int_0^t V_L(t) dt + K$$
$$(K = \frac{1}{L} \int_{-\infty}^{t_0} V_L(t) dt)$$

F) REDUCTION OF SERIES AND PARALLEL COMBINATIONS OF CAPACITORS AND INDUCTORS

1) CAPACITORS

$$a) \text{ IN PARALLEL: } C_{eq} = C_1 + C_2$$

$$b) \text{ IN SERIES: } \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

2) INDUCTORS

$$a) \text{ IN PARALLEL: } \frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$b) \text{ IN SERIES: } L_{eq} = L_1 + L_2$$

G) MOST IMPORTANT PLUGS AND CONCEPTS

$$1) i_c(t) = C \frac{dV_c(t)}{dt}$$

$$2) V_c(t) = \frac{1}{C} \int_0^t i_c(t) dt + k$$

$$3) p_c(t) = V_c(t) C \frac{dV_c(t)}{dt}$$

4) CAPACITOR ACTS AS AN OPEN CIRCUIT WHEN THE VOLTAGE ACROSS IT IS NOT CHANGING

5) A CAPACITOR CAN NOT HAVE AN IMMEDIATE VOLTAGE CHANGE ACROSS IT

$$6) V_L = L \frac{di}{dt} + i \frac{dL}{dt}$$

$$7) i_L = \frac{1}{L} \int_0^t V_L(t) dt + k$$

8) AN INDUCTOR BEHAVES AS A SHORT CIRCUIT WHEN THE CURRENT THRU IT IS NOT CHANGING

9) THERE CAN BE NO INSTANTANEOUS CURRENT CHANGE THRU AN INDUCTOR

VI) INTRODUCTION TO RL & RC CIRCUITS

A) WAVEFORM TERMINOLOGY

1) $v(t)$ IS PERIODIC IFF:

a) $v(t) = v(t+T)$ FOR ALL t

b) $T = \text{PERIOD (OF REPETITION)}$

2) $\frac{1}{T} \int_{t_0}^{t_0+T} v^2(t) dt < \infty > \frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) dt$


3) ANY WAVEFORM THAT IS NOT PERIODIC IS CALLED APERIODIC

4) SOME ARE "ALMOST PERIODIC"

EX: $\sin t + \sin \pi t$

5) RANDOM (ALL MIXED UP)

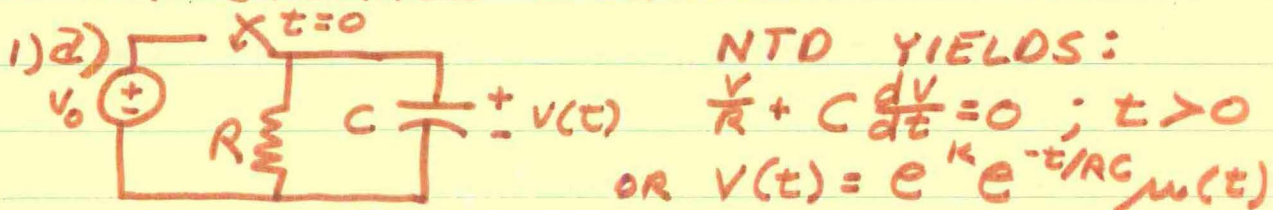B) SUDDEN CHANGES IN NETWORKS CONTAINING A DC. SOURCE, A RESISTOR, AND AN ENERGY STORAGE ELEMENT.



AT $t(0^-); v(0^-) = \ominus V_0$

AT $t(0^+); v(0^+) = V_0$


AT $t(\infty); v(\infty) = V_0$


$\therefore v(t) = V_0 \mu(-t) + V_0 e^{-\frac{t}{RC}} \mu(t)$

b) $\tau = (\text{TIME CONSTANT}) = RC$

AT τ FUNCTION DROPS

ONE "ETH," OR ABOUT 36.87%

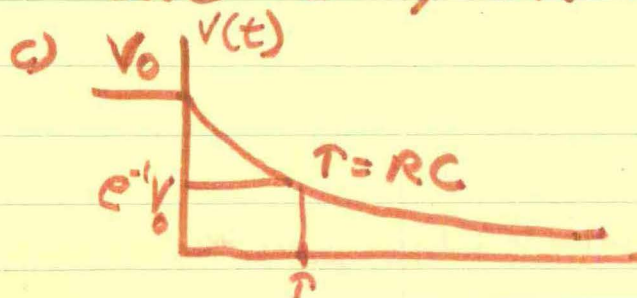

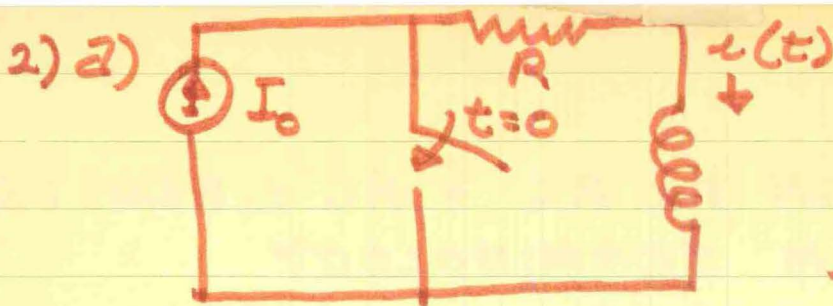


BY MESH:

$$Ri(t) + L \frac{di(t)}{dt} = 0$$

OR

$$i(t) = I_0 e^{-\frac{Rt}{L}} u(t)$$

b) $\tau = \frac{L}{R}$

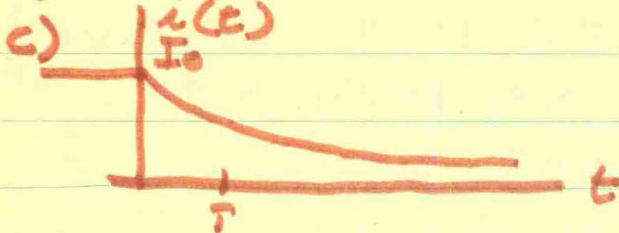

C) MORE GENERAL CIRCUITS CONTAINING ONE ENERGY STORAGE ELEMENT

1) ALL CIRCUITS CONTAINING ONE E.S.E. CAN HAVE AN EASILY DERIVED τ


a) $\tau = R_{eq}C$ OR $\tau = \frac{L}{R_{eq}}$

b) R_{eq} AS SEEN FROM ELEMENT'S TERMINALS

2) DETERMINE "4 NUGGETS OF KNOWLEDGE"

- a) $Y(0^-)$
- b) $Y(0^+)$
- c) $Y(\infty)$
- d) τ

3)

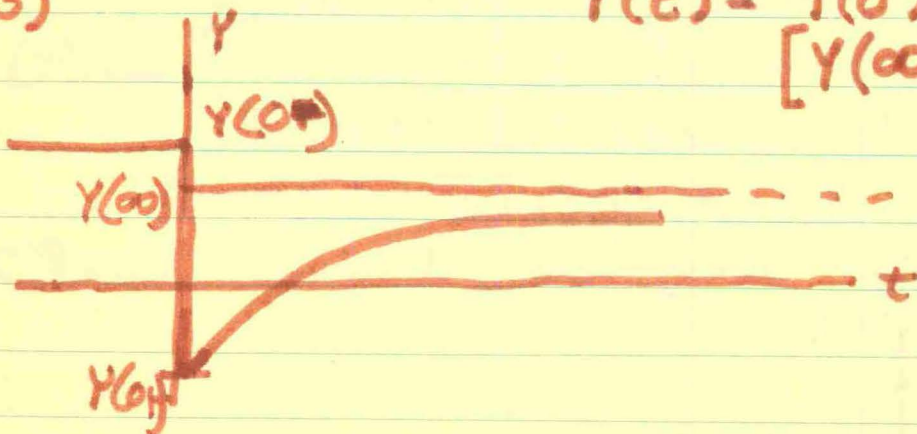

$$Y(t) = Y(0^-)u(-t) + [Y(\infty) + (Y(0) - Y(\infty))e^{-\frac{t}{\tau}}]u(t)$$

D) GENERAL OUTLINE FOR FINDING FOUR NUGGETS OF KNOWLEDGE

1) $Y(0^-)$ - FIND THE INITIAL STEADY STATE VALUE OF V OR i FOR THE NETWORK IN ITS CONDITION PRIOR TO CHARGE $C \cdot i$ AND $L \cdot V = 0$

2) $Y(0^+)$ - REPEAT ABOVE FOR $t > 0$, AGAIN. SWITCH ~~T~~ AGAIN $C \cdot i$ AND $L \cdot V = 0$

3) DETERMINE Y JUMP AT INSTANT OF CIRCUIT CHANGE. CAPACITOR VOLTAGE OR INDUCTOR CURRENT MUST REMAIN CONSTANT OVER THIS SHORT INTERVAL OF TIME


4) COMPUTE τ ($= RC$ OR $\frac{L}{R}$)

5) $Y(\infty)$ AGAIN CAP. i AND $L \cdot V$ IS ZERO

$$Y(t) = Y(0^-)u(t) + \left[Y(0) + \{ Y(\infty) - Y(0) \} e^{-\frac{t}{\tau}} \right] u(t)$$

V FOR INDUCTORS

i FOR CAPACITOR

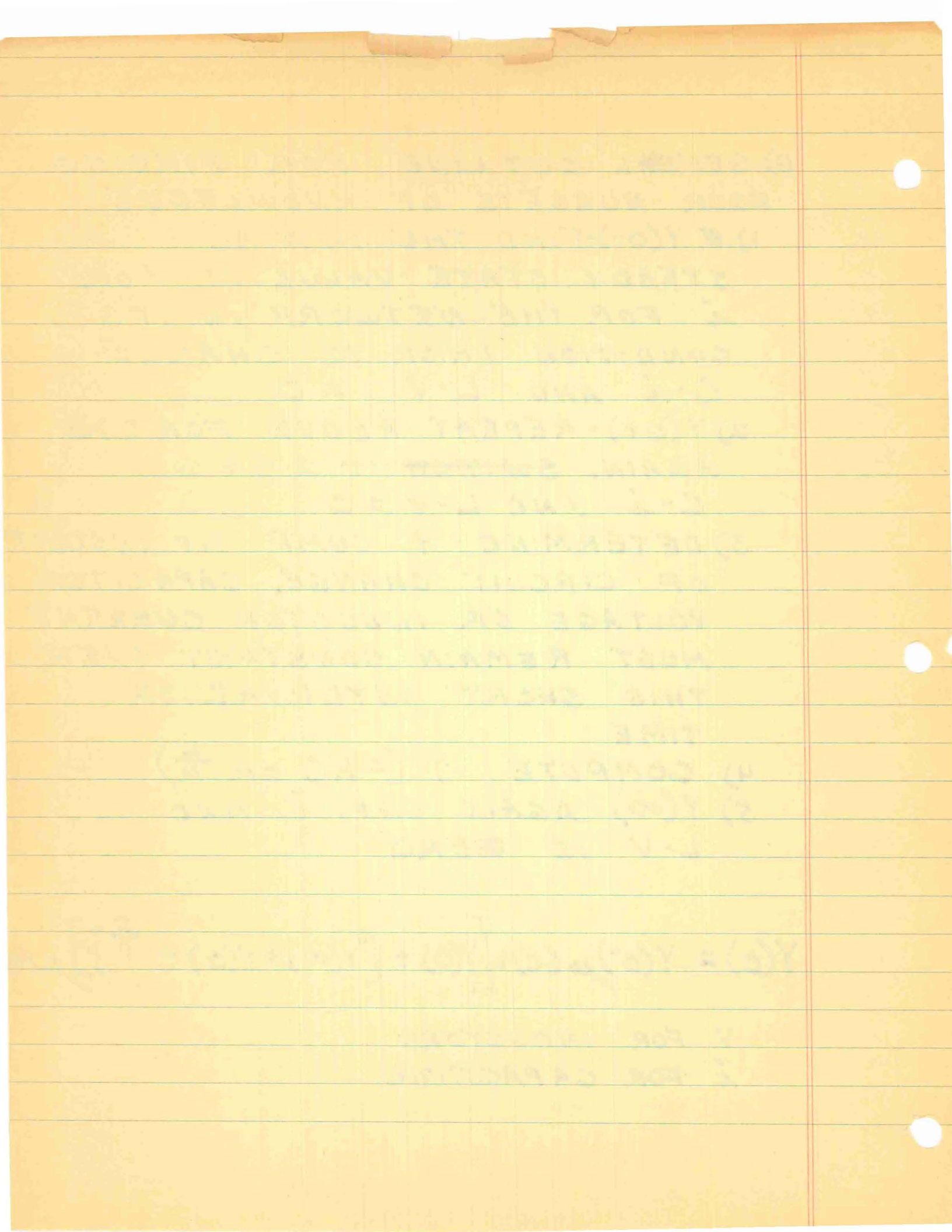

VII) SINUSOIDAL STEADY STATE ANALYSIS

A) THE PHASOR REPRESENTATION OF A SINUSOID

1) CONSIDER $i = I_m \cos(\omega t + \phi)$

a) PERIOD $T = \frac{2\pi}{\omega}$

b) FREQUENCY $f = \frac{1}{T}$

c) ANGULAR OR RADIAN FREQUENCY ω

d) ϕ IS THE PHASE ANGLE

2) SOME IDENTITIES

a) $e^{j\theta} = \cos\theta + j \sin\theta$

b) $\cos\theta = \frac{1}{2}(e^{j\theta} + e^{-j\theta})$

c) $\sin\theta = \frac{1}{2j}(e^{j\theta} - e^{-j\theta})$

d) $\therefore I_m \cos(\omega t + \phi) = i = \text{Re} [I_m e^{j(\omega t + \phi)}]$
(RE DENOTES REAL PART OF)

3) PHASOR - FOR ANY SINUSOIDAL FUNCTION

OF TIME, $a(t) = A_m \cos(\omega t + \phi)$, THE COMPLEX QUANTITY, $A = A_m \angle \phi = A_m e^{j\phi} =$

$A_m \cos\phi + j A_m \sin\phi$ IS THE PHASOR

REPRESENTATION OF $a(t)$, HENCE

$$a(t) = A_m \cos(\omega t + \phi) = \text{Re}(A e^{j\omega t})$$

WHERE

$$A = A_m e^{j\phi} = A_m \angle \phi = A_m \cos\phi + j A_m \sin\phi$$

B) PHASOR $v-i$ RELATIONSHIPS

1) IF $i = i_1 \pm i_2 \Rightarrow I = I_1 \pm I_2$

2) IF $v = Ri \Rightarrow V = RI$

3) IF $v = L \frac{di}{dt} \Rightarrow V = L j\omega I$

4) IF $v = \frac{1}{C} \int i dt \Rightarrow V = \frac{1}{Cj\omega} I$

C) IMPEDANCE

1) FOR R, L, C

a) $V = RI$

b) $V = j\omega L I$


c) $V = I / j\omega C$

2) DEFINITION: FOR 2 TERMINAL NETWORK COMPOSED OF IDEAL CIRCUIT ELEMENTS, OPERATING IN SINUSOIDAL STEADY STATE, THE RATIO OF PHASOR VOLTAGE V ACROSS THE TERMINALS TO PHASOR CURRENT I :

$$V = ZI$$

(Z MEASURED IN OHMS)

D) EQUIVALENTS (THEV) I (PHASOR)

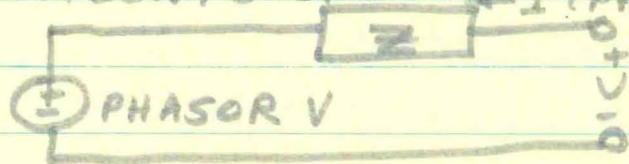

E) REACTANCE: $Z = R + jX$ ($X = \text{REACT.}$)

F) ADMITTANCE $Y = 1/Z$

G) SUSCEPTANCE B : $Y = G + jB$

H) POWER - RMS VALUE

1) FOR ANY PERIODIC WAVEFORM

$$P_{AV} = \overline{p(t)} = \frac{1}{T} \int_{t_0}^{t_0+T} v(t) i(t) dt$$

2) FOR SINUSOIDAL WAVE

$$P_{AV} = \frac{1}{2} V_m I_m \cos(\beta - \alpha)$$

3) FOR A SOURCELESS 2 TER. CIR.

$$P_{AVE} = \frac{1}{2} I_m^2 R_{eq} = \frac{1}{2} V_m^2 G_{eq}$$

I) RMS VALUE (TIME INDEPENDENT)

$$a) P_{AV} = I_{RMS}^2 R = \frac{R}{T} \int_{t_0}^{t_0+T} i^2(t) dt$$

$$b) I_{RMS} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) dt}$$

$$c) V_{RMS} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} v^2(t) dt}$$

d) IF $v(t)$ OR $i(t)$ IS SINUSOIDAL:

$$\textcircled{1} V_{RMS} = V_m / \sqrt{2} \quad (\text{SIN WAVE})$$

$$\textcircled{2} I_{RMS} = I_m / \sqrt{2}$$

COMPLEX NUMBERS
POLAR FORM CORRESPONDING TO RECTANGULAR FORM $1 + j Y$

Y	MAGNITUDE	PHASE ANGLE RADIANS DEGREES	Y	MAGNITUDE	PHASE ANGLE RADIANS DEGREES	Y	MAGNITUDE	PHASE ANGLE RADIANS DEGREES
0.025	1.000	0.0249 1.432	1.274	1.620	0.9056 51.892	2.599	2.785	1.2036 68.962
0.050	1.001	0.0499 2.862	1.299	1.640	0.9150 52.431	2.699	2.879	1.2160 69.676
0.075	1.002	0.0748 4.289	1.324	1.660	0.9242 52.957	2.799	2.973	1.2277 70.346
0.099	1.004	0.0996 5.710	1.349	1.680	0.9332 53.471	2.899	3.067	1.2387 70.974
0.124	1.007	0.1243 7.125	1.374	1.700	0.9419 53.972	2.999	3.162	1.2490 71.564
0.149	1.011	0.1488 8.530	1.399	1.720	0.9505 54.462	3.099	3.257	1.2587 72.121
0.174	1.015	0.1732 9.926	1.424	1.740	0.9588 54.940	3.199	3.352	1.2679 72.645
0.199	1.019	0.1973 11.309	1.449	1.761	0.9670 55.407	3.299	3.448	1.2765 73.141
0.224	1.025	0.2213 12.680	1.474	1.782	0.9750 55.863	3.399	3.543	1.2847 73.610
0.249	1.030	0.2449 14.036	1.499	1.802	0.9827 56.309	3.499	3.640	1.2924 74.054
0.274	1.037	0.2683 15.376	1.524	1.823	0.9903 56.745	3.599	3.736	1.2998 74.475
0.299	1.044	0.2914 16.699	1.549	1.844	0.9978 57.171	3.699	3.832	1.3068 74.875
0.324	1.051	0.3142 18.004	1.574	1.865	1.0050 57.587	3.799	3.929	1.3134 75.256
0.349	1.059	0.3366 19.290	1.599	1.886	1.0121 57.994	3.899	4.026	1.3197 75.618
0.374	1.068	0.3587 20.556	1.624	1.908	1.0191 58.392	3.999	4.123	1.3258 75.963
0.399	1.077	0.3805 21.801	1.649	1.929	1.0259 58.781	4.099	4.220	1.3315 76.292
0.424	1.086	0.4018 23.025	1.674	1.950	1.0325 59.162	4.199	4.317	1.3370 76.607
0.449	1.096	0.4228 24.227	1.699	1.972	1.0390 59.534	4.299	4.414	1.3422 76.907
0.474	1.107	0.4434 25.407	1.724	1.993	1.0454 59.898	4.399	4.512	1.3473 77.195
0.499	1.118	0.4636 26.565	1.749	2.015	1.0516 60.255	4.499	4.609	1.3521 77.471
0.524	1.129	0.4834 27.699	1.774	2.037	1.0577 60.603	4.599	4.707	1.3567 77.735
0.549	1.141	0.5028 28.810	1.799	2.059	1.0636 60.945	4.699	4.805	1.3611 77.988
0.574	1.153	0.5218 29.898	1.824	2.081	1.0695 61.279	4.799	4.903	1.3653 78.231
0.599	1.166	0.5404 30.963	1.849	2.102	1.0752 61.606	4.899	5.000	1.3694 78.465
0.624	1.179	0.5585 32.005	1.874	2.124	1.0808 61.927	4.999	5.098	1.3733 78.689
0.649	1.192	0.5763 33.023	1.899	2.147	1.0863 62.241	5.199	5.295	1.3808 79.114
0.674	1.206	0.5937 34.019	1.924	2.169	1.0916 62.548	5.399	5.491	1.3876 79.508
0.699	1.220	0.6107 34.991	1.949	2.191	1.0969 62.850	5.599	5.688	1.3940 79.875
0.724	1.235	0.6273 35.942	1.974	2.213	1.1020 63.145	5.799	5.885	1.4000 80.217
0.749	1.249	0.6435 36.869	1.999	2.236	1.1071 63.434	5.999	6.082	1.4056 80.537
0.774	1.265	0.6593 37.775	2.024	2.258	1.1120 63.718	6.199	6.280	1.4108 80.837
0.799	1.280	0.6747 38.659	2.049	2.280	1.1169 63.996	6.399	6.477	1.4157 81.119
0.824	1.296	0.6897 39.522	2.074	2.303	1.1217 64.269	6.599	6.675	1.4204 81.384
0.849	1.312	0.7044 40.364	2.099	2.325	1.1263 64.536	6.799	6.873	1.4247 81.634
0.874	1.328	0.7188 41.185	2.124	2.348	1.1309 64.798	6.999	7.070	1.4288 81.869
0.899	1.345	0.7328 41.987	2.149	2.371	1.1354 65.055	7.199	7.269	1.4327 82.092
0.924	1.362	0.7464 42.768	2.174	2.393	1.1398 65.308	7.399	7.467	1.4364 82.303
0.949	1.379	0.7597 43.531	2.199	2.416	1.1441 65.555	7.599	7.665	1.4399 82.504
0.974	1.396	0.7727 44.274	2.224	2.439	1.1484 65.798	7.799	7.863	1.4432 82.694
0.999	1.414	0.7853 44.999	2.249	2.462	1.1525 66.037	7.999	8.062	1.4464 82.874
1.024	1.431	0.7977 45.707	2.274	2.485	1.1566 66.271	8.199	8.260	1.4494 83.046
1.049	1.449	0.8097 46.397	2.299	2.507	1.1606 66.501	8.399	8.459	1.4523 83.210
1.074	1.468	0.8215 47.069	2.324	2.530	1.1646 66.726	8.599	8.657	1.4550 83.367
1.099	1.486	0.8329 47.726	2.349	2.553	1.1684 66.948	8.799	8.856	1.4576 83.516
1.124	1.505	0.8441 48.366	2.374	2.576	1.1722 67.166	8.999	9.055	1.4601 83.659
1.149	1.523	0.8550 48.990	2.399	2.599	1.1760 67.380	9.199	9.254	1.4625 83.796
1.174	1.542	0.8656 49.600	2.424	2.623	1.1796 67.590	9.399	9.452	1.4648 83.927
1.199	1.562	0.8760 50.194	2.449	2.646	1.1832 67.796	9.599	9.651	1.4670 84.053
1.224	1.581	0.8861 50.774	2.474	2.669	1.1868 67.999	9.799	9.850	1.4691 84.173
1.249	1.600	0.8960 51.340	2.499	2.692	1.1902 68.198	9.999	10.049	1.4711 84.289

43
BOB MARKS
E SCI I
CHAPT I, #5


CHAPTER 1

$$\begin{aligned}
 15) a) \quad i &= \frac{q}{t} \\
 &= \frac{10^{11} e (3 \times 10^7 \text{ m}) (1.06 \times 10^{-19} \text{ COUL})}{\text{m} \cdot \text{s}} \\
 &= 3.18 \times 10^{-1} \frac{\text{COUL}}{\text{SEC}} \\
 &= .318 \text{ AMPS} \leftarrow \quad .48
 \end{aligned}$$

$$\begin{aligned}
 b) \quad V &= \frac{W_{F2} - W_{F1}}{q} \\
 W_{F1} &= 0 \\
 V &= \frac{W_{F2}}{q} = \frac{\Delta K.E.}{q} \\
 &= \frac{mv^2}{2q}
 \end{aligned}$$

$$\begin{aligned}
 V &= \frac{(9.11 \times 10^{-31} \text{ kg}) (3 \times 10^7 \text{ m})^2}{2 (1.06 \times 10^{-19} \text{ COUL}) \text{ SEC}^2} \\
 &= 38.7 \times 10^2 \frac{\text{JOULE}}{\text{COUL}} \\
 &= 3.87 \times 10^3 \text{ VOLTS} \leftarrow \\
 &\quad 2.156
 \end{aligned}$$
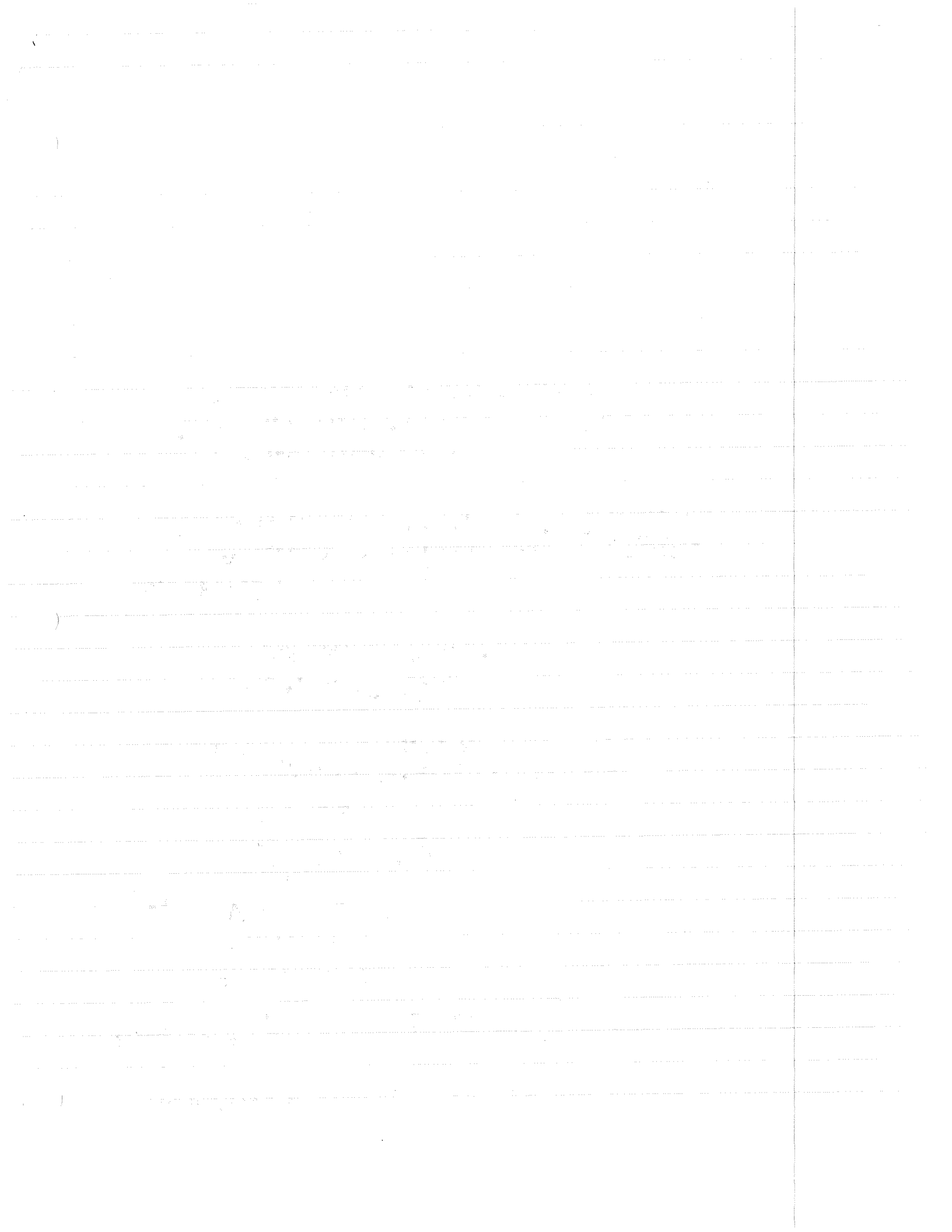
$$\begin{aligned}
 c) \quad P &= iV \\
 &= (.318 \text{ AMPS}) (3.87 \times 10^3 \text{ VOLTS}) \\
 &= 1.23 \times 10^4 \text{ WATTS} \left(\frac{1 \text{ KILOWATT}}{10^3 \text{ WATTS}} \right) \\
 &= 12.3 \text{ KILOWATTS} \\
 E &= (12.3 \text{ KILOWATTS}) (2 \text{ HOURS}) \\
 &= 24.6 \text{ KILOWATT-HOURS} \leftarrow
 \end{aligned}$$



16) a) $E_L = neV_0$ $E_S = (\frac{1}{2}n)eV_0$
 (ASSUMING $\frac{1}{2}$ THE ELECTRONS EMERGE FROM THE SMALLER FILAMENT)

$$\frac{E_S}{E_L} = \frac{\frac{1}{2}neV_0}{neV_0} = \frac{1}{2}$$

$$\therefore \rightarrow E_S = \frac{1}{2}E_L \leftarrow$$

b) $U_L = \sqrt{2eV_0/m_e}$ $U_S = \sqrt{2eV_0/m_e}$

$$U_L = U_S$$

$$\frac{d}{U} = t$$

$$t_L = \frac{d\sqrt{m_e}}{\sqrt{2eV_0}}$$

$$t_S = \frac{\frac{1}{2}d\sqrt{m_e}}{\sqrt{2eV_0}}$$

$$\frac{t_S}{t_L} = \frac{1}{2}$$

$$\therefore \rightarrow t_S = \frac{1}{2}t_L \leftarrow$$

c) FROM (b), $U_{Lx} = U_{Sx}$

$$U_{YL} = \frac{d_s U_0}{l_{ps}}$$

$$U_{YS} = \frac{\frac{1}{2}d_s U_0}{\frac{1}{2}l_s}$$

$$U_{YL} = U_{YS}$$

$$\therefore \rightarrow U_{fL} = U_{fS} \leftarrow$$

d) ~~V_L~~ $V_{dL} = \frac{d_s 2V_0 d_p}{l_p l_{ps}}$

$$V_{dS} = \frac{(\frac{1}{2}d_s) 2V_0 (\frac{1}{2}d_p)}{(\frac{1}{2}l_p) (\frac{1}{2}l_{ps})}$$

$$\therefore V_{dL} = V_{dS}$$

$$d_{sL} = U_{YL} \frac{l_{ps}}{U_{0L}}$$

$$d_{sS} = U_{YS} \frac{(\frac{1}{2}l_{ps})}{U_{0S}}$$

FROM (c) $U_{YL} = U_{YS}$ $V_{0L} = U_{0S} \Rightarrow \frac{d_{sS}}{d_{sL}} = \frac{1}{2}$

$$\therefore \left(\frac{d_s}{V_d}\right)_S = \frac{1}{2} \left(\frac{d_s}{V_d}\right)_L \leftarrow$$

BOB MARKS 1-12-70
E. SCI. I
CHAPTER I
15-16
35

Pg 56

$$5) a) i(V) = 2.33 \times 10^{-6} \frac{A}{d^2} V^{\frac{3}{2}}$$

$$\frac{A}{d^2} = \frac{i(V)}{(2.33 \times 10^{-6}) V^{3/2}}$$

$$= \frac{.1 \times 10^6}{(2.33)(10^3)^{3/2}} = \frac{10^5}{2.33 \times 10^3} = \frac{10^2}{2.33} = .429 \times 10^2 = 42.9$$

$$i(V) = (2.33 \times 10^{-6})(42.9)(400)^{3/2}$$
$$= (2.33 \times 10^{-6})(42.9)(8 \times 10^3)$$
$$= .800 \text{ AMPS}$$

$$i = \frac{\Delta q}{\Delta t}$$

$$\frac{\Delta q}{\Delta t} = .800 \text{ AMPS}$$

$$\Delta t = 1 \text{ SEC}$$

$$\Delta q = .800 \text{ COULOMBS}$$

$$\#e = \Delta q \left(\frac{\#e}{q} \right) = (.800 \text{ COUL}) \left(\frac{1 \text{ e}}{1.602 \times 10^{-19} \text{ C}} \right)$$

$$= .753 \times 10^{+19} \text{ ELECTRONS}$$

$$= 7.53 \times 10^{18} \text{ ELECTRONS } 8 \times 10^8$$

$$b) J = \frac{-4 V^{3/2}}{9 \times d^2 (1.90 \times 10^5)}$$

$$J = \rho \frac{V}{d^2}$$

$$\rho = \frac{-4 V^{3/2}}{9 \times d^2 (1.90 \times 10^5) V}$$

$$\rho = \frac{-4 V^{3/2}}{9 \times d^2 (1.90 \times 10^5) (5.93 \times 10^5) \sqrt{V}}$$

$$\rho = \frac{q}{Vol}$$

$$q = \frac{-4 V^{3/2}}{9 d^2 (1.90 \times 10^5) (5.93 \times 10^5)} \left(\frac{d^2}{A} \right) \left(\frac{1}{dt} \right)$$

$$= \frac{-4 \sqrt{V}}{9 (1.90 \times 10^{10}) (5.93) d^6} \left(\frac{d^2}{A} \right)$$

$$= \frac{-4 (20)}{9 (1.90 \times 10^{10}) (5.93) (10^{-18}) (42.9)}$$


$$= .0184 \times 10^8 \text{ COUL}$$

$$= 1.84 \times 10^6 \text{ COUL}$$



$$2.02 \times 10^{-10}$$

BOB MARKS
E. Sci. I. 1-14-70
CHAPT. 2, #53

11-10-70

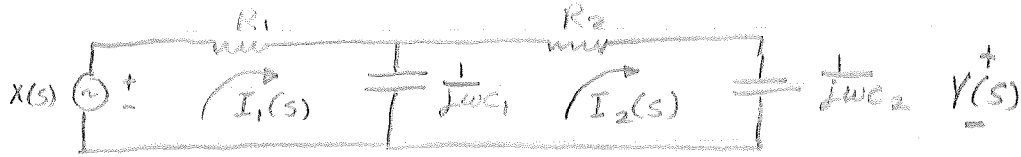
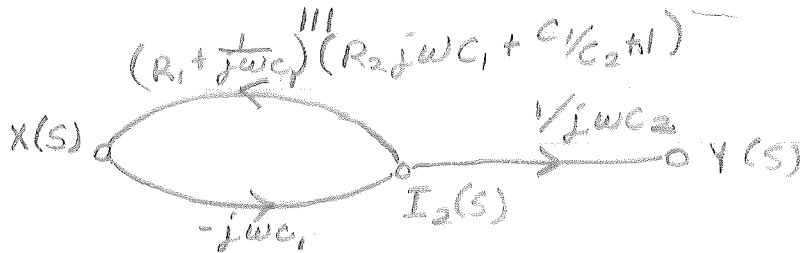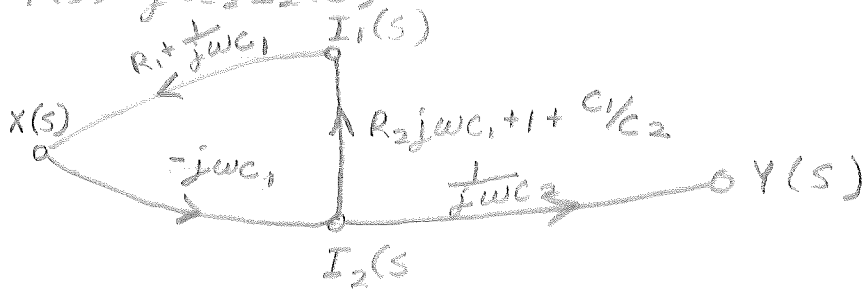
$$\begin{aligned}
 X(s) &= I_1(s) \left[R_1 + \frac{1}{j\omega C_1} \right] + I_2(s) \left[\frac{1}{j\omega C_1} \right] \\
 I_2(s) \left[R_2 + \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} \right] &= \frac{1}{j\omega C_1} I_1(s) \\
 \Rightarrow I_1(s) &= I_2(s) \left[R_2 j\omega C_1 + 1 + \frac{C_1}{C_2} \right] \\
 Y(s) &= \frac{1}{j\omega C_2} I_2(s)
 \end{aligned}$$



$$\begin{aligned}
 \frac{Y(s)}{X(s)} = H(j\omega) &= \frac{-j\omega C_1}{\left[1 - \left(R_1 + \frac{1}{j\omega C_1} \right) \left(R_2 j\omega C_1 + \frac{C_1}{C_2} + 1 \right) \right]} \frac{1}{j\omega C_2} \\
 &= \frac{C_1}{C_2 \left[\left(R_1 + \frac{1}{j\omega C_1} \right) \left(R_2 j\omega C_1 + \frac{C_1}{C_2} + 1 \right) - 1 \right]}
 \end{aligned}$$



TEST # 1; CRAM FORMULAS

I) CHAPTER 2: SYSTEM REPRESENTATION AND ANALYSIS

A) n^{th} ORDER DIFFER. EQ. (LINEAR):

$$a_n(t) \frac{d^n Y(t)}{dt^n} + a_{n-1}(t) \frac{d^{n-1} Y(t)}{dt^{n-1}} + \dots + a_1(t) \frac{dY(t)}{dt} + a_0(t) Y(t) = b_m(t) \frac{d^m X(t)}{dt^m} + b_{m-1}(t) \frac{d^{m-1} X(t)}{dt^{m-1}} + \dots + b_1(t) \frac{dX(t)}{dt} + b_0(t) X(t)$$

B) DEFINITION OF LINEAR SYSTEM:

$$x_1(t) \Rightarrow y_1(t) \text{ AND } x_2(t) \Rightarrow y_2(t), \text{ THEN } ax_1(t) + bx_2(t) \Rightarrow ay_1(t) + by_2(t)$$

C) 1) $V(t) = L \frac{di(t)}{dt} \Leftrightarrow i(t) = \frac{1}{L} \int_{-\infty}^t v(t) dt$

2) $i(t) = C \frac{dv(t)}{dt} \Leftrightarrow v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt$

D) NORMAL FORM:

$$\frac{dq_1(t)}{dt} = a_{11}(t)q_1(t) + a_{12}(t)q_2(t) + \dots + a_{1n}(t)q_n(t) + b_1(t)x(t)$$

$$\frac{dq_2(t)}{dt} = a_{21}(t)q_1(t) + a_{22}(t)q_2(t) + \dots + a_{2n}(t)q_n(t) + b_2(t)x(t)$$

$$\frac{dq_n(t)}{dt} = a_{n1}(t)q_1(t) + a_{n2}(t)q_2(t) + \dots + a_{nn}(t)q_n(t) + b_n(t)x(t)$$

$$Y(t) = c_1(t)q_1(t) + c_2(t)q_2(t) + \dots + c_n(t)q_n(t)$$

II) CHAPTER 3: REPRESENTATION OF SIGNALS

A) 1) ENERGY SIGNAL $\Rightarrow -\infty < \int_{-\infty}^{\infty} x^2(t) dt < \infty$

$$E = \int_{t_1}^{t_2} x^2(t) dt$$

2) POWER SIGNAL $\Rightarrow 0 < \lim_{T \rightarrow \infty} \frac{1}{2T} \int_{-T}^T x^2(t) dt < \infty$

$$P_{AVE} = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} x^2(t) dt$$

B) 1) $x(t) = \sum_{n=0}^M a_n \phi_n(t)$

2) ORTHOGONAL $\Rightarrow \int_{t_1}^{t_2} \phi_n(t) \phi_k(t) dt = 0 ; k \neq n$

FINALITY OF COEFFICIENTS $= \lambda_n ; k = n$

3) $a_n = \frac{1}{\lambda_n} \int_{t_1}^{t_2} \phi_n(t) x(t) dt$

4) INTEGRAL SQUARE ERROR $\Rightarrow I = \int_{t_1}^{t_2} (x(t) - \hat{x}(t))^2 dt$

5) ERROR ENERGY/SIGNAL $E_N = 1 - \frac{1}{E} \sum_{n=0}^M \lambda_n a_n^2$

6) FOURIER SERIES:

a) $e^{\pm jn\omega_0 t} = \cos n\omega_0 t \pm j \sin n\omega_0 t$

b) $\omega_0 = \frac{2\pi}{T}$

c) $\phi_n(t) = e^{jn\omega_0 t}$

d) $\lambda_n = T$

e) $a_n = \frac{1}{T} \int_{t_1}^{t_1+T} x(t) e^{-jn\omega_0 t} dt$

f) $x(t) = \sum_{n=-\infty}^{\infty} a_n e^{jn\omega_0 t}$ (F.S.E = $1 - \frac{1}{E} \sum_{n=-M}^M \lambda_n |a_n|^2$)

(CONT.)

III) FROM CLASS NOTES

PARSEVAL'S THEOREM

$$\int_{t_1}^{t_2} x^2(t) dt = \sum_{n=0}^{\infty} a_n^2 \lambda_n = E$$


TEST # 2; GRAM FORMULAS

IV) CHAPT. 3: SINGULARITY FUNCTIONS

A)  $r(t)$

B)  $\mu(t) = \frac{dr(t)}{dt}$ $\int_{-\infty}^{\infty} \mu(t) dt = r(t)$

C)  $\delta(t) = \frac{d\mu(t)}{dt}$ $\int_{-\infty}^{\infty} \delta(t) dt = 1 = \mu(t)$

D)  $\delta(bt) = \frac{1}{|b|} \delta(t)$
 $\delta'(t) = \frac{d\delta(t)}{dt}$

V) CHAPT. 4: CONVOLUTION

A) $f(t) = \int_{-\infty}^{\infty} f(\lambda) \delta(t-\lambda) d\lambda$

B) $f_1(t) * f_2(t) = \int_{-\infty}^{\infty} f_1(\lambda) f_2(t-\lambda) d\lambda$

C) TRAPEZOIDAL INTEGRATION PLUG

$$\int = \frac{\Delta t}{2} [Y_0 + 2Y_1 + 2Y_2 + 2Y_3 + \dots + 2Y_{n-1} + Y_n]$$

D) CONVOLUTION ALGEBRA

1) $f_1 * f_2 = f_2 * f_1$

4) $f(t) * \delta(t) = f(t)$

2) $f_1 * (f_2 * f_3) = (f_1 * f_2) * f_3$

5) $f(t) * \mu(t) = \int_{-\infty}^t f(\lambda) d\lambda$

3) $f_1 * (f_2 + f_3) = f_1 * f_2 + f_1 * f_3$

6) $f(t) * \delta'(t) = f'(t)$

E) SUPERPOSITION INTEGRAL

1) $w(t) = \mu(t) * h(t)$

2) $y(t) = x'(t) * w(t) = x(t) * w'(t) = x''(t) * \int_{-\infty}^t w(\lambda) d\lambda$

VI) FOURIER TRANSFORMS

A) $\tilde{F}[f(t)] = F(j\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$

B) $\tilde{F}^{-1}[F(j\omega)] = f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(j\omega) e^{j\omega t} d\omega$

C) $F(j\omega) = A(\omega) e^{j\theta(\omega)} \ni A(\omega) = |F(j\omega)|$

$\theta(\omega) = \tan^{-1} \left[\frac{\text{Im } F(j\omega)}{\text{Re } F(j\omega)} \right]$

D) $\int_{-\infty}^{\infty} f(t) dt \stackrel{\text{DURATION}}{=} \frac{f(0)}{F(0)} \stackrel{\text{BW}}{\cdot} \int_{-\infty}^{\infty} F(j\omega) d\omega = 2\pi$

E) $\tilde{F} \left\{ \frac{d^n f(t)}{dt^n} \right\} = (j\omega)^n F(j\omega); \tilde{F}[\delta(t-t_0)] = e^{-j\omega t_0}$

F) ELEMENTARY PROPERTIES OF FOURIER

TRANSFORMS:

1) $f(t) = f_e(t) + f_o(t)$
 $f_e(t) = \frac{f(t) + f(-t)}{2}$
 $f_o(t) = \frac{f(t) - f(-t)}{2}$
 $f_o(t) =$

2) FOR CAUSAL SYSTEMS
a) $f_e(t) = f_o(t) = f(t)/2$

b) $|F(j\omega)| \neq 0$

TEST # 3 ; GRAM FORMULAS

I) CHAPTER 4: FOURIER TRANSFORMS

1) FOURIER TRANSFORM: $\tilde{F}\{f(t)\} = F(j\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$
 $F(j\omega) = A(\omega) e^{j\theta(\omega)} \Leftrightarrow A(\omega) = |F(j\omega)| ; e^{j\theta(\omega)} = \tan^{-1} \left[\frac{\text{Im} F(j\omega)}{\text{Re} F(j\omega)} \right]$


2) INVERSE TRANSFORM: $\tilde{F}^{-1}[F(j\omega)] = f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(j\omega) e^{j\omega t} d\omega$

3) DIRICHLET CONDITIONS:

- $f(t)$ MUST BE ABSOLUTELY INTEGRABLE $\Rightarrow \int_{-\infty}^{\infty} |f(t)| dt < \infty$
- $f(t)$ MUST HAVE FINITE MAX & MIN IN FINITE AREA INTERVAL
- $f(t)$ MUST HAVE FINITE DISCONTINUITIES IN FINITE INTERVAL

B) SIMPLE TRANSFORMS

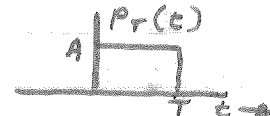1) $p_T(t) \Leftrightarrow A T e^{-j\frac{\omega T}{2}} \frac{\sin \omega T/2}{\omega T/2}$



2) $\underbrace{\int_{-\infty}^{\infty} f(t) dt}_{f(0)} \cdot \underbrace{\int_{-\infty}^{\infty} F(j\omega) d\omega}_{F(0)} = 2\pi$

EQUIVALENT DURATION; EQUIVALENT BANDWIDTH

3) $e^{-\alpha t} u(t) \Leftrightarrow \frac{1}{j\omega + \alpha}$

4) $e^{-\alpha |t|} \Leftrightarrow \frac{2\alpha}{\omega^2 + \alpha^2}$

5) $\tilde{F}\left[\frac{d^n}{dt^n} f(t)\right] = (j\omega)^n F(j\omega)$


6) $\left. \begin{aligned} F_e(j\omega) &= 2 \cdot \text{Re} [F_c(j\omega)] \\ F_o(j\omega) &= 2 \cdot \text{Im} [F_c(j\omega)] \end{aligned} \right\} f_c(t) \text{ IS CAUSAL}$

C) SYSTEM FUNCTION

1) $Y(j\omega) = X(j\omega) H(j\omega) \Rightarrow \tilde{F}\{f_1(t) * f_2(t)\} = F_1(j\omega) F_2(j\omega)$

2) $\delta(t) \Leftrightarrow 1$

3) $\frac{P_{X_1}}{P_{X_2}} \Big|_{\text{dB}} = 10 \log_{10} \frac{P_{X_1}}{P_{X_2}} = 20 \log_{10} \frac{X_1}{X_2}$

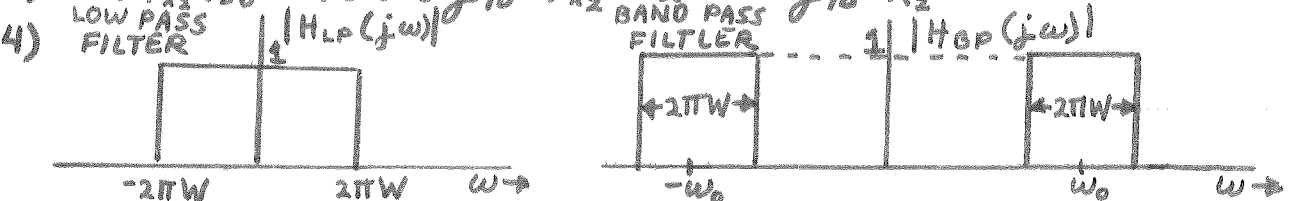

D) ENERGY SPECTRUM

1) PARSEVAL'S THEOREM $\Rightarrow E = \int_{-\infty}^{\infty} [f(t)]^2 dt = \frac{1}{2\pi} \int_{-\infty}^{\infty} |F(j\omega)|^2 d\omega$

2) $|F(j\omega)|^2 \Rightarrow$ ENERGY SPECTRUM

3) $|Y(j\omega)|^2 = |H(j\omega)|^2 |X(j\omega)|^2$

4) $|H(j\omega)|^2 \Rightarrow$ ENERGY TRANSFER FUNCTION

D) FOURIER TRANSFORMS MATHEMATICALLY

1) $\mathcal{F}\{f(at)\} \Leftrightarrow \frac{1}{|a|} F\left(\frac{\omega}{a}\right)$

2) DELAY: $\mathcal{F}\{f(t-t_0)\} \Leftrightarrow e^{-j\omega t_0} F(j\omega)$

3) MODULATION: $e^{j\omega_0 t} f(t) \Leftrightarrow F[j\omega - \omega_0]$

4) REVERSAL: $f(-t) \Leftrightarrow F(-j\omega)$

5) SYMMETRY: $F(j\omega) \Leftrightarrow 2\pi f(-\omega)$

$\frac{1}{2\pi} F(-\omega) \Leftrightarrow f(j\omega)$

E) FOURIER TRANSFORMS OF POWER SIGNALS

1) $1 \Leftrightarrow 2\pi \delta(\omega)$

2) $\sum_{n=-\infty}^{\infty} \delta(t-nT) \Leftrightarrow \frac{1}{T} \sum_{k=-\infty}^{\infty} \delta(j\omega - \frac{2\pi k}{T})$

F) CONVOLUTION ON THE FREQ. DOMAIN


~~$f_1(t) f_2(t) = F_1(j\omega) \otimes F_2(j\omega)$~~
 $f_1(t) f_2(t) \Leftrightarrow F_1(j\omega) * F_2(j\omega)$

G) SAMPLING THEOREM

1) SAMPLING $> 2W$ HZ \Rightarrow 2) SAMPLING $< \frac{1}{2W}$ SEC

Block Diagrams Block Diagrams

Graph of $y = Ax$

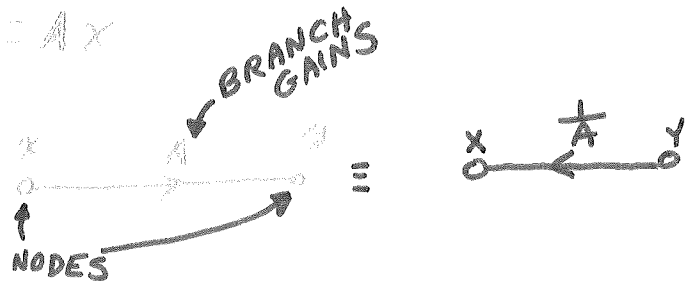

Graph of $y = Ax + Bk$



Graph of $y = (1 + A)x - 2y$



$$a_1 = z_{11} i_1 + z_{12} i_2$$

$$a_2 = z_{21} i_1 + z_{22} i_2$$

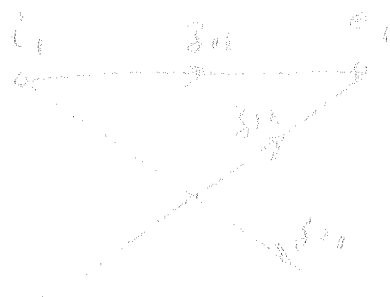


FIGURE 11

Equation:


Two graphs are no different because the graphs & the inputs are the same. Because each has 4 inputs the two voltages. Just the distance is the same as graph 6.

A more complicated set of equations:

$$x = 3x + 4y$$

$$x = 2k + y$$

The graph would be

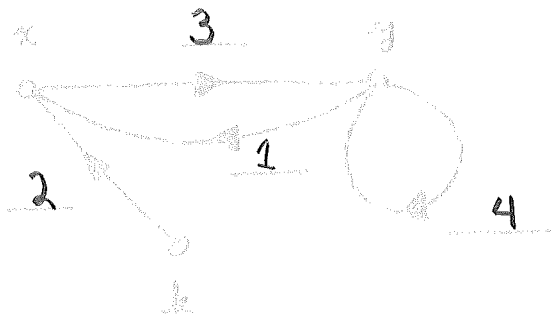


Draw the blanks in this graph using the equations above.


Draw that the graph has one input. This is the same as the variable k.

Let us investigate the gain of a common emitter amplifier in which the emitter bypass capacitor is removed.

CIRCUIT

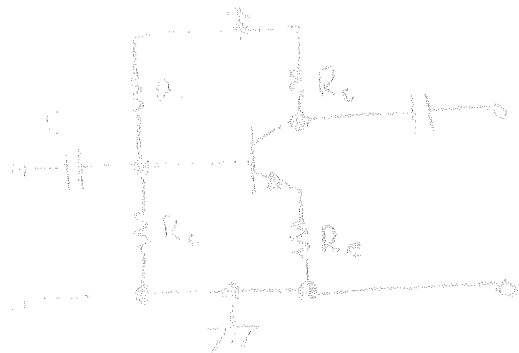

MODEL

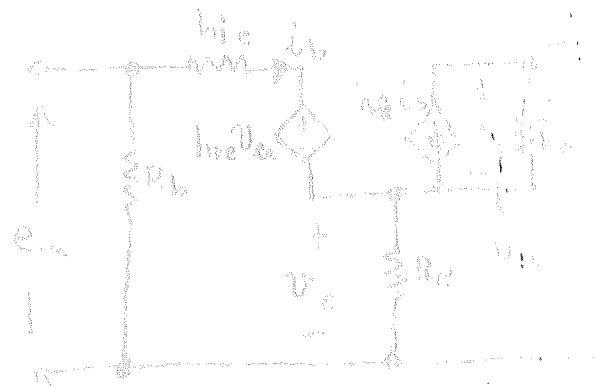


Equations

- (1) $e_{in} = i_b R_b$
- (2) $e_{in} = h_{ie} i_b + h_{oe} V_{ce}$
- (3) $V_{ce} = e_o - v_e$
- (4) $v_e = (i_b + i_c) R_e$
- (5) $i_b = \frac{e_{in} - h_{ie} i_b - h_{oe} v_e}{h_{ie}}$

note here that we have 5 unknowns in each equation here written to find out the unknowns in the equations above if all unknowns are satisfied.

As a step in solving this system of equations, you will draw the signal flow graph.

Write one equation at a time.

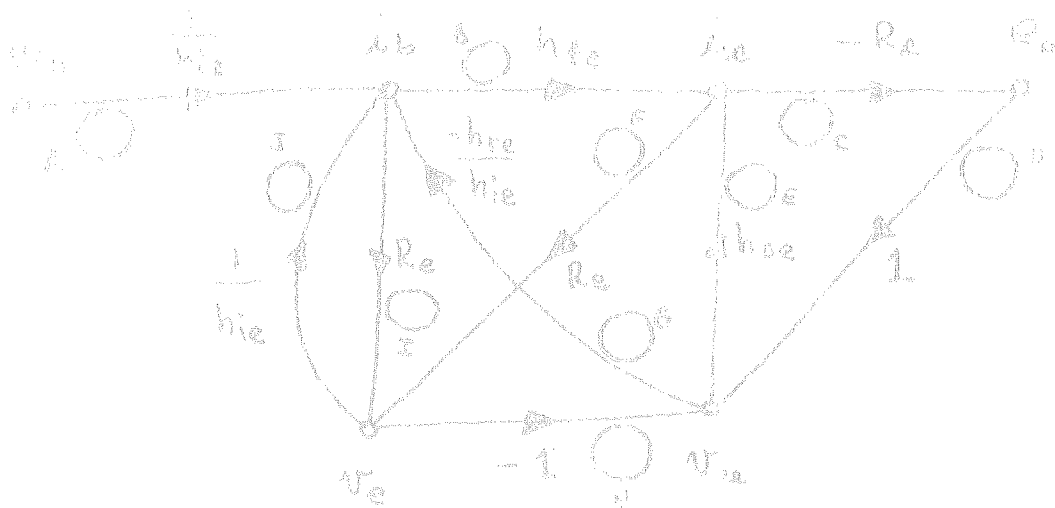

Draw in the complete signal flow graph for the network
 study it carefully. Note there are 5 unknowns and
 one known quantity, e_{in} .

In the circles drawn for each signal path
 place the equation number from the equations
 previous page.


The numbers in the circles in the previous part


- A - 5
- B - 2
- C - 1
- D - 3
- E - 2
- F - 4
- G - 5
- H - 3
- I - 4
- J - 5

Draw the signal flow graph for the equations shown.


$$\left. \begin{aligned} x &= -5a + 2y \\ a &= 5x + 17b \\ y &= a + x \\ b &= x - 3 \end{aligned} \right\}$$

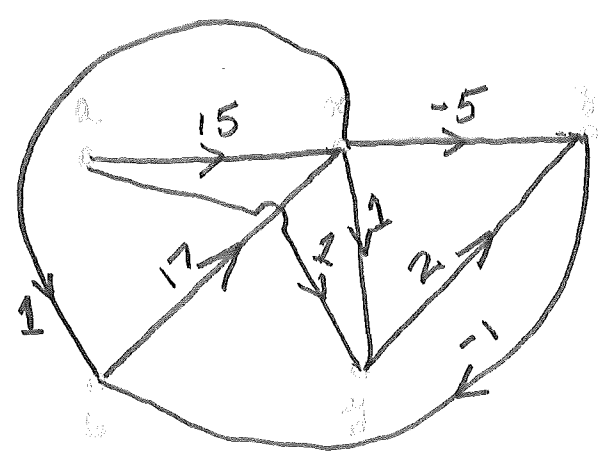For these equations, the input parameter is _____




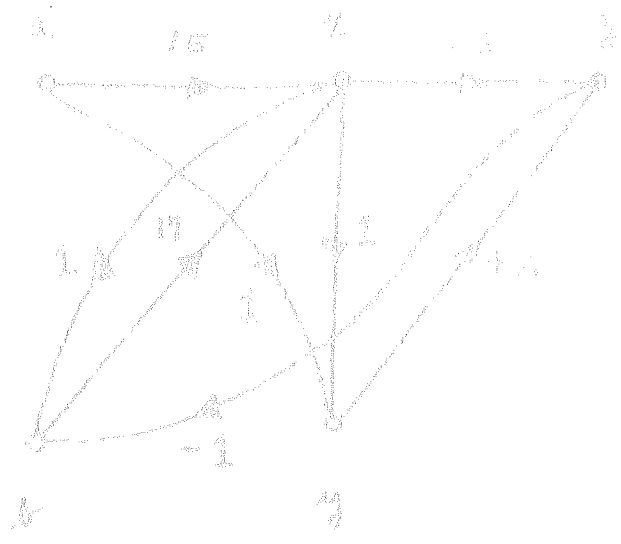

from network this may be redrawn below.

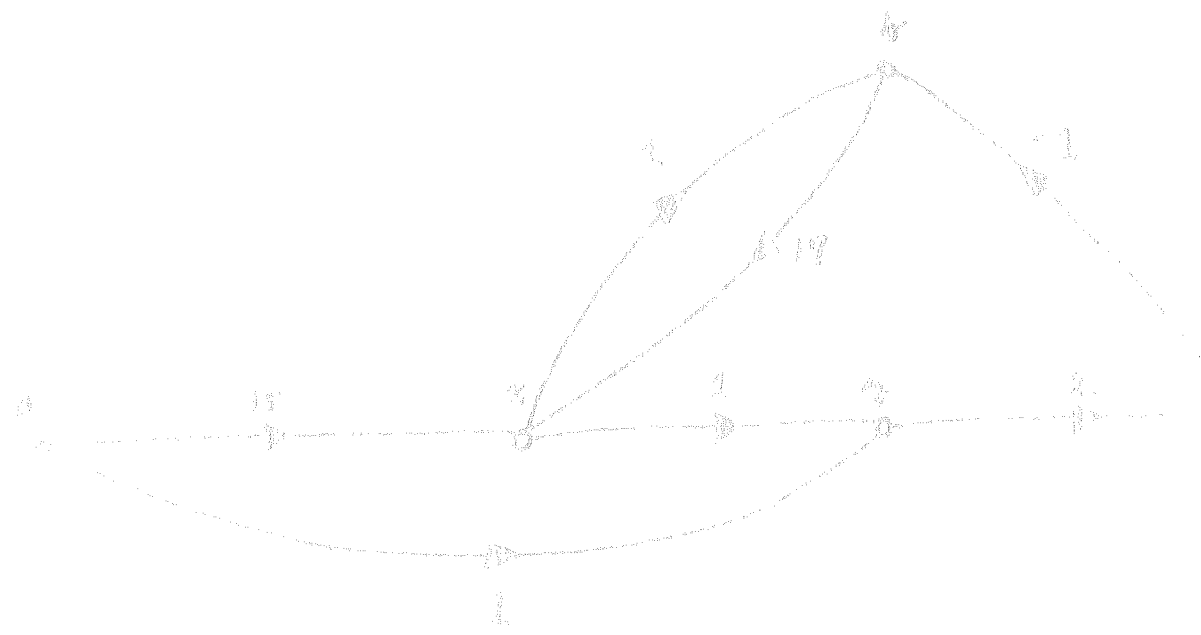

F low graph nodes cond.

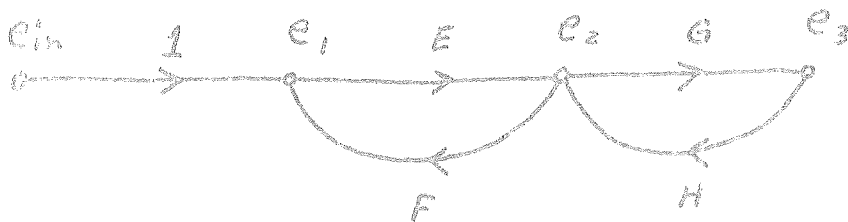

$$e_1 = e_{in} + Fe_2$$

$$Ee_1 = Ee_{in} + EFe_2$$

$$e_2 = Ee_1 + He_3 = Ee_{in} + EFe_2 + He_3$$

$$e_3 = Ge_2 \quad \frac{e_o}{G} = Ee_{in} + EFe_2 + He_3$$


$$\frac{e_o}{e_{in}} = \frac{E}{\frac{1}{G} - \frac{FE}{G} - H} = \frac{EG}{1 - (EF + GH)}$$

Rule for finding gain:

Forward gain


$$\text{Gain} = \frac{\text{Forward gain}}{1 - \sum (\text{loop gains})_{1 \text{ at a time}} + \sum (\text{loop gains})_{2 \text{ at a time, non-touching}} - \sum (\text{loop gains})_{3 \text{ at a time, non-touching}} + \sum (\text{loop gains})_{4 \text{ at a time, non-touching}} \dots}$$

Example

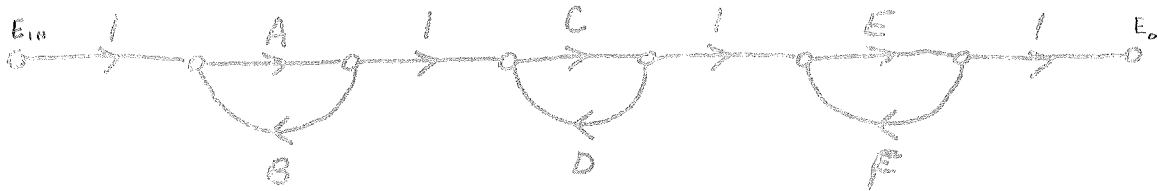

$$\frac{E_0}{E_1} = \frac{A}{1-AB} \cdot \frac{C}{1-CD} \cdot \frac{E}{1-EF}$$
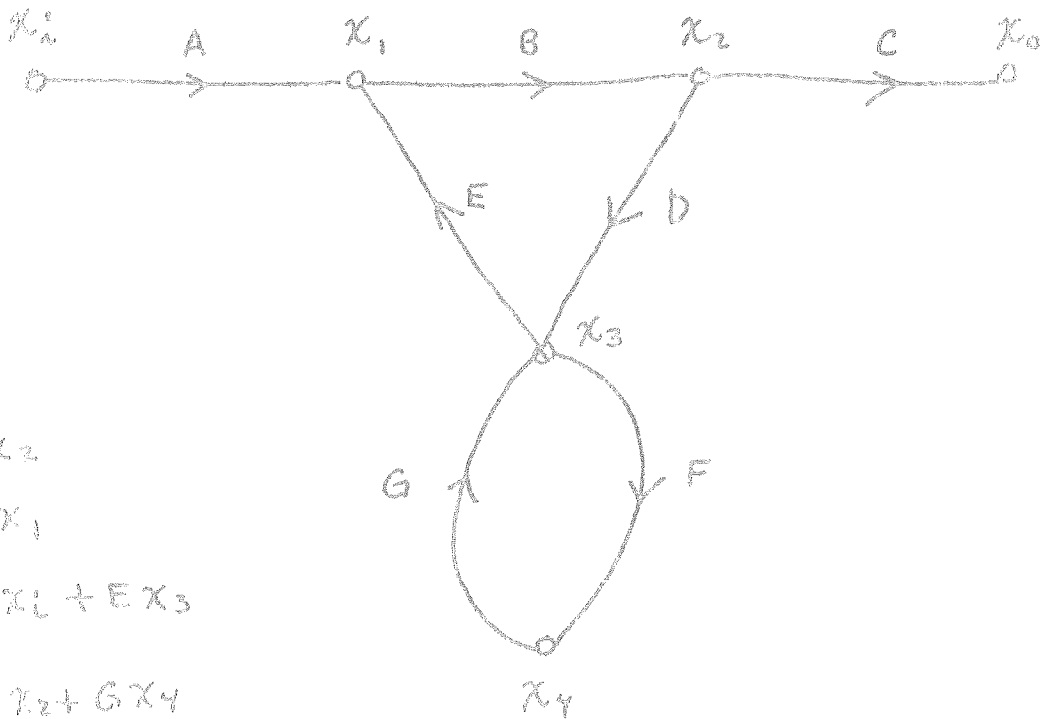
$$= \frac{ACE}{1 - (AB + CD + EF) + (ABCD + ABEF + CDEF) - (ABCDEF)}$$



$$X_0 = CX_2$$

$$X_2 = BX_1$$

$$X_1 = AX_1 + EX_3$$

$$X_3 = DX_2 + GX_4$$

$$X_4 = FX_3$$

$$\frac{X_o}{X_i} = \frac{ABC(1-GF)}{1-(BED+GF)}$$

loop not connected with a forward path

all terms in denominator not connected to forward path.

Final expression for Gain

$$\text{Gain} = \frac{G_1 \Delta_1 + G_2 \Delta_2 + \dots}{\Delta} = \frac{\sum_{i=1}^{n_F} G_i \Delta_i}{\Delta}$$

Δ = same denominator as before

G_i = forward path gain

Δ_i = all terms in denominator made ^{up} of loops not touching ~~crossed~~ i^{th} forward path.

$$\frac{d}{ds} = 1$$

$$K_1 \frac{2(s+2)}{(s+2)^2}$$

$$K_2 \frac{1}{(s+5)}$$


$$K_3 \frac{1}{(s+2)}$$

$$\begin{aligned} K_2 + K_3 &= 1 \\ s = -5 \Rightarrow \\ -4 &= 9K_1 - 3K_3 \\ s = 2 \Rightarrow -1 &= 3K_2 \Rightarrow K_2 = -\frac{1}{3} \end{aligned}$$

X


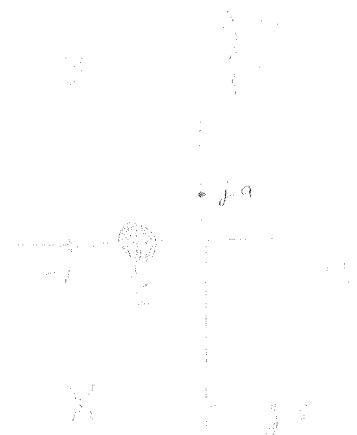
$$= \frac{s + \frac{1}{2}}{(s+1)^2 + 9} - \frac{s + \frac{1}{2}}{(s+1-j3)(s+1+j3)}$$






for $\omega = 0$ is not with given only

is a (b) high-pass filter

is a low-pass filter, is band-pass filter

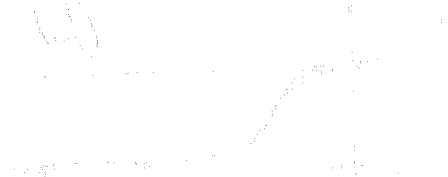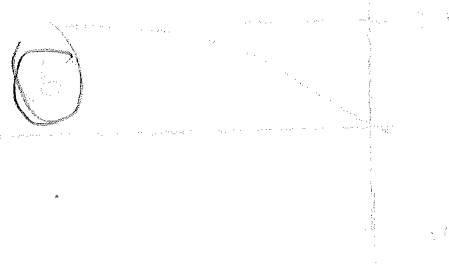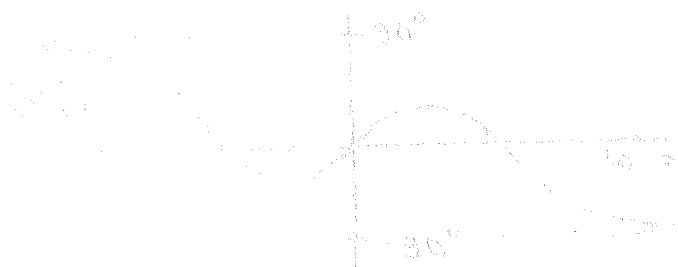for high ω is not given by $e^{j\theta} = \tan^{-1} \frac{j\omega}{2} + \tan^{-1} j(\omega+3) - \tan^{-1} j(\omega-3)$




1. June 1964

2. 1964

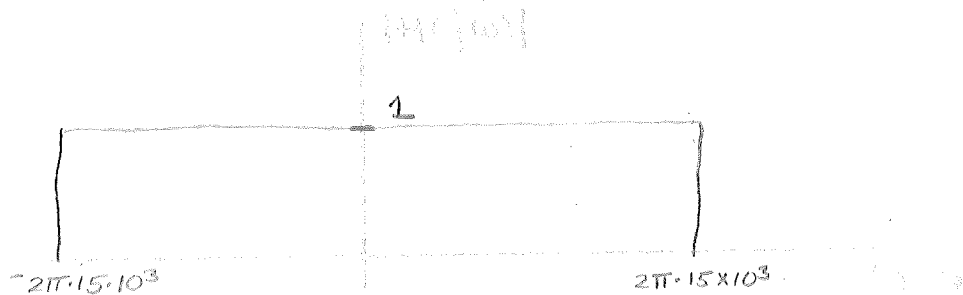3. 1964

The two main components are either a wave that can
 be sampled upon to obtain the transfer function of a filter
 or a filter which they can use to reconstruct a digital
 signal. The main problem is to sample the signal at a rate
 which is high enough to reconstruct the signal without
 aliasing. The main problem is to sample the signal at a rate
 which is high enough to reconstruct the signal without
 aliasing.



For a given filter, what minimum sampling rate is required
 for a good reproduction of the signal?

$$> 30 \times 10^3 \text{ Hz} \Rightarrow < \frac{1}{30} \times 10^{-3} \frac{\text{SEC}}{\text{SAMPLE}}$$

The signal is sampled and the samples from earth, recorded, and
 the signal is then in digital form at the minimum sampling
 rate. The signal is then sampled at any other sample point on the tape
 and the signal is then reproduced in digital form at the
 original sampling rate. The signal is then reproduced in digital form at
 the original sampling rate.



JUNE'S
 → WILL HAVE COMPLETE OVERLAP, WITH THE
 HIER FREQUENCIES PROBABLY
 SUFFERING MOST

Derive an integral representation of $\Gamma(s)$ for $\sigma > 0$ and $\sigma > -d$

$$\int_0^{\infty} t e^{-(s+d)t} dt$$

$$\frac{-t}{s+d} e^{-(s+d)t} \Big|_0^{\infty} + \int_0^{\infty} \frac{1}{s+d} e^{-(s+d)t} dt$$

$$e^{-j\omega(\infty)} e^{-d(\infty)} e^{-d\infty} \quad \sigma+d > 0$$

CONV $\sigma > -d$

(b) Find $\mathcal{L}\left\{\int_0^t \lambda e^{-3\lambda} d\lambda\right\}$

$$\int_0^t \lambda e^{-3\lambda} d\lambda$$

$$= \frac{\lambda}{3} e^{-3\lambda} \Big|_0^t + \int_0^t \frac{1}{3} e^{-3\lambda} d\lambda$$

$$= \frac{\lambda}{3} e^{-3\lambda} \Big|_0^t - \frac{1}{9} [e^{-3\lambda}]_0^t$$

$$= -\left[\frac{t}{3} e^{-3t}\right] - \frac{1}{9} [e^{-3t} - 1]$$

$$= -\frac{t}{3} e^{-3t} - \frac{1}{9} e^{-3t} + \frac{1}{9}$$

$$\mathcal{L}\{\cdot\} = \frac{d}{dt} \frac{1}{s+3} - \frac{1}{9(s+3)} + \frac{1}{9s}$$

$$= \frac{-1}{(s+3)^2} - \frac{1}{9(s+3)} + \frac{1}{9s}$$

(1) Find the Laplace transform of $t e^{-3t}$ using the definition of Laplace transform.

$$\frac{d}{dt} t e^{-3t} = t e^{-3t} \delta(t) + \left(\frac{d}{dt} t e^{-3t} \right) \mu(t) = (3t e^{-3t} + e^{-3t}) \mu(t)$$

$$1) \mathcal{L}\{t e^{-st}\} = -\frac{d}{ds} \frac{1}{s+d} = \frac{+1}{(s+d)^2} = \frac{1}{(s+3)^2}$$

$$2) \mathcal{L}\{t e^{-st}\} = \int_0^{\infty} t e^{-st} e^{-3t} dt$$

$$= \int_0^{\infty} t e^{-t(s+3)} dt$$


$$u = t \quad dv = e^{-t(s+3)} dt$$

$$du = dt \quad v = \frac{e^{-t(s+3)}}{-(s+3)}$$

$$\Rightarrow F(s) = \left[\frac{-t e^{-t(s+3)}}{(s+3)} \right]_0^{\infty} + \int_0^{\infty} \frac{e^{-t(s+3)}}{(s+3)} dt$$

$$= \left[\frac{-e^{-t(s+3)}}{(s+3)^2} \right]_0^{\infty} = \frac{1}{(s+3)^2}$$

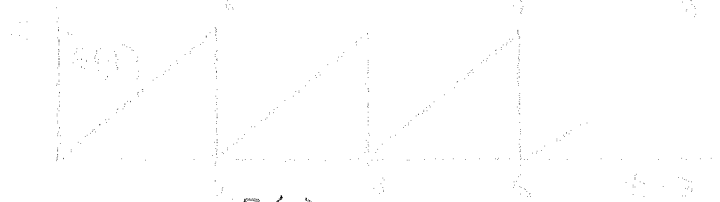(2) Find the Laplace transform of the unit triangle wave



$$F(s) = \frac{F_1(s)}{1 - e^{-sT}}$$

$$F_1(t) = \frac{5}{2}t - \frac{5}{2}t \mu(t-2)$$

$$\mathcal{L}\{F_1(t)\} = \int_0^2 \frac{5}{2} t e^{-st} dt$$

$$u = \frac{5}{2}t \quad dv = e^{-st} dt$$

$$du = \frac{5}{2} dt \quad v = \frac{e^{-st}}{-s}$$

$$\left[\frac{-5}{2s} t e^{-st} \right]_0^2 + \frac{5}{2s} \int_0^2 e^{-st} dt$$

$$\frac{5}{s} e^{-2s} - \frac{5}{2s^2} [e^{-2s} - 1]$$

$$\therefore F(s) = \frac{e^{-2s} \left[\frac{5}{s} + \frac{5}{2s^2} \right] + \frac{5}{2s^2}}{1 - e^{-2s}} = \frac{-e^{-2s} [10s + 5] + 5}{2s^2 [1 - e^{-2s}]}$$

$$H(s) = \frac{s^2 + 2s}{(s+4)(s^2+16)}$$

Expand $H(s)$ in partial fraction form and find $f(t)$.

$$H(s) \cdot (s+4)(s^2+16) = S(S+2)$$

$$\frac{S(S+2)}{(s+4)(s+j4)(s-j4)} = \frac{A}{s+4} + \frac{B}{s+j4} + \frac{C}{s-j4}$$

$$S(S+2) = A(s+j4)(s-j4) + B(s+4)(s-j4) + C(s+4)(s+j4)$$

$$S = -4 \Rightarrow B = A(32) \Rightarrow A = \frac{1}{4}$$

$$S = j4 \Rightarrow j4(j4+2) = -8 + j8 = C(j4+4)(j8) \\ = -32C + j32C \Rightarrow C = \frac{1}{4}$$

$$S = -j4 \Rightarrow -j4(-j4+2) = 16 - j8 = B(-j4+4)(-j8) \\ = j88(4-j4) = j88$$

Using the initial value theorem, find $f(0)$.

$$\lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow +\infty} s F(s)$$


$$= \lim_{s \rightarrow +\infty} \frac{s^2(s+2)}{(s+4)(s^2+16)} \rightarrow \frac{s^2 s}{s s^2} = 1$$

Q1


Transfer function $H(s) = \frac{(s+1-j2)(s+1+j2)}{(s+2-j)(s+2+j)}$

Sketch the pole-zero plot of $H(s)$

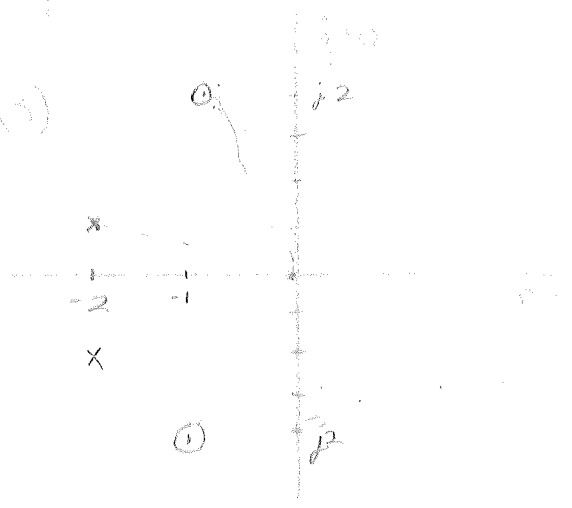
$$\frac{(s+1-j2)(s+1+j2)}{(s+2-j)(s+2+j)}$$



Sketch $|H(j\omega)|$ vs ω showing values at the origin and $\pm\infty$. Indicate roughly locations of maxima and minima.

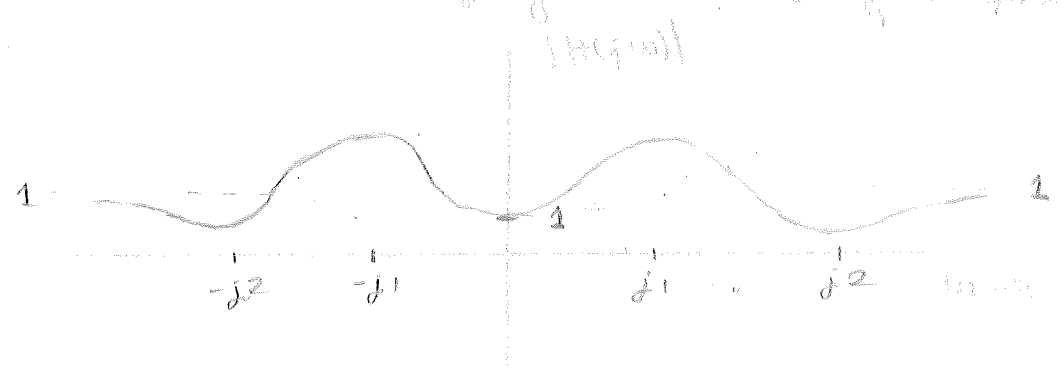

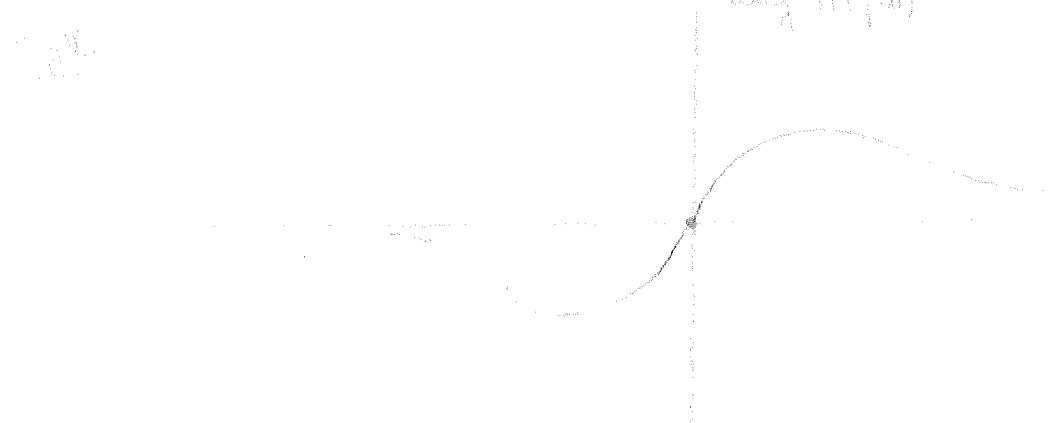Sketch $\angle H(j\omega)$ vs ω showing values at the origin and $\pm\infty$



$$\frac{s(s+2)}{(s+1)(s-j2)(s+j2)} = \frac{A}{s+1} + \frac{B}{s-j2} + \frac{C}{s+j2}$$

$$s(s+2) = A(s^2+4) + B(s+j2)(s+1) + C(s-j2)(s+1)$$

$$s=-1 \Rightarrow -1 = A(5) \Rightarrow A = -1/5$$

$$s=j2 \Rightarrow j2(j2+2) = -4+j4 = Bj2(j2+1) = Bj^4 + B4 \Rightarrow B = -1$$

$$s=-j2 \Rightarrow +j2(2-j2) = 4j+4 = C(+j4)(1-j2) = Cj^4 + C8 \Rightarrow C = 0$$

$$\therefore F(s) = \frac{-1}{5(s+1)} - \frac{1}{s-j2}$$

$$\Rightarrow f(t) = \mathcal{L}^{-1}\{F(s)\} = -\frac{1}{5}e^{-t} - e^{j2t}$$

$$\frac{s(s+2)}{(s+1)(s^2+4)} = \frac{A}{s+1} + \frac{B}{s^2+4}$$

$$s(s+2) = A(s^2+4) + B(s+1)$$

$$s=1 \Rightarrow -1 = 5A \Rightarrow A = -1/5$$

$$s=j2 \Rightarrow j2(j2+2) = B(j2+1)$$


$$-4+j4 = B+j2B$$

$$s+s+2 = 2s+2 = 2As+B$$

$$2s+2 = \frac{-2}{5}s+B$$


$$\frac{12}{5}s+2 = B$$

ARG!

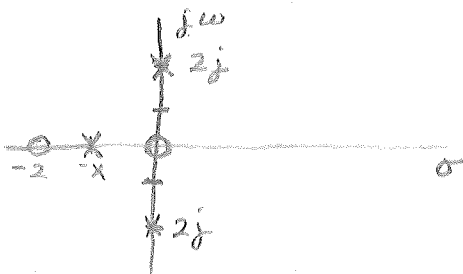

$$s^2+4 \Rightarrow (s+j2)(s-j2)$$

X-38)

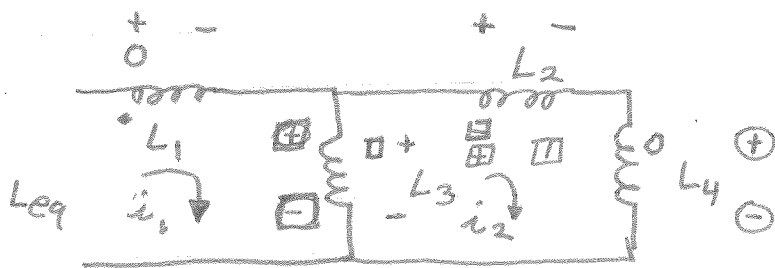

I) SIGNALS & SYSTEMS

A) INTRODUCTION-WHILE GENERAL DEFINITIONS OF SIGNALS & SYSTEMS IS VAGUE; ENGINEER SHOULD BE FAMILIAR WITH IN SPECIFIC UNDERTAKINGS

B) SYSTEMS-WHAT THEY ARE AND WHAT THEY DO

1) GENERAL DEFINITION: IT CONSISTS OF A GROUP OF OBJECTS WHICH INTERACT WITH ONE ANOTHER AND ARE ASSEMBLED IN A MANNER TO ACHEIVE A DESIRED OBJECTIVE.

2) MOST SYSTEM ANALYSIS CONSISTS OF A PORTION OF A MORE COMPLEX SYSTEM

3) ENGINEER IS RESPONSIBLE FORE DESIGN, PRODUCTION, & ANALYSIS OF SYSTEMS THRU MATHEMATICAL TOOLS

C) SIGNALS

1) SIGNALS DIRECT THE SYSTEM

2) INPUT/OUTPUT TYPE

3) MUST BE ABLE TO REPRESENT SIGNAL MATHEMATICALLY

D) SYSTEM ANALYSIS AND DESIGN

1) WHY ANALYSIS IS IMPORTANT

a) CHEAPER THAT EXPERIMENT

b) DETERMINING FEASIBILITY

c) MAY ASSUME IMPOSSIBLE OR DANGEROUS CONDITIONS

d) IMPORTANT PART OF DESIGN SYSTEM

2) PROBLEMS IN SYSTEM DESIGN

a) DETERMINE CHARACTERISTICS THAT WILL YEILD DESIRED RESPONSE FROM AN INPUT

b) DETERMINING BEST HARDWARE TO FIT MATHEMATICAL MODEL



(5)

(5)

(5)

II) SYSTEM REPRESENTATION AND ANALYSIS

A) INTRODUCTION

B) SYSTEM REPRESENTATION

- 1) NECESSARY TO REPRESENT SYSTEM MATHEMATICALLY BY USE OF A MATHEMATICAL MODEL
- 2) MATHEMATICAL MODEL ALWAYS AN APPROXIMATION
- 3) MATH MODEL IS A COMPROMISE BETWEEN ACCURACY & MATHEMATICAL SIMPLICITY

C) THE MATHEMATICAL MODEL

1) BLOCK DIAGRAM



b) MATH MODEL FOR SYSTEM IS EQUATION RELATING $x(t)$ AND $y(t)$ $[y(t) = f[x(t)]]$

- 2) MOST BASIC MATH MODEL IS DIFF. EQUATION
- 3) FIRST ORDER DIFF. EQUATION KNOWN AS "NORMAL FORM" OF SYSTEMS EQUATION

D) CLASSIFICATION OF SYSTEMS

- 1) ORDER OF SYSTEM - REFERS TO ORDER OF DIFF. EQUATION USED TO DESCRIBE THE SYSTEM
- 2) CAUSAL & NON-CAUSAL
 - a) CAUSAL SYSTEM - RESPONSE IS NOT A FUNCTION OF FUTURE INPUT (ASSUMED TO APPLY TO SYSTEMS EQUATION)
 - b) NON-CAUSAL - (NON PHYSICAL OR ANTICIPATORY) DON'T EXIST PHYSICALLY.
- 3) LINEAR & NON-LINEAR (D.E.)
 - a) LINEAR $\Leftrightarrow y_1(t) = f[x_1(t)]$ AND $y_2(t) = f[x_2(t)]$
THEN $a y_1(t) + b y_2(t) = a f[x_1(t)] + b f[x_2(t)]$
 - b) SUPERPOSITION APPLIES TO LINEAR SYSTEMS
- 4) FIXED VS. TIME VARIANT SYSTEMS
 - a) FIXED SYSTEMS HAVE CONSTANT COEFFICIENTS IN THEIR DIFFERENTIAL EQUATIONS.
ALSO $y(t) \leftarrow x(t) \Rightarrow y(t + \tau) \leftarrow x(t + \tau)$

4

5) LUMPED PARAMETER VS. DISTRIBUTED PARAMETER SYSTEM

a) LUMPED \Rightarrow DIFFERENTIAL EQUATION

b) DIST \Rightarrow PARTIAL DIFFER. EQUATIONS

6) CONTINUOUS VS. DISCRETE TIME SYSTEM

a) CONTINUOUS \Rightarrow DIFFERENTIAL EQUA.

b) DISCRETE TIME \Rightarrow DIFFERENCE EQN.

(FOR SHORT INSTANCES IN TIME)

7) INSTANTANEOUS VS. DYNAMIC SYSTEM

a) INSTANTANEOUS SYSTEM DOES NOT DEPEND ON FUTURE OR PAST EXCITATIONS OF THE SYSTEM

b) DYNAMIC SYSTEMS HAVE MEMORY (L & C)

8) THOSE SYSTEMS DISCUSSED IN THIS

COURSE ARE 1) CAUSAL, 2) LINEAR,

3) FIXED, 4) LUMPED PARAMETER 5) CONTINUOUS

TIME, 6) \neq DYNAMIC

MATH-WISE 1) ORDINARY 2) LINEAR,

3) D.E. WITH CONSTANT COEFF.

E) EXAMPLES OF MATHEMATICAL MODELS OF SYSTEMS

1) REVIEW

a) RESISTANCE

$$v(t) = R i(t)$$

$$i(t) = G v(t) ; G = 1/R$$

b) INDUCTANCE

$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\lambda) d\lambda ; \Gamma = 1/L$$

c) CAPACITANCE

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\lambda) d\lambda ; S = 1/C$$

$$i(t) = C \frac{dv(t)}{dt}$$

d) AMPLIFIER

$$v_2(t) = K v_1(t)$$

e) DELAY: $v_2(t) = v_1(t - \tau)$; $\tau > 0$

f) INTEGRATOR: $v_2(t) = \int_{-\infty}^t v_1(\lambda) d\lambda$

2) AMPLIFIER EXAMPLE



b) $v_1(t) = v_2(t) + \frac{1}{C} \int_{-\infty}^t i(\lambda) d\lambda$

$v_i(t) = v_1(t) - R i(t)$

$v_2(t) = -K v_i(t)$

c) $\therefore (K+1)RC \frac{dv_2(t)}{dt} + v_2(t) = -K v_1(t)$

THIS IS THE MATH MODEL FOR THE SYSTEM

F) THE NORMAL FORM OF SYSTEM EQUATIONS

1) FOR n EQUATIONS, MUST BE n UNKNOWN

2) UNKNOWN TIME FUNCTIONS CALLED "STATE VARIABLES"

b) IN AN ELECTRICAL SYSTEM, STATE VARIABLES REPRESENT v & i

2) IF ONLY ONE INPUT, WITH $q_n(t)$ AS STATE VARIABLES:

a) $\frac{dq_1}{dt} = a_{11}(t)q_1(t) + (a_{12}(t)q_2(t) + \dots + a_{1n}(t)q_n(t) + b_1(t)x(t)$

$\frac{dq_2}{dt} = a_{21}(t)q_1(t) + a_{22}(t)q_2(t) + \dots + a_{2n}(t)q_n(t) + b_2(t)x(t)$

$\frac{dq_n}{dt} = a_{n1}(t)q_1(t) + a_{n2}(t)q_2(t) + \dots + a_{nn}(t)q_n(t) + b_n(t)x(t)$

b) IF THERE IS A

SINGLE OUTPUT $y(t)$, THEN

$y(t) = c_1(t)q_1(t) + c_2(t)q_2(t) + \dots + c_n(t)q_n(t)$

c) THE ABOVE EQUATIONS FORM A MATHEMATICAL MODEL FOR THE GENERAL n TH ORDER, TIME VARYING SYSTEM (LINEAR)

d) IF SYSTEM IS FIXED $a_i(t)$, $b_i(t)$ & $c_i(t)$ ARE FIXED.

3) WHY THIS FORM IS USEFUL

a) MAY USE MATRICES

b) MAY BE APPLIED TO NON-LINEAR

c) STRAIGHTFORWARD SOLUTION

d) BETTER UNDERSTANDING OF

WHAT'S HAPPENING IN SYSTEM

e) COMPUTER USE

f) MULTIPLE INPUT/OUTPUT

g) INITIAL CONDITIONS DETERMINATION

1) SUPERPOSITION - ASSUME INITIAL

CONDITIONS ARE 0, AND ADD

RESPONSE TO RESULT

2) DERIVATIVES OF INPUT SIGNAL,

USED WITH n^{th} ORDER EQUATIONS

3) INITIAL CONDITIONS ARISE

WHEN SOLVING NORMAL FORM

III) REPRESENTATION OF SIGNALS

A) GENERAL METHODS OF SIGNAL REPRESENTATION - SHOULD BE QUANTITATIVE

B) CLASSIFICATION OF SIGNALS

1) PERIODIC & NON-PERIODIC

2) RANDOM & NON-RANDOM (PREDICTION)

3) ENERGY & POWER SIGNALS

a) FOR CURRENT, VOLTAGE

$$E = \int_{t_1}^{t_2} \frac{e^2(t)}{R} dt \quad \text{WATT SECONDS}$$

FOR CURRENT

$$E = \int_{t_1}^{t_2} R i^2(t) dt \quad \text{WATT SECONDS}$$

b) ENERGY SIGNAL DEFINED WHEN $x(t)$ FITS THE CONDITION:

$$\int_{-\infty}^{\infty} x^2(t) dt < \infty$$

c) POWER SIGNAL :

$$(1) P = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} x^2(t) dt$$

(2) MUST SATISFY CONDITION:

$$0 < \lim_{T \rightarrow \infty} \frac{1}{2T} \int_{-T}^T x^2(t) dt < \infty$$

d) SOME SIGNALS FIT BOTH

C) REPRESENTATION IN TERMS OF ELEMENTARY SIGNALS

1) BASIC FUNCTIONS - ELEMENTARY FUNC.

CHOSEN FOR THEIR SIMPLICITY & PROPERTIES

2) LINEAR COMBINATIONS OF BASIC FUNC.

a) WRITTEN $x(t) = \sum_{n=0}^{\infty} a_n \phi_n(t)$

b) FINALITY OF COEFFICIENTS: ANY a_n MAY BE COMPUTED INDEPENDENT OF ANY OTHER a_n

3) ORTHONORMAL:

$$a) \int_{t_1}^{t_2} \phi_n(t) \phi_k(t) dt \begin{cases} = 0 & \text{FOR } k \neq n \\ = \lambda_n & \text{FOR } k = n \end{cases}$$

(LIMITS OF INTEGRATION MAY BE $\pm\infty$)

b) COEFFICIENTS MAY BE DETERMINED:

$$a_j \lambda_j = \int_{t_1}^{t_2} \phi_j(t) x(t) dt$$

WHEN BASIC FUNCTION IS REAL AND ORTHONORMAL

4) CHECKING ERROR IN APPROXIMATION

$$a) x(t) = \sum_{n=0}^{\infty} a_n \phi_n(t); \hat{x}(t) = \sum_{n=0}^M \hat{a}_n \phi_n(t)$$

b) USE INTEGRAL SQUARED ERROR

$$1) I = \int_{t_1}^{t_2} [x(t) - \hat{x}(t)]^2 dt$$

$$= \int_{t_1}^{t_2} \left[x(t) - \sum_{n=0}^M \hat{a}_n \phi_n(t) \right]^2 dt$$

2) WISH TO FIND VALUES OF \hat{a}_n TO GIVE I MINIMUM VALUE

3) REARRANGING TERMS YIELDS:

$$\begin{aligned} I &= \int_{t_1}^{t_2} \left[x^2(t) - 2x(t) \sum_{n=0}^M \hat{a}_n \phi_n(t) \right. \\ &\quad \left. + \sum_{n=0}^M \hat{a}_n \phi_n(t) \sum_{k=0}^M \hat{a}_k \phi_k(t) \right] dt \\ &= \int_{t_1}^{t_2} x^2(t) dt - 2 \sum_{n=0}^M \hat{a}_n \int_{t_1}^{t_2} x(t) \phi_n(t) dt \\ &\quad + \sum_{n=0}^M \sum_{k=0}^M \hat{a}_n \hat{a}_k \int_{t_1}^{t_2} \phi_n(t) \phi_k(t) dt \end{aligned}$$

FIRST TERM INDEP. OF a_n

SECOND TERM = $2 \hat{a}_n \lambda_n$

$$\therefore I = K - 2 \sum_{n=0}^M \hat{a}_n a_n \lambda_n + \sum_{n=0}^M \hat{a}_n^2 \lambda_n$$

$$= K - \sum_{n=0}^M \lambda_n a_n^2 + \sum_{n=0}^M \lambda_n (\hat{a}_n - a_n)^2$$

⇒ I WILL BE MINIMUM WHEN $\hat{a}_n = a_n$

(4) $\frac{\text{ERROR ENERGY}}{\text{SIGNAL ENERGY}} = 1 - \frac{1}{E} \sum_{n=0}^{\infty} \lambda_n a_n^2$

5) EXAMPLE OF BASIS FUNCTION USE


a) USE RECTANGULAR WAVEFORMS

SYSTEM ORTHONORMAL ⇒ $\lambda_k = 1$ FOR $k \geq 0$

b) LET $\phi_0(t) = 1$ $0 \leq t \leq 1$
 $= 0$ ELSEWHERE

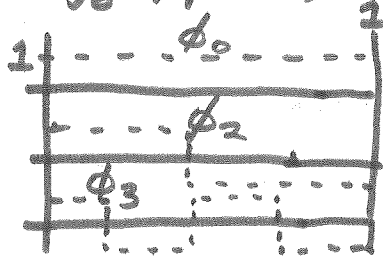c) ORTHONORMALTY REQUIRES:

$\int_0^1 \phi_0(t) \phi_1(t) dt = 0$
 AND $\int_0^1 \phi_1^2(t) dt = 1$



d) LET $x(t) = 6t$ $0 \leq t \leq 1$
 $= 0$ ELSEWHERE

e) $a_0 = \int_0^1 \phi_0(t) x(t) dt = \int_0^1 (1) 6t dt = 3$
 SIMILARLY $a_1 = \int_0^1 \phi_1(t) x(t) dt = \int_0^1 (1/2) 6t dt = 3/2$
 AND $a_2 = 3/4$; $a_3 = 3/8$

f) ∴ $\hat{x}(t) = 3\phi_0(t) - \frac{3}{2}\phi_1(t) - \frac{3}{4}\phi_2(t) \dots$

g) COMPUTING ERROR APPROXIMATION

$E = \int_0^1 (6t)^2 dt = 12$

FOR FIRST 4 ENTRIES:
 $\frac{\text{ERROR EN}}{\text{SIGNAL EN}} = 1 - \frac{1}{12} (3^2 + (\frac{3}{2})^2 + (\frac{3}{4})^2 + (\frac{3}{8})^2) = \frac{1}{256}$

10

D) FOURIER SERIES REPRESENTATION

1) FUNCTION MUST FIT DIRICHLET CONDITIONS

- a) $x(t)$ BE SINGLE VALUED
- b) FINITE MAX AND MIN
- c) FINITE # DISCONTINUITIES
- d) $\int_{t_1}^{t_2} |x(t)| dt < \infty$

2) $\phi_n(t) = e^{jn\omega_0 t}$; $n = 0, \pm 1, \pm 2, \dots$
 $\omega_0 = 2\pi/T$

3) BASIS FUNCTION ORTHOGONOL:

$$\int_{t_1}^{t_1+T} e^{jn\omega_0 t} e^{-jk\omega_0 t} dt \begin{cases} = 0 & n \neq k \\ = T & n = k \end{cases}$$


4) $a_n = \frac{1}{T} \int_{t_1}^{t_1+T} x(t) e^{-jn\omega_0 t} dt$

5) $x(t) = \sum_{n=-\infty}^{\infty} a_n e^{jn\omega_0 t}$

E) SINGULARITY FUNCTIONS

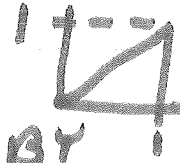1) UNIT RAMP FUNCTION


$$r(t) = \begin{cases} t & t \geq 0 \\ 0 & t < 0 \end{cases}$$



SLOPE MAY BE CHANGED BY MULTIPLICATION

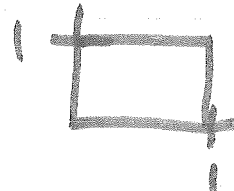2) UNIT STEP FUNCTION

$$\mu(t) = \begin{cases} 1 & t \geq 0 \\ 0 & t < 0 \end{cases}$$



3) $r(t) = \int_{-\infty}^t \mu(\lambda) d\lambda$

FOURIER TRANSFORMS

I) THE FOURIER TRANSFORM

A) CONSIDER FOURIER SERIES

$$f(t) = \sum_{n=-\infty}^{\infty} a_n e^{jn\omega_0 t} = \sum_{n=-\infty}^{\infty} a_n e^{j \frac{2\pi n t}{T}}$$

$$a_n = \frac{1}{T} \int_{-T/2}^{T/2} f(t) e^{-j \frac{2\pi n t}{T}} dt$$

$$\Rightarrow f(t) = \sum_{n=-\infty}^{\infty} e^{j \frac{2\pi n t}{T}} \left[\frac{\omega_0}{2\pi} \int_{-T/2}^{T/2} f(t) e^{-jn\omega_0 t} dt \right]$$

LET $T \rightarrow \infty \Rightarrow \omega_0 \rightarrow d\omega \Rightarrow n \rightarrow \infty$

$$f(t) = \int_{-\infty}^{\infty} e^{j\omega t} \left[\frac{d\omega}{2\pi} \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt \right]$$

$$= \frac{1}{2\pi} \int_{-\infty}^{\infty} \left[\int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt \right] e^{j\omega t} d\omega$$

FOURIER TRANSFORM

$$\mathcal{F}[f(t)] = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt = F(j\omega)$$

$$\mathcal{F}^{-1}[F(j\omega)] = f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(j\omega) e^{j\omega t} d\omega$$

$$F(j\omega) = A(\omega) e^{j\theta(\omega)}$$

$$\begin{matrix} \text{AMPLITUDE} \\ \text{SPECTRUM} \\ \text{PHASE} \\ \text{SPECTRUM} \end{matrix} \quad \begin{matrix} A(\omega) = |F(j\omega)| \\ e^{j\theta(\omega)} = \tan^{-1} \left[\frac{\text{Im } F(j\omega)}{\text{Re } F(j\omega)} \right] \end{matrix}$$

B) DIRICHLET CONDITIONS (ASSURE CONVERGENCE)

1) $f(t)$ MUST BE ABSOLUTELY INTEGRABLE, i.e.

$$\int_{-\infty}^{\infty} |f(t)| dt < \infty$$

2) $f(t)$ MUST HAVE FINITE NUMBER OF MAXIMA AND MINIMA IN ANY FINITE INTERVAL

3) $f(t)$ MUST HAVE A FINITE NUMBER OF DISCONTINUITIES IN A FINITE INTERVAL

II) CALCULATIONS OF SIMPLE TRANSFORMS

A) RECTANGULAR PULSE



$$P_T(j\omega) = \int_{-\infty}^{\infty} P_T(t) e^{-j\omega t} dt = \int_0^T e^{-j\omega t} dt = \left[\frac{e^{-j\omega t}}{-j\omega} \right]_0^T$$

$$= \frac{1 - e^{-j\omega T}}{j\omega}$$

$$= \frac{e^{-j\omega T/2}}{\omega/2} \left[\frac{e^{j\omega T/2} - e^{-j\omega T/2}}{2j} \right]$$

$$= T e^{-j\omega T/2} \frac{\sin \omega T/2}{\omega T/2}$$

$$= T e^{-j\omega T/2} \text{sinc } \frac{\omega T}{2}$$


B) NOTES

1) MORE COMPACT IN TIME, THE MORE SPREAD OUT THE FREQUENCY AND VISA VERSA


$$\frac{\int_{-\infty}^{\infty} f(t) dt}{f(0)} \cdot \frac{\int_{-\infty}^{\infty} F(j\omega) d\omega}{F(0)} = 2\pi$$

\Downarrow \Downarrow
 EQUIVALENT EQUIVALENT
 DURATION BANDWIDTH

C) ONE SIDED EXPONENTIAL PULSE

$f(t) = e^{-\alpha t} \mu(t)$

 $F(j\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$
 $F(j\omega) = \int_0^{\infty} e^{-\alpha t} e^{-j\omega t} dt$
 $= \left[\frac{e^{-(\alpha + j\omega)t}}{-(\alpha + j\omega)} \right]_0^{\infty} = \frac{1}{j\omega + \alpha}$

D) TWO SIDED EXPONENTIAL PULSE


 $f(t) = e^{\alpha t} \mu(-t) + e^{-\alpha t} \mu(t)$
 $F(j\omega) = \int_{-\infty}^{\infty} e^{\alpha t} e^{-j\omega t} dt + \int_0^{\infty} e^{-\alpha t} e^{-j\omega t} dt$
 $= \frac{1}{\alpha - j\omega} + \frac{1}{\alpha + j\omega} = \frac{2\alpha}{\omega^2 + \alpha^2}$

E) DERIVATIVE OF A TIME FUNCTION

$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(j\omega) e^{j\omega t} d\omega$
 $\frac{d}{dt} f(t) = \frac{d}{dt} \left[\frac{1}{2\pi} \int_{-\infty}^{\infty} F(j\omega) e^{j\omega t} d\omega \right]$
 $= \frac{1}{2\pi} \int_{-\infty}^{\infty} j\omega F(j\omega) e^{j\omega t} d\omega$

$\mathcal{F}^{-1} \{ j\omega F(j\omega) \} = \frac{df(t)}{dt}$
 $\mathcal{F} \left\{ \frac{df(t)}{dt} \right\} = j\omega F(j\omega)$

F) CIRCUIT ANALYSIS



$V(t) = 2 \frac{di(t)}{dt} + 4i(t)$
 $\frac{10}{j\omega + 1} = j2\omega I(j\omega) + 4I(j\omega) \Rightarrow I(j\omega) = \frac{5}{(j\omega + 1)(j\omega + 2)}$
 $I(j\omega) = \frac{5}{j\omega + 1} - \frac{5}{j\omega + 2} \Rightarrow i(t) = (5e^{-t} - 5e^{-2t}) \mu(t)$

III) ELEMENTARY PROPERTIES OF THE FOURIER TRANSFORMS

A) SYMMETRY OF $f(t)$ ABOUT THE TIME ORIGIN

$f(t) = f_e(t) + f_o(t)$
 $f_e(t) = \frac{f(t) + f(-t)}{2}; f_o(t) = \frac{f(t) - f(-t)}{2}$
 $\Rightarrow F(j\omega) = \underbrace{2 \int_{-\infty}^{\infty} f_e(t) \cos \omega t dt}_{\text{REAL}} - \underbrace{j2 \int_{-\infty}^{\infty} f_o(t) \sin \omega t dt}_{\text{IMAGINARY}}$

EVEN $f(t) \rightarrow$ REAL $F(j\omega)$
 ODD $f(t) \rightarrow$ IMAG $F(j\omega)$
 $|F(j\omega)|$ IS EVEN
 $e^{j\theta(\omega)}$ IS ODD

B) SYMMETRY OF $F(j\omega)$ ABOUT FREQ. ORIGIN

$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} [F_e(j\omega) + F_o(j\omega)] e^{j\omega t} d\omega$$

$$f_e(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F_e(j\omega) \cos \omega t d\omega = \frac{1}{2\pi} \int_{-\infty}^{\infty} \text{Re } F(j\omega) \cos \omega t d\omega$$

$$f_o(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F_o(j\omega) \sin \omega t d\omega = \frac{1}{2\pi} \int_{-\infty}^{\infty} \text{Im } F(j\omega) \sin \omega t d\omega$$

C) CAUSAL TIME FUNCTIONS


$$\left. \begin{aligned} f_e &= \frac{f(t) + f(-t)}{2} = \frac{1}{2} f(t) \\ f_o &= \frac{f(t) - f(-t)}{2} = \frac{1}{2} f(t) \end{aligned} \right\} \Rightarrow f(t) = 2f_e(t) = 2f_o(t)$$

$$f(t) = \frac{1}{\pi} \int_{-\infty}^{\infty} F_e(j\omega) \cos \omega t d\omega = \frac{1}{\pi} \int_{-\infty}^{\infty} \text{Re } F(j\omega) \cos \omega t d\omega$$

$$= \frac{j}{\pi} \int_{-\infty}^{\infty} F_o(j\omega) \sin \omega t d\omega = \frac{j}{\pi} \int_{-\infty}^{\infty} \text{Im } F(j\omega) \sin \omega t d\omega$$

PALEY-WIENER CRITERIA $\rightarrow \int_{-\infty}^{\infty} \frac{|\ln A(\omega)|}{1+\omega^2} d\omega < \infty$
FOR CAUSAL FUNCTIONS

IV) SYSTEM FUNCTIONS

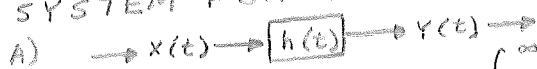

CONVOLUTION $\rightarrow y(t) = \int_{-\infty}^{\infty} h(\lambda) x(t-\lambda) d\lambda$


$$Y(j\omega) = \int_{-\infty}^{\infty} \left[\int_{-\infty}^{\infty} h(\lambda) x(t-\lambda) d\lambda \right] e^{-j\omega t} dt$$

$$= \int_{-\infty}^{\infty} h(\lambda) \left[\int_{-\infty}^{\infty} x(t-\lambda) e^{-j\omega t} dt \right] d\lambda$$

$$= X(j\omega) H(j\omega)$$

ie $\mathcal{F}\{f_1(t) * f_2(t)\} = F_1(j\omega) F_2(j\omega)$

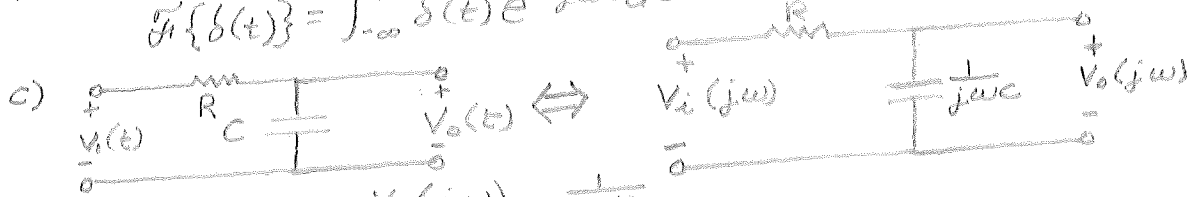B) $H(j\omega) = \mathcal{F}[h(t)] = \frac{Y(j\omega)}{X(j\omega)}$
 $\mathcal{F}\{\delta(t)\} = \int_{-\infty}^{\infty} \delta(t) e^{-j\omega t} dt = 1$




$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{1/j\omega C}{R + 1/j\omega C}$$

$$= \frac{1/RC}{j\omega + 1/RC}$$

ON A ONE OHM BASIS $|H(j\omega)| = \frac{1}{\sqrt{\omega^2 + 1}}$
 $|H(j\omega)|_{dB} = 10 \log_{10} |H(j\omega)|^2 = 10 \log_{10} \left(\frac{1}{\omega^2 + 1} \right) = -10 \log_{10}(\omega^2 + 1)$

D) FILTERS

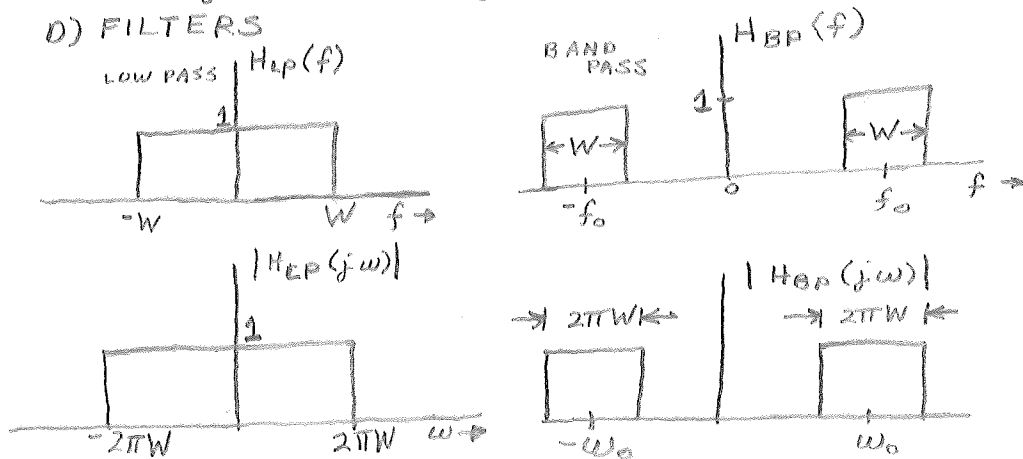

V) ENERGY SPECTRA

A) $E = \int_{-\infty}^{\infty} [f(t)]^2 dt = \frac{1}{2\pi} \int_{-\infty}^{\infty} |F(j\omega)|^2 d\omega \leftarrow \text{PARSEVAL'S THEM}$

B) $|Y(j\omega)|^2 = |H(j\omega)|^2 |X(j\omega)|^2$
 $\frac{|Y(f)|^2}{|V_i(f)|^2} = |H(f)|^2$

$$E_o = \int_{-\infty}^{\infty} |V_o(f)|^2 df$$

$$= 2 \int_{f_1 - \frac{W}{2}}^{f_1 + \frac{W}{2}} |V_i(f)|^2 df$$

$$\Rightarrow |V_i(f)|^2 = \frac{E_o}{2W} \Rightarrow \text{ENERGY PER UNIT BANDWIDTH}$$

VI) MATHEMATICAL OPERATIONS ON FOURIER TRANSFORMS

A) SCALING

$$f(at) \Leftrightarrow \frac{1}{|a|} F\left(\frac{j\omega}{a}\right)$$

B) DELAY

$$f(t-t_0) \Leftrightarrow e^{-j\omega t_0} F(j\omega)$$

C) MODULATION

$$e^{j\omega_0 t} f(t) \Leftrightarrow F\left[\frac{j}{\omega - \omega_0}\right] + \frac{1}{2} F\left[\frac{j}{\omega + \omega_0}\right]$$

$$f(t) \cos \omega_0 t \Leftrightarrow \frac{1}{2} F\left[\frac{j}{\omega - \omega_0}\right] + \frac{1}{2} F\left[\frac{j}{\omega + \omega_0}\right]$$

D) REVERSAL

$$f(-t) \Leftrightarrow F(-j\omega)$$

E) SYMMETRY

$$F(j\omega) \Leftrightarrow 2\pi f(-t)$$

$$\frac{1}{2\pi} F(-t) \Leftrightarrow f(j\omega)$$

VII) FOURIER TRANSFORMS OF POWER SIGNALS

A) $\mathcal{F}\{\text{sgn}(t)\} = \lim_{\alpha \rightarrow 0} \int_{-\infty}^{\infty} e^{-\alpha|t|} \text{sgn}(t) e^{-j\omega t} dt$

$$\text{sgn}(t) \Leftrightarrow \frac{2}{j\omega}$$

B) $\mathcal{F}\{1\} = \lim_{\alpha \rightarrow 0} \int_{-\infty}^{\infty} e^{-\alpha|t|} e^{-j\omega t} dt$

$$= \lim_{\alpha \rightarrow 0} \left[\frac{2\alpha}{\alpha^2 + \omega^2} \right] \quad \omega \neq 0 \Rightarrow 0$$

$$\omega = 0 \Rightarrow \infty$$


$$\mathcal{F}\{1\} \Leftrightarrow 2\pi \delta(\omega)$$

C) $\mathcal{F}\{u(t)\} = \mathcal{F}\left\{\frac{1}{2} + \frac{1}{2} \text{sgn}(t)\right\} = \pi \delta(\omega) + \frac{1}{j\omega}$

VIII) $f_1 \circledast f_2(t) = \frac{1}{2\pi} F_1(j\omega) \circledast F_2(j\omega)$

Pg 24-25 9-17-70

9)

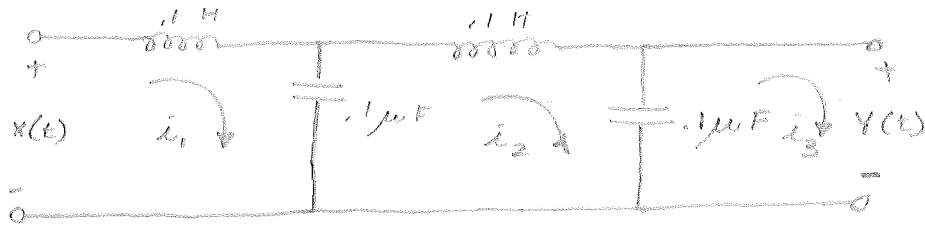

$$x(t) = (0.1) \frac{di_1}{dt} + 10^7 \int_{-\infty}^t i_1 dt - 10^7 \int_{-\infty}^t i_2 dt$$

$$0 = 10^7 \int_{-\infty}^t i_2 dt + 2 \frac{di_2}{dt} - \left(\frac{di_1}{dt} + \frac{di_3}{dt} \right) (0.1)$$

$$+ Y(t) = 10^7 \int_{-\infty}^t i_3 dt + 10^7 \int_{-\infty}^t i_2 dt$$

$$x'(t) = (0.1) \frac{d^2 i_1}{dt^2} + 10^7 i_1(t) - 10^7 i_2(t)$$

$$0 = 10^7 i_2(t) + 2 \frac{d^2 i_2}{dt^2} - (0.1) \frac{d^2 i_1}{dt^2} - \frac{d^2 i_3}{dt^2}$$


$$Y(t) = 10^7 i_2(t) - 10^7 i_3(t)$$

$$x'(t) = (0.1) \frac{d^2 i_1}{dt^2} + 10^7 i_1(t) - 10^7 i_3(t) - Y'(t)$$

ARG!

pg 25; 9-18-70

2-10)

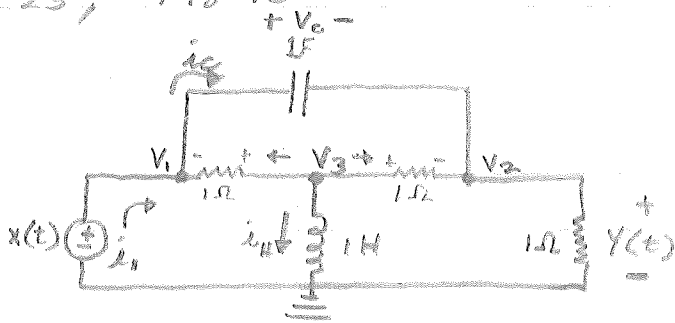

$$V_1 = x(t); V_2 = Y(t)$$

$$0 = (V_3 - V_2) + (V_3 - V_1) + \frac{dV_3}{dt} \Rightarrow 2V_3 + \frac{dV_3}{dt} - V_2 - V_1 = 0$$

$$V_c = V_1 - V_2 = x(t) - Y(t)$$

$$i_H = \frac{dV_3}{dt}$$

$$\text{Let } V_3 = q_1 \quad \& \quad V_c = q_2$$

$$0 = 2V_3 + \frac{dV_3}{dt} - Y(t) - X(t)$$

$$i_H = \frac{dV_3}{dt}; q_2 = x(t) - Y(t)$$

~~$$i_H = \frac{dV_3}{dt}; V_c = x(t) - Y(t)$$~~

$$i_H = \frac{dV_3}{dt}; V_c = x(t) - Y(t)$$

$$V_c = x(t) - Y(t); \quad 2V_3 + \frac{dV_3}{dt} - V_2 - V_1 = 0$$

$$2V_3 + \frac{dV_3}{dt} - Y(t) - X(t) = 0$$

$$-V_c - Y(t) + X(t) = 0$$

$$2V_3 + \frac{dV_3}{dt} + V_c - 2X(t) = 0$$

$$\frac{dq_1}{dt} = \frac{dV_3}{dt} = -2V_3 - V_c + 2X(t)$$

~~$$V_c = x(t) - Y(t)$$~~

~~$$\Rightarrow X(t) - Y(t) - V_c = 0$$~~

$$i_c = \frac{dV_c}{dt}$$

$$i_c = V_3 - V_1 = V_3 - X(t)$$

$$\therefore \frac{dV_c}{dt} = V_3 - X(t)$$

$$\frac{dV_3}{dt} = -2V_3 - V_c + 2X(t)$$

$$\frac{dV_c}{dt} = V_3 - X(t)$$

$$Y(t) = x(t) - V_c$$



$$3-8) a) f(t) = \sum_{n=-\infty}^{\infty} a_n \phi_n(t) ; g(t) = \sum_{n=-\infty}^{\infty} b_n \phi_n(t) dt$$

$$\begin{aligned} I &= \int_{t_1}^{t_2} f(t) g(t) dt \\ &= \int_{t_1}^{t_2} \left[\sum_{k=-\infty}^{\infty} a_k \phi_k(t) \sum_{n=-\infty}^{\infty} b_n \phi_n(t) \right] dt \\ &= \sum_{i=-\infty}^{\infty} a_i b_i \int_{t_1}^{t_2} \phi_k(t) \phi_n(t) dt \\ &= \sum_{i=-\infty}^{\infty} a_i b_i \end{aligned}$$

$$\begin{aligned} b) E &= \int_{t_1}^{t_2} i^2(t) dt \\ &= \int_{t_1}^{t_2} \sum_{i=-\infty}^{\infty} a_i b_i = \sum_{i=-\infty}^{\infty} a_i b_i \end{aligned}$$

Pp 50-51 9-23-70

3-10) a)

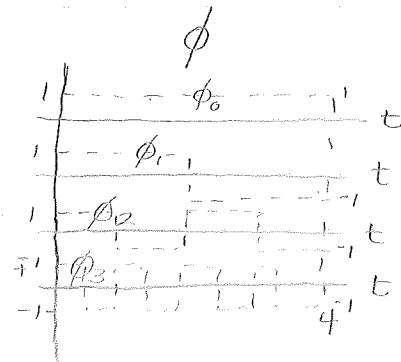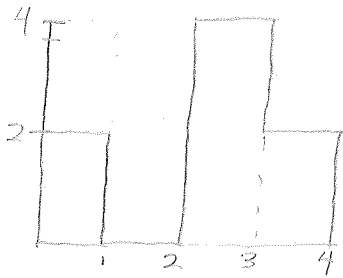

$$x(t) = \sum_{n=0}^M a_n \phi_n(t)$$

$$a_n = \frac{1}{\lambda_n} \int_{t_1}^{t_2} \phi_n(t) x(t) dt$$

$$\frac{1}{\lambda_n} = 1$$

$$a_0 = \int_0^4 (1) x(t) dt = \int_0^1 2 dt + \int_1^2 0 dt + \int_2^3 4 dt + \int_3^4 2 dt = 8$$

$$a_1 = \int_0^1 (1) 2 dt + \int_2^3 (-1) 4 dt + \int_3^4 (-1) 2 dt$$

$$= 2 - 4 - 2 = -4$$

$$a_2 = \int_0^1 (1)(2) dt + \int_2^3 (1)(4) dt - \int_3^4 2 dt$$

$$= 2 + 4 - 2 = 4$$

$$a_3 = a_4 = a_n \text{ (FOR } n > 2) = 0$$


$$\therefore x(t) = 8\phi_0(t) - 4\phi_1(t) + 4\phi_2(t)$$

$$b) \frac{\text{ERROR ENERGY}}{\text{SIGNAL ENERGY}} = 1 - \frac{1}{E} \sum_{n=0}^M \lambda_n a_n^2$$

$$E = \int_{t_1}^{t_2} x^2(t) dt = 64$$

$$\therefore ER = 1 - \frac{1}{64} [64 + 16 + 16]$$

3-16)d)

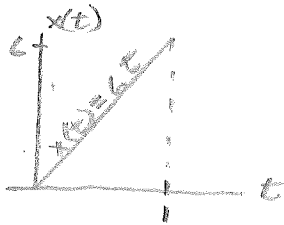

$$x(t) =$$

$$a_n = \frac{1}{T} \int_{t_1}^{t_1+T} x(t) e^{-jn\omega_0 t} dt$$

$$a_n = \int_0^T ct e^{-jn2\pi t} dt$$

$$u = ct \quad dv = e^{-jn2\pi t} dt$$

$$a_n = \left[ct e^{-jn2\pi t} - \int_0^T \frac{c e^{-jn2\pi t}}{jn2\pi} dt \right]_0^T$$

$$= \left[ct e^{-jn2\pi t} - \frac{c}{jn2\pi} \left[\frac{e^{-jn2\pi t}}{jn2\pi} \right]_0^T \right]$$

$$= \frac{-c}{jn2\pi} \left[t e^{-jn2\pi t} \right]_0^T + \frac{c}{n^2 4\pi^2} \left[e^{-jn2\pi t} \right]_0^T$$

$$= \frac{-c}{jn2\pi} \left[e^{-jn2\pi} \right] + \frac{c}{n^2 4\pi^2} \left[e^{-jn2\pi} - 1 \right]$$

$$= \frac{-c}{jn2\pi} \left[\cos n2\pi - j \sin n2\pi \right] + \frac{c}{n^2 4\pi^2} \left[\cos n2\pi - 1 \right]$$

$$= e^{-jn2\pi} \left[\frac{-c}{jn2\pi} + \frac{c}{n^2 4\pi^2} \right] - \frac{c}{n^2 4\pi^2}$$

$$= \left[\cos n2\pi - j \sin n2\pi \right] \left[\frac{-c}{jn2\pi} + \frac{c}{n^2 4\pi^2} \right] - \frac{c}{n^2 4\pi^2}$$

$$= \left[1 - 0 \right] \left[\frac{-c}{jn2\pi} + \frac{c}{n^2 4\pi^2} \right] - \frac{c}{n^2 4\pi^2} = \frac{-c}{jn2\pi}$$

$$\therefore x(t) = \sum_{-\infty}^{\infty} \frac{-3}{jn\pi} e^{jn2\pi t}$$

$$b) E = \frac{1}{T} \int_0^T 36t^2 dt$$

$$= 36 \frac{t^3}{3} = [12t^2]_0^T = 12$$

$$\frac{E_{AR}}{SIG} = 1 - \frac{1}{E} \sum_{n=0}^M \lambda_n a_n^2$$

$$\alpha_n = \frac{-6}{jn2\pi}$$

$$\alpha_{-3} = \frac{+6}{j6\pi} = -\frac{1}{\pi}$$


$$\alpha_{-2} = \frac{+6}{j4\pi} = -\frac{3}{2\pi}$$

$$\alpha_{-1} = \frac{+6}{j\pi} = -\frac{6}{\pi}$$

$$\alpha_0 = \infty \quad \text{ARG!}$$

$$\alpha_n = \frac{6}{n2\pi}$$

3-17)

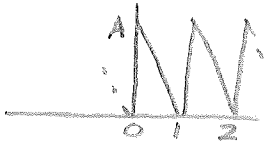

$$x(t) = -At + A$$

$$\alpha_n = \frac{1}{T} \int_0^T x(t) e^{-jn\omega_0 t} dt$$

$$\alpha_n = \frac{1}{T} \int_0^1 (A - At) e^{-jn2\pi t} dt$$

$$= A \int_0^1 e^{-jn2\pi t} dt - A \int_0^1 t e^{-jn2\pi t} dt$$

$$\frac{\alpha_n}{A} = \left[\frac{e^{-jn2\pi t}}{-jn2\pi} \right]_0^1 - \int_0^1 t e^{-jn2\pi t} dt$$

$$M = \int_0^1 t e^{-jn2\pi t} dt$$

$$U = t \quad dV = e^{-jn2\pi t}$$

$$dU = dt \quad V = \frac{e^{-jn2\pi t}}{-jn2\pi}$$

$$M = \left[t \frac{e^{-jn2\pi t}}{-jn2\pi} \right]_0^1 + \frac{1}{jn2\pi} \int_0^1 e^{-jn2\pi t} dt$$

$$= \frac{1}{jn2\pi} e^{-jn2\pi} - \frac{1}{4n^2\pi^2} [e^{-jn2\pi t}]_0^1$$

$$= \frac{1}{jn2\pi} e^{-jn2\pi} - \frac{1}{4n^2\pi^2} [e^{-jn2\pi} - 1]$$

$$= \frac{1}{jn2\pi} e^{-jn2\pi} - \frac{1}{4n^2\pi^2} e^{-jn2\pi} + \frac{1}{4n^2\pi^2}$$

$$\Rightarrow \frac{\alpha_n}{A} = \frac{1}{2n\pi} [e^{-jn2\pi} - 1] + \frac{1}{2n\pi} e^{-jn2\pi} + \frac{1}{4n^2\pi^2} e^{-jn2\pi} + \frac{1}{4n^2\pi^2}$$

$$\alpha_n = A \left[\frac{1}{jn2\pi} + \frac{1}{4n^2\pi^2} e^{-jn2\pi} - \frac{1}{4n^2\pi^2} \right]$$

$$= A \left[\frac{1}{jn2\pi} - \frac{1}{4n^2\pi^2} + \frac{1}{4n^2\pi^2} (\cos 2\pi n - j \sin 2\pi n) \right]$$

$$= A \left[\frac{1}{jn2\pi n} \right]$$

$$= \frac{A}{jn2\pi n}$$

$$\Rightarrow x(t) = \sum_{n=-\infty}^{\infty} \frac{A}{jn2\pi n} e^{jn2\pi t}$$

Pg 49 9-27-70

3-2) a) $x(t) = 10 \sin 20\pi t ; t \geq 0$

$= 0 ; t < 0$

$T = \frac{1}{10}$

$$\lim_{T \rightarrow \infty} \frac{50}{T} \int_{-T}^T \sin^2 20\pi t dt$$

$$\frac{25}{T} \int_{-T}^T [1 - \cos 40\pi t] dt$$

$$\frac{25}{T} \left[t - \frac{\sin 40\pi t}{40\pi} \right]_{-T}^T$$

$$\frac{25}{T} \left[\left(T - \frac{\sin 40\pi T}{40\pi} \right) - \left(-T - \frac{\sin 40\pi T}{40\pi} \right) \right]$$

$$\frac{25}{T} \left[2T - \frac{\sin 40\pi T}{20\pi} \right]$$

$$50 - \frac{5 \sin 40\pi T}{4\pi T}$$

$$-1 \leq \sin 40\pi T \leq 1$$

$\therefore 0 < \lim_{T \rightarrow \infty} < \infty$

POWER SIGNAL

$$P_{AVE} = \frac{100}{T} \int_0^T \sin^2 20\pi t dt$$

$$= \frac{50}{T} \int_0^T (1 - \cos 40\pi t) dt$$

$$= 500 \int_0^{1/10} (1 - \cos 40\pi t) dt$$

$$= 500 \left[t - \frac{\sin 40\pi t}{40\pi} \right]_0^{1/10}$$

$$= 500 \left[\frac{1}{10} - \frac{\sin 4\pi}{40\pi} \right] = 50$$

b) $x(t) = 10 e^{-5t} ; t \geq 0$

$= 0 ; t < 0$

$E = \int_{-\infty}^{\infty} 100 e^{-10t} dt$

$= 100 \left[\frac{e^{-10t}}{-10} \right]_{-\infty}^{\infty} \Rightarrow \text{NOT E SIGN.}$

$$\frac{100}{2T} \int_{-T}^T e^{-10t} dt$$

$$\frac{50}{T} \left[e^{-10t} \right]_{-T}^T = \frac{-5}{T} \left[e^{-10T} - e^{10T} \right]$$

$$= \frac{-5e^{-10T}}{T} + \frac{5e^{10T}}{T}$$

$$= 0 + \frac{50e^{10T}}{1} = \infty$$

(CONT)

$$b) \quad x(t) = 10e^{-5t} \quad t \geq 0$$

$$= 0 \quad t < 0$$

$$100 \int_0^{\infty} e^{-10t} dt$$

$$100 \cdot \frac{1}{10} [e^{-10t}]_0^{\infty}$$

$$-10 [0 - 1] = 10$$

$$\Rightarrow E = 10$$

$$c) \quad x(t) = 10 \sin 20\pi t + 5 \cos 22\pi t; \quad -\infty < t < \infty$$

$$\omega_1 = 20\pi = 2\pi f \Rightarrow 10 = f \Rightarrow T_1 = \frac{1}{10} = 0.1 \text{ s}$$

$$\omega_2 = 22\pi = 2\pi f \Rightarrow 11 = f \Rightarrow T_2 = \frac{1}{11} = 0.0909 \text{ s}$$

$$T \text{ FOR } x(t) = 1.10$$

$$\frac{1}{1.1} \int_0^{1.1} (10 \sin 20\pi t + 5 \cos 22\pi t)^2 dt$$


$$.911 \int_0^{1.1} (100 \sin^2 20\pi t + 50 \sin 20\pi t \cos 22\pi t + 25 \cos^2 22\pi t) dt$$

$$a = 20\pi, b = 22\pi$$


$$.911 \left[-\frac{1}{2} \frac{\cos 2 - 2\pi t}{-2\pi} + \text{ARG!} \right]$$

d)

4-2)

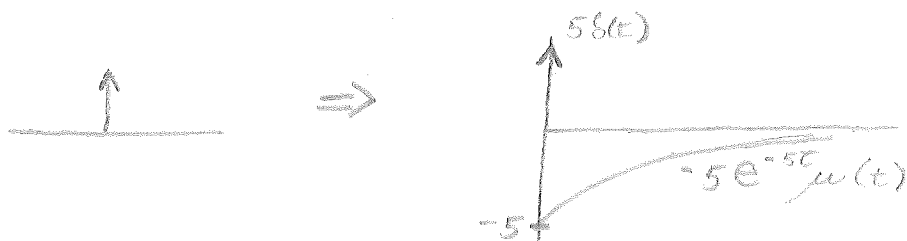

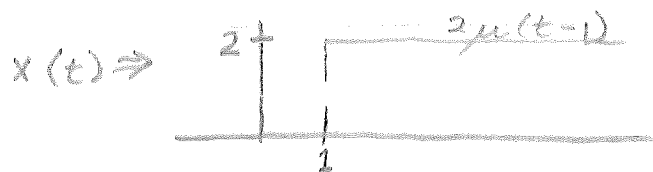
$$Y(t) = \int_{-\infty}^{\infty} x(\lambda) h(t-\lambda) d\lambda$$





$$Y(t) = \int_{-\infty}^{\infty} 2\mu(\lambda-1) [5\delta(t-\lambda) - 5e^{-5(t-\lambda)}\mu(t-\lambda)] dt$$
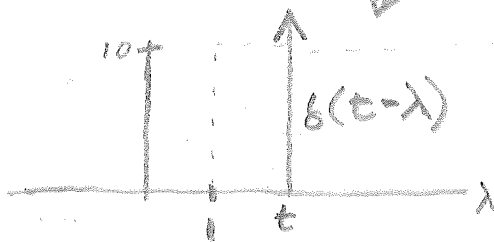
$$Y(t) = \int_{-\infty}^{\infty} 10\mu(\lambda-1)\delta(t-\lambda) dt - \int_{-\infty}^{\infty} 10\mu(\lambda-1)e^{-5(t-\lambda)}\mu(t-\lambda) dt$$



$$\begin{aligned}
 Y(t) &= 10\mu(t-1) - \int_1^t 10e^{-5t+5\lambda} dt \\
 &= 10 - 10 \left[\frac{e^{-5t+5\lambda}}{-5} \right]_1^t \\
 &= 10 - 2 \left[1 - e^{-5(t-1)} \right] \\
 &= [8 + 2e^{-5(t-1)}] \mu(t-1)
 \end{aligned}$$

4-3) a)

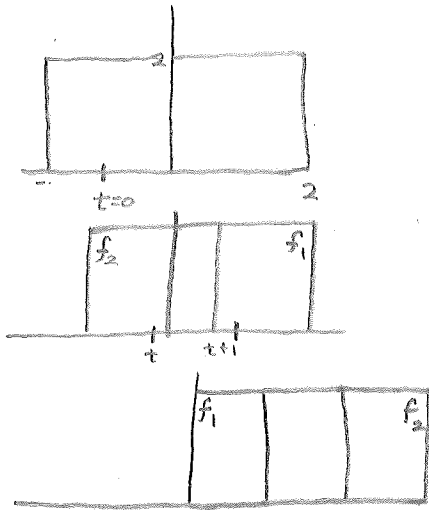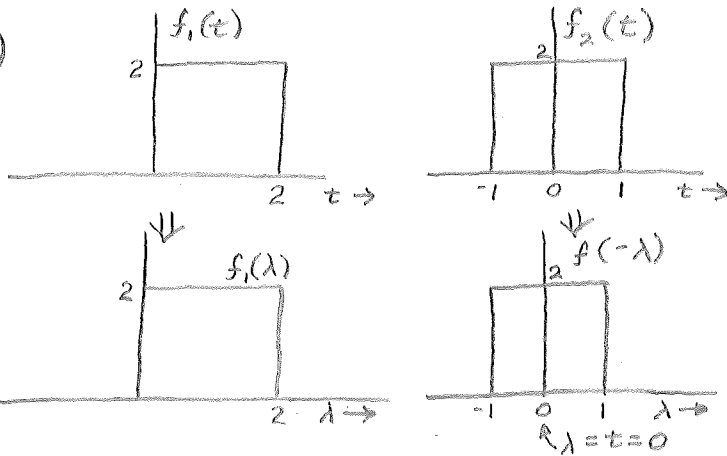







$$t < 0 \Rightarrow \int_{-\infty}^{\infty} f_1(\lambda) f_2(\lambda) d\lambda = 0$$

$$\begin{aligned} -1 < t < 1 &\Rightarrow \int_0^{t+1} f_1(\lambda) f_2(\lambda) d\lambda \\ &= \int_0^{t+1} 4 d\lambda = [4\lambda]_0^{t+1} \\ &= 4t + 4 \end{aligned}$$


$$\begin{aligned} 1 < t < 3 &\Rightarrow \int_{t-1}^2 4 d\lambda = [4\lambda]_{t-1}^2 \\ &= 8 - 4(t-1) \\ &= 12 - 4t \end{aligned}$$

$$3 < t \Rightarrow f_1 * f_2 = 0$$

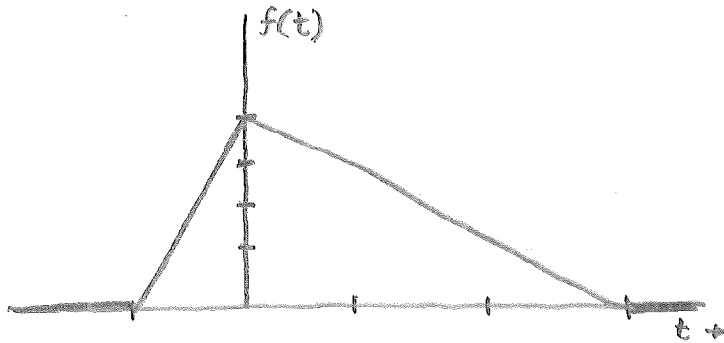

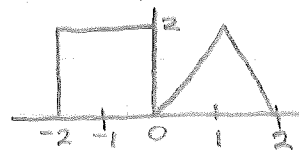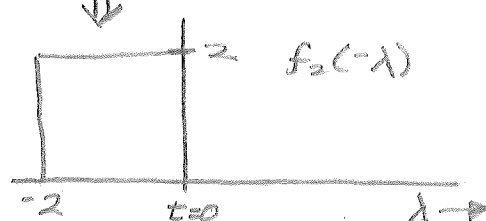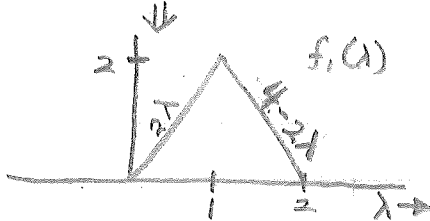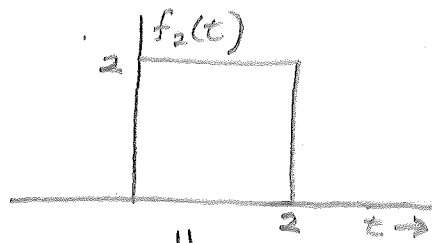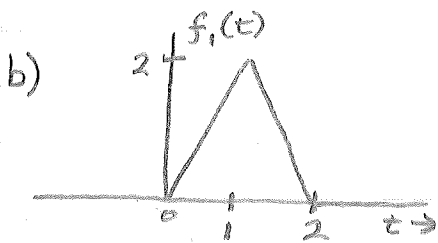

$$t < 0 \Rightarrow f_1 * f_2 = 0$$

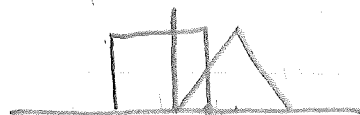


$$0 < t < 1 \Rightarrow \int_0^t 4\lambda d\lambda = 2\lambda^2 \Big|_0^t = 2t^2$$

$$\begin{aligned} 1 < t < 2 &\Rightarrow \int_0^1 4\lambda d\lambda + \int_1^t (8-4\lambda) d\lambda \\ &= 2 + [8\lambda - 2\lambda^2]_1^t \\ &= 2 + (8t - 2t^2) - (8 - 2) \\ &= -2t^2 + 8t - 4 \end{aligned}$$



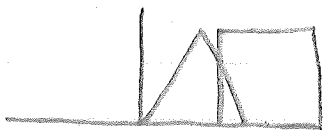
$$\begin{aligned} 2 < t < 3 &\Rightarrow \int_{t-2}^1 4\lambda d\lambda + \int_1^2 (8-4\lambda) d\lambda \\ &= [4\lambda^2]_{t-2}^1 + [8\lambda - 2\lambda^2]_1^2 \\ &= 4 - 4(t-2)^2 + (16-16) - 6 \\ &= -6 - (4t^2 - 16t + 16) \\ &= -4t^2 + 16t - 22 \end{aligned}$$




$$\begin{aligned} 3 < t < 4 &\Rightarrow \int_{t-2}^2 (8-4\lambda) d\lambda \\ &= [8\lambda - 2\lambda^2]_{t-2}^2 \\ &= (16-16) - 8(t-2) + 2(t-2)^2 \\ &= -8t + 16 + 2t^2 - 8t + 8 \\ &= 2t^2 - 16t + 24 \end{aligned}$$

$$4 < t \Rightarrow f_1 * f_2 = 0$$

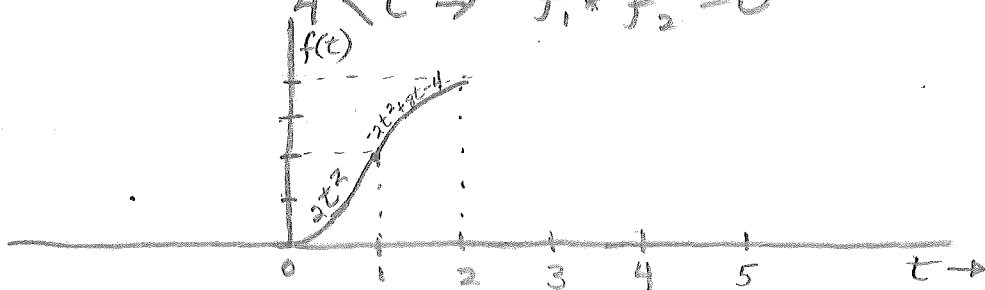

4-3) d)

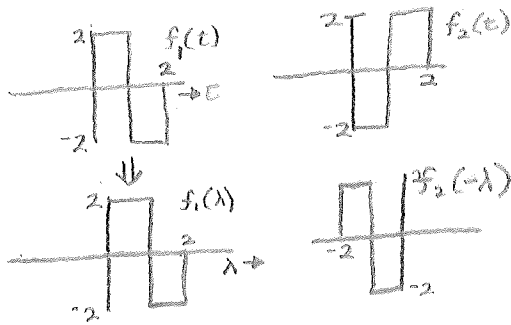


1) $t < 0 \Rightarrow f_1 * f_2 = 0$
 $f_1 * f_2 = \int_0^t -4 d\lambda = -4\lambda \Big|_0^t$



$f_1 * f_2 = \int_0^{t-1} 4 d\lambda + \int_{t-1}^1 -4 d\lambda + \int_1^t 4 d\lambda$
 $= 4\lambda \Big|_0^{t-1} - 4\lambda \Big|_{t-1}^1 + 4\lambda \Big|_1^t$
 $= 4(t-1) - [4 - 4(t-1)] + 4t - 4$
 $= 4t - 4 - 4 + 4t - 4 + 4t - 4$
 $= 12t - 16$




$f_1 * f_2 = \int_{t-2}^1 4 d\lambda - \int_1^{t-1} 4 d\lambda + \int_{t-1}^2 4 d\lambda$
 $= 4\lambda \Big|_{t-2}^1 - 4\lambda \Big|_1^{t-1} + 4\lambda \Big|_{t-1}^2$
 $= [4 - 4(t-2)] - [4(t-1) - 4] + [8 - 4(t-1)]$
 $= 4 - 4t + 8 - 4t + 4 + 4 + 8 - 4t + 4$
 $= -12t + 32$

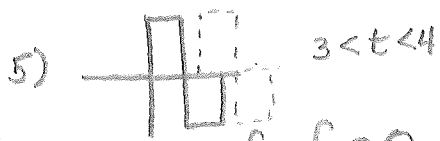


$f_1 * f_2 = \int_{t-2}^2 -4 d\lambda$
 $= -4\lambda \Big|_{t-2}^2$
 $= -8 + 4(t-2)$
 $= 4t - 16$

6) $t > 4 \Rightarrow f_1 * f_2 = 0$

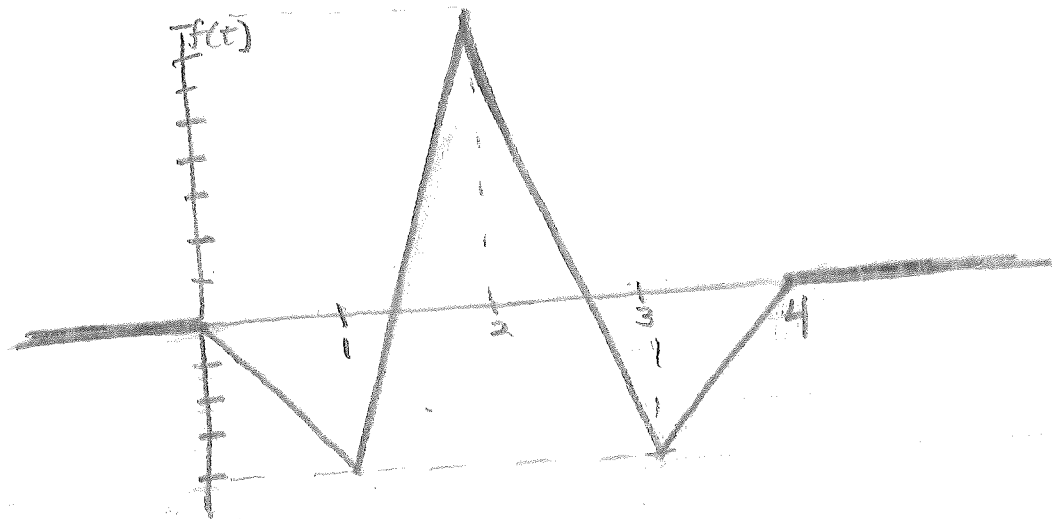


4-2)

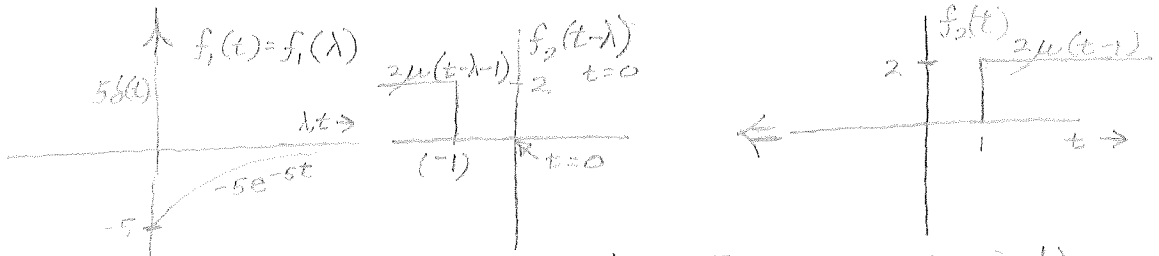

$$f_1 * f_2 = \int_{-\infty}^{\infty} [5\delta(\lambda) - 5e^{-5\lambda} u(\lambda)] 2u(t-\lambda-1) d\lambda$$

$$= \int_{-\infty}^{\infty} 10\delta(\lambda) u(t-\lambda-1) d\lambda - \int_{-\infty}^{\infty} 10e^{-5\lambda} u(\lambda) u(t-\lambda-1) d\lambda$$

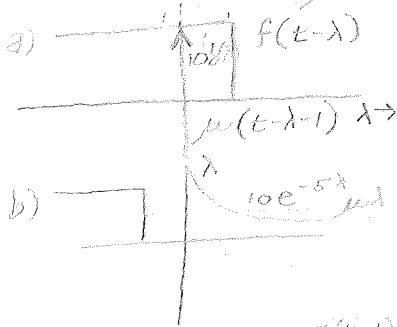a) $t \geq 1 \Rightarrow \int_{-\infty}^{\infty} 10\delta(\lambda) u(t-\lambda-1) d\lambda = 10$




$$t \geq 1 \Rightarrow \int_0^{t-1} 10e^{-5\lambda} d\lambda$$

$$= 10 \left[-\frac{1}{5} e^{-5\lambda} \right]_0^{t-1}$$

$$= -2e^{-5(t-1)} + 2$$


$$\therefore f_1 * f_2 = 10 + 20e^{-5(t-1)} - 2 = (8 + 20e^{-5(t-1)}) u(t-1)$$

4-7) b)

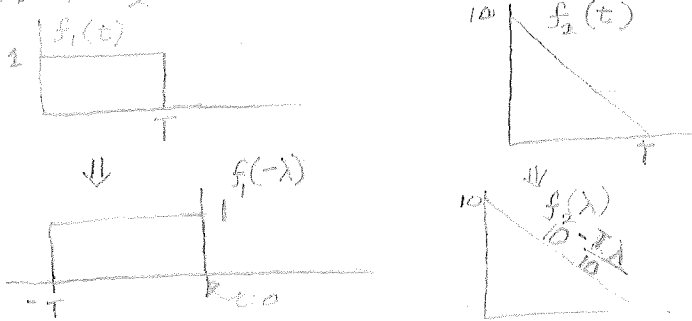

T = K

1) $t < 0 \Rightarrow f_1 * f_2 = 0$

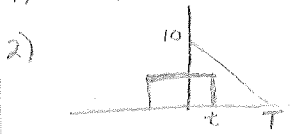

2) $0 \leq t \leq T \Rightarrow f_1 * f_2 = \int_0^t (10 - \frac{T\lambda}{10}) d\lambda = \left[10\lambda - \frac{T\lambda^2}{20} \right]_0^t$

$$= 10t - \frac{Kt^2}{20}$$



3) $T \leq t \leq 2T \Rightarrow f_1 * f_2 = \int_{t-T}^T (10 - \frac{T\lambda}{10}) d\lambda = \left[10\lambda - \frac{T\lambda^2}{20} \right]_{t-T}^T$

$$= \left[10T - \frac{T^3}{10} \right] - \left[10(t-T) - \frac{T(t-T)^2}{10} \right]$$


$$= 10T - \frac{T^3}{10} - 10t + 10T + \frac{Tt^2}{10} - \frac{2tT^2}{10} + \frac{T^3}{10}$$

$$= \frac{Tt^2}{10} - t(10 + \frac{2T}{10}) + 20T$$



4) $t \geq 2T \Rightarrow f_1 * f_2 = 0$

ETC,


4-9)

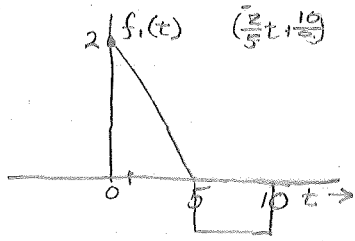


ASIGND. 10-12-70

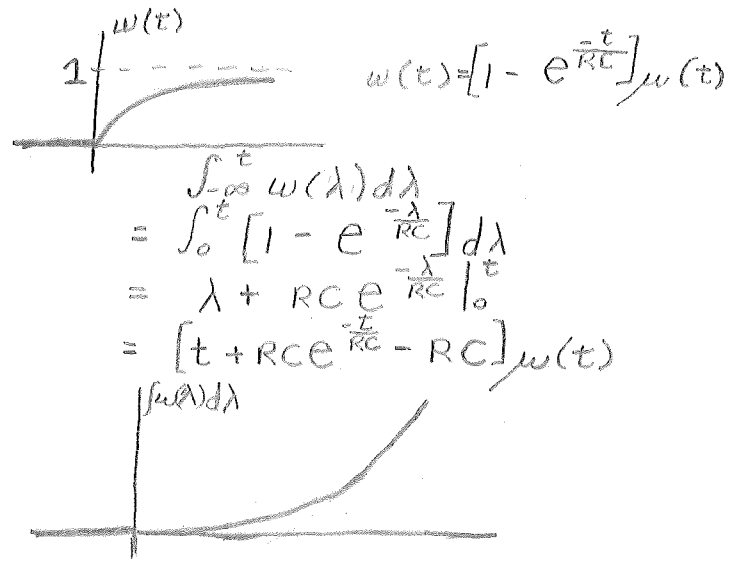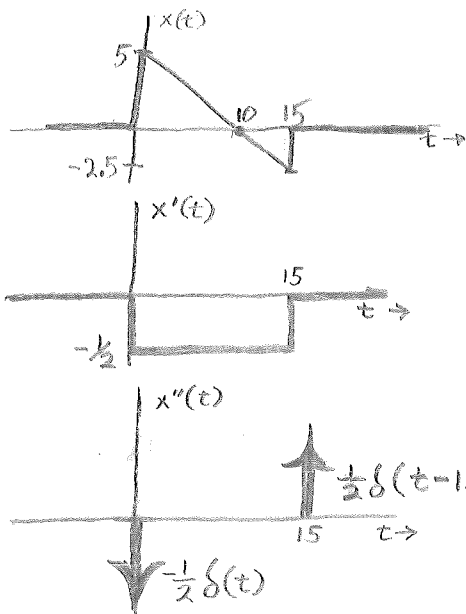
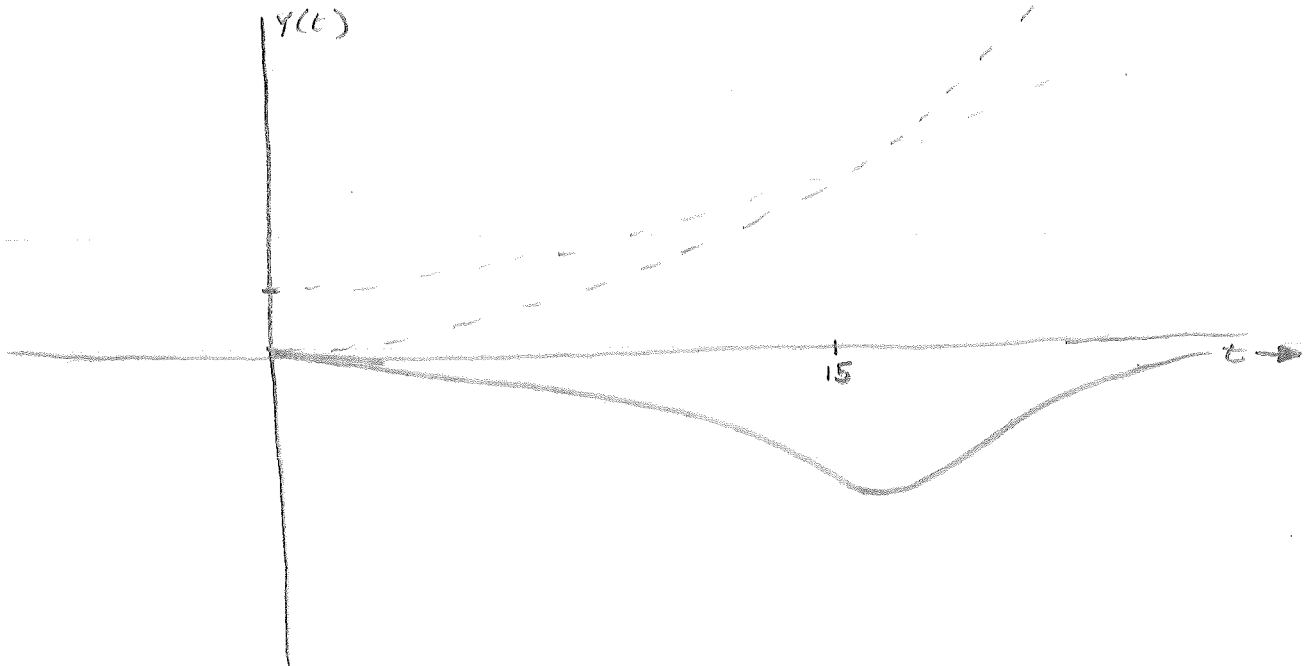
$$\begin{aligned}
 Y &= x''(t) * \int_{-\infty}^t w(\lambda) d\lambda \\
 &= -\frac{1}{2} [t + RCe^{-\frac{t}{RC}} - RC]\mu(t) + \frac{1}{2} [(t-15) + RCe^{-\frac{(t-15)}{RC}} - RC]\mu(t-15) \\
 &= \frac{1}{2} [t + RCe^{-\frac{t}{RC}} - (RC+15)]\mu(t) - \frac{1}{2} [t + RCe^{-\frac{t-15}{RC}} - RC]\mu(t-15)
 \end{aligned}$$



5-3)

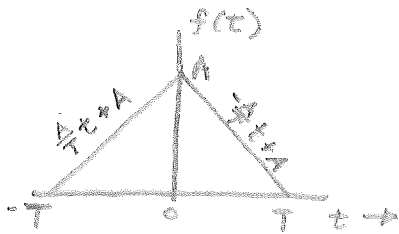

$$\mathcal{F}[f(t)] = F(j\omega)$$

$$= \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$$

$$= \int_{-T}^0 \left(\frac{A}{T}t + A\right) e^{-j\omega t} dt$$

$$+ \int_0^T \left(-\frac{A}{T}t + A\right) e^{-j\omega t} dt$$

$$F(j\omega) = \int_{-T}^0 \frac{A}{T}t e^{-j\omega t} dt + \int_{-T}^0 A e^{-j\omega t} dt + \int_0^T \frac{-A}{T}t e^{-j\omega t} dt + \int_0^T A e^{-j\omega t} dt$$

$$u = \frac{A}{T}t \quad dv = e^{-j\omega t}$$

$$du = \frac{A}{T}dt \quad v = \frac{e^{-j\omega t}}{-j\omega}$$

$$\left[\frac{-A}{Tj\omega} t e^{-j\omega t} \right]_{-T}^0 + \int_{-T}^0 \frac{A}{Tj\omega} e^{-j\omega t} dt$$

$$\left[\frac{-A}{Tj\omega} [0 + T e^{j\omega T}] \right] + \left[\frac{A}{Tj\omega^2} e^{-j\omega t} \right]_{-T}^0$$

$$\Rightarrow \frac{-AT}{Tj\omega} e^{j\omega T} + \frac{A}{T\omega^2} [1 - e^{j\omega T}]$$

$$\int_0^T \frac{-A}{T}t e^{-j\omega t} dt$$

$$u = \frac{-At}{T} \quad dv = e^{-j\omega t}$$

$$du = \frac{-A}{T}dt \quad v = \frac{e^{-j\omega t}}{-j\omega}$$

$$\left[\frac{A}{Tj\omega} t e^{-j\omega t} \right]_0^T - \int_0^T \frac{A}{Tj\omega} e^{-j\omega t} dt$$

$$\Rightarrow \frac{AT}{Tj\omega} e^{-j\omega T} - \frac{A}{T\omega^2} [e^{-j\omega T} - 1]$$

$$\int_{-T}^T A e^{-j\omega t} dt = \frac{-A}{j\omega} e^{-j\omega t} \Big|_{-T}^T = \frac{-A}{j\omega} [1 - e^{j\omega T}]$$

$$\Rightarrow \frac{-A}{j\omega} + \frac{A}{j\omega} e^{j\omega T}$$

$$\int_0^T A e^{-j\omega t} dt = \frac{-A}{j\omega} e^{-j\omega t} \Big|_0^T = \frac{-A}{j\omega} [e^{-j\omega T} - 1]$$

$$\Rightarrow \frac{A}{j\omega} - \frac{A}{j\omega} e^{-j\omega T}$$


$$\therefore F(j\omega) = \frac{-A}{j\omega} e^{j\omega T} - \frac{A}{T\omega^2} e^{j\omega T} + \frac{A}{T\omega^2} + \frac{A}{j\omega} e^{-j\omega T} - \frac{A}{T\omega^2} e^{-j\omega T} + \frac{A}{T\omega^2} - \frac{A}{j\omega} + \frac{A}{j\omega} e^{-j\omega T}$$

$$= \left[\frac{-A}{j\omega} - \frac{A}{T\omega^2} + \frac{A}{j\omega} \right] e^{j\omega T} + \left[\frac{A}{j\omega} - \frac{A}{T\omega^2} - \frac{A}{j\omega} \right] e^{-j\omega T} + \left[\frac{A}{T\omega^2} + \frac{A}{T\omega^2} \right]$$

$$= \frac{-A}{T\omega^2} [e^{j\omega T} + e^{-j\omega T}] + \frac{2A}{T\omega^2}$$

$$= \frac{-2A}{T\omega^2} \cos \omega T + \frac{2A}{T\omega^2}$$


5-6) a)

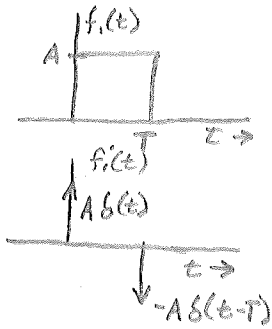

$$\begin{aligned} \mathcal{F}\{f_1'(t)\} &= A - Ae^{-j\omega T} \\ \Rightarrow \mathcal{F}\{f_1(t)\} &= \frac{A(1 - e^{-j\omega T})}{j\omega} \end{aligned}$$


$$\begin{aligned} F(j\omega) &= \frac{2A}{\omega} e^{-j\omega T/2} \frac{(e^{j\omega T/2} - e^{-j\omega T/2})}{2j} \\ &= \frac{2A}{\omega} e^{-j\omega T/2} \sin \frac{\omega T}{2} \\ &= 2AT e^{-j\omega T/2} \sin \frac{\omega T}{2} / \frac{\omega T}{2} \end{aligned}$$

b)

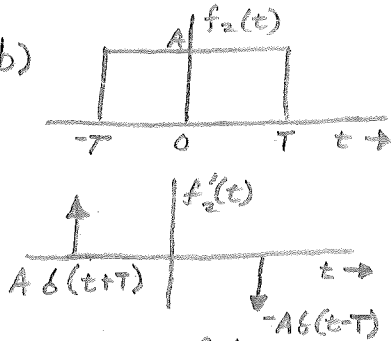

$$\begin{aligned} \mathcal{F}\{f_2'(t)\} &= Ae^{-j\omega T} - Ae^{j\omega T} \\ F(j\omega) &= \frac{-2A}{\omega} \frac{-e^{-j\omega T} + e^{j\omega T}}{2j} \\ &= \frac{-2A}{\omega} \sin \omega T \\ &= -2AT \frac{\sin \omega T}{\omega T} \end{aligned}$$

c)

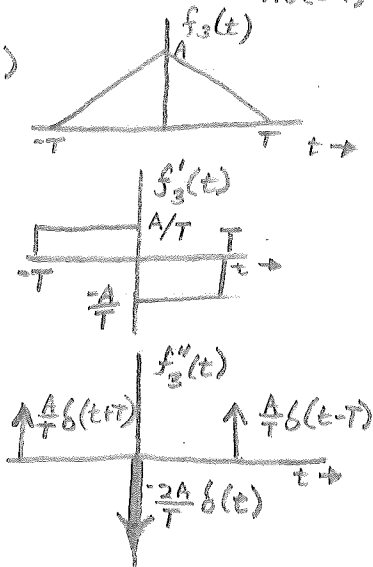


$$\begin{aligned} \mathcal{F}\{f_3''(t)\} &= \frac{2A}{T} \\ \mathcal{F}\{f_3'(t)\} &= \frac{2A}{T(j\omega)^2} \\ \mathcal{F}\{f_3(t)\} &= \frac{A}{T} e^{+j\omega T} - \frac{2A}{T} + \frac{A}{T} e^{-j\omega T} \\ F(j\omega) &= \frac{T(j\omega)^2 - \frac{2A}{T(j\omega)^2} + \frac{Ae^{-j\omega T}}{T(j\omega)^2}}{T\omega^2} \\ &= \frac{-Ae^{j\omega T} + \frac{2A}{T\omega^2} + \frac{Ae^{-j\omega T}}{T\omega^2}}{T\omega^2} \\ &= \frac{-A[2 + e^{j\omega T} + e^{-j\omega T}]}{T\omega^2} \\ &= \frac{4A[e^{j\omega T/2} - e^{-j\omega T/2}]^2}{T\omega^2 \cdot -4} \\ &= \frac{4A}{T\omega^2} \sin^2 \frac{\omega T}{2} \\ &= 2AT \left[\frac{\sin \frac{\omega T}{2}}{\frac{\omega T}{2}} \right]^2 \end{aligned}$$

$$5-8) F_c(j\omega) = 2 \operatorname{Re} [F_c(j\omega)]$$

$$F_s(j\omega) = 2 \operatorname{Im} [F_c(j\omega)]$$


a) EVEN FUNCTION

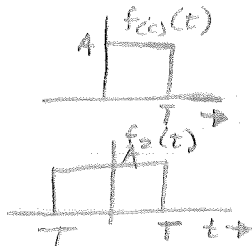

$$F_c(j\omega) = AT e^{-\frac{j\omega T}{2}} \frac{\sin \frac{\omega T}{2}}{\frac{\omega T}{2}}$$

$$F_2(j\omega) = 2TA \frac{\sin \frac{\omega T}{2}}{\frac{\omega T}{2}}$$

b) ODD FUNC.

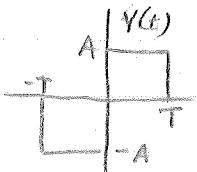

$$F_c(j\omega) = AT e^{-\frac{j\omega T}{2}} \frac{\sin \frac{\omega T}{2}}{\frac{\omega T}{2}}$$

$$= AT \left(\cos \frac{\omega T}{2} j \sin \frac{\omega T}{2} \right) \frac{\sin \frac{\omega T}{2}}{\frac{\omega T}{2}}$$

$$Y(j\omega) = 2jAT \frac{\sin^2 \frac{\omega T}{2}}{\frac{\omega T}{2}}$$




$$F(j\omega) = \frac{A}{(\alpha + j\omega)(\alpha - j\omega)}$$

$$= \frac{(\alpha - j\omega)A}{(\alpha^2 + \omega^2)}$$


$$Z(j\omega) = \frac{2A\alpha}{\alpha^2 + \omega^2}$$

5-2)

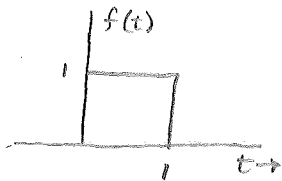


$$\begin{aligned}
 F(j\omega) &= \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt \\
 &= \int_0^1 e^{-j\omega t} dt \\
 &= \left[\frac{e^{-j\omega t}}{-j\omega} \right]_0^1 \\
 &= \frac{1}{-j\omega} [e^{-j\omega} - 1] \\
 &= \frac{1}{e^{j\omega/2}} \frac{[e^{j\omega/2} - e^{-j\omega/2}]}{-j\omega} \\
 &= \frac{1}{2} e^{-j\omega/2} \frac{\sin \frac{j\omega}{2}}{\omega/2}
 \end{aligned}$$

5-3) a)

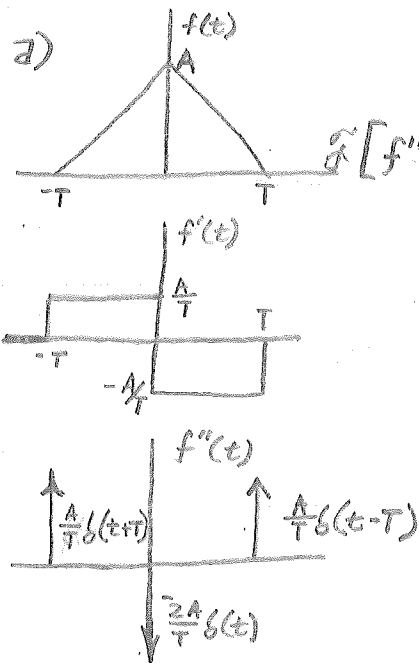

$$\begin{aligned}
 \mathcal{F}[f''(t)] F(j\omega) &= \frac{A}{T} [e^{j\omega T} - 2 + e^{-j\omega T}] \\
 &= \frac{A}{T} [e^{j\omega T/2} - e^{-j\omega T/2}]^2 \\
 &= \frac{-4A}{T} [e^{-j\omega T/2} - e^{j\omega T/2}]^2 \\
 &= -\frac{4A}{T} \sin^2 \frac{\omega T}{2} \\
 &= \frac{(-4AW^2)}{4} \frac{\sin^2 \frac{\omega T}{2}}{\omega^2 T^2} \\
 &= -TA\omega^2 \left[\frac{\sin \frac{\omega T}{2}}{\frac{\omega T}{2}} \right]^2 \\
 F(j\omega) &= TA \left[\frac{\sin \frac{\omega T}{2}}{\frac{\omega T}{2}} \right]^2
 \end{aligned}$$

~~EVEN FUNC~~

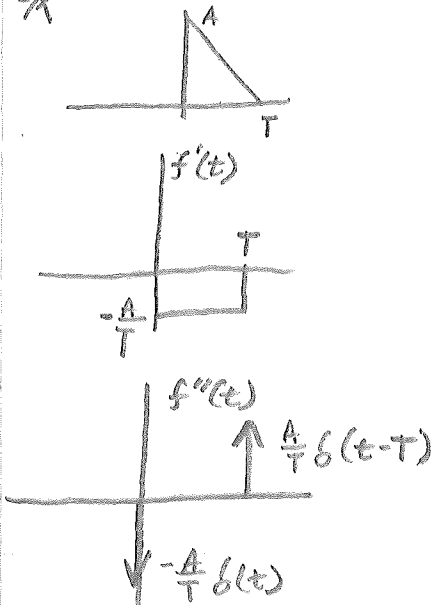


$$\begin{aligned}
 \mathcal{F}[f''(t)] &= \frac{A}{T} [-1 + e^{-j\omega T}] \\
 &= \frac{A}{T} [e^{-j\omega T} - 1] \\
 \mathcal{F}[f(t)] &= \frac{A}{-\omega^2 T} e^{-j\omega T/2} [e^{-j\omega T/2} - e^{j\omega T/2}]
 \end{aligned}$$

$$\begin{aligned}
 \text{5.1) } h(t) &= [e^{-t} - e^{-3t}] u(t) \\
 \mathcal{F}\{h(t)\} &= \frac{1}{2\pi} \int_{-\infty}^{\infty} h(t) e^{j\omega t} dt \\
 &= \frac{1}{2\pi} \int_0^{\infty} [e^{-t} - e^{-3t}] e^{j\omega t} dt \\
 &= \frac{1}{2\pi} \int_0^{\infty} [e^{t(j\omega-1)} - e^{t(j\omega-3)}] dt \\
 &= \frac{1}{2\pi} \left[\frac{1}{j\omega-1} e^{t(j\omega-1)} - \frac{1}{2\pi} \frac{1}{j\omega-3} e^{t(j\omega-3)} \right]_0^{\infty}
 \end{aligned}$$

Pg 83 10-19-70

4-10) $h(t) * x(t)$

$y(3) \sim 7$

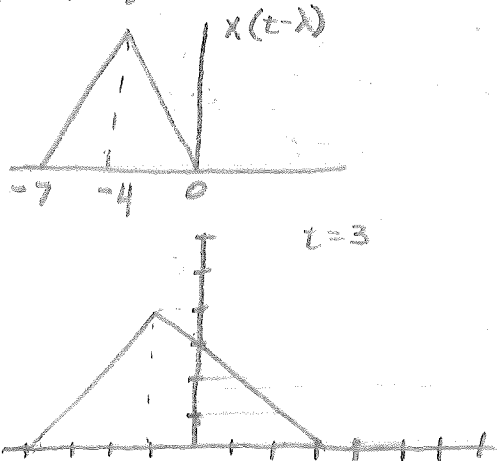

$$b) \frac{1}{2} (4.5 + 2(12.5) + 2(24) + 2(8.5) + 2)$$

$$\frac{1}{2} (4.5 + 25.0 + 48.0 + 17.0 + 2.0)$$

$$\frac{1}{2} (96.5) = 48.25$$

Pg 139

5-4) $f(t) = \frac{A}{T}t + A \quad -T \leq t \leq 0$
 $= -\frac{A}{T}t + A \quad 0 \leq t \leq T$
 $= 0 \quad \text{ELSEWHERE}$


$$F(j\omega) = AT \left[\frac{\sin \frac{\omega T}{2}}{\frac{\omega T}{2}} \right]^2$$


$$\int_{-\infty}^{\infty} f(t) dt = AT \quad f(0) = A$$

$$\int_{-\infty}^{\infty} \frac{\sin^2 \frac{\omega T}{2}}{\frac{\omega T}{2}} d\omega \stackrel{\Rightarrow \text{DURATION} = T}{=} \int_{-\infty}^{\infty} \frac{1 - \cos \omega t}{\omega T} d\omega$$

$$= 2 \int_{-\infty}^{\infty} \frac{1}{\omega T} d\omega = 2 \int_{-\infty}^{\infty} \frac{\cos \omega t}{\omega t} d\omega$$

$$F(0) = AT$$

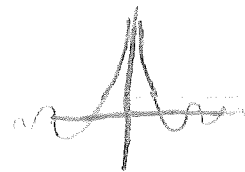

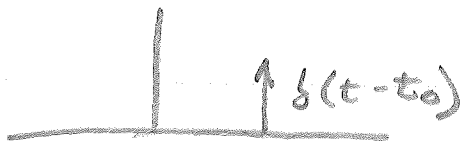~~5.5~~ a) 

$$F(j\omega) = \int_{-\infty}^{\infty} \delta(t-t_0) e^{-j\omega t} dt$$

$$u = e^{-j\omega t}$$

$$du = \frac{e^{-j\omega t}}{-j\omega} dt \quad dv = \delta(t-t_0) dt$$

$$v = u(t-t_0)$$

$$F(j\omega) = e^{-j\omega t} u(t-t_0) \Big|_{-\infty}^{\infty} + \frac{1}{j\omega} \int_{-\infty}^{\infty} e^{-j\omega t} u(t-t_0) dt$$

$$= e^{-j\omega t} \Big|_{t_0}^{\infty} + \frac{1}{j\omega} \int_{t_0}^{\infty} e^{-j\omega t} dt$$

$$= 0 - e^{-j\omega t_0} + \frac{1}{j\omega} \left[\frac{e^{-j\omega t}}{-j\omega} \right]_{t_0}^{\infty}$$

$$= -e^{-j\omega t_0} + \frac{1}{\omega^2} e^{-j\omega t} \Big|_{t_0}^{\infty}$$

$$= -e^{-j\omega t_0} + \frac{1}{\omega^2} [0 - e^{-j\omega t_0}]$$

$$= -e^{-j\omega t_0} \left[\frac{1}{\omega^2} + 1 \right]$$

$$13) \quad F(j\omega) = \frac{8}{4+j\omega}$$

$$|F(j\omega)| = \frac{8}{\sqrt{16+\omega^2}}$$

$$|F(j\omega)|^2 = \frac{64}{(16+\omega^2)}$$

$$E = \frac{1}{2\pi} \int_{-\infty}^{\infty} [F(j\omega)]^2 d\omega$$

$$= \frac{64}{2\pi} \int_{-\infty}^{\infty} \frac{1}{16+\omega^2} d\omega$$

$$\omega = 4 \tan x \Rightarrow d\omega = 4 \sec^2 x dx$$

$$E = \frac{32}{\pi} \int_{-\infty}^{\infty} \frac{1}{16 \sec^2 x} \sec^2 x dx$$

$$= \frac{8}{\pi} \int_{-\infty}^{\infty} dx$$

$$= \frac{8}{\pi} [x]_{-\infty}^{\infty}$$

$$= \frac{8}{\pi} \left[\tan^{-1} \frac{\omega}{4} \right]_{-\infty}^{\infty}$$

$$= \frac{8}{\pi} (\tan^{-1} \infty - \tan^{-1} -\infty)$$

$$= \frac{8}{\pi} \left(\frac{\pi}{2} - \left(-\frac{\pi}{2}\right) \right) = 8$$

14)



$$|Y(j\omega)|^2 = |V(j\omega)|^2 |H(j\omega)|^2$$

$$V(j\omega) = j \int_0^{\infty} \frac{1}{j\omega+1} dt = j \int_0^{\infty} (j\omega+1)^{-1} dt$$

$$= j \left[-\frac{1}{j\omega+1} \right]_0^{\infty} = \frac{1}{(j\omega+1)^2}$$

$$|V(j\omega)| = \frac{1}{\omega^2+1} \Rightarrow |V(j\omega)|^2 = \frac{1}{(\omega^2+1)^2}$$

$$|Y(j\omega)|^2 = \frac{1}{(\omega^2+1)^2} |H(j\omega)|^2$$

$$\therefore \int_0^{\infty} \frac{1}{(\omega^2+1)^2} d\omega = \int_{-2\pi W}^{2\pi W} \frac{1}{(\omega^2+1)^2} d\omega$$

$$\int \frac{1}{(\omega^2+1)^2} d\omega$$

$$\text{let } \omega = \tan x \Rightarrow d\omega = \sec^2 x dx$$

$$\int \frac{1}{\sec^4 x} \sec^2 x dx = \int \cos^2 x dx = \frac{1}{2} \int (1 + \cos 2x) dx$$

$$= \frac{1}{2} \left[x + \frac{1}{2} \sin 2x \right]$$

$$\omega_0 = 2\pi W$$


$$\left[\tan^{-1} \omega + \frac{1}{2} \sin(\tan^{-1} \omega) \right]_0^{\omega_0} = \left[\tan^{-1} \omega + \frac{1}{2} \sin(\tan^{-1} \omega) \right]_{-2\pi W}^{2\pi W}$$

$$\tan^{-1} \infty + \frac{1}{2} \sin(\tan^{-1} \infty) - \tan^{-1} 0 + \frac{1}{2} \sin \tan^{-1} 0 = \frac{\pi}{2} + \frac{1}{2} = \frac{\pi+1}{2}$$

$$\tan^{-1} \omega_0 + \frac{1}{2} \sin(\tan^{-1} \omega_0) - \tan^{-1} -\omega_0 - \frac{1}{2} \sin \tan^{-1} -\omega_0 = \frac{\pi+1}{2}$$

$$\frac{\pi+1}{2} = \tan^{-1} \omega_0 + \frac{1}{2} \sin \tan^{-1} \omega_0 - \tan^{-1} \omega_0 - \frac{1}{2} \sin \tan^{-1} \omega_0$$

$$\theta = \tan^{-1} \omega_0$$

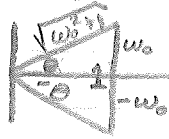

$$\frac{\pi+1}{2} = \theta + \frac{1}{2} \frac{\omega_0}{\sqrt{\omega_0^2 + 1}} + \theta + \frac{1}{2} \left[\frac{\omega_0}{\sqrt{\omega_0^2 + 1}} \right]$$

$$\frac{\pi+1}{2} = 2 \tan^{-1} \omega_0 + \frac{\omega_0}{\sqrt{\omega_0^2 + 1}}$$

$$\frac{\pi+1}{2} = 2X + \sin X \quad \text{GOOD LORD!}$$

$$Y = 2X + \sin X - \frac{\pi+1}{2}$$

$$PI = 3.1416 \dots$$

$$X = PI/6.$$

$$DO \quad 15 \quad J = 1, 20$$

$$Y = 2. * X + SIN(X) - (PI+1)/2.$$

$$DYDX = 2. + COS(X)$$

$$X = X - Y/DYDX$$

15 CONTINUE

$$W = ATAN(X)$$

$$F = W / (2. * PI)$$


WRITE (5,70) F

70 FORMAT (F10.8)

5-1) a) NOT - NOT ABSOLUTELY INTEGRABLE

$$\int_{-\infty}^{\infty} f(t) dt = \int_{-\infty}^0 t dt = \left[\frac{1}{2} t^2 \right]_{-\infty}^0 = \infty$$

b) NOT - HAS INFINITE MAX & MIN ON $[-1, 1]$

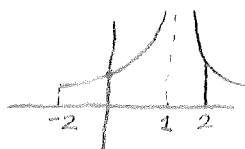
c) NOT ABSOLUTELY INTEGRABLE


$$\int_{-2}^2 \frac{1}{t-1} dt = \ln|t-1| \Big|_{-2}^2 = \ln 1 - \ln^{-1} = \infty$$

d) NOT ABSOLUTELY INTEGRABLE

$$\int_{-\infty}^{\infty} e^{-at} dt = \left[-\frac{1}{a} e^{-at} \right]_{-\infty}^{\infty} = 0 - (-\infty) = \infty$$

5-2)

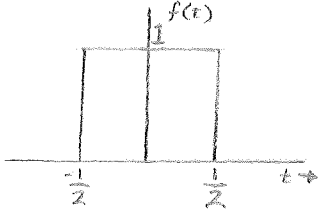

$$\begin{aligned} \tilde{f}\{f(t)\} &= \int_{-1/2}^{1/2} e^{-j\omega t} dt \\ &= \left[\frac{e^{-j\omega t}}{-j\omega} \right]_{-1/2}^{1/2} = \frac{e^{-j\omega/2} - e^{j\omega/2}}{-j\omega} \\ &= \frac{2 \sin \frac{\omega}{2}}{\omega} = \frac{2}{\omega} \frac{\sin \frac{\omega}{2}}{\omega/2} \end{aligned}$$

~~$$\alpha_n = \frac{1}{2} \int_{-1/2}^{1/2} e^{-jn\omega t} dt = \frac{1}{2} \int_{-1/2}^{1/2} e^{-jn\pi t} dt$$

$$= \frac{1}{2} \left[\frac{e^{-jn\pi t}}{-jn\pi} \right]_{-1/2}^{1/2} = \frac{-1}{2jn\pi} \left[e^{-jn\pi/2} - e^{jn\pi/2} \right]$$


$$= \frac{1}{2jn\pi} \left[e^{jn\pi/2} - e^{-jn\pi/2} \right] = \frac{2 \sin \frac{n\pi}{2}}{2jn\pi}$$

$$\alpha_n = \frac{1}{2} \int_{-1/2}^{1/2} e^{-jn\omega t} dt = \frac{1}{2} \int_{-1/2}^{1/2} e^{-jn\pi t} dt$$


$$= \frac{1}{2} \int_{-1/2}^{1/2} e^{-jn\pi t} dt = \frac{1}{2jn\pi} \left[e^{-jn\pi t} \right]_{-1/2}^{1/2}$$

$$= \frac{1}{2jn\pi} \left[e^{jn\pi/2} - e^{-jn\pi/2} \right] = \frac{2 \sin \frac{n\pi}{2}}{2jn\pi}$$
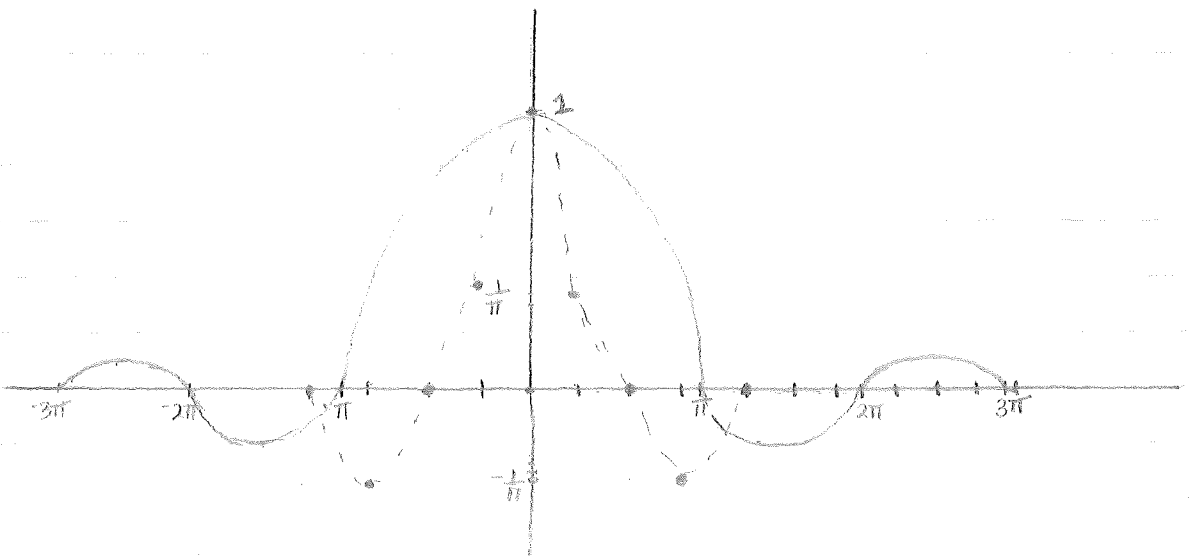
$$= \frac{1}{n\pi} \left[\frac{e^{jn\pi/2} - e^{-jn\pi/2}}{2j} \right] = \frac{\sin \frac{n\pi}{2}}{n\pi}$$~~



5-3)

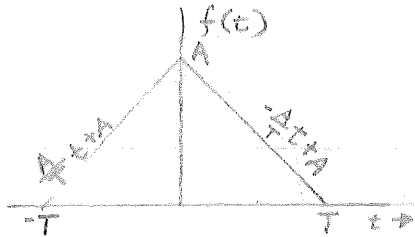

$$\mathcal{F}\{f(t)\} = F(j\omega) = \int_{-T}^0 \left(\frac{A}{T}t + A\right) e^{-j\omega t} dt + \int_0^T \left(-\frac{A}{T}t + A\right) e^{-j\omega t} dt$$

$$\frac{F(j\omega)}{A} = \int_{-T}^0 \frac{t}{T} e^{-j\omega t} dt + \int_{-T}^0 e^{-j\omega t} dt + \int_0^T e^{-j\omega t} dt - \int_0^T \frac{t}{T} e^{-j\omega t} dt$$

$$\int \frac{t}{T} e^{-j\omega t} dt \Rightarrow u = \frac{t}{T}; dv = e^{-j\omega t} dt$$

$$du = \frac{1}{T} dt; v = \frac{-e^{-j\omega t}}{j\omega}$$

$$\int \frac{t}{T} e^{-j\omega t} dt = \left[\frac{-t}{j\omega T} e^{-j\omega t} \right] + \int \frac{1}{j\omega T} e^{-j\omega t} dt$$

$$= \left[\frac{-t}{j\omega T} e^{-j\omega t} \right] + \left[\frac{1}{\omega^2 T} e^{-j\omega t} \right]$$

$$\Rightarrow \int_{-T}^0 \frac{t}{T} e^{-j\omega t} dt = \left[0 + \frac{1}{\omega^2 T} \right] - \left[\frac{1}{j\omega} e^{+j\omega T} + \frac{1}{\omega^2 T} e^{+j\omega T} \right]$$

$$= \frac{1}{\omega^2 T} - \frac{1}{j\omega} e^{+j\omega T} - \frac{1}{\omega^2 T} e^{+j\omega T}$$

$$\Rightarrow \int_0^T \frac{t}{T} e^{-j\omega t} dt = \left[\frac{-1}{j\omega} e^{-j\omega T} + \frac{1}{\omega^2 T} e^{-j\omega T} \right] - \left[0 + \frac{1}{\omega^2 T} \right]$$

$$= \frac{-1}{j\omega} e^{-j\omega T} + \frac{1}{\omega^2 T} e^{-j\omega T} - \frac{1}{\omega^2 T}$$

$$\int e^{-j\omega t} dt = \left[\frac{-e^{-j\omega t}}{j\omega} \right]$$


$$\Rightarrow \int_{-T}^0 e^{-j\omega t} dt = \left[\frac{-1}{j\omega} - \frac{e^{-j\omega T}}{j\omega} \right]$$

$$\Rightarrow \int_0^T e^{-j\omega t} dt = \left[\frac{-e^{-j\omega T}}{j\omega} + \frac{1}{j\omega} \right]$$


$$\therefore \frac{F(j\omega)}{A} = \frac{1}{\omega^2 T} - \frac{1}{j\omega} e^{+j\omega T} - \frac{1}{\omega^2 T} e^{+j\omega T} - \frac{1}{j\omega} - \frac{e^{-j\omega T}}{j\omega}$$

$$= \frac{2}{\omega^2 T} \quad \text{ETC} \quad (\text{ARG!})$$


Pg 140 11-7-70
5-6) a)

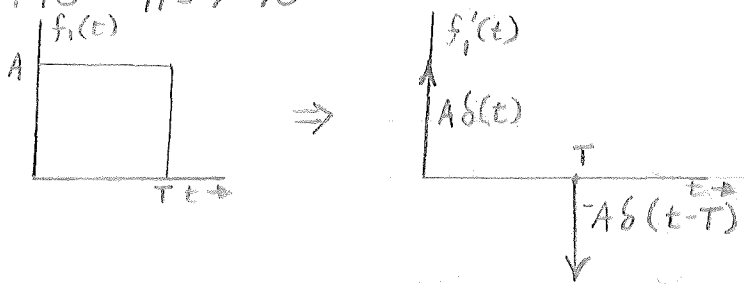

$$\begin{aligned} \tilde{f}_1 [f_1(t)] &= A + A e^{-j\omega T} \\ \tilde{f}_1 \left[\frac{d}{dt} f_1(t) \right] &= A - A e^{-j\omega T} \Leftrightarrow \tilde{f}_1 [f_1(t)] = \frac{A - A e^{-j\omega T}}{j\omega} \\ F(j\omega) &= \frac{A}{j\omega} (1 - e^{-j\omega T}) = \frac{A}{j\omega} e^{-j\frac{\omega T}{2}} (e^{j\frac{\omega T}{2}} - e^{-j\frac{\omega T}{2}}) \\ &= \frac{2A}{\omega} e^{-j\frac{\omega T}{2}} \left(\frac{e^{j\frac{\omega T}{2}} - e^{-j\frac{\omega T}{2}}}{2j} \right) \\ &= \frac{2A}{\omega} e^{-j\frac{\omega T}{2}} \sin \frac{\omega T}{2} = AT e^{-j\frac{\omega T}{2}} \frac{\sin \frac{\omega T}{2}}{\frac{\omega T}{2}} \end{aligned}$$

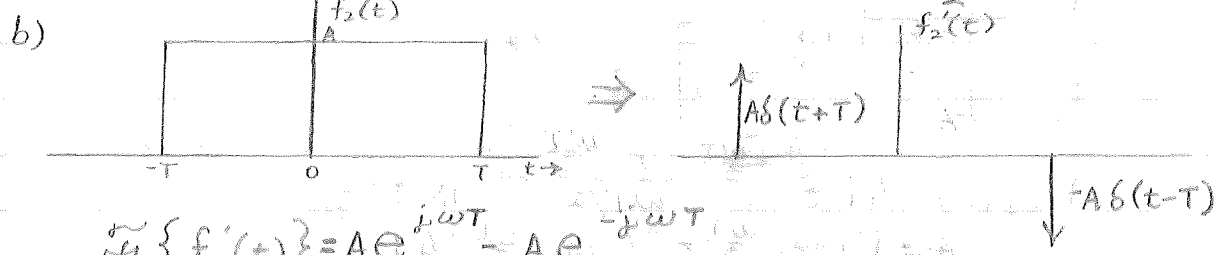

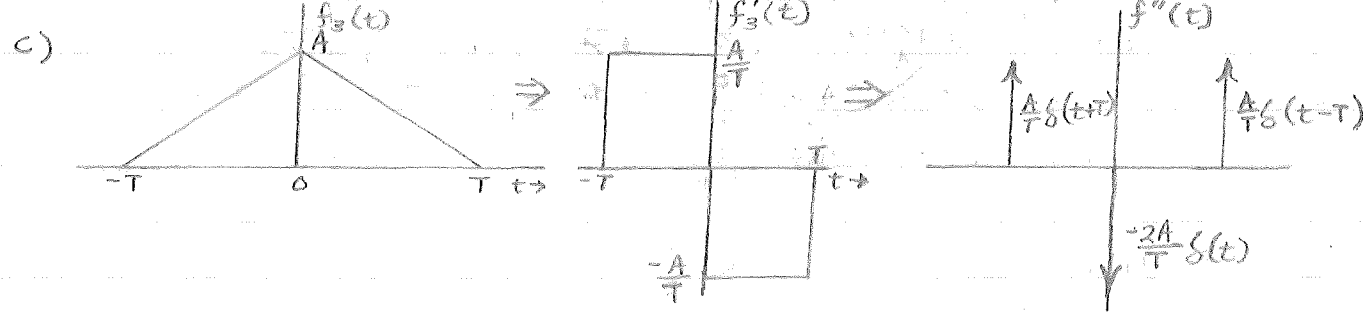
$$\begin{aligned} \tilde{f}_1 \{f_2'(t)\} &= A e^{j\omega T} - A e^{-j\omega T} \\ \Rightarrow \tilde{f}_1 \{f_2(t)\} &= \frac{2A}{\omega} (e^{j\omega T} - e^{-j\omega T}) = \frac{2A}{\omega} \sin \omega T \\ &= 2AT \frac{\sin \omega T}{\omega T} \end{aligned}$$



$$\begin{aligned} \tilde{f}_1 \{f_3''(t)\} &= \frac{A}{T} e^{j\omega T} - \frac{2A}{T} + \frac{A}{T} e^{-j\omega T} = \frac{A}{T} (e^{j\omega T} - 2 + e^{-j\omega T}) \\ \Rightarrow \tilde{f}_1 \{f_3(t)\} &= \frac{-A}{T\omega^2} [e^{j\omega T} + e^{-j\omega T} - 2] \\ &= \frac{-2A}{T\omega^2} \left[\frac{e^{j\omega T} + e^{-j\omega T}}{2} - 1 \right] \\ &= \frac{-2A}{T\omega^2} [\cos \omega T - 1] \\ &= \frac{-2A}{T\omega^2} [2 \cos^2 \frac{\omega T}{2} - 1] - 1 \\ &= \frac{4A}{T\omega^2} (1 - \cos^2 \frac{\omega T}{2}) \\ &= \frac{4A}{T\omega^2} \sin^2 \frac{\omega T}{2} \\ &= AT \frac{\sin^2 \frac{\omega T}{2}}{\frac{\omega^2 T^2}{4}} = AT \left[\frac{\sin \frac{\omega T}{2}}{\frac{\omega T}{2}} \right]^2 \end{aligned}$$

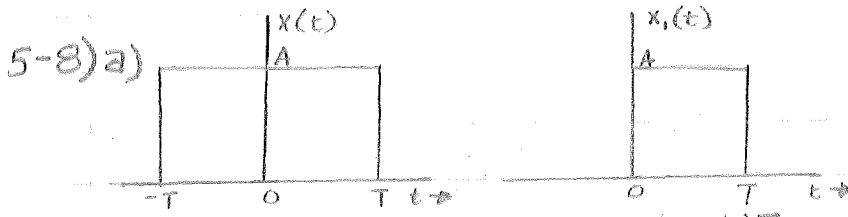
$$\begin{aligned} \cos^2 \frac{\omega T}{2} &= \frac{1}{2} + \frac{1}{2} \cos \omega T \\ \Rightarrow \cos \omega T &= 2 \cos^2 \frac{\omega T}{2} - 1 \end{aligned}$$



$$\mathcal{F}\{x_1(t)\} = AT e^{-j\frac{\omega T}{2}} \frac{\sin \frac{\omega T}{2}}{\omega T/2}$$

$$\text{RE}[\mathcal{F}\{x_1(t)\}] = AT \frac{\sin \frac{\omega T}{2}}{\omega T/2}$$
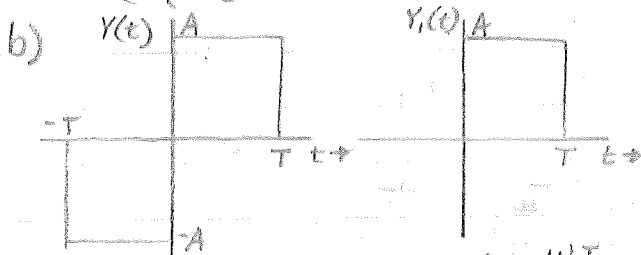
$$\Rightarrow \mathcal{F}\{x(t)\} = 2 \cdot \text{RE}[\mathcal{F}\{x_1(t)\}] = 2AT \frac{\sin \frac{\omega T}{2}}{\omega T/2}$$




$$Y_1(j\omega) = AT e^{-j\frac{\omega T}{2}} \frac{\sin \frac{\omega T}{2}}{\omega T/2}$$

$$= (\cos \frac{\omega T}{2} - j \sin \frac{\omega T}{2}) AT \frac{\sin \frac{\omega T}{2}}{\omega T/2}$$

$$\text{Im} Y_1(j\omega) = -j \sin \frac{\omega T}{2} AT \frac{\sin \frac{\omega T}{2}}{\omega T/2}$$
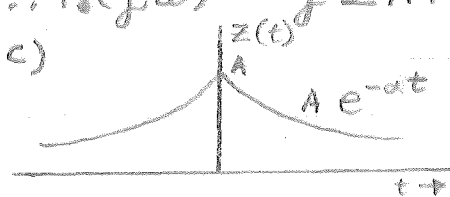
$$\therefore Y_2(j\omega) = -j 2AT \frac{\sin \frac{\omega T}{2}}{\omega T/2}$$



$$Z_1(j\omega) = \frac{1}{j\omega + \alpha} = \frac{j\omega - \alpha}{j\omega - \alpha}$$

$$= \frac{-\alpha}{-\omega^2 - \alpha^2}$$

$$= \frac{\alpha}{\omega^2 + \alpha^2}$$

$$\Rightarrow Z(j\omega) = \frac{2\alpha}{\alpha^2 + \omega^2}$$

5-9) a) $h(t) = [e^{-t} - e^{-3t}] \mu(t)$

$$\Rightarrow H(j\omega) = \frac{1}{j\omega + 1} - \frac{1}{j\omega + 3} = \frac{j\omega + 3 - j\omega - 1}{(j\omega + 1)(j\omega + 3)}$$

$$= \frac{2}{(j\omega + 1)(j\omega + 3)}$$

b) $h(t) = \delta(t) - e^{-2t} \mu(t)$

$$= 1 - \frac{1}{j\omega + 2} = \frac{j\omega + 1}{j\omega + 2}$$


c) $h(t) = e^{-t} \cos t \mu(t)$

$$= e^{-t} \left[\frac{e^{jt} + e^{-jt}}{2} \right] \mu(t)$$

$$= \frac{1}{2} \left[e^{t(j-1)} + e^{-t(j+1)} \right] \mu(t)$$

11-7-70 pg 141

5-10)

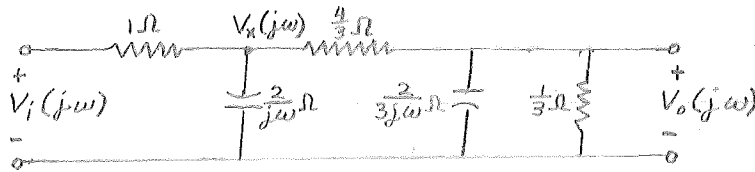

$$\text{AT } V_x \Rightarrow \frac{3(V_x - V_o)}{4} + \frac{j V_x \omega}{2} + V_x - V_i = 0$$

$$3V_x - 3V_o - j2V_x\omega + 4V_x - V_i = 0$$

$$V_x(7 - j2\omega) = 3V_o + V_i \Rightarrow V_x = \frac{3V_o + V_i}{7 - j2\omega}$$

$$\text{AT } V_o \Rightarrow \frac{3(V_o - V_x)}{4} + V_o \left(\frac{2}{j3\omega} + \frac{1}{3} \right) = 0$$

$$3V_o - 3V_x + 4V_o \left(\frac{2}{j3\omega} + \frac{1}{3} \right) = 0$$

$$V_o \left(\frac{10}{3\omega} + \frac{10}{3} \right) = 3V_x \Rightarrow V_x = V_o \left(\frac{10}{9} - \frac{j2}{9\omega} \right)$$

$$\therefore V_o \left(\frac{10}{9} - \frac{j2}{9\omega} \right) = V_o \left(\frac{3}{7 - j2\omega} \right) + \frac{V_i}{7 - j2\omega}$$

$$V_o \left[\frac{10}{9} - \frac{j2}{9\omega} + \frac{3}{j2\omega - 7} \right] = \frac{V_i}{7 - j2\omega}$$

$$H(j\omega) \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{1}{\left(\frac{10}{9} - \frac{j2}{9\omega} + \frac{3}{j2\omega - 7} \right) (7 - j2\omega)}$$

I QUIT!

$$5-13) \quad F(j\omega) = \frac{8}{4+j\omega}$$

$$|F(j\omega)| = \frac{8}{\sqrt{\omega^2+16}}$$

$$|F(j\omega)|^2 = \frac{64}{\omega^2+16}$$

$$E = \frac{1}{2\pi} \int_{-\infty}^{\infty} |F(j\omega)|^2 d\omega$$

$$= \frac{64}{2\pi} \int_{-\infty}^{\infty} \frac{1}{\omega^2+16} d\omega$$

$$\omega = 4 \tan x \Rightarrow d\omega = 4 \sec^2 x dx$$

$$\Rightarrow E = \frac{32}{\pi} \int_{-\infty}^{\infty} \frac{1}{4 \sec^2 x} \sec^2 x dx$$

$$= \frac{8}{\pi} [x]_{-\infty}^{\infty}$$

$$= \frac{8}{\pi} [\tan^{-1} \omega]_{-\infty}^{\infty}$$

$$= \frac{8}{\pi} \left[\frac{3\pi}{2} - \frac{\pi}{2} \right]$$

$$= 8$$

$$5-14) \quad v_2(t) = t e^{-t} \Rightarrow j \frac{d}{d\omega} \frac{1}{j\omega+1} = j \cdot j \frac{1}{(j\omega+1)^2} = V(j\omega)$$

$$= -\frac{1}{(j\omega+1)^2}$$

$$\frac{1}{2} \int_{-\infty}^{\infty} |V(j\omega)|^2 d\omega = \int_{-\omega_0}^{\omega_0} \frac{1}{(\omega^2+1)^2} d\omega \quad \forall \omega_0 = 2\pi W$$

CHUG + PLUG + CHUG

SOLVING FOR W: (FUNSIES!)

$$5-16) \quad x(t) \rightarrow \boxed{h(t)} \rightarrow x(t-t_0)$$

$$\rightarrow H(j\omega) = e^{-j\omega t_0}$$

$$5-17) \quad F(j\omega) = \frac{1}{8-\omega^2+j6\omega}$$

$$a) \mathcal{F}\{f(3t)\} = \frac{1}{a} \left[\frac{1+j\omega/a}{8-\omega^2/a^2+j6\omega/a} \right]$$

$$= \frac{1}{a} \left[\frac{3+j\omega}{80^2-\omega^2+j18\omega} \right]$$


$$= \frac{3+j\omega}{72+\omega^2+18j\omega}$$

$$b) \mathcal{F}\{f(t-2)\} = e^{-j\omega 2} \left[\frac{1+j\omega}{8-\omega^2+j6\omega} \right]$$

$$c) \mathcal{F}\{f(3t-2)\} = e^{-j2\omega} \left[\frac{3+j\omega}{72-\omega^2+\omega j 18} \right]$$

$$d) \mathcal{F}\{5f(\frac{1}{2}t)\} = 5 \left[\frac{1+2j\omega}{8-4\omega^2+j12\omega} \right]$$
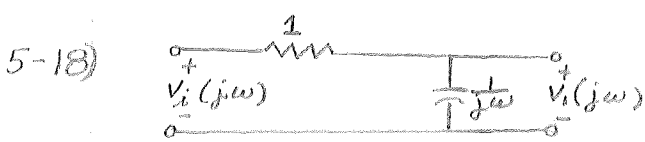
$$= \frac{5+10j\omega}{8-4\omega^2+j12\omega}$$



$$\frac{V_1}{V_i} = \frac{\frac{1}{j\omega}}{1 + \frac{1}{j\omega}} = \frac{1}{j\omega + 1} \Rightarrow V_1 = \frac{V_i}{j\omega + 1}$$

$$V_2(t) = V_1(t-1) \Rightarrow V_2(j\omega) = e^{-j\omega} V_1(j\omega)$$

$$V_o(j\omega) = V_1(j\omega) - V_2(j\omega)$$

$$= V_1(j\omega) \left(\frac{1}{j\omega + 1} - e^{-j\omega} \right)$$

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{1}{j\omega + 1} - e^{-j\omega} = \frac{1 - (j\omega + 1)e^{-j\omega}}{j\omega + 1}$$

5-19) $F(j\omega) = \int_0^{\infty} e^{-j\omega t} f(t) dt$
 $\int_0^{\infty} e^{-j\omega t} e^{-\alpha t} f(t) dt = \int_0^{\infty} e^{-t(j\omega + \alpha)} f(t) dt = F(j\omega + \alpha)$

5-20) $F(j\omega) = \frac{1 + j\omega}{s - \omega^2 + j6\omega}$

a) $\mathcal{F}\{f(t-2)\} = e^{-j2\omega} \left[\frac{1 + j\omega}{s - \omega^2 + j6\omega} \right]$

$\mathcal{F}\{e^{j6t} f(t-2)\} = e^{-j2(\omega-6)} \left[\frac{1 + j(\omega-6)}{s - (\omega-6)^2 + j6(\omega-6)} \right]$

b) $\mathcal{F}\{6 \frac{d}{dt} f(t)\} = 6j\omega \left[\frac{1 + j\omega}{s - \omega^2 + j6\omega} \right]$

c) $\mathcal{F}\{f(2t)\} = \frac{1}{2} \left[\frac{1 + j\omega/2}{s - \omega^2/4 - j3\omega} \right]$
 $= \frac{1}{2} \left[\frac{4 - j\omega^2}{32 - \omega^2 - j12\omega} \right] = \frac{2 - j\omega}{32 - \omega^2 - j12\omega}$

d) $\mathcal{F}\{f(3t)\} = \frac{1}{3} \left[\frac{1 + j\omega/3}{s - \omega^2/9 + j2\omega} \right] = \frac{1}{3} \left[\frac{9 + j\omega^3}{72 - \omega^2 + j18\omega} \right]$

$$= \frac{3 + j\omega}{72 - \omega^2 + j18\omega} = \frac{j\omega}{72 - \omega^2 + j18\omega} + \frac{3}{72 - \omega^2 + j18\omega}$$

$\frac{d}{d\omega} \mathcal{F}\{f(3t)\} = \mathcal{F}\{t f(3t)\}$

$$= \frac{3(-2\omega + j18)}{(72 - \omega^2 + j18\omega)^2} + \frac{j\omega(-3\omega + j18)}{(72 - \omega^2 + j18\omega)^2} + \frac{j}{72 - \omega^2 + j18\omega}$$

$\mathcal{F}\{5t f(3t)\} = 5 \text{ TIMES THE ABOVE MESS}$

e) $\mathcal{F}\{f(-t)\} = \frac{3 - j\omega}{72 - \omega^2 - j18\omega}$

$\mathcal{F}\{f(2-t)\} = e^{-j2\omega} \left[\frac{3 - j\omega}{72 - \omega^2 - j18\omega} \right]$

f) ?


$$5-21) F(j\omega) = \frac{1}{j\omega+1} \cdot \frac{(j\omega-1)}{(j\omega-1)} = \frac{j\omega-1}{-\omega^2-1} = \frac{1-j\omega}{\omega^2+1}$$

$$a) F_a(j\omega) = 2 \cdot \operatorname{Re} F(j\omega) = \frac{2}{\omega^2+1}$$

$$b) F_b(j\omega) = 2 \cdot \operatorname{Im} F(j\omega) = \frac{-2j\omega}{\omega^2+1}$$

$$\begin{aligned} c) F_c(j\omega) &= j \frac{d}{d\omega} \left(\frac{1-j\omega}{\omega^2+1} \right) \\ &= j \left[\frac{-2j}{\omega^2+1} - \frac{4j\omega^2}{(\omega^2+1)^2} \right] \\ &= \frac{2\omega^2+2+4\omega^2}{(\omega^2+1)^2} \\ &= \frac{1}{(j\omega+1)^2} \end{aligned}$$

5-27) a)

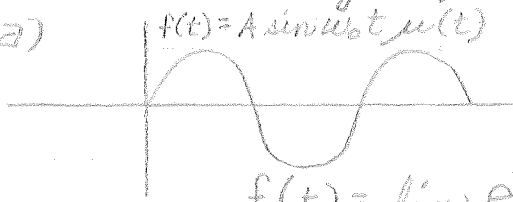

$$f(t) = \lim_{\alpha \rightarrow 0} e^{-\alpha t} \sin \omega_0 t \mu(t)$$

$$\begin{aligned} \mathcal{F}\{f(t)\} &= A \lim_{\alpha \rightarrow 0} \int_0^{\infty} e^{-\alpha t} \sin \omega_0 t e^{-j\omega t} dt \\ &= A \lim_{\alpha \rightarrow 0} \frac{\omega_0}{(\alpha+j\omega)^2 + \omega_0^2} \end{aligned}$$

$$\begin{aligned} F(j\omega) &= \frac{A\omega_0}{-j\omega^2 + \omega_0^2} \quad \pm \omega \neq \omega_0 \\ &= \delta(\omega \pm \omega_0) \quad \pm \omega = \omega_0 \end{aligned}$$

$$\begin{aligned} b) f(t) &= (1+m \cos \omega_1 t) \cos \omega_0 t \\ &= \cos \omega_0 t + m \cos \omega_1 t \cos \omega_0 t \\ &= \cos \omega_0 t + m \cos(\omega_1 - \omega_0) + m \cos(\omega_1 + \omega_0) \\ F(j\omega) &= \pi [\delta(\omega - \omega_0) + \delta(\omega + \omega_0)] + m\pi [\delta(\omega - \omega_1 + \omega_0) \\ &\quad + \delta(\omega + \omega_1 - \omega_0) + \delta(\omega - \omega_1 - \omega_0) + \delta(\omega + \omega_1 + \omega_0)] \end{aligned}$$

11-8-70

5-28) $\mathcal{F}\left\{ \sum_{n=-\infty}^{\infty} \alpha_n e^{\frac{j2\pi n t}{T}} \right\} = 2\pi \sum_{n=-\infty}^{\infty} \alpha_n \delta\left(\omega - \frac{2\pi n}{T}\right)$

$$\alpha_n = \frac{1}{T} \int_{-T/2}^{T/2} f(t) e^{-jn\omega_0 t} dt$$



$$\alpha_n = \frac{1}{T} \int_{-T/2}^0 (e^t - 3) e^{-jn\omega_0 t} dt + \frac{1}{T} \int_0^{T/2} (2e^{-t}) e^{-jn\omega_0 t} dt$$

$$= \frac{1}{T} \int_{-T/2}^0 e^{t(1-jn\omega_0)} dt - \frac{3}{T} \int_{-T/2}^0 e^{-jn\omega_0 t} dt + \frac{1}{T} \int_0^{T/2} e^{-t(1+jn\omega_0)} dt$$

$$= \frac{1}{T(1-jn\omega_0)} \left[e^{t(1-jn\omega_0)} \right]_{-T/2}^0 - \frac{3}{jTn\omega_0} \left[e^{-jn\omega_0 t} \right]_{-T/2}^0 + \frac{1}{T(1+jn\omega_0)} \left[e^{-t(1+jn\omega_0)} \right]_{0}^{T/2}$$

$$= \frac{1}{T(1-jn\omega_0)} \left[1 - e^{-\frac{T(1-jn\omega_0)}{2}} \right] - \frac{3}{jTn\omega_0} \left[1 - e^{\frac{jn\omega_0 T}{2}} \right] + \frac{1}{T(1+jn\omega_0)} \left[e^{-\frac{T(1+jn\omega_0)}{2}} - 1 \right]$$

(ARG!)

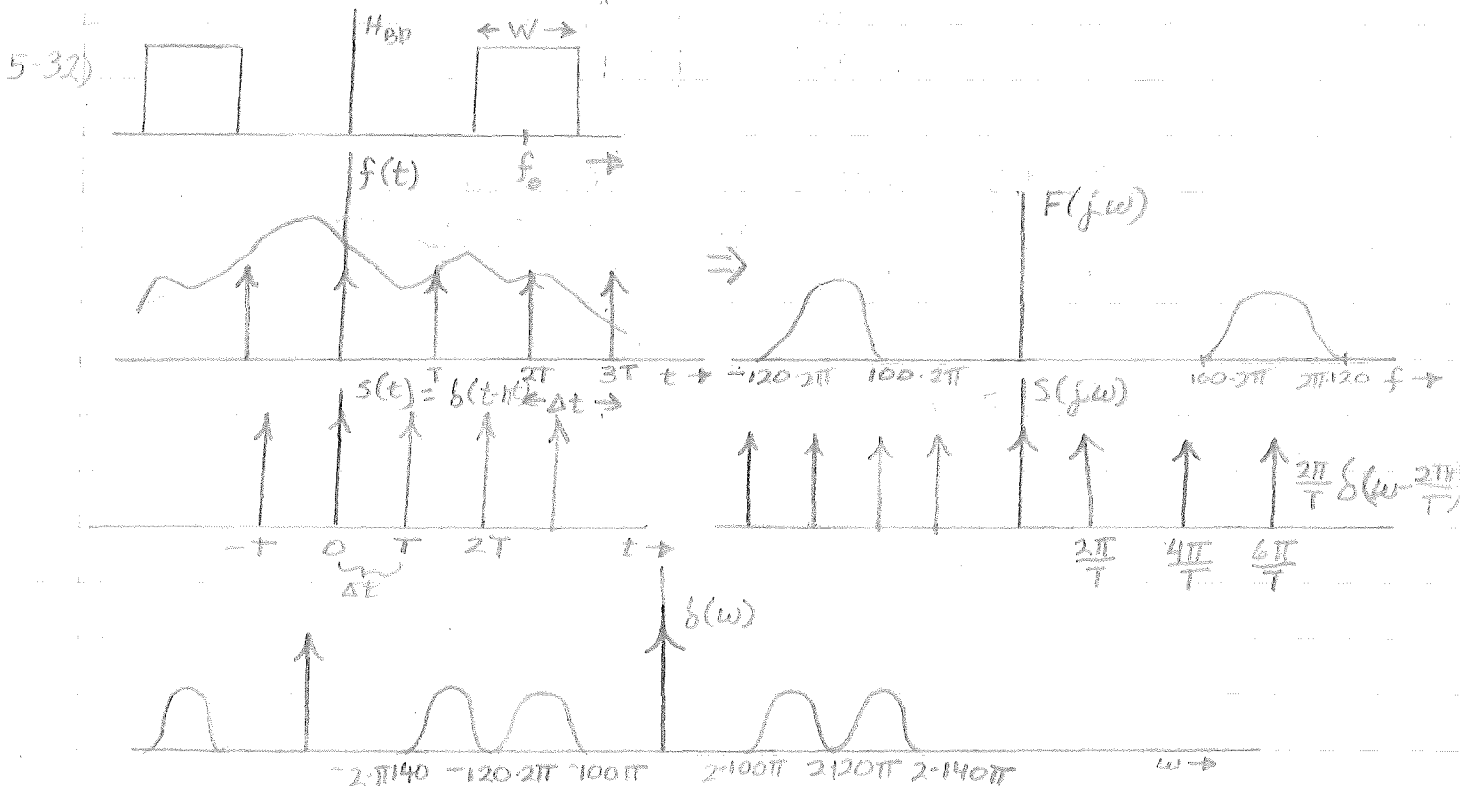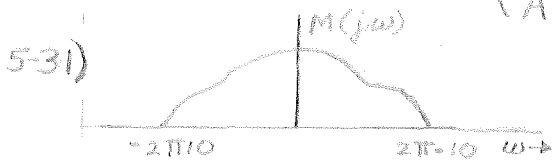


$$W = 20 \text{ HZ}$$

$$\frac{1}{2W} = \frac{1}{2 \cdot 20} = \frac{1}{40} \text{ SEC}$$

SAMPLING MUST BE AT $< \frac{1}{40} \text{ SEC}$ OR $> 40 \text{ HZ}$

$$\begin{aligned}
 5-33) \quad f(t) &= 5 \cos(2\pi \cdot 500t) \cos^2(2\pi \cdot 1000t) \\
 &= 5 \cos(2\pi \cdot 500t) \left[\frac{1}{2} + \frac{1}{2} \cos 2\pi \cdot 2000t \right] \\
 &= \frac{5}{2} \cos 2\pi \cdot 500t + \frac{5}{2} \cos 2\pi \cdot 500t \cos 2\pi \cdot 2000t \\
 &= \frac{5}{2} \cos 2\pi \cdot 500t + \frac{5}{4} \cos 2\pi \cdot 1500t + \frac{5}{4} \cos 2\pi \cdot 2500t \\
 s(t) &= \sum_{n=0}^{\infty} \delta(t - \frac{n}{4500})
 \end{aligned}$$

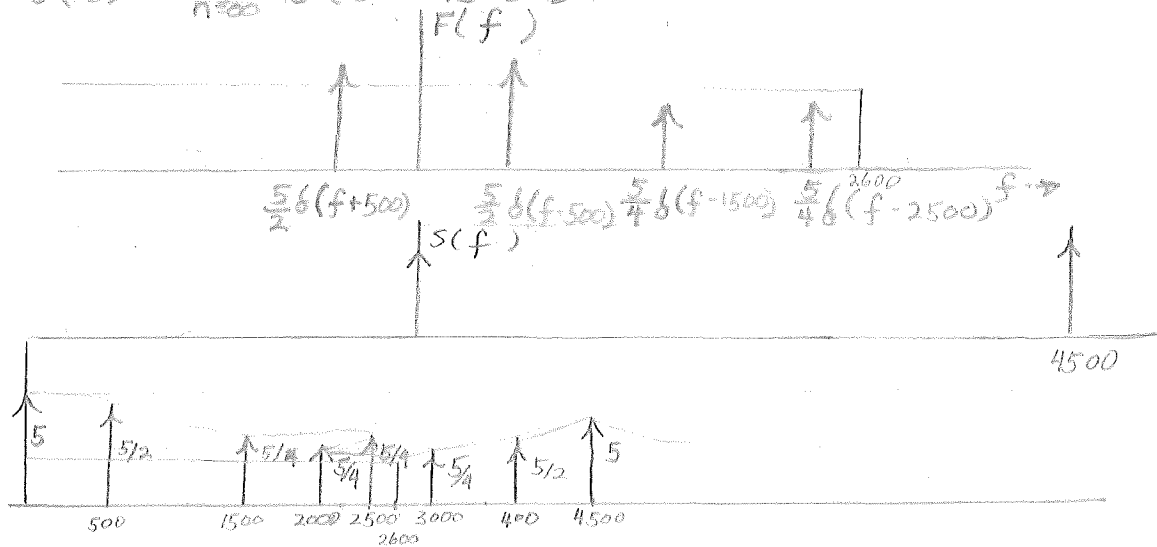

$$\begin{aligned}
 f_0(t) &= 5 + \frac{5}{2} \cos 2\pi \cdot 500t + \frac{5}{4} \cos 2\pi \cdot 1500t \\
 &\quad + \underbrace{\frac{5}{4} \cos 2\pi \cdot 2000t + \frac{5}{4} \cos 2\pi \cdot 2500t}_{\text{DISTORTION}}
 \end{aligned}$$

FOR NO DISTORTION, SAMPLING MUST OCCUR
 > 5000 HZ


11-8-70

Pp. 147-8


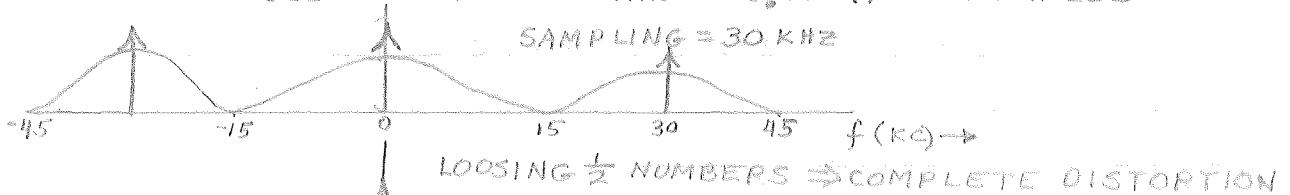
5-34) ASSUME SINGER'S RANGE IS $0 < f < 15$ KC

\Rightarrow SAMPLING RATE $> 30 \times 10^3$ HZ OR $< \frac{1}{30 \times 10^{-3}}$ SEC

$$3 \times 10^4 \frac{\text{SAMPLES}}{\text{SEC}} \cdot 3 \text{ MIN} \cdot \frac{60 \cdot \text{SEC}}{\text{MIN}} = 540 \times 10^6 \text{ SAMPLES}$$



5-35)

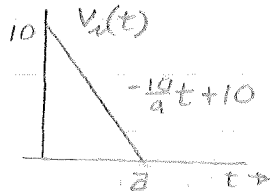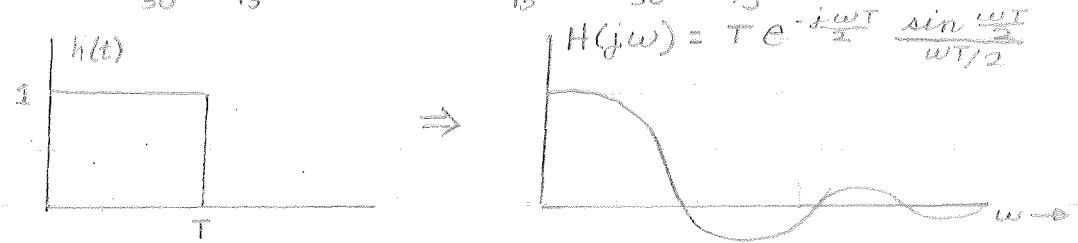

$$V(jw) = \int_0^a (-\frac{10}{a}t + 10) e^{-j\omega t} dt$$

$$= \int_0^a -\frac{10}{a}t e^{-j\omega t} dt + \int_0^a 10 e^{-j\omega t} dt$$

$$u = -\frac{10}{a}t \quad dv = e^{-j\omega t} dt$$

$$du = -\frac{10}{a} dt \quad v = \frac{-e^{-j\omega t}}{j\omega}$$

$$\frac{10}{j\omega} \left[\frac{10t}{j\omega} e^{-j\omega t} \right]_0^a - \int_0^a \frac{10}{j\omega} e^{-j\omega t} dt$$

$$+ \frac{10}{j\omega} \left[\frac{t+1}{j\omega} e^{-j\omega t} \right]_0^a$$

$$\frac{10}{j\omega} e^{-j\omega t} - \frac{10}{a\omega^2} [e^{-j\omega a} - 1]$$

$$\int_0^a 10 e^{-j\omega t} dt = \frac{-10}{j\omega} (e^{-j\omega a} - 1) = \frac{-10}{j\omega} e^{-j\omega a} + \frac{10}{j\omega}$$


$$\Rightarrow V(jw) = \frac{10}{j\omega} e^{-j\omega a} - \frac{10}{a\omega^2} e^{-j\omega a} + \frac{10}{a\omega^2} - \frac{10}{j\omega} e^{-j\omega a} + \frac{10}{j\omega}$$

$$= 10 \left(\frac{1}{j\omega} - \frac{10}{a\omega^2} \right) - \frac{10}{a\omega^2}$$

NUTZ!

(OVER!)

5-35) a)

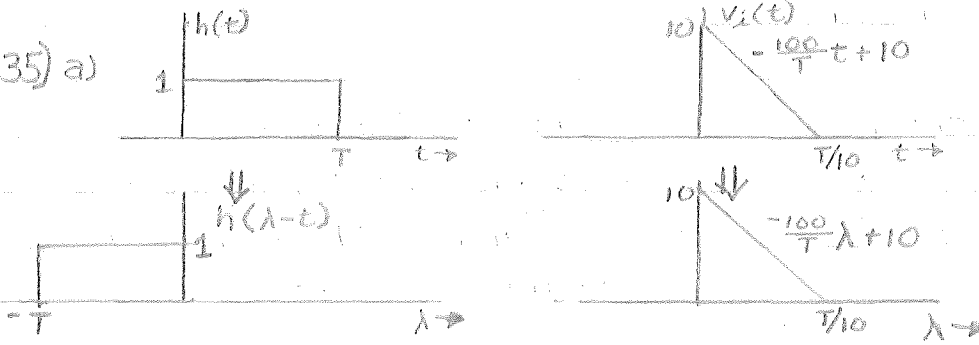

$$t \leq 0 \Rightarrow h * v = 0$$



$$h * v = \int_0^t \left(-\frac{100}{T}\lambda + 10\right) d\lambda$$

$$= \left[-\frac{50}{T}\lambda^2 + 10\lambda\right]_0^t = -\frac{50}{T}t^2 + 10t$$

$$h * v = \int_{T/10}^T \left(-\frac{100}{T}\lambda + 10\right) d\lambda$$

$$= \left[-\frac{50}{T}\lambda^2 + 10\lambda\right]_{T/10}^T = -\frac{50T^2}{4T} + \frac{10T}{2}$$

$$= -\frac{50}{4}T + \frac{20T}{4} = \frac{30T}{4}$$

$$h * v = \int_{t-T}^{T/2} \left(-\frac{100}{T}\lambda + 10\right) d\lambda$$

$$= \left[-\frac{50}{T}\lambda^2 + 10\lambda\right]_{t-T}^{T/2} = \frac{30T}{4} + \frac{50}{T}(t-T)^2 - 10(t-T)$$

$$= \frac{30T}{4} + \frac{50}{T}t^2 - \frac{100}{T}tT + \frac{50}{T}T^2 - 10t + 10T$$

$$= \frac{30T}{4} + \frac{50}{T}t^2 - 100t + 50T - 10t + 10T$$

$$t \geq \frac{21T}{2}$$

SO DAMN WHAT?!

11-9-70 Pg 148

$$\begin{aligned} 5-37) a) v_1(t) v_2(t) &= 10 e^{-.01t} \cos^2(2\pi \times 10^6 t) \mu(t) \\ &= 10 e^{-.01t} \left[\frac{1}{2} + \cos(4\pi \times 10^6 t) \right] \mu(t) \\ &= \left[5 e^{-.01t} + 10 e^{-.01(t)} \cos(4\pi \times 10^6 t) \right] \mu(t) \end{aligned}$$

$$\mathcal{F}\{v_1(t)v_2(t)\} = \frac{5}{j\omega + .01} + \frac{.01 + j\omega}{(.01 + j\omega)^2 + 16\pi^2 \times 10^{12}}$$


$$\Rightarrow \mathcal{F}\{v_0(t)\} \approx \frac{5}{j\omega + .01}$$

$$\begin{aligned} b) v_1(t) v_2(t) &= 10 e^{-.01t} \cos 2\pi \cdot 10^6 t \sin 2\pi \cdot 10^6 t \mu(t) \\ &= 5 e^{-.01t} \sin 4\pi \cdot 10^6 t \mu(t) \end{aligned}$$

$$\mathcal{F}\{v_1(t)v_2(t)\} = \frac{5 \cdot 4\pi \cdot 10^6}{(.01 + j\omega)^2 + 16\pi^2 \cdot 10^{12}}$$

$$\Rightarrow \mathcal{F}\{v_0(t)\} \approx 0$$

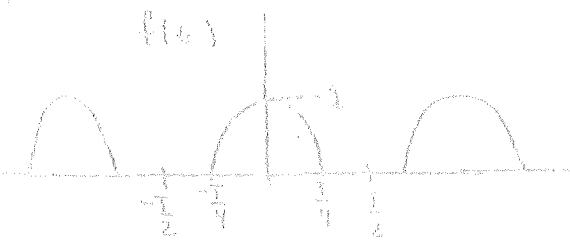Example: $f(t) = \cos(\omega_0 t)$ for $0 \leq t \leq T/4$ and $f(t) = \cos(\omega_0 t)$ for $T/4 \leq t \leq T/2$



$$T = \frac{\pi}{\omega_0}$$

$b_n = 0$ $\forall n$ since $f(t)$ is even function

$$a_n = \frac{2}{T} \int_0^{T/4} \cos \omega_0 t \cos n \omega_0 t dt + \frac{2}{T} \int_{T/4}^{T/2} \cos \omega_0 t \cos n \omega_0 t dt$$

$$= \frac{2}{T} \left\{ \frac{\sin(n+1)\omega_0 t}{(n+1)\omega_0} \Big|_0^{T/4} + \frac{\sin(n-1)\omega_0 t}{(n-1)\omega_0} \Big|_{T/4}^{T/2} \right\}$$

$$= \frac{1}{\pi} \left\{ \frac{1}{n+1} \left[\sin(n+1)\frac{\pi}{2} - 0 \right] + \frac{1}{n-1} \left[\sin(n-1)\frac{\pi}{2} - 0 \right] \right\}$$

$$= \frac{1}{\pi} \left[\frac{\sin(n+1)\frac{\pi}{2}}{n+1} + \frac{\sin(n-1)\frac{\pi}{2}}{n-1} \right]$$

$$= \frac{1}{2} \left[\frac{\sin(n+1)\frac{\pi}{2}}{(n+1)\frac{\pi}{2}} + \frac{\sin(n-1)\frac{\pi}{2}}{(n-1)\frac{\pi}{2}} \right]$$

Use $\frac{\sin x}{x}$ form.

$$a_0 = \frac{2}{\pi} \Rightarrow \text{dc-value} = \frac{a_0}{2} = \frac{1}{\pi} \quad \checkmark \text{ (correct for } \frac{1}{2} \text{ wave)}$$


$$a_1 = \frac{1}{2} \left[\frac{\sin \frac{\pi}{2}}{\frac{\pi}{2}} + 1 \right] = \frac{1}{2}$$

$$a_2 = \frac{1}{2} \left[\frac{\sin \frac{3\pi}{2}}{\frac{3\pi}{2}} + \frac{\sin \frac{\pi}{2}}{\frac{\pi}{2}} \right] = \frac{1}{2} \left[-\frac{2}{3\pi} + \frac{2}{\pi} \right] = \frac{1}{2} \left[\frac{4}{3\pi} \right] = \frac{2}{3\pi}$$

$$n = 0 \Rightarrow \sin(n \pm 1)\frac{\pi}{2} = 0 \quad \text{EXCEPT } n=1$$

$$n = \text{EVEN} \Rightarrow \sin(n+1)\frac{\pi}{2} = (-1)^{\frac{n}{2}} \quad \Rightarrow a_{n_{\text{odd}}} = \frac{1}{\pi} \left[\frac{(-1)^{\frac{n}{2}}}{n+1} + \frac{(-1)^{\frac{n}{2}+1}}{n-1} \right]$$
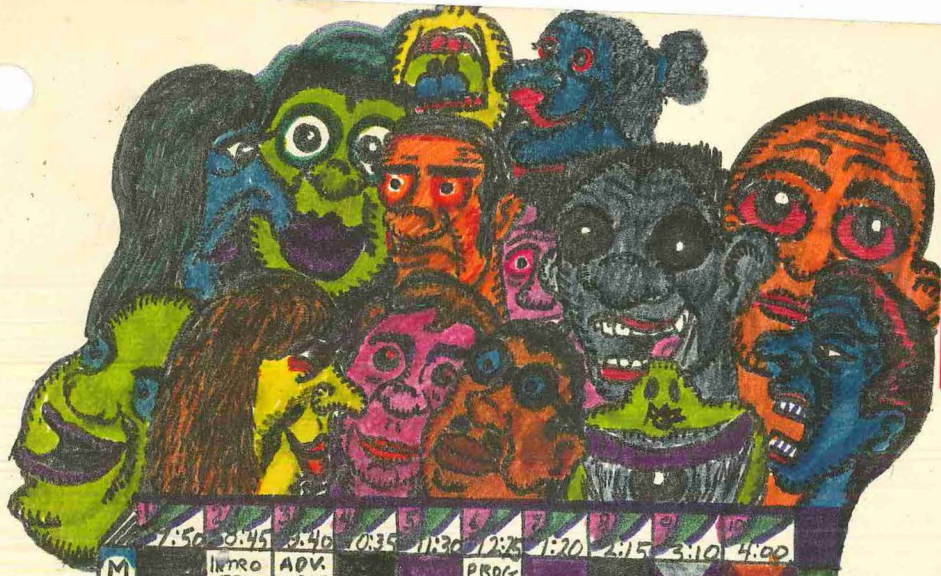
$$\sin(n-1)\frac{\pi}{2} = (-1)^{\frac{n}{2}+1}$$



E. Sci.


	7:50	8:45	9:40	10:35	11:30	12:25	1:20	2:15	3:10	4:00
MORNING		INTRO TO PROB DOI AVS	ADV. CALC. F208 DO			PROG PRINC A241 TFK				
AFTERNOON		INTRO TO PROB DOI AVS	ADV. CALC. F208 DO					E.SCI III TFK		
EVENING						PROG PRINC A241 TFK		E.SCI II TFK		
NIGHT		INTRO TO PROB DOI AVS	ADV. CALC F208 DO			PROG PRINC A241 TFK		E.SCI II TFK		
WEEKEND		INTRO TO PROB DOI AVS	ADV. CALC F208 DO			PROG PRINC A241 TFK		E.SCI III TFK		

METHOD OF SIGNAL AND
SYSTEMS ANALYSIS
COOPER; MCGILLEM

9-11-70

FIRST SEVEN CHAPTERS

9-15-70

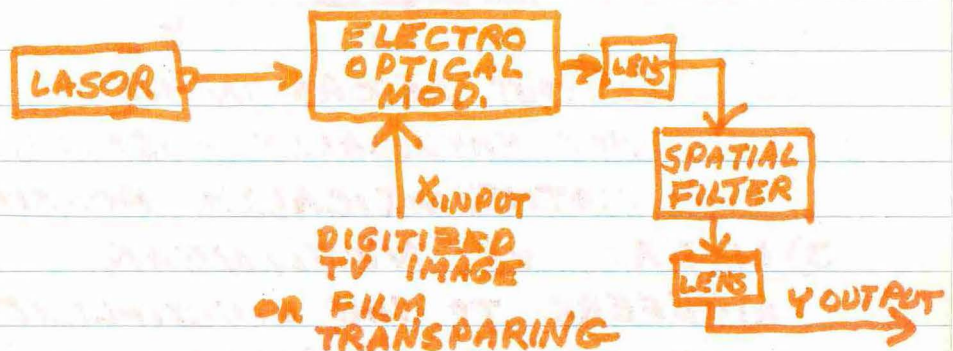

MUST HAVE MATHEMATICAL MODEL
TO FIT EACH COMPONENT,
FOR INPUT/OUTPUT

FOR BLACK BOX:

$$a_n y^n(t) + a_{n-1} y^{n-1}(t) + \dots + a_0 y(t)$$

$$= b_n x^m(t) + b_{m-1} x^{m-1}(t) + \dots + b_0 x(t)$$

\Rightarrow n^{TH} ORDER D.E.

LINEAR D.E.


CONSTANT COEFFICIENT D.E.

CLASSIFICATION OF SYSTEMS

1) ORDER: n TH ORDER OF HIGHEST ORDER DEPENDENT VARIABLE

2) CAUSAL, NON-CAUSAL:

a) NON CAUSAL

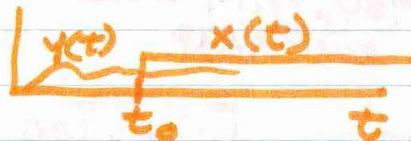


(OUTPUT BEFORE INPUT

NOT PHYSICALLY POSSIBLE, YET MATHEMATICALLY POSSIBLE)

3) LINEAR VS NONLINEAR

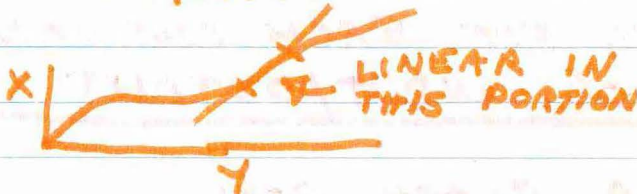a) REFERS TO THE MULTIPLICITY OF THE DERIVATIVES IN THE EQUATION



b) LINEARITY WILL IMPLY SUPERPOSITION (IF x_1 RESULTS IN OUTPUT y_1 , & x_2 YIELDS y_2 , THEN $x_1 + x_2$ INPUT YIELDS $y_1 + y_2$ OUTPUT)

4) FIXED TIME VS. TIME VARIANT

CONSTANT COEFF VS. TIME VARIANT COEFF. IN O.E.



5) LUMPED PARAMETER VS.
DISTRIBUTED PARAMETER

a) LUMPED \Rightarrow ORDINARY D.E. \neq D.E.

b) DIST. PARA \Rightarrow PARTIAL D.E.

6) CONTINUOUS OR DISCRETE
D.E. DIFFERENCE EQUATION

7) INSTANTANEOUS VS. DYNAMIC
COMBINATIONAL LOGIC | MEMORY (ENERGY
RESISTIVE STORAGE)

9-15-70

NORMAL FORM ON EQNS. n 1ST ORDER
WITH n VARIABLES ("STATE VARIABLES")

DEFINE STATES: $q_1(t), q_2(t), \dots, q_n(t)$

WRITE SYSTEM OF EQNS:

$$q_1'(t) = a_{11}q_1(t) + a_{12}q_2(t) + \dots + a_{1n}q_n(t) + b_1x(t)$$

$$q_2'(t) = a_{21}q_1(t) + a_{22}q_2(t) + \dots + a_{2n}q_n(t) + b_2x(t)$$

$$\vdots$$
$$q_n'(t) = a_{n1}q_1(t) + \dots + a_{nn}q_n(t) + b_nx(t)$$

OUTPUT

$$y(t) = c_1q_1(t) + c_2q_2(t) + \dots + c_nq_n(t)$$

$$\underline{Q}'(t) = \begin{bmatrix} \dot{q}_1(t) \\ \dot{q}_2(t) \\ \dot{q}_n(t) \end{bmatrix} \quad C = \begin{bmatrix} c_1 \\ c_2 \\ c_n \end{bmatrix}$$

$$\underline{Q}(t) = \begin{bmatrix} q_1(t) \\ \vdots \\ q_n(t) \end{bmatrix}$$

$$A = \begin{bmatrix} a_{11} & a_{12} & \dots & a_{1n} \\ \vdots & \vdots & & \vdots \\ a_{n1} & a_{n2} & & a_{nn} \end{bmatrix}$$


$$b = \begin{bmatrix} b_1 \\ b_2 \\ b_n \end{bmatrix} \quad x(t) \text{ IS A SCALAR}$$

$$\underline{Q}'(t) = A \underline{Q}(t) + b x(t)$$

$$Y(t) = C^T \underline{Q}(t)$$

PROBLEM EXAMPLE

2.7a)

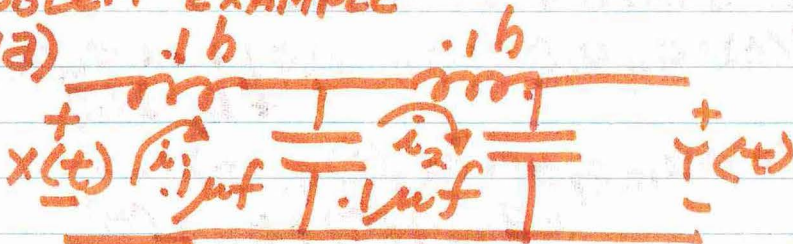

$$x(t) = .1 \frac{di_1}{dt} + 10^7 \int_{-\infty}^t [i_1(\lambda) - i_2(\lambda)] d\lambda$$

$$0 = 10^7 \int_{-\infty}^t [i_2(\lambda) - i_1(\lambda)] d\lambda + .1 \frac{di_2}{dt}$$

$$+ 10^7 \int_{-\infty}^t i_2(\lambda) d\lambda$$

(CONT PG. FOLLO)

TO SOLVE:

WHAP ON LAPLACE

$s \rightarrow \frac{1}{s}$

$$\frac{I_1(s)}{s} \Leftrightarrow \int_0^t i_1(\lambda) d\lambda$$

$$sI(s) - i(0) \Leftrightarrow \frac{d i}{dt}$$

$$a_{11} I_1(s) + a_{12} I_2(s) = \frac{x(s)}{s}$$

$$a_{21} I_1(s) + a_{22} I_2(s) = 0$$

$$\underline{\tilde{I}} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \quad A = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \quad \underline{V_s} = \begin{bmatrix} \frac{V_s}{s} \\ 0 \end{bmatrix}$$

$$\underline{A} \underline{I} = \underline{V_s} \Rightarrow \underline{I} = \underline{A}^{-1} \underline{V_s}$$

KRAMER:

$$I_1 = \frac{\begin{vmatrix} \frac{x}{s} & a_{12} \\ 0 & a_{22} \end{vmatrix}}{\begin{vmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{vmatrix}}$$

(CONT FROM 2 PGS AGO)

$$Y(t) = 10^7 \int_{-\infty}^t i_2(\lambda) d\lambda$$

GET RID OF INTEGRALS

$$Y'(t) = 10^7 i_2(t) \Rightarrow Y''(t) = 10^7 \frac{d^2 i_2}{dt^2}$$

FROM BEFORE

$$\frac{d^2 i_2}{dt^2} = 10^8 \int i_1(\lambda) d\lambda - 10^8 \int i_2(\lambda) d\lambda - 10^8 \int i_2(\lambda) d\lambda$$

$$\frac{d^2 i_2}{dt^2} = 10^8 i_1 - 2 \times 10^8 i_2$$

$$\frac{d^3 i_2}{dt^3} = 10^8 \frac{d i_1}{dt} - 2 \times 10^8 \frac{d i_2}{dt}$$

← PLUG IN FROM ABOVE →

FROM THE PREVIOUS

$$10^8 \int i_1 = 10^{-5} Y''(t) + 20 Y(t)$$

$$10^8 \frac{d i_1}{dt} = 10^{-7} Y'''(t) + 2 \times 10^{15} Y^{(2)}(t)$$

PLOP THESE QUANTITIES


INTO ORIGINAL MESH EQNS.

$$X(t) = 10^{-16} Y'''(t) + 2 \times 10^{-6} Y^{(2)}(t) + 10^{-9} Y^2(t) + 2Y(t) - Y(t)$$

HOWEVER, SOMEONE SKREWED UP THE PROBLEM, SO 'DE ANSWER AIN'T RIGHT

9-17-70

7

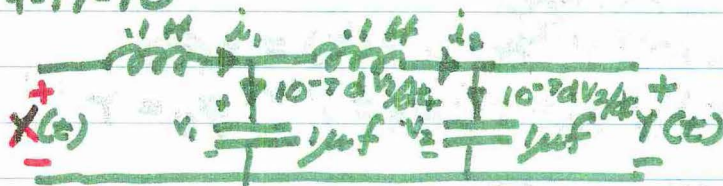

(M CONTROLS MAG. FIELD)

LET $q_1 = i_1$, $q_2 = i_2$, $q_3 = V_1$, $q_4 = V_2 (= Y(t))$

$$\left. \begin{aligned} X(t) - V_1 &= .1 \frac{di_1}{dt} \\ V_1 - V_2 &= .1 \frac{di_2}{dt} \end{aligned} \right\} \begin{aligned} X(t) - q_3 &= .1 \frac{dq_1}{dt} \\ q_3 - q_4 &= .1 \frac{dq_2}{dt} \end{aligned}$$

$$q_1' = -10q_3 + 10X(t)$$

$$q_3' = 10q_3 - 10q_4$$

$$(i = C \frac{dV}{dt})$$

$$\left. \begin{aligned} i_1 &= i_2 + 10^{-7} \frac{dV_1}{dt} \\ i_2 &= 10^{-7} \frac{dV_2}{dt} \end{aligned} \right\} \begin{aligned} q_1 &= q_2 + 10^{-7} q_3' \\ q_2 &= 10^{-7} \frac{dq_4}{dt} \end{aligned}$$

NORMAL FORM:

$$q_1' = -10q_3 + 10X(t)$$

$$q_2' = 10q_3 - 10q_4$$

$$q_3' = 10^7 q_1 - 10q_2$$

$$q_4' = 10^7 q_2$$

$$Y = q_4$$

NORMAL FORM EQUATIONS NOT UNIQUE

Faded handwritten notes in red ink, possibly showing alternative equations or derivations.

(FROM SAME SYSTEM)

$$10^{-16} y^{(4)} + 3 \times 10^{-8} y^{(2)} + y = x$$

LET $q_1 = y$; $q_2 = y'$; $q_3 = y''$; $q_4 = y'''$

$$q_1^{(1)} = q_2$$

$$q_2^{(1)} = q_3$$

$$q_3^{(1)} = q_4$$


$$q_4^{(1)} = -3 \times 10^8 q_2 - 10^{16} q_1 + 10^{16} x$$

$$y = q_1$$

SAYS SAME THING AS PREVIOUS NORMAL FORM, IF INITIAL CONDITIONS ARE KNOWN

9-18-70

2-10)

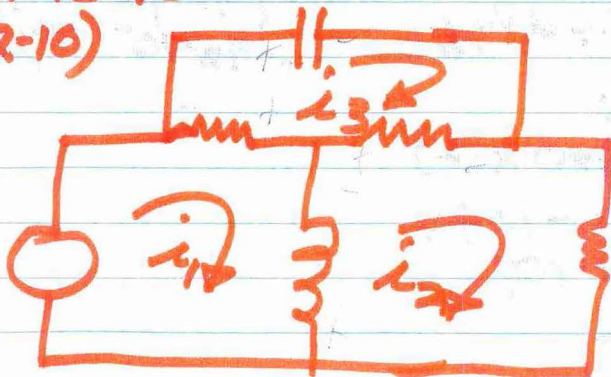

$$y = i_3$$

$$x = i_1 + i_2 - i_2 - i_3$$

$$0 = i_2 - i_1 + i_2 - i_3 + i_2$$

$$0 = i_3 - i_1 + i_3 - i_2 + \int i_3$$

$$x = i_1 + i_1' - y' - i_3$$

$$0 = y' - i_1' + 2y - i_3$$

$$0 = 2i_3 - i_1 + y + \int i_3$$

$$x(t) - y(t) = \int i_3(t) \Rightarrow x'(t) - y'(t) = i_3$$

$$x = i_1 + i_1' - y' - x' + y'$$

$$\text{a) } 0 = y' - i_1' + 2y - x' + y'$$

$$\hookrightarrow 0 = 2x' - 2y' - i_1 + y + x - y$$

$$\hookrightarrow i_1 = 2x' - 2y' + x$$

$$i_1' = 2x'' + 2y'' + x'$$

PLUG INTO b

$$0 = y' - 2x'' + 2y'' - x' + 2y - x' + y'$$

$$\text{ALGEBRA} \Rightarrow 2y'' + 4y' + 2y = 2x'' + 2x'$$

$$2y'' + 2y' + y = x' + x''$$

WHAP ON LAPLACE


$$(s^2 + 2s + 1)Y(s) = (s^2 + s)X(s)$$

$$(s+1)^2 Y(s) = s(s+1)X(s)$$

$$\text{OR } Y' + Y = X'$$

\therefore SYSTEM IS OF FIRST ORDER

2-10)

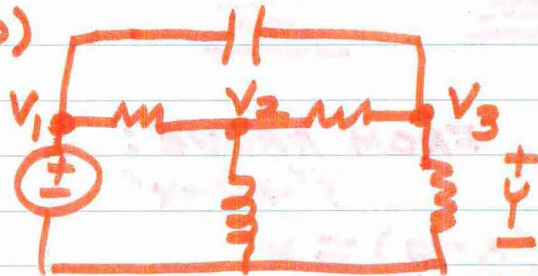

$$V_1 = x(t); \quad V_3 = Y(t)$$

$$\text{ON NODE 2: } V_1 - X + \frac{1}{s} \int V_2 + V_2 - Y = 0$$

$$\text{ON NODE 3: } Y - V_2 + Y + Y' - X' = 0$$

(CONT.)

SOLVE FOR V_2 :

$$V_2 = 2Y + Y' - X'$$

PLUG INTO TOP EQ:
 $2Y + Y' - X' - X + \int (2Y + Y' - X') + 2Y + Y' - X' - Y = 0$


DIFFERENTIATE

$$2Y' + Y'' + X'' - X' + 2Y + Y' - X' + 2Y' + Y'' - X'' - Y' = 0$$

$$\Rightarrow Y'' + 2Y' + Y = X'' + X$$

PUT IN NORMAL FORM

STATE VARIABLE IS CAP. V
 $+q -$

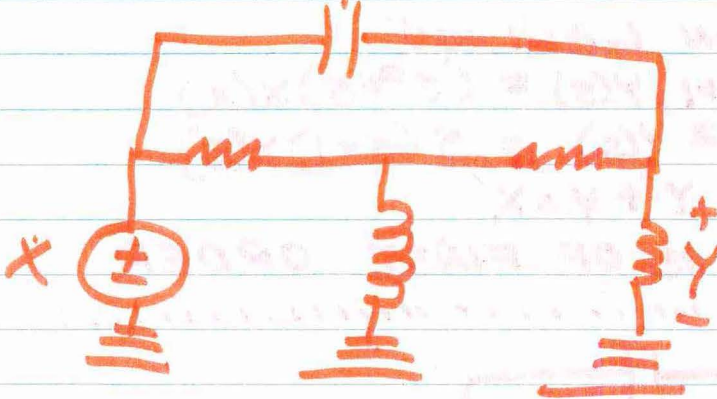

$$q = X - Y \quad \text{FROM ABOVE:}$$

$$q' = X' - Y' \quad Y' + Y = X'$$

$$\therefore Y' + (X - q) = X'$$

$$\Rightarrow Y' = X' - X + q$$

$$q' = X' - Y' \Rightarrow q' = -q + X(t)$$

$$\text{ALSO } Y = X - q$$

CHAPTER III

CLASS OF SIGNALS

- ① PERIODIC VS NON-PERIODIC (APERIODIC)
- ② RANDOM VS. DETERMINISTIC
- ③ ENERGY VS POWER


9-23-70

③ ENERGY VS POWER

A) ENERGY: $x(t)$ WHICH SATISFIES $E = \int_{-\infty}^{\infty} x^2(t) dt < \infty$

$$(E = \int P(t) dt)$$

$$P = I^2 R = V^2 / R$$

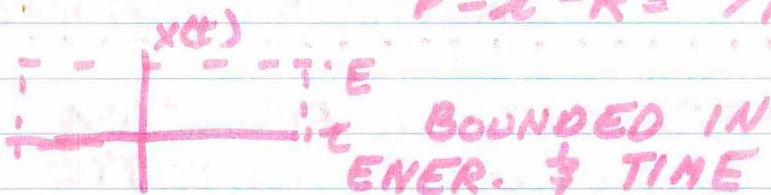

B) POWER SIGNALS.

(i) PERIODIC SIGNALS
TALK OF AVER PWR.

$$P_{AVE} = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} x^2(t) dt$$

IF $x(t)$ IS A PWR SIGNAL:

$$0 < P = \lim_{T \rightarrow \infty} \frac{1}{2T} \int_{-T}^T x^2(t) dt < \infty$$

(CONT.)

EX) $x(t) = e^{-at}$; $-\infty < t < \infty$

$$E = \int_{-\infty}^{\infty} e^{-2at} dt$$

$$= \frac{1}{-2a} e^{-2at} \Big|_{-\infty}^{\infty} \rightarrow \infty$$

∴ NOT ENERGY SIGNAL

$$P = \lim_{T \rightarrow \infty} \frac{2}{T} \int_{-T}^T e^{-2at} dt$$

$$= \lim_{T \rightarrow \infty} \frac{2}{T} \left[\frac{-1}{2a} e^{-2at} \right]_{-T}^T$$

$$= \lim_{T \rightarrow \infty} \left(\frac{1}{aT} e^{-2aT} + \frac{1}{aT} e^{2aT} \right)$$

MUST APPLY L'HOSPITAL'S RULE

REPRESENTING FUNCTIONS FROM BASE FUNCTION

$$x(t) = \sum_{n=0}^{\infty} a_n \phi_n(t)$$

1) SHOULD BE ABLE TO FIND a_n WITHOUT KNOWING ANY OTHERS (CALLED FINALITY OF COEFF)


- FINALITY OF COEFFICIENTS: OBTAINED BY INSISTING ON

ORTHOGONAL BASIC FUNC. $\phi_n(t)$

ORTH: $\int_{t_1}^{t_2} \phi_n(t) \phi_m(t) dt = \begin{cases} 0 & \text{IF } n \neq m \\ \lambda_n & \text{IF } n = m \end{cases}$

INNER PROD OR DOT PROD

IF BASES ARE ORTH

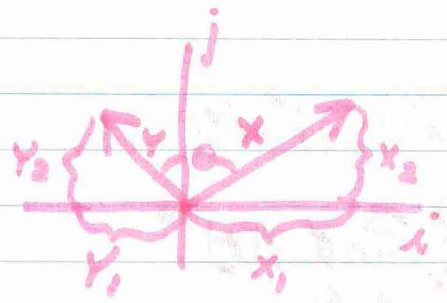

$$\hat{x} = x_1 i + x_2 j$$

$$\hat{y} = y_1 i + y_2 j$$

$$\hat{x} \cdot \hat{y} = |\hat{x}| |\hat{y}| \cos \theta = \sum_{\ell=1}^2 x_{\ell} y_{\ell}$$

$$= x_1 y_1 + x_2 y_2$$

ANALOGOUS TO BASIC FUNCTION

$$\int_{t_1}^{t_2} \phi_n(t) x(t) dt = \int_{t_1}^{t_2} \phi_n(t) \sum_{n=0}^{\infty} a_n \phi_n(t) dt$$

$$= \sum_{n=0}^{\infty} a_n \int_{t_1}^{t_2} \phi_n(t) \phi_n(t) dt$$

$\lambda_j \Rightarrow (n=j)$

$$= a_j \lambda_j$$

$$\lambda_j = \int_{t_1}^{t_2} \phi_j(t) \phi_j(t) dt$$

$$a_j = \frac{1}{\lambda_j} \int_{t_1}^{t_2} \phi_j(t) x(t) dt$$

9-23-70

$$I = \int_{t_1}^{t_2} [x(t) - \hat{x}(t)]^2 dt$$

$$= \int_{t_1}^{t_2} \left[x(t) - \sum_{n=0}^M \hat{a}_n \phi_n(t) \right]^2 dt$$

$$\hat{a}_n = a_n = \frac{1}{\lambda_n} \int_{t_1}^{t_2} x(t) \phi_n(t) dt$$

$$I = \int_{t_1}^{t_2} \left[x(t)^2 - 2x(t) \sum \hat{a}_n \phi_n(t) \right] dt$$

$$+ \sum_{i=0}^M \sum_{j=0}^M a_i a_j \phi_i(t) \phi_j(t) dt$$

$$I = \int_{t_1}^{t_2} x^2(t) dt - 2 \sum a_n \int_{t_1}^{t_2} x(t) \phi_n(t) dt$$

$$+ \sum \sum a_i a_j \int_{t_1}^{t_2} \phi_i(t) \phi_j(t) dt$$

WANT TO MINIMIZE I , \rightarrow ALL STATEMENTS MAY BE TREATED AS A CONSTANT WITH a_n IN THEM. THUS, STATEMENT REDUCES TO:

$$I = K - 2 \sum_{n=0}^M \hat{a}_n a_n \lambda_n$$

$$I = K - 2 \sum_{n=0}^M \hat{a}_n a_n \lambda_n + \sum_{n=0}^M \hat{a}_n^2 \lambda_n$$

$$I = K + \sum_{n=0}^M \lambda_n (a_n - \hat{a}_n)^2$$

$$- \sum_{n=0}^M a_n^2 \lambda_n$$

MINIMUM OCCURS AT $a_n = \hat{a}_n$

$$I = K - \sum_{n=0}^M a_n^2 \lambda_n = \text{MINIMUM M.S. ERROR}$$

→ = ENERGY OF ERROR

$$\frac{\text{ERROR EN.}}{\text{SIGNAL EN}} = \frac{I}{K} = 1 - \frac{\sum_{n=0}^M a_n^2 \lambda_n}{K}$$


RATIO BETWEEN 0 & 1

$$\int_{t_1}^{t_2} x^2(t) dt = \sum_{n=0}^{\infty} a_n^2 \lambda_n$$

PARSEVAL'S THEOR.

3-11 $\phi_1(t) = \sqrt{2} e^{-t}$

$$\phi_2(t) = A e^{-2t} + B e^{-t}$$

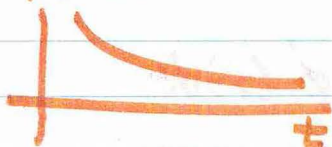

$$\lambda_1 = \int_0^{\infty} \phi_1(t) dt = 1$$

$$0 = \int_0^{\infty} \phi_1(t) \phi_2(t) dt$$

$$= \int_0^{\infty} (\sqrt{2} A e^{-3t} + \sqrt{2} B e^{-2t}) dt$$

$$= -\frac{\sqrt{2}A}{3} e^{-3t} - \frac{\sqrt{2}A}{2} e^{-2t} \Big|_0^{\infty}$$

$$\Rightarrow A = -\frac{3}{2} B$$


$$\int_0^{\infty} (A^2 e^{-4t} + 2AB e^{-3t} + B^2 e^{-2t}) dt = 1$$

$$= \frac{A^2}{4} + \frac{2}{3} AB + \frac{B^2}{2} = 1$$

$$\text{PLUG IN } A = -\frac{3}{2} B$$

$$\Rightarrow B = \pm 4 \Rightarrow A = \mp 6$$
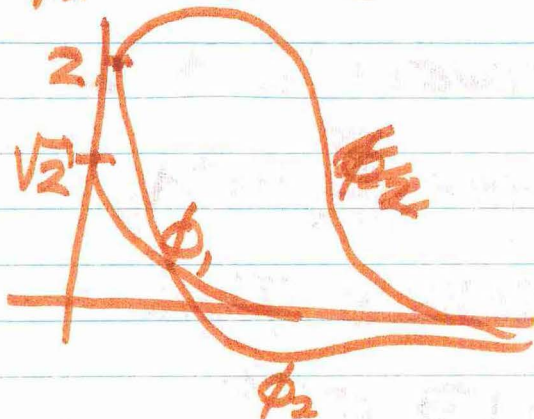
$$\text{LET: } \phi_2(t) = 6e^{-3t} + 4e^{-2t}$$



TRYING TO REPRESENT $x(t)$

$$a_1 = \frac{1}{\lambda_1} \int_0^{\infty} x(t) \phi_1(t) dt$$

$$= \int_0^{\infty} 10e^{-\frac{1}{2}t} \sqrt{2} e^{-t} dt$$

$$= 4\sqrt{2}$$

$$\therefore \hat{x} = \sum_{n=1}^{\infty} a_n \phi_n(t) = a_1 \phi_1(t) + a_2 \phi_2(t)$$

(CONT.)

$$= (4\sqrt{2})(\sqrt{2}e^{-t}) + a_2 [6e^{-2t} - 4e^{-t}] \quad 17$$

COMPUTE a_2 ,

$$\text{THEN } \frac{I}{K} = 1 - \frac{\sum_{n=1}^2 a_n \lambda_n}{\int_0^{\infty} x^2(t) dt}$$

9-24-70

$$\text{ERROR} = 1 - \frac{\sum \lambda_n a_n^2}{\int x^2(t) dt}$$

WALSH (4 UNITS)

$$\begin{bmatrix} 1 & 1 & 1 & 1 \\ 1 & 1 & -1 & -1 \\ 1 & -1 & 1 & 1 \\ 1 & -1 & -1 & 1 \end{bmatrix} \begin{bmatrix} 2 \\ 0 \\ 4 \\ 2 \end{bmatrix} = \frac{1}{2} \begin{bmatrix} 8 \\ 4 \\ 4 \\ 4 \end{bmatrix} = \begin{bmatrix} 4 \\ 2 \\ 2 \\ 2 \end{bmatrix} \quad W$$

$$w_j = \sum_{k=1}^4 c_k \frac{1}{K} x_k$$

FOURIER BASIS FUNCTIONS (EXP.)

$$\text{BASIS FUNC} \rightarrow e^{jn\omega_0 t} \quad n = 0, \pm 1, \pm 2, \dots$$

$$\omega_0 = \frac{2\pi}{T} = 2\pi f_0$$

SHOW $\phi_n(t)$ ARE ORTHOGONAL ∇

FIND λ TO MAKE THEM ORTHONORMAL

$$\int_{t_0}^{t_0+T} \phi_n(t) \phi_k^*(t) dt$$

$$= \int_{t_0}^{t_0+T} e^{jn\omega_0 t} e^{-jk\omega_0 t} dt$$

(CONT. OF PAGE)

$$\begin{aligned}
&= \int_{t_0}^{t_0+T} e^{j(n-k)\omega_0 t} dt \\
&= \frac{1}{j(n-k)\omega_0} e^{j(n-k)\omega_0 t} \Big|_{t_0}^{t_0+T} \\
&\quad \omega_0 = \frac{2\pi}{T} \\
&= \frac{1}{j(n-k)\omega_0} e^{j(n-k)\pi 2t_0/T} e^{j(n-k)\frac{2\pi T}{T}} \\
&\quad - \frac{1}{j(n-k)\omega_0} e^{j(n-k)\frac{2\pi t_0}{T}} \\
&= \frac{1}{j(n-k)\omega_0} e^{j(n-k)\frac{2\pi t_0}{T}} \left(e^{j(n-k)2\pi} - 1 \right) \\
&\quad \quad \quad \downarrow \\
&\quad \quad \quad e^{j(2\pi M)2\pi} \\
&\quad \quad \quad = \cos 2\pi M + j \sin 2\pi M - 1
\end{aligned}$$

$\therefore \lambda_n = 0$ FOR ALL $n \neq k$

MUST USE L'HOPITAL'S RULE

$$\lim_{(n-k) \rightarrow 0} \frac{j 2\pi e^{j(n-k)2\pi}}{j \omega_0} = T = \lambda$$


EXP. ORTHOGONAL, BUT NOT ORTHONORMAL

TO BE ORTHONORMAL:

$$\phi_n = \frac{1}{\sqrt{T}} e^{jn\omega_0 t}$$

9-25-70

19

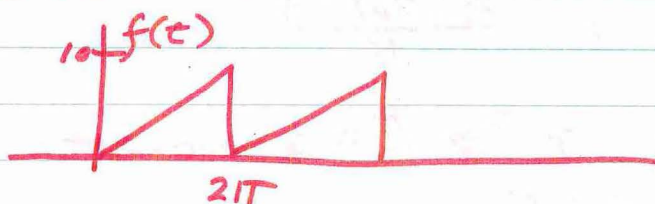

$$f(t) = \frac{5}{\pi} t \begin{cases} 0 \leq t \leq 2\pi \\ 0 \text{ ELSEWHERE} \end{cases}$$

$$T = 2\pi \Rightarrow \frac{2\pi}{T} = 1$$

$$C_n = \frac{1}{T} \int_0^{2\pi} f(t) \phi^*(t) dt \quad (\phi_n(t) = e^{jn\omega t})$$

$$= \frac{1}{2\pi} \int_0^{2\pi} \frac{5t}{\pi} e^{-jnt} dt$$

$$du = \frac{5}{\pi} dt \quad v = \frac{1}{jn} e^{-jnt} = v$$

$$C_n = \frac{-1}{2\pi} \frac{5t}{\pi} \frac{1}{jn} e^{-jnt} \Big|_0^{2\pi} + \int_0^{2\pi} \frac{1}{jn} e^{-jnt} \frac{5}{\pi} dt$$

$$= \frac{-5(1)}{2\pi^2 jn} - 0 + \left[\frac{1}{(jn)^2} e^{-jnt} \right]_0^{2\pi}$$

$$= \frac{5}{2\pi^2 jn} ; n = 0, \pm 1, \pm 2, \dots$$

BUT $n \neq 0$

$$\Rightarrow C_n = \frac{5}{2\pi^2 jn} \quad n = \pm 1, \pm 2, \pm 3, \dots$$

$$\star C_0 = \text{D.C. VALUE} = 5$$

$$C_0 = 5$$

$$C_n = \frac{j5}{2\pi^2 n} ; n = \pm 1, \pm 2, \pm 3, \dots$$

$$f(t) = 5 \pm \frac{j5}{2\pi^2} e^{+j\omega t} \pm \frac{j5}{4\pi^2} e^{-j\omega t} \dots$$

(CONT.)

$$F.S.E. = 1 - \frac{\sum |a_n|^2 \lambda_n}{K}$$

$$(f(t))^2 = 3t^2 \Rightarrow E = \frac{1}{3} \cdot 100 \cdot 2\pi$$

$$C_0 = a_0 = 5$$

$$C_1 = |a_1| = \frac{5}{2\pi^2}$$

$$C_1 = |a_2| = \frac{5}{2\pi^2} \quad \lambda_n = \frac{1}{T}$$

CHUG & PLUG & CHUG

PARCEVAL'S THEOREM:

SUM OF INFINITE COEFF EQUAL
TO TOTAL OF ENERGY

TEST OVER;

OVER FOURIER-MALSH
BASIS FUNCTIONS

9-29-70

UNIT IMPULSE


$$\delta(t) = \begin{cases} 0, & t \neq 0 \\ \downarrow, & t = 0 \end{cases}$$

REFERS TO AREA, NOT MAGN.

GENERATE $\delta(t)$ VIA GAUSSIAN OPERATOR

$$G = \frac{1}{\sqrt{\pi}a} e^{-\frac{x^2}{2a^2}}$$

(BELL SHAPED CURVE)

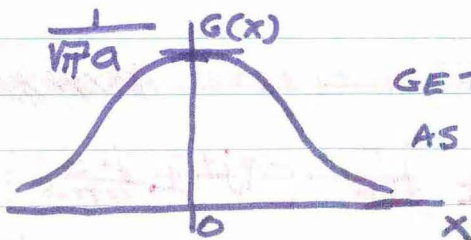


GET NARROWER
AS a GETS
SMALLER

(CONT)

$$\int \delta = 1$$

$$\lim_{a \rightarrow 0} G(x) = \delta(x) \quad \begin{array}{l} \text{(CENTERED AROUND} \\ \text{ORIGIN)} \\ \downarrow \\ \text{DIRAC DELTA FUNCTION} \end{array}$$

CAN ALSO DERIVE $\delta(x)$ AS FOLLOWS:

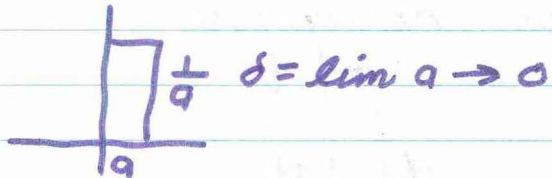

$$\delta(x - x_0) \Rightarrow \text{graph of a narrow peak at } x_0$$


IF SCALE IS CHANGED: x_0

$$\delta(bx) \text{ TO KEEP UNIT AREA}$$

$$\dots \dots \dots \text{ie) } \int f(t) \delta(t) dt = \int f(bt) \delta(bt) dt$$


$$\int_{t_1}^{t_2} \delta(t_0 - t_0) dt = 1; \quad t_1 < t_0 < t_2$$

= 0 IF NOT

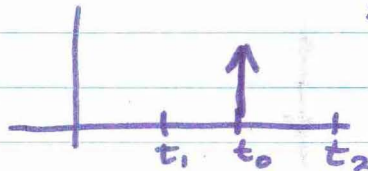

$$\int_{-\infty}^{\infty} f(t) \delta(t - t_0) dt = f(t_0)$$


(SIFTING PROP. OF DEL. FUNCTION)

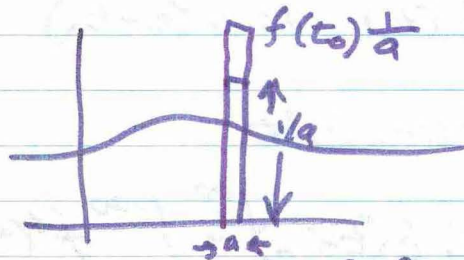

$$\int f(t) \frac{1}{a} \cdot a$$


RIG?

DOUBLET:

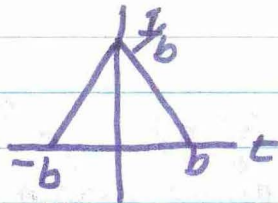

$\sim \delta(t)$ AS $b \rightarrow 0$

TAKING DERIVATIVE

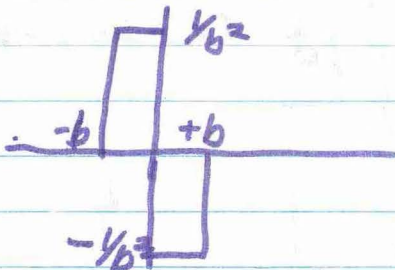


CALLED UNIT DOUBLET

$\sim \delta'(t)$ AS $b \rightarrow 0$

$$\int_{-\infty}^{\infty} \delta'(t) dt = 0$$

REPRESENTED:

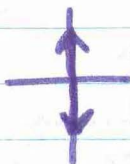

$$\int_{-\infty}^{\infty} f(t) \delta'(t-t_0) dt$$

INTEGRATING BY PARTS

$$du = f'(t) \quad v = \delta(t-t_0)$$

$$\Rightarrow \int_{-\infty}^{\infty} f(t) \delta'(t-t_0) dt$$

$$= \underbrace{f(t) \delta(t-t_0)}_{=0} \Big|_{-\infty}^{\infty} - \int_{-\infty}^{\infty} f'(t) \delta(t-t_0) dt$$

(CONT.)

$$\Rightarrow \int_{-\infty}^{\infty} f(t) \delta'(t-t_0) dt = -f'(t_0)$$


SINGULARITIES
RAMP \leftrightarrow UNIT STEP \leftrightarrow IMPULSE \leftrightarrow DOUBLET
 $r(t) \leftrightarrow \mu(t) \leftrightarrow \delta(t) \leftrightarrow \delta'(t)$

\Rightarrow TAKE DERIV.


\leftarrow TAKE INTEGRALS

9-30-70

3-22)
b)

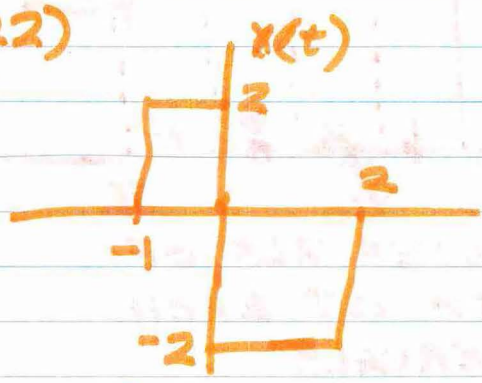

d)

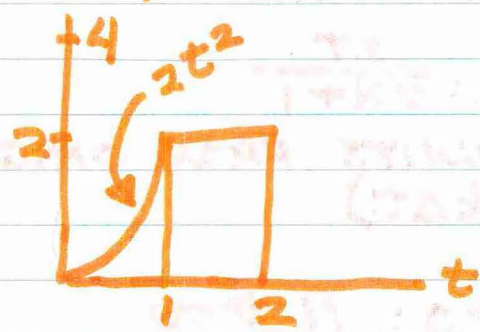

$$2t^2 \mu(t) = 2t^2 \mu(t-1) + 2t \mu(t-1) - 2 \mu(t-2)$$


(CONT.)

INTEGRAL TRANSFORMS:

$$\int f(t) e^{-st} dt = \mathcal{L}\{f(t)\}$$

$$y' = Ax + B$$
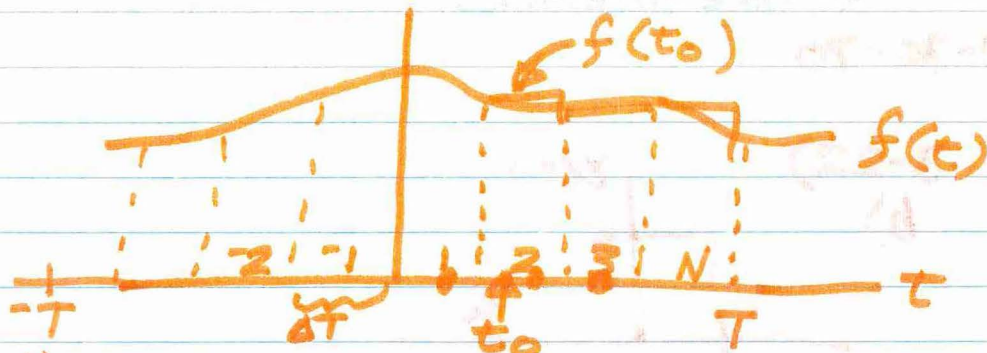
$$\int e^{-st} y' dt = \int Ax e^{-st} dt + \int B e^{-st} dt$$



N INTERVALS OF
WIDTH ΔT EACH

$2N+1$ INTERVALS

$$\Delta T = \frac{2T}{2N+1}$$

$$t_0 = k\Delta T \text{ UNITS FROM ORIGIN}$$

$$f(t_0) = f(k\Delta T)$$


AS $\Delta T \rightarrow 0$; $N \rightarrow \infty$

$$N\Delta T = 2T$$

$k\Delta T \Rightarrow \lambda$ A CONT. VARIABLE
(BEFORE IT WAS DISCRETE)


$$f(t) \approx \sum_{k=-N}^N f(k\Delta T) \mu\left(t - k\Delta T$$
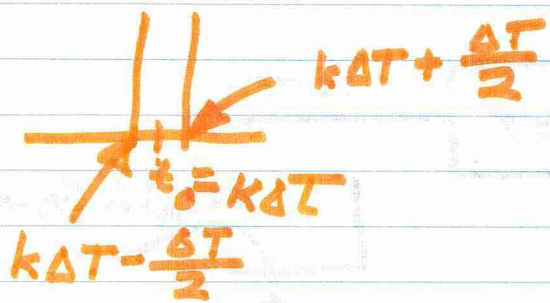
$$+ \frac{\Delta T}{2}\right) = \mu\left(t - k\Delta T - \frac{\Delta T}{2}\right)$$




$\lim_{\Delta T \rightarrow 0} = d\lambda$

$k\Delta T = \lambda$

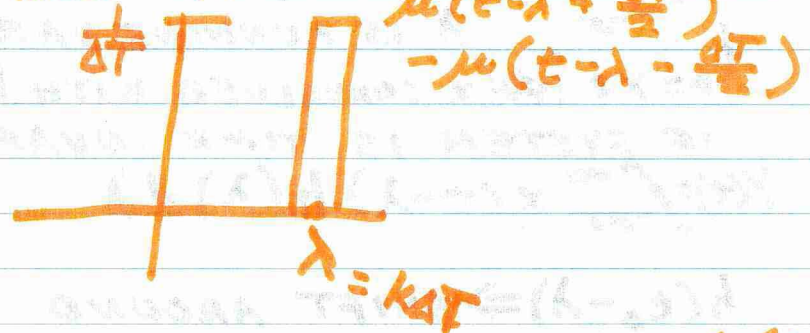


AS $\Delta T \rightarrow 0$; FUNC. APPROACHES $\delta(t - \lambda)$

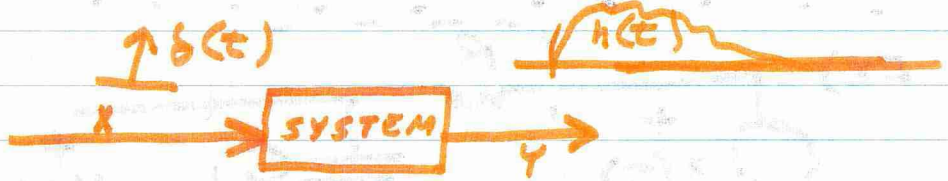
$f(t) = \int_{-\infty}^{\infty} f(\lambda) \delta(t - \lambda) d\lambda$



$h(t) =$ IMPULSE RESPONSE

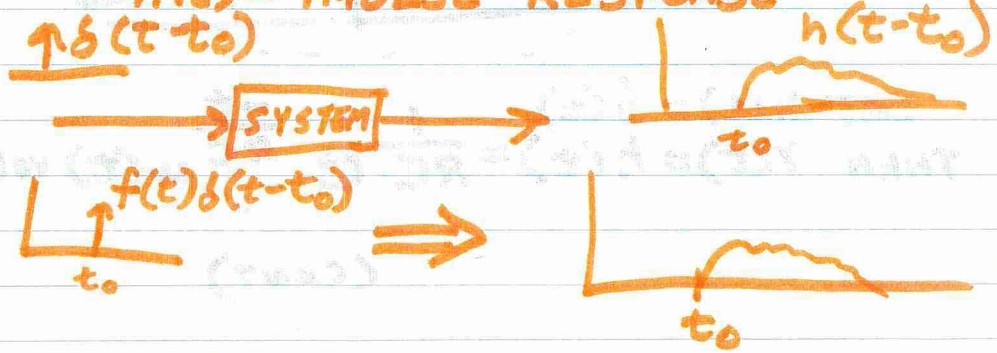

10-1-70

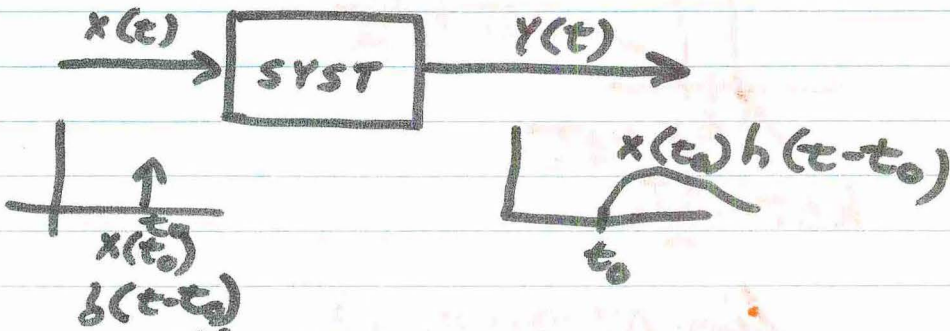

$$y(t) = \int_{-\infty}^{\infty} x(\lambda) h(t-\lambda) d\lambda$$

λ IS RUNNING VARIABLE

$\Rightarrow x * h \Rightarrow$ (X CONVOLVED WITH h)

IF SYSTEM IS TIME INVARIANT


$$y(t) = \int_{-\infty}^{\infty} x(t-\lambda) h(\lambda) d\lambda$$

$h(t_0-\lambda) \Rightarrow$ SHIFT AROUND
Y AXIS (ROTATED)

$\therefore 1$


$$\delta(\lambda-t) = \delta(t-\lambda)$$

EX)

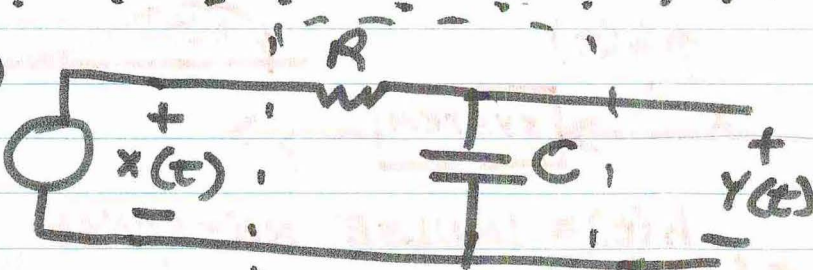

LET $x(t) = \delta(t)$
THEN $y(t) = h(t) = \frac{1}{RC} e^{-\frac{t}{RC}} u(t)$ VOLTS

(CONT)

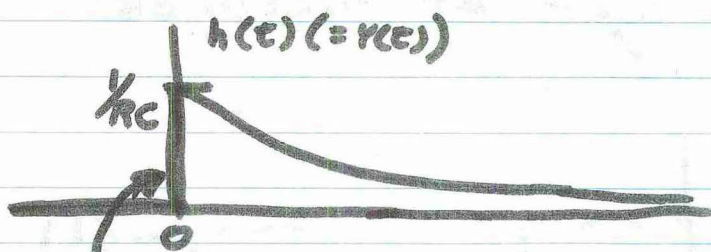

CAN JUMP, FOR δ HAS INFINITE EN.

$$i(0+) = \frac{\delta(t)}{R}$$

$$V_c = \frac{1}{C} \int i dt$$


$$= \frac{1}{C} \int \frac{\delta(t)}{R} dt$$

$$= \frac{1}{RC} \text{ VOLT}$$


$$\tau = RC$$

$$\therefore y(t) = h(t) = \frac{1}{RC} e^{-\frac{t}{RC}}$$

MAY NOW BE REPRESENTED:

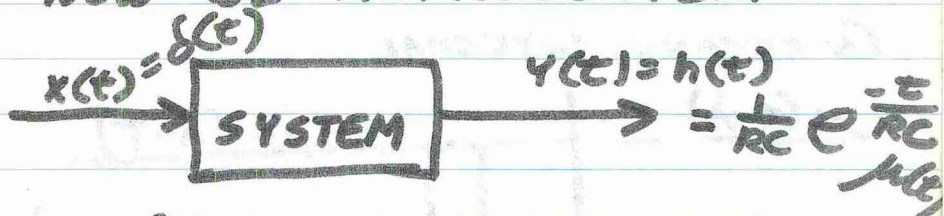

$$y(t) = \int_{-\infty}^{\infty} x(\lambda) h(t-\lambda) d\lambda$$

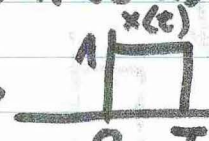LET $x(t) \Rightarrow$  $x(t) = A \mu(t) - A \mu(t-T)$


$$\therefore y(t) = \int_{-\infty}^{\infty} [A \mu(\lambda) - A \mu(\lambda-T)] \cdot \frac{1}{RC} e^{-\frac{(t-\lambda)}{RC}} \mu(t-\lambda) d\lambda$$

$$= \int_{-\infty}^{\infty} A \mu(\lambda) e^{-\frac{(t-\lambda)}{RC}} \mu(t-\lambda) d\lambda$$

$$- \int_{-\infty}^{\infty} \frac{A}{RC} \mu(\lambda-T) e^{-\frac{(t-\lambda)}{RC}} \mu(t-\lambda) d\lambda$$

GOOD TO LOOK AT PICTURES:


① FIRST \int

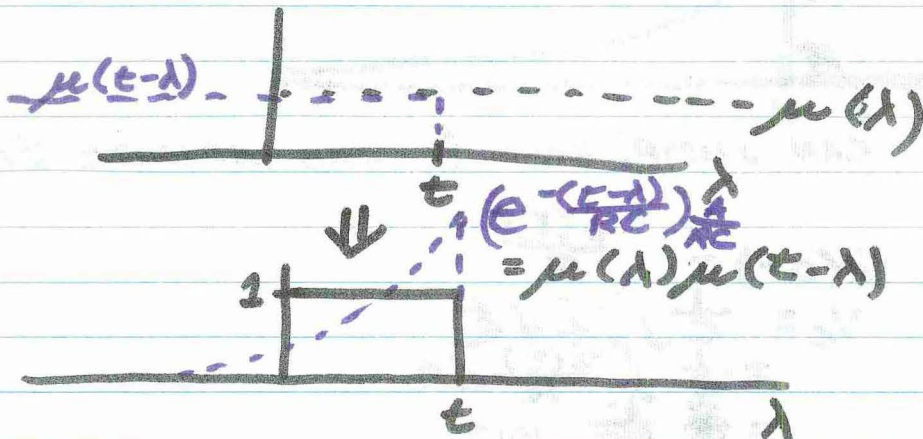

\Rightarrow FIRST INTEGRAL BECOMES

$$\int_0^t \frac{A}{RC} e^{-\frac{(t-\lambda)}{RC}} d\lambda$$

② SECOND INTEGRAL

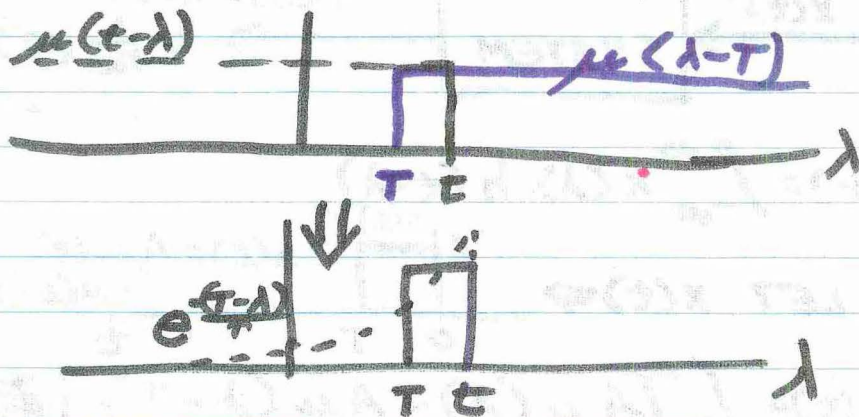


\Rightarrow SECOND INTEGRAL BECOMES

$$-\int_T^t \frac{A}{RC} e^{-\frac{(t-\lambda)}{RC}} d\lambda$$





WHOLE SHABANG:
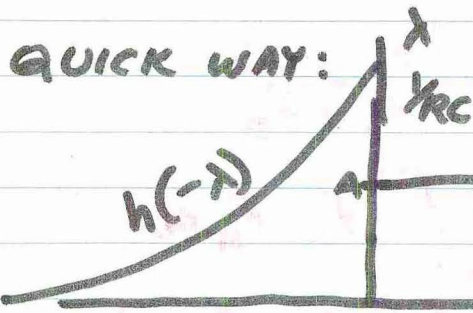
$$Y(t) = \underbrace{\int_0^t \frac{A}{RC} e^{-\frac{(t-\lambda)}{RC}} d\lambda}_{t > 0} - \underbrace{\int_T^t \frac{A}{RC} e^{-\frac{(t-\lambda)}{RC}} d\lambda}_{\text{FOR } t > T}$$



SHIFT THIS WAY AND THAT (\leftarrow, \rightarrow)

10-2-70 Pg 80

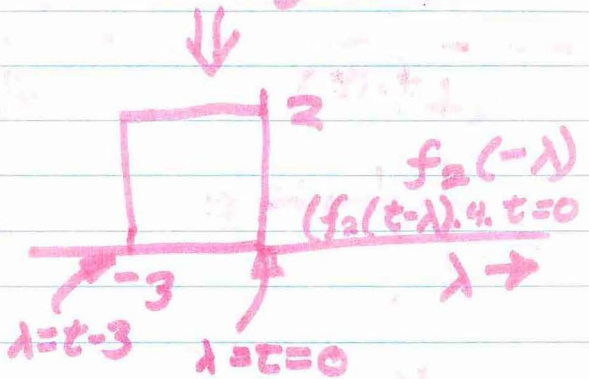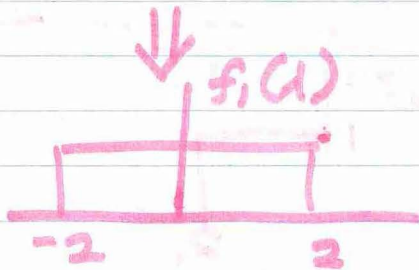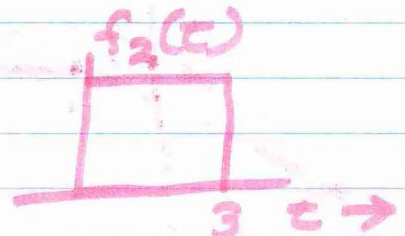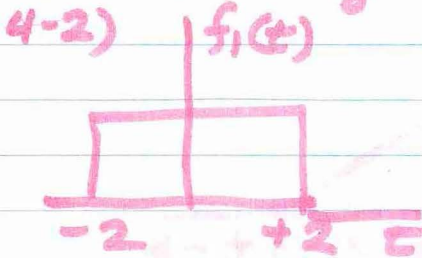

MUST FIRST MULTIPLY
2 FUNCTIONS TOGETHER

(CONT.)

FOR $t \leq -2$, $f_1 * f_2 = 0$






FOR $-2 \leq t \leq 1$, $f_1 * f_2$

$$= \int_{-2}^t f_1 \cdot f_2 d\lambda$$

FOR $1 \leq t \leq 2$; $\int_{t-3}^t f_1 \cdot f_2 d\lambda$

FOR $2 \leq t \leq 5$; $\int_{t-3}^2 f_1 \cdot f_2 d\lambda$

FOR $t \geq 5$; $f_1 * f_2 = 0$

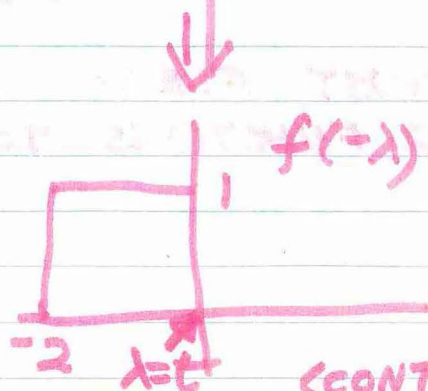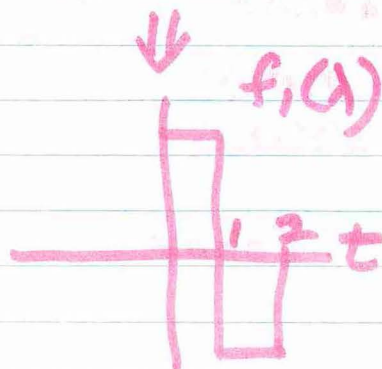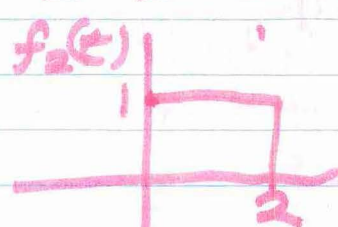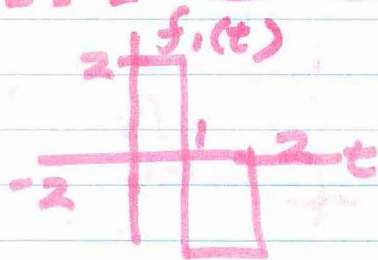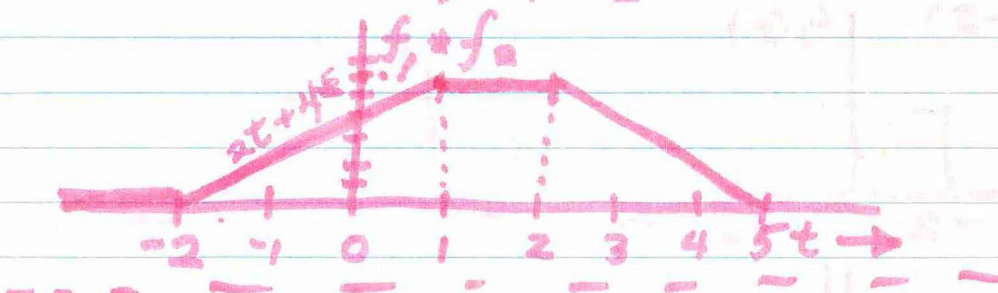

(CONT)

$-\infty < t < 0 \Rightarrow f_1 * f_2 = 0$

$0 < t < 1 \Rightarrow \int_0^t f_1 \cdot f_2 d\lambda$



$1 < t < 2 \Rightarrow \int_0^1 2 d\lambda + \int_1^t -2 d\lambda$

$2 < t < 3 \Rightarrow \int_{t-2}^1 2 d\lambda + \int_1^2 -2 d\lambda$


$3 < t < 4 \Rightarrow \int_{t-2}^2 (-2) d\lambda$

$t < 4, f_1 * f_2 = 0$

10-6-70

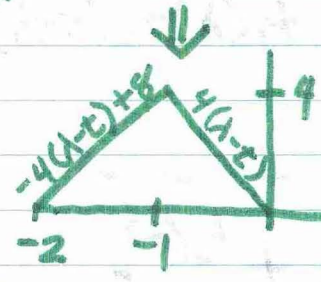
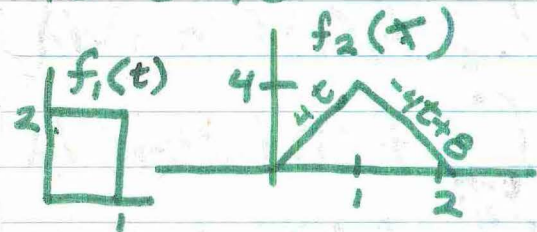


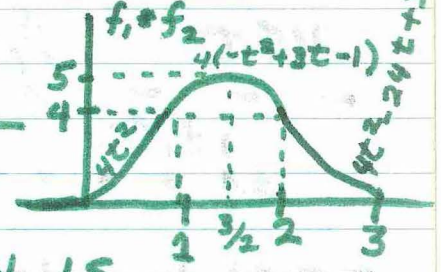REPLACE t BY (lambda - t)
(WORKED IN CLASS)



TIME OF CONVOLUTION IS
SUM OF BASES OF TWO
FUNCTIONS
(FOR ABOVE FUNC., TIME
FOR CONV = 3)

10-7-70

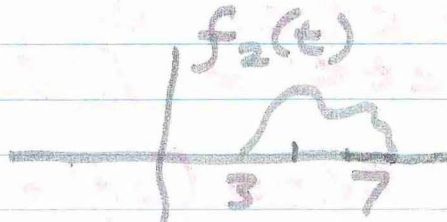
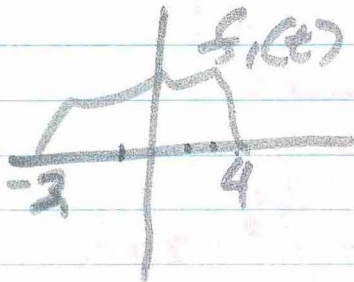


$t \leq 1 \quad f_1 * f_2 = 0$
 $1 \leq t \leq 5 \quad f_1 * f_2 = \int_{-2}^{t-3} f_1(\lambda) f_2(t-\lambda) d\lambda$

$5 \leq t \leq 7 \quad = \int_{t-7}^{t-3} f_1(\lambda) f_2(t-\lambda) d\lambda$



$7 \leq t \leq 11 \quad = \int_{t-7}^4 f_1(\lambda) f_2(t-\lambda) d\lambda$

$11 \leq t \quad f_1 * f_2 = 0$

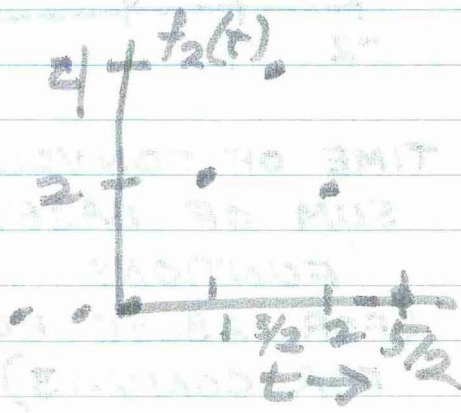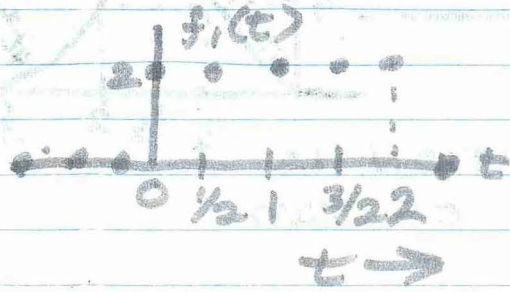

NUMERICAL CONVO.

$t=0$

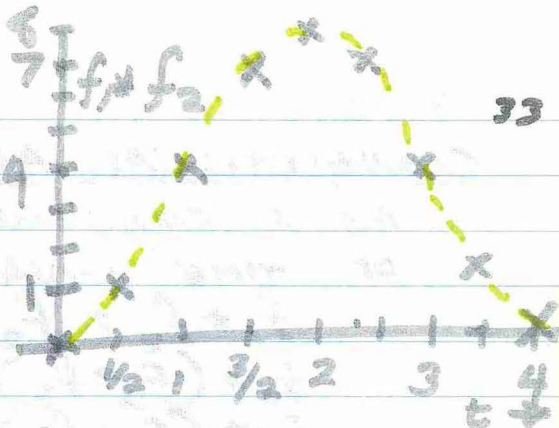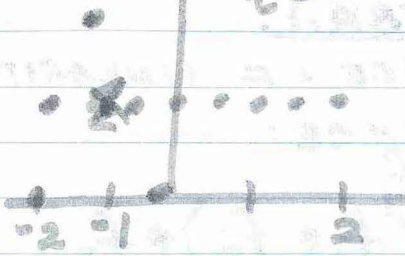


33

$t = \frac{1}{2} \Rightarrow \int = (\frac{1}{2})(\frac{1}{2})(4+0)$

USE:

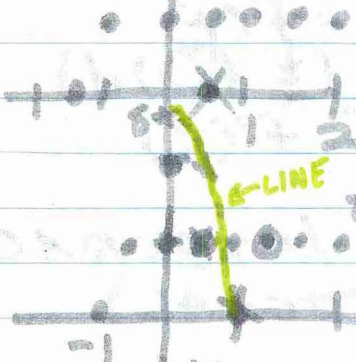
$\int = \frac{A \Delta t}{2} (x_0 + 2x_1 + 2x_2 + \dots + x_n)$



← LINE

$t=1 \Rightarrow \frac{1}{2} \frac{1}{2} (8 + 2(4) + 0) = 4$

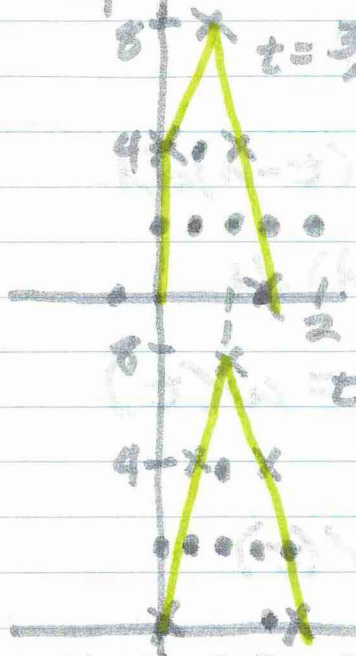$t = \frac{3}{2} \Rightarrow (\frac{1}{2})(\frac{1}{2})(4 + 2(8) + 2(4) + 0) = 7$



$t = 2 \Rightarrow \frac{1}{2} \frac{1}{2} (0 + 2(4) + 2(8) + 2(4) + 0) = 8$

GOING FURTHER
WILL GIVE SAME
POINT. i.e.) FUNCTION
IS SYMETRIC

10-9-70

34

CONVOLUTIONAL ALGEBRA:

AS A CONSEQUENCE OF LINEARITY
OF TIME INVARIANCE:

$$f_1 * f_2 = f_2 * f_1$$

$$f_1 * (f_2 * f_3) = (f_1 * f_2) * f_3$$

$$f_1 * (f_2 + f_3) = f_1 * f_2 + f_1 * f_3$$

OTHER PROPERTIES

$$f(t) * \delta(t) = f(t)$$

$$f(t) * \mu(t) = \int_{-\infty}^t f(\lambda) d\lambda$$

$$f(t) * \delta'(t) = f'(t)$$

THE SUPERPOSITION INTEGRAL
(DUMAMEL'S INTEGRAL)

$$w(t) = \mu(t) * h(t)$$

$$= \int_{-\infty}^{\infty} \mu(\lambda) h(t-\lambda) d\lambda$$

$$= \int_0^t h(t-\lambda) d\lambda$$

$$= \int_0^t h(\lambda) d\lambda = w(t)$$

$$\Leftrightarrow \Downarrow$$

$$h(t) = w'(t)$$


$w(t)$ = UNIT STEP RESPONSE

$$x'(t) * w(t) = x(t) * w'(t) = y(t)$$


FOR CAUSAL $x(t) = x_c(t) = 0$ FOR $t < 0$
 $y(t) = x_c(t) * w'(t) = x_c'(t) * w(t)$

$$= \int_{0^-}^{\infty} x_c'(\lambda) w(t-\lambda) d\lambda$$
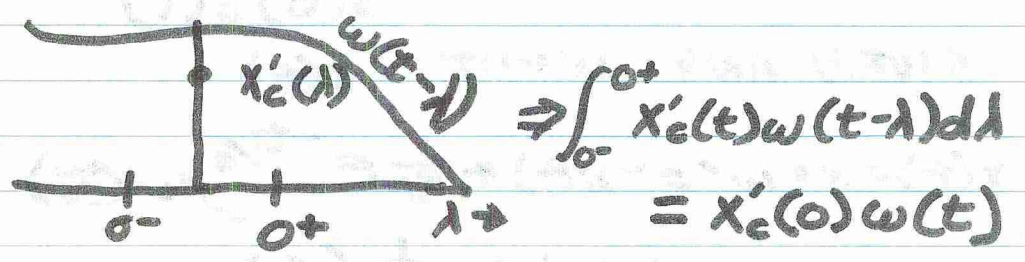
$$= \int_{0^-}^{0^+} x_c'(t) w(t-\lambda) d\lambda + \int_{0^+}^{\infty} x_c'(\lambda) w(t-\lambda) d\lambda$$


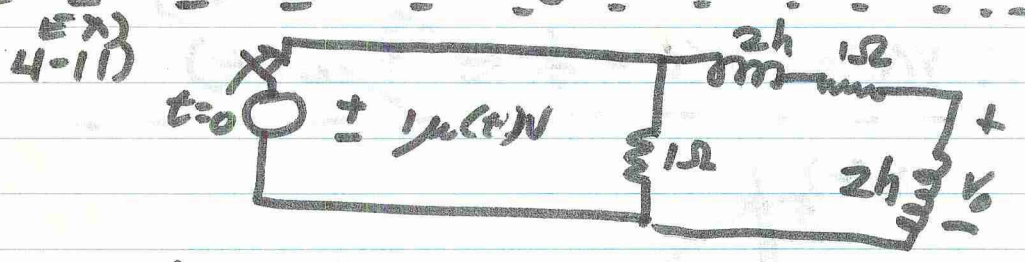
$$\therefore y(t) = x_c'(0) w(t) + \int_{0^+}^{\infty} x_c'(\lambda) w(t-\lambda) d\lambda$$



$$x(t) = 1/\mu(t) ; y(t) = V_o$$

$$V_o(t) = V_o(\infty) + V_{on}(t)$$

$$= 0 + V_{on}(t)$$

$$V_{on}(t) = A e^{-t/\tau} \mu(t)$$

(CONT.)

(CONT)

$$\tau = \frac{L}{R} = \frac{4}{1}$$
$$A = V_0(0) = \frac{dV}{dt} = \frac{1}{2}$$

$$\therefore V_n(t) = \frac{1}{2} e^{-t/4} \mu(t) = w(t)$$

$$h(t) = w'(t) = -\frac{1}{8} e^{-t/4} \mu(t) + \frac{1}{2} e^{-t/4} \delta(t)$$

$$\Rightarrow -\frac{1}{8} e^{-t/4} \mu(t) + \frac{1}{2} \delta(t)$$


||
f(0) \delta(t)

GIVEN ANY INPUT $x(t)$

$$y(t) = x * w' = -x(t) * \frac{1}{8} e^{-t/4} \mu(t) + x(t) * \frac{1}{2} \delta(t)$$





$$\Downarrow \frac{1}{2} x(t)$$
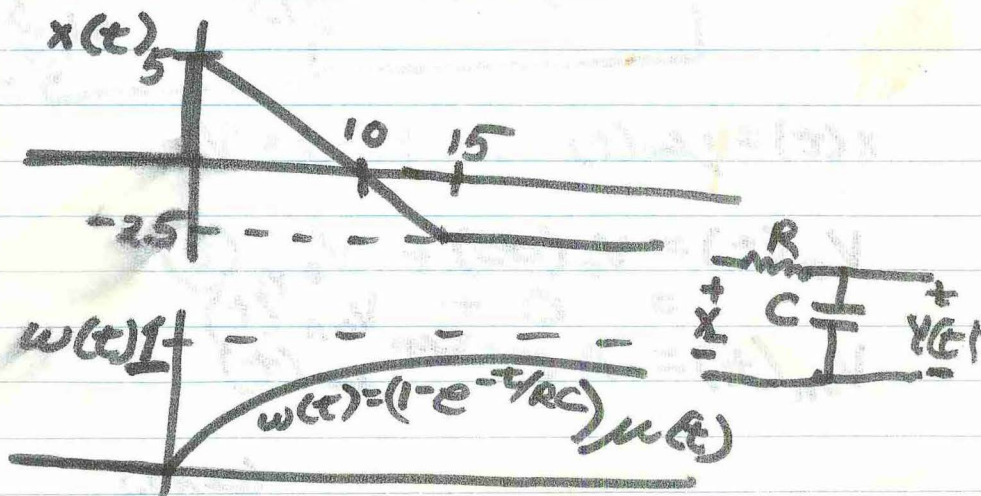
$$\therefore y(t) = -x(t) * \frac{1}{8} e^{-t/4} \mu(t)$$




10-10-70

37

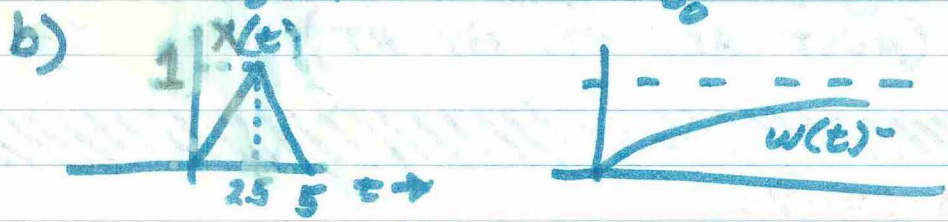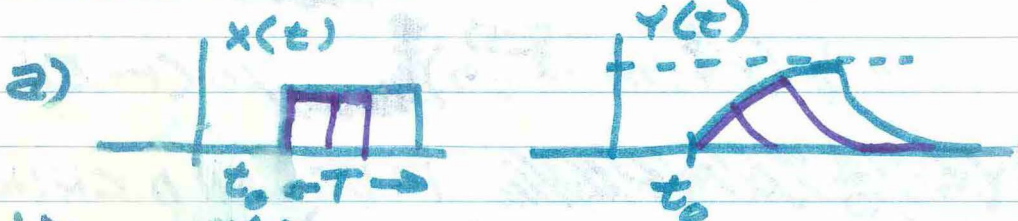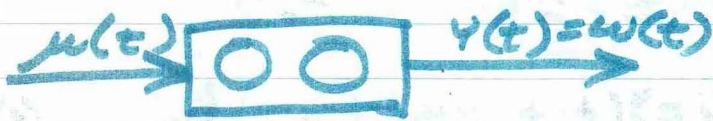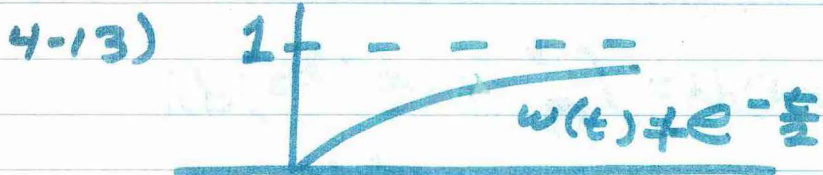

$y(t) = x'(t)w(t)$

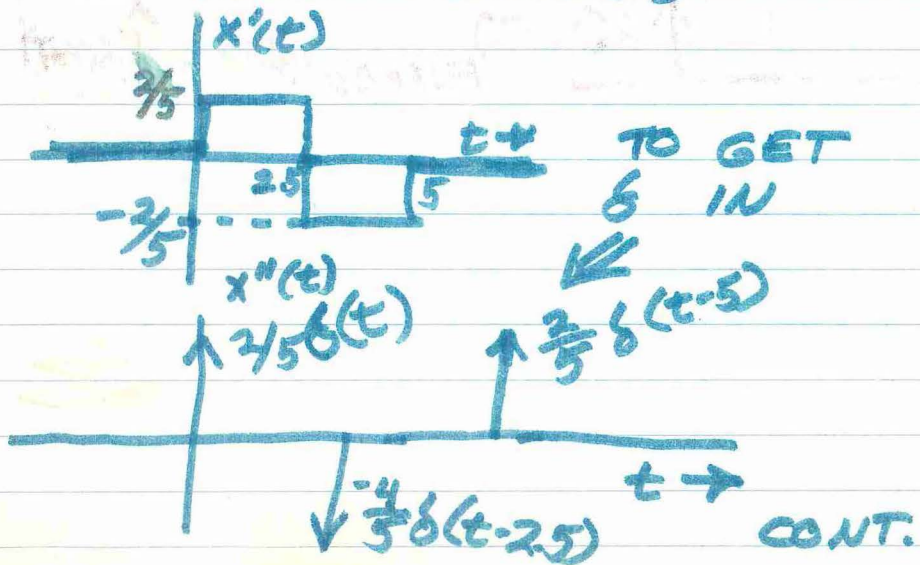

(CONT.)

$$Y = x'' + \int_{-\infty}^{\infty} w(\lambda) d\lambda$$

$$\int_{-\infty}^{\infty} w(\lambda) d\lambda = \int_{-\infty}^{\infty} (1 - e^{-\lambda/2}) d\lambda = t + 2e^{-t/2} - .2$$



$$Y = x'' + \int w(\lambda) d\lambda = \frac{3}{5}(t + .2e^{-\frac{t}{5}} - .2) \mu(t) - \frac{4}{5}(t + .2e^{-\frac{t-2.5}{5}} - .2) \mu(t-2.5) + \frac{2}{5}(t + .2e^{-\frac{t-5}{5}} - .2) \mu(t-5)$$

~~PLUG AND CHUG~~ PLUG AND CHUG (MUST ADD PT. BY PT)

~~10-13-70~~
10-13-70



FOURIER TRANSFORMS AND SUCH

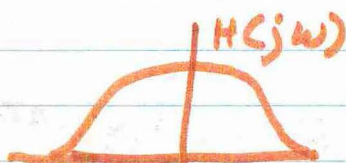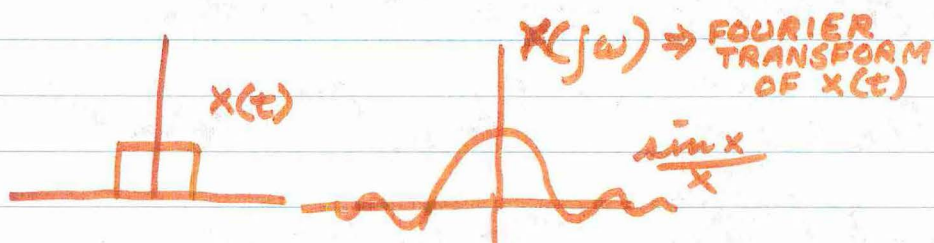


$$f(t) = \sum_{n=-\infty}^{\infty} c_n e^{jn\omega_0 t}$$

$$\text{AND } c_n = \frac{1}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} f(t) e^{-jn\omega_0 t} dt$$

$$\text{AND } \omega_0 = \frac{2\pi}{T}$$
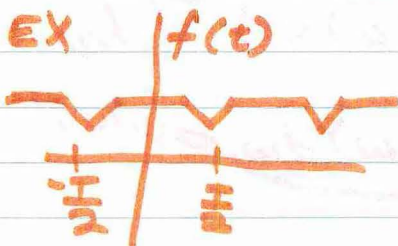
$$\Rightarrow f(t) = \sum_{n=-\infty}^{\infty} e^{jn\omega_0 t} \frac{1}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} f(t) e^{-jn\omega_0 t} dt$$



$$\text{AS } T \rightarrow \infty; \omega_0 = \frac{2\pi}{T} \rightarrow d\omega$$

$$n\omega_0 \rightarrow \omega \text{ (ANOTHER CONT. VARIABLE)}$$

(CONT.)

$$f(t) \rightarrow F(j\omega) \quad \frac{1}{T} = \frac{\omega_0}{2\pi} \rightarrow d\omega/2\pi$$


$$f(t) = \int_{-\infty}^{\infty} e^{j\omega t} \left[\frac{1}{2\pi} d\omega \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt \right]$$

$$F(\omega) = \frac{1}{2\pi} \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt \quad \left[e^{j\omega t} d\omega \right]$$

= $\mathcal{F}\{f(t)\}$ = FOURIER TRANSFORM OF $f(t)$

$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(j\omega) e^{j\omega t} d\omega$$

(INVERSE FOURIER TRANSFORM)

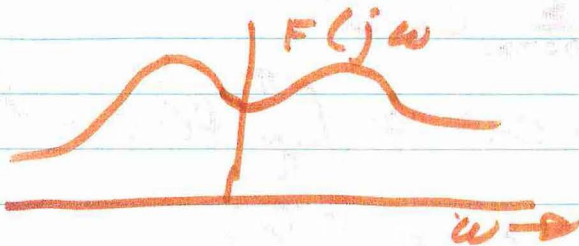


10-14-70

$$f(t) = \sum_{n=-\infty}^{\infty} C_n e^{jn\omega_0 t}$$

$$= \frac{1}{2\pi} \int_{-\infty}^{\infty} F(j\omega) e^{j\omega t} d\omega$$

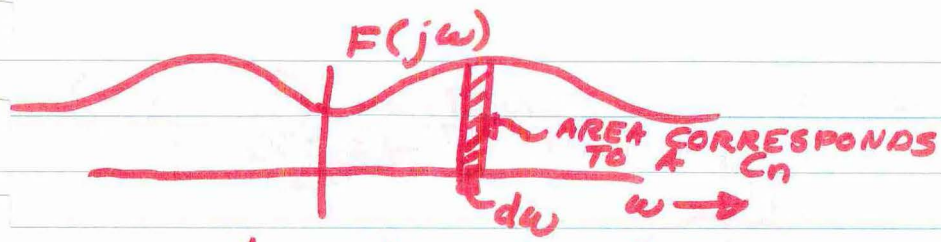
$$= \int_{-\infty}^{\infty} \underbrace{\frac{1}{2\pi} F(j\omega) d\omega}_{C_n} e^{j\omega t}$$



$$\frac{1}{2\pi} \int F(j\omega) d\omega \Rightarrow C_n$$

$$F(j\omega) \Rightarrow \frac{2\pi C_n}{d\omega}$$

AS OPPOSED TO

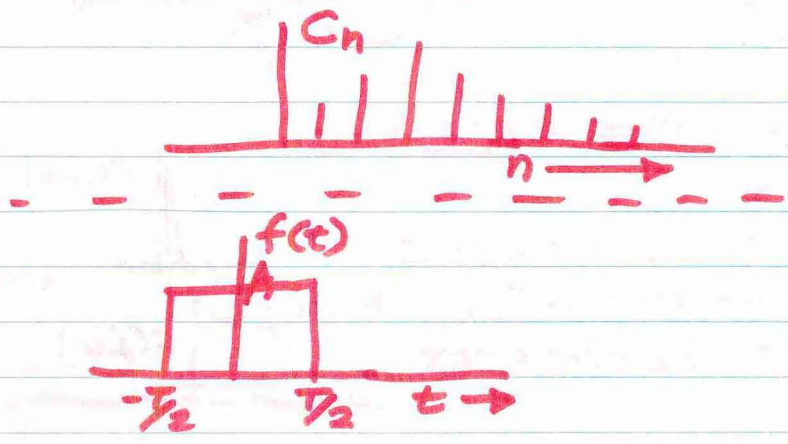

$$f(j\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$$

$$f(j\omega) = \int_{-T/2}^{T/2} A e^{-j\omega t} dt = \frac{-A}{j\omega} e^{-j\omega t} \Big|_{-T/2}^{T/2}$$

$$= \frac{TA}{j\omega} \left[e^{-j\frac{\omega T}{2}} + e^{j\frac{\omega T}{2}} \right]$$


$$f(j\omega) = \frac{2A}{\omega} \sin\left(\frac{\omega T}{2}\right) \quad \left(\frac{e^{j\theta} + e^{-j\theta}}{2} = \cos\theta \right)$$

$$= \frac{TA \sin\left(\frac{\omega T}{2}\right)}{\left(\frac{\omega T}{2}\right)}$$

(CONT.)

A PURE REAL FUNCTION (NO j 's)
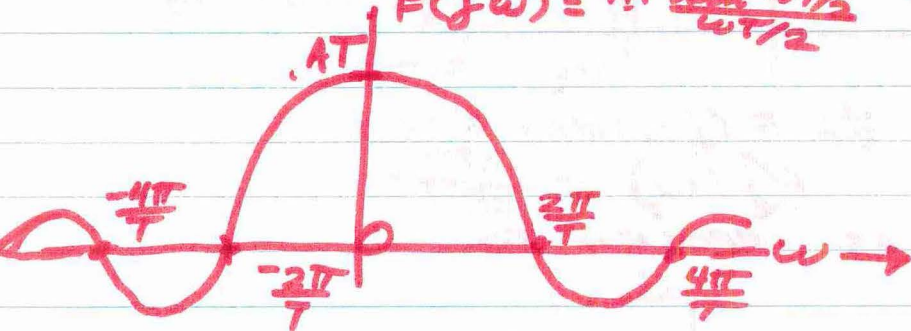
$$F(j\omega) = AT \frac{\sin \frac{\omega T}{2}}{\frac{\omega T}{2}}$$




$$\frac{\omega T}{2} = \pi \Rightarrow F(j\omega) = 0$$



AS T INCREASES

AS $T \rightarrow \infty$; $F(j\omega) \rightarrow \delta(j\omega)$

AS T DECREASES

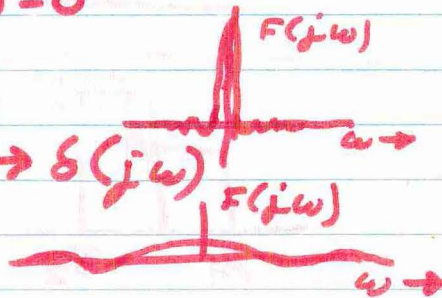

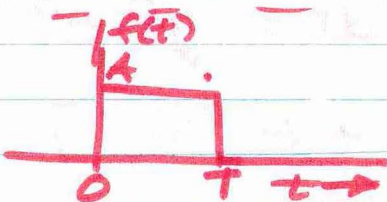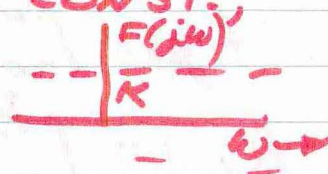AS $T \rightarrow 0$, AT KEPT A CONST.,
TRANSFORM OF $\delta(t) \Rightarrow$




$$\Rightarrow F(j\omega) = e^{-j\frac{\omega T}{2}}$$


$$\bullet AT \frac{\sin \frac{\omega T}{2}}{\frac{\omega T}{2}}$$

$e^{-j\frac{\omega T}{2}}$ PHASE
JUST ADDS ANGLE
INFORMATION ($\angle \frac{\omega T}{2}$)

10-15-70

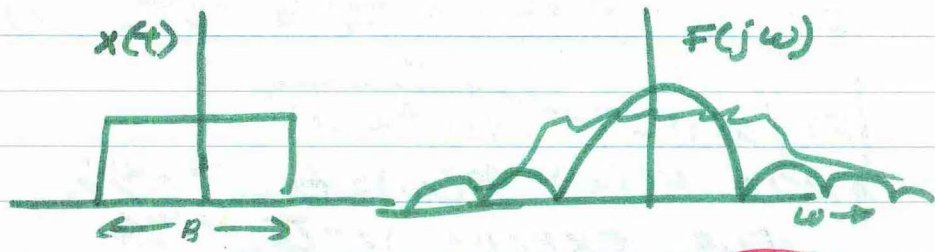

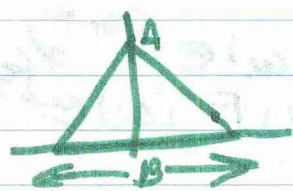TIME WIDTH x FREQ WIDTH = CONST
 $BW = \frac{\int f(t) dt}{f(0)} = \frac{\text{AREA}}{\text{HT. AT ORIGIN}}$



$$BW = \frac{\frac{1}{2}BA}{A} = \frac{1}{2}B$$

$$\therefore \frac{\int_{-\infty}^{\infty} f(t) dt}{f(0)} = \frac{\int_{-\infty}^{\infty} |F(jw)|}{f(0)} = ? = 2\pi$$


$$f(t) = \frac{1}{2\pi} \int F(jw) e^{jw t} dw$$

$$f(0) = \frac{1}{2\pi} \int F(j\pi) dW$$

$$= \int F(jw) dw = 2\pi f(0)$$

$$\Rightarrow ? = 2\pi$$

SOME TRANSFORMS

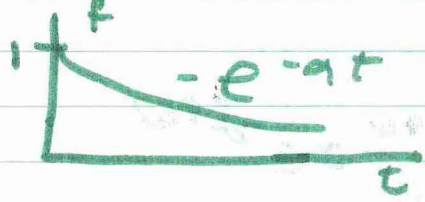

$$F(jw) = \int_{-\infty}^{\infty} e^{-at} f(t) e^{-jw t} dt$$

$$= \int_0^{\infty} e^{-(a+jw)t} dt$$

$$= \frac{1}{a+jw} \quad (\text{CONT.})$$

$$F(j\omega) = \frac{\alpha - j\omega}{\alpha^2 + \omega^2} \frac{\alpha}{\alpha^2 + \omega^2} = -\frac{j\omega}{\alpha^2 + \omega^2}$$

$$|F(j\omega)| = \frac{1}{\sqrt{\alpha^2 + \omega^2}}$$

ANGLE $F(j\omega) = \theta(\omega) = \tan^{-1} \frac{-\omega}{\alpha}$

FOR EXPD: $\angle = -\tan^{-1} \frac{\omega}{\alpha}$

$$F(j\omega) = \frac{1}{\alpha + j\omega}$$

2) $\mathcal{F}\left\{\frac{df(t)}{dt}\right\} = ?$


$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(j\omega) e^{j\omega t} d\omega$$

$$f'(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} j\omega F(j\omega) e^{j\omega t} d\omega$$

3) $\mathcal{F}\{\delta(t)\} = 1$

4) $\mathcal{F}\{\delta(t-t_0)\} = e^{j\omega t_0}$

EX)

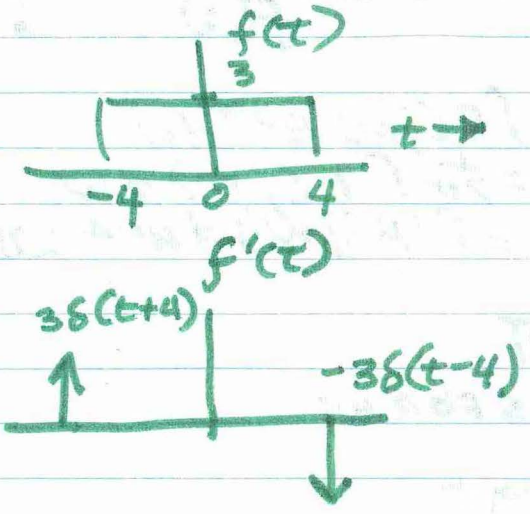

$$\mathcal{F}\{f'(t)\} = 3e^{j4\omega} - 3e^{-j4\omega}$$

$$\mathcal{F}\{f(t)\} = \frac{\mathcal{F}\{f'(t)\}}{j\omega} = F(j\omega)$$

$$= \frac{6}{j\omega} \sin 4\omega = 24 \frac{\sin 4\omega}{4\omega}$$

10-16-70

$$f(t) = f_e(t) + f_o(t)$$

(EVEN + ODD)

$$f_e = \frac{f(t) + f(-t)}{2}$$

$$f_o = \frac{f(t) - f(-t)}{2}$$

EVEN FUNC $\Rightarrow f(t) = f(-t)$

ODD FUNC $\Rightarrow f(t) = -f(-t)$

EX) $e^{jt} = \cos t + j \sin t$

$$f_e = \frac{e^{jt} + e^{-jt}}{2}$$

$$f_o = \frac{e^{jt} - e^{-jt}}{2j} = \sin t$$


$$F(j\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$$

$$= \int_{-\infty}^{\infty} [f_e(t) + f_o(t)] \cdot [\cos \omega t - j \sin \omega t] dt$$

$$= \int_{-\infty}^{\infty} [f_e \cos \omega t - j f_o(t) \sin \omega t] dt$$


EVEN \cdot ODD = ODD

EX)

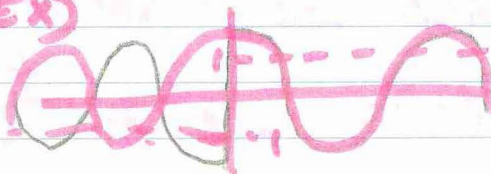

$$\int_{-\infty}^{\infty} \text{ODD} = 0$$

ODD · ODD = EVEN

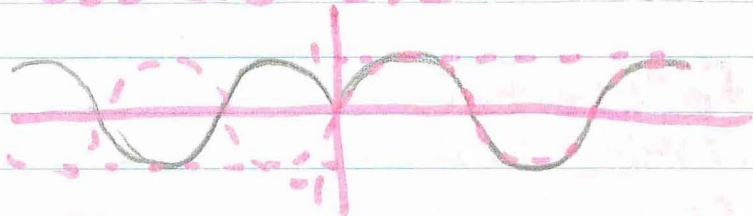

RETURNING TO PROB:

$$F(j\omega) = \int_{-\infty}^{\infty} [f_e(t) \cos \omega t + j f_o(t) \sin \omega t] dt$$

$$F(j\omega) = F_{\text{REAL}}(j\omega) + F_{\text{IMAG}}(j\omega)$$

$$F_{\text{REAL}} = \int_{-\infty}^{\infty} f_e(t) \cos \omega t dt$$

F_{REAL} IS EVEN

$$F_{\text{IMAG}} = - \int_{-\infty}^{\infty} f_o(t) \sin \omega t dt$$

F_{IMAG} IS ODD

1) $|F(j\omega)|$ IS EVEN

$$(|F(j\omega)| = \sqrt{F_{\text{REAL}}^2 + F_{\text{IMAG}}^2})$$

2) ANGLE $F(j\omega)$ IS ODD

$$(\text{ANGLE } F(j\omega) = \text{atan} \frac{F_{\text{IMAG}}}{F_{\text{REAL}}})$$


TALKING OF CAUSAL SYSTEM

* SIGNALS $x(t) = X(\omega) = 0$ FOR $t < 0$


$$f_e(t) = f_o(t) = \frac{f(t)}{2}$$

FOR PHYSICALLY REALIZABLE SYSTEMS (CAUSAL) WE FIND

$|F(j\omega)| = A(\omega)$ MUST NOT GO TO ZERO FOR ANY FINITE BAND WIDTH

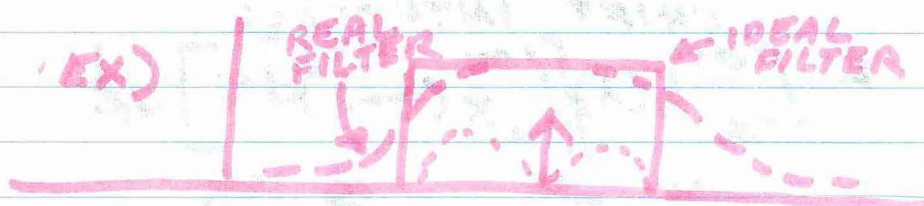

$$e^{j\theta} = 1 \angle \theta$$

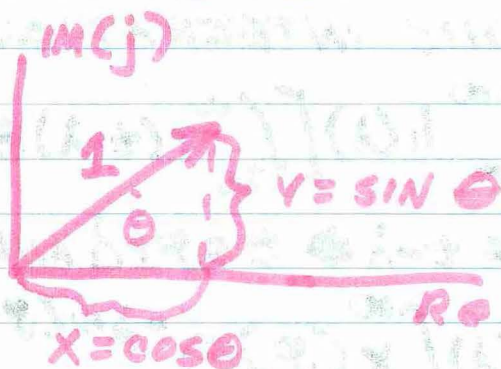

10-20-70

$$Y(t) = x(t) * h(t) = \int_{-\infty}^{\infty} h(\lambda) x(t-\lambda) d\lambda$$

$$\begin{aligned} \mathcal{F}\{Y(t)\} &= Y(j\omega) = \int_{-\infty}^{\infty} Y(t) e^{-j\omega t} dt \\ &= \int_{-\infty}^{\infty} \left[\int_{-\infty}^{\infty} h(\lambda) x(t-\lambda) d\lambda \right] e^{-j\omega t} dt \end{aligned}$$

SHIFT INTEGRALS

$$= \int_{-\infty}^{\infty} h(\lambda) \left[\int_{-\infty}^{\infty} x(t-\lambda) e^{-j\omega t} dt \right] d\lambda$$

$$\sum_{\lambda=-\infty}^{\infty} \sum_{t=-\infty}^{\infty} \Rightarrow \sum_{t=-\infty}^{\infty} \sum_{\lambda=-\infty}^{\infty}$$

⇒ FOR THIS INTEGRATION

$$\mathcal{F}\{Y(t)\} = \int_{-\infty}^{\infty} h(\lambda) \left[\int_{-\infty}^{\infty} x(t-\lambda) e^{-j\omega t} dt \right] d\lambda$$

DEFINE $\rho = t - \lambda \Rightarrow t = \rho + \lambda$ AND $d\rho = dt$

$$\therefore Y(j\omega) = \int_{-\infty}^{\infty} h(\lambda) \left[\int_{-\infty}^{\infty} x(\rho) e^{-j\omega(\rho+\lambda)} d\rho \right] d\lambda$$

$$= \int_{-\infty}^{\infty} h(\lambda) e^{-j\omega\lambda} \left[\int_{-\infty}^{\infty} x(\rho) e^{-j\omega\rho} d\rho \right] d\lambda$$

$X(j\omega) = f(\omega)$


$$= X(j\omega) \int_{-\infty}^{\infty} h(\lambda) e^{-j\omega\lambda} d\lambda$$

(CONT.)

$$= H(j\omega) X(j\omega)$$

$$\therefore Y(t) = x(t)h(t) \Rightarrow Y(j\omega) = X(j\omega) H(j\omega)$$

EX)
①

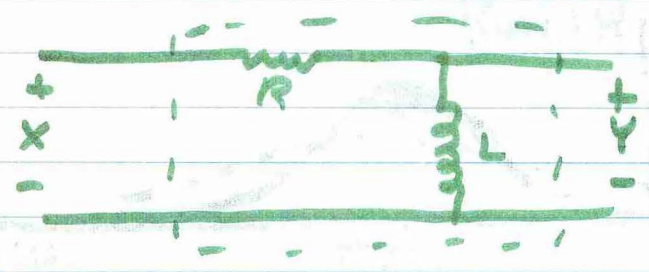

$$H(j\omega) = \frac{Y(j\omega)}{X(j\omega)} \Rightarrow \text{TRANSFER FUNCTION}$$

USING IMPEDENCES:


$$R \rightarrow R ; L \rightarrow j\omega L$$



$$Y(j\omega) = \frac{X(j\omega) j\omega L}{[R + j\omega L]}$$

$$\Rightarrow H(j\omega) = \frac{j\omega L}{R + j\omega L} \leftarrow \text{FOURIER TRANSFORM OF } h(t)$$


$$|H(j\omega)| = \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}}$$

$|H(j\omega)|$ A HI PASS FILTER

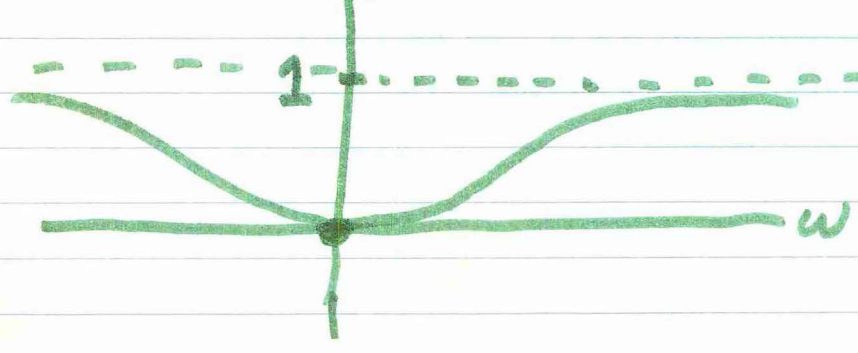

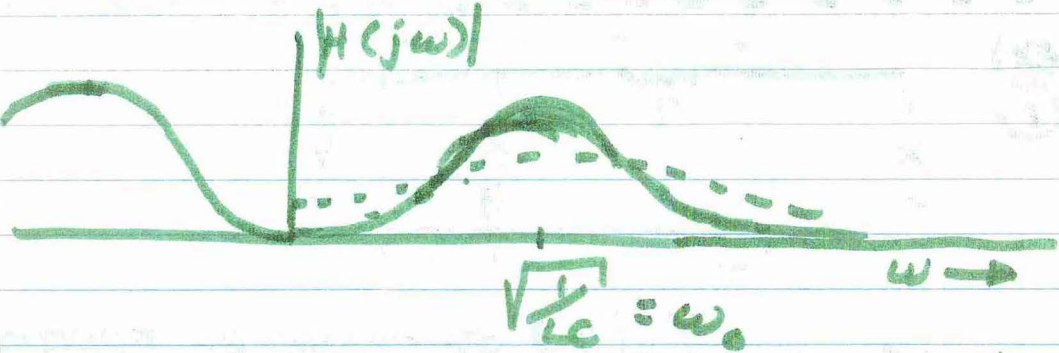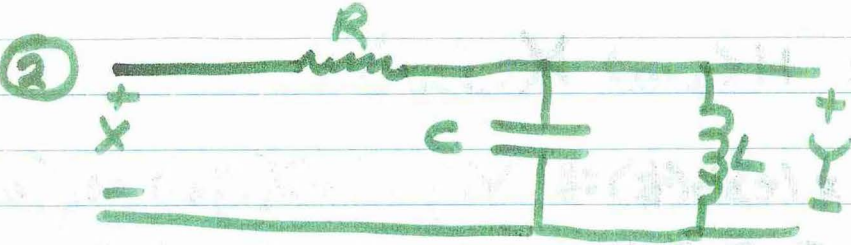

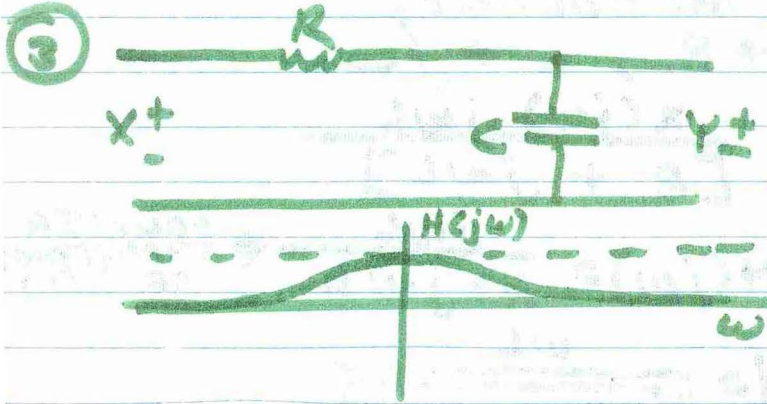R DETERMINES WIDTH OF CURVE
 $(Q = \omega_0 R C = \omega_0 R C)$



10-29-30

! BODE PLOTS!

$$\text{ENERGY SPECTRUM: } E = \int_{-\infty}^{\infty} p(t) dt$$

$$= \int_{-\infty}^{\infty} f^2(t) dt$$

$$E = \int_{-\infty}^{\infty} f(t) \left[\frac{1}{2\pi} \int_{-\infty}^{\infty} F(j\omega) e^{j\omega t} d\omega \right] dt$$

CHANGING ORDER OF LIMITS

$$E = \int_{-\infty}^{\infty} \frac{1}{2\pi} F(j\omega) \left[\int_{-\infty}^{\infty} f(t) e^{j\omega t} dt \right] d\omega$$


COMPLEX CONJUGATE
OF $F(j\omega) = F^*(j\omega)$ AND $f(t)$ MUST BE REAL

$$\therefore E = \int_{-\infty}^{\infty} \frac{1}{2\pi} F(j\omega) F^*(j\omega) d\omega$$

$$= \frac{1}{2\pi} \int_{-\infty}^{\infty} |F(j\omega)|^2 d\omega$$

$$\Rightarrow E = \int_{-\infty}^{\infty} f^2(t) dt = \frac{1}{2\pi} \int_{-\infty}^{\infty} |F(j\omega)|^2 d\omega$$

PARSEVAL'S THEOREM

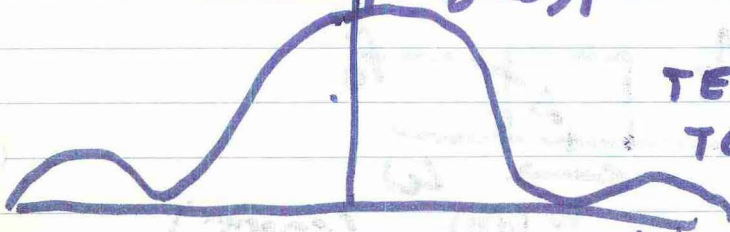 $|F(j\omega)|^2$ TELLS WHERE
TO PUT THE
FILTER

$|F(j\omega)|^2$ ENERGY SPECTRAL DENSITY




$$Y(t) = x(t) * h(t)$$

$$Y(j\omega) = X(j\omega) H(j\omega)$$


$$Y(j\omega) Y^*(j\omega) = [X(j\omega) H(j\omega)] [X^*(j\omega) H^*(j\omega)]$$

$$\therefore [Y(j\omega)]^2 = [X(j\omega)]^2 \cdot [H(j\omega)]^2$$

ENERGY TRANSFER FUNC.

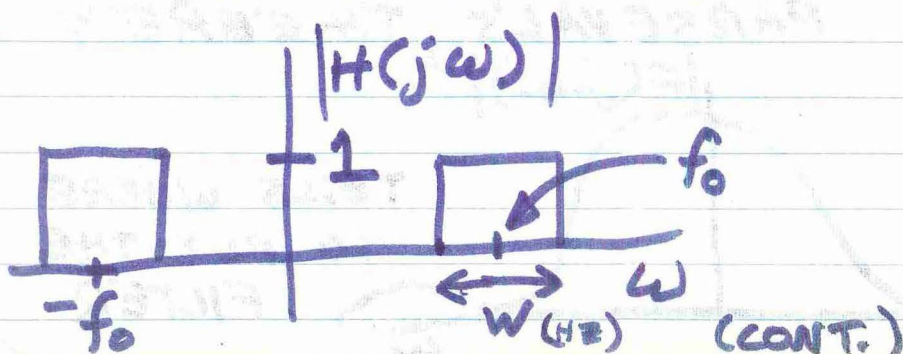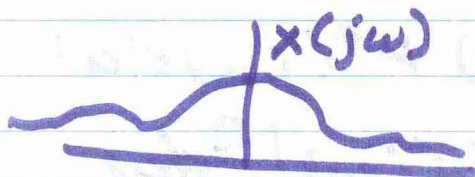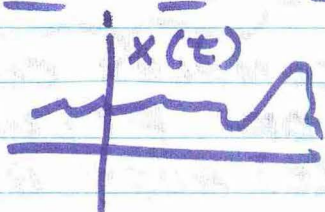

$$E_{OUT} \propto \int |H(j\omega)|^2 |x(j\omega)|^2 d\omega$$

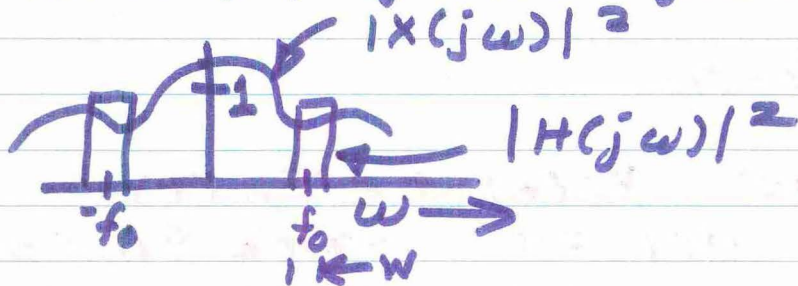

$$E_{OUT} = 2 \int_{f_0 - \frac{W}{2}}^{f_0 + \frac{W}{2}} |x(j\omega)|^2 d\omega$$

$$\approx 2 |x(j2\pi f_0)|^2 \cdot W$$

FOR SHORT B.W.


$$\Rightarrow |x(j2\pi f_0)|^2 = \frac{E_{OUT}}{2W}$$

MATHEMATICAL THINGS FOR FM

TIME SCALE: $f(t) \leftrightarrow F(j\omega)$; $f(at) \leftrightarrow \frac{1}{|a|} F(j\omega/a)$

DELAY: $f(t-t_0) \leftrightarrow e^{-j\omega t_0} F(j\omega)$

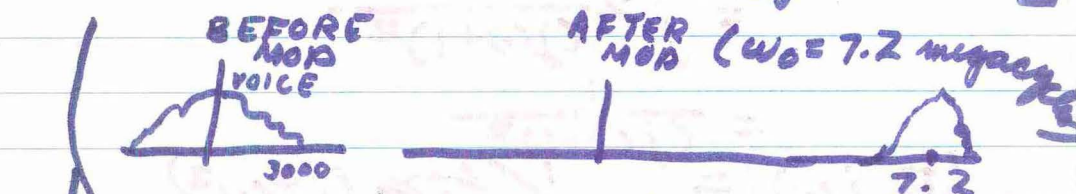MODULATION: $e^{+j\omega_0 t} f(t) \leftrightarrow F[j(\omega - \omega_0)]$



$$\cos(\omega_0 t) f(t) \leftrightarrow \frac{1}{2} F(j\omega - \omega_0)$$

$$\sin(\omega_0 t) f(t) \leftrightarrow \frac{j}{2} F(j\omega - \omega_0) + \frac{j}{2} F(j\omega + \omega_0)$$

54

$$\mathcal{F}\{x\} = Y \Leftrightarrow \mathcal{F}\{Y\} = X$$



10-²⁹30-70

$$5-14) \quad v_i(t) = t e^{-t} u(t)$$

$$H(j) = 1 \quad -2\pi W \leq \omega \leq 2\pi W$$

$$= 0 \quad \text{ELSEWHERE}$$

$$(R=1)$$

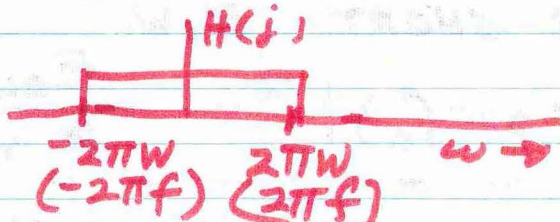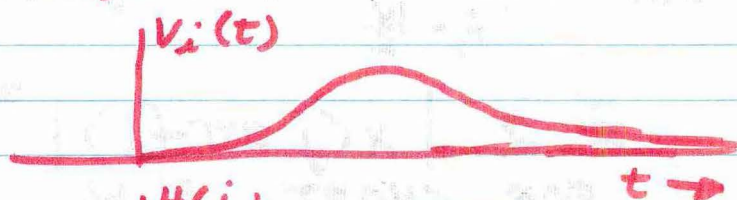

$$\mathcal{F}\{v_i(t)\} = j \frac{d}{d\omega} \left(\frac{1}{j\omega + 1} \right)$$



$$= F(j\omega) = \int_0^{\infty} t e^{-t} e^{-j\omega t} dt$$

$$= -j^2 \frac{1}{(j\omega + 1)^2}$$

$$= \frac{1}{(j\omega + 1)^2}$$

$$|F(j\omega)| = \frac{1}{\sqrt{1 + \omega^2}}$$

$$|F(j\omega)| = \frac{1}{(1 + \omega^2)^2}$$

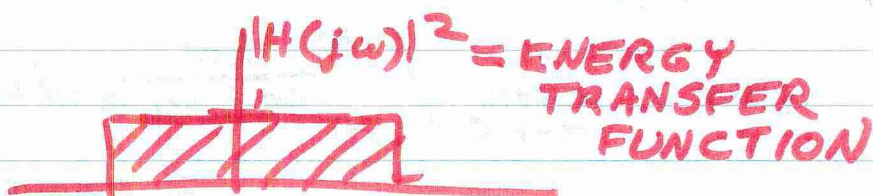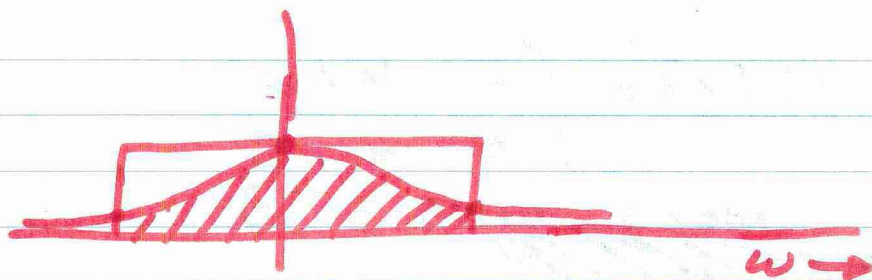


$|H(j\omega)|^2 = \text{ENERGY TRANSFER FUNCTION}$

“TOTAL ENERGY”

$$\int_{-\infty}^{\infty} \left(\frac{1}{1+\omega^2}\right)^2 d\omega = \int_{-2\pi f}^{2\pi f} \left(\frac{1}{1+\omega^2}\right)^2 d\omega$$

10-30-70

TRANSFORMS OF POWER SIGNALS

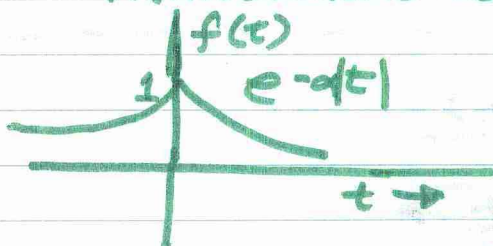

AREA IS FINITE
AS $t \rightarrow 0, f(t) = 1$

WANT NOW TO TAKE LIMIT OF TRANSFORM

$$F(j\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$$

$$= \int_{-\infty}^{\infty} e^{\alpha t} e^{-j\omega t} dt + \int_0^{\infty} e^{-\alpha t} e^{-j\omega t} dt$$

$$= \frac{e^{(\alpha - j\omega)t}}{\alpha - j\omega} \Big|_{-\infty}^0 + \frac{e^{(-\alpha - j\omega)t}}{-\alpha - j\omega} \Big|_0^{\infty}$$

$$= \frac{1}{\alpha - j\omega} + \frac{1}{\alpha + j\omega} = \frac{2\alpha}{\alpha^2 + \omega^2}$$

$$F(1) = \lim_{\alpha \rightarrow 0} \frac{2\alpha}{\alpha^2 + \omega^2} = \begin{cases} 0 & \text{IF } \omega \neq 0 \\ \infty & \text{IF } \omega = 0 \end{cases}$$

$$\therefore \mathcal{F}\{1\} = \begin{cases} 0 & \omega \neq 0 \\ \infty & \omega = 0 \end{cases}$$

LOOKS LIKE $\delta(t)$
~~DOES NOT~~


$$\text{DOES } \lim_{\alpha \rightarrow 0} \int_{-\infty}^{\infty} \frac{2\alpha}{\alpha^2 + \omega^2} d\omega$$

= CONST ?


IT DOES, BY GEORGE \Rightarrow
 CONST. = 2π

$$\therefore \mathcal{F}\{1\} = 2\pi \delta(\omega)$$
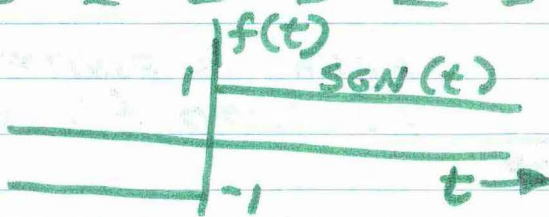
$$\mathcal{F}\{K\} = 2\pi K \delta(\omega)$$



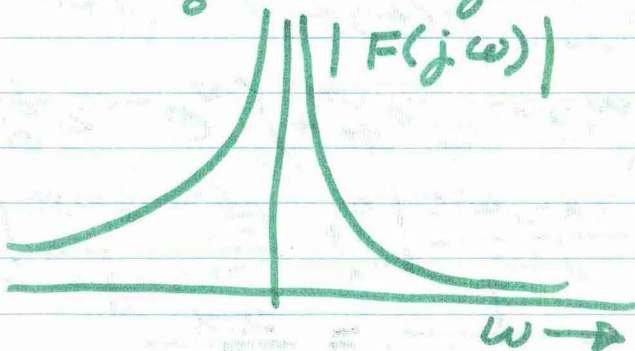
$$\mathcal{F}\{\text{sgn}(t)\} = \frac{2}{j\omega}$$




$$\mathcal{F}\{\mu(t)\} = \mathcal{F}\left\{\frac{1}{2}(\operatorname{sgn}(t) + 1)\right\}$$
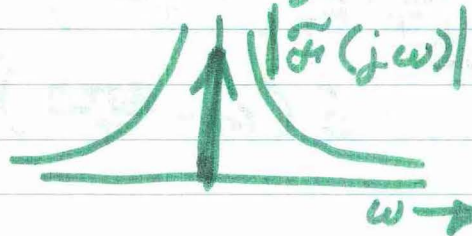
$$= \frac{1}{j\omega} + \pi\delta(\omega)$$



$$\mathcal{F}\{e^{j\omega_0 t}\} = \mathcal{F}\{e^{j\omega_0 t} (1)\}$$

$$= 2\pi\delta(\omega - \omega_0)$$

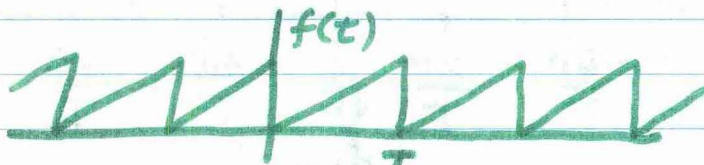

$$f(t) = \sum_{n=-\infty}^{\infty} \alpha_n e^{jn\omega_0 t}$$


$$\mathcal{F}\{f(t)\} = \mathcal{F}\left\{\sum_{n=-\infty}^{\infty} \alpha_n e^{jn\omega_0 t}\right\}$$

$$= \sum_{n=-\infty}^{\infty} \alpha_n \mathcal{F}\{e^{jn\omega_0 t}\}$$

$$= \sum_{n=-\infty}^{\infty} \alpha_n 2\pi\delta(\omega - n\omega_0)$$

$$\alpha_n = \frac{1}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} f(t) e^{-jn\omega_0 t} dt$$
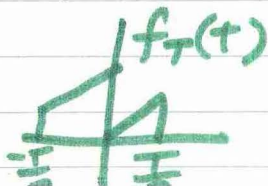
$$= \frac{1}{T} \int_{-\infty}^{\infty} f_T(t) e^{-jn\omega_0 t} dt$$




$$= \frac{1}{T} F_T(jn\omega_0)$$

(CONT)

$$\omega_0 = 2\pi T$$
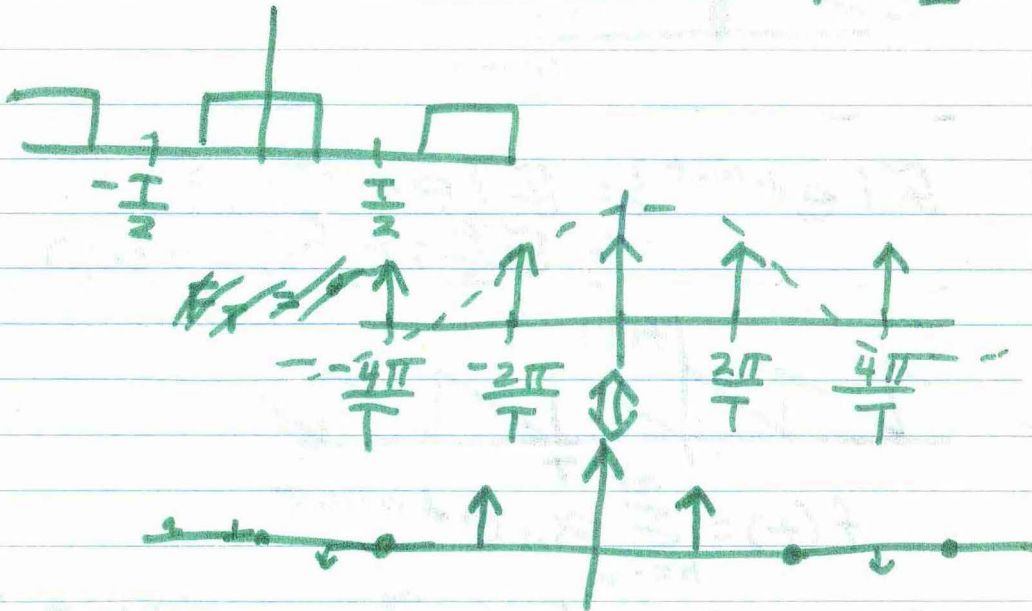
$$\therefore \mathcal{F}[f(t)] = \sum_{n=-\infty}^{\infty} \left[\frac{2\pi}{T} F_T \left(j \frac{2\pi n}{T} \right) \cdot \delta \left(\omega - \frac{2\pi n}{T} \right) \right]$$



11-3-70

$$\mathcal{F}\{f_1 * f_2\} = F_1(j\omega) F(j\omega)$$


$$\mathcal{F}\{f_1 \cdot f_2\} = F_1(j\omega) \otimes F(j\omega)$$

↑
CONVOLUTION OF
COMPLEX NUMBERS

LATTER CONCERNED WITH
MODULATION (MULTIPLYING 2
FUNCTIONS TOGETHER)




a.m. (AMPLITUDE MODULATION)
HIT RECORD
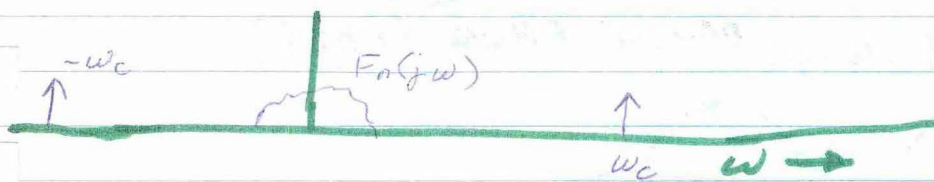
$$f(t) = \underbrace{(1 + f_m(t))}_{f_1(t)} \underbrace{\cos(\omega_c t)}_{f_2(t)}$$








$$f(t) = \cos \omega_c t + f_m(t) \cos \omega_c t$$

TOTAL MODULATED SPECTRUM.

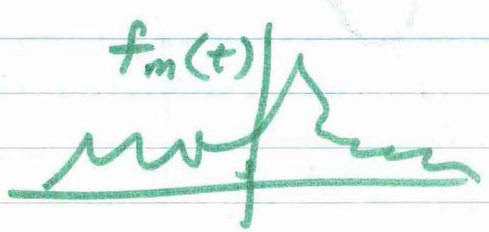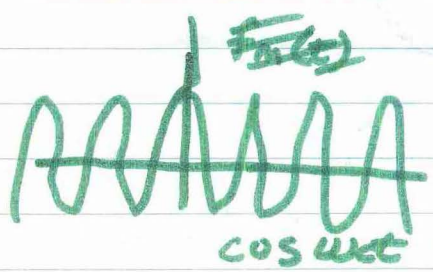
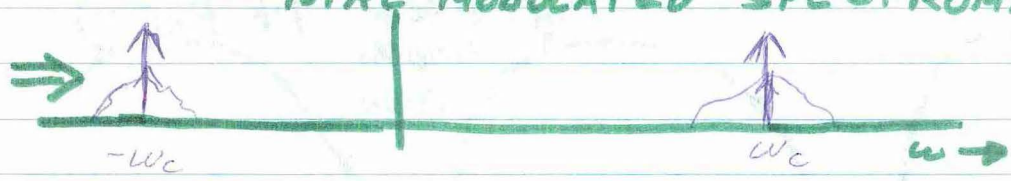


(CONT)

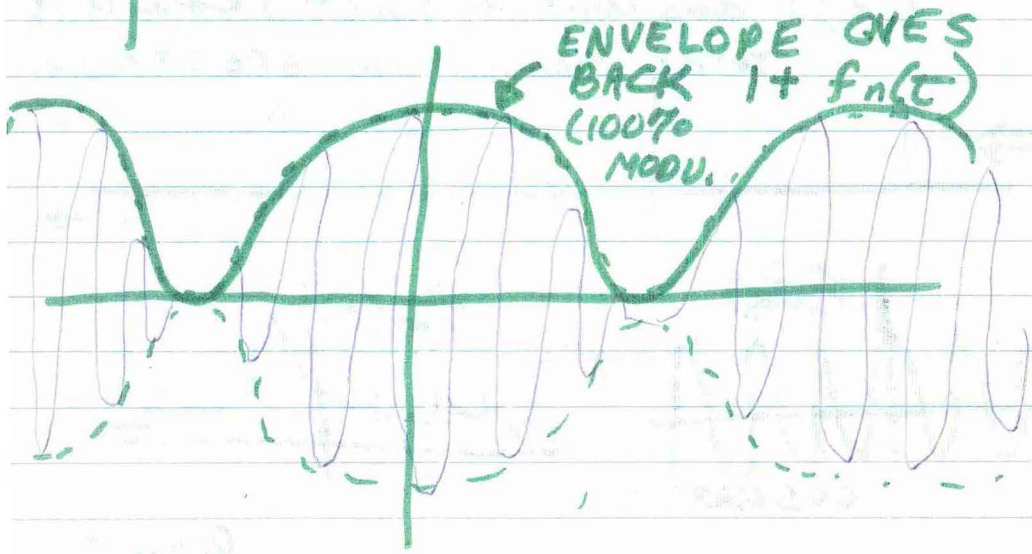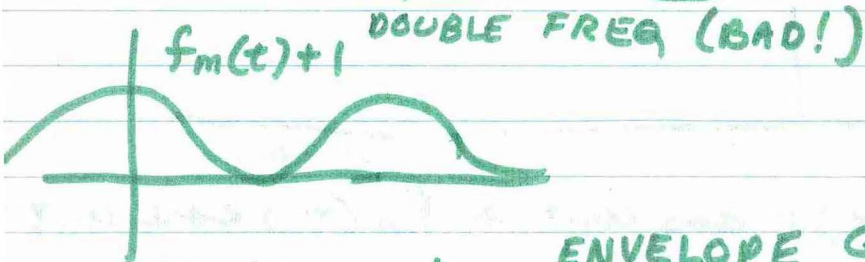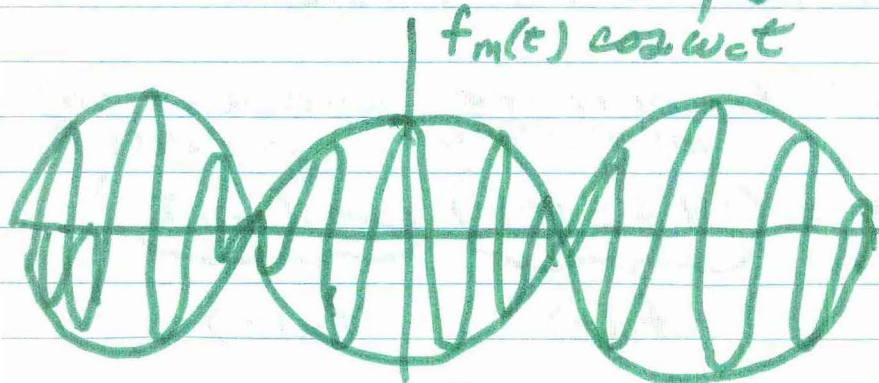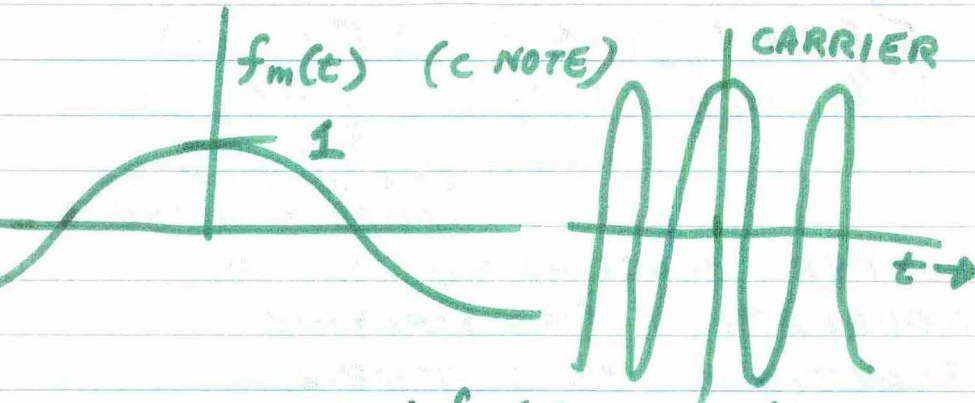


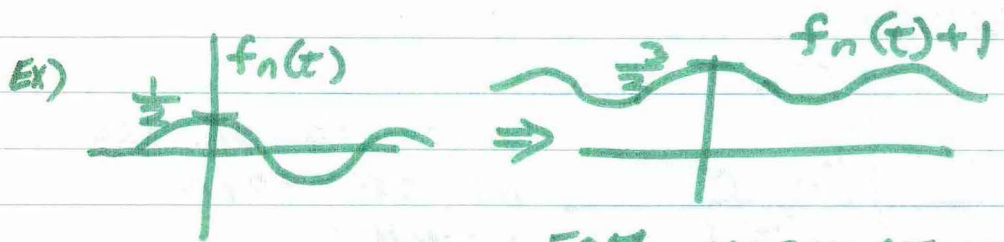

50% MODULATION

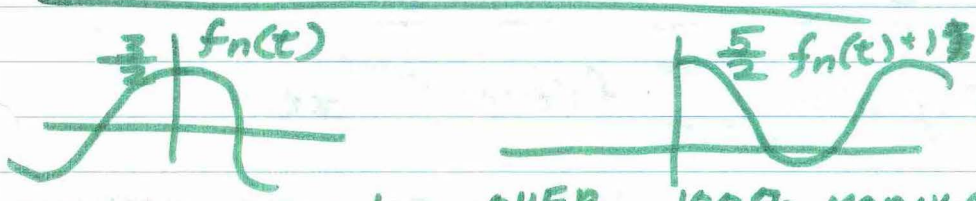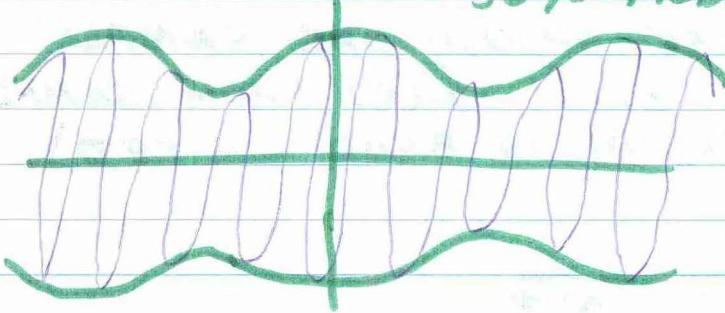


OVER 100% MODULATION

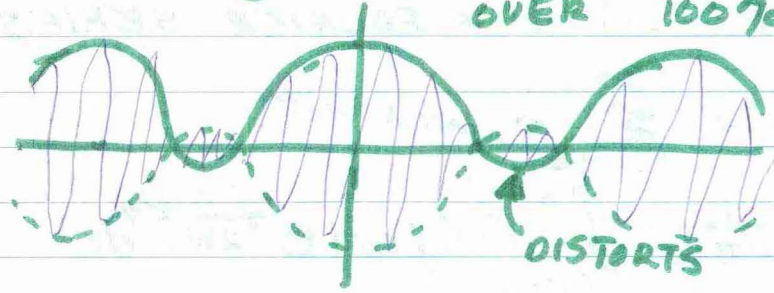

DISTORTS


SAMPLING

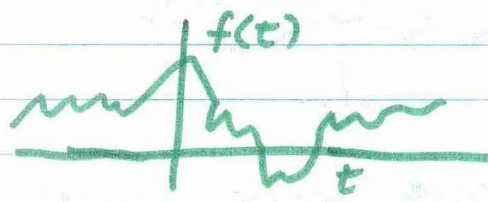

WANT TO SAMPLE AT CERTAIN VALUES.

HOW CLOSE SHOULD ONE SAMPLE TO GET BACK $f(t)$ FROM SAMPLES?

(IF $F(j\omega)$ IS BAND LIMITED)

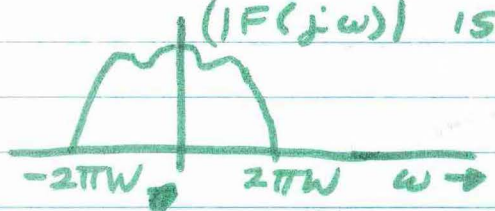

$$F(j\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$$

EXPAND $F(j\omega)$ IN A FOURIER SERIES

$$F(j\omega) = \sum_{n=-\infty}^{\infty} a_n e^{j\omega_n t}$$

$$a_n = \frac{1}{4\pi W} \int_{-2\pi W}^{2\pi W} F(j\omega) e^{-\frac{j n \omega}{2W}} d\omega$$


COMPARE

$$\text{BUT } f(t) = \frac{1}{2\pi} \int_{-2\pi W}^{2\pi W} F(j\omega) e^{j\omega t} d\omega$$

LET $t = \frac{n}{2W}$

$$f(t) = f\left(\frac{n}{2W}\right) = \frac{1}{2\pi} \int_{-2\pi W}^{2\pi W} F(j\omega) e^{j\frac{\omega n}{2W}} d\omega$$

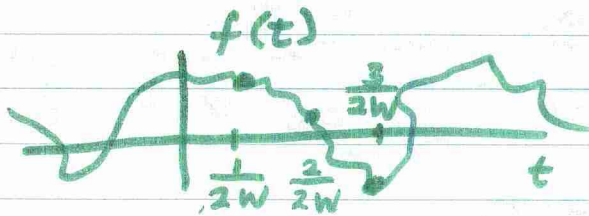
$$\Rightarrow a_n = \frac{1}{2W} f\left(\frac{n}{2W}\right)$$



THUS: KNOWING $f(t)$ AT DISCRETE
 SAMPLING POINTS ($t = \frac{n}{2W}$)
 DETERMANS a_n EXACTLY.
 KNOWING a_n EXACTLY, WE
 CAN FIND $F(j\omega)$ EXACTLY
 KNOWING $F(j\omega)$ EXACTLY,
 WE CAN FIND $f(t)$ EXACTLY
 FOR ALL TIMES t .

SAMPLING RATE MUST BE $> 2W$ ^{SAMPLES} SEC
 " INTERVAL " " $< 2W$ SECS


11-4-70

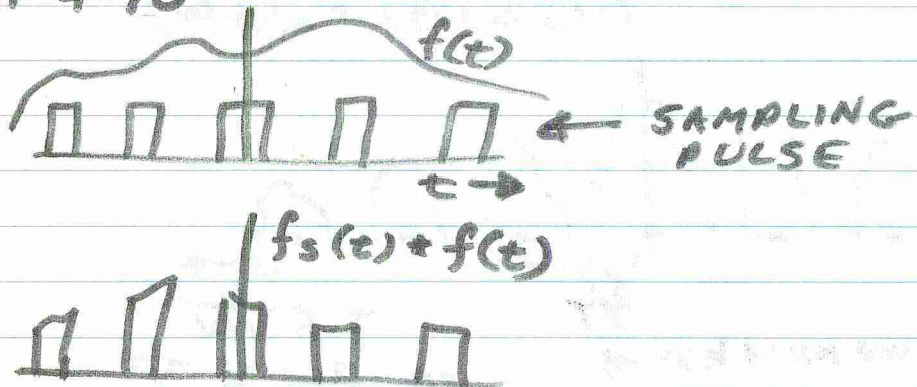



$$\mathcal{F}\{f_s(t)f(t)\}$$

$$= F_s(j\omega) \otimes F_f(j\omega)$$
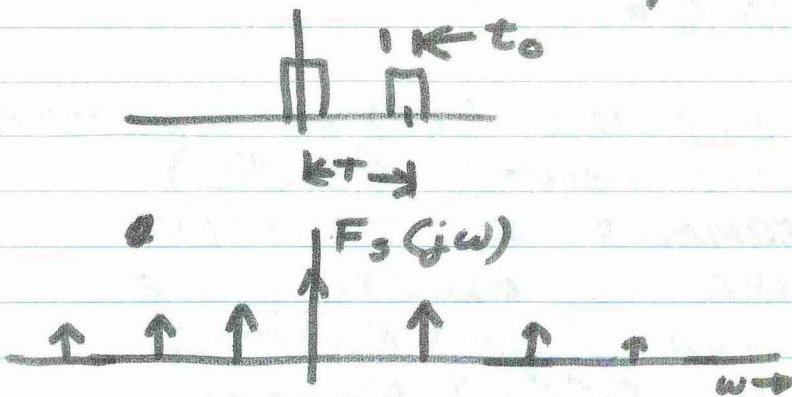
$$F_s(j\omega) = \frac{t_0}{T} \sum_{n=0}^{\infty} \frac{\sin \frac{n\pi t_0}{T}}{\frac{n\pi t_0}{T}} \delta\left(t - \frac{n}{T}\right)$$





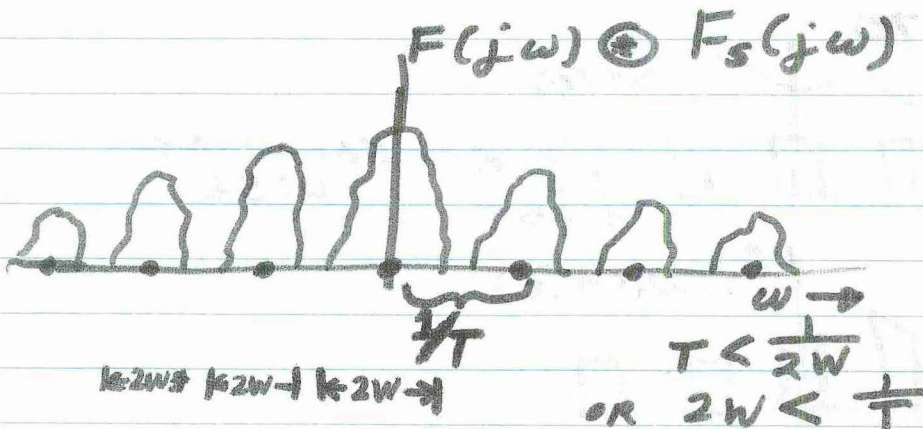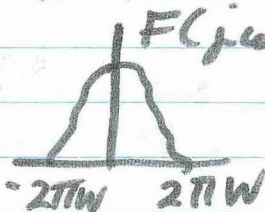INCREASING T FURTHER
BUNCHES UP δ FUNCTIONS



FOR NO INTERFERENCE,
 $\frac{1}{T} > 2W$

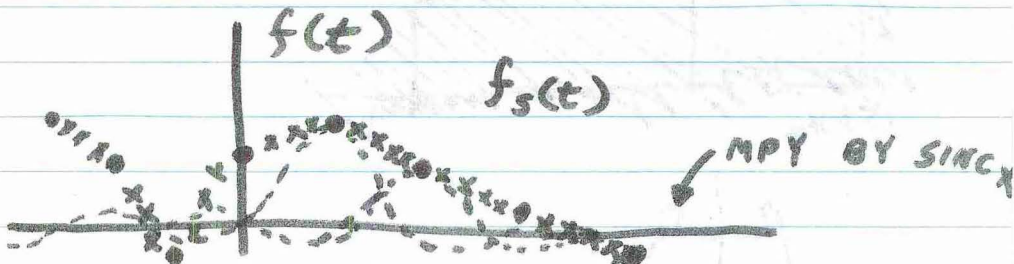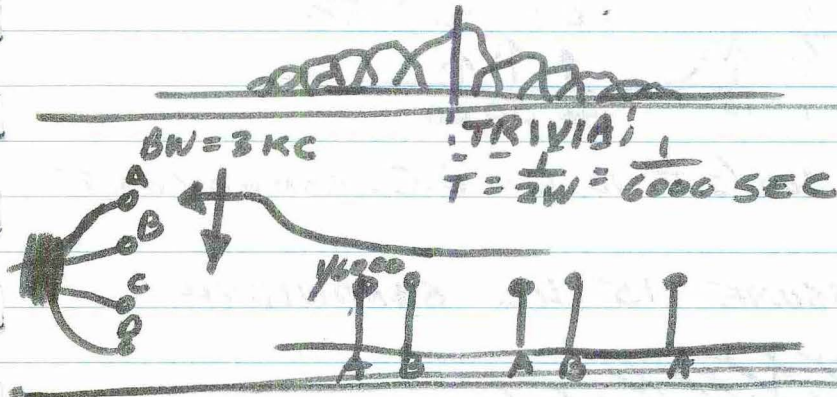SPREADING OUT DELS (SAMPLES)
WILL SMASH ^{SPECTRA} THINGS TOGETHER




SUM UP ALL SINX FOR
EVERY POINT, WILL GET
BACK $f(t)$

11-5-70



#31) $f_s > 20 \text{ Hz} = 2f(t)$

BUT USING A REAL FILTER




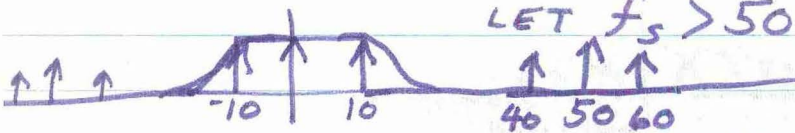
LET $f_s > 50$ 


$$f(t) = \cos(2\pi \cdot 10)t + \text{D.C. COMPONENT}$$

#34) ASSUME 15 KC BANDWIDTH

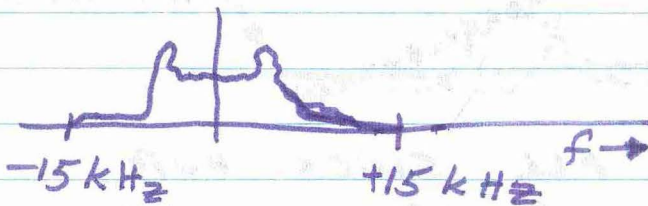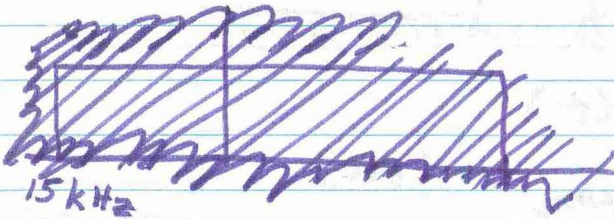SAMPLING RT $> 30 \text{ kHz}$ HIGHER FREQ. WOULD
BE DISTORTED

11-6-70

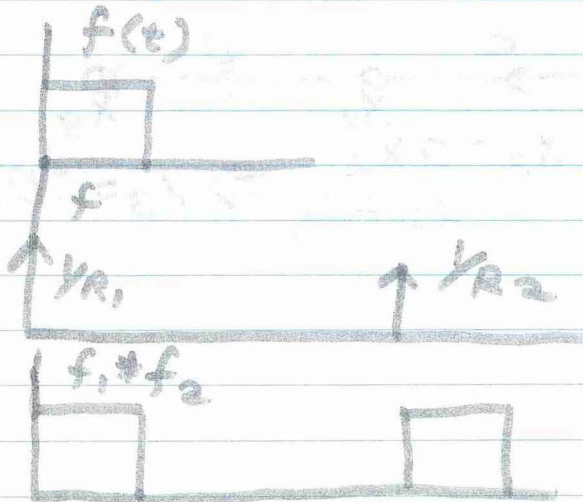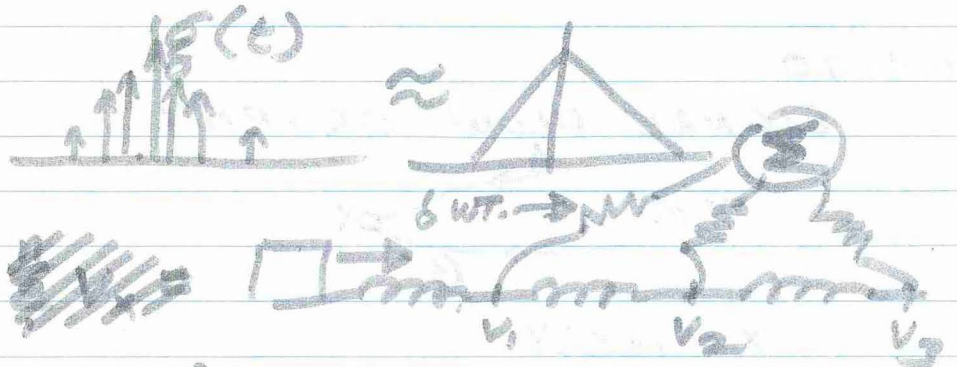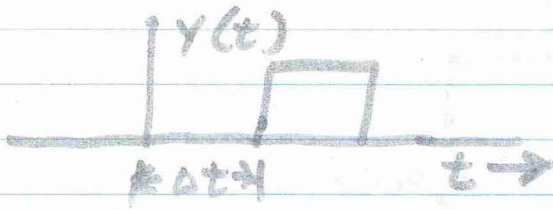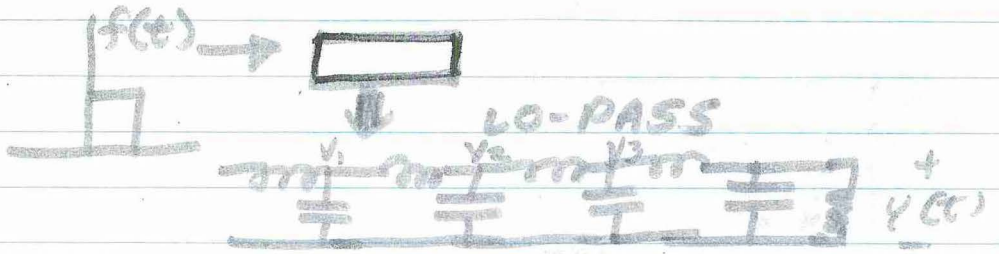

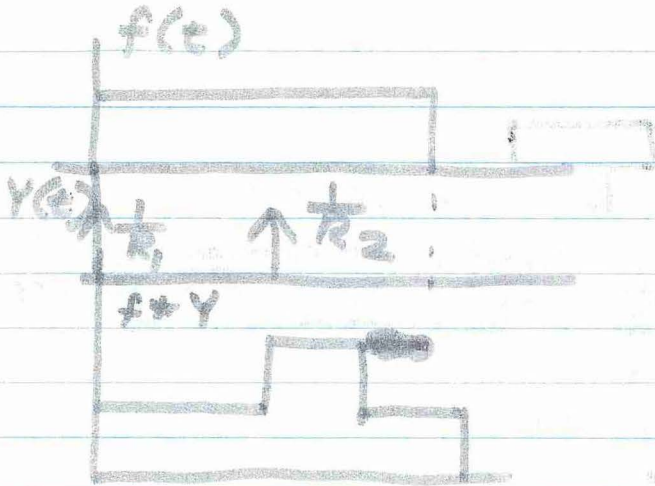


$\sigma = 1 - 11$

VARYING DEL WTS, MAY GET




11-9-70

SIGNAL FLOW GRAPH Y


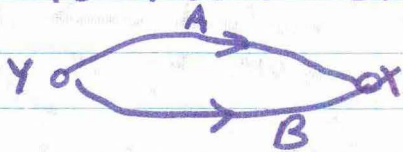


$$X = (A + B)Y$$

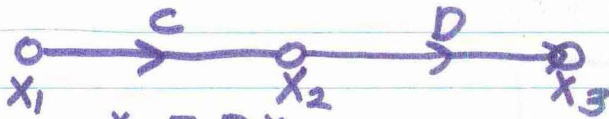

$$X_3 = D X_2 \Rightarrow X_3 = C D X_1$$


$$X_2 = C X_1$$

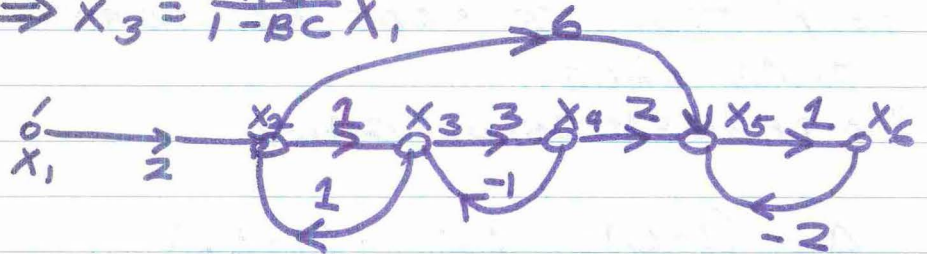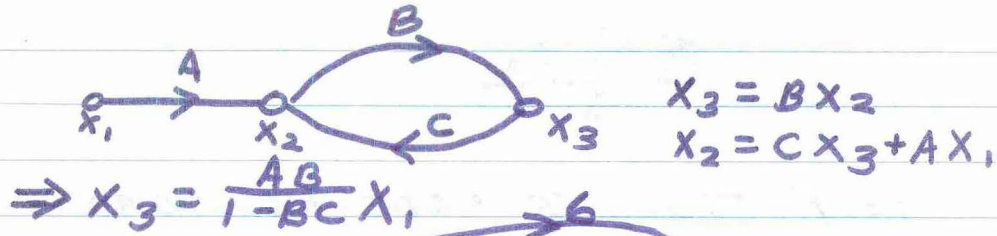

$$As^2 x_1(s) + Bs x_1(s) + Cx_1(s) + Dx(s) = U(s)$$


FACTOR OUT HIGHEST TERM
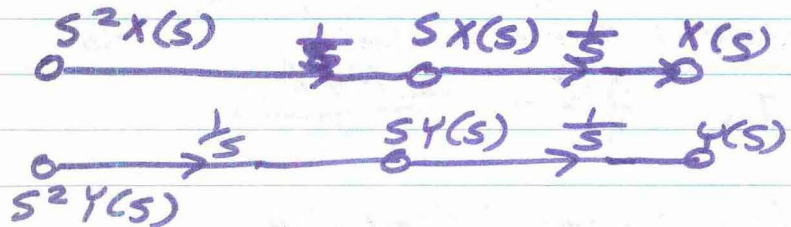
$$s^2 Y(s) + sY(s) + Y(s) + sX_1(s) = 0$$



$$s^2 x(s) = -\frac{B}{A} s x_1(s) - \frac{C}{A} x_1(s) - \frac{D}{A} Y(s) + U(s)/A$$

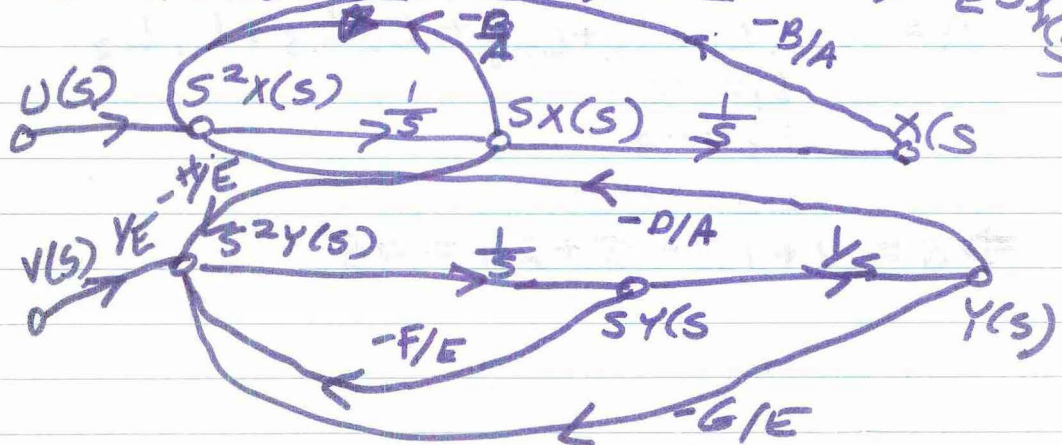
$$s^2 Y(s) = -\frac{F}{E} s Y(s) - \frac{G}{E} Y(s) + \frac{H}{E} s X_1(s)$$



$$T = \frac{\sum P_k \Delta_k}{\Delta}$$

LOOP TOUCHES NODE NO MORE THAN ONCE

T = TRANSMISSION GAIN

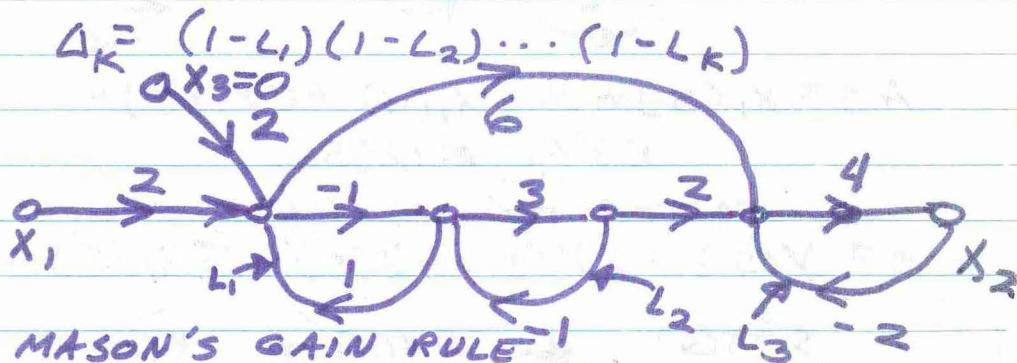

$$T_A = \frac{X_2}{X_1} = \frac{\sum P_k \Delta_k}{\Delta}$$

$$\Delta = (1-L_1)(1-L_2)(1-L_3)$$

$$= 1 - (L_1 + L_2 + L_3) + L_1 L_2 + L_2 L_3 - L_1 L_2 L_3$$

IF TWO LOOPS SHARE A NODE

OR A BRANCH, STRIKE OUT

$$\therefore \Delta = 1 - (L_1 + L_2 + L_3) + L_2 L_3 + L_1 L_3$$

$$L_1 = -1$$

$$L_2 = -3$$

$$L_3 = -8$$

$$\Rightarrow \Delta = 1 + 12 + 8 + 24 = 45$$


● STRIKE OUT ALL LOOPS WITH COMMON NODES

$$\Rightarrow \Delta_1 = 4 ; \Delta_2 = 1$$


$$\therefore T = \frac{X_2}{X_1} = \frac{\sum P_k \Delta_k}{\Delta} = \frac{P_1 \Delta_1 + P_2 \Delta_2}{\Delta}$$

$$\begin{aligned} \text{GAIN OF PATH 1} &= P_1 = 48 \\ \text{" " " 2} &= P_2 = -48 \end{aligned}$$
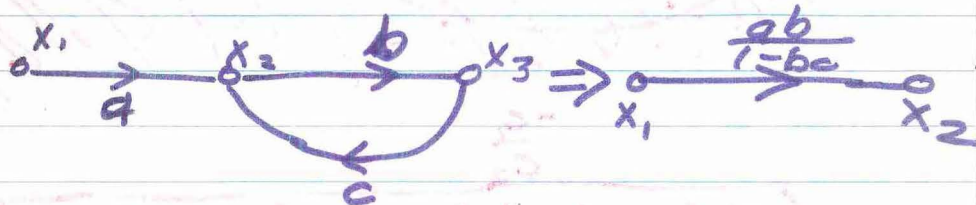
$$\begin{aligned} \Rightarrow T &= \frac{(48 \cdot 4) + (-48 \cdot 1)}{45} = \frac{3 \cdot 48}{45} \\ &= \frac{144}{45} = 3 \frac{1}{5} \end{aligned}$$




11-10-70

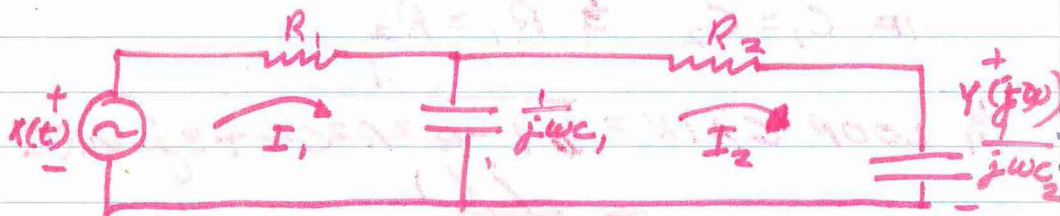

$$X(s) = I_1(s) [R_1 + \frac{1}{j\omega c_1}] + I_2 (\frac{1}{j\omega c_1})$$

$$Y(t) = \frac{1}{j\omega c_1} (I_2 - I_1) - R_2 I_3$$

$$Y(t) = j\omega c_2 I_2$$

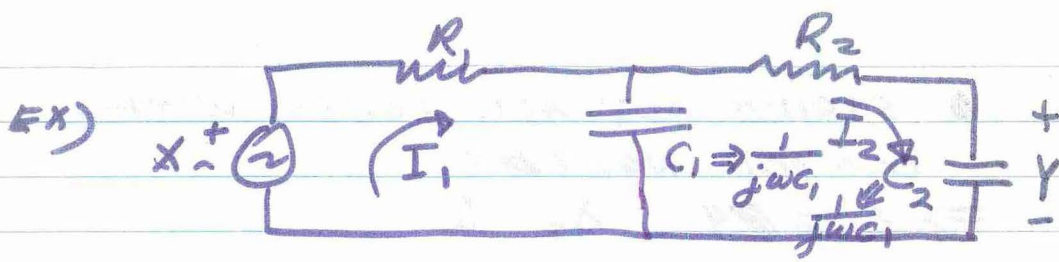


WILL GET 2 SIMUL. D.E.S

$$Y(j\omega) = \frac{1}{j\omega C_2} I_2(j\omega)$$

(PLAY WIT. IT)

11-10-70

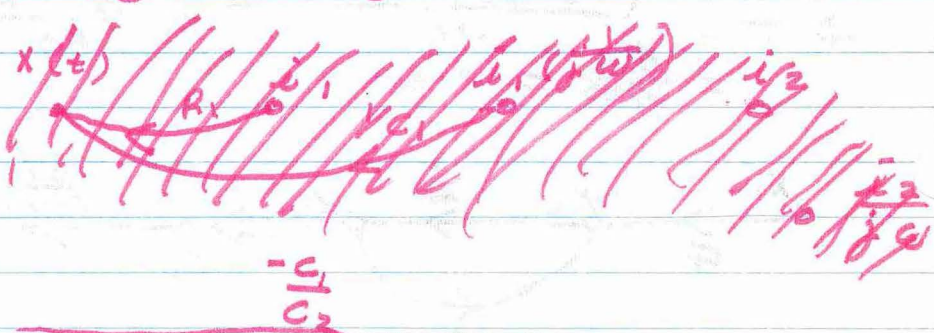

$$\frac{-\frac{C_1}{C_2}}{(1 + R_1 C_1 j\omega)(j\omega C_2 R_2 + 1 + C_1 C_2 \omega^2)}$$

IF $C_1 = C_2$ & $R_1 = R_2$

$$\text{LOOP GAIN} = \frac{1}{(1 + j\omega RC)^2}$$

(5.11)

10-12-70

$$Y(s) = H(s)X(s) = \frac{P(s)}{Q(s)}$$

$$= \frac{K[s^m + a_1 s^{m-1} + \dots + a_{m-1} s + a_m]}{s^n + b_1 s^{n-1} + \dots + b_{n-1} s + b_n}$$

SHOULD MAKE $n \geq m$

$$\text{EX) } Y(s) = \frac{s^2 + 2s + 3}{s + 1}$$

$$s+1 \overline{) \frac{s+1 + \frac{2}{s+1}}{s^2 + 2s + 3}}$$

$$\mathcal{L}\{\delta(t)\} = 1; \quad \mathcal{L}\{\delta'(t)\} = s$$

$$\text{ASSUME } m < n \quad \text{THEN } Y(s) = \frac{K(s+z_1)(s+z_2)\dots(s+z_m)}{(s+p_1)(s+p_2)\dots(s+p_n)}$$

z = ZERO DETERMINES MAGNET. OF RESP.
 POLE = DETERMINE "FORM" OF RESP.
 POLES RTS. OF $Q(s) = -p_1, -p_2, \dots, -p_n$

PARTIAL FRACTION EXPANSION:

$$Y(s) = \frac{K_1}{s+p_1} + \frac{K_2}{s+p_2} + \dots + \frac{K_i}{s+p_i} + \dots + \frac{K_n}{s+p_n}$$

FOR DISTINCT, NON REPEATED RTS

K_i 'S ARE RESIDUES AT THE
 POLES p_i

$$K_i = (s+p_i)Y(s) \Big|_{s=-p_i}$$

$$\text{EX) } Y(s) = \frac{24(s+1)(s+2)}{s(s+3)(s+4)(s^2+2s+4)}$$

$$(s+1+j\sqrt{3})(s+1-j\sqrt{3})$$

$$= \frac{K_1}{s} + \frac{K_2}{s+3} + \frac{K_3}{s+4} + \frac{K_4}{s+1+j\sqrt{3}} + \frac{K_5}{s+1-j\sqrt{3}}$$

$$K_1=1; K_2 = \frac{-16}{7}; K_3=3; K_4 = -0.86-j.99$$

$$K_4^* = K_5 = -0.86+j.99$$

REPEATED LINEAR FACTORS

$$Y(s) = \frac{K(s+z_1) \cdots (s+z_n)}{(s+p_1)^r (s+p_2) \cdots (s+p_n)}$$

$$= \frac{C_1}{s+p_1} + \frac{C_2}{(s+p_1)^2} + \cdots + \frac{C_{r-1}}{(s+p_1)^{r-1}} + \frac{C_r}{(s+p_1)^r}$$

$$+ \frac{K_2}{s+p_2} + \frac{K_3}{s+p_3} + \cdots + \frac{K_n}{s+p_n}$$

SOLVE FOR ALL K_i 'S

TO FIND C_r MPY BY $(s+p_1)^r$

$$\Rightarrow \left. Y(s)(s+p_1)^r \right|_{s=-p_1} = C_r$$

$$\frac{d}{ds} (s+p_1)^r Y(s) \Big|_{s=-p_1} = (r-1)(s+p_1)^{r-2} + \dots + 1 C_{r-1} + 0$$

$$\frac{d}{ds} [(s+p_1)^r Y(s)] \Big|_{s=-p_1} = C_{r-1}$$

$$C_{r-n} = \frac{1}{n!} \frac{d^n}{ds^n} [(s+p_1)^r Y(s)] \Big|_{s=-p_1}$$

10-13-70

$$F(s) = \frac{s^2}{(s+1)^2(s+2)}$$

ALTERNATE METHOD FOR REPEATED RTS.

$$\frac{s^2}{(s+1)^2(s+2)} \approx \frac{s^2}{(s+.99)(s+1.01)(s+2)}$$

$$= \frac{k_1}{s+.99} + \frac{k_2}{s+1.01} + \frac{k_3}{s+2} \quad \textcircled{A}$$

$$\text{REALLY } \frac{s^2}{(s+1)^2(s+2)} = \frac{C_1}{s+1} + \frac{C_2}{(s+1)^2} + \frac{K}{s+2} \quad \textcircled{B}$$

ARE ANTI. LAPLACE ABOUT THE SAME

FOR $\mathcal{L}^{-1} \textcircled{A} = k_1 e^{-\alpha t}$

$\mathcal{L}^{-1} \textcircled{B} = k_2 e^{-\alpha t} + k_3 t e^{-\alpha t}$

GIVES ABOUT SAME THING

FROM \textcircled{A}

$$k_1 = \frac{(-.99)^2}{(-.99+1.01)(-.99+2)} = 48.5$$

$$k_2 = -51.5 \quad k_3 = 4$$

$$f(t) = \mathcal{L}^{-1}\{f(s)\} = 48.5 e^{-.99t} - 51.5 e^{-1.01t} + 4 e^{-2t}$$

FOR \textcircled{A}

$$f(s) \textcircled{B} = \frac{-3}{s+1} + \frac{1}{(s+1)^2} + \frac{4}{s+2}$$

$$\Rightarrow f(t) \textcircled{B} = -3 e^{-t} + t e^{-t} + 4 e^{-2t}$$

ALTHOUGH THEY DON'T LOOK VERY EQUAL, BUT THEY JUST ABOUT ARE

(HOW ABOUT THAT)


<10% ERROR

POLE-ZERO PLOTS

PHYSICAL REALIZABILITY & STABILITY
IN TERMS OF $H(s)$


$h(t) \rightarrow$ CAUSAL (ALL LAPLACE $u(t)$)

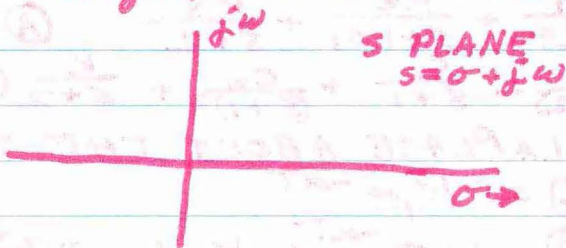$H(j\omega) \rightarrow$ PALEY-WEINER SAYS OKAY



POLE-ZERO PLOT OF $H(s)$ IN s PLANE,
ie) PLOT SINGULARITIES OF $H(s)$

EX)

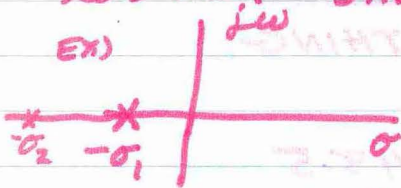

$$\Rightarrow H_1(s) = \dots + \frac{K}{s + \sigma_1}$$

$$\Rightarrow h_1(t) = \dots + K e^{-\sigma_1 t}$$


$$\sigma_2 > \sigma_1 \Rightarrow h_2(t) = \dots + e^{-\sigma_2 t}$$

(DECAYS QUICKER)

$$\Rightarrow h_0(t) = K [u(t)]$$

$$\Rightarrow h_4(t) = K e^{\sigma_4 t}$$

(BLOWS UP)

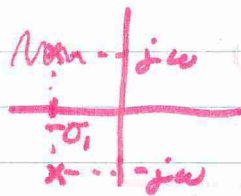


WILL ALWAYS HAVE CONJUGATE PAIRS


$$\Rightarrow H(s) = \dots + \frac{k}{(s+\sigma_1)^2 + \omega_0^2} = \dots + \frac{k}{(s+\sigma_1+j\omega_0)(s+\sigma_1-j\omega_0)}$$

(EX) $s^2 + 2s + 3 \Leftrightarrow (s+1)^2 + 2 \Rightarrow \sigma = -1, \omega_0 = \sqrt{2}$


$h(t) = \dots +$ DECAYING SINUSOID

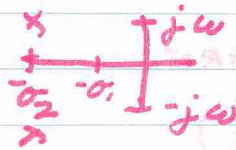

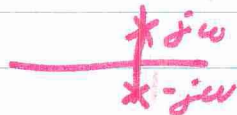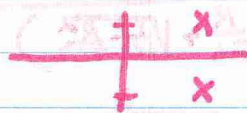
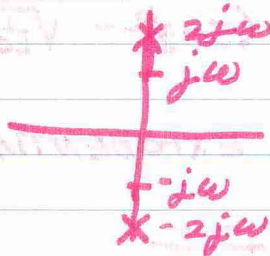
\Rightarrow FASTER DECAY 



\Rightarrow PURE SINUSOIDAL 




\Rightarrow EXPOD. INCR. SINUSOID 



\Rightarrow GREATER ω_0

EVERYTHING IN LFT. HALF OF PLANE IS STABLE, ON $j\omega$ AXIS, MARGINALLY STABLE, ON RT HALF, UNSTABLE (THEY BLOW UP)

79)

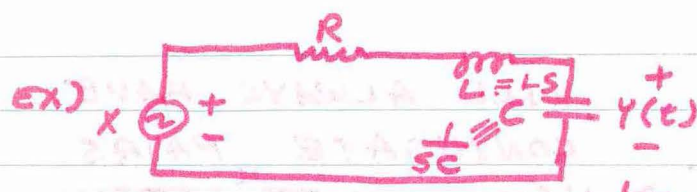

$$H(s) = \frac{Y(s)}{X(s)} = \frac{1/sC}{R + sL + 1/sC}$$


$$H(s) = \frac{1}{s^2LC + sCR + 1}$$

$$= \frac{1}{LC} \left[\frac{1}{s^2 + s\frac{R}{L} + \frac{1}{LC}} \right]$$


COMPLETING SQUARE:

$$H(s) = \frac{1}{LC} \frac{1}{\left(s + \frac{R}{2L}\right)^2 + \left(\frac{1}{LC} - \frac{R^2}{4L^2}\right)}$$
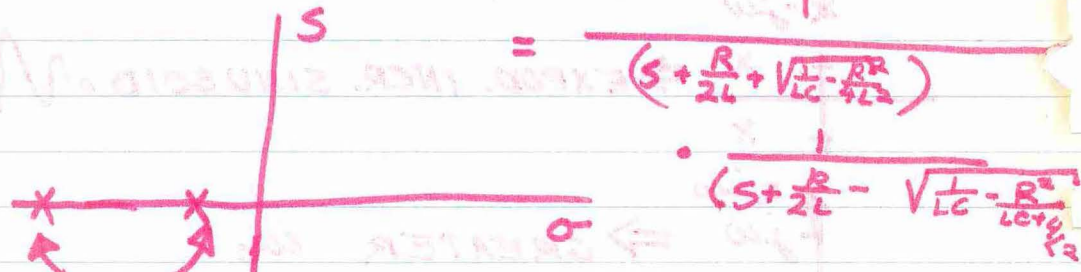
$$= \frac{1}{LC} \left[\frac{1}{(s+d)^2 + (\omega_0)^2} \right]$$




$h(t) = \text{SUM OF 2 EXPONENTIALS}$

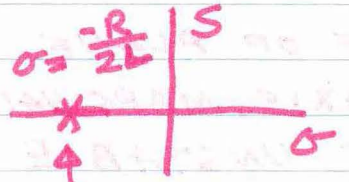







IF 2 POLES EQUAL

CRITICAL DAMPING

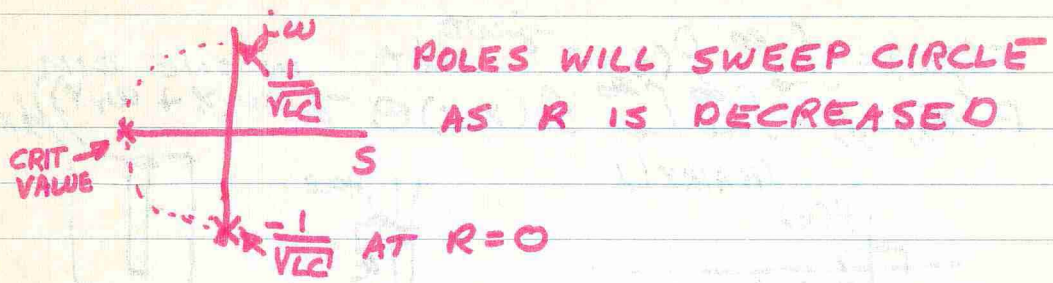


HAVE ZEROS AT $\pm \infty$
 $H(s)$ HAS EQUAL # OF POLES AND ZEROS
 READ SECTION 7-8

10-17-70

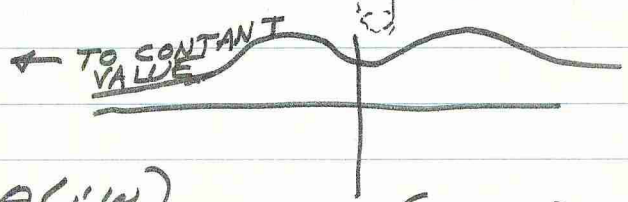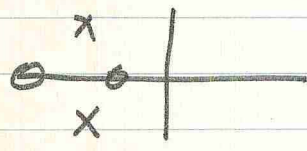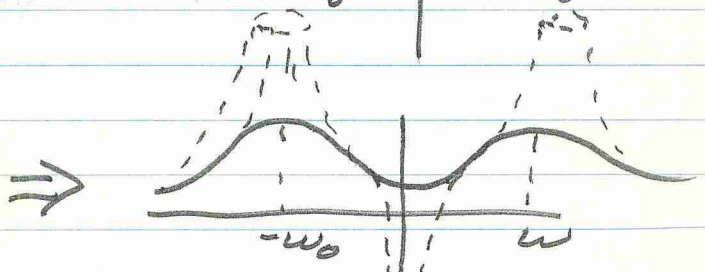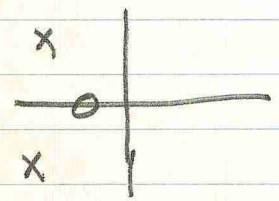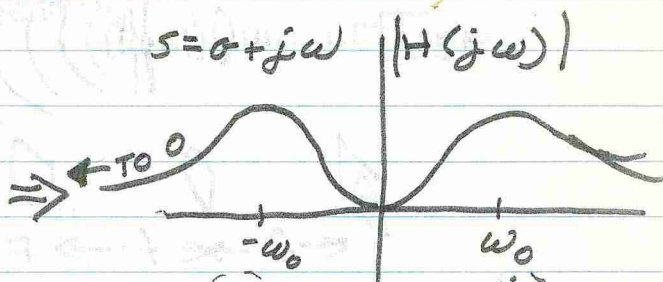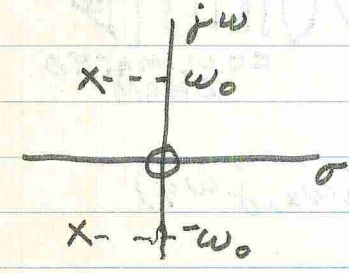

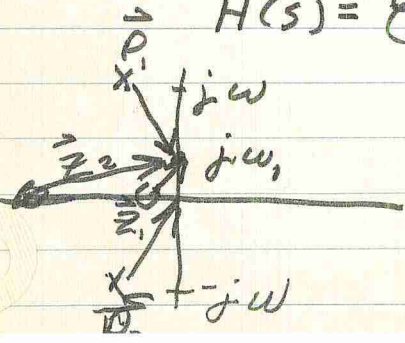HOW TO FIND $\theta(jw)$
 $H(s) = \frac{(s+z_1)(s+z_2)\dots(s+z_m)}{(s+p_1)\dots(s+p_n)}$



$$H(jw) = \frac{\vec{z}_1 \vec{z}_2}{p_1 p_2}$$




$$H(jw) = \frac{|z_1| |z_2| \angle z_1 + z_2}{p_1 p_2 \angle p_1 + p_2}$$

$$= \frac{|z_1| |z_2| \angle z_1 + z_2 - p_1 - p_2}{p_1 p_2}$$

$$F(j\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt \quad \text{IN ONE DIM}$$

$$F(\omega_x, \omega_y) = \int_{-\infty}^{\infty} \int_{-\infty}^{\infty} f(x, y) e^{-j(\omega_x x + \omega_y y)} dx dy$$


(HAIRY!)

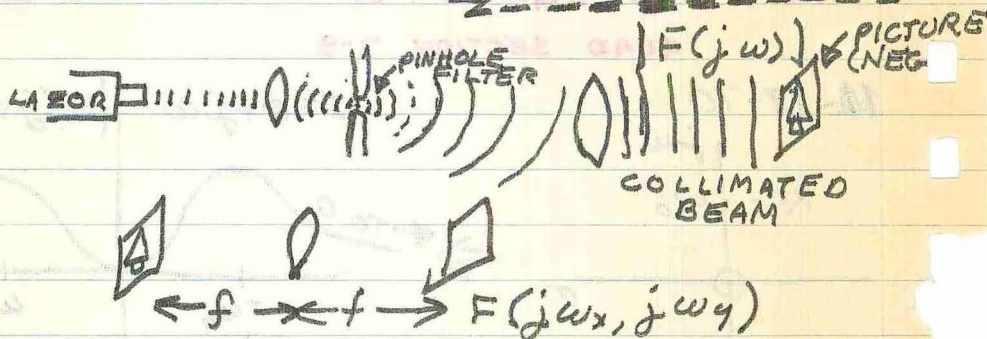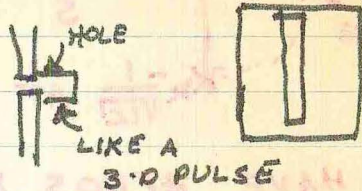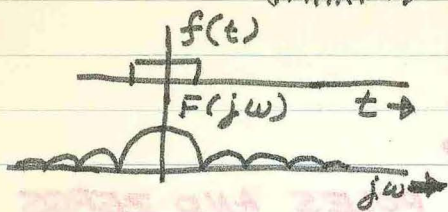

	1	2	3	4	5	6	7	8	9	10
MON	1	2	3	4	5	6	7	8	9	10
TUE	1	2	3	4	5	6	7	8	9	10
WED	1	2	3	4	5	6	7	8	9	10
THURS	1	2	3	4	5	6	7	8	9	10
FRI	1	2	3	4	5	6	7	8	9	10

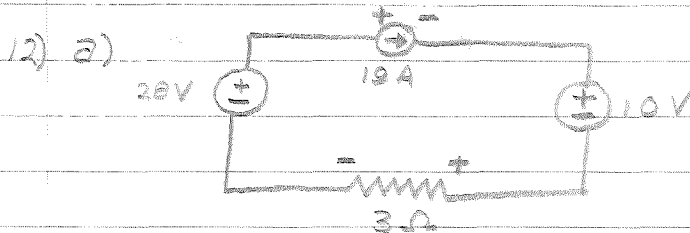7:50 8:45 9:40 10:35 11:30 12:25 1:20 2:15 3:15 4:05
 INTRO TO PROB DDI AVS
 ADV. CALC. I F208 DFO
 PROG PRINC A241 TFK
 E SCI III TFK
 GLEE CLUB
 CONVO
 GLEE CLUB
 GLEE CLUB
 GLEE CLUB





$$P_{28V} = -Vi = (28V)(19A) = -532 \text{ WATTS}$$

$$P_{10V} = Vi = (10V)(19A) = 190 \text{ WATTS}$$

$$P_{cs} = Vi = (10V - 28V)(19A) = -242 \text{ WATTS}$$

$$P_R = Vi = i^2 R = (19A)^2 (3\Omega) = 1083 \text{ WATTS}$$

$$P_s = 29(19) = 741V$$



$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} \begin{bmatrix} 2 & -2 & 0 & 0 \\ 2 & 6 & -4 & 0 \\ 0 & -4 & 10 & -6 \\ 0 & 0 & -6 & 18 \end{bmatrix}$$

$$2(i_1 - i_2) + 4(i_2 - i_3) = 0 \Rightarrow -2i_1 + 6i_2 - 4i_3 + 0 = 0$$

$$4(i_3 - i_2) + 6(i_3 - i_4) = 0 \Rightarrow 0 - 4i_2 + 10i_3 - 6i_4 = 0$$

$$6(i_4 - i_3) + 12i_4 = 0 \Rightarrow 0 + 0 - 6i_3 + 18i_4 = 0$$

$$i_1 + i_2 + i_3 + i_4 = 6.7$$

$$2i_1 = 4i_2 = 6i_3 = 12i_4 \Rightarrow i_1 = 2i_2 = 3i_3 = 6i_4$$

$$6.7 = i_4 + 2i_4 + 3i_4 + 6i_4 = 12i_4 \Rightarrow i_4 = .556 \text{ A}$$

$$i_3 = 2i_4 = 2(.556) = 1.01 \text{ A}$$

$$i_2 = 3i_4 = 3(.556) = 1.67 \text{ A}$$

$$i_1 = 6i_4 = 6(.556) = 3.33 \text{ A}$$

$$P_{2\Omega} = R_i i_1^2 = (2)(3.33)^2 = 22.2 \text{ W} = Vi_1 \Rightarrow V = 6.67 \text{ V}$$


$$P_{cs} = Vi = (6.67)(6.7) = 44.6 \text{ WATTS}$$

$$P_{4\Omega} = R_i i_2^2 = (4)(1.67)^2 = 11.16 \text{ WATTS}$$

$$P_{6\Omega} = R_i i_3^2 = (6)(1.01)^2 = 6.12 \text{ WATTS}$$

$$P_{12\Omega} = R_i i_4^2 = (12)(.556)^2 = 3.70 \text{ WATTS}$$

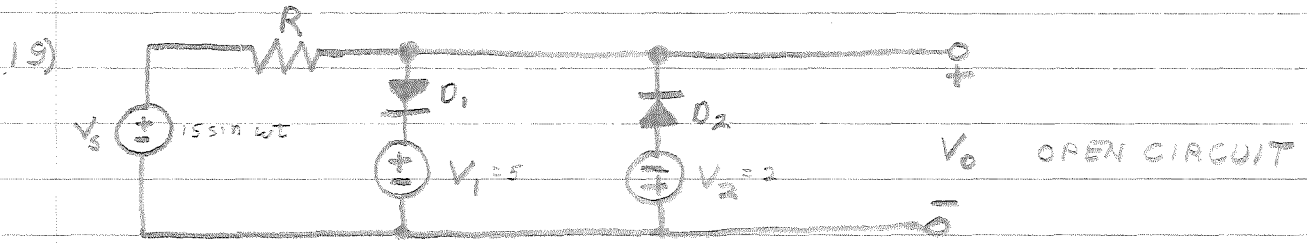
18) BOTH WOULD BE STORED OPEN-
CIRCUITED (A DRY CELL)



$V_s = 15 \sin \omega t$ VOLTS

$V_1 = 5$ VOLTS

$V_2 = 2$ VOLTS

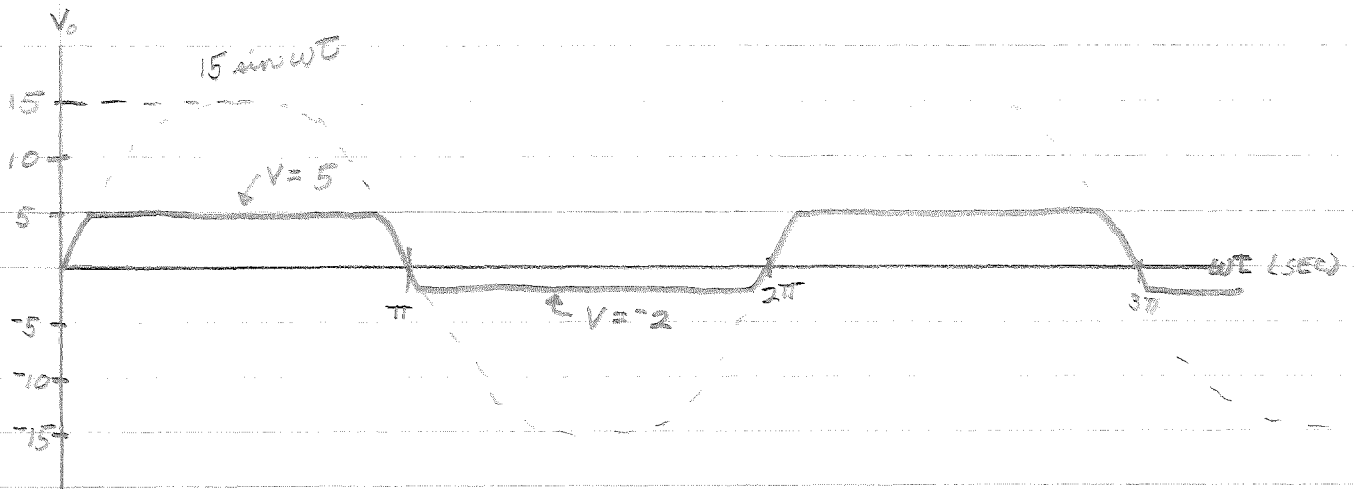


$-2 \leq 15 \sin \omega t \leq 5$

D_1 OPERATES WHEN $0 < V_s \leq 5$

D_2 OPERATES WHEN $-2 \leq V_s < 0$

CHAPT. 3 pp. 91-2

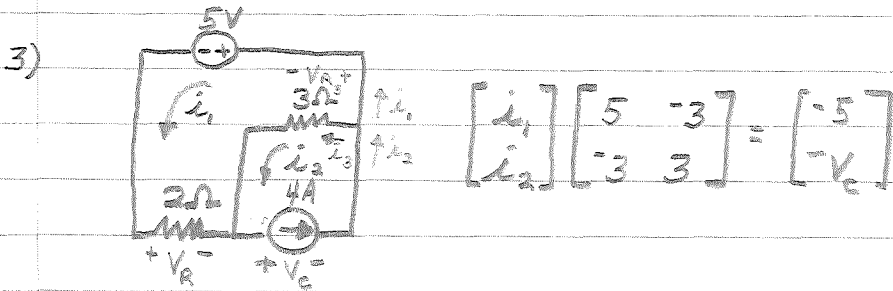

$$2(i_1) + 3(i_1 - i_2) + 5 = 0 \Rightarrow 5i_1 - 3i_2 = -5$$

$$3(i_2 - i_1) + V_C = 0 \Rightarrow -3i_1 + 3i_2 = V_C$$

$$i_2 = 4$$

$$5i_1 - 12 = -5 \Rightarrow 5i_1 = 7 \Rightarrow i_1 = \frac{7}{5}$$

$$V_C = 3\left(\frac{7}{5}\right) - 12 = \frac{21}{5} - \frac{60}{5} = -\frac{39}{5}$$

$$V_R = i_1 R$$


$$V_R = \left(\frac{7}{5}\right)(2) = \frac{14}{5}$$

$$(i_1 + i_3) = i_2 \Rightarrow i_3 = i_2 - i_1 = 4 - \frac{7}{5} = \frac{13}{5}$$

$$V_{R_3} = R_3 i_3 = (3)\left(\frac{13}{5}\right) = \frac{39}{5}$$

	V_{SOURCE}	i_{SOURCE}	R_3	R_2
i	$\left(\frac{7}{5}\right) AMP$	$4 AMP$	$\left(\frac{13}{5}\right) AMP$	$\left(\frac{7}{5}\right) AMP$
V	$4 V$	$\left(-\frac{39}{5}\right) V$	$\left(\frac{39}{5}\right) V$	$\left(\frac{14}{5}\right) V$

CHAPT 3 pg 93

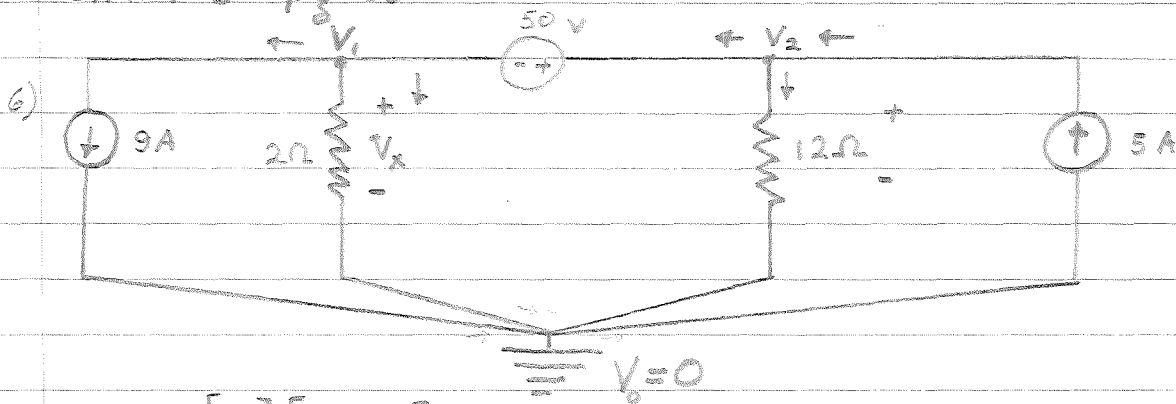

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \begin{bmatrix} 2 & 0 \\ 0 & 12 \end{bmatrix}$$

$$9 + \frac{V_1}{2} - (5 + \frac{V_2}{12}) = 0$$

$$V_1 - V_2 = 50$$

$$9 + \frac{V_1}{2} - 5 + \frac{V_1 - 50}{12} = 0$$

$$V_2 = V_1 - 50$$

$$108 + 6V_1 - 60 + V_1 - 50 = 0$$


$$7V_1 = 12$$

$$V_1 = \frac{12}{7}$$

$$V_1 = V_x = \frac{12}{7} \text{ VOLTS}$$

-14 ✓

13)

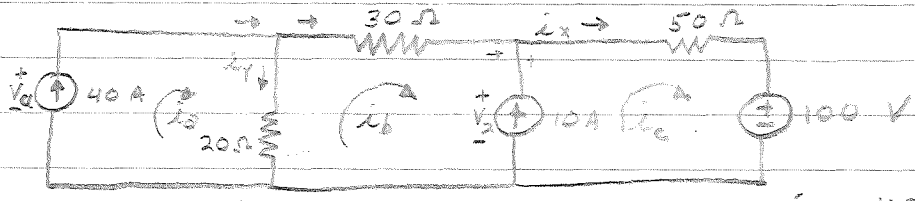

$i_a = 40$

$$20(i_a - i_b) - V_a = 0 \Rightarrow 20i_a - 20i_b = V_a$$

$$20i_b = 800 - V_a$$

$$20(i_b - i_a) + 30i_b + V_2 = 0 \Rightarrow -20i_a + 50i_b = -V_2$$

$$50i_b = 800 - V_2$$

$$50i_c + 100 - V_2 = 0 \Rightarrow 50i_c = V_2 - 100$$

$i_x = 40 - i_b ; i_c = i_x$

$$\begin{bmatrix} i_b \\ i_c \end{bmatrix} \begin{bmatrix} 50 & 0 \\ 0 & 50 \end{bmatrix} = \begin{bmatrix} 800 - V_a \\ V_2 - 100 \end{bmatrix} \quad i_b + 10 = i_c$$


$$800 - 50i_b = 50i_c + 100$$

$$800 - 50i_b = 50i_b + 600$$

$$100i_b = -200 \Rightarrow i_b = -2 \Rightarrow i_x = 42 \text{ AMPS}$$

$$50i_c = 800 \Rightarrow i_c = 40 \Rightarrow i_x = 40 \text{ AMPS}$$

14)

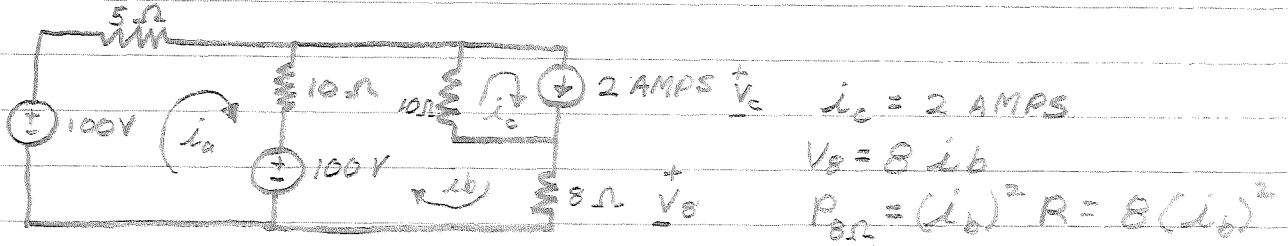

$$\begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} \begin{bmatrix} 15 & -5 & 0 \\ -10 & 28 & -10 \\ 0 & -10 & 10 \end{bmatrix} = \begin{bmatrix} 0 \\ 100 \\ -V_c \end{bmatrix}$$

$$5i_a + 10(i_a - i_b) = 0 \Rightarrow 15i_a - 10i_b = 0$$

$$10(i_b - i_a) - 100 + 10(i_b - i_c) + 8i_b = 0$$

$$\Rightarrow -10i_a + 28i_b - 10i_c = 100$$

$$10(i_c - i_b) + V_c = 0$$

$$15i_a - 10i_b = 0 \Rightarrow 3i_a = i_b$$

$$-10i_a + 28i_b = 120 \Rightarrow -5i_a + 14i_b = 60$$

$$-5i_a + 14(3i_a) = 60$$

$$-5i_a + 42i_a = 37i_a = 60 \Rightarrow i_a = 1.62 \text{ AMPS}$$

$$i_b = 48.6 \text{ AMPS}$$

$$V_8 = 8i_b = 8(48.6) = 389 \text{ VOLTS}$$


$$P_{8\Omega} = i_b^2 R = 18900 \text{ WATTS}$$

ROSE POLYTECHNIC INSTITUTE


EE 201

Special Problems

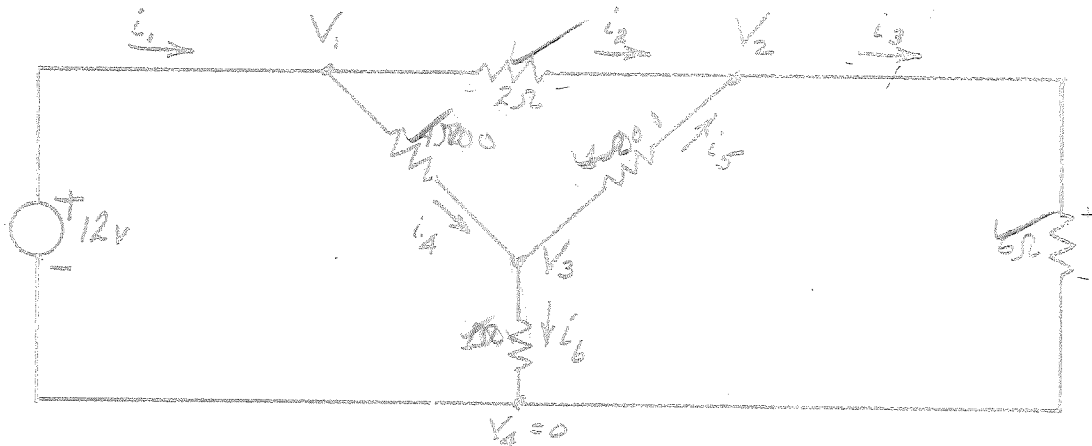
(1) Find all currents and voltages in the following circuit.



(2) Solve for v_1 , v_2 , and v_3 .

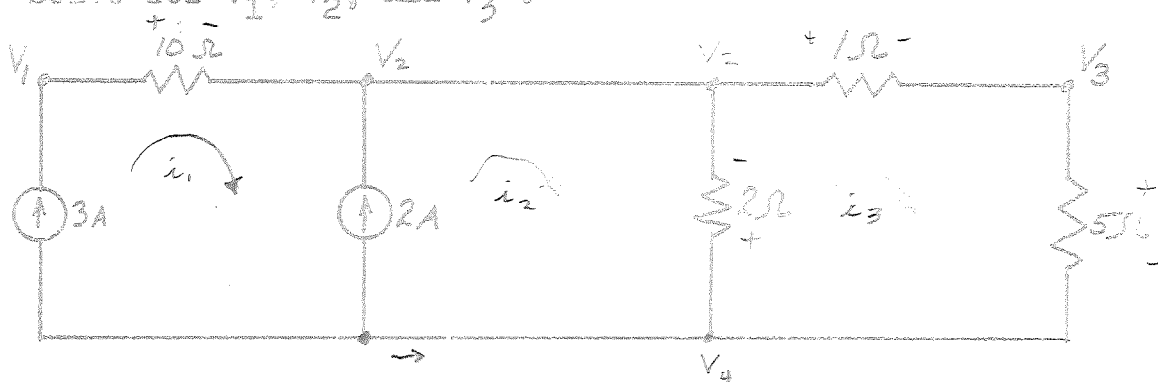

(3) Find V_s and i_2 .

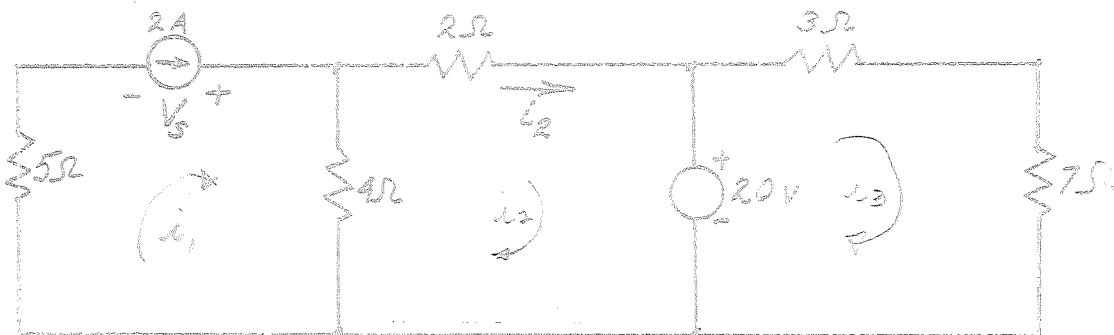

SPECIAL PROBLEM

$$1) \frac{V_1 - V_3}{4} + \frac{V_1 - V_2}{2} = i \Rightarrow V_1 - V_3 + 2V_1 - 2V_2 = 4i$$

$$3V_1 - 2V_2 - V_3 = 4i$$

$$\frac{V_2 - V_1}{2} + \frac{V_2}{6} + \frac{V_2 - V_3}{1} = 0 \Rightarrow 3V_2 - 3V_1 + V_2 + 6V_2 - 6V_3 = 0$$

$$-3V_1 + 10V_2 - 6V_3 = 0$$

$$\frac{V_3}{1} + \frac{V_3 - V_2}{1} + \frac{V_3 - V_1}{4} = 0 \Rightarrow 4V_3 + 4V_3 - 4V_2 + V_3 - V_1 = 0$$

$$-V_1 - 4V_2 + 9V_3 = 0$$

$$V_1 = 12 \Rightarrow 10V_2 - 6V_3 = 36 \Rightarrow 60V_2 - 36V_3 = 216$$

$$\Rightarrow -4V_2 + 9V_3 = 12 \Rightarrow \underline{76V_2 + 36V_3 = 48}$$

$$44V_2 = 264 \Rightarrow V_2 = 6$$

$$60 - 6(V_3) = 36 \Rightarrow V_3 = 4$$

$$V_1 = 12 \text{ V} ; V_2 = 6 \text{ V} ; V_3 = 4 \text{ V} ; V_4 = 0.0 \text{ V}$$

$$i_2 = \frac{V_1 - V_2}{2} = \frac{12 - 6}{2} = 3 \text{ AMPS}$$

$$i_3 = \frac{V_2 - V_4}{6} = \frac{6}{6} = 1 \text{ AMP}$$


$$i_4 = \frac{V_1 - V_3}{4} = \frac{12 - 4}{4} = 2 \text{ AMPS}$$

$$i_5 = \frac{V_2 - V_2}{1} = \frac{4 - 6}{1} = -2 \text{ AMPS}$$

$$i_6 = \frac{V_3 - V_4}{1} = \frac{4}{1} = 4 \text{ AMPS}$$


$$i_1 = i_2 + i_4 = 3 + 2 = 5 \text{ AMPS}$$

28) a)

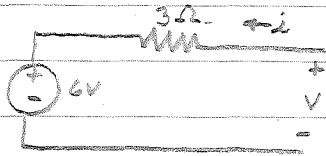


$$V = 3i + 6$$

$$i = \frac{V}{3} - 2$$

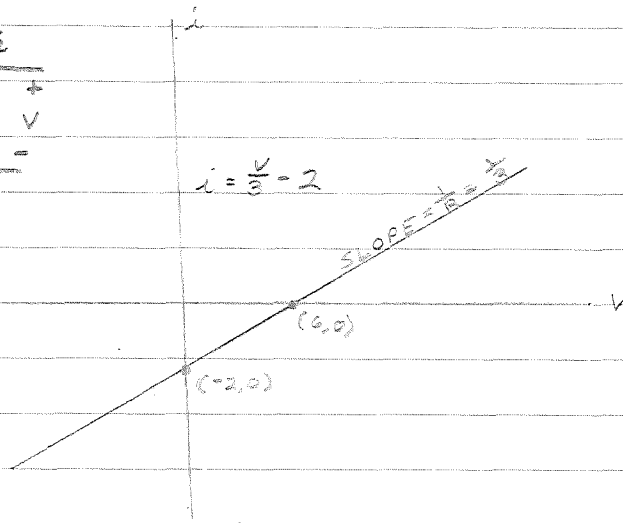


b)

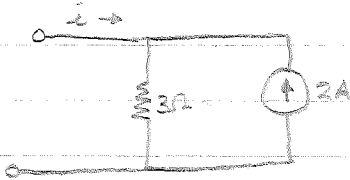


$$V = 3(i + 2)$$

$$i = \frac{V}{3} - 2$$

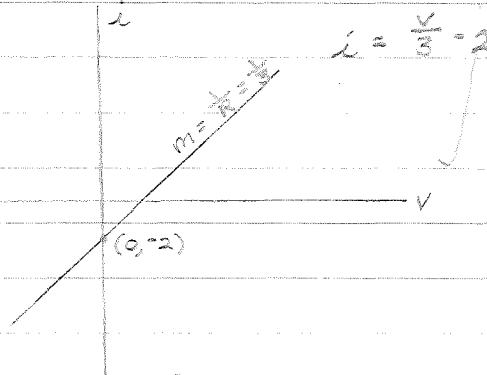

c)

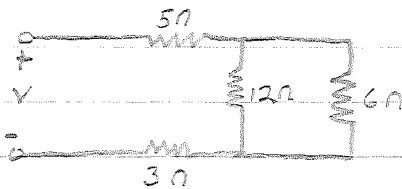




$$\frac{1}{12} + \frac{1}{6} = \frac{3}{12} = \frac{1}{4}$$

$$\therefore R_{eq} = 12$$

$$V = i \cdot 12$$

$$i = \frac{V}{12}$$

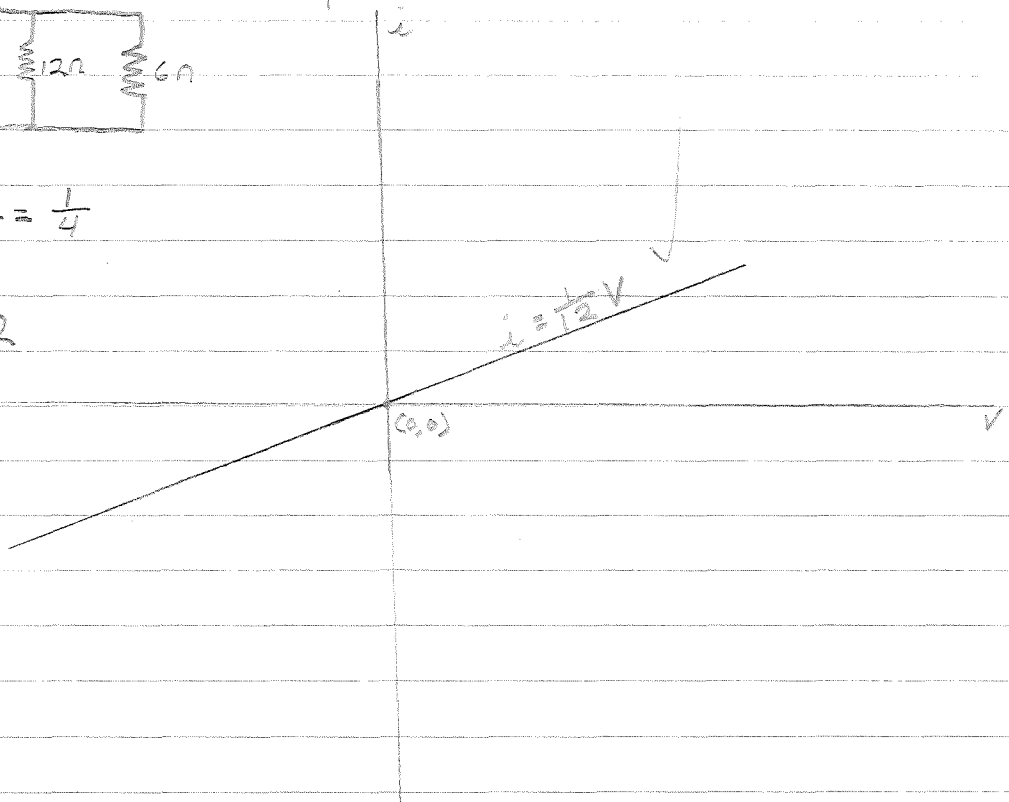

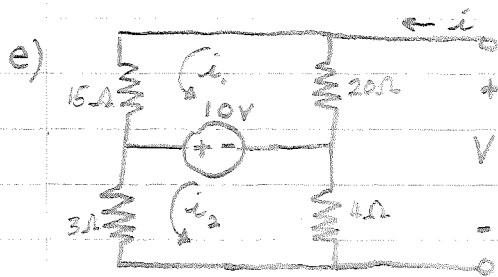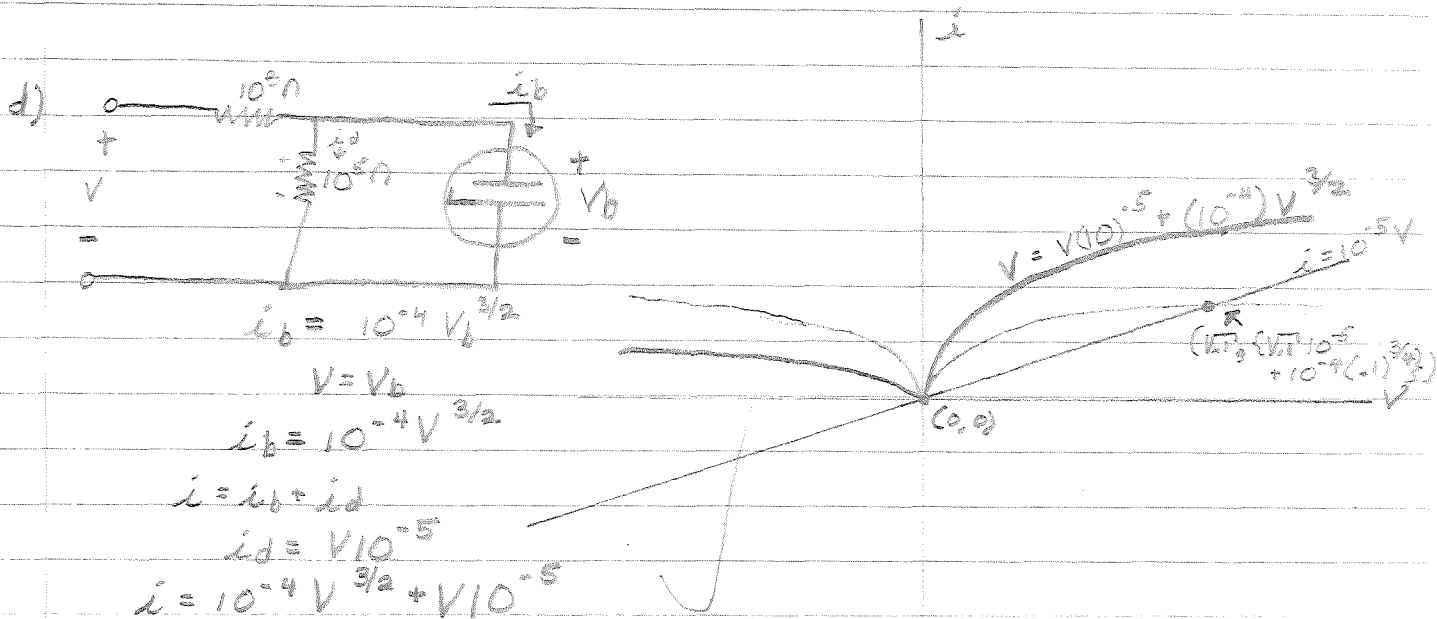

by MESH CURRENT;

$$35i_1 - 20i_2 = -10 \Rightarrow 35i_1 - 20i_2 = -10$$

$$7i_2 - 4i_1 = +10 \Rightarrow -35i_2 + 20i_1 = +50$$

$$\therefore 35i_1 - 35i_2 = -60 \Rightarrow i_1 = i_2 - \frac{12}{7}$$

$$24i_1 - 20i_2 - 4i_2 = V$$

$$24i_1 - 24i_2 + \frac{240}{7} = V$$


ALSO $i = i_1 + i_2$


$$i = 2i_2 - \frac{12}{7} \Rightarrow i_2 = \frac{i}{2} + \frac{6}{7}$$

$$\therefore V = 24i_1 - 24\left(\frac{i}{2} + \frac{6}{7}\right) + \frac{240}{7}$$

$$V = 12i + \frac{46}{7}$$
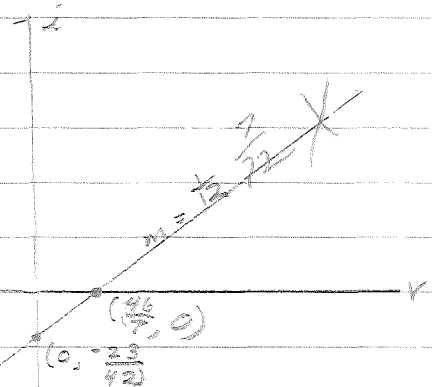
$$\Rightarrow i = \frac{V}{12} - \frac{23}{42}$$



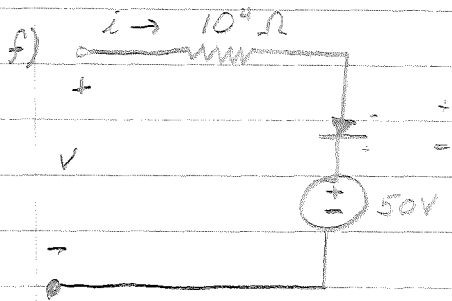

FOR $i > 0$


$$V = 10^4 i + 50$$

$$i = 10^{-4} V - 5 \times 10^{-3}$$

FOR $i = 0, V = 50$



FOR $i < 0, V = 0$

$i = 0$

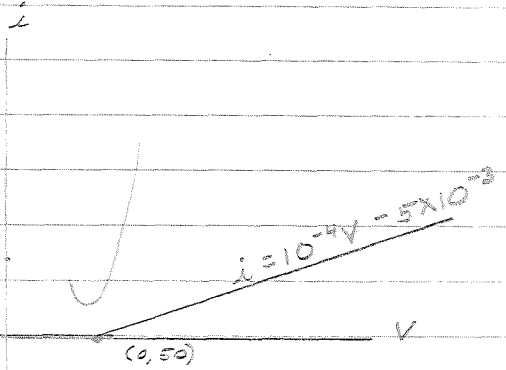


SPECIAL PROBLEM 4

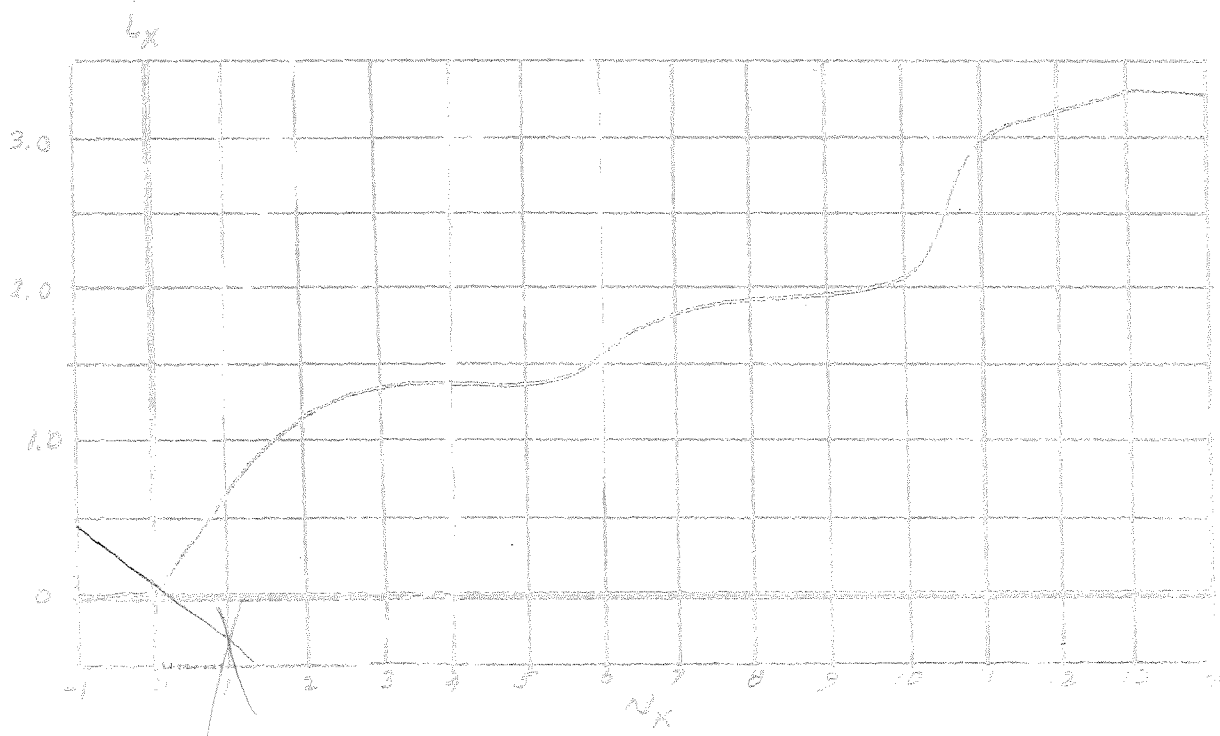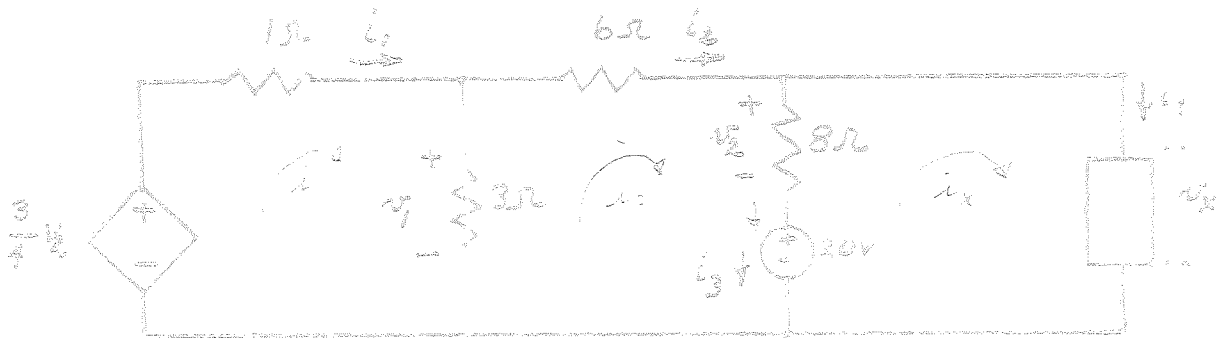ELEMENT N_6 IS A NONLINEAR DEVICE WHOSE CHARACTERISTICS ARE SKETCHED BELOW. FIND i_x , i_1 , i_2 , AND i_3 . ALSO FIND v_1 , v_2 , AND v_x . DETERMINE THE POWER ASSOCIATED WITH EACH ELEMENT IN THE CIRCUIT.



SPECIAL PROBLEM #4

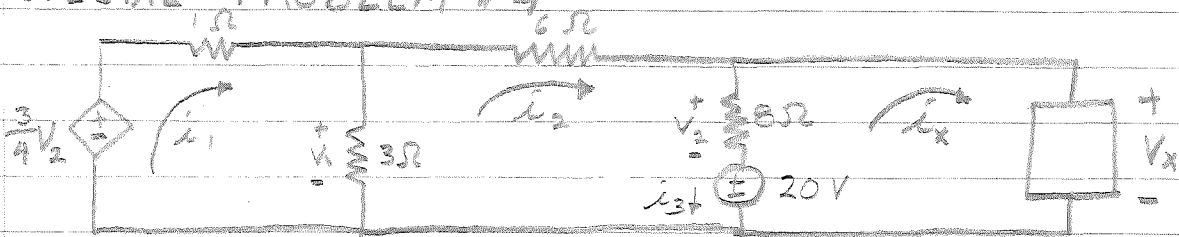

$$1) \quad 4i_1 - 3i_2 = \frac{3}{4} V_2 ; \quad V_2 = 8i_3 = 8(i_x - i_2)$$

$$\therefore 4i_1 - 3i_2 = 6(i_x - i_2) = 6i_x - 6i_2$$

$$4i_1 + 3i_2 - 6i_x = 0$$

$$2) \quad -17i_2 + 3i_1 + 8i_x = -20$$

$$3) \quad -8i_x + 8i_2 + V_x = 20$$

$$\begin{aligned} i_1 &= \frac{3}{2} i_x - \frac{3}{4} i_2 = \frac{-20}{3} + \frac{17}{3} i_2 - \frac{8}{3} i_x \\ &= \frac{18}{12} i_x - \frac{9}{12} i_2 = \frac{-20}{3} + \frac{68}{12} i_2 - \frac{32}{12} i_x \\ \Rightarrow \frac{18}{12} i_x + \frac{32}{12} i_x + \frac{20}{3} &= \frac{68}{12} i_2 + \frac{9}{12} i_2 \\ &= \frac{77}{12} i_2 = \frac{50}{12} i_x + \frac{20}{3} \\ \Rightarrow i_2 &= \frac{50}{77} i_x + \frac{80}{77} \end{aligned}$$

FROM 3:

$$i_2 = \frac{-20}{8} + \frac{V_x}{8} + i_x \left(= \frac{50}{77} i_x + \frac{80}{77} \right)$$

$$\Rightarrow i_x = \frac{50}{77} i_x = \frac{-V_x}{8} + \frac{545}{154}$$

$$\frac{22}{77} i_x = \frac{-V_x}{8} + \frac{545}{2(77)}$$

$$\Rightarrow i_x = \frac{-77V_x}{8(77)} + \frac{545(77)}{2(77)(154)}$$

$$= \frac{-77}{176} V_x + \frac{545}{44}$$

$$= -.437 V_x + .124$$

FROM GRAPH:

$$i_x \approx .1 ; \quad V_x \approx .1$$

$$a) V_x = 20 - V_2 = 0$$

$$V_2 = (1 - 20) = 19.9 \text{ V}$$

$$b) V_2 = 8 i_3 \Rightarrow i_3 = 2.49 \text{ AMPS}$$

$$c) i_3 + i_x = i_2$$

$$(2.49 + .1) = i_2 = 2.59 \text{ AMPS}$$

$$d) 4i_1 - 3i_2 - \frac{3}{4}V_2 = 0$$

$$4i_1 = 2.21 + 7.78 = 9.99$$

$$i_1 = 2.49$$

$$e) V_1 = 3(i_1 - i_2)$$

$$= 3(2.49 - 2.59)$$

$$= -.30 \text{ VOLTS}$$

$$V_1 = -.30 \text{ VOLTS}$$

$$V_2 = 2.49 \text{ VOLTS}$$

$$V_x = .1 \text{ VOLTS}$$



$$i_1 = 2.49 \text{ AMPS}$$

$$i_2 = 2.59 \text{ AMPS}$$

$$i_x = .1 \text{ AMP}$$

Power 7
0


Pg. 143

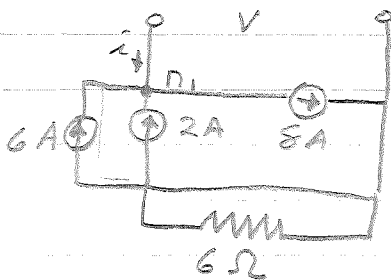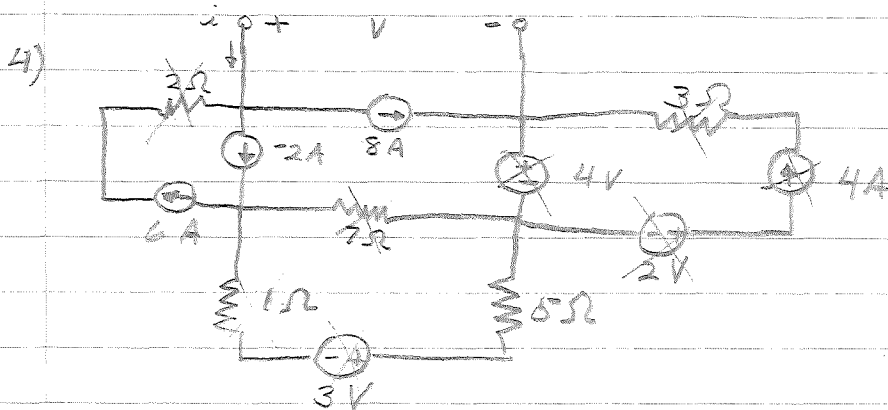

$$\sum i_n = 6 + 2 + i - 8 = 0 \Rightarrow i = 0 \text{ FOR ALL } V$$

Pg 146

9) CIRCUIT REDUCES TO:

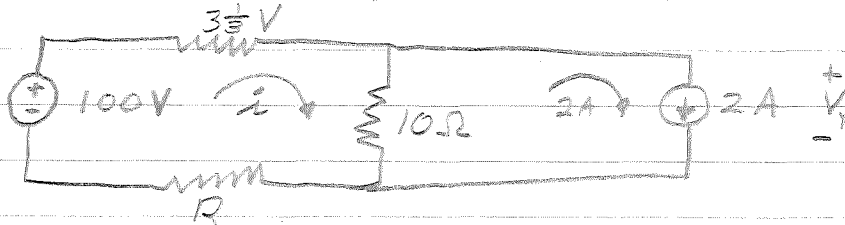

$$i \left(R + \frac{10}{3} + 10 \right) - 20 = 100 \Rightarrow i \left(R + \frac{40}{3} \right) = 120$$

$$V_Y + 10(2 - i) = 0 \Rightarrow V_Y - 10i = -20$$

SOLVE FOR i IN BOTH EQUATIONS:

$$i = \frac{120}{R + \frac{40}{3}} = \frac{360}{3R + 40}$$

$$i = \frac{V_Y + 20}{10}$$

$$\therefore \frac{V_Y + 20}{10} = \frac{360}{3R + 40} \Rightarrow (V_Y + 20)(3R + 40) = 3600$$

$$\Rightarrow 3V_Y R + 40V_Y + 60R + 800 = 3600$$

$$\Rightarrow R(3V_Y + 60) = 40V_Y + 2800$$

$$\Rightarrow R = \frac{2800 - 40V_Y}{3V_Y + 60}$$

$$\Rightarrow \frac{dR}{dV_Y} = \frac{-40}{3V_Y + 60} - \frac{3(2800 - 40V_Y)}{(3V_Y + 60)^2}$$

$$\Rightarrow \frac{1600 - 8400 + 120V_Y}{(3V_Y + 60)^2} = 0$$

$$\Rightarrow 120V_Y = 6800 \Rightarrow V_Y = \frac{170}{3}$$


$$\therefore R = \frac{2800 - 40\left(\frac{170}{3}\right)}{170 + 60} = \frac{533}{230} = 2.32 \Omega$$

$$\left(\frac{d^2R}{dV_Y^2} \right)_{V_Y = \frac{170}{3}} < 0 \Rightarrow \text{MAXIMUM}$$

$$i = \frac{120}{15.6} = 7.67$$

$$P = i^2 R = \cancel{395} 136 \text{ WATTS}$$

4-12)

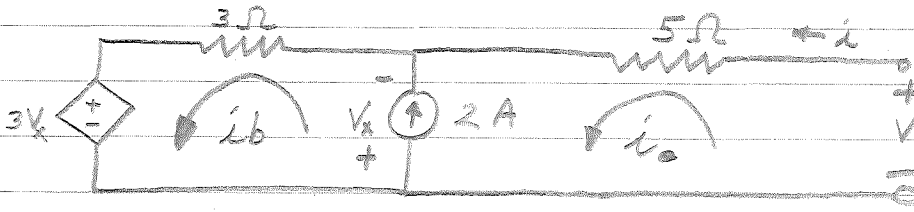

FOR V_{oc}

$$i_b = 2$$

$$3V_x + V_x + 3i_b = 0 \Rightarrow 4V_x = -6$$

$$-V_{oc} + 6 + 3V_x = 0 \Rightarrow V_{oc} = -(6 + 3V_x) = -(6 + 3\left(\frac{-6}{4}\right)) = \frac{9}{2}$$

FOR i_{sc}

$$5i_{sc} = V_x$$

$$V_x + 3i_b + 3V_x = 0 \Rightarrow 4V_x = -3i_b$$


$$i_b - i_{sc} = 2 \Rightarrow 4V_x = -3(2 + i_{sc})$$

$$= -(6 + i_{sc}) = 20i_{sc} \Rightarrow -6 = 21i_{sc} \Rightarrow i_{sc} = \frac{-6}{21} = -\frac{2}{7}$$

$$\Rightarrow I_{eq} = \frac{2}{7} \text{ AMPS}$$

$$V_{eq} = -\frac{3}{2} \text{ VOLTS}$$

$$R_{eq} = \frac{21}{4} \Omega$$

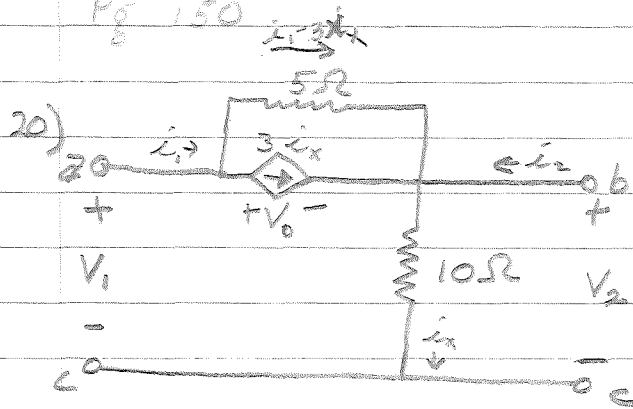

$$10i_x = V_2$$

$$V_0 + 10i_x = V_1$$

$$5(i_1 - 3i_x) + 10i_x = V_1$$


$$5i_1 - 5i_x = V_1$$

$$i_1 - 3i_x + i_2 + 3i_x - i_x = 0$$

$$i_1 + i_2 = i_x$$

$$V_1 = 5i_1 - 5(i_1 + i_2) = -5i_2$$

$$V_2 = 10i_x = 10i_1 + 10i_2$$

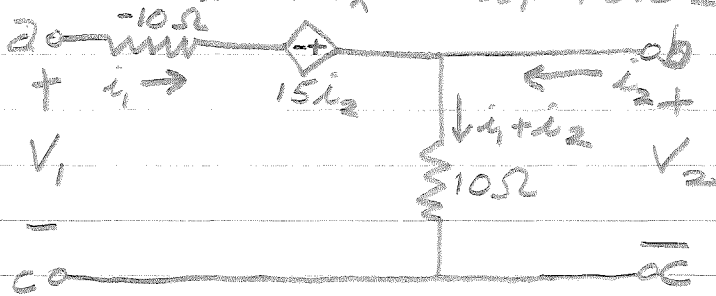

$$V_1 = -10i_1 - 15i_2 + 10i_1 + 10i_2 = -5i_2$$

$$V_2 = 10i_1 + 10i_2$$


\therefore THE TWO CIRCUITS ARE EQUIVALENT

ROSE POLYTECHNIC INSTITUTE

EE 201

Special Problem 6

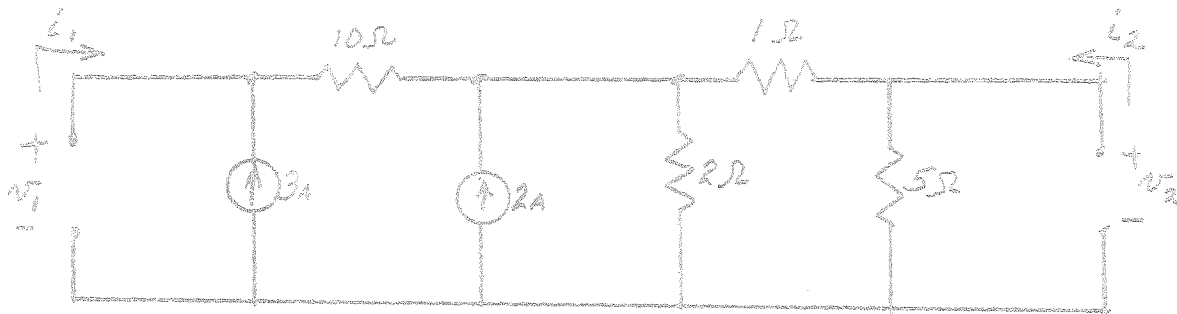Determine the equivalent three terminal network (in both T and π forms) for the following circuit.




12) a) $C = \frac{q}{V}$

$$i = C \frac{dV}{dt}$$

$$V = 2t - 2t\mu(t-1) + 2\mu(t-1) - 2\mu(t-2) + 4\mu(t-2) - 4\mu(t-3) \\ + (-2t+10)\mu(t-3) - (-2t+10)\mu(t-4)$$

$$V = 2t + (2-2t)\mu(t-1) + 2\mu(t-2) + (-2t+6)\mu(t-3) + (2t-10)\mu(t-4)$$
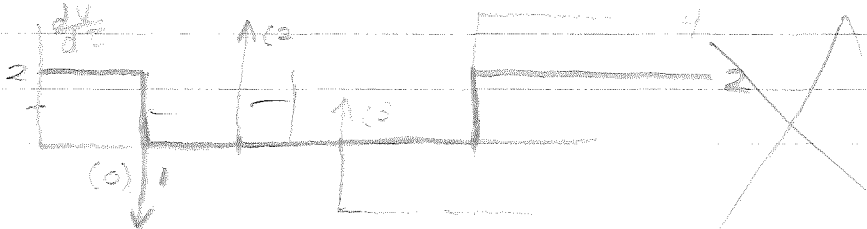
$$\frac{dV}{dt} = 2 - 2\mu(t-1) + (2-2t)\delta(t-1) + 2\delta(t-2) - 2\mu(t-3) + (2t+6)\delta(t-3) \\ + 2\mu(t-4) + (2t-10)\delta(t-4)$$



AT $t > 4$; $\frac{dV}{dt} = 2 \frac{V}{SEC}$

$$i = C \frac{dV}{dt} = (2F)(2 \frac{V}{SEC}) = 4 \text{ AMPS}$$

$$b) V = \frac{1}{C} \int_0^4 i dt \\ = \frac{1}{2} [2+2-2+1-3] = 0$$

c) $V = \frac{L}{R} \frac{di}{dt}$


$$\frac{di}{dt} = 2 \frac{AMP}{SEC} \text{ AT } t > 4 \quad (\text{FROM PART 2})$$

$$\therefore V = 2 \text{ VOLTS}$$


d) $i = 0$ (FROM MATH IN PART b)

sketches?

$$5) a) f(t) = 3U(t-1) \\ = 3Ut - 3U$$

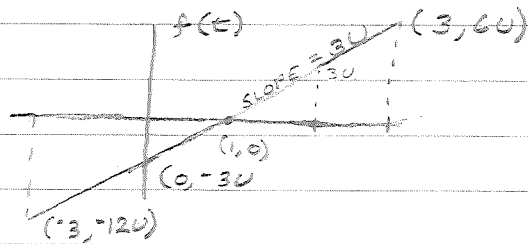

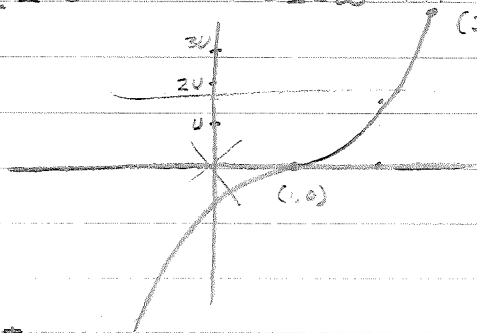
$$\cancel{A} \#(t) = \int_{-\infty}^t (3Ut - 3U) dt \\ = \left[\frac{3}{2} Ut^2 - 3Ut \right]_{-\infty}^t \text{ - MAY NOT BE EVALUATED IN THIS MANNER}$$



$$b) \#(t) = \int_{-\infty}^t (3Ut - 3U) dt \\ = \int_{-\infty}^{-3} (3Ut - 3U) dt + \int_{-3}^t (3Ut - 3U) dt$$

IF $\int_{-\infty}^{-3} (3Ut - 3U) dt$ IS FINITE

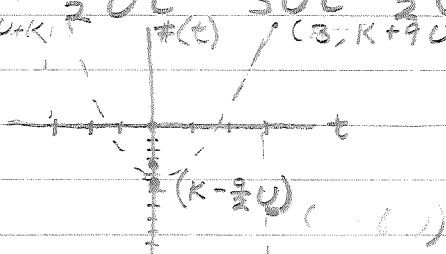
$$\begin{aligned} \#(t) &= \int_{-3}^t (3Ut - 3U) dt + K \\ &= \left[\frac{3}{2} Ut^2 - 3Ut \right]_{-3}^t + K \\ &= \frac{3}{2} Ut^2 - 3Ut - \frac{27}{2} U + 9U + K \\ &= \frac{3}{2} Ut^2 - 3Ut - \frac{9}{2} U + K \end{aligned}$$




$$c) g(t) = 3U$$



$$d) f(-t) = -3Ut - 3U$$

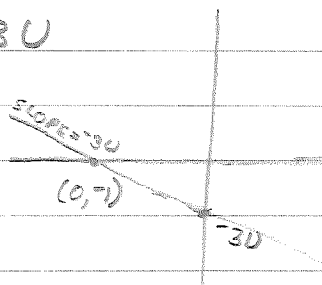

$$3) \quad i_s = -8 + 13u(t)$$

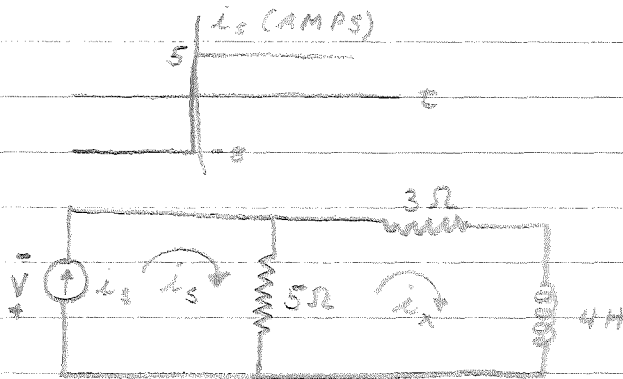

$$V + 5i_s - 5i_x = 0$$

$$8i_x - 5i_s + 4 \frac{di_x}{dt} = 0$$

FOR $t > 0$; $i_s = 5$

$$8i_x + 4 \frac{di_x}{dt} = 25$$

$$8\bar{i}_x + 4s\bar{i} - i_0 = \frac{25}{s} \quad (i_0 = i \text{ at } t=0)$$

$$\bar{i}_x 4(s+1) = \frac{25}{s} + i_0$$

$$\bar{i}_x = \frac{\frac{25}{s}}{4(s+1)s} + \frac{i_0}{4(s+1)}$$

$$= \frac{25}{4s} - \frac{25}{4(s+1)} + \frac{i_0}{4(s+1)}$$

$$i_x = \frac{25}{4} + e^{\left(\frac{i_0 - 25}{4}\right)t} e^{-\left(\frac{s+1}{4}\right)t}$$

$$P_L = V_L i_x = 4 \left(\frac{i_0 - 25}{4}\right) e^{-\left(\frac{s+1}{4}\right)t}$$

$$P_{3\Omega} = 3i_x^2 = 3 \left(\frac{25}{4} + e^{\frac{25-i_0}{4}t}\right)^2$$

$$P_{5\Omega} = 5(i_x - i_s)^2 = 5 \left(-\frac{75}{4} + e^{\frac{25-i_0}{4}t}\right)^2$$

$$P(t) = (25 - i_0) e^{\frac{25-i_0}{4}t} + 3 \left(\frac{25}{4} + e^{\frac{25-i_0}{4}t}\right)^2 + 5 \left(-\frac{75}{4} + e^{\frac{25-i_0}{4}t}\right)^2$$

$t > 0$

Pg 8

$$\begin{aligned}
 \text{X-1) a) } F &= \frac{q_1 q_2}{4\pi \epsilon_0 r^2} \\
 &= \frac{(10^{-13})(1.06 \times 10^{-19})(9 \times 10^9)}{10^{-12}} \\
 &=
 \end{aligned}$$

$$\begin{aligned}
 \text{b) } E &= 3 \times 10^6 \frac{\text{V}}{\text{m}} \\
 F &= Eq = (3 \times 10^6)(1.06 \times 10^{-19}) \\
 &=
 \end{aligned}$$

$$\begin{aligned}
 \text{c) } E &= \frac{Q}{A \epsilon_0} ; F = eQ \\
 \therefore F &= \frac{(10^{-6})(1.06 \times 10^{-19})}{(8.85 \times 10^{-12})(.1)} \\
 &=
 \end{aligned}$$

X-2)



$$\begin{aligned}
 Q &= 10^{-6} \text{ C} \quad \text{a) } E = \frac{Q}{\epsilon_0 A} \Rightarrow F = \frac{q_e Q}{\epsilon_0 A} = ma \\
 a_e &= \frac{q_e Q}{\epsilon_0 A m_e}
 \end{aligned}$$

$$x = \frac{1}{2} a t^2 ; v = at \Rightarrow x = \frac{v^2}{2a}$$

$$\begin{aligned}
 \therefore x &= \frac{v^2 \epsilon_0 A m_e}{2 q_e Q} \\
 &= \frac{(5 \times 10^7)^2 (8.85 \times 10^{-12})(10^{-2})(9.11 \times 10^{-31})}{2 (1.06 \times 10^{-19})(10^{-6})} \\
 &=
 \end{aligned}$$

$$\text{b) } K = 10^{-15} \text{ J} = \frac{1}{2} m_e v^2$$

$$\begin{aligned}
 v &= \sqrt{\frac{2K}{m_e}} \\
 x &= \frac{v^2 \epsilon_0 A m_e}{2 q_e Q} \\
 &= \frac{2K \epsilon_0 A m_e}{2 m_e q_e Q} \\
 &= \frac{K \epsilon_0 A}{q_e Q} = \frac{(10^{-15})(8.85 \times 10^{-12})(10^{-2})}{(1.06 \times 10^{-19})(10^{-6})} \\
 &=
 \end{aligned}$$

$$\text{c) } t = 10^{-12}$$

$$\begin{aligned}
 a_e &= \frac{q_e Q}{\epsilon_0 A m_e} \\
 x &= \frac{1}{2} a t^2 ; v = at \Rightarrow a = \frac{2x}{t^2}
 \end{aligned}$$

$$\begin{aligned}
 \frac{2x}{t^2} &= \frac{q_e Q}{\epsilon_0 A m_e} \\
 x &= \frac{q_e Q t^2}{2 \epsilon_0 A m_e} \\
 &= \frac{(1.06 \times 10^{-19})(10^{-6})(10^{-24})}{2 (8.85 \times 10^{-12})(10^{-2})(9.11 \times 10^{-31})} \\
 &=
 \end{aligned}$$

$$x1-6) a) q = .02 \cos(100t - 1.5\pi)$$

$$\frac{dq}{dt} = i = -2.0 \sin(100t - 1.5\pi)$$

at $t=0$

$$i = -2 \sin(-1.5\pi) = -2.0 \text{ AMPS}$$

$$b) (4 \times 10^{20} e^{-.2t} \text{ elec}) \left(\frac{1.6 \times 10^{-19} \text{ coul}}{\text{elec}} \right)$$

$$q = 64 e^{-.2t}$$

$$\frac{dq}{dt} = i = -12.8 \text{ AMPS at } t=0$$

$$c) V = 10t - 3 \quad ; \quad W = Vi$$

$$i = \frac{4}{10t - 3}$$

$$\text{at } t=0, i = -1.33 \text{ AMPS}$$

$$x1-7) P (=W) = Vi$$

$$a) = 7.79$$

$$b) = 8.19$$

$$c) 7.59$$

$$x1-8) a) U_e = 5.93 \times 10^{-5} \sqrt{V_0}$$

$$V = \frac{U_e^2}{(5.93 \times 10^{-5})^2}$$

$$= \frac{(1.5 \times 10^6)^2}{(5.93 \times 10^{-5})^2}$$

$$= 640 \text{ VOLTS}$$

Pg. 67

$$\begin{aligned} \text{X3.2)} \quad 40 - 15 + V_3 - V_2 &= 0 \Rightarrow V_3 - V_2 = -25 \\ 60 - V_2 - V_7 &= 0 \Rightarrow V_2 + V_7 = 60 \\ -15 - 12 + V_6 &= 0 \Rightarrow V_6 = 27 \text{ V} \\ 27 - 40 - V_7 &= 0 \Rightarrow V_7 = -13 \text{ V} \\ 60 + 13 + V_2 &= 0 \Rightarrow V_2 = -73 \text{ V} \end{aligned}$$


$$\text{X3.3)} \quad i_3 = 1 \text{ A}$$

$$i_1 - 2 + 8 + 1 = 0 \Rightarrow i_1 = 7 \text{ A}$$

$$i_2 = -7$$

Pg. 79
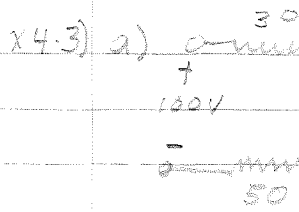
$$\begin{aligned} \text{X3.7)} \quad -11 + .2i + V_s &= 0 \\ -V_s + .1(5 - i) + 12 &= 0 \\ V_s = 11 - .2i &= -12 + .1(i - 5) \\ 11 - .2i &= -12 + .1i - .5 \\ 23.5 &= .3i \Rightarrow i = 6 \end{aligned}$$




$$\frac{1}{30} + \frac{1}{20} = \frac{1}{R}$$

$$\frac{5}{60} = \frac{1}{R} \Rightarrow R = 12$$

$$R_{\text{eq}} = 92$$
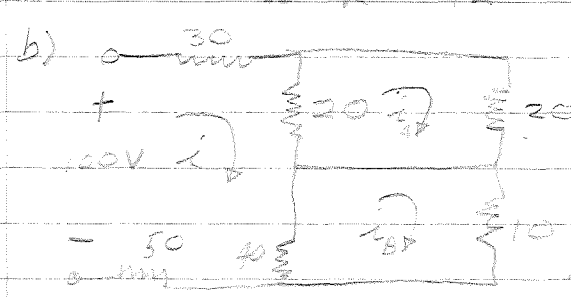
$$i = \frac{V}{R} = \frac{100}{92} = 1.09 \text{ AMPS}$$




$$100 = 140i - 20i_A - 40i_B$$

$$40i_A = 20i$$



$$50i_B = 40i$$


$$100 = 140i - 10i - 80i$$

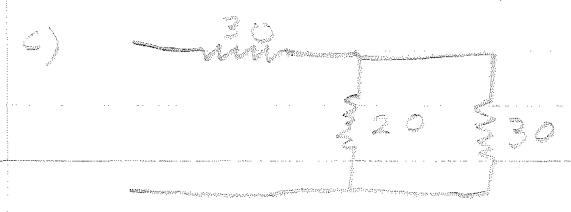
$$50i = 100 \Rightarrow i = 2 \text{ AMPS}$$



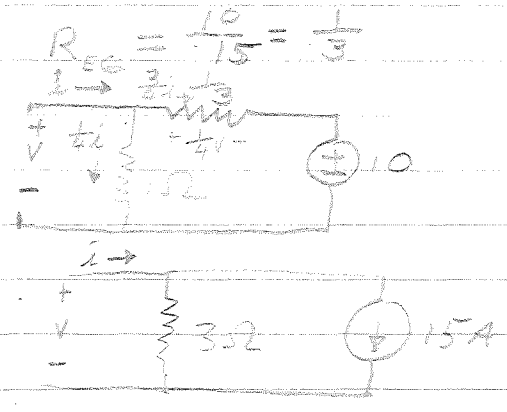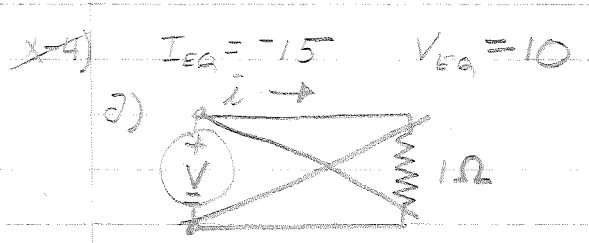
$$i = \frac{V}{R} = \frac{100}{42} = 2.38 \text{ A}$$



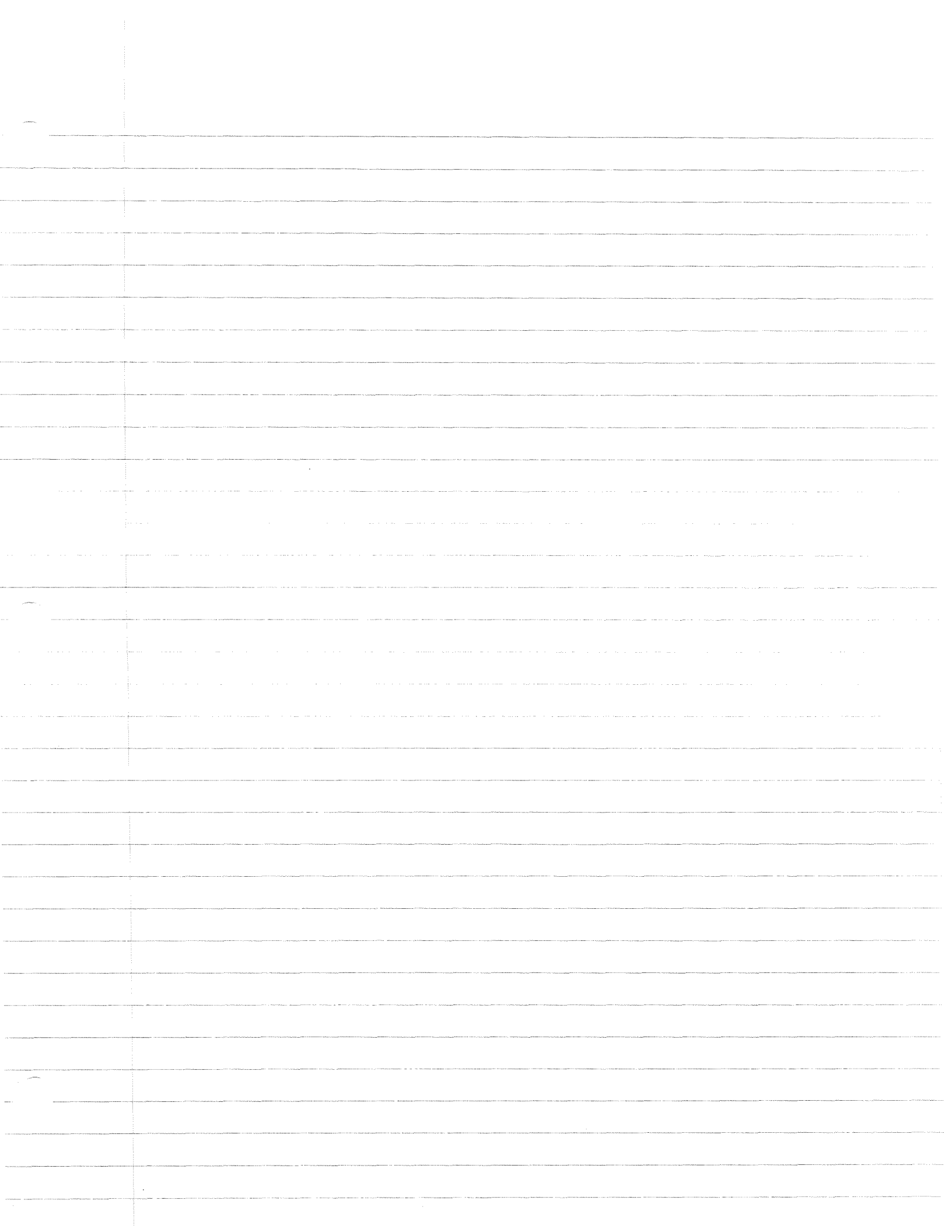

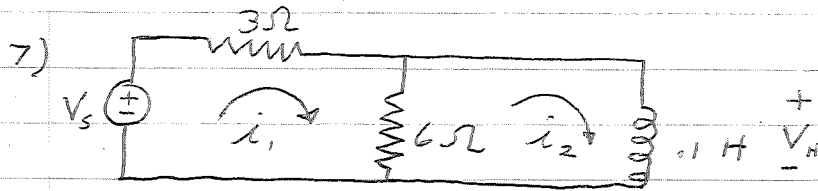

$$V_s = 24 u(t)$$

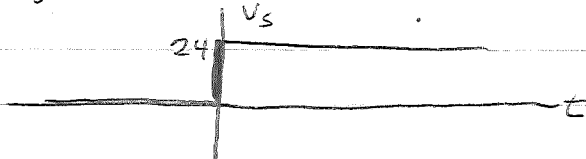

$$-V_s + 9i_1 - 6i_2 = 0 \Rightarrow i_1 = \frac{6i_2 + V_s}{9}$$

$$6i_2 + L \frac{di_2}{dt} = 6i_1 \Rightarrow 6i_2 + 0.1 \frac{di_2}{dt} = \frac{12i_2 + 2V_s}{3}$$

AT $t > 0$


$$2i_2 + 0.1 \frac{di_2}{dt} - 16 = 0$$

$$2\bar{i} + 0.15\bar{i} = \frac{16}{5}$$

$$\bar{i} = \frac{16}{5(5+2)} = \frac{16}{.015(5+200)} = \frac{1600}{5(5+200)}$$

$$= \frac{8}{5} - \frac{8}{5+200}$$

$$i_2 = 8 - 8e^{-200t}$$

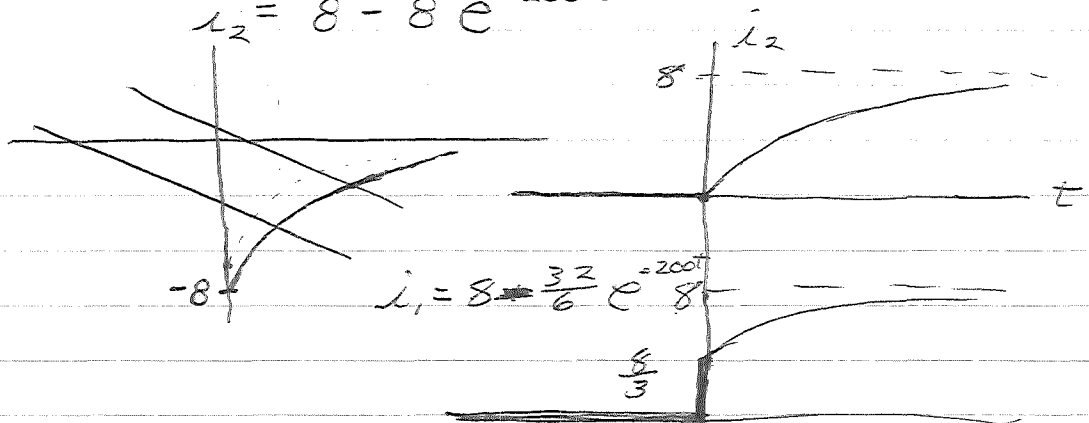


$$\textcircled{0} E = Pt$$

$$E_{3\Omega} \approx \left(\frac{8}{3}\right)^2 \cdot 3(2.2) = 47 \text{ J}$$

$$E_{6\Omega} \approx \left(\frac{8}{3}\right)^2 \cdot 6(2.2) = 94 \text{ J}$$

$$E_{V_s} \approx V_s i_1 \approx (24)\left(\frac{8}{3}\right) = 64 \text{ J}$$

$$E_{IND} = V_H i_2 \approx 0$$

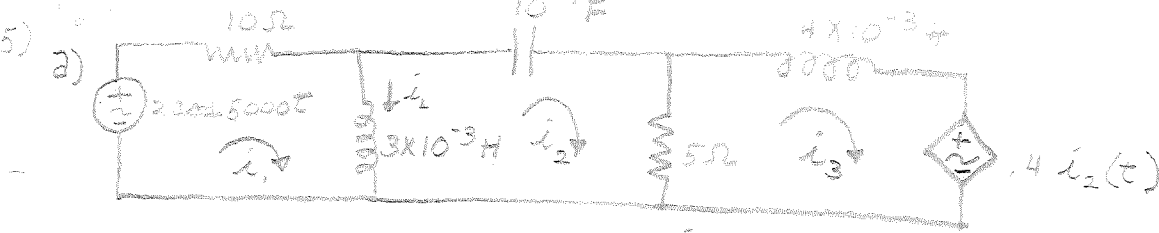


$$-2 \cos 5000t + 10i_1 + 3 \times 10^{-3} \frac{di_1}{dt} = 0$$

$$-3 \times 10^{-3} \frac{di_1}{dt} + 10^4 \int i_2(t) dt + 5i_2 - 5i_3 = 0$$

$$5i_3 - 5i_2 + 4 \times 10^{-3} \frac{di_3}{dt} + 4i_2 = 0$$

$$i_1 = i_1 - i_2$$

$$\frac{-i}{5} = -2j\Omega$$

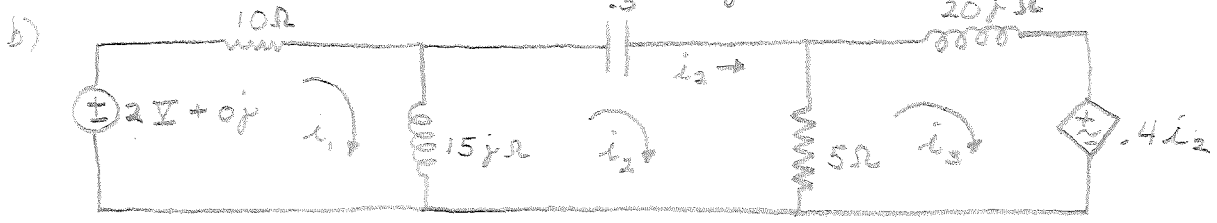

$$2 = 10i_1 + 15ji_1 - 15ji_2$$

$$15ji_2 - 15ji_1 - 2ji_2 + 5i_2 - 5i_3 = 0$$

$$5i_3 - 5i_2 + 20ji_3 + 4i_2 = 0$$

TABLE OF LAPLACE TRANSFORMS

$f(t)$	$F(s)$
$f(t)$	$F(s) = \int_0^{\infty} e^{-st} f(t) dt$
$A f_1(t) + B f_2(t)$	$A F_1(s) + B F_2(s)$
unit impulse $\delta(t)$	1
unit step $u(t)$	$1/s$
A	A/s
t	$1/s^2$
t^n	$n! / s^{n+1}$
$d/dt [f(t)]$	$sF(s) - f(0+)$
$d^2/dt^2 [f(t)]$	$s^2F(s) - sf(0+) - f'(0+)$
$d^n/dt^n [f(t)]$	$s^n F(s) - s^{n-1} f(0+) - s^{n-2} f'(0+) - \dots - f^{(n-1)}(0+)$
$\int_0^t f(t) dt$	$[F(s) - \int_0^a f(t) dt] / s$
$f(t-a) [f(t)=0, t < a]$	$e^{-as} F(s)$
$e^{-at} f(t)$	$F(s+a)$
$f(t/a)$	$aF(as)$
$\lim_{t \rightarrow 0} [f(t)]$	$\lim_{s \rightarrow \infty} [sF(s)]$
$\lim_{t \rightarrow \infty} [f(t)]$	$\lim_{s \rightarrow 0} [sF(s)]$
e^{-at}	$1 / (s+a)$
$t e^{-at}$	$1 / (s+a)^2$
$t^{n-1} e^{-at} / (n-1)!$	$1 / (s+a)^n$

(2)

$$\sin wt$$

$$\cos wt$$

$$e^{-at} \sin wt$$

$$e^{-at} \cos wt$$

$$w / (a^2 + w^2)$$

$$a / (a^2 + w^2)$$

$$w / [(a+aw)^2 + w^2]$$

$$(a+aw) / [(a+aw)^2 + w^2]$$

$$\frac{1}{r\sqrt{1-c^2}} e^{-ct/T} \sin(\sqrt{1-c^2} \frac{t}{T})$$

$0 < c < 1$

$$\frac{1}{T^2 a^2 + 2cT a + 1}$$

$$1 + \frac{a+ct/T \sin(\sqrt{1-c^2} \frac{t}{T})}{\sqrt{1-c^2}}$$

$$\frac{1}{T^2 a^2 + 2cT a + 1}$$

$$\phi = \tan^{-1} [\sqrt{1-c^2} / -1]$$

$$0 < c < 1$$

$$A \cos (wt + \phi)$$

$$A = \sqrt{r^2 + (1/w)^2}$$

$$\phi = \tan^{-1} [-1/wr]$$

$$\frac{T a + 1}{T^2 a^2 + w^2}$$

$$\frac{82}{100} = 82\%$$

ROSE POLYTECHNIC INSTITUTE

EE 201
Winter 1970
NEM

EXAM 1


BOB MARKS

Name

I.D. #8069

(20 pts) 1. Fill in the following table by placing an "X" in the appropriate column for each combination of elements.

ELEMENTS		SERIES	PARALLEL	NEITHER
R ₁	R ₂			X
V ₀	R ₃	X ✓		
R ₅	R ₈			X
R ₄	R ₈		X	X
R ₆	R ₈		X	X
R ₇	R ₉			X
R ₉	R ₁₀			X
R ₉	R ₁₁		X	
R ₁₀	R ₇	X		

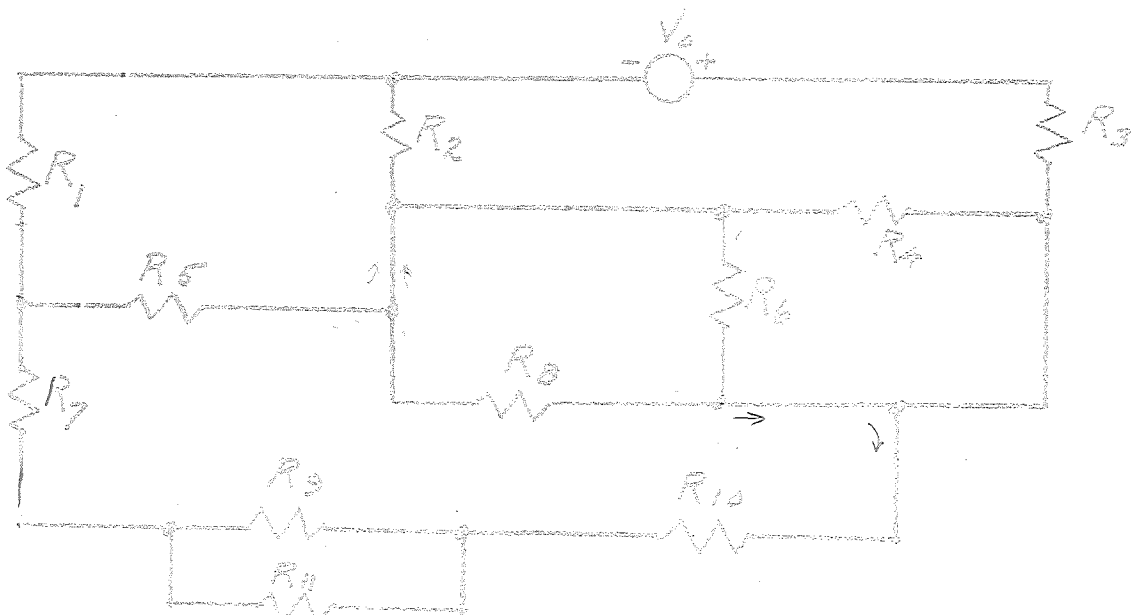


(46 pts)

2. Suppose you are the manager of a baseball team where all the players are electrons. The score is tied when your leadoff batter reps a single into short left (magnetic) field. The next batter sacrificed, moving the runner to second base. You are trying to decide whether to call for a steal or a hit-and-run. From previous observations you know that the catcher can throw to third base in 17 ns. (1 ns = 10^{-9} sec.) If the voltage at third base is +300 v with respect to second base

DISTANCE BETWEEN BASES 90mm

Is it wise to call for a steal?

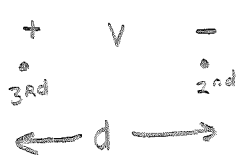

$$d = 90 \times 10^{-3} \text{ m}$$

$$V = 300 \text{ V}$$

$$V = EL$$

$$E = \frac{300 \times 10^2}{9.00 \times 10^{-3}} = \frac{1}{3} \times 10^5 = 3.33 \times 10^4$$

$$F = Eq = (3.33 \times 10^4)(1.6 \times 10^{-19}) = 3.53 \times 10^{-15} \text{ Nt.}$$

$$F = ma$$

$$a = \frac{3.53 \times 10^{-15}}{9.11 \times 10^{-31}} = 3.87 \times 10^{16} \frac{\text{m}}{\text{SEC}^2}$$

$$x = \frac{1}{2} at^2$$

$$t = \sqrt{\frac{2x}{a}} = \left(\frac{2(90 \times 10^{-2})}{3.87 \times 10^{16}} \right)^{\frac{1}{2}} = \left(\frac{1.8 \times 10^{-1}}{3.87} \right)^{\frac{1}{2}} \times 10^{-8}$$

$$= 1.444 \times 10^{-8}$$

$$t = 6.82 \times 10^{-8} \text{ SEC}$$


NO

$\frac{1.8 \times 10^{-1}}{3.87}$

EN 20 M 1 (2, 1)

(40 pts) 3. Find i_x and the power delivered or absorbed (state which) by the 20 volt source.

-1/0

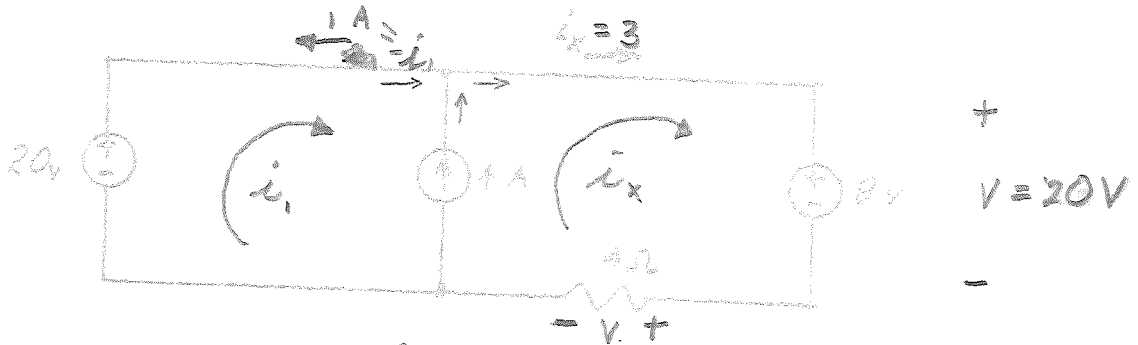

$$i_1 + 4 = i_x$$

~~$$20 + 8 + 4i_x = 0$$~~

$$4i_x = (20 - 8)$$

$$i_x = 3 \text{ AMPS} \rightarrow i_1 = -1 \text{ AMP}$$

$$P_{20V} = (1)(20) = +20 \text{ WATTS}$$

$$P_{4A} = -iV = -(20)(4) = -80 \text{ WATTS}$$

$$P_{8V} = (8)(3) = +24 \text{ WATTS}$$


$$P_{4\Omega} = i^2 R = (3)^2(4) = +36 \text{ WATTS}$$

(*) INDICATES DELIVERED) } Wrong
 (*) INDICATES ABSORBED) } Conclusions

-10

EE 201, EXAM 1 (cont'd)

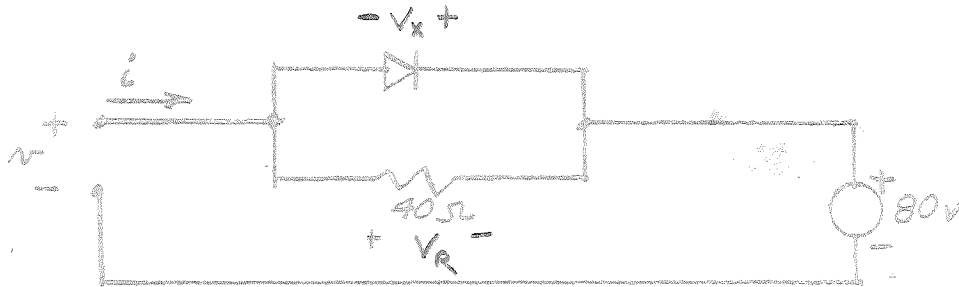(40 pts) 4. Sketch and label the $i-v$ curve for the following circuit. The diode is ideal.



$i < 0 \rightarrow$ DIODE IS OPEN CIRCUIT

$$V = V_1 + 40i$$


$$= 80 + 40i$$

$$i = \frac{V}{40} - 2$$

$i > 0 \rightarrow V_x = 0 \rightarrow$ DIODE IS SHORT CIRCUIT

$$V_R = 0$$

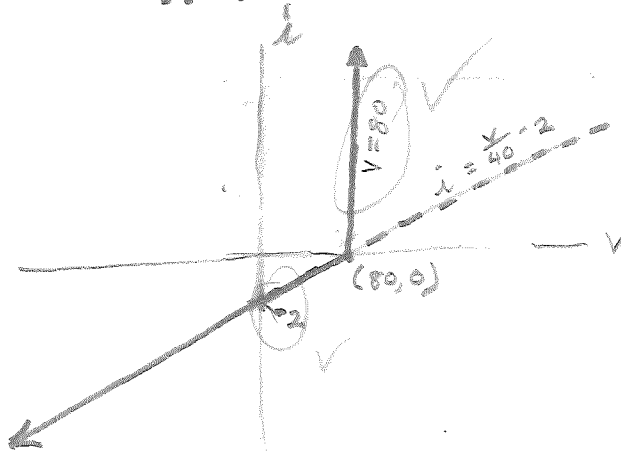
$$\therefore V = 80 \text{ V} \rightarrow i = 0$$



EE 201, EXAM 1 (cont'd)

(20 pts) 5. What settings on a type 503 oscilloscope should be used to display 3 cycles of normal line voltage (nominal value 115v, RMS) ?

115 V A.C.

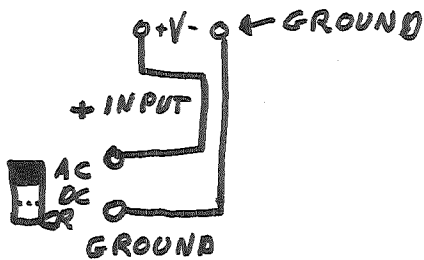

SENSITIVITY: ~~20~~ $\frac{\text{VOLTS}}{\text{CM}}$

HORIZONTAL DISPLAY: NORMAL

TIME SWEEP: 5 m SEC *cm* ✓

SLOPE = + (~~+~~) (ARBITRARY)

COUPLING - AC

SOURCE - ~~LINE~~ LINE

LEVEL - AUTO

$$\frac{184}{200} = 92.7\%$$


ROSE POLYTECHNIC INSTITUTE

EE 201
Winter 1970
NEM

EXAM 2

BOB MARKS
Name

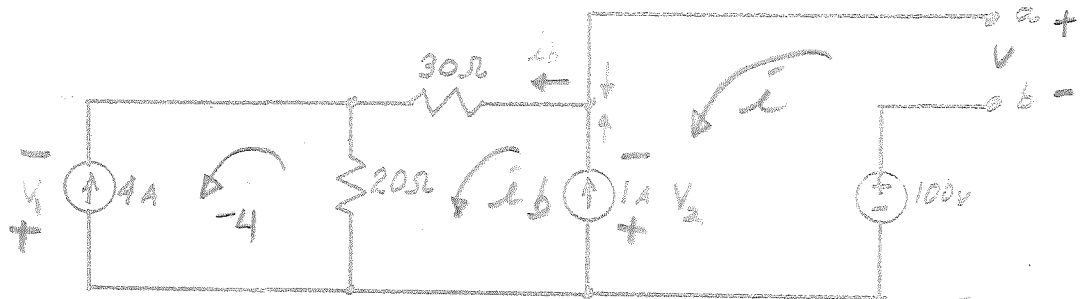- ✓ (60 pts) 1. Find either the Thevenin or the Norton equivalent circuit, viewed from terminals a & b.



$$-V_1 + 20(-4 - i_b) = 0 \Rightarrow V_1 = 20(4 + i_b)$$

$$V_1 = 80 + 20i_b$$


$$50i_b + 4(20) + V_2 = 0 \Rightarrow V_2 = -50i_b - 80$$

$$+V_2 + 100 + V = 0 \Rightarrow V = -V_2 - 100$$


$$V = 50i_b - 20$$

$$i + 1 = i_b \Rightarrow V = 50(i + 1) - 20$$

$$V = 50i + 30$$

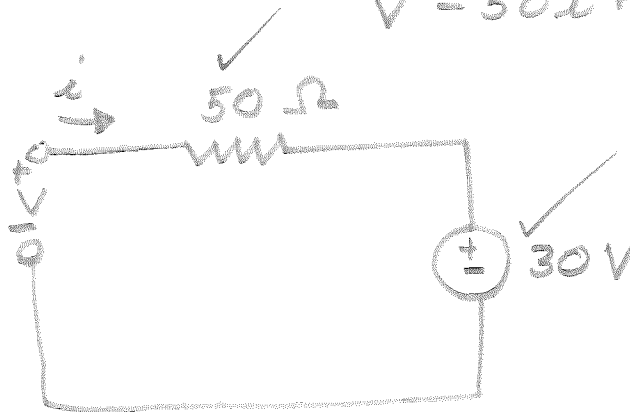

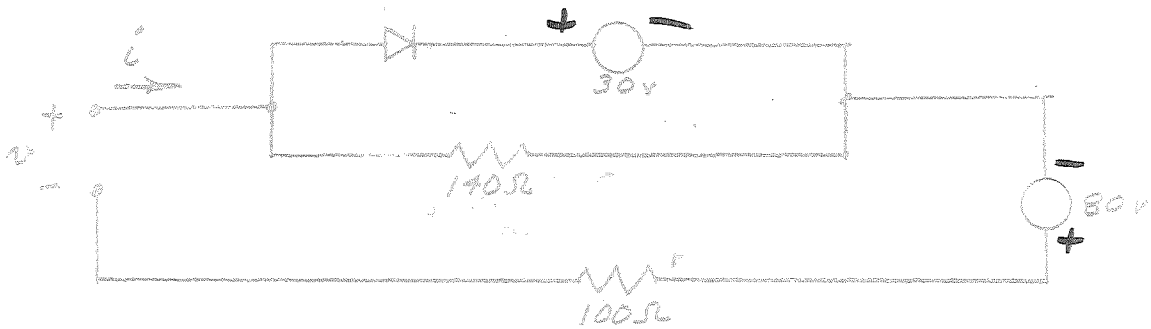-15 (40 pts) 3. Sketch and label the i - v curve for the following circuit. The diode is ideal.



~~$i < 0$~~

$$140i - 80 + 100i = v$$

$$240i = v + 80$$

$$i = \frac{v}{240} + \frac{1}{3}$$


(-5)

~~$i > 0 \Rightarrow$ DIODE IS SHORT CIRCUIT~~

$$(30 - 80 + 100i) = v$$

$$100i = v + 50$$

$$i = \frac{v}{100} + \frac{1}{2}$$

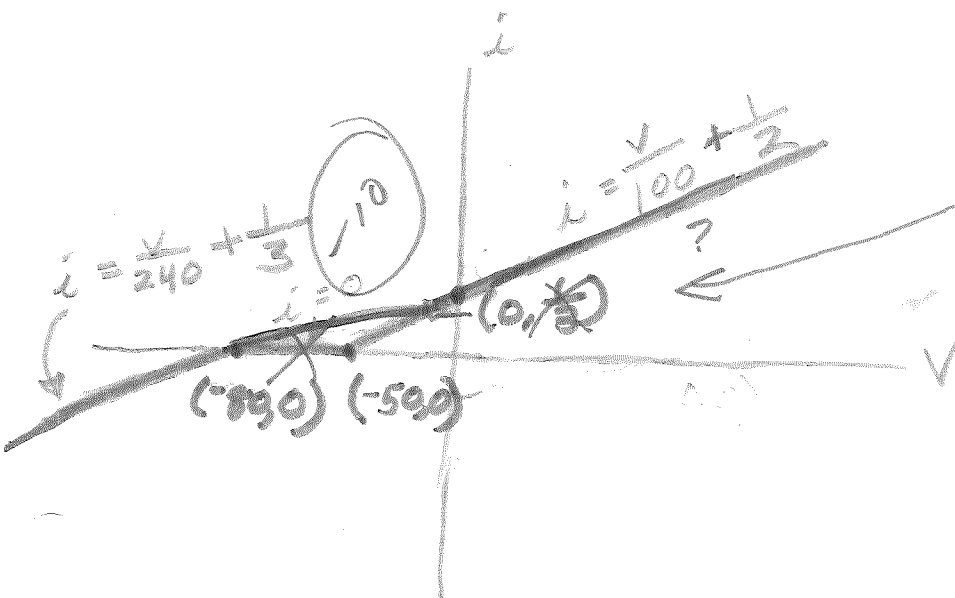

Good

$$V^x + 3V_1 = 0$$

$$V^x = -3(8.82) = -26.5V$$

$$P = V^x i = (26.5)(3) = 79.5 \text{ WATTS}$$

ABSORBED

b) $V_2 = 2V_1 = 2(-8.82) = -17.64V = V^2$

c) $30i_3 = V_1 = -8.82 \Rightarrow i_3 = -0.294 \text{ AMPS} = i_3$

d) $i_1 = \frac{50 - V_1}{100} = \frac{58.8}{100} = 0.588 \text{ AMPS} = i_1$

e) $i_2 = \frac{60 - V_2}{20} = \frac{77.6}{20} = 3.88 \text{ AMPS} = i_2$

$$10V_1 - 30V_1 + 3V_1 = \frac{300}{2} = 150$$

$$\frac{10V_1 - 30V_1 + 3V_1}{-17V_1} = \frac{150}{-17} \Rightarrow V_1 = \frac{300}{17} = 17.64V$$

$\sum i$ AROUND N = 0

$$V_2^x = (3 - i_2)20 \Rightarrow i_2 = \frac{60 - V_2}{20}$$

$$V_2^x = 2V_1 \Rightarrow V_2 = 2V_1$$


$$\Rightarrow i_3 = \frac{30}{V_1}$$

$$V_1 - 50 + 100i_1 = 0 \Rightarrow i_1 = \frac{50 - V_1}{100}$$

(BROWN)
(ORANGE)
-1

EE 201, EXAM 2 (cont'd)

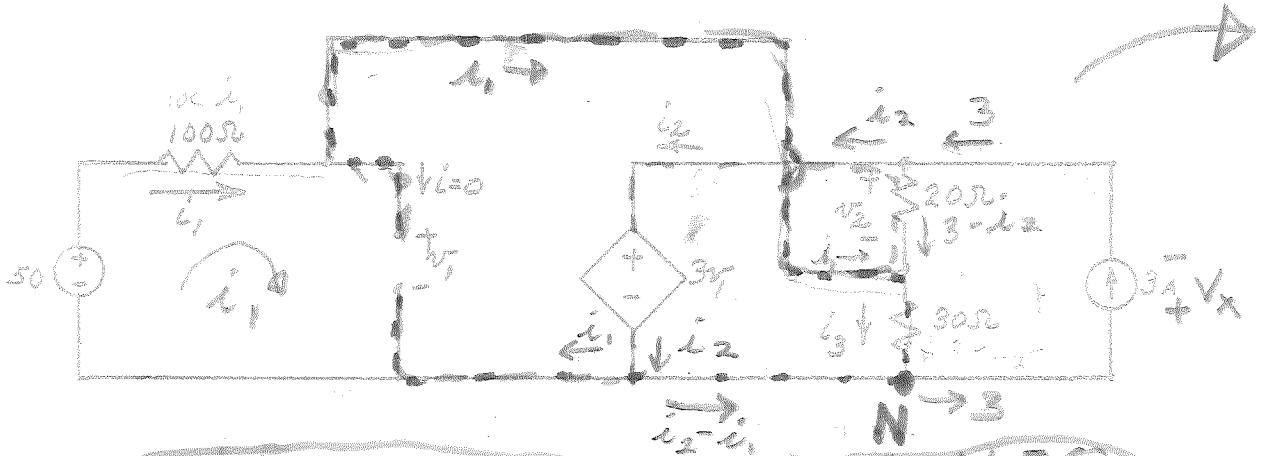(120pts) 2. Find i_1 , i_2 , i_3 , V_1 , and V_2 . Also find the power associated with the current source. State whether the source is absorbing or delivering power.



~~$$1) -50 + 100i_1 + V_1 = 0$$

$$2) 30i_3 - V_1 = 0$$

$$3) 3V_1 = 30i_3 - V_2 = 0$$

$$6) V_2 + 30i_3 + V_x = 0$$

$$7) V_2 = (3 - i_2)20 = 60 - 20i_2$$

$$2) V_1 = 30i_3 \Rightarrow 3V_1 = 90i_3$$

$$3) 90i_3 - 30i_3 - V_2 = 0$$

$$60i_3 = V_2 = 60 - 20i_2$$

$$6i_3 = 6 - 2i_2$$

$$6i_3 = 6i_1 - 6i_2 + 18$$

$$-12 = 6i_1 + 4i_2 = 0$$

$$3V_1 = 30i_3 - V_2$$

$$60i_3 = V_2 = 0$$~~

messy

114
140

8170

ROSE POLYTECHNIC INSTITUTE


EE 201
Winter 1970
NEM

EXAM 3

BOB MARKS
Name

-21

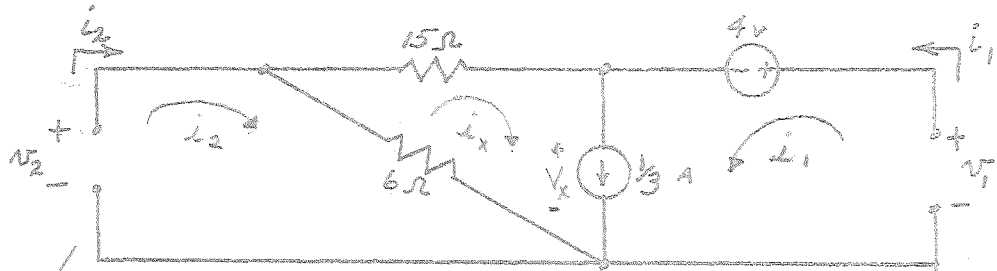(60 pts) 1. Find the three terminal π equivalent of the following network. Express your answer both as a set of equations and as a circuit. In the circuit, use resistances rather than conductances.



$$V_2 = 6i_2 - 6i_x \quad i_x = \frac{1}{3} - i_1$$

$$21i_x + V_x - 6i_2 = 0$$

$$V_1 = 4 + V_x$$

$$V_2 = 6i_2 - 6i_x \Rightarrow \frac{V_2}{6} = i_2 - i_x \quad \textcircled{A}$$

$$21i_x + V_x = 6i_2 \Rightarrow i_x = \frac{6i_2 - V_x}{21}$$

$$V_1 = 4 + V_x \Rightarrow \frac{6i_2 + 4 - V_1}{21} = i_x$$

$$\text{FROM } \textcircled{A}; \quad \frac{V_2}{6} = i_2 - \frac{6i_2 + 4 - V_1}{21}$$

$$= i_2 - \frac{6i_2}{21} - \frac{4}{21} + \frac{V_1}{21}$$

$$\frac{V_2}{6} = \frac{15i_2}{21} - \frac{4}{21} + \frac{V_1}{21}$$

$$\frac{15i_2}{21} = \frac{-V_1}{21} + \frac{V_2}{6} + \frac{4}{21}$$

$$15i_2 = -V_1 + \frac{V_2 \cdot 21}{6} + 4$$

$$\rightarrow i_2 = \frac{-V_1}{15} + \frac{7}{30} V_2 + \frac{4}{15}$$

FROM \textcircled{A}

$$\frac{V_2}{6} = i_2 - i_x \Rightarrow i_x = i_2 - \frac{V_2}{6}$$

ALSO: $i_x = \frac{1}{3} - i_1$

$$\therefore i_2 - \frac{V_2}{6} = \frac{1}{3} - i_1$$

OR $i_2 = \frac{1}{3} - i_1 + \frac{V_2}{6}$


$$i_2 = \frac{-V_1}{15} + \frac{7V_2}{30} + \frac{4}{15}$$

$$\therefore \frac{1}{3} - i_1 + \frac{V_2}{6} = \frac{-V_1}{15} + \frac{7V_2}{30} + \frac{4}{15}$$

$$\frac{V_2}{6} - \frac{7V_2}{30} = \frac{-V_1}{15} - \frac{4}{15} + i_1$$

$$i_1 = \frac{V_2}{15} - \frac{V_1}{15} + \frac{1}{15}$$

$\textcircled{3}$

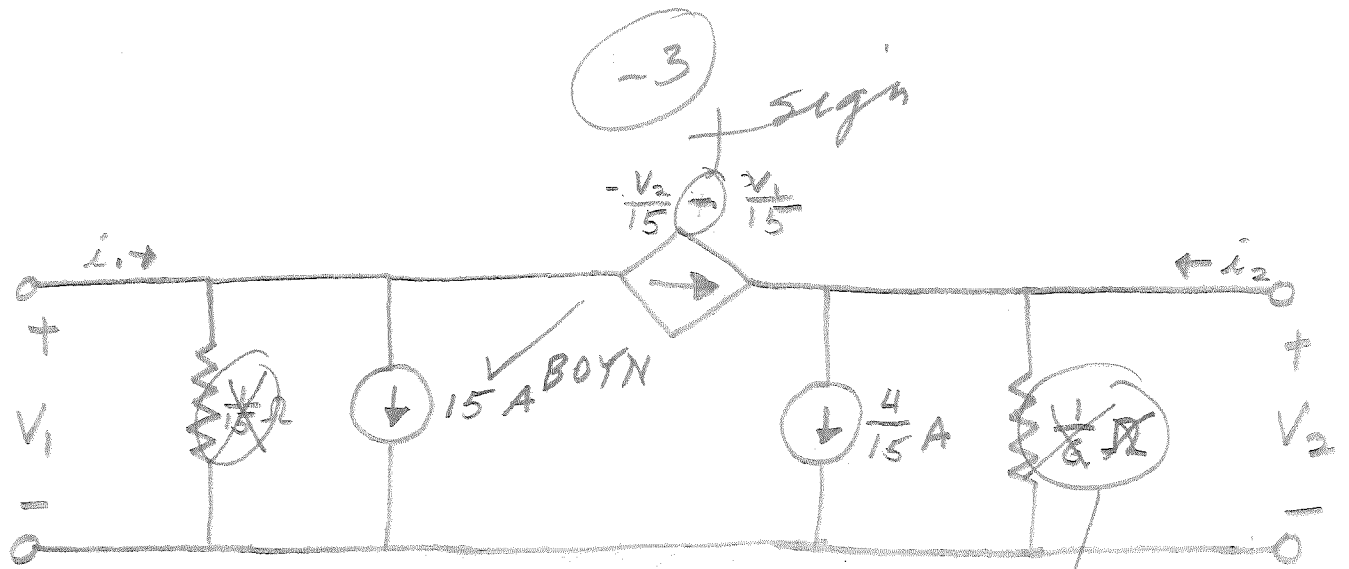

-3 sign

THIS CIRCUIT HAS RECIPROACITY

not resistance


-15

(80 pts) 2. A Mystery Problem! (Aren't they all!)

The following network has one of the listed sub-circuits connected to terminals a and b.

If the power delivered to the subcircuit is 30w which subcircuit is connected and how is it connected (what terminal is connected to terminal a) ?

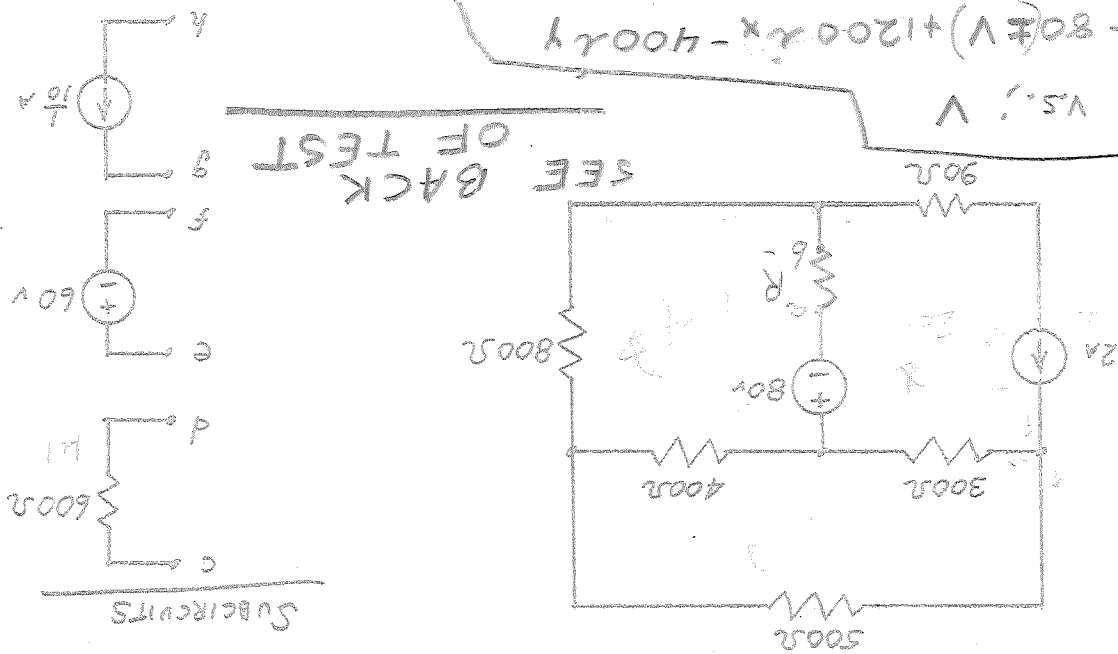Explain your method for solving the problem.



1) PWT IN V.S., V

$$0 = -80 \pm V + 1200x - 400x$$

$$0 = (1200x - 400x - 600)$$

$$0 = -240 \pm 3V + 3600x - 1200x$$


$$-(3200)x = -840 \pm 3V$$

$$x = \frac{84}{320} \pm 3V$$

$$|V| = 60, V = +60 \Rightarrow x \approx 180A \Rightarrow P \neq 3$$

$$V = -60 \Rightarrow x \approx -180A \Rightarrow P \neq 3$$

2) PUT IN RESISTOR

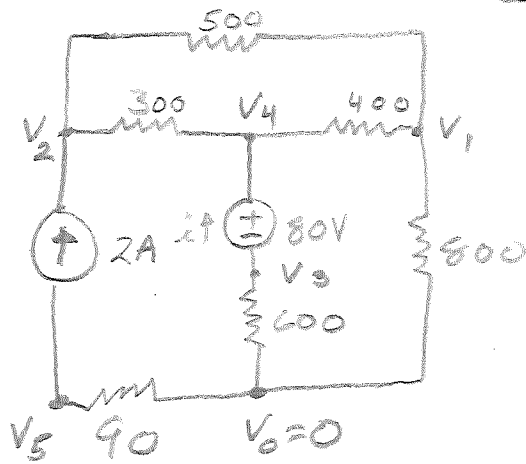

$$-\frac{V_3}{600} - \frac{V_1}{800} - \frac{V_5}{90} = 0$$

$$V_4 - V_3 = 80$$

$$\frac{V_2 - V_4}{300} - 2 + \frac{V_2 - V_1}{500} = 0$$

$$-i + \frac{V_4 - V_1}{400} + \frac{V_4 - V_2}{300} = 0$$

$$i = \frac{V_4}{300} + \frac{V_4}{400} - \frac{V_1}{400} - \frac{V_2}{300}$$

$$\frac{V_1 - V_2}{500} + \frac{V_1 - V_4}{400} + \frac{V_1}{800} = 0$$

~~$$\frac{V_1 - V_2}{500} + \frac{V_1}{800} = 80$$~~

$$V_1 - V_4 = 80 \quad V_1 = V_4 + 80$$

~~$$\frac{V_1 - V_2}{500} + \frac{V_1}{800} = 80$$~~

$$\frac{V_2}{500} = \frac{V_1}{500} + \frac{V_1}{800} - 80$$

$$\frac{V_2}{300} = \frac{V_1}{300} + \frac{5V_1}{2400} - \frac{400}{3}$$

$$\frac{400}{3} i = \frac{V_4}{300} + \frac{V_4}{400} - \left(\frac{V_1}{400} + \frac{V_1}{300} + \frac{5V_1}{2400} \right)$$

$$i = \frac{V_4}{300} + \frac{V_4}{400} - \frac{V_4}{400} + \frac{80}{400} - \frac{V_4}{800} + \frac{80}{300} - \frac{5V_4}{2400} + \frac{400}{2400}$$

$$i = \frac{1}{3} + \frac{8}{30} - \frac{5V_4}{2400}$$

~~$$= \frac{1}{3} + \frac{8}{30} - \frac{V_4}{480}$$~~

50 WOT!

for comp 2025



$$\frac{R}{V_2} = \frac{I}{3}$$

$$R = \frac{I}{3} \cdot 3$$

$$3V_2 = I \cdot 3$$

$$\frac{V_3 - V_1}{400} + I + \frac{V_3 - V_4}{300} = 0$$

$$\frac{V_4 - V_3}{300} - 2 + \frac{300}{V_4 - V_1} = 0$$

BY N.T.D.

$$I_x(3200 + 3R) = 840 + 6R$$

~~$$R(I_x - 2)(80) + 1200I_x - 400I_x$$~~

$$P = \left(\frac{840 + 6R}{3200 + 3R} - 2 \right)^2 R = 3$$

$$V_R = (I_x - 2)R$$

$$I_x = \frac{840 + 6R}{3200 + 3R}$$

$$I_x(3200 + 3R) = 840 + 6R$$


$$3200I_x + 3RI_x - 6R = 840$$

$$3200I_x + 3R(I_x - 2) - 840 = 0$$

$$3R(I_x - 2) - 240 + 3600I_x - 1200I_x = 0$$

$$1200I_x - 400I_x - 600 = 0$$
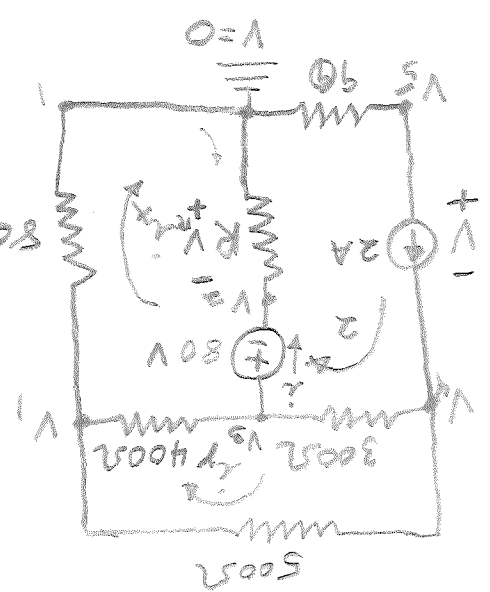
$$R(I_x - 2) - 80 + 1200I_x - 400I_x = 0$$



$$\frac{107}{130} = 8270$$

ROSE POLYTECHNIC INSTITUTE

EE 201
Winter 1970
NEM

EXAM 4

BOB MARKS
Name

✓ (10 pts) 1. Find A and B.

$$\frac{10s}{(s+3)(s+4)} = \frac{A}{s+3} + \frac{B}{s+4}$$

$$10s = A(s+4) + B(s+3)$$

$$s = -4 \Rightarrow -40 = B \Rightarrow B = 40$$


$$s = -3 \Rightarrow -30 = A$$

$$B = 40 \checkmark$$

$$A = -30 \checkmark$$

$$\left[\mathcal{L}^{-1} \left\{ \frac{10s}{(s+3)(s+4)} \right\} = -30e^{-3t} + 40e^{-4t} \right]$$

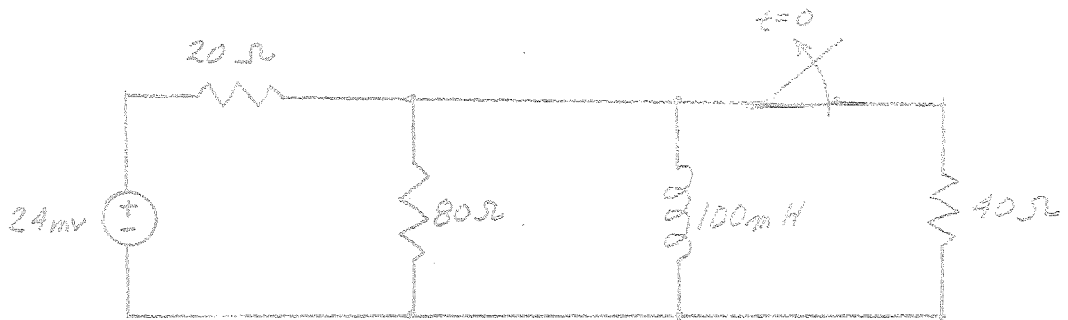-10 (20 pts) 2. What is the time constant of the following circuit?



$$\tau = \frac{L}{R_{eq}}$$

$$\frac{1}{R_{eq}} = \frac{1}{20} + \frac{1}{80} + \frac{1}{40}$$

$$\frac{10}{R_{eq}} = \frac{4}{4} + \frac{1}{8} + \frac{2}{4}$$


$$= \frac{4+1+2}{8} = \frac{7}{8}$$

$$R_{eq} = \frac{80}{7} \Omega$$


$$\tau = \frac{(0.1)7}{80} = .0875 \text{ SEC}$$

-10
40Ω not in circuit during transient portion.

-08 (80 pts) 3. Find and sketch $v_R(t)$

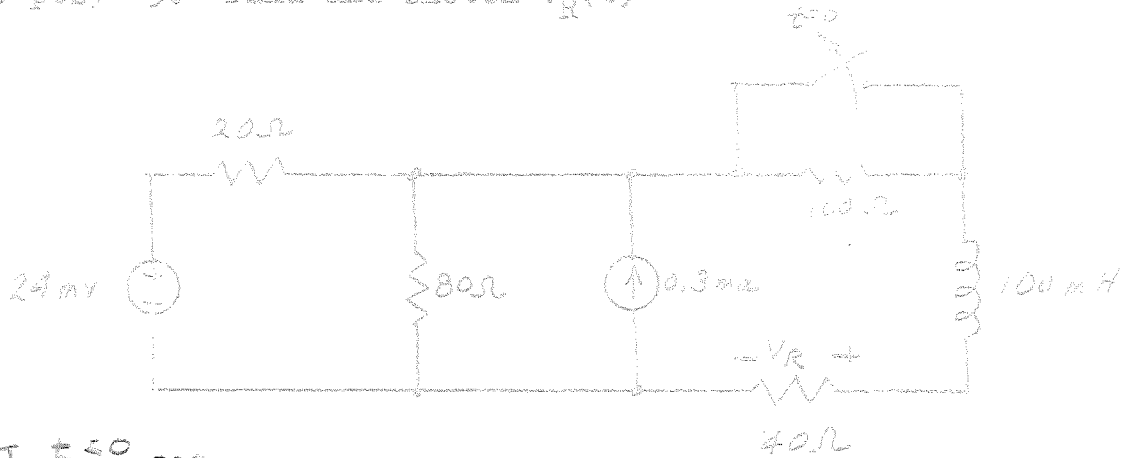

I) AT $t < 0$

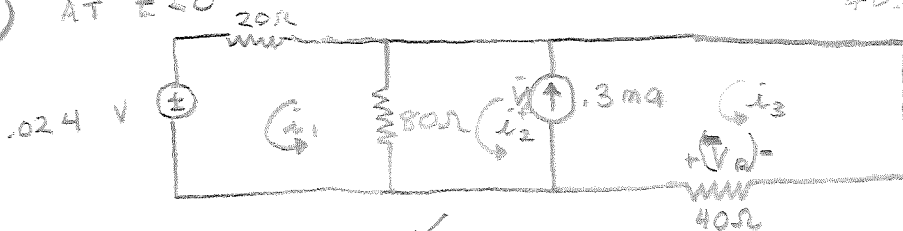

? $\begin{cases} 1) .024 + 100i_1 - 80i_2 = 0 \\ 2) 80i_1 - 80i_2 + V_S = 0 \\ 3) -V_S + V_R = 0 \\ 4) 40i_3 = V_R \\ 5) i_2 - i_3 = .3 \times 10^{-3} \end{cases}$

6) $V_S = V_R$ (FROM 3)

7) $i_1 = \frac{-.024 + 80i_2}{100}$ (FROM 1)

8) $i_1 = \frac{80i_2 + V_R}{80}$ (FROM 2 & 6)

9) $\frac{-.024 + 80i_2}{10} = \frac{80i_2 + V_R}{8}$ (7 & 8)

10) $i_2 = 3 \times 10^{-4} + i_3$ (5)

11) $\frac{-.024 + 80(3 \times 10^{-4} + i_3)}{10} = \frac{80(3 \times 10^{-4} + i_3) + V_R}{8}$ (10 & 9)

12) $i_3 = \frac{V_R}{40}$ (4)


13) $\frac{-.024}{10} + 24 \times 10^{-4} + \frac{8V_R}{40} = 30 \times 10^{-4} + \frac{10V_R}{40}$ (10 & 9)

14) $\frac{2}{40} V_R = -3 \times 10^{-3}$

15) $V_R = -60 \times 10^{-3} \Rightarrow V_R = 60 \times 10^{-3} \text{ VOLTS}$

SR -3

II) AT $t > 0$

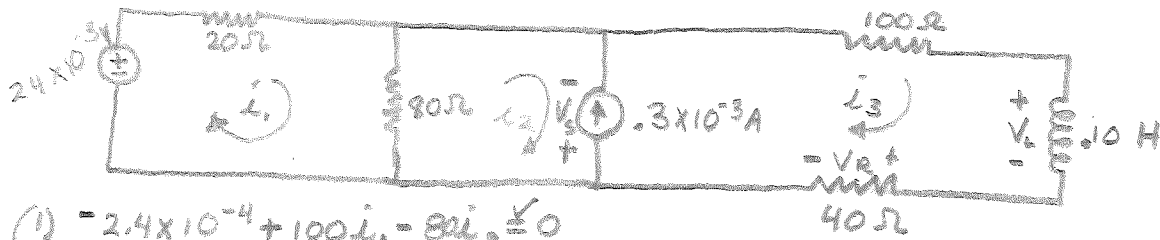

Why change i_3 ?

- 1) $-2.4 \times 10^{-4} + 100i_1 - 80i_2 \neq 0$
- 2) $-V_s + 80i_2 - 80i_1 = 0$
- 3) $V_s + V_R + 100i_3 + (10) \frac{di_3}{dt} = 0$
- 4) $i_3 - i_2 = 3 \times 10^{-4} \checkmark$
- 5) $V_R = 40i_3 \checkmark$

- 6) $\frac{-2.4 \times 10^{-4}}{5} + 100I_1 - 80I_2 = 0$
- 7) $-V_s + 80I_2 - 80I_1 = 0$
- 8) $V_s + V_R + 100I_3 + (10)SI_3 - (10)i_3(0) = 0$
- 8b) $V_s + V_R + 100I_3 + (10)SI_3 - 1.5 \times 10^{-3} = 0$

$$i_3(0+) = \frac{V_R}{R} = \frac{60 \times 10^{-3}}{40} = 1.5 \times 10^{-3} \text{ A}$$


- 9) $I_3 - I_2 = \frac{3 \times 10^{-4}}{5}$
- 10) $V_R = 40I_3$
- 11) $V_s = 1.5 \times 10^{-3} - V_R - 100I_3 - (10)SI_3$ (8b)
- 12) $V_s = 80I_2 - 80I_1$ (7)

- 13) $1.5 \times 10^{-3} - V_R - 100I_3 - (10)SI_3 = 80I_2 - 80I_1$ (11 & 12)
- 14) $I_1 = \frac{80I_2 + 2.4 \times 10^{-4}}{100} = \frac{80I_2}{500} + \frac{2.4 \times 10^{-4}}{500}$ (6)
- 15) $1.5 \times 10^{-3} - V_R - 100I_3 - (10)SI_3 = 80I_2 - 64I_2 - \frac{1.92 \times 10^{-4}}{5}$ (13 & 14)
- 16) $I_2 = I_3 - \frac{3 \times 10^{-4}}{5}$ (9)
- 17) $1.5 \times 10^{-3} - V_R - 100I_3 - (10)SI_3 = 16I_3 - \frac{48 \times 10^{-4} + 1.92 \times 10^{-4}}{5}$ (15, 16)

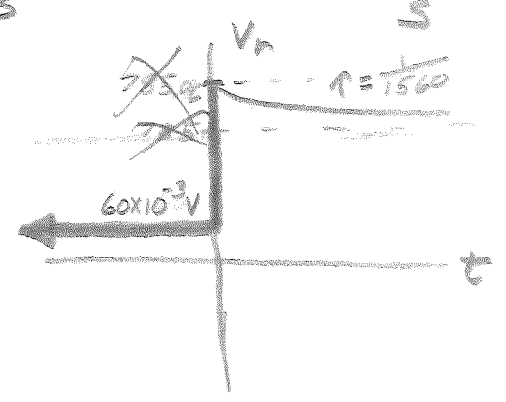
- 18) $I_3 = \frac{V_R}{40}$ (10)
- 19) $1.5 \times 10^{-3} - V_R - \frac{100V_R}{40} - (10)S \frac{V_R}{40} = 16 \frac{V_R}{40} - \frac{48 \times 10^{-4} + 1.92 \times 10^{-4}}{5}$ (17, 18)
- 20) $V_R \left[-1 + \frac{5}{2} + \frac{5}{400} + \frac{16}{40} \right] = 1.5 \times 10^{-3} + \frac{48 \times 10^{-4} + 1.92 \times 10^{-4}}{5}$
- 20) $V_R \left[\frac{39}{10} + \frac{5}{400} \right] = 1.5 \times 10^{-3} + \frac{50 \times 10^{-4}}{5}$ (-5)

$$21) V_R = \frac{600 \times 10^{-3}}{1560 + 5} + \frac{2}{5(1560 + 5)} = \frac{600 \times 10^{-3} + 1.28 \times 10^{-3}}{1560 + 5} + \frac{785}{5}$$

$$V_r = .601 e^{-1560t} + 785 \text{ For } t > 0$$



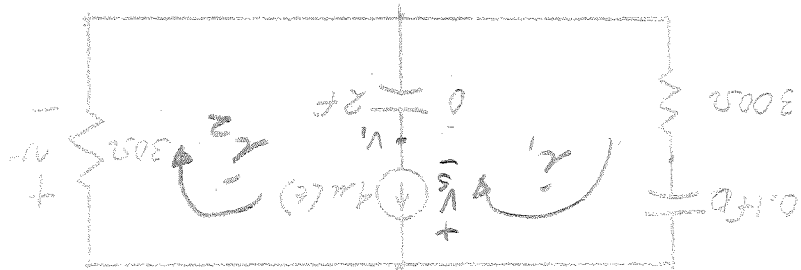3 (20 pts) 4: What is $v(0^+)$? (Initial capacitor voltages are zero.)



A CAPACITOR CANNOT HAVE AN IMMEDIATE VOLTAGE CHANGE ACROSS IT.

SP (1)

AT $t = (0^+)$, $300i_1 + v_1 = 0$
 $300i_2 - v_2 = 0$

$-300i_1 = 3\phi i_2$
 $-10i_1 = i_2$

ALSO $i_2 - i_1 = 4$

$i_1 = i_2 - 4$

$\therefore -10(i_2 - 4) = i_2$

$-10i_2 + 40 = i_2$
 $11i_2 = 40$

$i_2(0^+) = \frac{40}{11} = 3.53$ AMPS

SP (2)

$v(0^+) = R i_2(0^+) = (30)(3.53) = 106$ V

REQ OF PULSE & SINUSOIDAL GENERATORS

I) PULSE GENERATOR PRF=300 $\tau=1\text{ms}$

A) AT AMP. ON FULL

$$V_{eq} = 50\text{V} ; R_{eq} = 620 \text{ } \underline{\text{Low}}$$

B) AT 60%

$$V_{eq} = 30\text{V} ; R_{eq} = 550$$

C) AT 30%

$$V_{eq} = 13\text{V} \quad R_{eq} = 240$$

II) FOR SINUSOIDAL, $f = 30,000\text{ Hz}$

A) AMPLITUDE ON FULL

$$V_{eq} = 2.0\text{V} ; R_{eq} = 500\Omega$$

B) AT 50%


$$\sqrt{R_{eq}} = 8.25\text{V} ; R_{eq} = 180\Omega \quad \underline{\text{Nope!}}$$

BOB MARKS


Dennis English

Mike Fether

Russ MAGERS

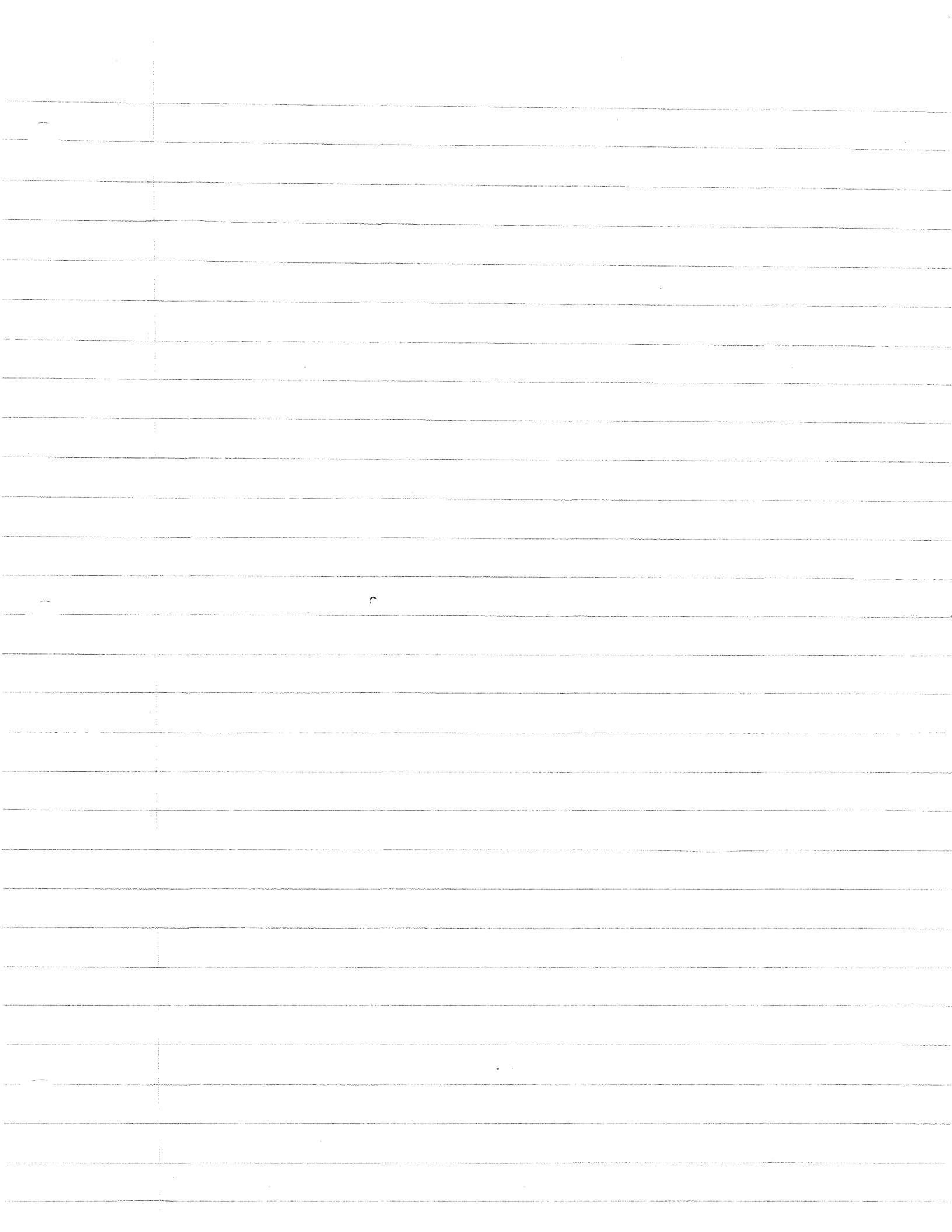

E-sci I

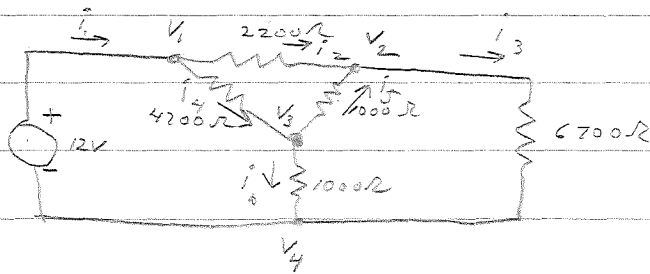

$$i_1 = 4.1 \text{ mA} \quad V_1 = 12 \text{ V}$$

$$i_2 = 2.5 \text{ mA} \quad V_2 = 5.8 \text{ V}$$

$$i_3 = +8 \text{ mA} \quad V_3 = 3.8 \text{ V}$$

$$i_4 = 3.4 \text{ mA}$$

$$i_5 = 1.6 \text{ mA}$$


$$i_5 = -1.6 \text{ mA}$$

Bob Marks

Mike Jeter

Dennis Engler

Bruce Magers

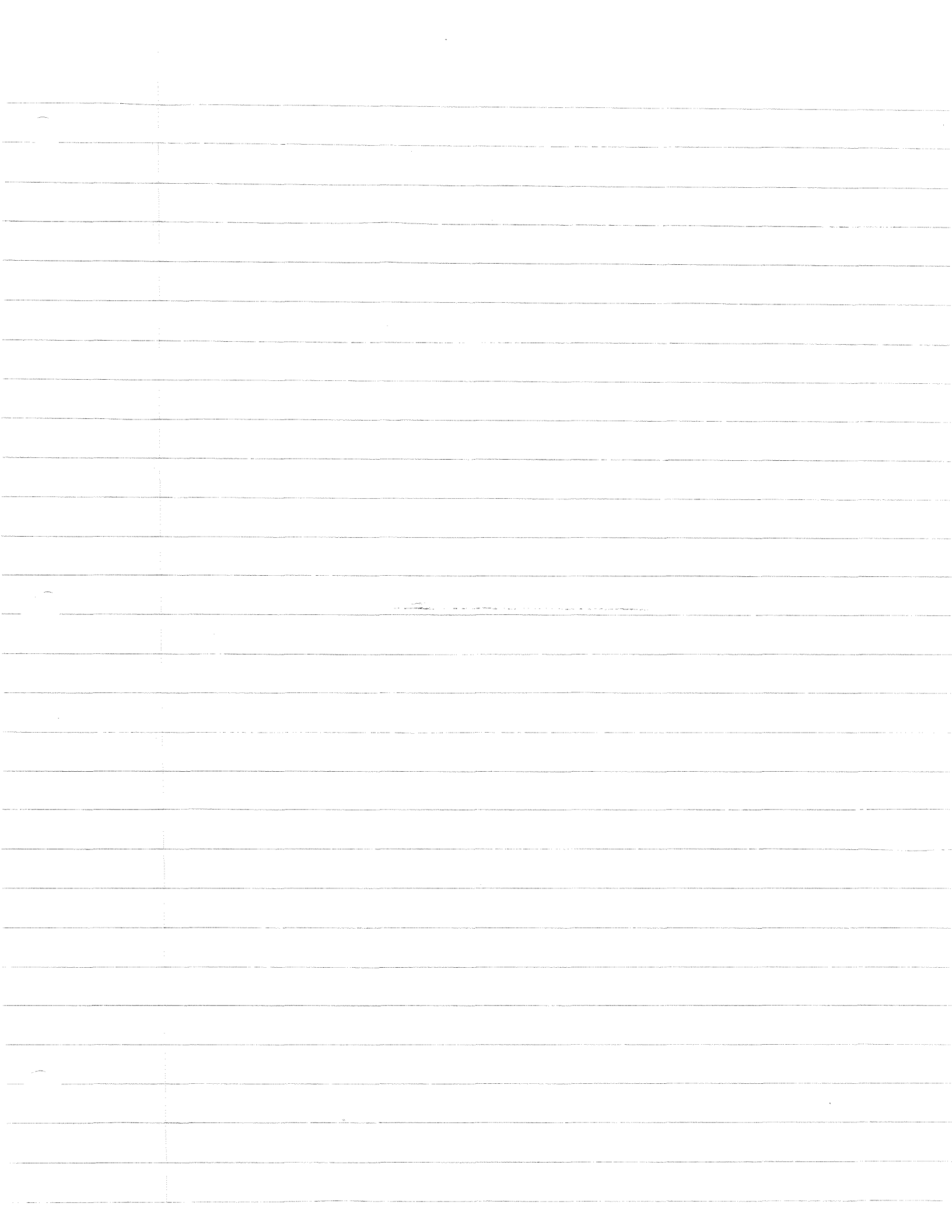







EE208 Laboratory
 Frequency response experiment
 Uses software, not hardware.

Use the computer program stored in EE204A to compute $|H(j\omega)|$ and $\angle H(j\omega)$ for the particular circuit shown below. In each case $H(s) = V_o(s)/V_i(s)$.






Plot $|H(j\omega)|$ on log-log paper as a function of f .

Plot $\angle H(j\omega)$ on semi logarithmic graph paper as a function of f .

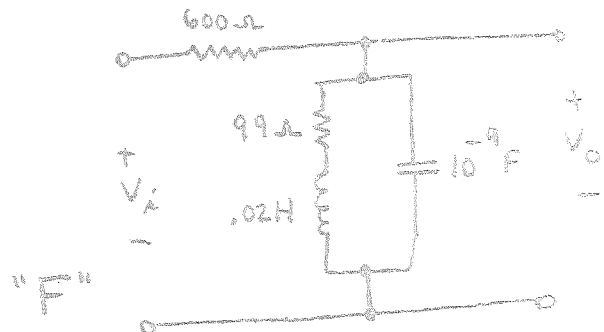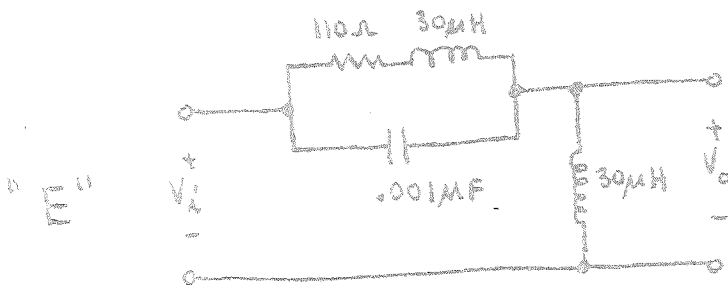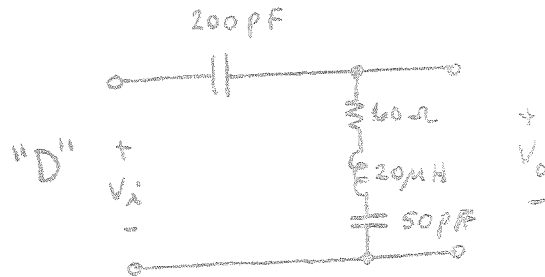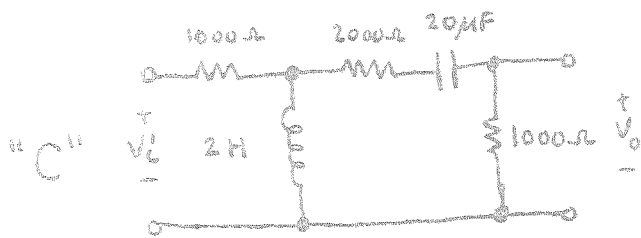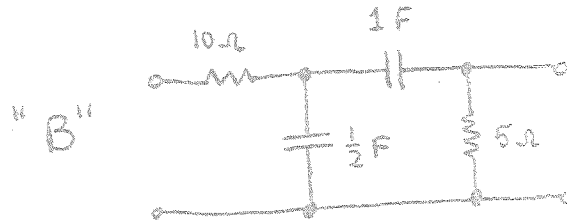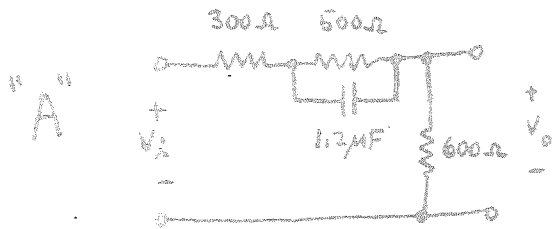Show your entire computer program to the lab instructor or his assistant by 4:00 pm Thursday, February 11, 1971, in order to receive credit for this assignment.



"G"

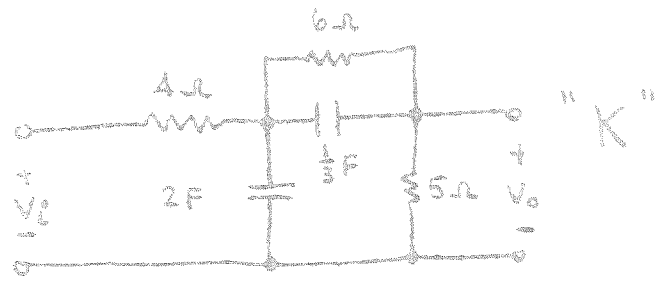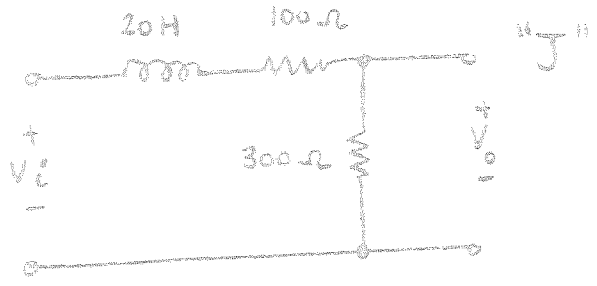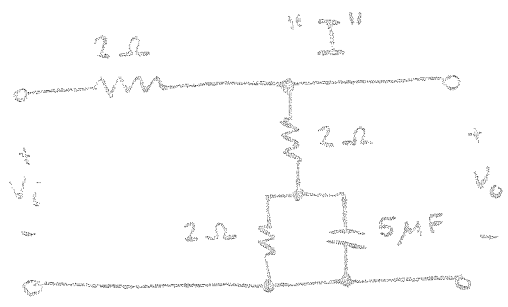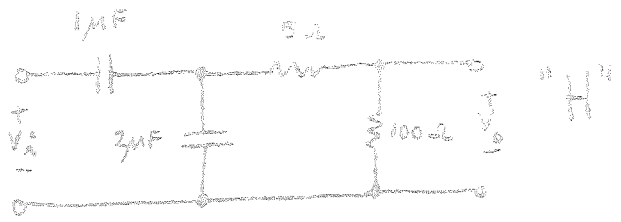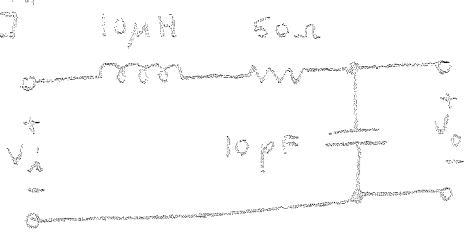

EE204 and EE205 Laboratory

Helpful hints for happy lab books.

1. Always keep the notebook in ink.
2. No loose pages will be allowed.
3. Always keep all lab notes on the notebook as you are doing the experiment.
4. Keep accurate records which would enable you to repeat your experiment at a later date and get the same results.
5. Make sure a complete circuit diagram is included for all measurements.
6. Record instrument information and numbers. Some are used in calculations.
7. All tables should have column headings and appropriate units.
8. Fill in as it is that you are doing; preferably in duplicate. When in doubt write it down.
9. All graphs should be on appropriate graph paper and attached to the notebook. Each graph should have a clearly labelled axes, and units. The preparer of the graph should put his name on the graph.
10. Always use straight edge or curves to draw the graph.
11. In general put all writing in the lab notebook. It is much easier to keep track of all your notes this way.
12. The experiment instruction sheets are usually to all the guide in most cases. Do not "Parrot" these instructions in your notebook.

EE 208 ELECTRICAL SCIENCE LABORATORY

EXPERIMENT NO. _____


SERIES RESONANCE

Introduction:


Resonant circuits find many practical applications in electrical engineering. In this experiment we will investigate a few of the more important characteristics of the series resonant circuit. Among these are frequency of resonance, bandwidth, and Q.

Equipment:

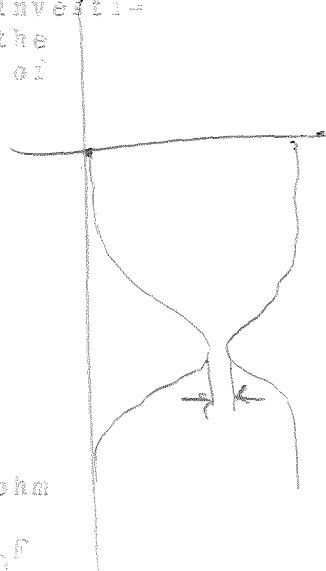- Audio Oscillator
- Cathode-Ray Oscilloscope
- Vacuum Tube Voltmeter
- Laboratory Resistor Decade
- Laboratory Capacitor Decade
- .03H Inductor



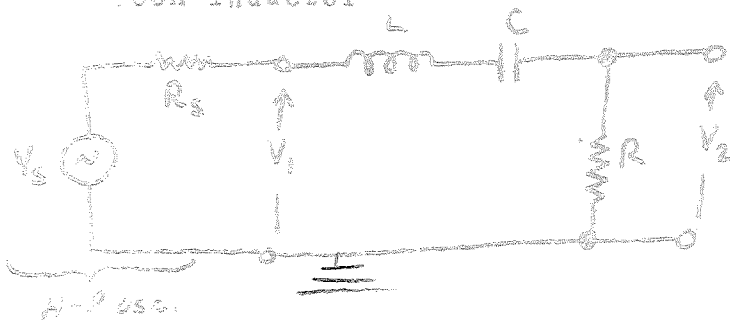- $R = 1000 \text{ ohm}$
- $C = .001 \mu\text{F}$
- $L = .03 \text{ H}$




1. Measure the value of R_s for the H-P audio oscillator.
2. Keeping \dot{V}_s constant at 10V R.M.S. plot a curves of $|\dot{V}_2|$ AND $|\dot{V}_1|$ vs. frequency which clearly shows the resonant frequency.
3. From the curve of part 2 determine the resonant frequency and the upper and lower half power frequencies.
4. Determine the bandwidth of the circuit and thus the value of Q_0 .

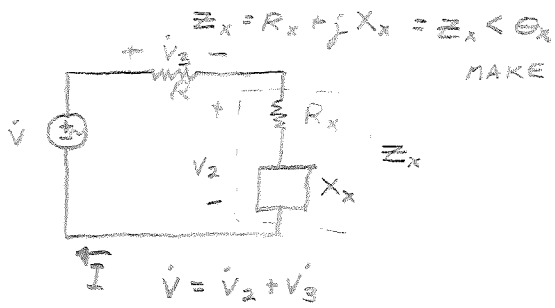5. Use the Q_0 above to determine the total series resistance of the circuit. From this determine R_s and compare with result of part 1.
6. Connect the CRO to display \dot{V}_1 on the vertical and \dot{V}_2 on the horizontal axes. Describe the appearance of the Lissajous pattern as the frequency is varied through resonance.
7. Determine the frequency where the maximum voltage across the capacitor occurs.

12-10-70

3 VOLT METER METHOD OF IMPEDENCE MEASUREMENT




MAKE 3 VOLTAGE MEASUREMENTS

PHASOR DIAGRAM



(BREAK INTO COMPONENTS)

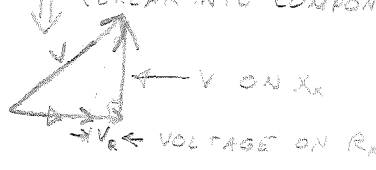

USE LAW OF COSINES TO DETERMINE θ

$\phi = 180^\circ - \theta$

$V^2 = V_3^2 + V_2^2 - 2V_3V_2 \cos \phi \Rightarrow \cos \phi = \frac{V_3^2 + V_2^2 - V^2}{2V_3V_2} = -\cos \theta$


$|Z_x| = \frac{V_2}{V_3} R$



12-17-70


LAB PARTNERS, LN \neq LAWRENCE

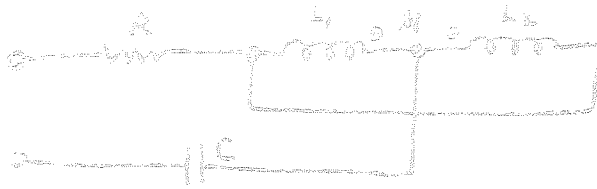2. Find the lower half power frequency and bandwidth for the series RLC circuit shown.



$$\begin{aligned} L_1 &= 100 \text{ mH} \\ L_2 &= 300 \text{ mH} \\ M &= 120 \text{ mH} \\ C &= 2000 \text{ pF} \\ R &= 100 \text{ } \end{aligned}$$

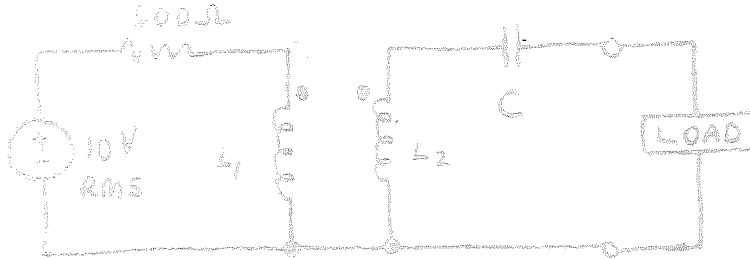
2. Find the load impedance which will extract maximum power from the source shown. How many watts is this power?



$$\begin{aligned} \omega L_1 &= 300 \text{ } \\ \omega L_2 &= 1000 \text{ } \\ \frac{1}{\omega C} &= 600 \text{ } \\ W_M &= 500 \text{ } \end{aligned}$$


3. Two coils, L_1 and L_2 , have a mutual inductance equal to K . If $M = \frac{1}{2} \sqrt{L_1 L_2}$, show and tell how you may use these two coils to obtain at least 4 different values of inductance. What are these values?

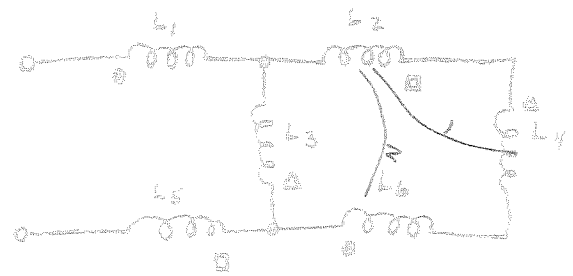
4. Use the T-equivalent circuit where possible to find the equivalent inductance of the interconnection of coils shown



$$\begin{aligned} L_1 &= 1H & L_7 &= 5H \\ L_2 &= 2H & L_8 &= 6H \\ L_3 &= 3H & L_9 &= 7H \\ L_4 &= 4H & L_{10} &= 8H \end{aligned}$$

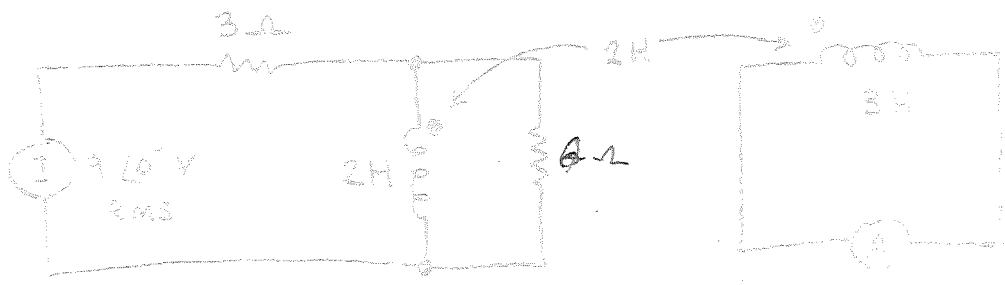5. Find the reading of the ideal a-c ammeter.



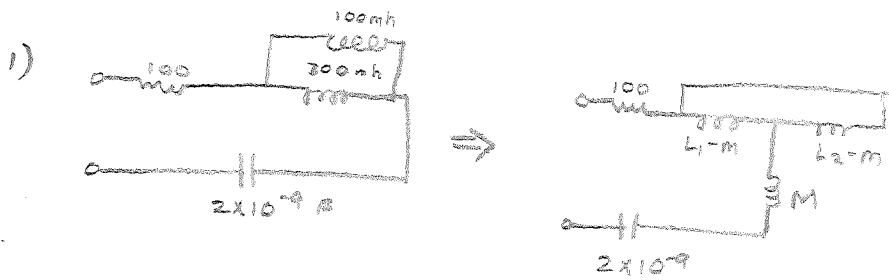

$$L_{eq} = \frac{1}{\frac{1}{100} + \frac{1}{200}} + 120 = 97.5 \text{ mH} = .0975 \text{ H}$$





$$\omega_0 = \frac{1}{\sqrt{LC}} = 7.16 \times 10^4 \text{ RAD/SEC}$$

$$f = 1.14 \times 10^4 \text{ Hz}$$


$$W_{UHP} = \omega_0 \sqrt{1 + \frac{1}{4Q^2}} + \frac{\omega_0}{2Q} = 7.21 \times 10^4 \frac{\text{RAD}}{\text{SEC}} = 1.15 \times 10^4 \text{ Hz}$$

$$W_{LHP} = \omega_0 \sqrt{1 + \frac{1}{4Q^2}} - \frac{\omega_0}{2Q} = 7.11 \times 10^4 \frac{\text{RAD}}{\text{SEC}} = 1.13 \times 10^4 \text{ Hz}$$
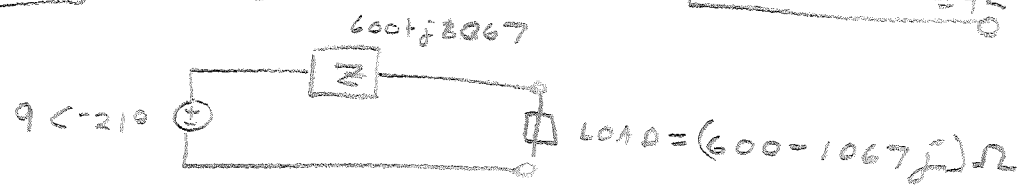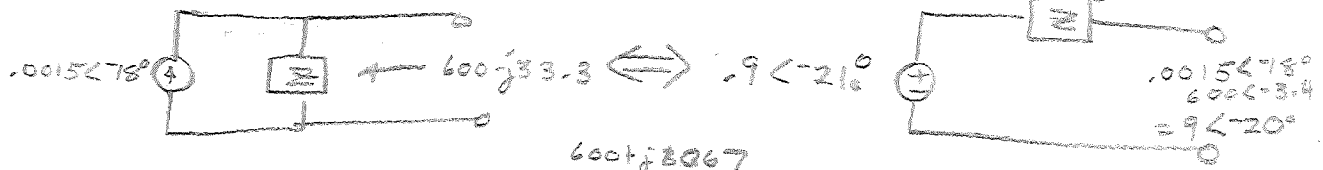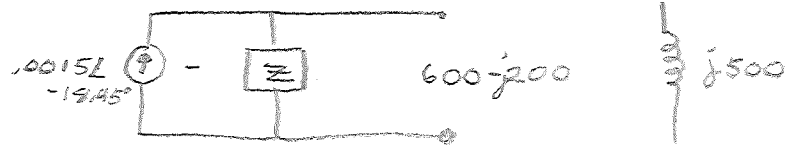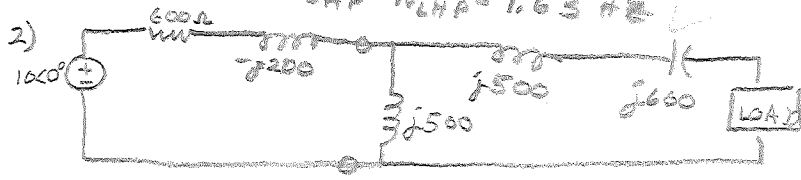
$$BW = W_{UHP} - W_{LHP} = 1.63 \text{ kHz}$$


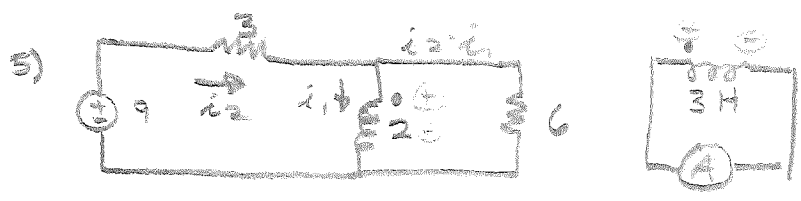
$$\text{POWER} = \frac{V^2}{R} = \frac{0.81}{1200} = 5.75 \times 10^{-2} \text{ WATTS}$$




$$\begin{aligned}
 9 &= 3I_2 + j2I_1 + j2I_3 \\
 0 &= 6(I_2 - I_1) + [j2I_1 - j2I_3] \\
 &= -(6 + j2)I_1 + 6I_2 - j2I_3 \\
 0 &= j3I_3 + j2I_1
 \end{aligned}$$

$$\begin{bmatrix}
 j2 & 3 & j2 \\
 -(6+j2) & 6 & -j2 \\
 j2 & 0 & j3
 \end{bmatrix} \Rightarrow -14 + j42$$

$$\begin{bmatrix}
 j2 & 3 & 0 \\
 -(6+j2) & 6 & 0 \\
 j2 & 0 & 9
 \end{bmatrix} \Rightarrow 54 + j126$$

$$\frac{54 + j126}{-14 + j42} = \frac{137 \angle 66^\circ}{44.3 \angle 110^\circ} = 3.04 \angle -44^\circ$$

304 AMPS X

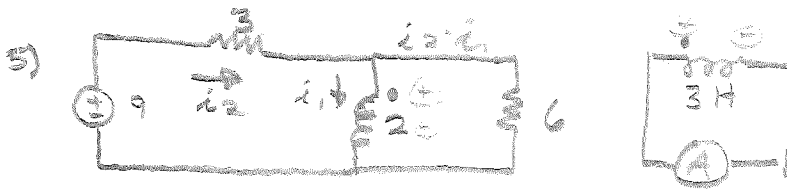

$$\begin{aligned}
 9 &= 3I_2 + j2I_1 + j2I_3 \\
 0 &= 6(I_2 - I_1) + [j2I_1 - j2I_3] \\
 &= -(6 + j2)I_1 + 6I_2 - j2I_3 \\
 0 &= j3I_3 + j2I_1
 \end{aligned}$$

$$\begin{bmatrix}
 j2 & 3 & j2 \\
 -(6+j2) & 6 & -j2 \\
 j2 & 0 & j3
 \end{bmatrix} \Rightarrow -14 + j42$$

$$\begin{bmatrix}
 j2 & 3 & 0 \\
 -(6+j2) & 6 & 0 \\
 j2 & 0 & 9
 \end{bmatrix} \Rightarrow 54 + j126$$


$$\frac{54 + j126}{-14 + j42} = \frac{137 \angle 66^\circ}{44.3 \angle 110^\circ} = 3.04 \angle -44^\circ$$

304 AMPS X



Department of
 Electrical and Computer
 Engineering
 January 7, 2020

EE 208 - LABORATORY
 PROBLEM SESSION
 SOLUTIONS

PROBLEM 1

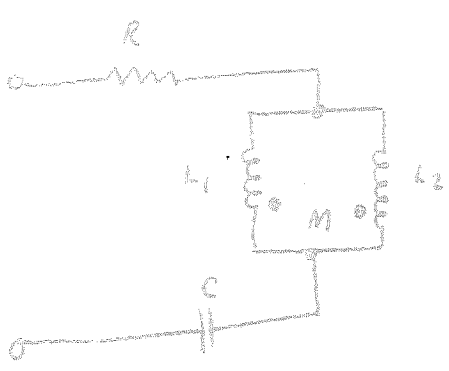

Use equivalent

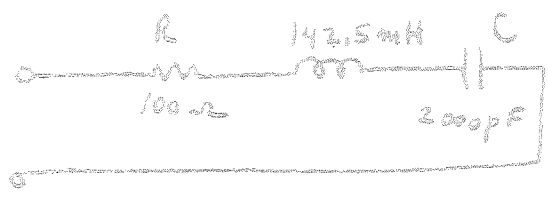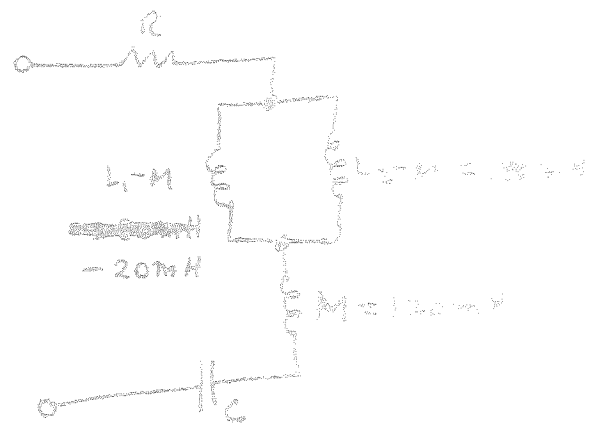

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = \boxed{9427 \text{ Hz}}$$



$$Q_0 = \frac{2\pi f_0 L}{R} = \boxed{84.4}$$

$$f_u = \frac{1}{2\pi} \left[\sqrt{1 + \frac{1}{4Q_0^2}} + \frac{1}{2Q_0} \right]$$

$$f_l = \frac{1}{2\pi} \left[\sqrt{1 + \frac{1}{4Q_0^2}} - \frac{1}{2Q_0} \right]$$

$$\text{BW} = f_u - f_l = \boxed{111.7 \text{ Hz}}$$

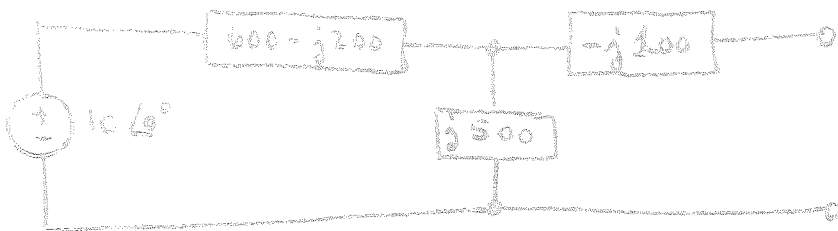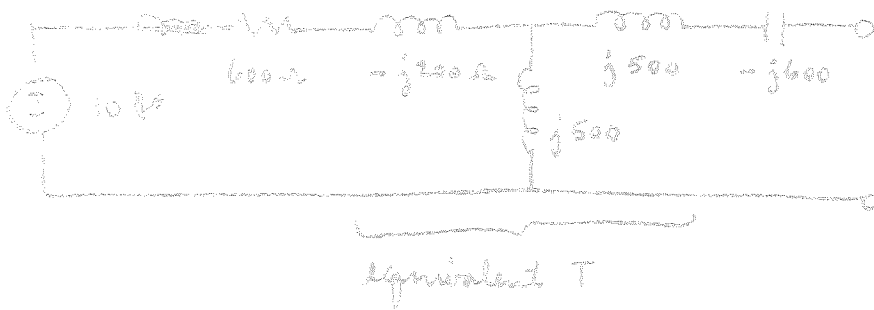Use Thevenin's theorem for the portion of the circuit to the left of the load terminals



$$\vec{E}_{THEV} = -j100 + \frac{(j500)(600 - j200)}{600 - j200 + j500} = -j100 + \frac{500(600 - j200)}{400 + j300}$$

$$= -j100 + 10^3 \left(\frac{1 + j3}{6 + j3} \right) = -j100 + 10^3 \left(\frac{5 \angle 71.5^\circ}{6.71 \angle 26.5^\circ} \right)$$


$$= -j100 + 1000 (1.472 \angle 45^\circ) = -j100 + 717 + j717$$

$$= \boxed{333 + j233 \Omega} \quad \text{make } \vec{E}_T = \boxed{1000 \angle 45^\circ}$$

$$V_{THEV} = \frac{j500}{400 + j300} \cdot 10 \angle 0^\circ = \frac{5000 \angle 90^\circ}{100(6.71 \angle 26.5^\circ)} = \frac{5000 \angle 90^\circ}{671 \angle 26.5^\circ}$$


$$\vec{V}_{THEV} = \frac{7.45^\circ}{6.71} \boxed{1091.6 \angle 63.5^\circ}$$

1

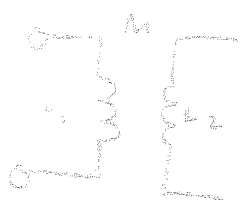

Equivalent circuit:


2

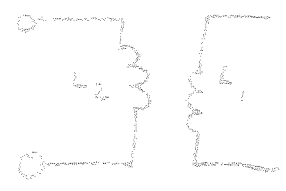

ii

$Z_{eq} = L_1$


3

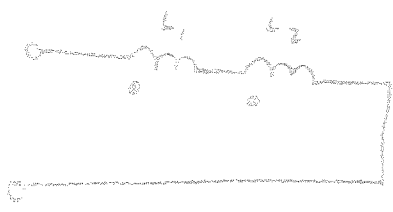

iii

$Z_{eq} = L_1 + L_2$


4

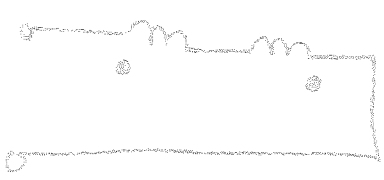

iv

$Z_{eq} = L_1 + L_2 + 2M$


5

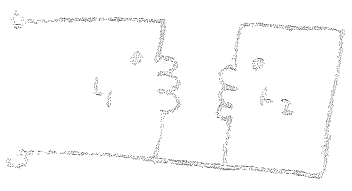

v





$Z_{eq} = \frac{L_1 L_2}{L_1 + L_2 + 2M}$

6



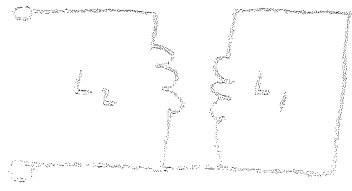


vi

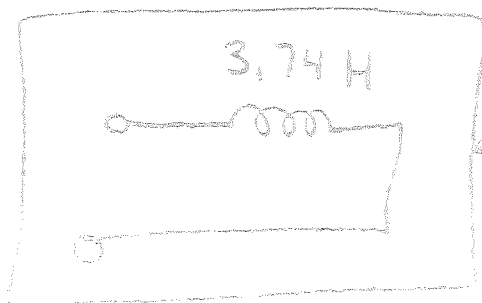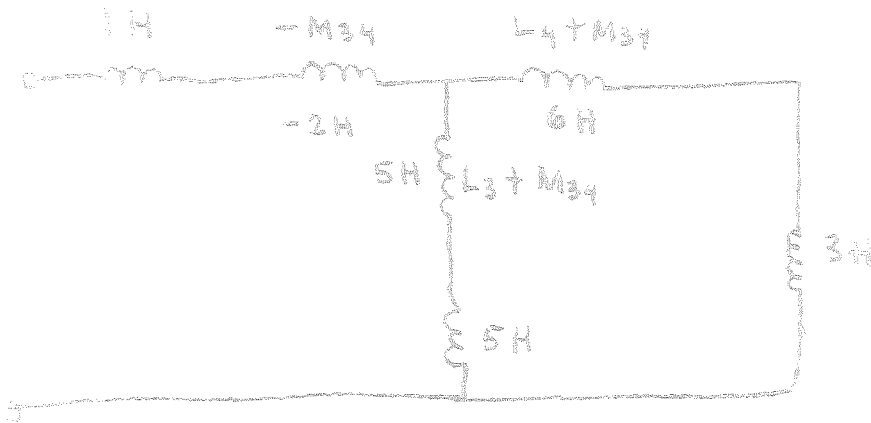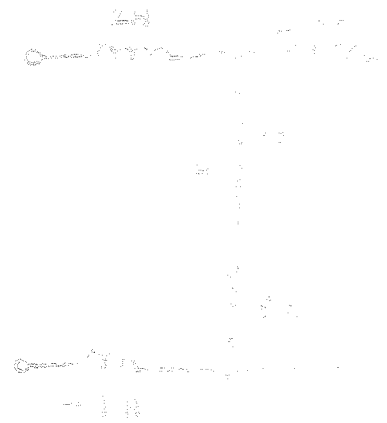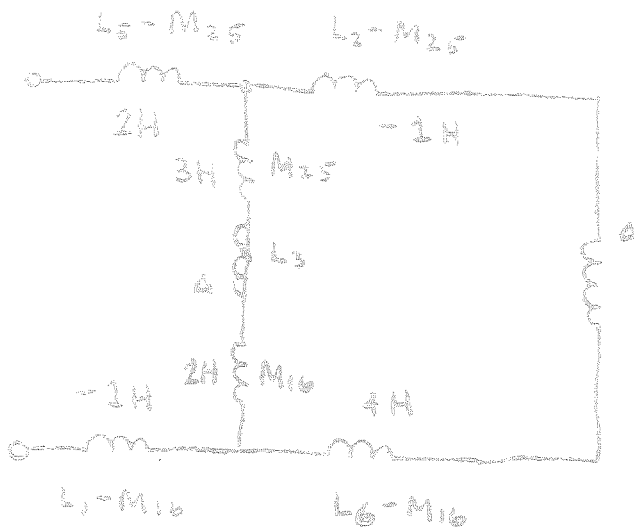$Z_{eq} = \frac{L_1 L_2}{L_1 + L_2 - 2M}$




Equivalent circuit

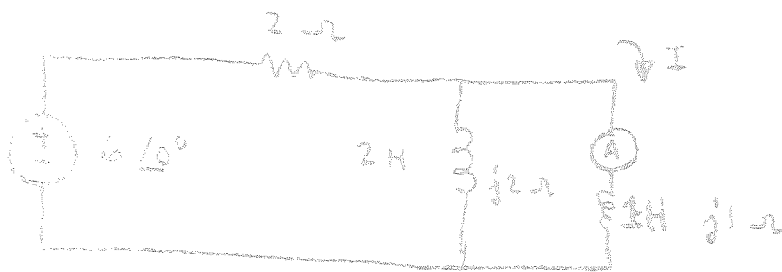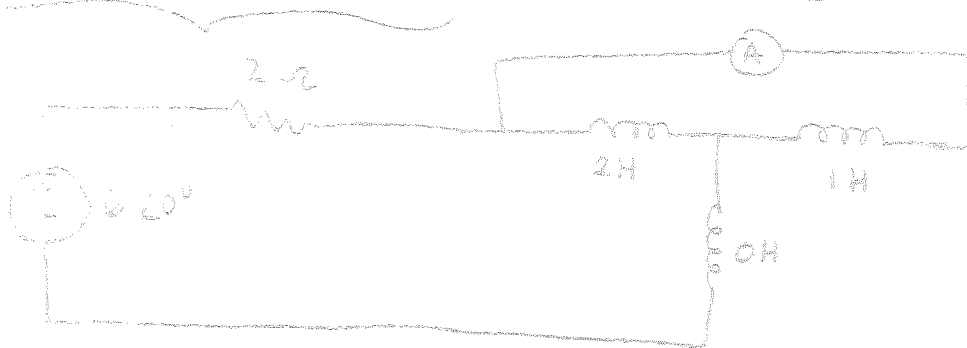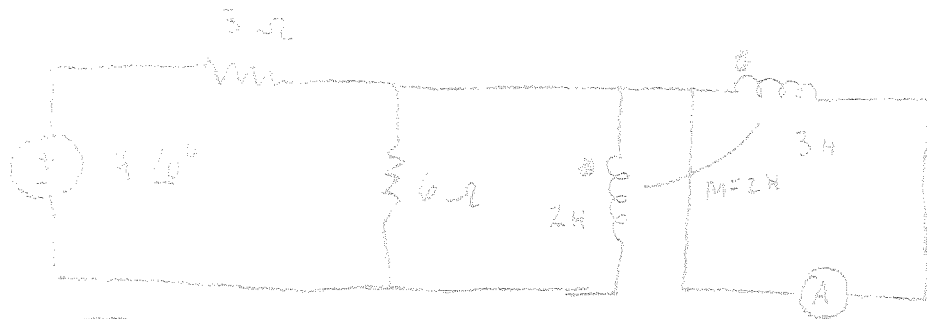

$$I = \left(\frac{6}{2 + j\frac{2}{3}} \right) \frac{j2}{j3} = \frac{4}{2 + j.67} = \frac{4}{2.11 \angle 18.5^\circ}$$

$$= \boxed{1.89 \angle -18.5^\circ \text{ A}}$$

Ammeter reads $\boxed{1.89 \text{ A}}$

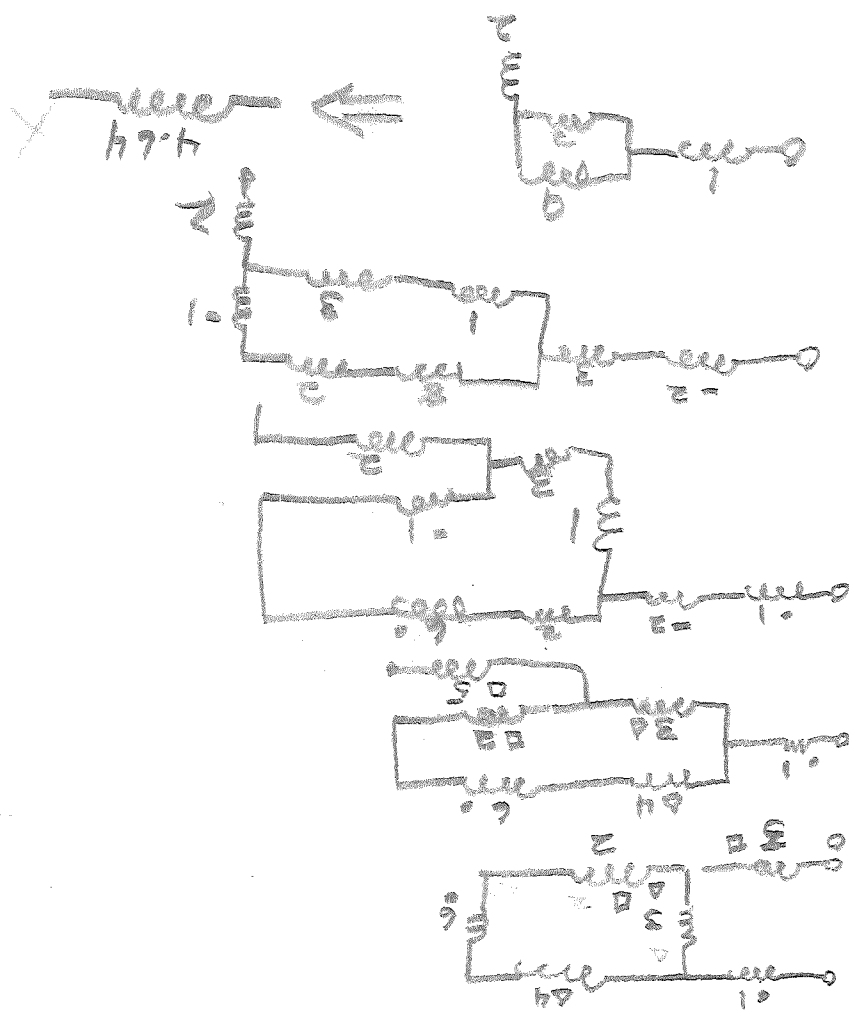

(4)


$$W + \frac{\frac{274 \sqrt{L^2 + 27} + 27}{L^2} + \frac{27 \sqrt{L^2 + 17}}{L}}{1} = 6 \Omega$$

$$W + \frac{W = 27 + \frac{W = 17}{L}}{1} = 6 \Omega$$

$$L \Omega = \sqrt{L^2 + 27} + 17 = 6 \Omega$$




$$L \Omega = \sqrt{L^2 + 27} + 17 = 6 \Omega$$
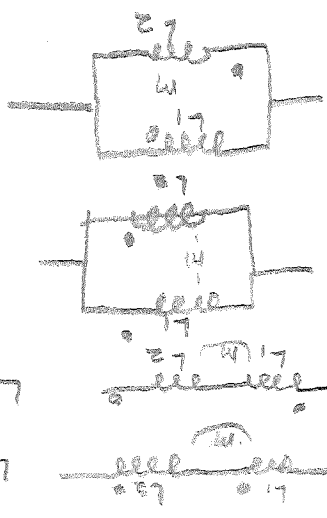
$$L \Omega = \sqrt{L^2 + 27} + 17 = 6 \Omega$$



(5)

2

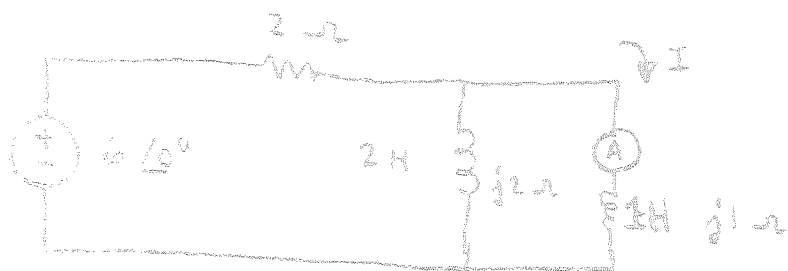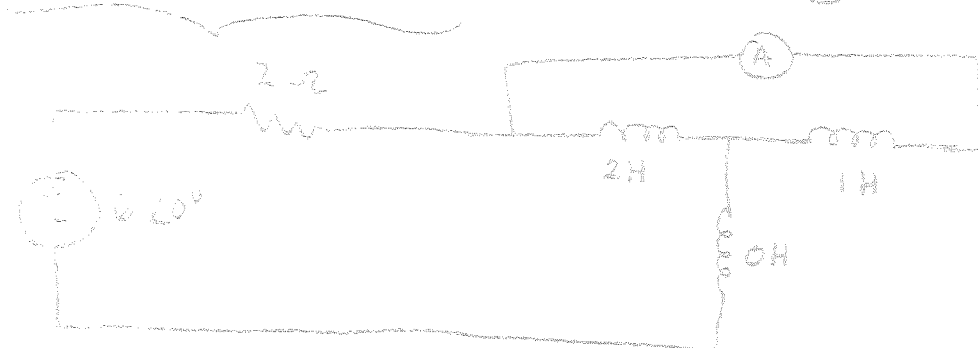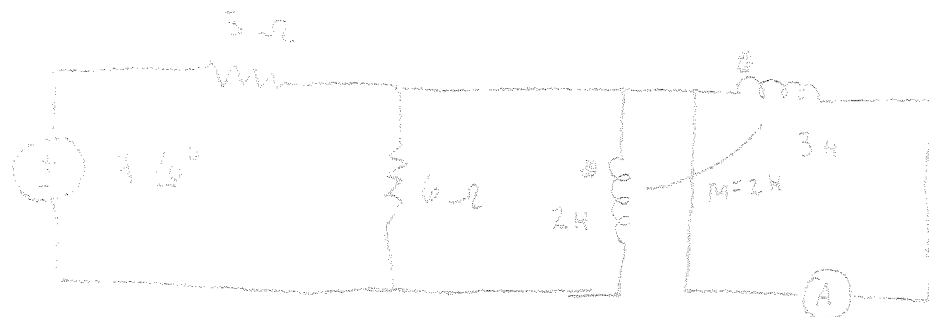


$$I = \left(\frac{6}{2 + j\frac{2}{3}} \right) \frac{j2}{j3} = \frac{4}{2 + j.67} = \frac{4}{2.112}$$

$$= \boxed{1.89 \angle -18.5^\circ \text{ A}}$$

Ammeter reads $\boxed{1.89 \text{ A}}$


Mutual Inductance

A. Concepts

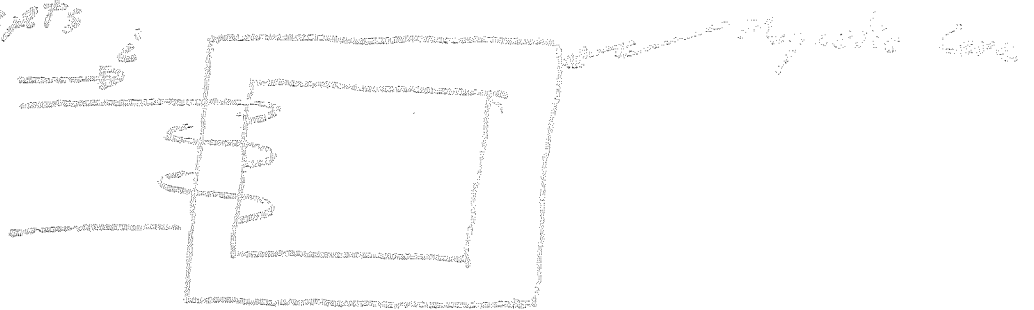

If $i > 0$, the magnetic flux Φ is clockwise in the magnetic core (the "right-hand-rule" is applicable.)

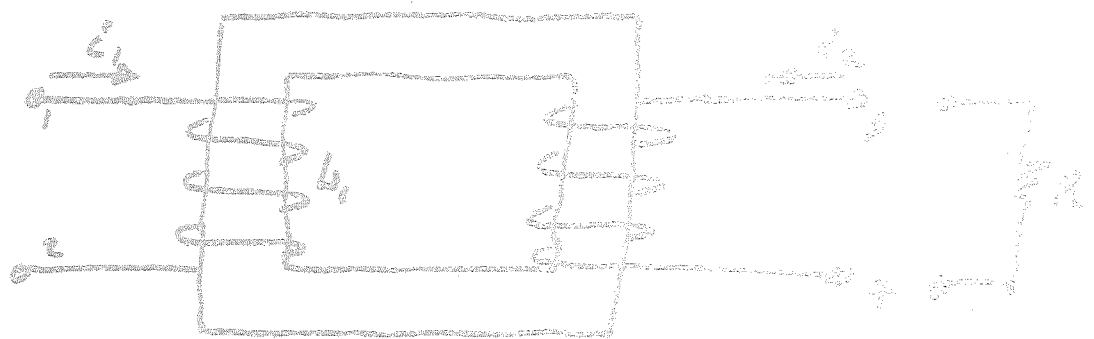If $\frac{di}{dt} > 0$, the top terminal is positive w.r.t. the bottom terminal and the flux in the c.w. direction is increasing.



If $i_L = 0$ (open-circuit) and $\frac{di_1}{dt} > 0$, then terminal 4 is positive w.r.t. term. 3. Thus, when a resistive load is connected between 3 & 4, i_2 flows.

When i_2 is increasing

$$v_{12} = L_1 \frac{di_1}{dt}$$

↑
potential of 1 w.r.t. 2


$$v_{43} = + M \frac{di_2}{dt}$$

↑
Mutual Inductance in 4, 3 direction


When the resistor is connected, the current will cause a flux component in the clockwise direction (right-hand rule) which will tend to decrease the flux caused by the current. A changing i_2 current in the secondary will induce a negative voltage in the primary circuit,

$$v_{12} = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

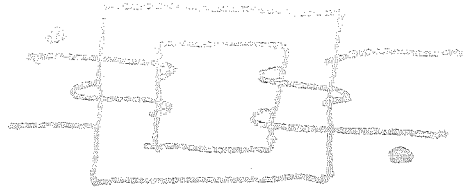where it is assumed that M is the same in both directions



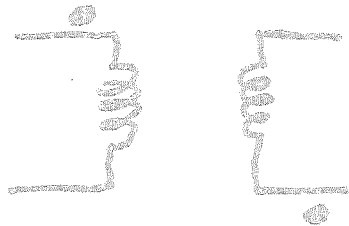Positive currents into the marked terminals produce additive fluxes in the core, with this convention the drawing of the core is not required.



B. Complete system of Equations for Mutual Coupling



$$\left. \begin{aligned} v_1 &= L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} \\ v_2 &= -M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{aligned} \right\} (a)$$

If the positive current sense for both currents - enter (or leave) at the polarity marks, then the M -term has the same sign as the L -term; otherwise the signs are opposite.

Mutual Coupling with Steady-State Sinusoidal Inputs

In the same way that

$$v = L \frac{di}{dt}$$

for the self-inductance leads to

$$V = j\omega L I$$

in phasor notation,

$$v_2 = M \frac{di_1}{dt} \quad \Rightarrow \quad V_2 = j\omega M I_1$$

for mutual inductance.


Thus, Equations (1) become

$$V_1 = j\omega L_1 I_1 - j\omega M I_2$$

$$V_2 = -j\omega M I_1 + j\omega L_2 I_2$$

(2)

Example

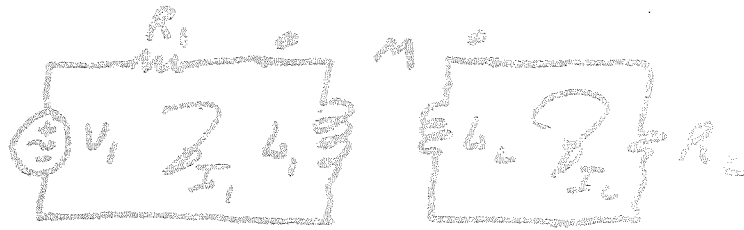

$$V_1 = (R_1 + j\omega L_1) I_1 - j\omega M I_2$$

$$0 = -j\omega M I_1 + (R_2 + j\omega L_2) I_2$$

1. The 8 ft uniform rod AB in Figure 1 weighs 50 lb. A 30 lb weight D is attached to rod AB by a cable that passes over a smooth pulley C. DETERMINE the work done by the two weights as the rod rotates clockwise from a vertical position to the horizontal position shown as dashed lines. Pin A is smooth. (ANS. + 100 ft lb.)

2. The 17 lb block B in Figure 2 slides along a smooth vertical rod under the action of a 50 lb vertical force P. The rod has one end fixed at A and the other end attached to E. The modulus of the spring, K, is 20 lb/ft and its unstretched length is 3 ft. DETERMINE the work done on B during a displacement from $y = 2$ ft to $y = 4$ ft. (ANS. + 29.7 ft lb.)

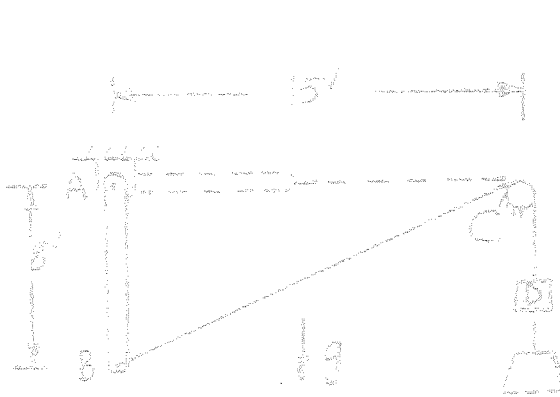


FIGURE 1


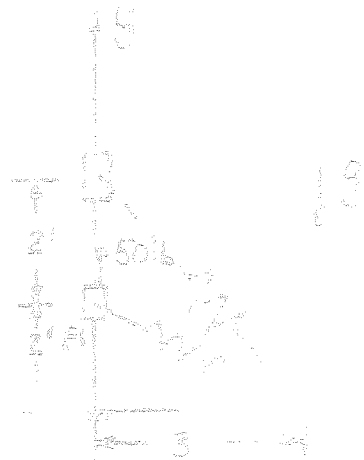


FIGURE 2

Experiment: Sequence Lab

circuit shown below

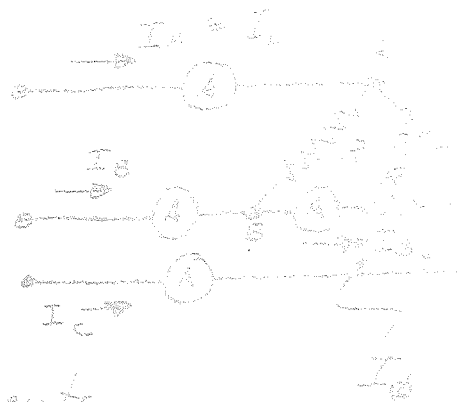cord line currents $I_A, I_B, \& I_C$ and the line-to-line voltage (Assume balanced line voltages).



- Record the phase current I_{BC}
- Verify the $\sqrt{3}$ relationship between I_L and phase currents
- Calculate the total power to the load by assuming phase currents & line voltages

$$P_{total} = 3 I_{\phi} V_{AB} \cos \theta$$

Calculate total power using $P_{total} = \sqrt{3} V_{LL} I_L \cos \theta$ and compare with results of d.

2. Assume ABC sequence for the generated voltages. Calculate the line currents I_A and I_C to show which lamp will be the brightest, lamp A or lamp C.

- Which lamp was brightest in the lab circuit?
- What phase sequence exists in the circuit?


Assume the following

$$V_{AB} = 208 \angle 30^\circ \text{ V}$$

$$V_{BC} = 120 \angle 0^\circ$$

$$V_{CA} = 120 \angle -120^\circ$$

$$V_{CN} = 120 \angle +120^\circ$$

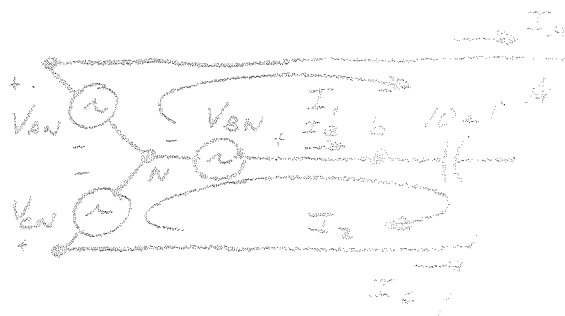

3. The two-wattmeter Method was used to measure the power in a three-phase motor as shown below

FINAL REVIEW

$$1) A = \begin{bmatrix} 1 & 3 \\ 2 & -2 \\ 0 & 4 \end{bmatrix} \quad B = \begin{bmatrix} 3 & -1 \\ 1 & 0 \\ 2 & -1 \end{bmatrix} \quad C = \begin{bmatrix} 1 & 2 & 0 \\ 2 & 1 & 0 \end{bmatrix}$$

$$a) A+B = \begin{bmatrix} 4 & 2 \\ 3 & -2 \\ 2 & 3 \end{bmatrix}$$

$$b) AC = \begin{bmatrix} 1 & 3 \\ 2 & -2 \\ 0 & 4 \end{bmatrix} \begin{bmatrix} 1 & 2 & 0 \\ 2 & 1 & 0 \end{bmatrix} = \begin{bmatrix} 7 & 5 & 0 \\ -2 & 2 & 0 \\ 8 & 4 & 0 \end{bmatrix}$$

$$c) CA = \begin{bmatrix} 1 & 2 & 0 \\ 2 & 1 & 0 \end{bmatrix} \begin{bmatrix} 1 & 3 \\ 2 & -2 \\ 0 & 4 \end{bmatrix} = \begin{bmatrix} 5 & -1 \\ 4 & 4 \end{bmatrix}$$

$$4) \left[\begin{array}{cccc|c} 1 & 1 & 1 & 1 & 0 \\ 1 & 1 & 1 & -1 & 4 \\ 1 & 1 & -1 & 1 & -4 \\ 1 & -1 & 1 & 1 & 2 \end{array} \right] \Rightarrow \left[\begin{array}{cccc|c} 1 & 1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 2 & -4 \\ 0 & 0 & 2 & 0 & 4 \\ 0 & 2 & 0 & 0 & -2 \end{array} \right] \Rightarrow \left[\begin{array}{cccc|c} 1 & 1 & 1 & 1 & 0 \\ 0 & 1 & 0 & 0 & -1 \\ 0 & 0 & 1 & 0 & 2 \\ 0 & 0 & 0 & 1 & -2 \end{array} \right]$$

$$\Rightarrow \left[\begin{array}{cccc|c} 1 & 0 & 0 & 0 & 1 \\ 0 & 1 & 0 & 0 & -1 \\ 0 & 0 & 1 & 0 & 2 \\ 0 & 0 & 0 & 1 & -2 \end{array} \right] \quad \begin{array}{l} x_4 = -2 \\ \therefore x_3 = 2 \\ x_2 = -1 \\ x_1 = 1 \end{array}$$

$$5) \begin{bmatrix} 3 & 4 \\ 1 & 2 \end{bmatrix} \xrightarrow{F_2 \times 2} \begin{bmatrix} 3 & 4 \\ 2 & -4 \end{bmatrix} \xrightarrow{G_{21} (+1)} \begin{bmatrix} 3 & 4 \\ 5 & 0 \end{bmatrix} \xrightarrow{G_{12} (-1)} \begin{bmatrix} 0 & 4 \\ 5 & 0 \end{bmatrix} \xrightarrow{F_1 (\frac{1}{5})} \begin{bmatrix} 0 & 4 \\ 1 & 0 \end{bmatrix} \\ \Rightarrow \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \xrightarrow{E_{12}} \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \therefore \begin{bmatrix} 3 & 4 \\ 1 & 2 \end{bmatrix} \xrightarrow{F_2 (-2)} \xrightarrow{G_{21} (1)} \xrightarrow{G_{12} (-1)} \xrightarrow{F_1 (\frac{1}{5})} \xrightarrow{E_{12}} I$$

$$6) \begin{bmatrix} 1 & 2 & 3 \\ 2 & 3 & 2 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 0 & -2 \\ 0 & +1 & +4 \end{bmatrix} ; \begin{bmatrix} 2 & 3 & 2 \\ 1 & 1 & -1 \end{bmatrix} \Rightarrow \begin{bmatrix} 2 & 4 & 6 \\ 0 & 1 & 4 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 0 & -2 \\ 0 & 1 & 4 \end{bmatrix}$$

FINAL REVIEW

$$1) \left[\begin{array}{cccc|c} 1 & 1 & 2 & 1 & 3 & 1 \\ 2 & -1 & 2 & 2 & 6 & 2 \\ 3 & 2 & -4 & 3 & 9 & 3 \end{array} \right] \Rightarrow \left[\begin{array}{cccc|c} 1 & 0 & 0 & 1 & 3 & 1 \\ 0 & -3 & 6 & 0 & 0 & 0 \\ 0 & -1 & 2 & 0 & 0 & 0 \end{array} \right] \Rightarrow \left[\begin{array}{cccc|c} 1 & 0 & 0 & 1 & 3 & 1 \\ 0 & -1 & 2 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \end{array} \right]$$

$$\therefore \begin{bmatrix} x_1 \\ x_2 \\ x_3 \\ x_4 \\ x_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 2 \\ 1 \\ 0 \\ 0 \end{bmatrix} + x_3 \begin{bmatrix} -1 \\ 0 \\ 0 \\ 1 \\ 0 \end{bmatrix} + x_4 \begin{bmatrix} -3 \\ 0 \\ 0 \\ 0 \\ 1 \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{aligned} x_1 + x_4 + 3x_5 &= 1 \\ x_2 - 2x_3 &= 0 \\ \therefore x_1 &= -x_4 - 3x_5 + 1 \\ x_2 &= 2x_3 \end{aligned}$$

$$2) \quad x - 4y + 5z = 1; \quad 2x - y + 3z = 2; \quad 3x + 2y + z = p$$

$$\left[\begin{array}{ccc|c} 1 & -4 & 5 & 1 \\ 2 & -1 & 3 & 2 \\ 3 & 2 & 1 & p \end{array} \right] \Rightarrow \left[\begin{array}{ccc|c} 1 & -4 & 5 & 1 \\ 0 & 7 & -7 & 0 \\ 0 & 14 & -14 & p-3 \end{array} \right] \Rightarrow \left[\begin{array}{ccc|c} 1 & 0 & 1 & 1 \\ 0 & 1 & -1 & 0 \\ 0 & 0 & 0 & p-3 \end{array} \right]$$

CONSISTENT IFF $p=3$

$$3) \left[\begin{array}{cccc} 3 & 1 & 2 & 4 \\ 5 & 2 & 3 & 6 \\ 4 & 1 & 3 & 6 \\ 5 & 1 & 4 & 8 \end{array} \right] \Rightarrow \left[\begin{array}{cccc} 1 & 0 & 1 & 2 \\ 0 & 1 & -1 & -2 \\ 1 & 0 & 1 & 2 \\ 1 & 1 & 0 & 0 \end{array} \right] \Rightarrow \left[\begin{array}{cccc} 1 & 0 & 1 & 2 \\ 0 & 1 & -1 & -2 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{array} \right] \Rightarrow \left[\begin{array}{cccc} 1 & 0 & 1 & 2 \\ 0 & 1 & -1 & -2 \\ 0 & 1 & -1 & -2 \\ 0 & 0 & 0 & 0 \end{array} \right] \Rightarrow \left[\begin{array}{cccc} 1 & 0 & 1 & 2 \\ 0 & 1 & -1 & -2 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{array} \right]$$

$\therefore \text{RANK} = 2$

$$4) \left[\begin{array}{ccc|ccc} 1 & 2 & 3 & 1 & 0 & 0 \\ 2 & 4 & 5 & 0 & 1 & 0 \\ 3 & 5 & 6 & 0 & 0 & 1 \end{array} \right] \Rightarrow \left[\begin{array}{ccc|ccc} 1 & 2 & 3 & 1 & 0 & 0 \\ 0 & 0 & -1 & -2 & 1 & 0 \\ 0 & -1 & -3 & -3 & 0 & 1 \end{array} \right] \Rightarrow \left[\begin{array}{ccc|ccc} 1 & 0 & -3 & -5 & 0 & 2 \\ 0 & 1 & 3 & 3 & 0 & -1 \\ 0 & 0 & 1 & 2 & -1 & 0 \end{array} \right]$$

$$\Rightarrow \left[\begin{array}{ccc|ccc} 1 & 0 & 0 & 1 & -3 & 2 \\ 0 & 1 & 0 & -3 & 3 & -1 \\ 0 & 0 & 1 & 2 & -1 & 0 \end{array} \right] \Rightarrow A^{-1} = \begin{bmatrix} 1 & -3 & 2 \\ -3 & 3 & -1 \\ 2 & -1 & 0 \end{bmatrix}$$

$$\begin{aligned}
 5) & \begin{vmatrix} x & 3x & 2x \\ e^x & e^x & e^x \\ 2 & 3 & -2 \end{vmatrix} = xe^x \begin{vmatrix} 1 & 3 & 2 \\ 1 & 1 & 1 \\ 2 & 3 & -2 \end{vmatrix} = xe^x \begin{vmatrix} 0 & 2 & 1 \\ 1 & 1 & 1 \\ 0 & 1 & -4 \end{vmatrix} = xe^x \begin{vmatrix} 0 & 0 & 9 \\ 1 & 0 & 5 \\ 0 & 1 & -4 \end{vmatrix} \\
 & = 9xe^x \begin{vmatrix} 0 & 0 & 1 \\ 1 & 0 & 5 \\ 0 & 1 & -4 \end{vmatrix} = 9xe^x \begin{vmatrix} 1 & 0 & 5 \\ 0 & 1 & -4 \end{vmatrix} = 9xe^x
 \end{aligned}$$

$$\begin{aligned}
 a) & \begin{vmatrix} 2 & 2 & -2 \\ 1 & 2 & 3 \\ 2 & 3 & 4 \end{vmatrix} = 2 \begin{vmatrix} 2 & 3 & -2 \\ 3 & 4 & \end{vmatrix} - 2 \begin{vmatrix} 1 & 3 & -2 \\ 2 & 4 & \end{vmatrix} + 2 \begin{vmatrix} 1 & 2 \\ 2 & 3 \end{vmatrix} = 2(-1) + 2(+2) + 2(+1) = 4
 \end{aligned}$$

$$\begin{aligned}
 b) & \begin{vmatrix} 2 & 2 & -2 \\ 1 & 2 & 3 \\ 2 & 3 & 4 \end{vmatrix} = -2 \begin{vmatrix} 1 & 3 \\ 2 & 4 \end{vmatrix} + 2 \begin{vmatrix} 2 & -2 \\ 2 & 4 \end{vmatrix} - 3 \begin{vmatrix} 2 & -2 \\ 1 & 3 \end{vmatrix} = -2(-2) + 2(12) - 3(8) = 4
 \end{aligned}$$

$$\text{COF. OF } a_{12} = - \begin{vmatrix} 1 & 3 \\ 2 & 4 \end{vmatrix} = 2$$

$$\text{COF. OF } a_{22} = \begin{vmatrix} 2 & -2 \\ 2 & 4 \end{vmatrix} = 12$$

FINAL REVIEW

$$1) \begin{bmatrix} 1 & 1 & 2 & 2 \\ 0 & -2 & -3 & -5 \\ 6 & 4 & 9 & 7 \\ -5 & 1 & -1 & 5 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 1 & 2 & 2 \\ 0 & 6 & 9 & 15 \\ 1 & 5 & 8 & 12 \\ 0 & 6 & 9 & 15 \end{bmatrix} \Rightarrow \begin{bmatrix} 0 & 4 & 6 & 10 \\ 0 & 4 & 6 & 10 \\ 1 & 5 & 8 & 12 \\ 0 & 6 & 9 & 15 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} 0 & 2 & 3 & 5 \\ 1 & 5 & 8 & 12 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} \Rightarrow S \text{ IS OF SECOND DIMENSION}$$

$$\begin{bmatrix} 1 & 1 \\ 0 & -2 \\ 6 & 4 \\ -5 & 1 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 0 & 0 \\ 0 & 0 \end{bmatrix} \Rightarrow \vec{a} \neq \vec{b} \text{ ARE LINEARLY IND.}$$

$\therefore \vec{a} \neq \vec{b}$ MAY BE BASIS FUNCTIONS FOR S

$$2) \begin{bmatrix} 1 & 0 & 0 & 3 \\ 1 & 2 & 2 & 5 \\ 1 & 3 & -1 & -2 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 0 & 0 & 3 \\ 0 & 2 & 2 & 2 \\ 0 & 3 & -1 & -5 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 0 & 0 & 3 \\ 0 & 1 & 1 & 1 \\ 0 & 0 & -4 & -8 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} 1 & 0 & 0 & 3 \\ 0 & 1 & 1 & 1 \\ 0 & 0 & 1 & 2 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 0 & 0 & 3 \\ 0 & 1 & 0 & -1 \\ 0 & 0 & 1 & 2 \end{bmatrix}$$

$$\therefore \vec{0} = 3\vec{e}_1 - \vec{e}_2 + 2\vec{e}_3$$

$$4) \begin{bmatrix} 1 & 2 & 3 & 1 \\ -1 & 1 & 1 & 2 \\ 1 & 1 & 2 & 0 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 2 & 3 & 1 \\ 0 & 3 & 4 & 3 \\ 0 & 1 & 1 & 1 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 1 & 2 & 0 \\ 0 & 1 & 1 & 1 \\ 0 & 0 & 1 & 0 \end{bmatrix} \text{ ETC}$$

BY INSPECTION, $\vec{a} = \vec{b} - \vec{a}$

$$4) \begin{matrix} A^T = \\ \end{matrix} \begin{bmatrix} 3 & 1 & 1 & 5 \\ 1 & 0 & 1 & 1 \\ 2 & 1 & 0 & 4 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 0 & 1 & 1 \\ 1 & 0 & 1 & 1 \\ 2 & 1 & 0 & 4 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 0 & 1 & 1 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 0 & 1 & 1 \\ 0 & 1 & -2 & 2 \\ 0 & 0 & 0 & 0 \end{bmatrix} \therefore \text{rank } A = 2$$

$$A = \begin{bmatrix} 3 & 1 & 2 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \\ 5 & 1 & 4 \end{bmatrix} \Rightarrow \begin{bmatrix} 2 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \\ 2 & 0 & 2 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 0 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \\ 1 & 0 & 1 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 1 & 0 \\ 1 & 0 & 1 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \therefore \text{rank } A = 2$$

$$A\vec{x} = 0 \Rightarrow \text{DIM. SPACE} = 3 - 2 = 1$$

$$A^T\vec{y} = 0 \Rightarrow \text{DIM. SPACE} = 4 - 2 = 2$$

$$5) \begin{bmatrix} 2 & 1 & 0 & 3 & 0 & 1 \\ 1 & 2 & 0 & 0 & 1 & 2 \\ 3 & 0 & 3 & 2 & 2 & 3 \\ 0 & 0 & -1 & 1 & -2 & -1 \end{bmatrix} \begin{bmatrix} \alpha_1 \\ \alpha_2 \\ \alpha_3 \\ -\beta_1 \\ -\beta_2 \\ -\beta_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} 1 & -1 & 3 & -1 & 2 & 2 \\ 0 & -3 & 0 & 3 & -2 & -3 \\ 0 & 0 & 1 & -1 & 2 & 1 \\ 1 & 2 & 0 & 0 & 1 & 2 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 0 & 0 & 0 & -19 & 0 \\ 0 & 1 & 0 & 0 & 29 & 1 \\ 0 & 0 & 1 & 0 & 5 & 1 \\ 0 & 0 & 0 & 1 & 3 & 0 \end{bmatrix}$$

$$\alpha_1 = 19\beta_2; \alpha_2 = 29\beta_2 + \beta_3; \alpha_3 = 5\beta_2 + \beta_3; \beta_1 = -3\beta_2$$

$$\vec{w} = \alpha_1 a + \alpha_2 b + \alpha_3 c = \beta_1 d + \beta_2 e + \beta_3 f$$

$$\vec{w} = (-19\beta_2)\vec{a} + (29\beta_2 + \beta_3)\vec{b} + (5\beta_2 + \beta_3)\vec{c}$$

$$= \beta_1(0) + \beta_2(29\vec{b} - 19\vec{a} + 5\vec{c}) + \beta_3(\vec{b} + \vec{c})$$

BASIS FOR SNT (SECOND DIMENSION)

$$v_1 = 29\vec{b} - 19\vec{a} + 5\vec{c}$$

$$v_2 = \vec{b} + \vec{c}$$

FINAL REVIEW

$$A = \begin{bmatrix} 0 & -2 & 2 \\ -3 & 1 & 3 \\ -1 & 1 & 3 \end{bmatrix} \quad \text{WITH EIGEN VALUES } -2 \ 2 \ 4$$

FOR $\lambda = -2$

$$\begin{bmatrix} 2 & -2 & 2 \\ -3 & 3 & 3 \\ -1 & 1 & 5 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & -1 & 1 \\ -1 & 1 & 1 \\ -1 & 1 & 5 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & -1 & 1 \\ 0 & 0 & 1 \\ 0 & 0 & 0 \end{bmatrix} \quad \begin{matrix} z=0 \\ x=y \\ \therefore \vec{v}_1 = \begin{bmatrix} 1 \\ 1 \\ 0 \end{bmatrix} \alpha_1 \end{matrix}$$

FOR $\lambda_2 = 2$

$$\begin{bmatrix} -2 & -2 & 2 \\ -3 & -1 & 3 \\ -1 & 1 & 1 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 1 & -1 \\ -3 & -1 & 3 \\ 0 & 2 & 0 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 1 & -1 \\ 0 & 2 & 0 \\ 0 & 0 & 0 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 0 & -1 \\ 0 & 1 & 0 \\ 0 & 0 & 0 \end{bmatrix} \therefore V_2 = \begin{bmatrix} 1 \\ 0 \\ 1 \end{bmatrix} \alpha_2$$

FOR $\lambda_3 = 4$

$$\begin{bmatrix} -4 & -2 & 2 \\ -3 & -3 & 3 \\ -1 & 1 & -1 \end{bmatrix} \Rightarrow \begin{bmatrix} -2 & -1 & 1 \\ 1 & 1 & -1 \\ 0 & 2 & -2 \end{bmatrix} \Rightarrow \begin{bmatrix} 0 & 1 & -1 \\ 1 & 1 & -1 \\ 0 & 0 & 0 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & -1 \\ 0 & 0 & 0 \end{bmatrix} \therefore V_3 = \begin{bmatrix} 0 \\ 1 \\ 1 \end{bmatrix} \alpha_3$$

$$\Rightarrow P = \begin{bmatrix} 1 & 1 & 0 \\ 1 & 0 & 1 \\ 0 & 1 & 1 \end{bmatrix} \Rightarrow P^T = \begin{bmatrix} 1 & 1 & 0 \\ 1 & 0 & 1 \\ 0 & 1 & 1 \end{bmatrix} \Rightarrow \text{adj } P^T = \begin{bmatrix} -1 & -1 & 1 \\ -1 & 1 & -1 \\ 1 & -1 & -1 \end{bmatrix}$$

$$\det P = -2$$

$$\Rightarrow -\frac{1}{2} \begin{bmatrix} 1 & 1 & 0 \\ 1 & 0 & 1 \\ 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} -1 & -1 & 1 \\ -1 & 1 & -1 \\ 1 & -1 & -1 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \Rightarrow P^{-1} = -\frac{1}{2} \begin{bmatrix} -1 & -1 & 1 \\ -1 & 1 & -1 \\ 1 & -1 & -1 \end{bmatrix}$$

$$P^{-1}AP = -\frac{1}{2} \begin{bmatrix} -1 & -1 & 1 \\ -1 & 1 & -1 \\ 1 & -1 & -1 \end{bmatrix} \begin{bmatrix} 0 & -2 & 2 \\ -3 & 1 & 3 \\ -1 & 1 & 3 \end{bmatrix} \begin{bmatrix} 1 & 1 & 0 \\ 1 & 0 & 1 \\ 0 & 1 & 1 \end{bmatrix}$$

$$= -\frac{1}{2} \begin{bmatrix} 2 & 2 & -2 \\ -2 & 2 & -2 \\ 4 & -4 & -4 \end{bmatrix} \begin{bmatrix} 1 & 1 & 0 \\ 1 & 0 & 1 \\ 0 & 1 & 1 \end{bmatrix} = \begin{bmatrix} -1 & -1 & 1 \\ 1 & -1 & -1 \\ 2 & 2 & 2 \end{bmatrix} \begin{bmatrix} 1 & 1 & 0 \\ 1 & 0 & 1 \\ 0 & 1 & 1 \end{bmatrix}$$


$$= \begin{bmatrix} -2 & 0 & 0 \\ 0 & 2 & 0 \\ 0 & 0 & 4 \end{bmatrix}$$

E. Sci 1

II

E. SCI. II

	1	2	3	4	5	6	7	8	9
	8:50	8:45	9:40	10:35	11:30	12:25	1:20	2:15	3:10
MON				PHYS V RAL C 126	ELECT POS DOH		HUMAN. VI AUD		E. SCI. II →
TUES							HUM II OV A 205		E. SCI. II D-132
WED	ELECTRONICS LAB				ELECT POS DOH	E. SCI. II DOH	HUM III OV A 205		E. SCI. II A 124
THUR				PHYS V RAL C 126	E. SCI. SOME- TIMES		HUM III OV A 205	PHYS V LAB PRM	A-205
FRI				PHYS V RAL C 126	ELECT POS DOH				

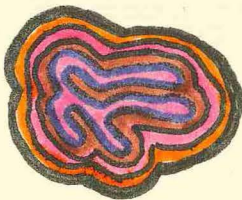

4-1-70


I METHODS OF REPRESENTING SINUSOIDS

PROPERTIES:

- 1) AMPLITUDE
- 2) FREQUENCY
- 3) PHASE

LET FREQUENCY BE UNDERSTOOD

II) PHASOR

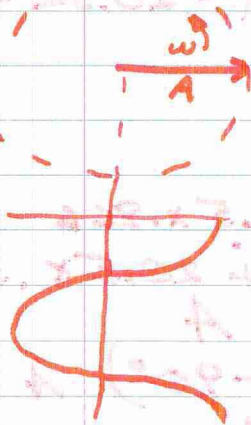

SIDE YIELDS SIMPLE HARMONIC MOTION

PHASOR CAN REPRESENT SINUSOID:

$$v(t) = A \cos \omega t$$



$$v(t) = A \cos(\omega t + \phi)$$



III) A) TIME FUNCTION \rightarrow PHASOR (STILL)
 PHASOR \rightarrow COMPLEX #


$$B) v(t) = A \cos(\omega t + \phi) \rightarrow \sqrt{A} \angle \phi$$

$$\rightarrow A \angle \phi = A \cos \phi + j A \sin \phi$$

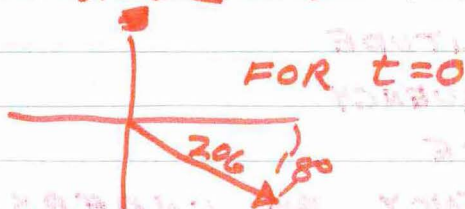EXAMPLE:


$$1) v(t) = 206 \cos(377t - 18^\circ) \text{ V}$$

$$\dot{V} = 206 \angle -18^\circ \text{ V}$$



$$2) v(t) = -20.5 \cos(\omega t + 30^\circ) \text{ V}$$
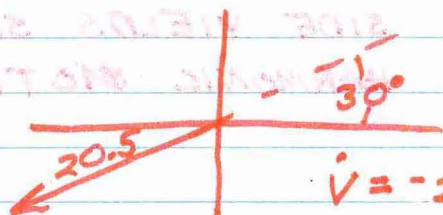
$$\dot{V} = -20.5 \angle 30^\circ \text{ V} (= 20.5 \angle 210^\circ \text{ V})$$




$$\dot{V} = -20.5 \times 0.866$$

$$-j 20.5 \times 0.5$$

$$3) i(t) = 10 \sin 10t \text{ A}$$

$$= 10 \cos(10t - 90^\circ) \text{ A}$$
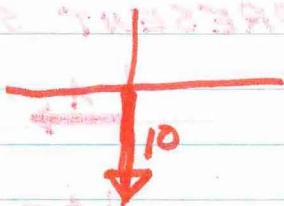
$$\dot{I} = 10 \angle -90^\circ \text{ A}$$



1) CURRENT PHASORS HAVE

CLOSED HEADS

2) VOLTAGE PHASORS HAVE

OPEN HEADS


3) INCLUDE UNITS ON EQUATIONS

4) PHASORS CAPITALIZED WITH
DOTS ON 'EM


$$x = A \sin(\omega t + \phi) = A \cos(\omega t + \phi - 90^\circ)$$

$$\dot{x} = A \angle \phi - 90^\circ$$

EX)

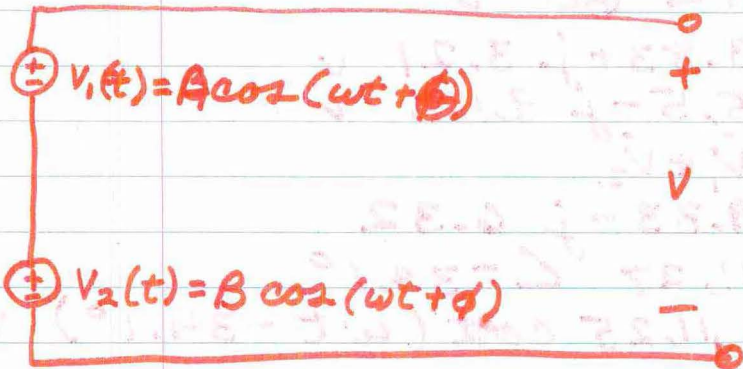
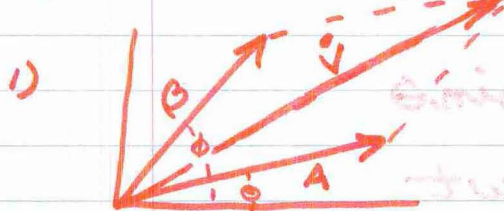
$$\dot{V}_1 = A \angle \theta \quad \dot{V}_2 = B \angle \phi$$



$$2) \dot{V}_1 = A \angle \theta; \dot{V} = A \cos \theta + j A \sin \theta$$

$$\dot{V}_2 = B \angle \phi; \dot{V} = B \cos \phi + j B \sin \phi$$

$$\dot{V} = \dot{V}_1 + \dot{V}_2 = A \cos \theta + B \cos \phi + j (A \sin \theta + B \sin \phi)$$

$$= C \angle \gamma$$

$$C \angle \gamma = \sqrt{(A \cos \theta + B \cos \phi)^2 + j^2 (A \sin \theta + B \sin \phi)^2}$$

$$\angle \tan^{-1} (\text{MESS}) \frac{A \sin \theta + B \sin \phi}{A \cos \theta + B \cos \phi}$$

EXAMPLE

$$V_1(t) = 5 \cos(\omega t + 40^\circ) \text{ V}$$

$$V_2(t) = 11 \sin(\omega t + 30^\circ) \text{ V}$$

$$\dot{V}_1 = 5 \angle 40^\circ \text{ V}$$

$$\dot{V}_2 = 11 \angle -80^\circ \text{ V}$$

$$\dot{V}_1 = 3.83 + j 3.21 \text{ V}$$

$$\dot{V}_2 = 5.5 - j 9.53 \text{ V}$$

$$\dot{V} = \dot{V}_1 + \dot{V}_2$$

$$= 9.33 - j 6.32$$


$$= 11.27 \angle -34.1^\circ$$

$$V(t) = 11.25 \cos(\omega t - 34.1^\circ) \text{ V}$$

$$\frac{e^{j\theta} + e^{-j\theta}}{2} = \cos\theta$$

$$\frac{e^{j\theta} - e^{-j\theta}}{2j} = \sin\theta$$

$$\theta = \omega t$$

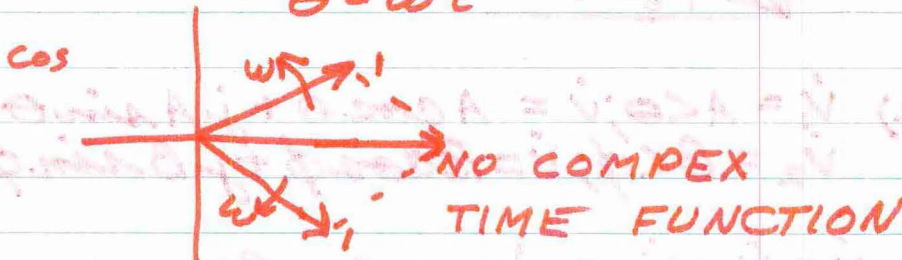


SUMMATION IS ALWAYS REAL
GOES BACK AND FORTH

DIR. OF PH.

$$x(t) = X \cos(\omega t + \theta) \Rightarrow \dot{x} = -X \sin \theta$$

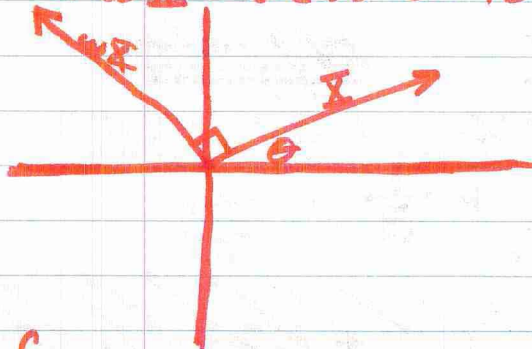
$$x'(t) = -\omega X \sin(\omega t + \theta) \\ = \omega X \cos(\omega t + \theta + 90^\circ) \Rightarrow \dot{x} = \omega X \angle \theta + 90^\circ$$



II) ∫ OF PHAS

$$x(t) = A \cos(\omega t + \theta) \\ \int_{-\infty}^t x(\lambda) d\lambda = \frac{A}{\omega} \cos(\omega t + \theta - 90^\circ)$$

4-7-70

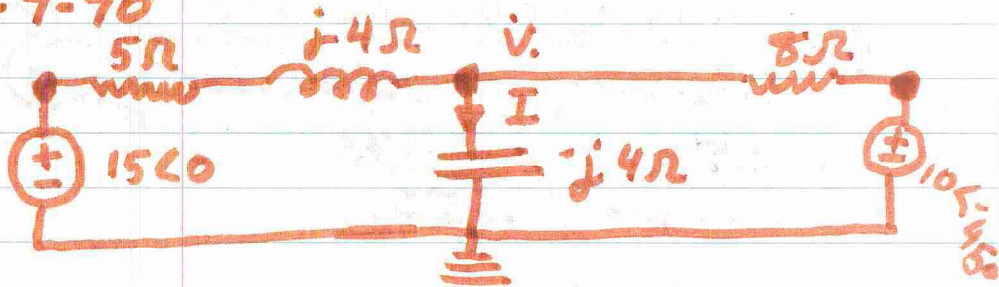

TO GET I, SOLVE FOR V ≠
USE OHM'S LAW

$$\frac{15 \angle 0^\circ - V}{5 + j4} + \frac{10 \angle 45^\circ - V}{8} + \frac{0 - V}{-j4} = 0$$

$$\frac{15 \angle 0^\circ}{5 + j4} + \frac{10 \angle 45^\circ}{8} = V \left(\frac{1}{5 + j4} + \frac{1}{8} - \frac{1}{j4} \right)$$

CONT

$$\hat{V} = \frac{15 \angle 0^\circ}{5 + 4j} + \frac{10 \angle -45^\circ}{8}$$

$$\frac{1}{5 + 4j} + \frac{1}{8} - \frac{1}{4j}$$

$$= \frac{15 \angle 0^\circ}{6.4 \angle 38.6^\circ} + \frac{1.25 \angle -45^\circ}{8}$$

$$\frac{1}{6.4 \angle 38.6^\circ} + \frac{1}{8} - \frac{1}{4j}$$

~~$$= 2.38 \angle -38.6^\circ + 1.25 \angle -45^\circ$$~~

~~$$\hat{V} =$$~~

$$\hat{V} = \frac{(1.86 - j1.46) + (.885 - j.885)}{(.0103 - j.0982) + (.125 + j.25)}$$

$$= \frac{2.745 - j2.345}{.228 + j.152}$$


$$= \frac{3.56 \angle -41.2^\circ}{.274 \angle 33.7^\circ}$$

$$= 13 \angle -74.9^\circ$$

$$\hat{I} = \frac{13 \angle -74.9^\circ}{4 \angle -90^\circ}$$

$$= 3.25 \angle 15.1^\circ \text{ AMPS}$$

4-8-70

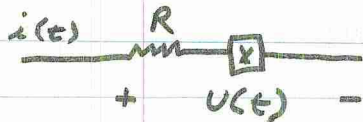

$$v(t) = V \cos \omega t$$

$$\tilde{z} = R + jX = Z \angle \theta_z$$

$$v(t) = V \cos \omega t \Rightarrow \tilde{v} = V \angle 0^\circ$$

$$\tilde{i} = \tilde{v} / \tilde{z} = I \angle -\theta_z, \text{ WHERE } I = V/Z$$

$$i(t) = I \cos(\omega t - \theta_z)$$

POWER $p(t) = v(t)i(t) = VI \cos \omega t \cos(\omega t - \theta_z)$

$\dot{p} \Leftrightarrow \text{NEVER}$

$$p(t) = VI \cos \omega t (\cos \omega t \cos \theta_z + \sin \omega t \sin \theta_z)$$

TO FIND AVERAGE POWER

$$P_{\text{AVE}} = \int_{\omega t=0}^{2\pi} p(t) d(\omega t)$$

$$P_{\text{AVE}} = \frac{VI}{2\pi} \int_0^{2\pi} \cos \theta_z \cos^2 \omega t d(\omega t)$$

$$+ \frac{VI}{2\pi} \int_0^{2\pi} \sin \theta_z \sin \omega t \cos \omega t d(\omega t)$$

$$= \frac{VI \cos \theta_z}{2\pi} \int_0^{2\pi} \frac{1 + \cos 2\omega t}{2} d(\omega t)$$

$$+ \frac{VI \sin \theta_z}{2\pi} \int_0^{2\pi} \frac{\sin 2\omega t}{2} d(\omega t)$$

$$= \frac{VI \cos \theta_z}{2\pi} \int_0^{2\pi} \frac{1 + \cos 2\omega t}{2} d(\omega t)$$

$$= \frac{VI \cos \theta_z}{2\pi} \Rightarrow P_{\text{AV}} = \frac{VI \cos \theta_z}{2}$$


$\cos \theta_z \Rightarrow$ POWER FACTOR

$$P = \frac{V}{\sqrt{2}} \frac{I}{\sqrt{2}} \cos \theta_z$$
$$= V_{\text{EFF}} I_{\text{EFF}} \cos \theta_z$$

$$VI \cos \theta_z \Rightarrow V_{\text{RMS}}, I_{\text{RMS}}$$


$$\frac{VI \cos \theta_z}{2} \Rightarrow V_{\text{MAX}}, I_{\text{MAX}}$$

THE POWER TRIANGLE

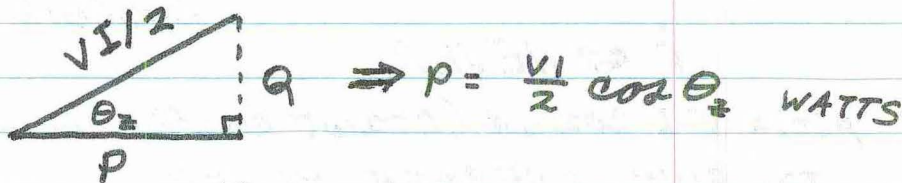

$$Q = \frac{VI}{2} \sin \theta_z$$

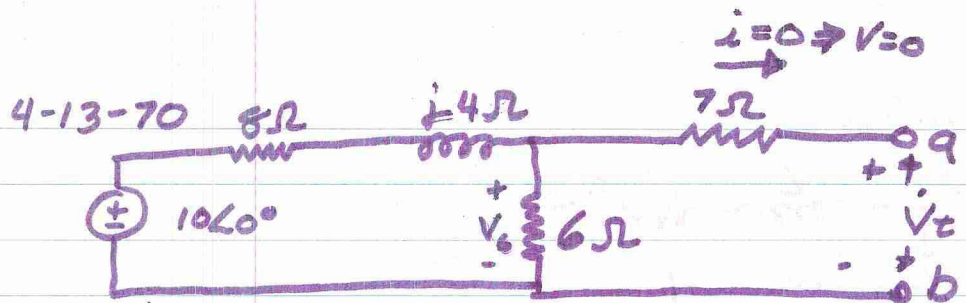Q IS CALLED REACTIVE POWER,
MEASURED IN VARs
(VOLT AMPERE REACTIVE)



$$V_o = \frac{6}{6+j4+8} \cdot 10\angle 0^\circ$$

$$= \frac{60\angle 0^\circ}{14+j4} = \frac{60\angle 0^\circ}{14.55\angle 15.95^\circ}$$

$$= 4.13\angle -15.95^\circ \text{ V}$$

REPLACE V.S. BY SHORT CIRCUIT

$$Z_T = 7 + \frac{1}{\frac{1}{6} + \frac{1}{8+j4}}$$


$$= 7 + \frac{6(8+j4)}{14+j4}$$

$$= 7 + \frac{6(8.93\angle 26.6^\circ)}{14.55\angle 15.95^\circ}$$


$$= 7 + 3.68\angle 10.65^\circ$$

$$= 7 + 3.62 + j.68$$

$$= 10.62 + j.68$$

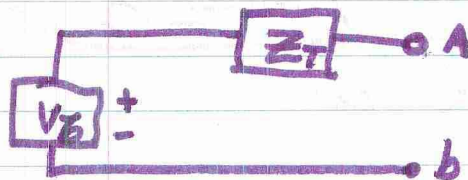

4-15-70

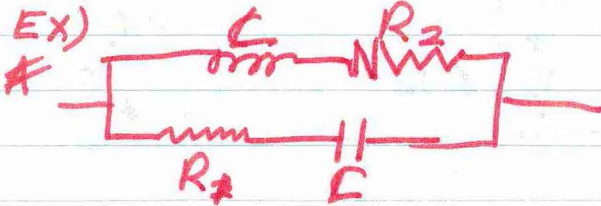

FIND ω SUCH THAT Z_{eq} IS REAL

$$\begin{aligned} A) Z &= \frac{(R_1 + \frac{1}{j\omega C})(R_2 + j\omega L)}{R_1 + R_2 + j\omega L + \frac{1}{j\omega C}} \\ &= \frac{(1 + j\omega R_1 C)(R_2 + j\omega L)}{1 - \omega^2 LC + j\omega C(R_1 + R_2)} \\ &= \frac{R_2 + j\omega R_1 C L + j\omega R_1 R_2 C + \omega^2 L C}{1 - \omega^2 LC + j\omega C(R_1 + R_2)} \end{aligned}$$

WILL BE REAL WHEN
 $\angle \text{NUM} = \angle \text{DEN}$

$$\theta_N = \theta_D$$

$$\tan \theta_N = \tan \theta_D$$

$$\frac{\omega R_1 R_2 C + \omega L}{R_2 - \omega^2 R_1 C L} = \frac{\omega C(R_1 + R_2)}{1 - \omega^2 LC}$$

SOLVE FOR ω

B) $R_1 C$ ADMITTANCE

$$\frac{1}{R_1 + \frac{1}{j\omega C}} = \frac{j\omega C}{1 + j\omega C R_1} \left(\frac{1 + j\omega R_1 C}{1 - j\omega R_1 C} \right)$$

$$= \frac{\omega^2 R_1 C^2 + j \omega C}{1 + \omega^2 R_1^2 C^2}$$

L.L ADMITTANCE

$$\frac{R_2 - j \omega L}{R_2^2 + \omega^2 L^2}$$


$$Y_{eq} = \text{sum} = G + jB \leftarrow \text{SUSCEPTANCE}$$

WANT $B = 0$

$$\frac{\omega C}{1 + \omega^2 R_1^2 C^2} = \frac{\omega L}{R_2^2 + \omega^2 L^2}$$


$$\omega^2 = \frac{L^2 C R_2^2}{C L^2 - L R_1^2 C^2}$$

POWER (SEE HANDOUT)

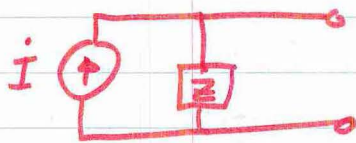


$$P_{MAX} = \frac{|\dot{Z}_g \dot{I}|^2}{4 R_g}$$

(I IS RMS)

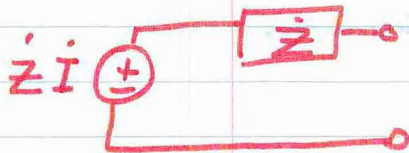

(OVER)

EX)

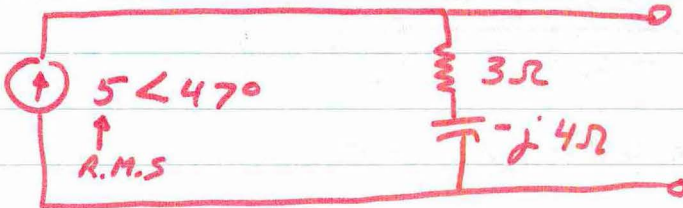

WHAT IS P_{MAX}



~~$$P_{MAX} = \frac{(3-j4)^2 (5/\sqrt{2})^2}{(4)(3)}$$~~


$$|Z_g| = 5$$

$$\therefore P_{MAX} = \frac{(5 \cdot 5)^2}{4 \cdot 3} = 32.08 \text{ WATTS}$$

4-16-70

FIND PWR MAX AT Z_L

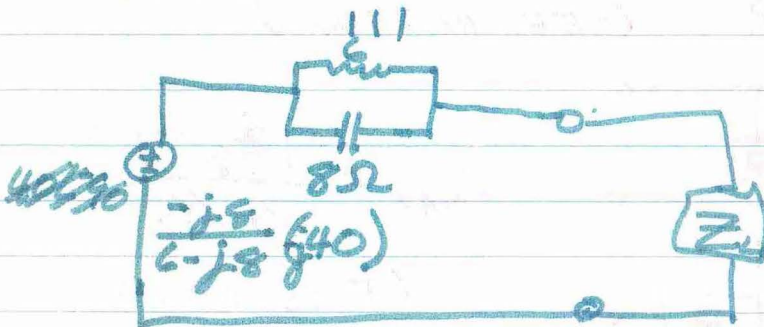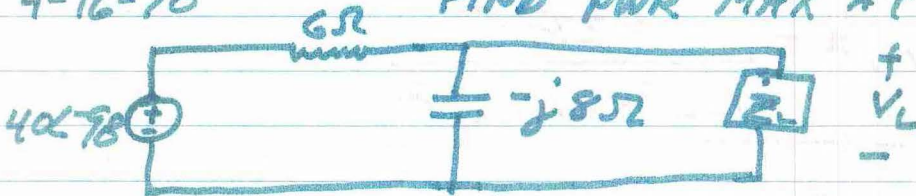

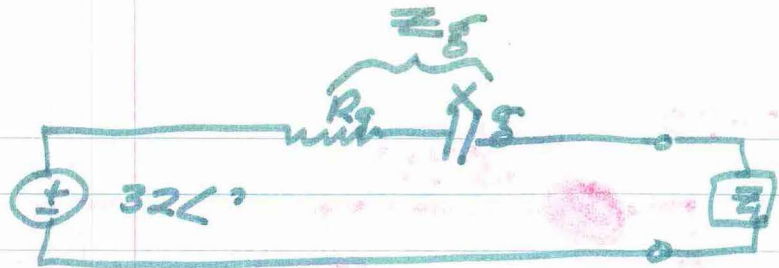


$$Z_g = \frac{6(-j8)}{6-j8} = \frac{48\angle-90^\circ}{10\angle-53.1^\circ}$$

$$= 4.8\angle-36.9^\circ$$

$$= 3.84 - j2.88$$

$$\therefore Z_L = 4.8\angle36.9^\circ = 3.84 + j2.88\Omega$$

$$P_{MAX} = \frac{|V_g|^2}{4R_g} = \frac{32^2}{4 \times 3.84} = 66.7 \text{ WATTS}$$

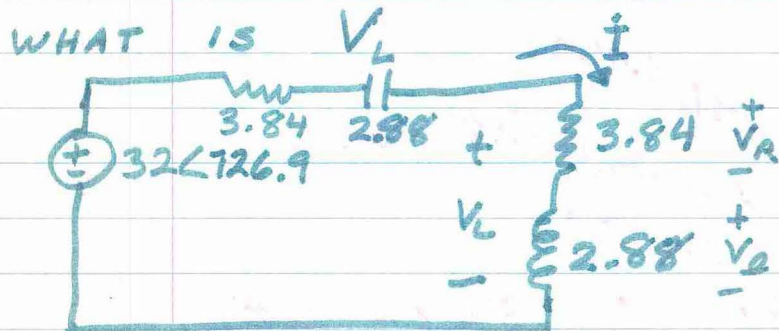


$$\dot{V}_L = I Z_L$$

$$I = \frac{32}{7.68} = 4.17$$

$$V_L = 2.88 \times 4.17 = 12$$


$$V_R = 3.84 \times 4.17 = 16$$

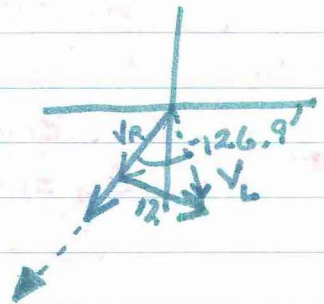

$$V_L = 20\angle-90^\circ \text{ V}$$

4-20-70

X-12)

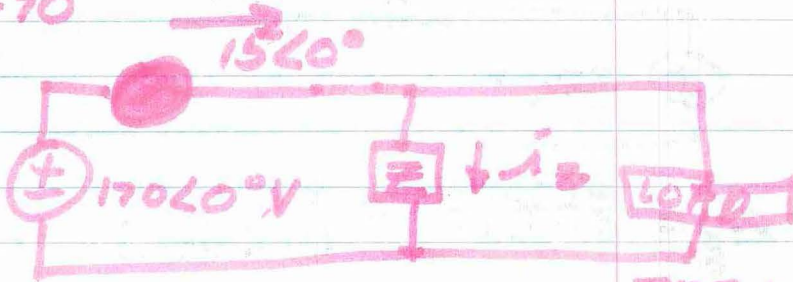


700 WATTS
.8 POWER
FACTOR

(LAGGING
→ INDUCTIVE)


$$P_{\text{GEN}} = (170) \cdot 15 = 2550 \text{ WATT}$$

POWER Δ FOR THE LOAD

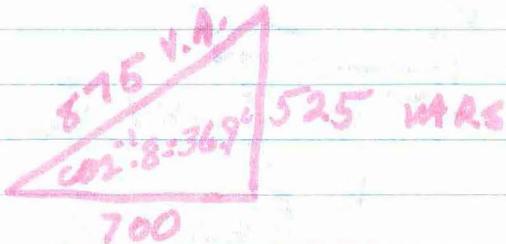

POWER Δ FOR GEN
2550 W

POWER Δ FOR Z
 $2550 - 700 = 1850$

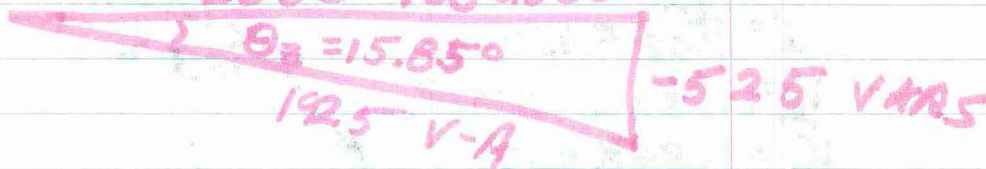

(CONT)



$$P = V_1 \cos \theta_2$$

$$I_2 = \frac{1850}{170 \times 963} = 11.3 \text{ A}$$


$$I_2 = 11.3 \angle 15.85^\circ$$

$$Z = \frac{V}{I} = \frac{170}{11.3} = 15.05 \Omega$$

$$= 15.05 \angle 15.85^\circ$$

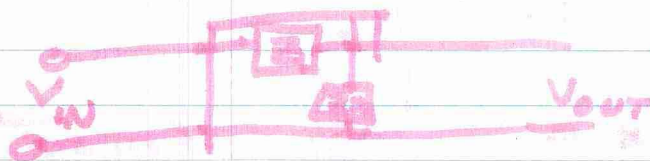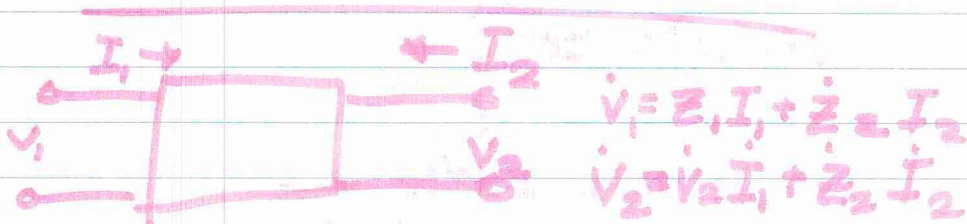

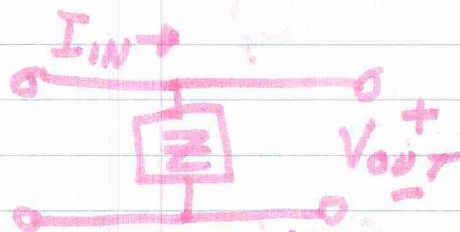
$$\frac{V_{OUT}}{V_{IN}} = H = \frac{Z_2}{Z_1 + Z_2} = F(f) (= F(\omega))$$



$$H(\omega) = \frac{V_{OUT}}{I_{IN}} = Z(\omega)$$

THINK OF INPUT & OUTPUT

EX)

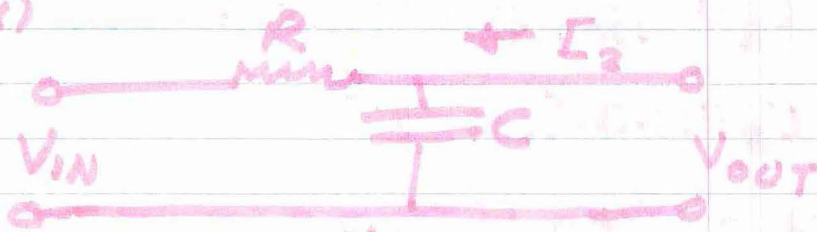

$$H(\omega) = \frac{V_{IN}}{V_{OUT}} \Big|_{I_2=0}$$

$$H(\omega) = \frac{Z_C}{Z_R + Z_C}$$

$$= \frac{1}{R + j\omega C}$$

$$= \frac{1}{1 + j\frac{\omega}{\omega_0}} \quad (\omega_0 = \frac{1}{RC})$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_0})^2}}$$

$$\theta_H = \tan^{-1} \frac{\omega}{\omega_0}$$


FOR LOW ω (SAY $\omega < 0.1\omega_0$)

$$\sqrt{1 + (\frac{\omega}{\omega_0})^2} \approx 1; \quad \theta_H \approx \frac{\omega}{\omega_0}$$

HIGH FREQ. RES
(SAY $\omega > 10\omega_0$)

$$|H(\omega)| \approx \frac{1}{\frac{\omega}{\omega_0}} = \frac{\omega_0}{\omega}$$

HAVE INVENTED THE
'LOW PASS FILTER'

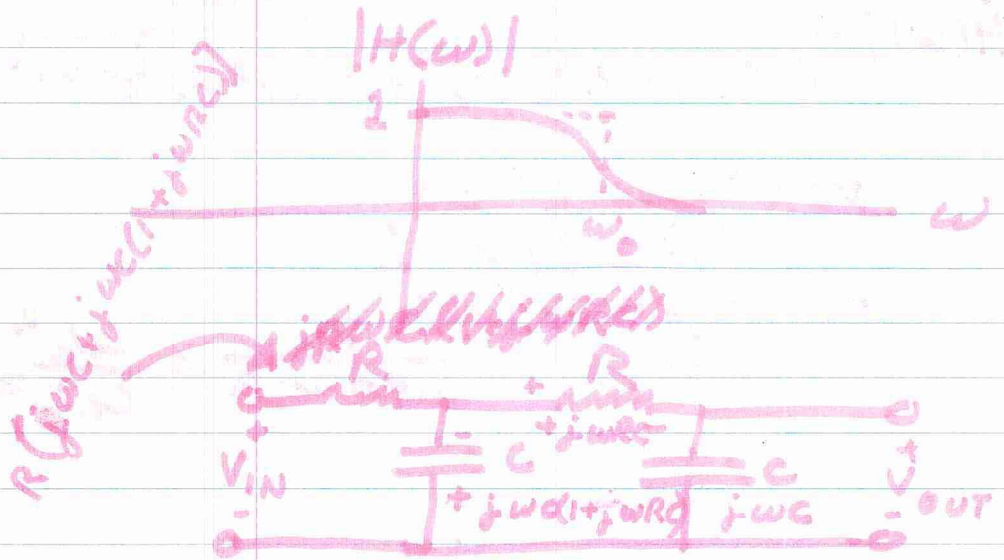

ASUME $V_{OUT} \neq$ WORK BACK
 $V_{OUT} = (1 \angle 0^\circ)$

~~$$V_{IN} \left[(1 + j\omega RC) + j\omega RC(1 + j\omega RC) \right] = 1 \angle 0^\circ$$~~

~~V_{IN}~~

(OVER)

$$V_{in} = 1 + j\omega RC + R(j\omega C + R(j\omega C)^2)$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{(j\omega)^2 (RC)^2 + j\omega 3RC + 1}$$
$$= H(\omega)$$


$$|H(\omega)| = \frac{1}{\sqrt{(1 - \omega^2 R^2 C^2)^2 + 9\omega^2 R^2 C^2}}$$

FOR 'SMALL' ω

$$|H(\omega)| \approx 1$$

FOR 'LARGE' ω

$$|H(\omega)| \approx \frac{1}{\omega^2 R^2 C^2} = \frac{\omega_0^2}{\omega^2}$$


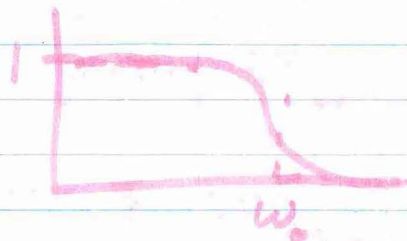


4-21-70



$$V_{OUT} = H V_{IN}$$

H IS THE SYSTEM FUNCTION

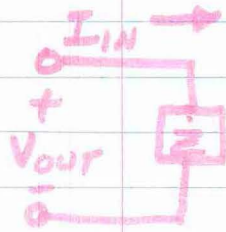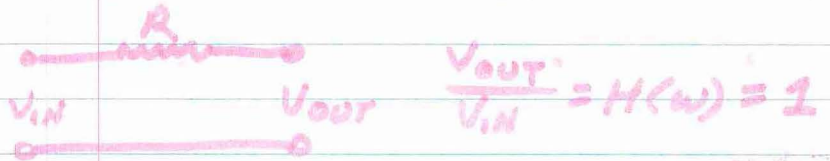

$$\frac{V_{OUT}}{V_{IN}} = Z = H$$

(CALLED DRIVING POINT IMPEDANCE)



AT RESONANT FREQUENCY
 $\theta = 0$, OR Z IS REAL

FOR RLC NETWORK



$$\omega = \sqrt{\frac{1}{LC}} \text{ AT RESONANCE}$$

$$\text{WHEN } Z = R$$

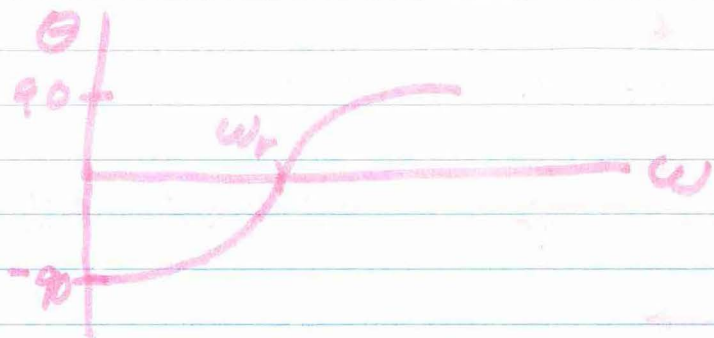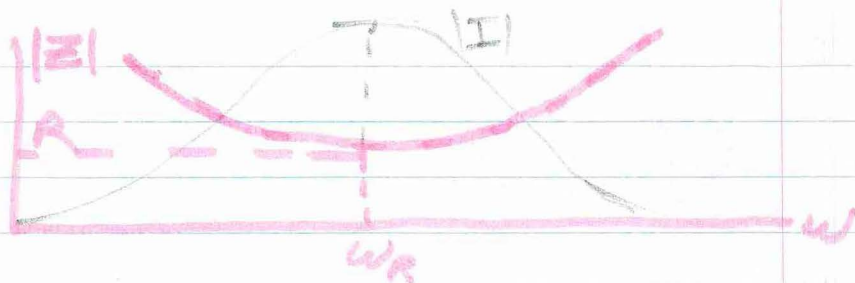

$$P = |I|^2 R = \left| \frac{V}{Z} \right|^2 R$$

WHEN $|I| = \frac{1}{\sqrt{2}} I_{\text{max}}$, $P = \frac{1}{2} P_{\text{max}}$

THEN $|Z| = \frac{1}{.707} Z_{\text{min}} = 1.414 R$, TH
(Z AT $\frac{1}{2}$ POWER FREQUENCY)

SOLVE FOR $\frac{1}{2}$ PWR, ω

$$2R^2 = R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2$$

$$R^2 = \left(\omega L - \frac{1}{\omega C} \right)^2$$

$$R = \left(\omega L - \frac{1}{\omega C} \right)$$

(CONT)

$$\omega^2 RC - \omega RC - 1 = 0$$

$$\omega = \frac{RC \pm \sqrt{R^2 C^2 + 4LC}}{2LC}$$

4-22-70

$$\omega L - \frac{1}{\omega C} = \pm R$$

USING +

$$1) \omega = \frac{R}{2L} \pm \sqrt{\frac{1}{LC} + \left(\frac{R}{2L}\right)^2}$$

USING +

$$2) \omega = \frac{R}{2L} + \sqrt{\frac{1}{LC} + \left(\frac{R}{2L}\right)^2}$$

↓

↓

$$\omega = \pm \frac{R}{2L} + \sqrt{\frac{1}{LC} + \left(\frac{R}{2L}\right)^2}$$


ω_U IS UPPER $\frac{1}{2}$ PWR FREQ

ω_L IS LOWER " " "

$$\text{let } \frac{R}{2L} = a; \quad \frac{1}{LC} = \omega_0^2$$

$$\omega_L = \omega_0 \sqrt{1 + \left(\frac{a}{\omega_0}\right)^2} - a$$
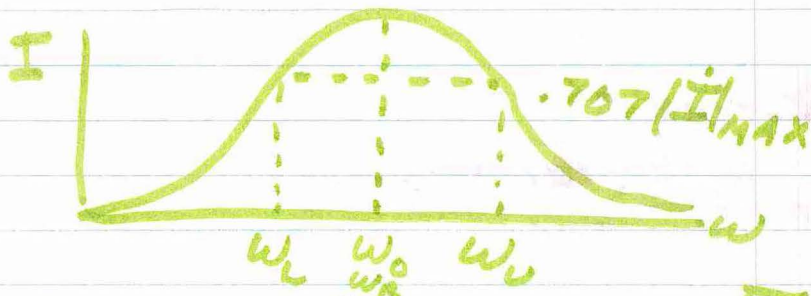
$$\omega_U = \omega_0 \sqrt{1 + \left(\frac{a}{\omega_0}\right)^2} + a$$



DEFINITION BANDWIDTH $\overline{BW} = \omega_U - \omega_L$


$$\overline{BW} = 2\alpha = R/L$$

FOR THIS CIRCUIT

$$Q_0 = \frac{\omega_r L}{R}$$

$$\therefore \overline{BW} = \frac{\omega_r}{Q_0} \leftarrow$$
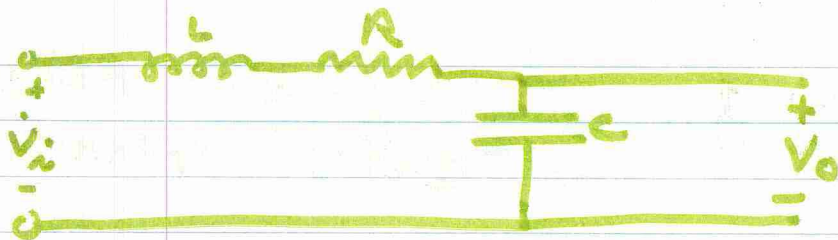
$$\frac{Q}{\omega_r} = \frac{R/2L}{1/\sqrt{LC}} = \frac{R}{2} \sqrt{\frac{C}{L}}$$



$$\frac{V_o}{V_i} = H(\omega) = \frac{\frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}}$$

$$= \frac{1}{1 - \omega^2 LC + j\omega RC}$$

$$|H(\omega)| = \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}}$$

$$\angle H = \tan^{-1} \frac{\omega RC}{1 - \omega^2 LC}$$

WHERE IS $|H(\omega)|$ MAX

WANT TO MINIMIZE DEN

$$\sqrt{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}$$

OR

$$(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2$$

$$0 = \frac{d}{d\omega} = 2(1 - \omega^2 LC)(-2\omega LC) + 2\omega R^2 C^2$$

$$\omega_p^2 = \frac{1}{LC} - \frac{1}{2} \left(\frac{R}{L} \right)^2$$

(10 = no prob)

CONT.

CASE I $\frac{1}{LC} > \frac{1}{2} \left(\frac{R}{L}\right)^2$ DEFINITE PEAK
 CASE II $\frac{1}{LC} \leq \frac{1}{2} \left(\frac{R}{L}\right)^2$ "PEAK" AT 0

$$\omega_p = \sqrt{\frac{1}{LC} - \frac{1}{2} \left(\frac{R}{L}\right)^2}$$

$$\Rightarrow \omega_p = \omega_r \sqrt{1 - \frac{1}{2} Q_0^{-2}} \leftarrow$$

IF Q_0 IS LARGE ENOUGH;
 $\omega_p = \omega_r$

CONSIDER $H(\omega_r)$


$$|H(\omega_r)| = \frac{1}{\omega_r RC}$$

$$= \frac{L/R}{\frac{\omega_r L}{R} \cdot RC} = \frac{1}{Q_0 R C} = \frac{1}{Q_0} = \frac{\sqrt{LC}}{RC}$$

↑
PEAK FREQUENCY


$$Q_0 = \frac{\omega_r L}{R} = \frac{1}{\omega_r RC}$$

4-23-70

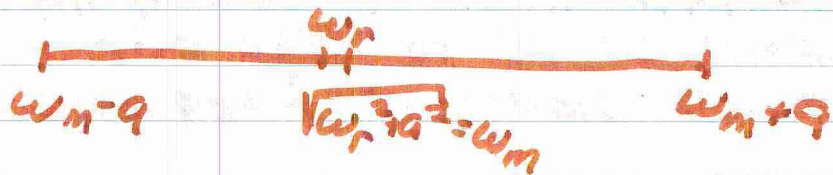

$$\begin{aligned}\omega_m &= \omega_r \sqrt{1 + \left(\frac{q}{\omega_r}\right)^2} \\ &= \omega_r \sqrt{1 + \left(\frac{BW}{2\omega_r}\right)^2} \\ &= \omega_r \sqrt{1 + \left(\frac{1}{2Q_0}\right)^2}\end{aligned}$$


$$BW = \frac{R}{L}$$

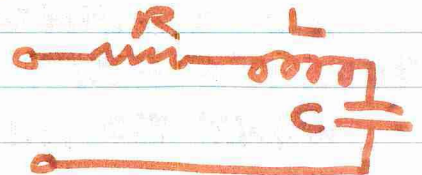

$$\omega_r = \sqrt{1/CL}$$

~~Q = R/L~~

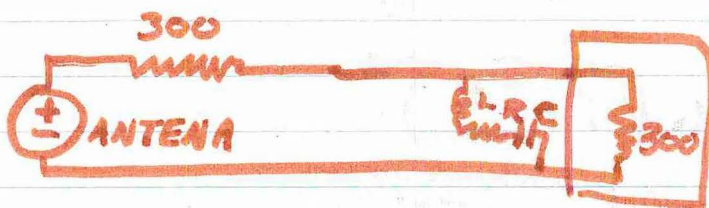DESIGN A TRAP CIRCUIT TO USE AT THE
TERMINALS OF TV TO TRAP OUT
INTERFERING SIGNAL AT $f = 89 \text{ MHz}$



AT $f = f_r$, TRAP IMPEDENCE = R
CAN GET COILS AT $Q = 200$
AT 89 MHz

MUST SELECT $L \neq C$

WANT TO MAKE R LOW (10Ω)


$$\frac{\omega L}{R} = Q = 200 \Rightarrow L = \frac{200 \cdot 10}{6.28 \cdot 89 \cdot 10^6}$$

$$= 3.58 \mu\text{H}$$

$$\omega_r = \frac{1}{\sqrt{LC}}$$

$$C = \frac{1}{\omega_r^2 L} = \frac{10^6}{6.28^2 \times 89^2 \times 10^{12} \times 3.58}$$

$$= .894 \text{ pF}$$

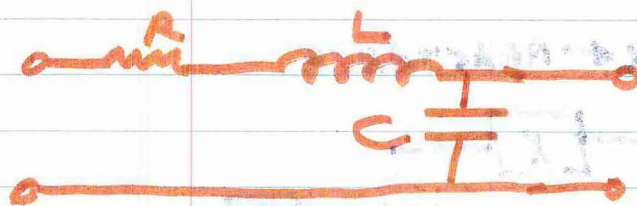

$$H(\omega) = \frac{1/j\omega C}{R + j(\omega L - 1/\omega C)}$$


$$= \frac{1}{1 - \omega^2 LC + j\omega RC}$$

$$\omega_p = \sqrt{\frac{1}{LC} - \frac{1}{2} \left(\frac{R}{L}\right)^2}$$

$$= \sqrt{\omega_r^2 - \frac{1}{2} \alpha^2}$$

$$= \omega_r \sqrt{1 - \frac{1}{2} \left(\frac{\alpha}{\omega_r}\right)^2}$$
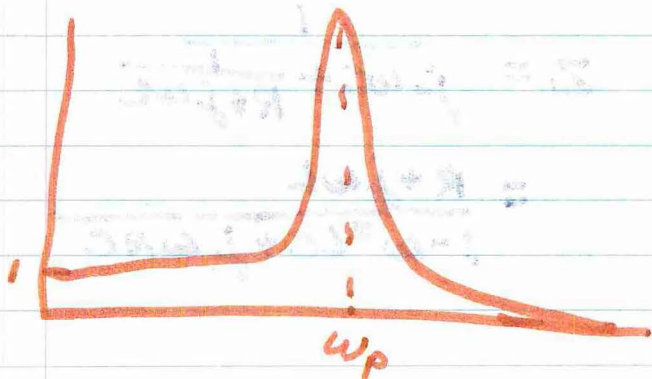
$$= \omega_r \sqrt{1 - \frac{1}{2} \alpha_0^2}$$




4-27-70

$$\dot{Z} = R + jX \leftarrow \text{REACTANCE}$$




$$\dot{Y} = G + jB$$

↑ CONDUCTANCE ↑ SUSCEPTANCE

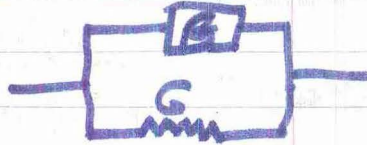

+ SUS ⇒ - REACTANCE

x-14)

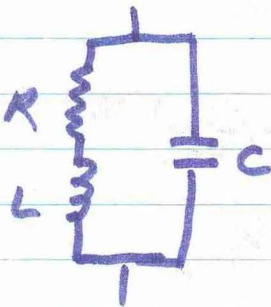

$$L = 30 \text{ mH}$$

$$R = 10 \Omega$$


$$C = .5 \mu\text{F}$$

$$Z = \frac{1}{j\omega C + \frac{1}{R + j\omega L}}$$
$$= \frac{R + j\omega L}{1 - \omega^2 LC + j\omega RC}$$

DRIVING PT. IMPEDENCE:



X-17)

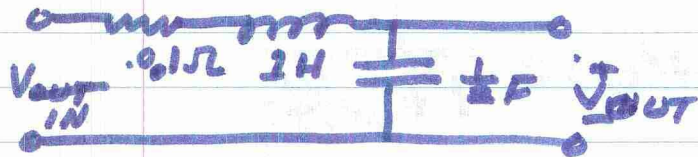

$$\frac{V_{OUT}}{V_{IN}} = \frac{1}{1 - \omega^2 LC + j\omega RC}$$

MINIMIZE


$$\frac{d}{d\omega} [(1 - .5\omega^2)^2 + 25 \times 10^{-4} \omega^2] = 0$$
$$2(1 - .5\omega^2)(-1\omega) + 50 \times 10^{-4} \omega = 0$$
$$\omega^2 = 2$$
$$\omega = \sqrt{2} \frac{RAD}{SEC}$$

4-30-70


LOG-LOG PLOT $|H(\omega)|$ & $\angle H(\omega)$

$$H(\omega) = \frac{(1+j\frac{\omega}{\omega_1})(1+j\frac{\omega}{\omega_2})(1+j\frac{\omega}{\omega_3})}{(1+j\frac{\omega}{\omega_a})(1+j\frac{\omega}{\omega_b}) \dots (j\frac{\omega}{\omega_c})}$$
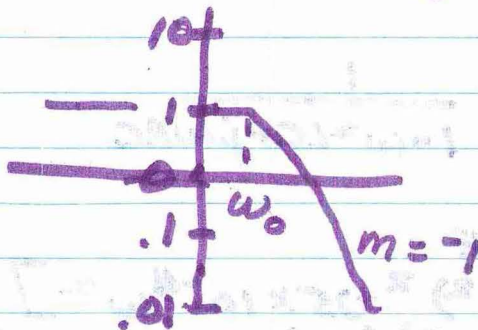
$$H(\omega) = \frac{1}{1+j\frac{\omega}{\omega_0}}$$


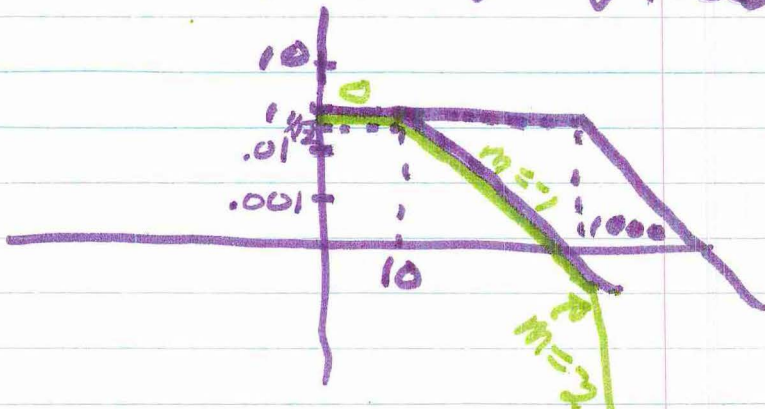
$$H(\omega) = (1+j\frac{\omega}{10})(1+j\frac{\omega}{1000})$$




ADD LOGS OF 2 COMPONENT CURVES

FOR REAL CURVE, ROUND
OFF CORNERS

$$H(\omega) = \frac{10^3}{(10+j\omega)(100+j\omega)}$$

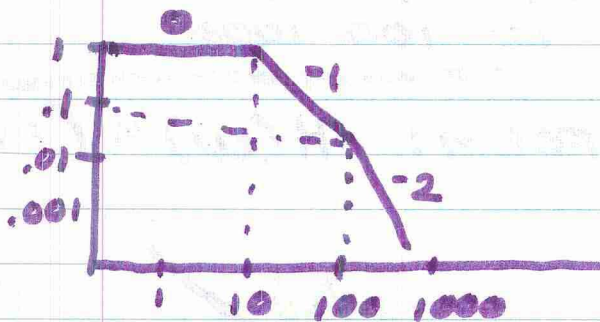
$$= \frac{1}{\left(1+j\frac{\omega}{10}\right)\left(1+j\frac{\omega}{100}\right)}$$




$$H(31.6) = \sqrt{(1+3.16^2)(1+31.6^2)}$$

$$= \sqrt{1/12.1} = .287$$

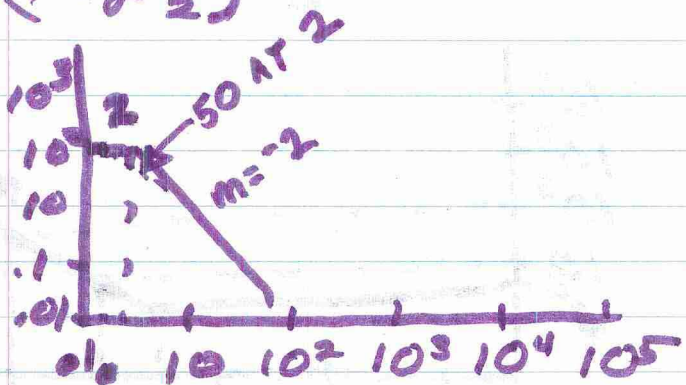
$$H(\omega) = \frac{100}{\left(1+j\frac{\omega}{2}\right)^2}$$



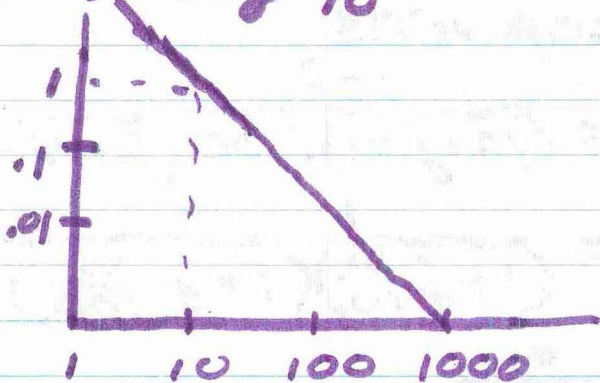
$$H(j\omega) = \frac{1}{j \frac{\omega}{10}}$$



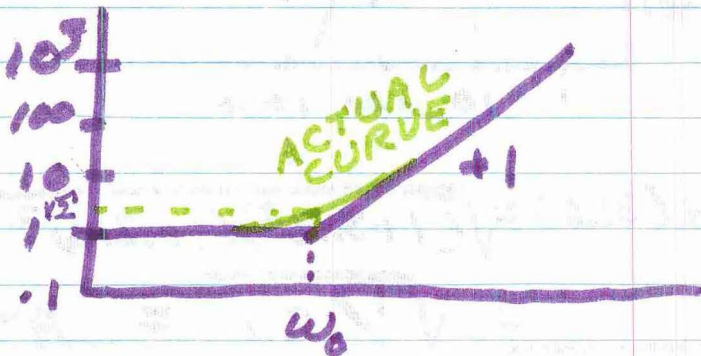NEW FORM: $H(\omega) = (1 + j \frac{\omega}{\omega_0})$



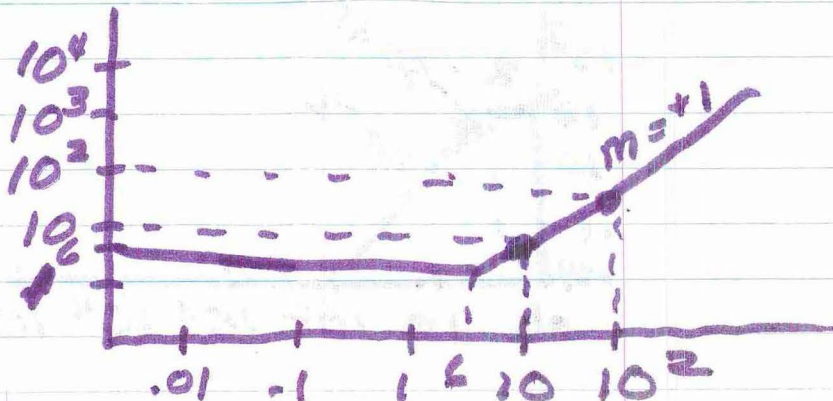
$$H(\omega) = 6 + j\omega = 6(1 + j \frac{\omega}{6})$$




$$H(\omega) = (1 + j 3\omega)(1 + j .13\omega)$$

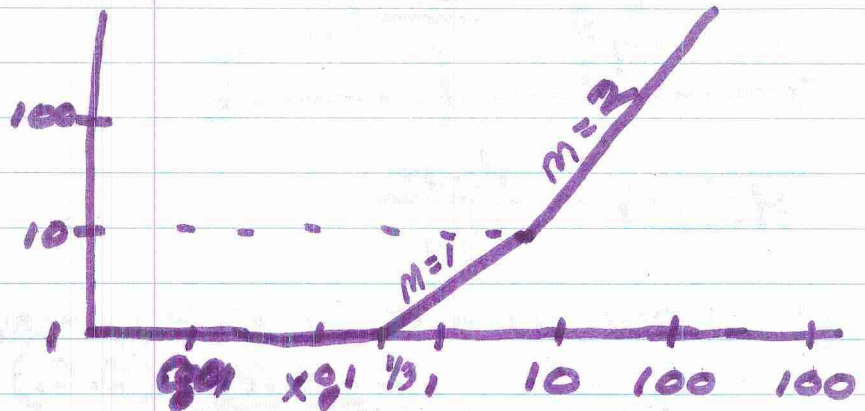
$$= \left(1 + j \frac{\omega}{1/3}\right) \left(1 + j \frac{\omega}{10}\right)$$




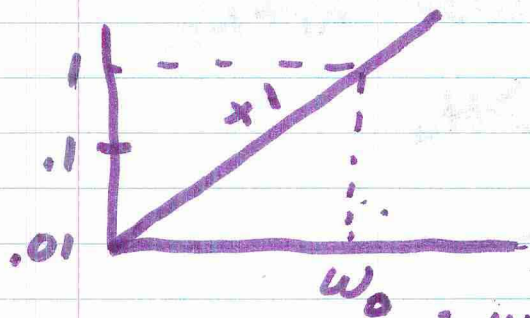NEW FORM: $H(\omega) = j \frac{\omega}{\omega_0}$


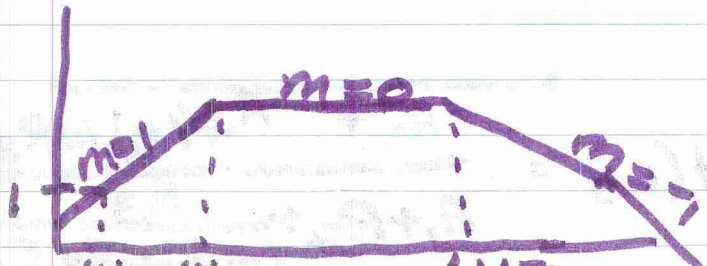
$$H(\omega) = \frac{j \frac{\omega}{\omega_1}}{\left(1 + j \frac{\omega}{\omega_2}\right) \left(1 + j \frac{\omega}{\omega_3}\right)} \quad \omega_1 < \omega_2 < \omega_3$$



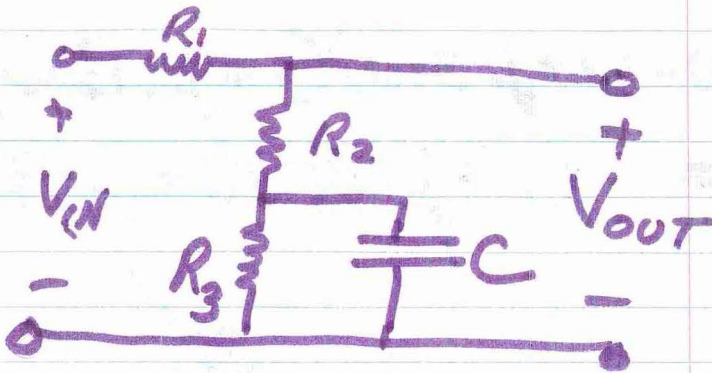

$$H(\omega) = \frac{V_{OUT}}{V_{IN}}$$


AT LOW ω - C IS NEGLIGIBLE

$$H_L(\omega) = \frac{R_2 + R_3}{R_1 + R_2 + R_3} \text{ (O.C.)}$$

AT HIGH ω ; C IS SHORTED

$$H_H(\omega) = \frac{R_2}{R_1 + R_2}$$

$$H_L > H_H$$

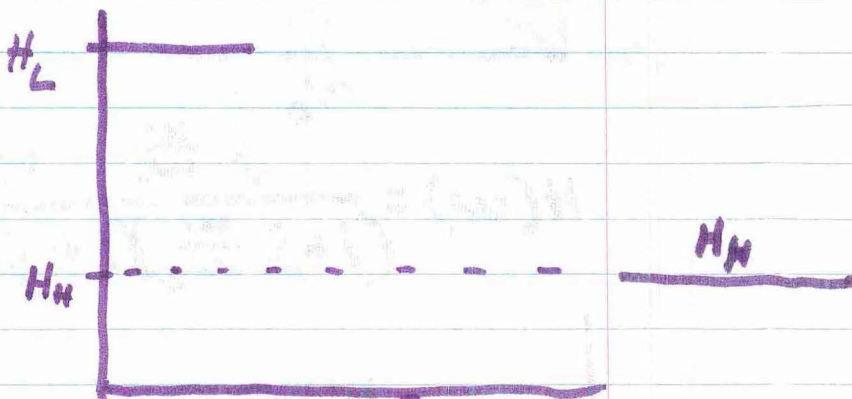


$$H(\omega) = \frac{R_2 + \frac{R_3}{1 + j\omega R_3 C}}{R_1 + R_2 + \frac{R_3}{1 + j\omega R_3 C}} \quad \uparrow \text{ (CONT.)}$$

$$\begin{aligned}
 H(\omega) &= \frac{R_3 + R_2 + j\omega R_2 R_3 C}{R_3 + R_2 + R_1 + j\omega R_3 (R_1 + R_2) C} \\
 &= \frac{R_2 + R_3 \left(1 + j\omega C \frac{R_2 R_3}{R_2 + R_3}\right)}{R_1 + R_2 + R_3 \left(1 + j\omega C \frac{(R_1 + R_2) R_3}{R_1 + R_2 + R_3}\right)} \\
 &= H_L \frac{1 + j \frac{\omega}{\omega_N}}{1 + j \frac{\omega}{\omega_0}}
 \end{aligned}$$

$$\omega_N = \frac{1}{CR_2 R_3 (R_2 + R_3)}$$
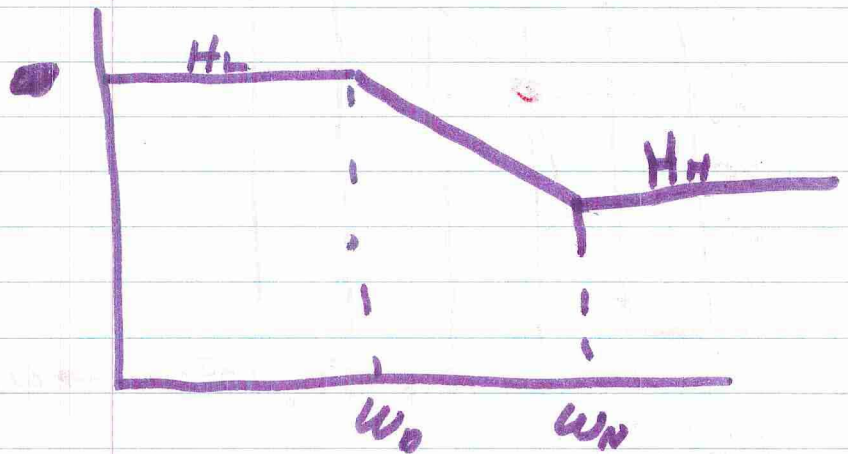
$$\omega_0 = \frac{1}{CR_3 (R_1 + R_2) (R_1 + R_2 + R_3)}$$



$$\frac{H_L}{H_H} = \frac{\omega_N}{\omega_0} \Rightarrow H_H = H_L \frac{\omega_0}{\omega_N}$$

5-4-70

5-5-70

$$H(\omega) = \frac{(1 + j\frac{\omega}{\omega_1})(1 + j\frac{\omega}{\omega_2}) \dots j\frac{\omega}{\omega_z}}{(1 + j\frac{\omega}{\omega_h})(1 + j\frac{\omega}{\omega_b}) \dots (1 + j\frac{\omega}{\omega_p}) j\frac{\omega}{\omega_z}}$$

ONE LINEAR FACTOR


$$H(\omega) = (1 + j\frac{\omega}{\omega_0})^{\pm 1}$$

$$\angle H(\omega) = \Theta_H = \pm \tan^{-1} \frac{\omega}{\omega_0}$$

FOR $\omega \ll \omega_0$, $\Theta_H = 0$

FOR $\omega \gg \omega_0$, $\Theta_H = \pm 90^\circ$

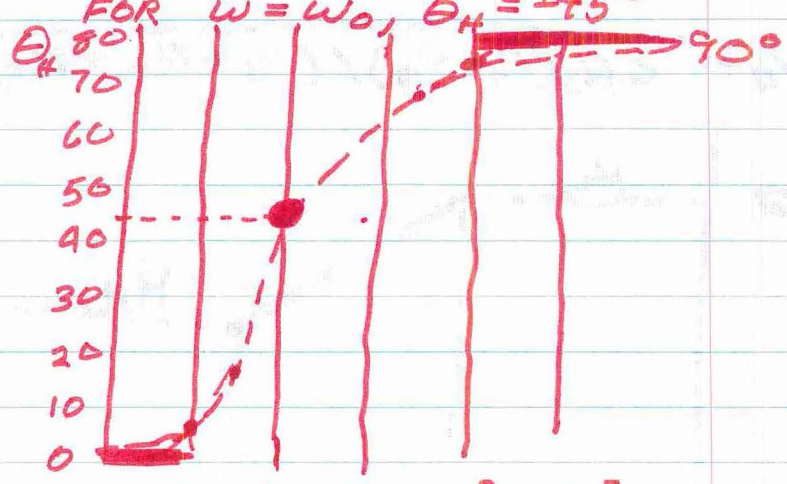FOR $\omega = \omega_0$, $\Theta_H = \pm 45^\circ$



$.1\omega_0 \quad \omega_0 \quad 10\omega_0 \quad 10^2\omega_0 \quad 10^3\omega_0 \rightarrow \omega \text{ (log scale)}$

ω	Θ_H
$.1\omega_0$	5.47°
$.316\omega_0$	17.55°
$1.00\omega_0$	45°
$3.16\omega_0$	72.45°
$10\omega_0$	84.26°
$.017\omega_0$	1°

FOR ASYMPTOTE, TAKE TANGENT
AT 45°

$$\theta = \tan^{-1} \frac{\omega}{\omega_0}$$

$$\theta = \tan^{-1} \log \frac{\omega}{\omega_0}$$

$$\omega = \omega_0 \Rightarrow \theta = 45^\circ$$

$$\omega = 1.01\omega_0 \Rightarrow \theta = 45.3^\circ$$


$$\text{slope} = \frac{.3}{.01} \text{ (# DECADE)}$$

$$(1.01)^x = 10 \Rightarrow x = 231.$$



$$\text{slope} = \frac{30^\circ}{(1/231) \text{ DECADES}} = \frac{69.3^\circ}{\text{DECADE}}$$

$$\begin{aligned} \# \text{ DECADES FROM } 45^\circ - 90^\circ &= \frac{45}{69.3} \text{ DECADES} \\ &= .659 \text{ DECADES} \end{aligned}$$

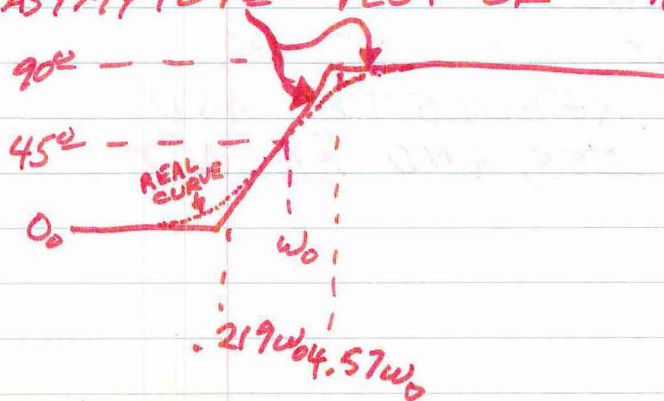AT $\theta = 90^\circ$; $\omega = 4.57$
ASYMPTOTE PLOT OF θ


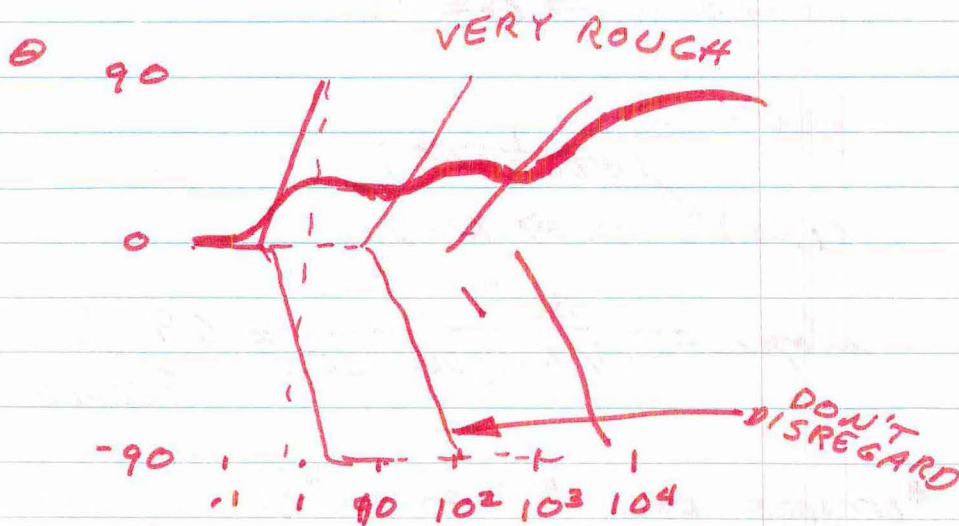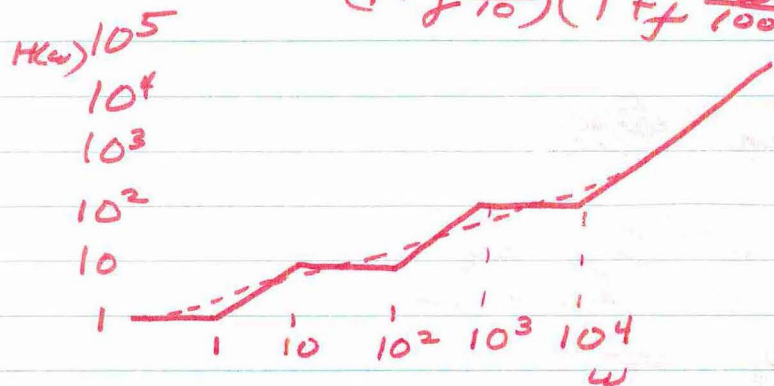
$$H(\omega) = \frac{(1 + j\omega)(1 + j\frac{\omega}{100})(1 + j\frac{\omega}{10^{-1}})}{(1 + j\frac{\omega}{10})(1 + j\frac{\omega}{1000})}$$




ASYMPTOTIC PLOTS FOR
 PHASE ANGLES ARE
 WORTHLESS, AND STINK,
 AND ARE REPULSIVE, AND
 ARE USELESS, AND AREN'T
 SO NICE.

COMPUTER DO \Rightarrow

PLOT MAG. & PHASE FOR

$$H(\omega) = \frac{(1 + j\omega)(1 + j\frac{\omega}{100})(1 + j\frac{\omega}{10^4})}{(1 + j\frac{\omega}{10})(1 + j\frac{\omega}{10^2})(1 + j\frac{\omega}{10^5})}$$

5-6-70

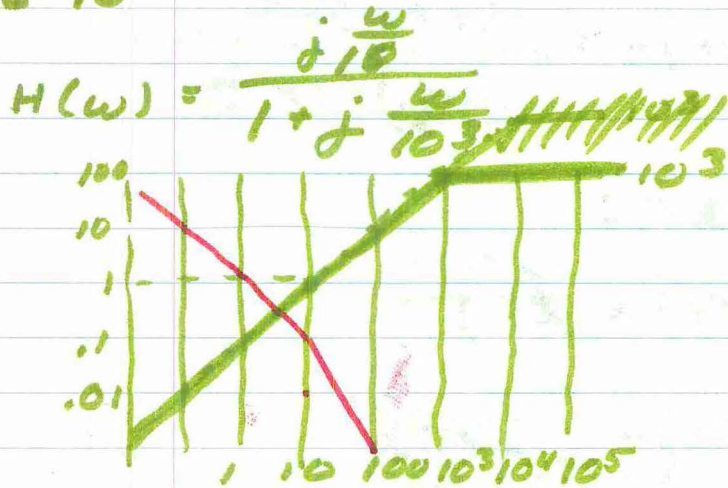

$$H(\omega) = \frac{1}{j\omega(1 + j\frac{\omega}{10})}$$

$$H(\omega) = \frac{j\frac{\omega}{10}}{(1 + j\frac{\omega}{10^2})(1 + j\frac{\omega}{10^3})}$$

$$H(s) = \frac{s+10}{(s+100)(s+1000)}$$

$$s = j\omega$$

$$\begin{aligned} H(\omega) &= \frac{j\omega + 10}{(j\omega + 100)(j\omega + 1000)} \\ &= 10^{-4} \frac{(1 + j\frac{\omega}{10})}{(1 + j\frac{\omega}{100})(1 + j\frac{\omega}{1000})} \end{aligned}$$

CONSIDER:

$$H(s) = \frac{Y(s)}{X(s)}$$

$$Y(s) = \mathcal{L}\{y(t)\}$$


$$X(s) = \mathcal{L}\{x(t)\}$$

NO INITIAL CONDITIONS

$$H(s) = \frac{P(s)}{Q(s)} \text{ WHERE BOTH ARE POLYNOMIALS}$$

$$s = \sigma + j\omega$$


$$H(s) = \frac{1}{s+a}$$

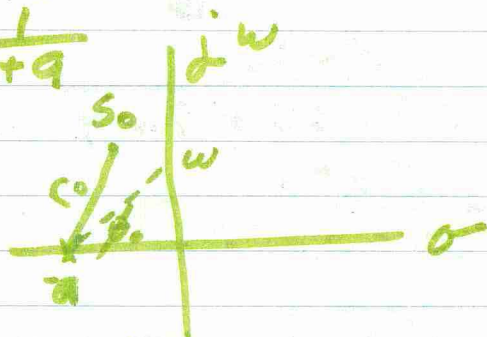

$$|H(s_0)| = \frac{1}{r_0}$$

$$\theta_H(\omega_0) = -\phi_0$$
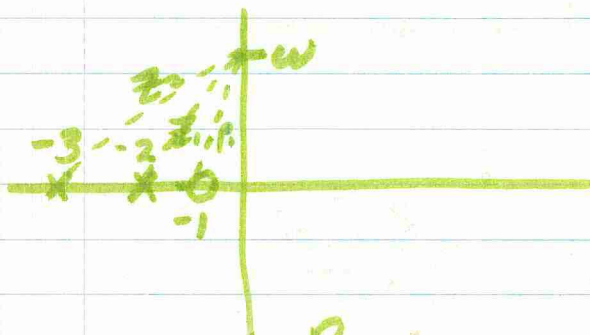
$$H(s) = \frac{s+1}{s^2+5s+6} = \frac{s+1}{(s+3)(s+2)}$$



$$|H(\omega_0)| = \frac{r_1}{z_1 \cdot z_2}$$

$$\angle H(\omega_0) = \theta_H(\omega_0)$$


$$= \phi_1 - \phi_2 - \phi_3$$

$$H(s) = \frac{s+2}{s^2+6s+13}$$

$$= \frac{s+2}{s^2+6s+9+4}$$

$$= \frac{s+2}{(s+3)^2+2^2}$$

$$= \frac{s+2}{(s+3+j2)(s+3-j2)}$$

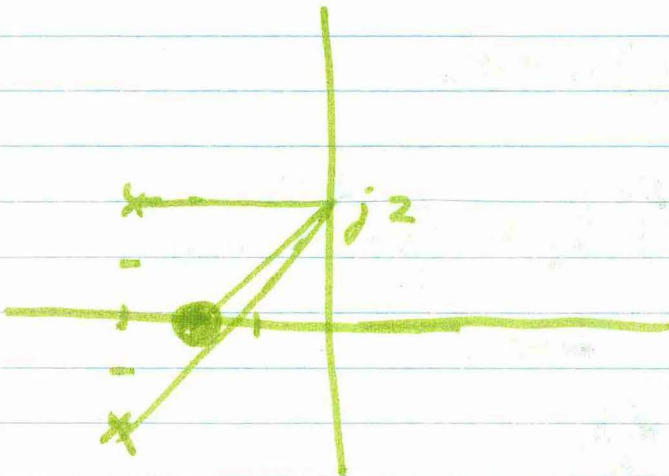

$$H(j2) = \frac{2\sqrt{2}}{3 \cdot 5}$$

$$\theta_H(j2) = 45^\circ - 0^\circ - 53.9^\circ$$
$$= -8.9^\circ$$

5-11-70

$$z = x + jy = |z| \angle \theta$$

x	y	QUADRANT
+	+	I
+	-	IV
-	+	II
-	-	III

} WORRY

$\tan^{-1}(\frac{y}{x})$ ON IBM RANGES
ONLY FROM -90 TO 0 TO +90

~~508~~


FUNCTION ATAN 2 (Y, X)
ATAN 2 = ATAN (Y/X)


IF X 1, 1, 2

1 ATAN 2 = ATAN 2 + 3.1415926537

2 RETURN


END

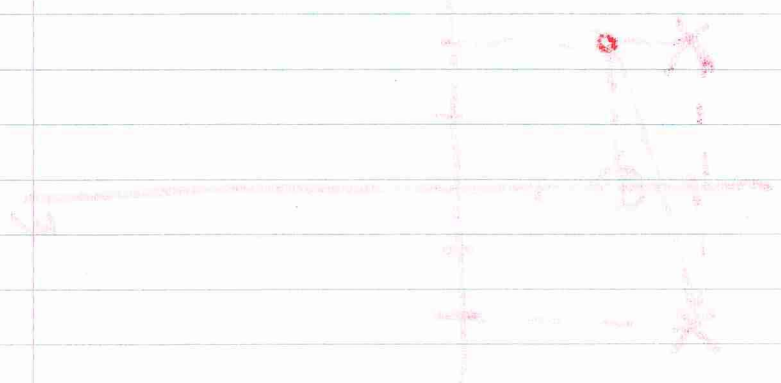


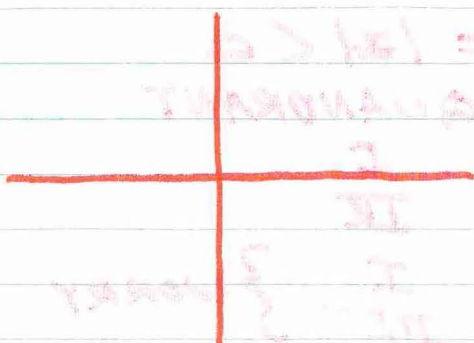

$$\begin{aligned}
 H(s) &= \frac{s+2}{s^2+6s+13} = \frac{s+2}{s^2+6s+9+13-9} \\
 &= \frac{s+2}{(s+3)^2+2^2} \\
 &= \frac{s+2}{(s+3+j2)(s+3-j2)}
 \end{aligned}$$

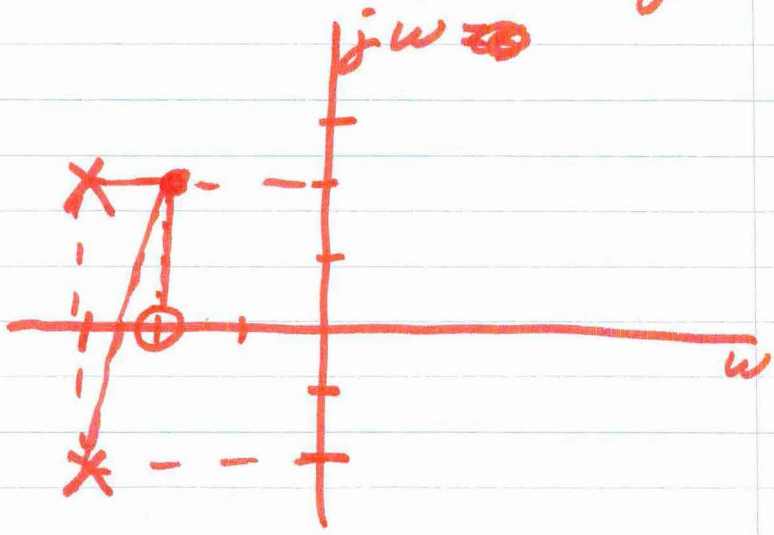O AT $s = -2$
 POLES AT $s = -3 - j2$
 $s = -3 + j2$



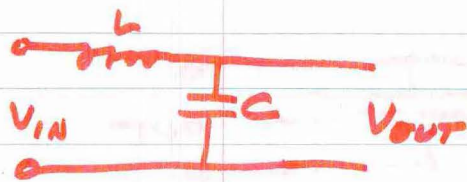


$$\begin{aligned}
 H &= \frac{V_o}{V_{IN}} = \frac{j\omega C}{j\omega L + \frac{1}{j\omega C}} \\
 &= \frac{1}{1 + s^2 LC} = \frac{\sqrt{LC}}{s^2 + 1/LC} \\
 &= \frac{1/LC}{(s + j\sqrt{1/LC})(s - j\sqrt{1/LC})}
 \end{aligned}$$

$$H(-2 + j2) = ?$$

$$\begin{aligned}
 |H(-2 + j2)| &= \frac{2}{\sqrt{1+7}} \\
 &= .486
 \end{aligned}$$
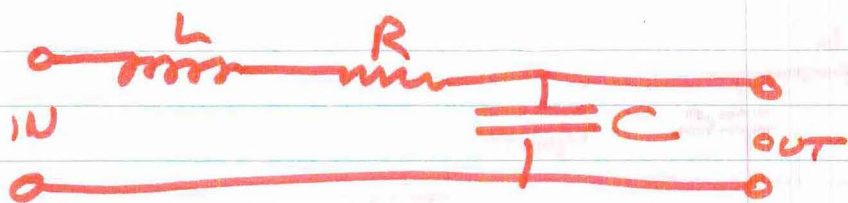
$$\begin{aligned}
 \angle H(-2 + j2) &= 90 - 0 - \tan^{-1} 4 \\
 &= 14.05^\circ
 \end{aligned}$$



$$\frac{V_o}{V_i} = \frac{\frac{1}{sC}}{R + sL + \frac{1}{sC}}$$

$$= \frac{1}{LCs^2 + RCs + 1}$$

$$= \frac{1}{LC} \cdot \frac{1}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$= \frac{1}{LC} \frac{1}{s^2 + \frac{R}{L}s + \left(\frac{R}{2L}\right)^2 + \frac{1}{LC} - \frac{R^2}{4L^2}}$$

$$H(s) = \frac{1}{LC} \cdot \frac{1}{\left(s + \frac{R}{2L}\right)^2 + \left[\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}\right]^2}$$

$$= \frac{1}{LC} \frac{1}{\left(s + \frac{R}{2L} + j\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}\right)}$$


$$\bullet \frac{1}{s + \frac{R}{2L} - j\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}}$$

LET $\frac{1}{LC} = \omega_0^2 = \beta$


AND $\frac{R}{2L} = \alpha$

$$H(s) = \frac{\omega_0^2}{(s + \alpha + j\beta)(s + \alpha - j\beta)}$$

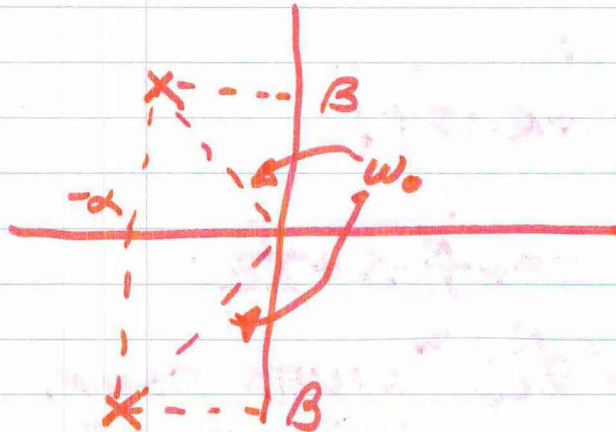LET $\beta^2 > 0 \Rightarrow \beta$ IS REAL




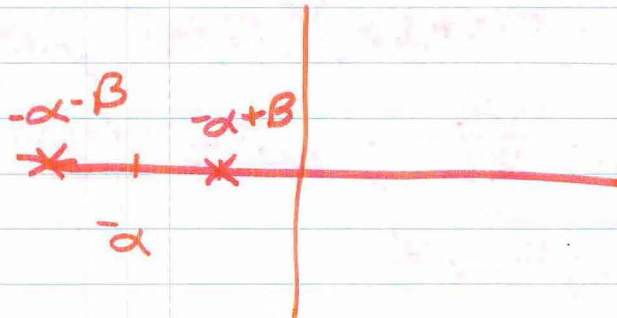IF $\beta^2 \leq 0 \Rightarrow \beta$ IS IMAGINARY



- 1) MAKE R LARGER, POLES SWEEP A COICLE
- 2) VARY C, POLES GO UP & DOWN
- 3) VARY L, GOES HAY WIRE

5-12-70

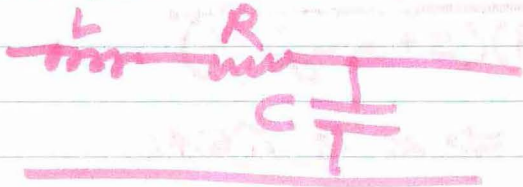

$$H(s) = \frac{1}{s^2 LC + RCs + 1}$$


$$= \frac{1}{LC} \frac{1}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$\frac{1}{LC} > \left(\frac{R}{2L}\right)^2$ GIVES COMP.
CONJ. POLES

$$H(s) = \frac{1}{LC} \frac{1}{(s + \alpha + j\beta)(s + \alpha - j\beta)}$$

WHERE $\alpha = \frac{R}{2L}$; $\omega_0^2 = \frac{1}{LC}$

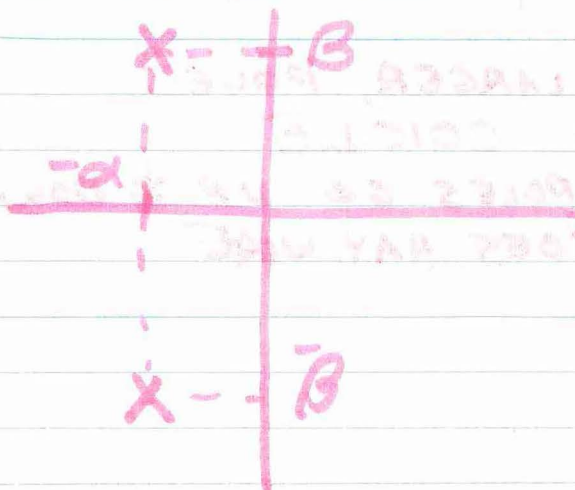AND $\beta = \sqrt{\omega_0^2 - \alpha^2}$




$$\beta = \sqrt{\omega_0^2 - \alpha^2} = \omega_0 \sqrt{1 - \left(\frac{\alpha}{\omega_0}\right)^2}$$

WHERE $\frac{\alpha}{\omega_0} = \frac{R\sqrt{LC}}{2L}$

$$= \frac{R}{2L\omega_0} = \frac{1}{2Q_0}$$

$$\left(Q_0 = \frac{\omega_0 L}{R} = \frac{\text{REACTANCE}}{\text{RESISTANCE}} \right)$$
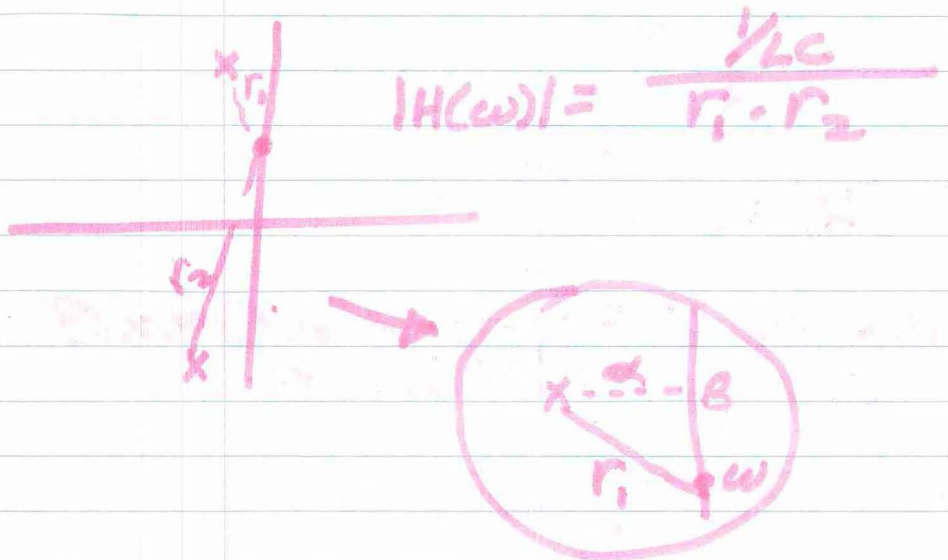
$$\beta = \omega_0 \left(1 - \frac{1}{4Q_0^2} \right)^{\frac{1}{2}}$$




γ_2 ALMOST CONSTANT
IN VICINITY; $\gamma_2 \approx 2\beta$

$$\therefore |H(\omega)| = \frac{\sqrt{LC}}{2\beta \gamma_1}$$

(CONT.)

$$(H(\omega))_{\text{MAX}} \approx \frac{1}{2\beta LC} \frac{1}{\alpha}$$

$$\approx Q_0$$

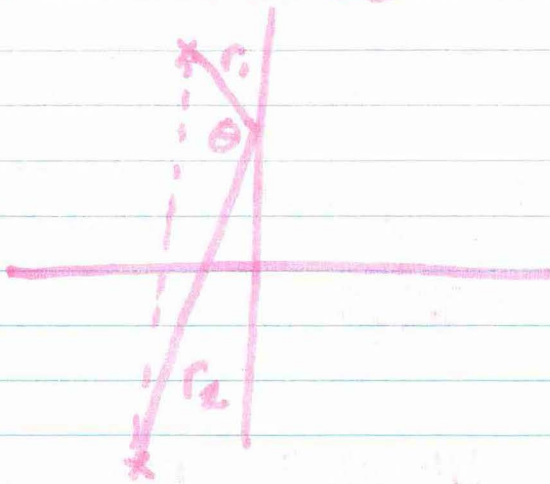


$$|H| = \frac{1/LC}{r_1 \cdot r_2}$$

$$\text{AREA OF } \Delta = r_1 \cdot r_2 \cdot \sin \theta = \alpha \beta$$

$$\therefore r_1 r_2 = \alpha \beta / \sin \theta$$

$$\Rightarrow |H| = \frac{1}{LC \alpha \beta \sin \theta}$$

$$|H|_{\text{MAX}} = \frac{1}{LC \alpha \beta} \quad (\theta = 90^\circ)$$

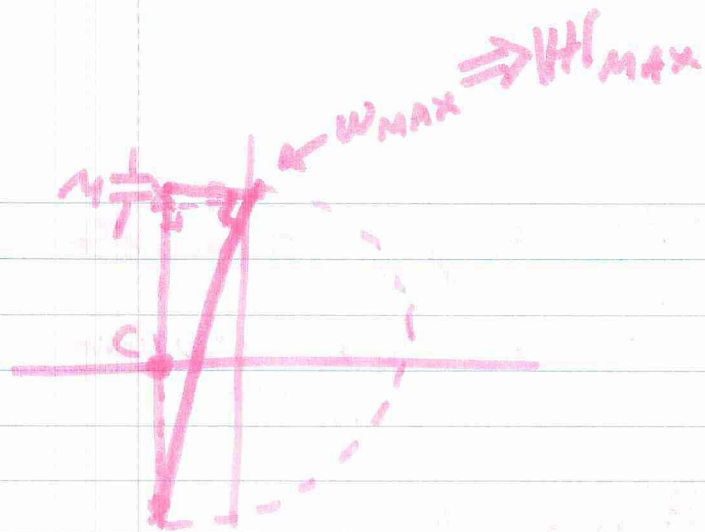

$$W_{MAX} \approx B$$

$$= B - m$$

~~$$\frac{m}{B} = \frac{\alpha}{B}$$~~

$$\frac{m}{\alpha} = \frac{\alpha}{2B - m}$$

$$0 = \alpha \pm (m - B - \sqrt{B^2 - \alpha^2})(m - B + \sqrt{B^2 - \alpha^2})$$

$$m = B \pm \sqrt{B^2 - \alpha^2}$$

$$\therefore W_{MAX} = \sqrt{B^2 - \alpha^2}$$

$$\text{ALSO } W_{MAX} = \omega_0 \sqrt{1 - \frac{2\alpha^2}{\omega_0^2}}$$

$$= \omega_0 \sqrt{1 - \frac{1}{2Q_0^2}}$$

COMPARE WITH:

$$B = \omega_0 \sqrt{1 - \frac{1}{4Q_0^2}}$$

$$|H(\omega)| = |H|_{\text{MAX}} \sin \theta$$

FIND $\frac{1}{2}$ POWER VALUES
(AT 45° & 135°)


$$\omega_L \approx \omega_0 - \alpha$$

$$\omega_U \approx \omega_0 + \alpha$$

$$BW = 2\alpha = \frac{R}{L}$$

5-14-70

PRACTICAL ANTI-RESONANT CIRCUIT

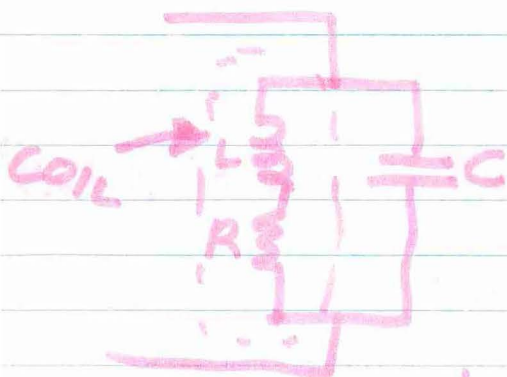

$$Z(s) = \frac{\frac{1}{sC}(R + sL)}{R + sL + \frac{1}{sC}}$$

$$= \frac{R + sL}{s^2 LC + \frac{R}{s} + 1}$$


$$= \frac{1}{C} \frac{R + sL}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

ROOTS OF DEN. ARE COMP. CONJ.

$$H(s) = \frac{1}{C} \frac{s + \gamma/L}{(s + \alpha)^2 + \beta^2}$$

$$\begin{cases} \alpha = R/2L \\ \beta = \sqrt{\omega_0^2 - \alpha^2} \\ \omega_0^2 = 1/LC \end{cases}$$
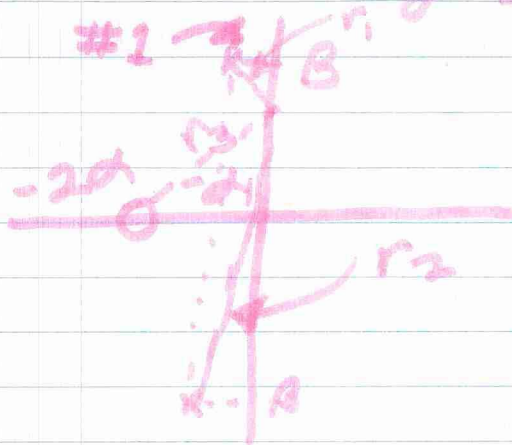
$$H(s) = \frac{1}{C} \frac{s + 2\alpha}{(s + \alpha + j\beta)(s + \alpha - j\beta)}$$



APPROXIMATIONS - $\omega_0 \gg \alpha$
~~IN VICINITY OF POLE #1~~

$$|H(\omega)| = \frac{1}{C} \cdot \frac{r_3}{r_1 r_2}$$

IN VICINITY OF POLE 1

$$r_2 \approx 2\beta; r_3 \approx \beta$$

$$|H(\omega)| \approx \frac{1}{C} \frac{\beta}{\alpha \cdot 2\beta} \approx \frac{1}{2C\alpha}$$

$$H(\omega)_{\text{MAX}} \doteq \frac{1}{2RC}$$

$$= \frac{1}{2C \frac{R}{L}} = \frac{1}{RC}$$

$$\frac{L}{RC} = \frac{\omega_0 L}{\omega_0 RC} = \frac{Q_0}{\omega_0 C} = Q_0 \omega_0$$

$$= \frac{\omega_0 L R}{\omega_0 R^2 C} = \left(\frac{\omega_0 L}{R}\right) \left(\frac{1}{\omega_0 RC}\right) R$$

$$= Q_0^2 R$$

$Q_0 = \frac{1}{\omega_0 RC}$ IS SERIES
 $Q_0 = \frac{\omega_0 L}{R}$ IN PARALLEL

$$\omega_{\text{MAX}} = \sqrt{1/LC} = \omega_0$$

$$\omega_L = \omega_0 + \alpha$$

$$\omega_P = \omega_0 - \alpha$$

$$BW = 2\alpha$$

$$\angle \approx (\omega_P) \approx 0$$

FIND $Z(\omega)$ MAX

$$Z(\omega) = \frac{R + j\omega L}{1 - \omega^2 LC + j\omega RC}$$

$$|Z|^2 = \frac{R^2 + \omega^2 L^2}{(1 - \omega^2 LC)^2 + \omega^2 RC^2}$$

$$x = \omega^2$$

$$|Z|^2 = \frac{R^2 + xL^2}{(1 - xLC)^2 + xRC^2}$$

~~$$= \frac{R^2 + xL^2}{1 - 2LCx + L^2Cx^2 + RCx}$$~~

~~$$= \frac{R^2 + L^2x}{LCx^2 + (RC - 2LC)x + 1}$$~~

~~$$= \frac{\frac{R^2}{LC} + \frac{L^2}{C}x}{x^2 + \left(\frac{R}{L} - 2\right)x + \frac{1}{LC}}$$~~

$$= \frac{R^2 + L^2x}{L^2C^2x^2 + (R^2C^2 - 2LC)x + 1}$$

$$= \frac{1}{C^2} \frac{R^2x + \left(\frac{R}{L}\right)^2}{x^2 + \left(\frac{R^2}{L^2} - \frac{2}{LC}\right)x + \frac{1}{L^2C}}$$

DIFFERENTIATE $\frac{d}{dx}$
SET TO 0

(CONT)

$$\omega_n = \sqrt{\lambda}$$

$$x = \sqrt{\left(\frac{0}{2}\right)^2 - \epsilon} - \frac{0}{2}$$

HAIRY !!

5-18-70

FOURIER SERIES

$$x(t) = \sum_{n=N_1}^{N_2} a_n \underbrace{\phi_n(t)}_{\text{BASIS FUNCTIONS}}$$

BASIS FUNCTIONS

FOR FOURIER SERIES,
 $\phi_n(t)$ ARE SINUSOIDS

$$\therefore x(t) = \frac{c_0}{2} + \sum_{n=1}^{\infty} c_n \sin(n\omega_0 t + \theta_n)$$

DC. VALUE

$$t_1 < t < t_2$$

(c_n) ARE THE COEFFICIENTS
WHICH MUST BE
DETERMINED

ANOTHER REPRESENTATION:

$$x(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} a_n \cos n\omega_0 t + \sum_{n=1}^{\infty} b_n \sin n\omega_0 t$$


$t_1 < t < t_2$

ω_0 IS FUNDAMENTAL FREQ OF F.S.

$$\omega_0 = 2\pi f_0$$

$$f_0 = \frac{1}{t_2 - t_1} = \frac{1}{T} = \frac{1}{\text{PERIOD}}$$

EX)

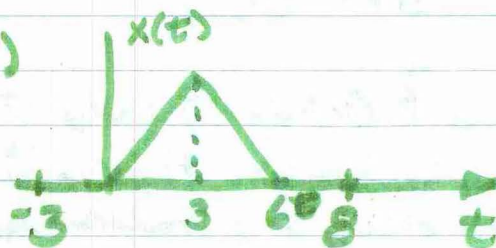

$$T = 11 \text{ SEC}$$

COMPLEX FOURIER SERIES

$$x(t) = \sum_{n=-\infty}^{\infty} \alpha_n e^{jn\omega_0 t}$$

$t_1 < t < t_2$

$$(\) = [\alpha_n + \alpha_{-n}] \cos n\omega_0 t + j [\alpha_n - \alpha_{-n}] \sin n\omega_0 t$$

$\alpha_n + \alpha_{-n}$ MUST BE REAL

$\alpha_n - \alpha_{-n}$ MUST BE IMAG.

(CONT.)

$$\text{Re}(\alpha_n) + j \text{Im}(\alpha_n) + \text{Re}(\alpha_{-n}) + j \text{Im}(\alpha_{-n}) = \text{REAL}$$

$$\text{Re}(\alpha_n) + \text{Re}(\alpha_{-n}) + j [\text{Im}(\alpha_n) + \text{Im}(\alpha_{-n})]$$

$$\therefore \text{Im}(\alpha_n) = -\text{Im}(\alpha_{-n})$$

$$\alpha_n - \alpha_{-n} = \text{imag}$$

$$\text{Re}(\alpha_n) = \text{Re}(\alpha_{-n})$$

ERGO α_n IS COMPLEX
CONJUGATE OF α_{-n}

$$\begin{aligned} () &= 2 \text{Re} \{ \alpha_n \} \cos n \omega_0 t \\ &\quad - 2 \text{Im} \{ \alpha_n \} \sin n \omega_0 t \\ &= a_n \cos n \omega_0 t + 2 \text{Im} \{ \alpha_n \} \\ &\quad - b_n \sin n \omega_0 t \end{aligned}$$

CONCLUSION:

$$a_n = 2 \text{Re} \{ \alpha_n \}$$

$$b_n = 2 \text{Im} \{ \alpha_n \}$$


$$a_n = \frac{2}{T} \int_{t_1}^{t_2} x(t) \cos n\omega_0 t dt$$

$$b_n = \frac{2}{T} \int_{t_1}^{t_2} x(t) \sin n\omega_0 t dt$$

$$\tilde{a}_n = \frac{1}{T} \int_{t_1}^{t_2} x(t) e^{-j n \omega_0 t} dt$$

5-20-70
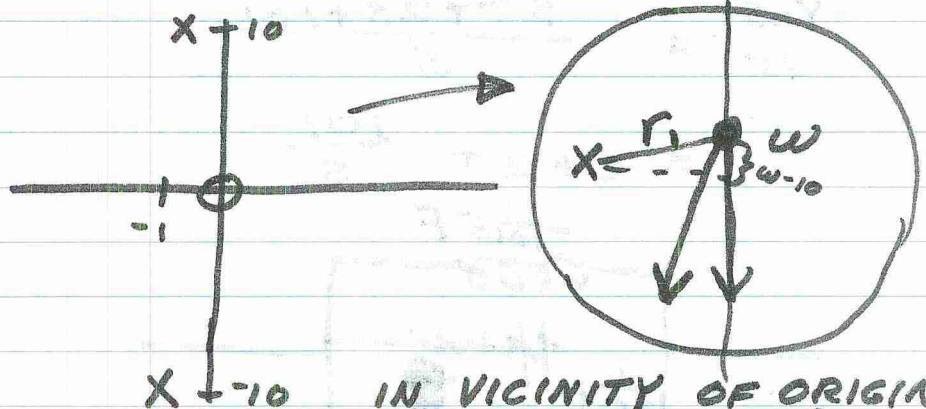
$$18.34) Z(s) = \frac{1}{10} \frac{s}{(s+1+j10)(s+1-j10)}$$



IN VICINITY OF ORIGIN
 a) $H(w) = \frac{1}{10} \frac{10}{20 \cdot r_1}$

$$= .05 / r_1$$

$$= .05 / \sqrt{1 + (w-1)^2}$$

Z(S) IN RESONANCE WHEN

CNUM = C DEN OR WHEN FUNC.
 PEAKS (TWO DEF.)

(CONT.)

$$b) Z(s) = \frac{1}{10} \frac{s}{(s+1+j10)(s+1-j10)}$$

$$= \frac{.1s}{s^2+2s+101}$$

$$\angle Z(\omega) = 0 \text{ at } \omega = \sqrt{101}$$


$$c) Z(j\sqrt{101}) = \frac{j \cdot .01 \times \sqrt{101}}{j 2 \cdot \sqrt{101}}$$

$$= .05 \Omega$$

HOW DRAW CIRCUIT FROM

$$\frac{Y(s)}{10} = \frac{s^2+2s+101}{s}$$

$$= s + 2 + \frac{101}{s}$$

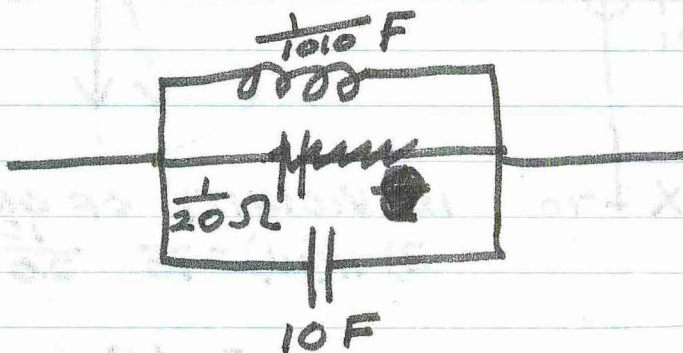

MORE ON SWELL FOURIER SERIES

$$x(t) = \sum_{n=-\infty}^{\infty} \alpha_n e^{jn\omega_0 t}$$

$$= \frac{a_0}{2} + \sum_{n=1}^{\infty} a_n \cos n\omega_0 t + \sum_{n=1}^{\infty} b_n \sin n\omega_0 t$$

$$\alpha_n = \frac{1}{T} \int_T x(t) e^{-jn\omega_0 t} dt$$

$$a_n = 2 \operatorname{Re} \{ \alpha_n \} = \frac{2}{T} \int_T x(t) \cos n\omega_0 t dt$$

$$b_n = -2 \operatorname{Im} \{ \alpha_n \} = \frac{2}{T} \int_T x(t) \sin n\omega_0 t dt$$

Let $x(t)$ BE AN EVEN FUNCTION

$$b_n = \frac{2}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} \underbrace{x(t)}_{\text{EVEN}} \underbrace{\sin n\omega_0 t}_{\text{ODD}} dt = 0$$

ODD

$\Rightarrow \alpha_n$ IS REAL $\{ \operatorname{Im} \{ \alpha_n \} = 0 \}$

$$\alpha_n = \frac{1}{T} \int_T x(t) [\cos n\omega_0 t - j \sin n\omega_0 t] dt$$

$$= \frac{1}{T} \int_T x(t) \cos n\omega_0 t dt$$

$$- j \frac{1}{T} \int_T x(t) \sin n\omega_0 t dt$$

1) IF $x(t)$ IS EVEN

$$b_n = 0$$

$$\text{Im} \{ \alpha_n \} = 0$$

$$\alpha_n = \frac{1}{T} \int_T x(t) \cos n\omega_0 t dt$$

2) IF $x(t)$ IS ODD

$$a_n = 0$$

$$\text{Re} \{ \alpha_n \} = 0$$

$$\alpha_n = \frac{1}{T} \int_T x(t) \sin n\omega_0 t dt$$

SHIFTED TIME FUNCTIONS

$$f(t-t_0)$$

$$\alpha_n = \frac{1}{T} \int_{t_2}^{t_1} f(t-t_0) e^{-jn\omega_0 t} dt$$

$$\text{Let } t-t_0 = u$$

$$\alpha_{n_s} = \frac{1}{T} \int_{t_1-t_0}^{t_2-t_0} f(u) e^{-jn\omega_0 u} \cdot e^{-jn\omega_0 t_0} du$$


$$\alpha_{n_s} = e^{-jn\omega_0 t_0} \left[\frac{1}{T} \int_{t_1}^{t_2} f(u) e^{-jn\omega_0 u} du \right]$$

$$\alpha_{n_s} = e^{-jn\omega_0 t_0} \alpha_n$$

$$e^{jx} = \cos x + j \sin x$$

$$|e^{-jn\omega_0 t_0}| = 1 \quad (\text{CHANGING MAGNITUDE OF } \angle)$$

EXAMPLE

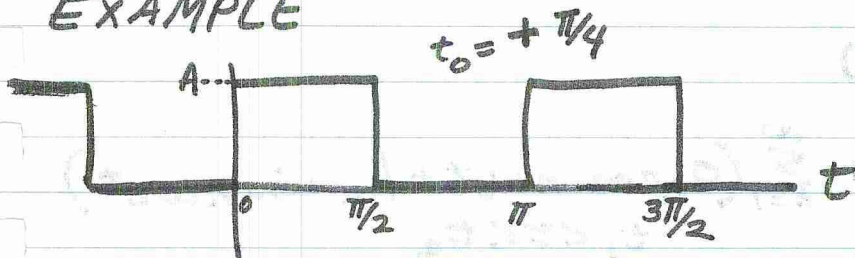

$$\dot{\alpha}_{n_0} = \frac{A}{2} \left(\sin \frac{n\pi}{2} \right) / n\pi/2$$

$$\alpha_n = \frac{A}{2} \frac{\sin \frac{n\pi}{2}}{\frac{n\pi}{2}} \cdot e^{-jn \left(\frac{2\pi}{T} \right) \frac{T}{4}}$$

$$= \frac{A}{2} \frac{\sin \frac{n\pi}{2}}{\frac{n\pi}{2}} e^{-jn \frac{\pi}{2}}$$

$$n=0, \alpha_n = \frac{A}{2}$$

$$n=1; \alpha_n = \frac{A}{2} \frac{2}{\pi} \cdot j$$

$$n=2; \alpha_n = () - 1$$

$$n=3;$$

$$\frac{\sin \frac{n\pi}{2}}{\frac{n\pi}{2}} \text{ IS NEAT}$$


5-21-70

$$x(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t) \quad t_1 < t < t_2$$

LOOK AT

$$a_n \cos n\omega_0 t + b_n \sin n\omega_0 t$$
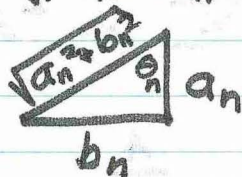
$$\sqrt{a_n^2 + b_n^2} \left(\frac{a_n}{\sqrt{a_n^2 + b_n^2}} \cos n\omega_0 t + \frac{b_n}{\sqrt{a_n^2 + b_n^2}} \sin n\omega_0 t \right)$$



$$\begin{aligned} &= \sqrt{a_n^2 + b_n^2} (\sin \theta_n \cos n\omega_0 t + \cos \theta_n \sin n\omega_0 t) \\ &= \sqrt{a_n^2 + b_n^2} \sin(n\omega_0 t + \theta_n) \\ &= c_n \sin(n\omega_0 t + \theta_n) \end{aligned}$$

$$f(t) = \sum_{n=-\infty}^{\infty} \alpha_n e^{jn\omega_0 t}$$


$$f(t-t_0) = \sum_{n=-\infty}^{\infty} (\alpha_n e^{-jn\omega_0 t_0}) e^{jn\omega_0 t}$$

CHANGES PHASE
OF THE
COMPONENT

$$f(t) = \sum_{n=-\infty}^{\infty} \alpha_n e^{jn\omega_0 t}$$

$$\frac{d}{dt} f(t) = \sum_{n=-\infty}^{\infty} \alpha_n jn\omega_0 e^{jn\omega_0 t}$$

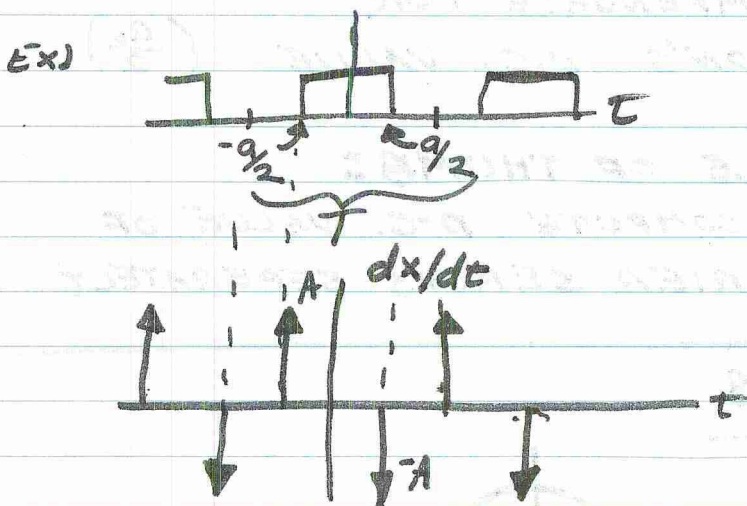THE COEFFICIENTS OF df/dt
ARE $j \alpha_n n \omega_0$



COMPUTE FOURIER COEFFICIENTS
FOR $\frac{dx}{dt}$ ALONE

$$\alpha_n = \frac{1}{T} \int_{-T/2}^{T/2} [A\delta(t + \frac{T}{2}) - A\delta(t - \frac{T}{2})] e^{-jn\omega_0 t} dt$$

$$= \frac{A}{T} [e^{-jn\omega_0 \frac{T}{2}} - e^{-jn\omega_0 \frac{T}{2}}]$$

FOR $x = t$, $\alpha_n = \alpha_n / jn\omega_0$

$$\alpha_n = \frac{A}{jn\omega_0 T} (e^{jn\omega_0 T/2} - e^{-jn\omega_0 T/2})$$

SIFTING PROPERTY OF DELTA FUNCTION

$$\int_{t_1}^{t_2} \delta(t-x) f(t) dt = f(x)$$


$$\begin{aligned} \alpha_n &= \frac{2A}{n\omega_0 T} \sin \frac{n\omega_0 a}{2} \\ &= \frac{Aa}{T} \frac{\sin n\omega_0 a/2}{n\omega_0 a/2} \end{aligned}$$

MUST COMPENSATE FOR
FUNCTION'S D.C. VALUE $\left(\frac{a_0}{2}\right)$


GOOD RULE OF THUMB:

ALWAYS COMPUTE D.C. VALUE OF
A FOURIER SERIES SEPERATELY
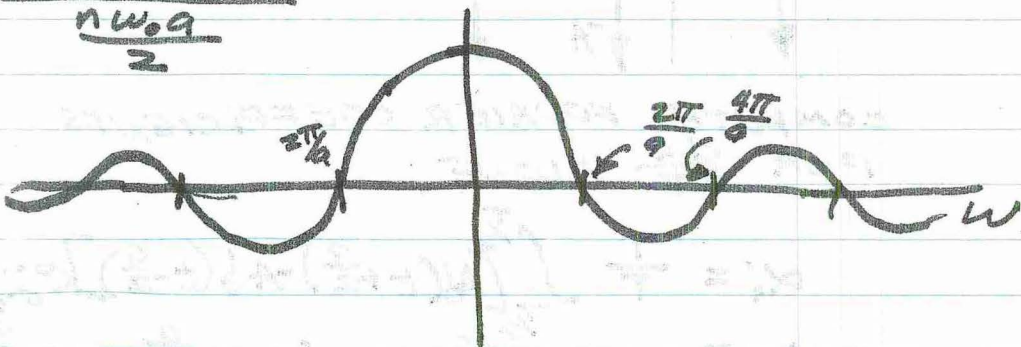
$$\frac{\sin \frac{n\omega_0 a}{2}}{\frac{n\omega_0 a}{2}}$$




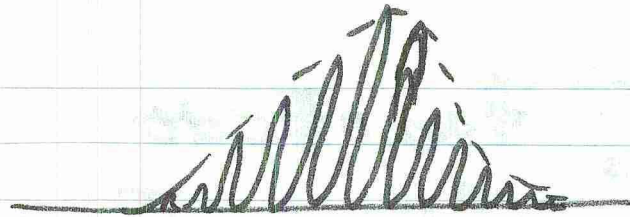0'S OF FUNCTION OCCUR WHEN
 $\frac{\omega a}{2} = \pm n\pi$; $\omega = \pm \frac{2n\pi}{a}$



WITH PULSE TRAIN

INCREASE T , INCREASE LENGTH

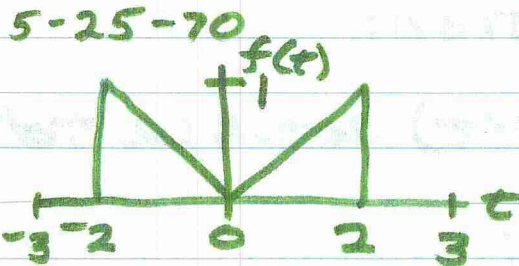

FIND FOURIER EXPANSION

~~$$f(t) = \sum_{n=1}^{\infty} \frac{1}{n^2}$$~~

NEED TO FIND $\{a_n\}$ & $\{b_n\}$
EVEN FUNC. \Rightarrow ALL $b_n = 0$

$$a_n = \frac{2}{T} \int_{-T/2}^{T/2} f(t) \cos n\omega_0 t dt$$

$$T = 6 \Rightarrow \omega_0 = \frac{\pi}{3}$$

$$a_n = \frac{1}{3} \int_{-3}^3 f(t) \cos n \frac{\pi}{3} t dt$$

$$= \frac{1}{3} \left[\int_{-2}^0 -\frac{t}{2} \cos n \frac{\pi}{3} t dt \right.$$

$$\left. + \int_0^2 \frac{t}{2} \cos n \frac{\pi}{3} t dt \right] \text{ (CONT.)}$$

$$a_n = \frac{1}{3} \left[\int_{-2}^0 \frac{t}{2} \cos n \frac{\pi}{3} t dt + \int_0^2 \frac{t}{2} \cos n \frac{\pi}{3} t dt \right]$$

$$= \frac{2}{3} \int_0^2 \frac{t}{2} \cos n \frac{\pi}{3} t dt$$

FOR EVEN FUNCTION:


$$a_n = \frac{4}{T} \int_0^{\frac{T}{2}} f(t) \cos n \omega_0 t dt$$

ODD FUNCTION:

$$f(-t) = -f(t)$$



EVEN FUNCTION:

$$f(t) = f(-t)$$

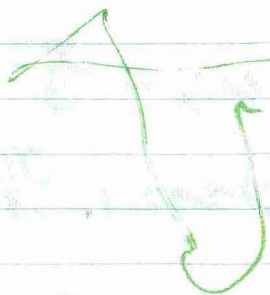

5-26-70

$$a_0 = \frac{2}{T} \int_0^T f(t) dt$$

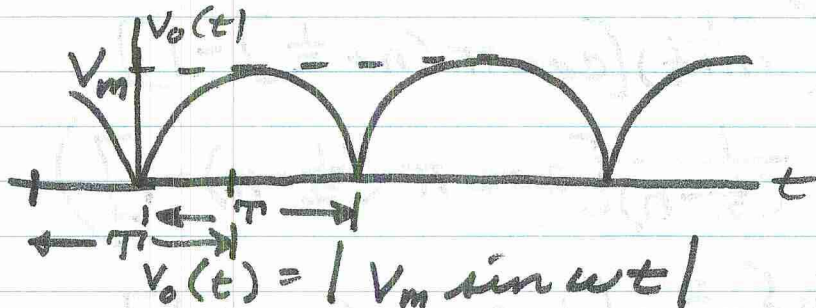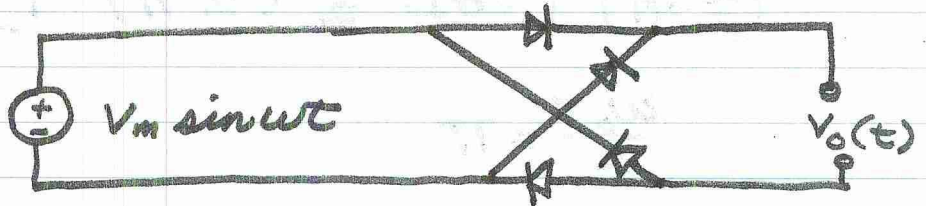

EVEN FUNC \Rightarrow NO SIN TERMS ($a_n b_n = 0$)

$$a_n = \frac{4}{T} \int_0^{\frac{T}{2}} \sin \omega t \cos n \omega_0 t dt$$

$$\omega_0 = 2\omega ; T = \frac{2\pi}{\omega_0}$$

$$a_n = \frac{2}{T} \int_0^{\frac{T}{2}} \sin(\omega + n\omega_0)t dt$$

$$+ \frac{2}{T} \int_0^{\frac{T}{2}} \sin(\omega - n\omega_0)t dt$$

$$\frac{2}{T} \left(\frac{-\cos(2\omega + n\omega_0)t}{\omega + n\omega_0} \Big|_0^{\frac{T}{2}} - \frac{-\cos(\omega - n\omega_0)t}{\omega - n\omega_0} \Big|_0^{\frac{T}{2}} \right)$$

(CONT.)

$$a_n = \frac{2}{\pi \omega_0} \left\{ \frac{-1}{(n+\frac{1}{2})} \left[\cos \frac{\omega_0 t}{2} (n+\frac{1}{2}) - 1 \right] - \frac{1}{(\frac{1}{2}-n)} \left[\cos \frac{\omega_0 t}{2} (\frac{1}{2}-n) - 1 \right] \right\}$$

$$\frac{\omega_0 T}{2} = \pi$$

$$a_n = \frac{V_m}{\pi} \left(\frac{-1}{(n+\frac{1}{2})} \left[\cos \pi (n+\frac{1}{2}) - 1 \right] - \frac{1}{(\frac{1}{2}-n)} \left[\cos \pi (\frac{1}{2}-n) - 1 \right] \right)$$

$$a_n = \frac{V_m}{\pi} \left\{ \frac{2}{2n+1} \left[1 - \cos \pi (n+\frac{1}{2}) \right] + \frac{2}{1-2n} \left[1 - \cos \pi (n-\frac{1}{2}) \right] \right\}$$

$$1) n=0 \Rightarrow a_0 = \frac{4V_m}{\pi} \Rightarrow \text{d.c. VALUE} = \frac{2V_m}{\pi}$$

$$2) n=1 \Rightarrow a_1 = \frac{V_m}{\pi} \frac{4}{3}$$

FIND RATIO OF a_1 TO d.c.:

$$\frac{\frac{4}{3\pi} V_m}{\frac{2}{\pi} V_m} = \frac{2}{3}$$



IF $V_m = 100$
 d.c. = 63.7 V

~~FOR~~ a_n MAY BE SIMPLIFIED

$$a_n = \frac{2V_m}{\pi} \left\{ \frac{1}{2n+1} + \frac{1}{1-2n} \right\}$$

$$= \frac{4V_m}{\pi(1-4n^2)}$$

HALF WAVE RECTIFIER

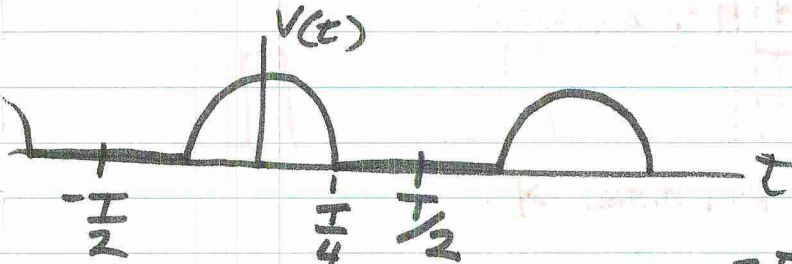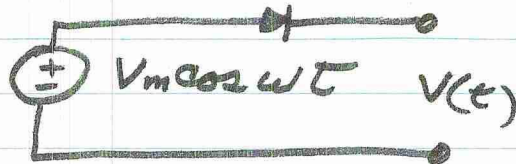

$$T = \frac{2\pi}{\omega}; \omega = \omega_0$$

$$a_n = \frac{4}{T} \int_0^{T/4} \cos \omega t \cos n \omega t dt$$

$$= \frac{2}{T} \int_0^{T/4} [\cos(n+1)\omega t + \cos(n-1)\omega t] dt$$

$$= \frac{2}{T} \left[\frac{\sin(n+1)\omega t}{(n+1)\omega} \Big|_0^{T/4} + \frac{\sin(n-1)\omega t}{(n-1)\omega} \Big|_0^{T/4} \right]$$

(CONT.)

~~$$a_n = \frac{1}{T} \left\{ \frac{\sin(n\pi)}{(n+1)\omega} + \frac{\sin(n\pi)}{(n-1)\omega} \right\}$$~~

~~$$\frac{\sin(n\pi)}{n} = \frac{\pi}{2}$$~~

$$a_n = \frac{1}{\pi} \left\{ \frac{\sin(n+1)\frac{\pi}{2}}{n+1} + \frac{\sin(n-1)\frac{\pi}{2}}{n-1} \right\} \quad n \neq 1$$

$$a_n = 2 \operatorname{Re} \{ \alpha_n \}$$

$$b_n = -2 \operatorname{Im} \{ \alpha_n \}$$

$$\omega_0 T = 2\pi$$

6-1-70



$$a_n = \frac{2Aq}{T} \frac{\sin \frac{n\omega_0 q}{2}}{\frac{n\omega_0 q}{2}}$$


$$A = 10$$

$$q = 10^{-6}$$

$$T = 10^{-3}$$

$$\omega_0 = \frac{2\pi}{T} = 2000\pi$$

PLUG AND CHUG

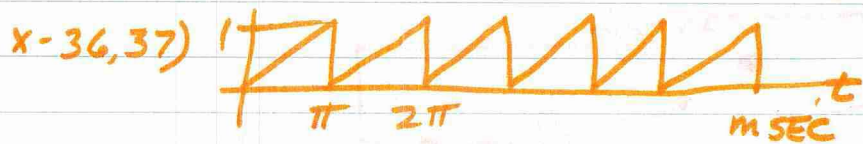


$$f(t) = \frac{a_0}{2} + a_1 \cos \omega_0 t + a_2 \cos 2\omega_0 t + \dots + b_1 \sin \omega_0 t + b_2 \sin 2\omega_0 t + \dots$$

$$\omega_0 = \frac{2\pi}{T} = 2000 \frac{\text{RAD}}{\text{SEC}}$$



only let
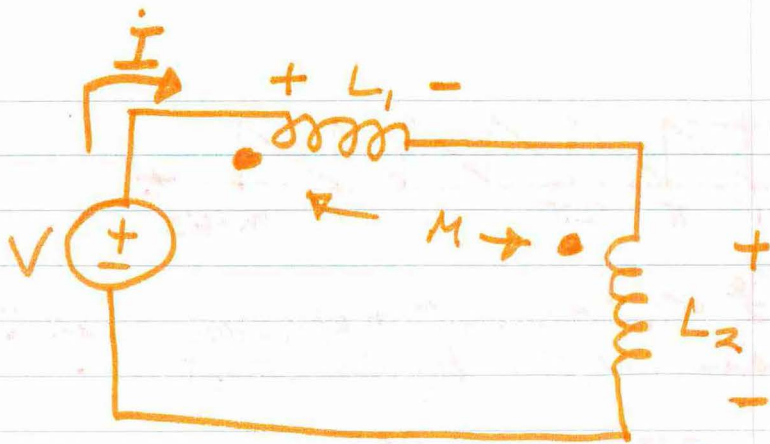
$$f_F(t) = \frac{a_0}{2} + a_1 \cos 1000t + b_1 \sin 1000t$$



WHAT ARE POLARITIES?

USING KIRCHHOFF'S LAW

$$V = I(j\omega L_1)_{\text{SELF}} + I(j\omega M)_{\text{MUT. INDUCED}}$$

$$+ I(j\omega L_2)_{\text{SELF}} + I(j\omega M)_{\text{MUT INDUCED}}$$


$$\frac{V}{I} = Z_{eq} = L_1 + L_2 + 2M = L_{eq}$$

$$\parallel$$

$$j\omega L_{eq}$$

SERIES CONNECTION OF TWO COILS WITH INDUCTANCES $L_1 \neq L_2$ AND MUTUAL INDUCTANCE OF M , GIVEN EQUIVALENT INDUCTANCE OF $L_{eq} = L_1 + L_2 \pm 2M > 0$
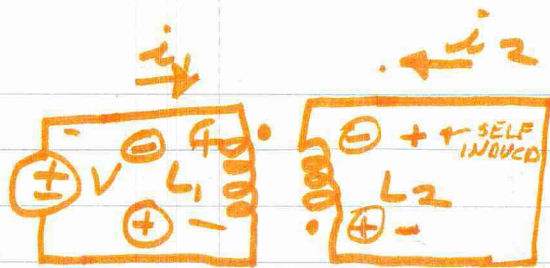
$$\rightarrow \therefore M \leq \frac{L_1 + L_2}{2}$$



$$L_{eq} \quad V = L_{eq} \frac{di_1}{dt}$$

$$V - L \frac{di_1}{dt} + M \frac{di_2}{dt} = 0$$

$$L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} = 0$$


SOLVING YIELDS:

$$V - L \frac{di_1}{dt} + \frac{M^2}{L_2} \frac{di_1}{dt}$$

$$\text{OR } V = \left(L - \frac{M^2}{L_2} \right) \frac{di_1}{dt}$$

$$\therefore L_{eq} = L - \frac{M^2}{L_2} \geq 0$$

$$\rightarrow M \leq \sqrt{L_1 L_2}$$

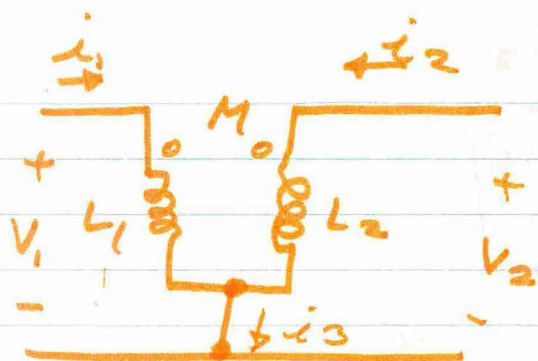

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{d(i_3 - i_2)}{dt}$$


$$V_2 = L_2 \frac{di_2}{dt} + M \frac{d(i_3 - i_2)}{dt}$$

$$V_1 = (L_1 - M) \frac{di_1}{dt} + M \frac{di_3}{dt}$$


$$V_2 = (L_2 - M) \frac{di_2}{dt} + M \frac{di_3}{dt}$$

ANALOGOUS TO
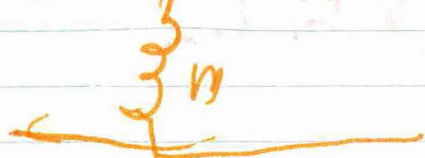
$$\frac{L_1 - M}{m} \quad \frac{L_2 + M}{m}$$





6-2-70

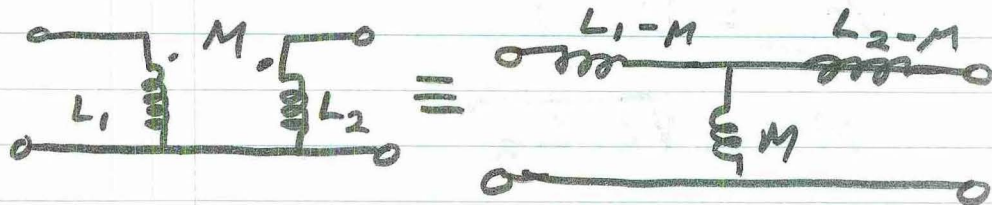

CHANGE DOT POLARITY ON
LEFT CIRCUIT, ^(ONE DOT) CHANGE ALL
SIGNS ON RT. CIRCUIT.

AS AN OPEN CIRCUIT, DON'T KNOW

TWO COILS IN //

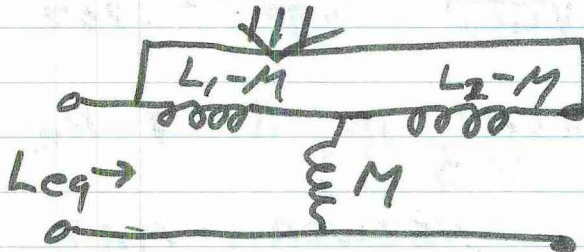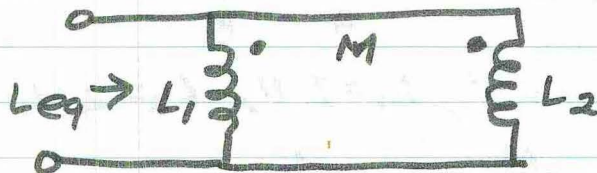

$$L_{eq} = M + \frac{(L_1 - M)(L_2 - M)}{L_1 + L_2 - 2M}$$

$$= \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$


$$M \leq \sqrt{L_1 L_2}$$

$$M_{\text{MAX}} = \sqrt{L_1 L_2}$$

$$M = k \sqrt{L_1 L_2}$$

$k = \text{COEFFICIENT OF COUPLING}$
 ~~$k \leq 1$~~

EXAMPLE:

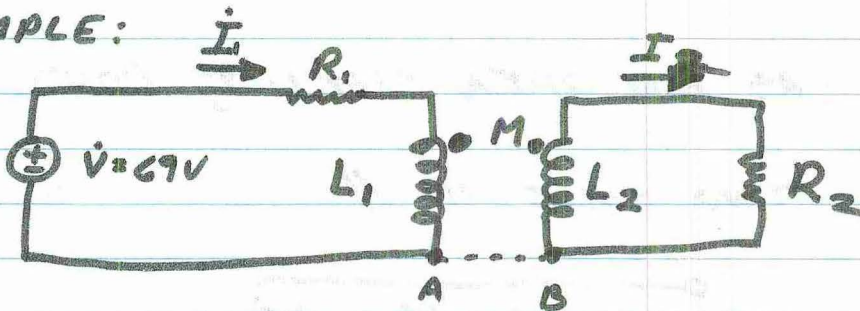



$$\omega = 1; R_1 = 2\Omega; R_2 = 6\Omega; L_1 = 1\text{H}; L_2 = 2\text{H}; M = 1\text{H}$$

$$k = \frac{M}{\sqrt{L_1 L_2}} = \frac{1}{\sqrt{2}} = .707$$

FIND CURRENT IN R_1 & R_2
 (ASSIGN V & i)

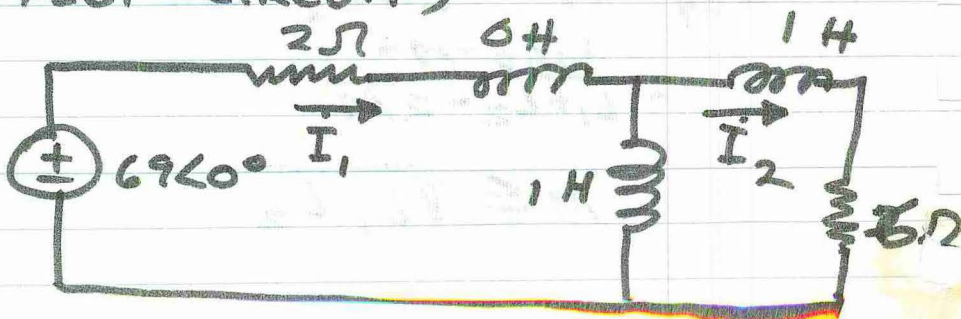(FIND EQ T NETWORK - MAY
 CONNECT A & B AND NOT
 EFFECT CIRCUIT)



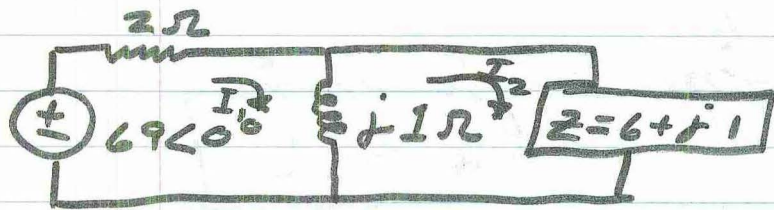

MESH EQUATIONS YIELD

$$69\angle 0^\circ = (2 + j1)I_1 - jI_2$$

$$0 = -jI_1 + (6 + j1)I_2$$


$$I_1 = \frac{6 + j1}{j} I_2 = (2 - j6)I_2$$

$$69 = (2 + j1)I_1 - j(2 - j6)I_2$$

$$I_2 = \frac{69}{10 - j11} = \frac{69\angle 0^\circ}{14.2\angle -45.5^\circ}$$

$$= 4.85\angle 45.5^\circ$$

ETC.

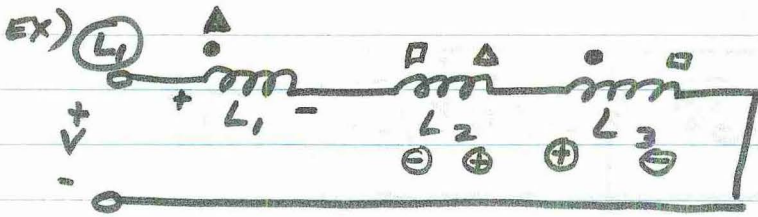



$$M_{12}, M_{23}, M_{13} \neq 0$$

FOR L_1, L_2, L_3 :

$$V = L_1 \frac{di}{dt} + M_{12} \frac{di}{dt} + M_{13} \frac{di}{dt} \Rightarrow L_1$$

$$+ L_2 \frac{di}{dt} - M_{12} \frac{di}{dt} - M_{23} \frac{di}{dt} \Rightarrow L_2$$

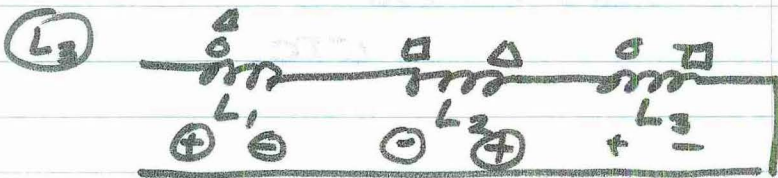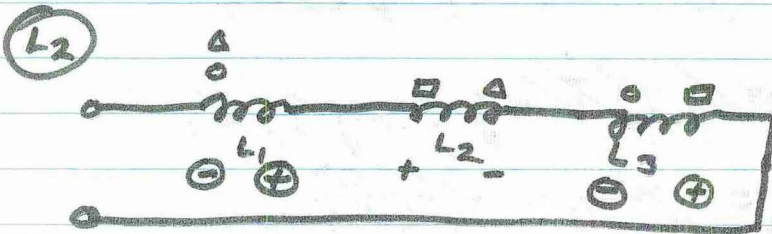
$$+ M_{13} \frac{di}{dt} - M_{23} \frac{di}{dt} + L_3 \frac{di}{dt}$$




ALL SIGNS ON M_{xy} ARE
SAME ALWAYS.

$$L_{eq} = L_1 + L_2 + L_3 - 2M_{12} + 2M_{13} - 2M_{23}$$


6-3-70

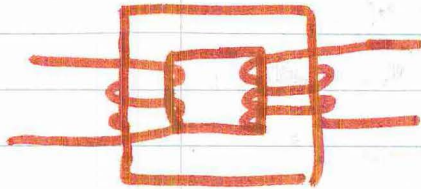

WHERE DO DOTS GO?

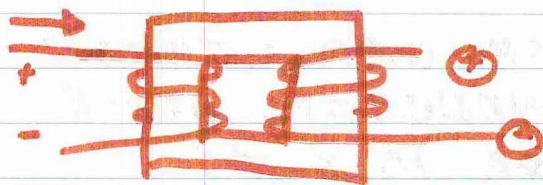


USING LENZ'S
LAW & RT
HAND RULE

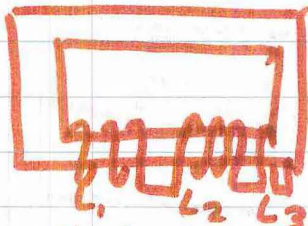


$$L_{eq} = L_1 + L_2 + L_3 + 2M_{12} + 2M_{23} + 2M_{13}$$

MAY MAKE L_{eq} LARGER BY
1) INCREASING # OF COILS
2) SLIDING COILS CLOSER
TOGETHER

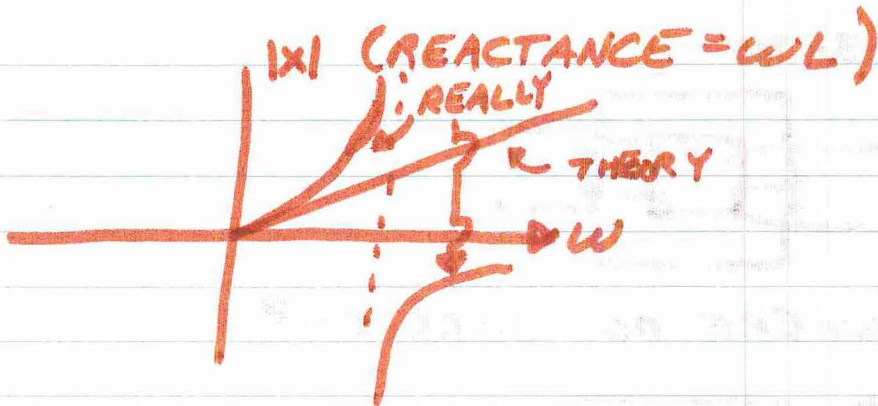
MAY THINK OF EACH COIL, OR
½ CORE AS SEPARATE INDUCTOR.



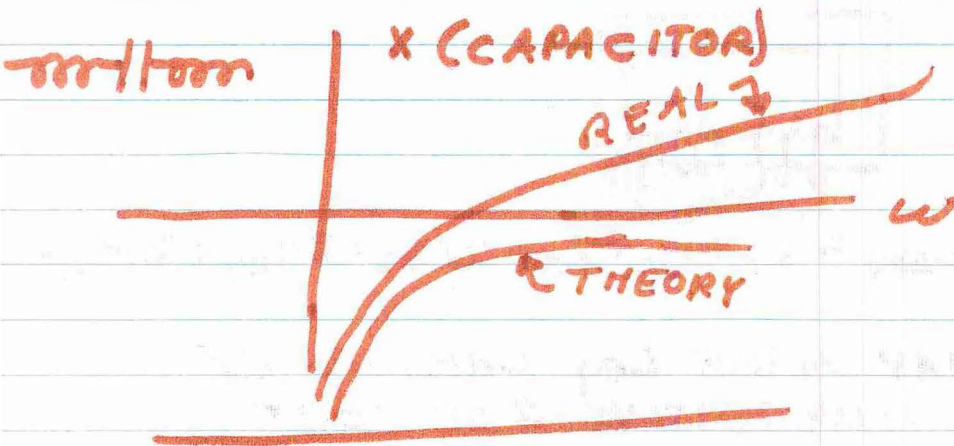BECAUSE OF CAPACITANCE
IN THE INDUCTOR, ABOVE
 ω_0 , INDUCTOR ACTS AS
~~INDUCTOR~~ STRANGE CAPACITOR.



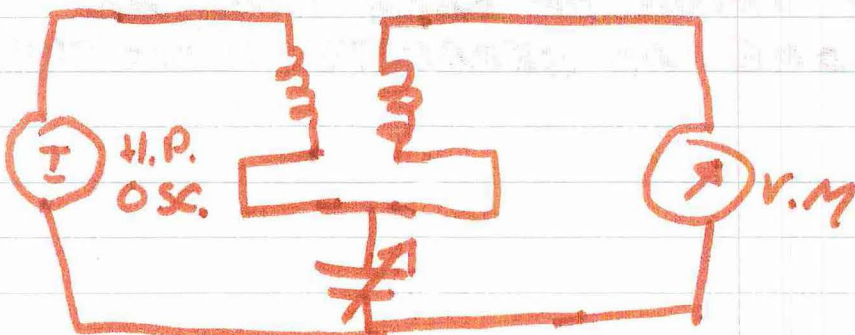MEASUREMENTS ON MUTUAL INDUCTANCE SYSTEMS




VARY C UNTIL VOLTS ON
VOLT METER IS MAXIMUM.
MINIMIZES.

$$M = \omega^2 C \quad (\omega M = \frac{1}{\omega C})$$

CIRCUIT AS RESONANCE.

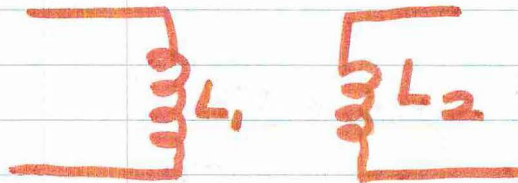
MEASURE INDUCTANCE $\&$ M
USING INDUCTION METER




MEASURE L_{eq} OF TWO
INDUC. IN // OR SERIES
FOR SER.

$$L_{eq} = L_1 + L_2 \pm 2M$$

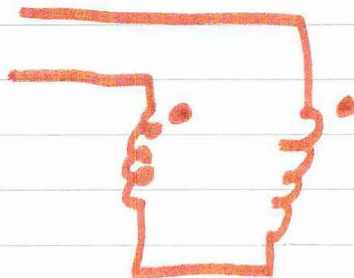
$L_1 = 2; L_2 = 5; L_{eq} = 1$
 $\therefore M = 3$. CIRCUIT IN
SERIES



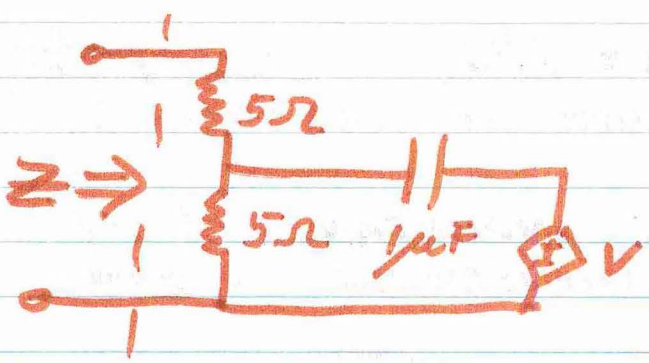INDUCTORS LESS IDEAL THAN RESIS.,
CAPAC., TRANSISTOR, ETC.
MUST SIMULATE L:



$$Z = 10^4 + j\omega 25$$

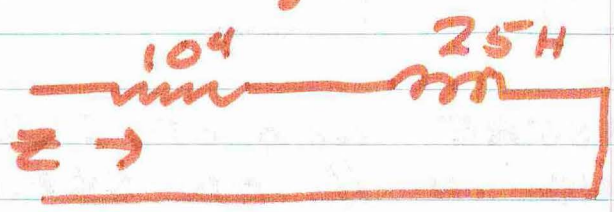


6-4-70


REVIEW

6-8-70


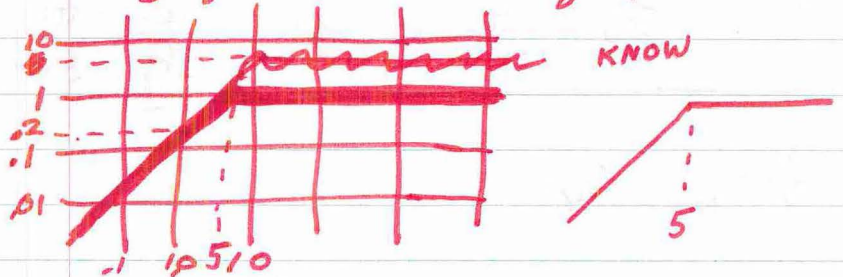
$$H(j\omega) = \frac{j\omega}{5 + j\omega} = .2 \frac{j\omega}{1 + j\frac{\omega}{5}}$$




PICK A FREQ, LIKE $\omega = 1$

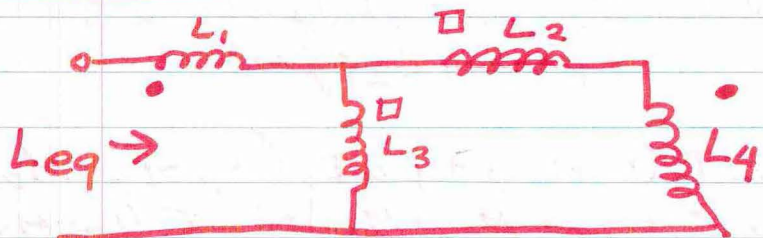

FIND L_{eq}

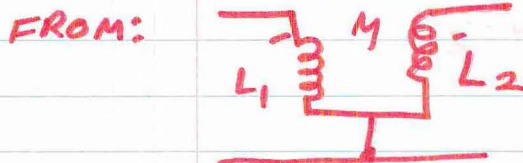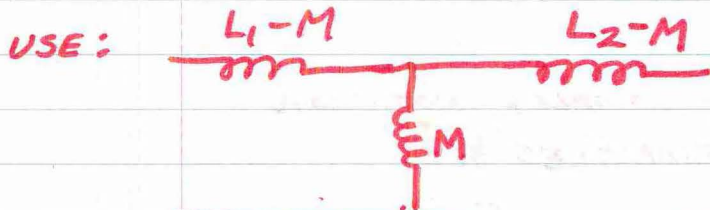

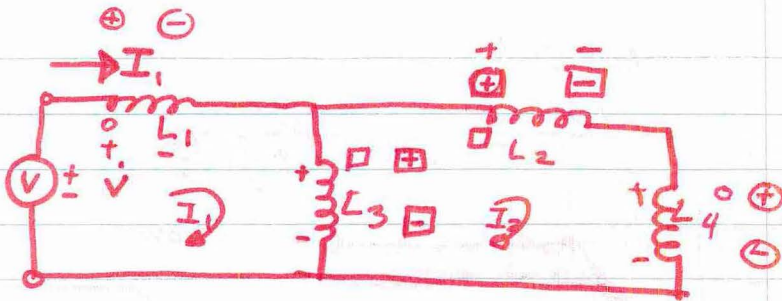

$$\frac{V}{I} = j\omega L(\text{eq})$$

$$V = I_1 j\omega L_1 + j\omega M_{14} I_2 + j\omega L_3 (I_1 - I_2) + j\omega M_{23} I_2$$

$$0 = -j\omega L_3 (I_1 - I_2) - j\omega M_{23} I_2 + j\omega L_2 I_2 + j\omega M_{23} (I_1 - I_2) + j\omega L_4 I_2 + j\omega M_{14} I_1$$

$$V = j\omega I_1 (L_1 + L_3) + j\omega I_2 (M_{14} - L_3 + M_{23})$$

$$0 = j\omega I_1 (-L_3 + M_{23} + M_{14}) + j\omega I_2 (L_3 - M_{23} + L_2 - M_{23} + L_4)$$

COVERED
~~I-A-C ANALYSIS~~
~~1) PHASORS - COMPLEX NOTATION~~
~~POWER TRIANGLES & ST~~

$$\text{COV } P_{\text{MAX RMS}} = \frac{E_g^2}{4 R_g}$$

COVERED

I) A-C ANALYSIS

A) PHASORS

B) COMPLEX REPRESENTATION

1) RECT. FORM

2) POLAR FORM

II) POWER IN A-C CIRCUITS

A) EQUATIONS FOR

B) MAXIMUM POWER & IMPEDENCE MATCHING

→ III) TRANSFER FUNCTIONS

A) BODE DIAGRAM

1) MAGNITUDE PLOTS (LOG-LOG)

2) PHASE PLOTS (SEMI-LOG)

B) POLE-ZERO PATTERNS

1) NARROW BAND NETWORKS

2) HOW TO FIND MAGNITUDE } FROM

3) HOW TO FIND PHASE } FROM

IV) FOURIER ANALYSIS

A) COMPLEX COEFFICIENTS

B) ~~WITH~~ SIN-COSINE COEFFICIENTS

C) PROPERTIES

1) SHIFTING

2) EVEN & ODD FUNCTIONS

V) MUTUAL INDUCTANCE

A) DOT POLARITY & HOW TO COPE WITH IT


B) EQUIVALENT T CIRCUIT

time function

phasor


complex notation

$$v(t) = 100 \cos 377t \text{ V}$$

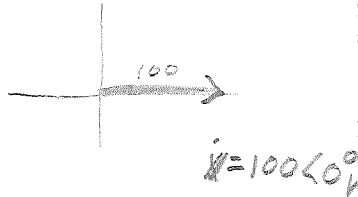


$$100 \text{ V}$$
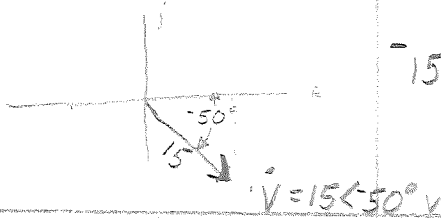
$$v(t) = 15 \cos(100t - 50^\circ) \text{ V}$$




$$15j \sin 50^\circ + 15 \cos 50^\circ$$
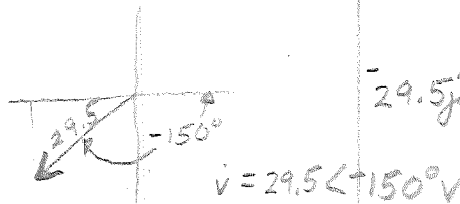
$$v(t) = 29.5 \cos(2\pi t - 150^\circ) \text{ V}$$




$$29.5j \sin 150$$
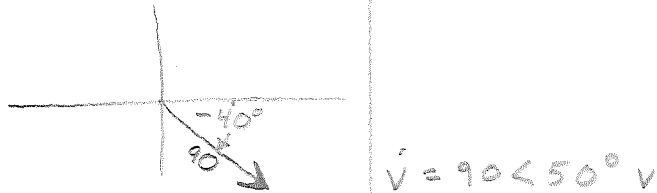
$$v(t) = 90 \sin(10t + 50^\circ) \text{ V}$$




$$V = 90 \angle 50^\circ \text{ V}$$
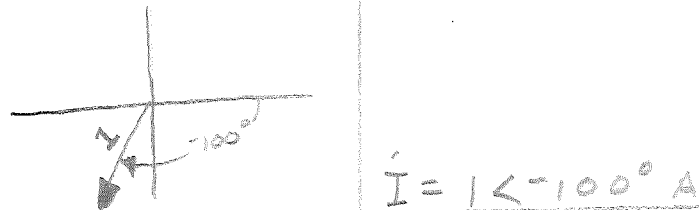
$$i(t) = \cos(5t - 100^\circ) \text{ A}$$




$$I = 1 \angle -100^\circ \text{ A}$$
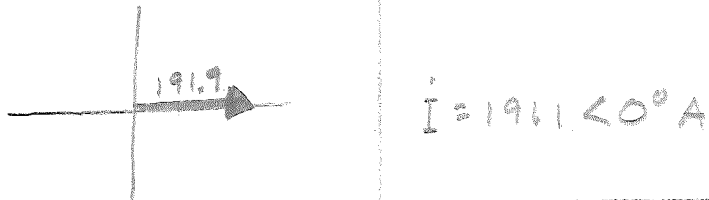
$$i(t) = 191.1 \cos(2\pi \cdot 10^6 t) \text{ A}$$




$$I = 191.1 \angle 0^\circ \text{ A}$$
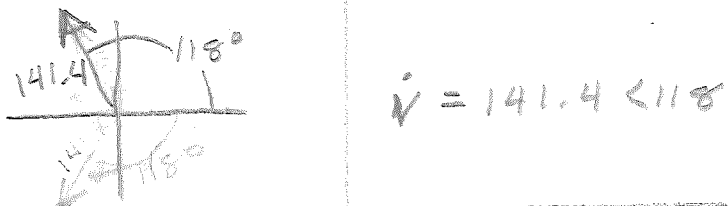
$$v(t) = 141.4 \sin(40t + 208^\circ) \text{ V}$$



$$V = 141.4 \angle 118$$

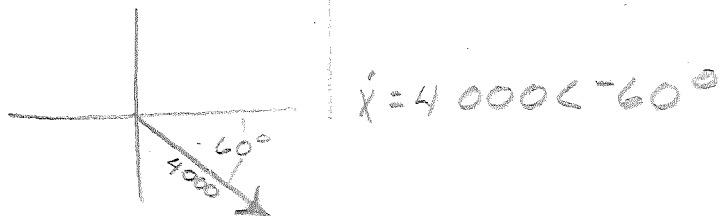

$$V = 4000 \angle -60^\circ$$

Time function

Phasor

Complex notation

$$v(t) = 100 \cos 377t \text{ V.}$$



$$\dot{V} = 100 \angle 0^\circ \text{ V.}$$

$$v(t) = 15 \cos(100t - 50^\circ) \text{ V.}$$




$$\dot{V} = 15 \angle -50^\circ \text{ VOLTS}$$

$$v(t) = 29.5 \cos(2\pi t - 150^\circ) \text{ V}$$



$$\dot{V} = 29.5 \angle -150^\circ \text{ VOLTS}$$
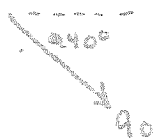
$$v(t) = 90 \sin(10t + 50^\circ) \text{ V.}$$



$$\dot{V} = 90 \angle -40^\circ \text{ V.}$$

$$i(t) = \cos(5t - 100^\circ) \text{ A.}$$



$$\dot{I} = 1 \angle -100^\circ \text{ A.}$$

$$i(t) = 191.1 \cos(2\pi \cdot 10^6 t) \text{ A.}$$



$$\dot{I} = 191.1 \angle 0^\circ \text{ V.}$$

$$v(t) = 141.4 \sin(40t + 208^\circ) \text{ V.}$$



$$\dot{V} = 141.4 \angle +118^\circ \text{ V.}$$

$$v(t) = 4000 \sin(2000t + 60^\circ) \text{ V}$$



$$\dot{V} = 4000 \angle 60^\circ \text{ V.}$$

Change to	polar form		
	Angle	Magnit.	polar form
$j6$	90°	6	$6 \angle 90^\circ$
$1-j2$	63.4°	2.24	$2.24 \angle -63.4^\circ$
$-1-j2$	116.6°	2.24	$2.24 \angle -116.6^\circ$
$3+j4$	53.2°	5	$5 \angle 53.2^\circ$
$4.7+j6.3$	53.3°	7.81	$7.8 \angle 53.5^\circ$
$-11.3+j4$	70.5°	12.0	$12.0 \angle 70.5^\circ$

Change to	polar form	Angle	magnit.	polar form
$j6$		90°	6	$6 / 90^\circ$
$1-j2$		-63.4°	2.23	$2.23 / -63.4^\circ$
$-1-j2$		243.4°	2.23	$2.23 / 243.4^\circ$
$3+j4$		53.1°	5	$5 / 53.1^\circ$
$4.7+j6.3$		53.3°	7.86	$7.86 / 53.3^\circ$
$-11.3+j4$		170.5°	12	$12 / 170.5^\circ$

$$\begin{array}{r} 180 \\ - 63.4 \\ \hline 243.4 \end{array}$$

$$\begin{array}{r} 180.0 \\ - 19.5 \\ \hline 170.5 \end{array}$$

4-8-70

Note the second integral is zero because the integrand, $\frac{1}{2} \sin(2\omega t)$, is just a sinusoid and it is integrated over two periods.

So

$$P_{avg} = \frac{VI \cos \theta_z}{4\pi} \int_0^{2\pi} d(\omega t) + \frac{VI \cos \theta_z}{4\pi} \int_0^{2\pi} \cos(2\omega t) d(\omega t)$$

The second integral here is also zero for the same reason

$$\text{So: } P_{avg} = \frac{VI \cos \theta_z}{4\pi} [2\pi] = \boxed{\frac{VI \cos \theta_z}{2}}$$

When we write P without the subscript, we are meaning P_{avg} unless otherwise specified.

So we see

$$P = \frac{VI \cos \theta_z}{2} = \frac{V}{\sqrt{2}} \cdot \frac{I}{\sqrt{2}} \cos \theta_z = V_{eff} I_{eff} \cos \theta_z$$

Since $V_{eff} = \frac{1}{\sqrt{2}} V$ for a sinusoid. We may see the formula for power written then two ways.


$$P = VI \cos \theta_z \quad \text{and} \quad P = \frac{VI \cos \theta_z}{2}$$

In the first case V and I are PEAK values while in the second case they are RMS values of the sinusoid.

Power factor

The quantity θ_z is called power factor. It relates the power in the circuit to the volt-ampere product.

We may draw a POWER TRIANGLE.

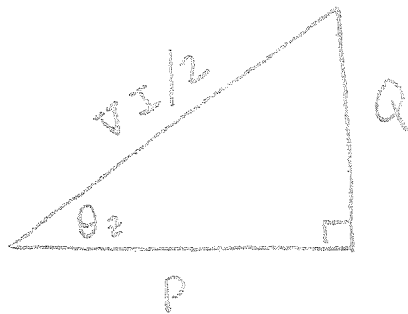

Note that θ_z is determined entirely by the nature of the .

In the diagram above (i.e., the power triangle) P is the real power in the circuit measured in WATTS, Q is known as the reactive power (not really power) measured in VARs.

The product $\frac{VI}{2}$ is called APPARENT POWER; this is measured in volt-amperes.

EXAMPLE (Students to work)



$i = 5 \cos(377t) \text{ A.}$

Compute the power in the circuit first by $\frac{I^2 R}{2}$.

$$P = \frac{I^2 R}{2} = \frac{5^2 \times 5}{2} = \boxed{62.5 \text{ W}}$$

Now check this by $P = \frac{VI}{2} \cos \theta_z$

$$Z = \underline{5 + j2} = \underline{5.39 \angle 21.8^\circ}$$

$$V = IZ = \underline{26.9 \angle 21.8^\circ}$$


$$\theta_z = \underline{21.8^\circ}$$

$$\text{Power factor, } \cos \theta_z = \underline{0.5}$$

$$P = \frac{VI}{2} \cos \theta_z = \underline{\hspace{2cm}} \text{ (should be } 62.5 \text{ W)}$$

Maximum Power Transfer

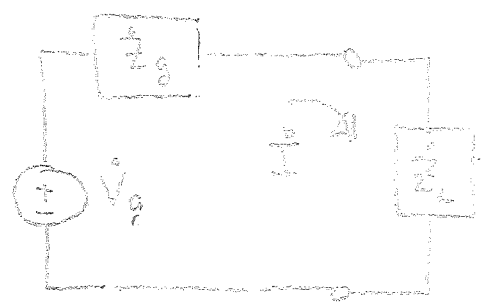Question: what should Z_L be so that maximum power is extracted from the source?




SOURCE

$$Z_L = R_L + jX_L$$

$$P_i = |I|^2 R_L \quad (\text{here } I_0 \text{ is a phasor value})$$

We want to maximize P_i with respect to Z_L

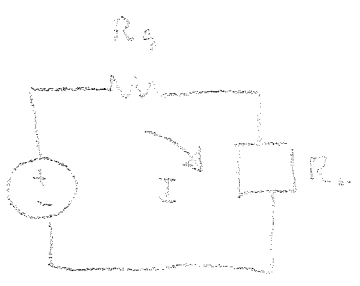Special case Z_g is real = $R_g + j0$ and $Z_L = R_L + j0$



$$P = I^2 R_L$$

$$I = \frac{V_g}{R_g + R_L}$$

$$P = \frac{V_g^2 R_L}{(R_g + R_L)^2}$$

$$\frac{dP}{dR_L} = \frac{(R_g + R_L)^2 V_g^2 - V_g^2 R_L \cdot 2(R_g + R_L)}{(R_g + R_L)^4}$$


$$\frac{V_g^2 (R_g^2 + 2R_g R_L + R_L^2 - 2R_L(R_g + R_L))}{(R_g + R_L)^4}$$

$$P_{\text{MAX}} = \frac{V_{\text{S}}^2}{4 R_{\text{S}}}$$

TO GET MAX PWR. WHEN R_{L} IS FIXED $\neq R_{\text{S}}$ VARIABLE
IS $R_{\text{S}} = 0$

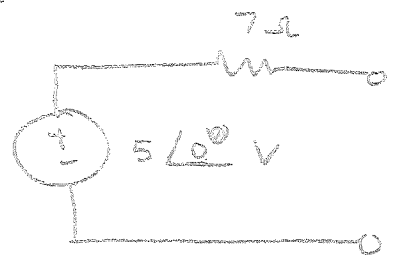
Q. 2.6

What is the maximum power which may be drawn from the sources below? (V_{RMS})




$P_{max} = \underline{\hspace{2cm}} \text{ W.}$

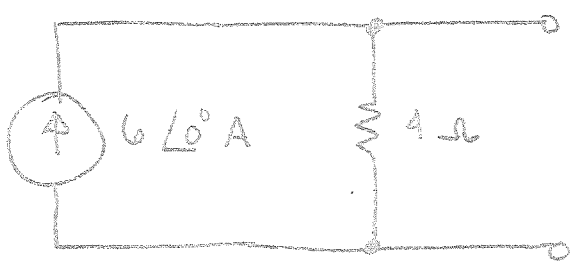What is the maximum power which may be drawn



$P_{max} = \underline{36} \text{ W.}$

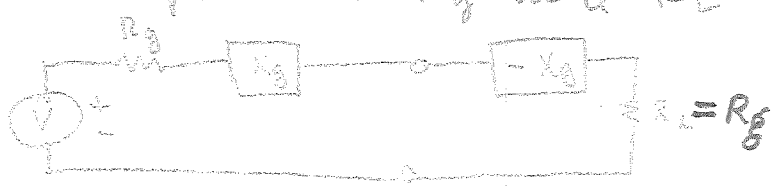
Now if the source impedance is complex, we may ~~not~~ use a complex load impedance to extract maximum power in the following way. ~~But~~ Let the reactance of the load equal the negative of the reactance of the source, then all that remains in the series path is R_g and R_L



**FOR MAX PWR.,
USE COMPLEX
CONJUGATE OF
 Z_g .
 $P_{max} = \frac{V_g^2}{2R_g}$**

$$P_{MAX} = \frac{V_g^2}{4R_g} \text{ or } V_{g,eff} \text{ OR } P_{MAX} = \frac{V_g^2}{8R_g} \Rightarrow V_g = \text{MAGNITUDE}$$

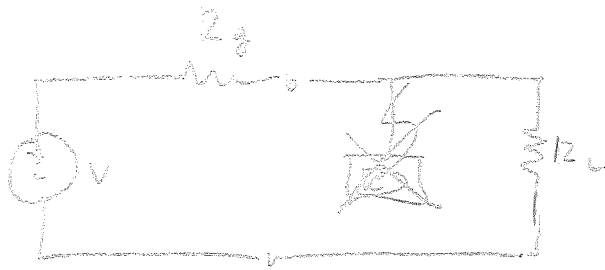So if $X_L = -X_g$ the circuit reduces to




), which should be how
 lol.

$$R_L = \underline{\hspace{2cm}}$$

Thus to get maximum power from a source which has complex impedance. Set $Z_L = R_g - jX_g$

$$Z_L = Z_g^*$$

Ex.

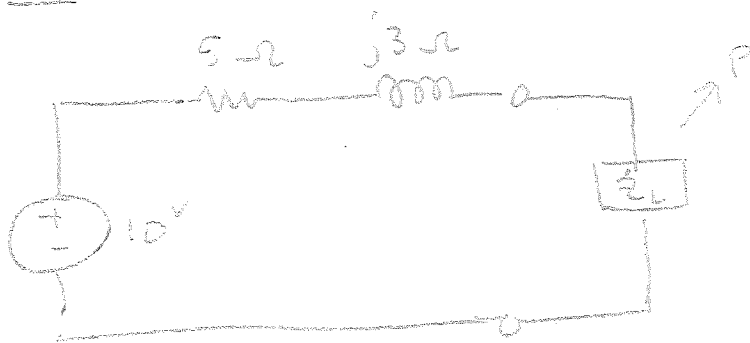

for $P = P_{max}$
 what should the
 value of Z_L be?



$$Z_L = \underline{\hspace{2cm}}$$

Driving point impedance and current in an R-L-C series circuit.


$$Z(\omega) = R + j(\omega L - \frac{1}{\omega C})$$

$\omega_r \hat{=}$ (definition) frequency where $\theta_z = \tan^{-1} \frac{X}{R} = 0$

$$\omega_r L - \frac{1}{\omega_r C} = 0 \quad \omega_r = \sqrt{\frac{1}{LC}}$$


At $\omega > \omega_r$, the impedance is inductive

$\omega < \omega_r$ " " " Capacitive

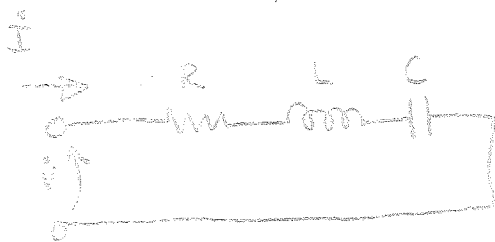

$$\dot{I} = \frac{\dot{V}}{R + j(\omega L - \frac{1}{\omega C})}$$

As a function of frequency $|\dot{I}|$ is shown below

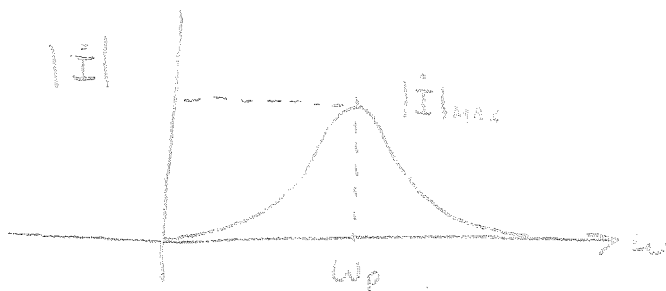

Note that $|\dot{I}|$ is maximum when $|Z|$ is minimum.

min $|Z| = R$, at $\omega = \omega_r$, then

$$\boxed{\omega_p = \omega_r}$$

$$|\dot{I}|_{\max} = \boxed{\frac{|\dot{V}|}{R}}$$

EE 3117
NOTES (2)

The half power frequencies ~~occur~~ are those where $|I|^2 = \frac{|I|_{\max}^2}{2}$ or when $|Z| = \sqrt{2} Z_{\min} = \sqrt{2} R$

$$\sqrt{2} R = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$2R^2 = R^2 + (\omega L - \frac{1}{\omega C})^2$$

$$R^2 = (\omega L - \frac{1}{\omega C})^2$$

$$\pm R = \omega L - \frac{1}{\omega C}$$

using + sign

$$\omega R C = \omega^2 L C - 1$$

$$\omega = \frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

one of these roots is neg.
disregard it

~~use~~
call the positive root the upper half power freq, ω_U

$$\omega_U = \frac{R}{2L} + \sqrt{\frac{1}{LC} + \left(\frac{R}{2L}\right)^2}$$

Using - sign

$$\omega = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

one of these roots is neg.

use + root, call it the lower half power frequency, ω_L

EE 202
NOTES (3)

$$\omega_L = \sqrt{\frac{1}{LC} + \left(\frac{R}{2L}\right)^2} - \frac{R}{2L}$$

Calling $\frac{1}{LC} = \omega_r^2$ and $\frac{R}{2L} = a$

$$\omega_L = \sqrt{\omega_r^2 + a^2} - a$$

$$\omega_U = \sqrt{\omega_r^2 + a^2} + a$$

Define bandwidth BW as $\omega_U - \omega_L$

$$BW = 2a = \boxed{\frac{R}{L}}$$

Thus we can see that larger R gives larger bandwidth, i.e., the circuit is less selective.

Define $Q_0 = \frac{\omega_r L}{R}$; $\left(\frac{X_L}{R}\right)$

$$Q_0 = \frac{\omega_L}{R/L} = \boxed{\frac{\omega_L}{BW}} \quad \leftarrow \text{relates } Q_0, BW, \text{ and } \omega_r$$

Ex. $R = 10 \Omega$ $L = 1.0 \text{ mH}$ $C = .01 \mu\text{F}$

$$\omega_r = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{10^{-4} \cdot 10^{-8}}} = \sqrt{10^{12}} = \boxed{10^6 \frac{\text{rad}}{\text{sec}}} \\ (159 \text{ kHz})$$

EE 202
NOTES (4)

$$BW = \frac{R}{L} = \frac{100}{10^{-4}} = \boxed{10^6 \text{ rad/sec}}$$

$$Q = \frac{\omega_r}{\Delta\omega}$$

$$Q = \frac{\omega_r}{BW} = \frac{10^6}{10^4} = \boxed{100}$$

$$= 5000$$

Half power frequencies

$$\omega_L = \sqrt{10^{12} + 25 \times 10^6} - 5000$$


$$\approx 10^6 - 5000 \text{ rad/sec}$$

$$\omega_U \approx 10^6 + 5000 \text{ rad/sec}$$

E Sc 2

Homework

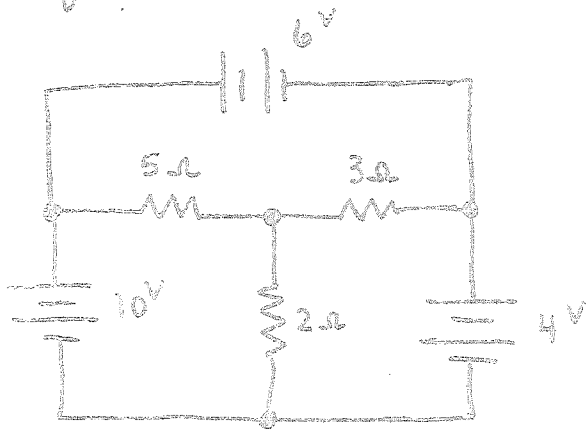1. Solve the circuit shown by writing mesh equations.




2. $V_1(t) = 169 \sin(377t + 30^\circ) \text{ V}$


$$V_2(t) = 47.2 \sin(377t - 41^\circ) \text{ V}$$

Find $V_1(t) + V_2(t)$ as a sinusoid

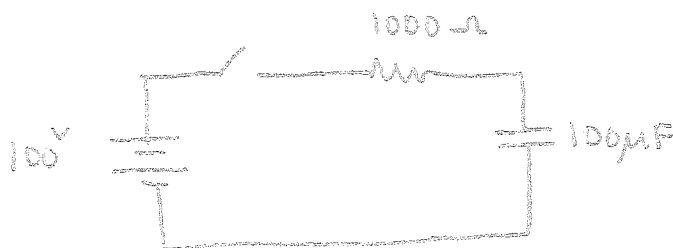3. Find the ~~power~~^{energy} dissipated by the resistor as the capacitor charges up. C is initially uncharged.




2.2 - 4.0 V

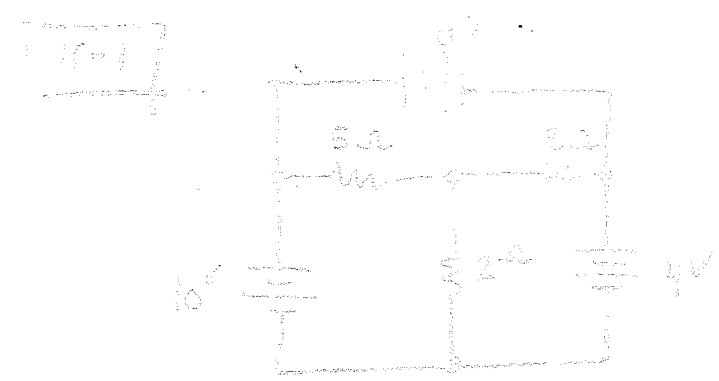

Note: for purposes of solution of this problem it is seen that only 2 voltage sources are of interest. The remainder

Use 10V and 4V source

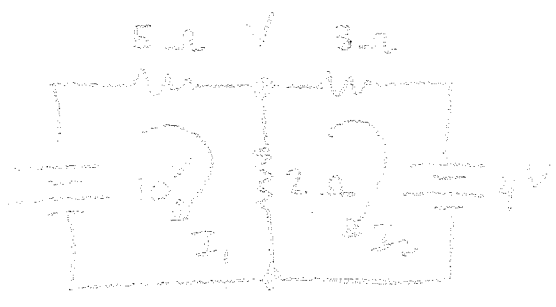

Using mesh currents

$$10 = 7I_1 - 2I_2$$

$$-4 = -2I_1 + 5I_2$$

DIVIDE FIRST EQUATION BY 2, SECOND BY 5

$$\begin{aligned} 5 &= 3.5 I_1 - I_2 \\ -0.8 &= -0.4 I_1 + I_2 \end{aligned}$$

} Add eqns

$$4.2 = 3.1 I_1 \Rightarrow$$

$$I_1 = \frac{4.2}{3.1} = 1.3548 \text{ A}$$

FROM FIRST EQUATION

$$I_2 = 3.5 I_1 - 5$$

$$= 3.5 \times 1.3548 - 5$$

$$= 4.7413 - 5 = -0.2586 \text{ A}$$

Use 2 eqns

Esercizi
Dimensioni

K-2


$$v_1(t) = 169 \sin(377t + 30^\circ) \Rightarrow \dot{V}_1 = 169 \angle 30^\circ - 90^\circ = 169 \angle -60^\circ \text{ V}$$

$$v_2(t) = 47.2 \sin(377t - 41^\circ) \Rightarrow \dot{V}_2 = 47.2 \angle -41^\circ - 90^\circ = 47.2 \angle -131^\circ \text{ V}$$

$$\dot{V}_1 = 84.5 - j146.5$$

$$\dot{V}_2 = -31.3 - j35.3$$
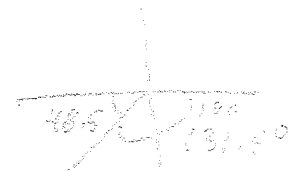
$$\dot{V}_1 + \dot{V}_2 = 53.2 - j181.8 = 189.5 \angle -73.7^\circ$$



$$\Downarrow$$

$$v_1(t) + v_2(t) = \boxed{189.5 \sin(377t - 73.7^\circ) \text{ V}}$$

K-3 (WORKED IN CLASS)

$$RC = 10^{-4} \cdot 10^3 = 0.1$$

$$i(t) = \frac{100}{1000} e^{-\frac{t}{RC}} = 0.1 e^{-10t} \text{ A}$$

$$p_R(t) = [i(t)]^2 R = 10^3 \times 10^{-2} e^{-20t} \quad \omega_1 = 10 e^{-10t}$$

$$W = \int_0^{0.1} p_R(t) dt = \int_0^{0.1} 10 e^{-20t} dt = \frac{10}{-20} (e^{-20 \cdot 0.1} - 1) = \boxed{0.45 \text{ Joule}}$$

SOLUTION

$$\begin{aligned}
 \frac{1}{2} &= \frac{1}{2} \\
 \frac{1}{2} &= \frac{1}{2}
 \end{aligned}$$

Let's assume the angle is θ .

$$\frac{1}{2} = \frac{1}{2} \cos \theta$$

$$\cos \theta = 1$$

$$\theta = 0^\circ$$

$$\begin{aligned}
 \frac{1}{2} &= \frac{5 \cos 30^\circ}{5 \cos \theta} = \frac{5 \cdot \frac{\sqrt{3}}{2}}{5 \cos \theta} = \frac{\frac{5\sqrt{3}}{2}}{5 \cos \theta} \\
 &= \frac{5\sqrt{3}}{2 \cdot 5 \cos \theta} = \frac{\sqrt{3}}{2 \cos \theta} \\
 &= 2.5 \Rightarrow \cos \theta = 0.4
 \end{aligned}$$

$$\theta = \cos^{-1}(0.4) = 66.4^\circ$$


$$\theta = 66.4^\circ$$

4-22-70

HOMEWORK
 DUE 4.27.70

X-14

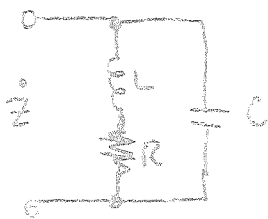Find the driving point impedance as a function of ω




$$L = 30 \text{ mH}$$

$$C = 0.5 \mu\text{F}$$


$$R = 10 \Omega$$

X-15

Find the r.m.s. value of the waveform shown.

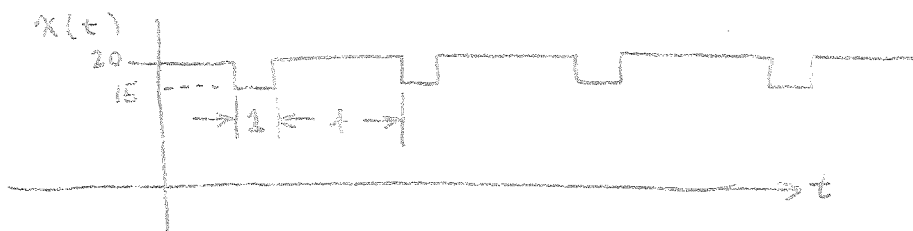
X-16

Find the r.m.s. value of $i(t)$

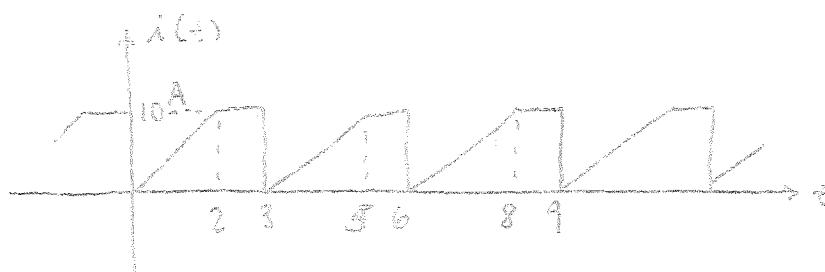


EE 202-- HOMEWORK

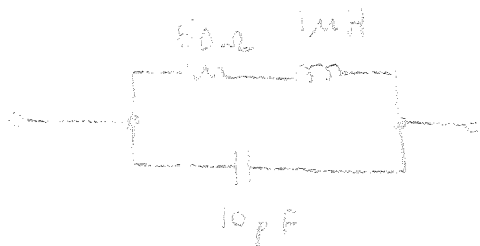
X-10 Find the frequency, where the circuit becomes
 has a real impedance



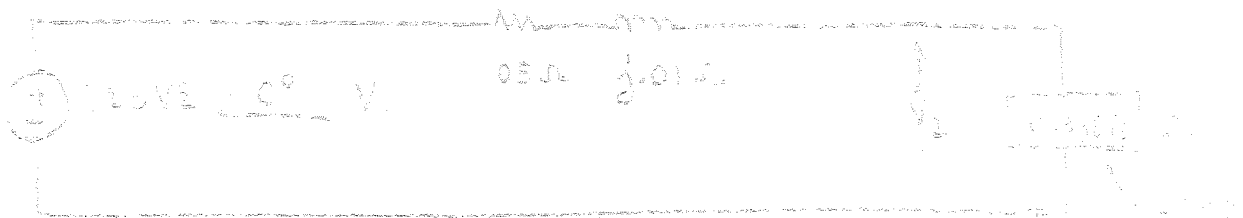X-11 SOLVE FOR THE POWER AT THE
 LOAD. FIND \hat{V} .



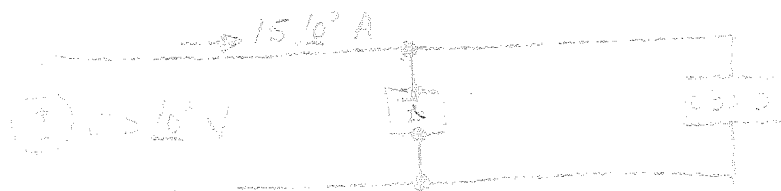
X-12 The load shown dissipates 100 W.
 It's power factor is 0.8 and the load
 is known to be inductive. Find \hat{V} .



EE DEPT
RPI
4-28-70

EE 202
Answers to homework

X-14

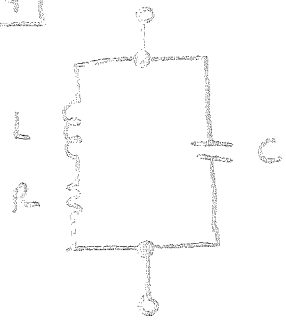


$$Z = \frac{(R + j\omega L) \frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}}$$

$$= \frac{R + j\omega L}{1 - \omega^2 LC + j\omega RC}$$

$$= \frac{10 + j\omega 0.03}{1 - \omega^2 \cdot 0.03 \times 5 \times 10^{-7} + j\omega 5 \times 10^{-2}}$$

X-15

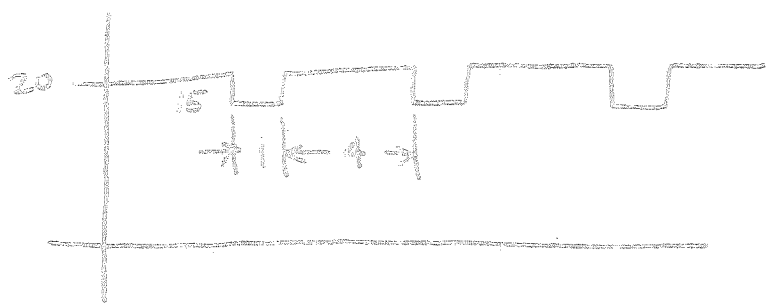

$$X_{rms} = \sqrt{\frac{1}{5} (20^2 \cdot 4 + 15^2)} = \sqrt{\frac{1}{5} (2250 + 200)}$$

$$= \sqrt{\frac{1}{5} 1825} = \sqrt{365} = 19.1$$


EE 202
RJE
4-29-70

homework answers

X-16

$$\begin{aligned} I &= \sqrt{\frac{1}{3} \left[\int_0^2 25t^2 dt + 100 \right]} \\ &= \sqrt{\left\{ \frac{1}{3} [25 \times 4 + 100] \right\}} = \sqrt{\left\{ \frac{200}{3} \right\}} = \sqrt{66.7} \\ &= \boxed{8.15 \text{ A.}} \end{aligned}$$

X-17

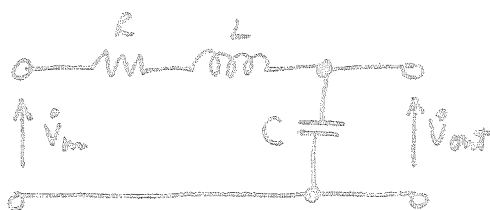

$$\begin{aligned} R &= 0.1 \Omega \\ L &= 2 \text{ H} \\ C &= 0.5 \text{ F} \end{aligned}$$

$$\frac{1}{2} H(\omega) = \frac{1}{1 - \omega^2 LC + j\omega RC} = \boxed{\frac{1}{1 - \omega^2 5 \times 10^{-9} + j\omega 5 \times 10^{-9}}}$$

$$\omega_p = \omega_r \quad \omega_r = \sqrt{\frac{1}{5 \times 10^{-9}}} = \sqrt{\frac{10^9}{5}}$$


$$= \sqrt{2} \times 10^3 = \boxed{1414 \text{ rad/sec.}}$$

Note: This problem was discussed in detail in class!

EE 202
homework answers

X-1P

Scott 16.12

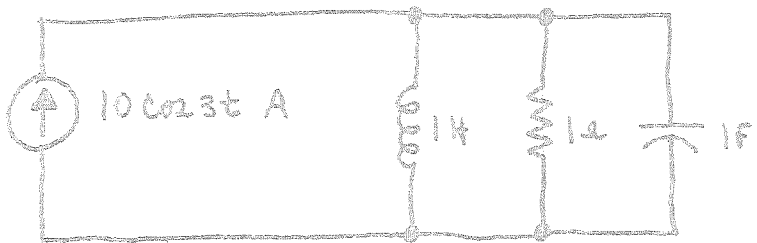

$$Z_{eq} = \frac{1}{j\omega \cdot 1 + 1 + \frac{1}{j\omega}} = \frac{j\omega}{1 - \omega^2 + j\omega}$$


$$Z(3) = \frac{j3}{1 - 9 + j3} = \frac{j3}{-8 + j3} = \frac{3 \angle 90^\circ}{8.3 \angle -20.5^\circ}$$

$$= 0.36 \angle 290.5^\circ$$

$$\dot{V} = (10 \angle 0^\circ)(0.36 \angle 290.5^\circ) = 3.6 \angle 290.5^\circ = \boxed{3.6 \angle -69.5^\circ \text{ V}}$$

EE 202
QUIZ #1

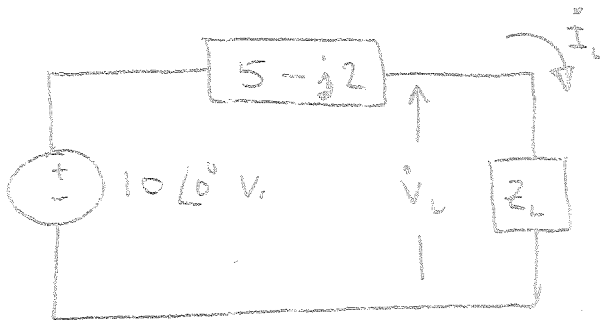Find the power in the load when \vec{Z}_L is adjusted so that there is maximum power in \vec{Z}_L .



(a) $P_L = \underline{\hspace{2cm}}$

(b) $\vec{V}_L = \underline{\hspace{2cm}}$

(c) $\vec{I}_L = \underline{\hspace{2cm}}$

(d) Find the ~~max~~ reactive power in vars that the load bears.

Solution


(a) $P_{max} = \frac{|V_g|^2}{4R_g} = \frac{100}{20} = \boxed{5 \text{ watts}}$

(c) $\vec{I}_L = \frac{\vec{V}_g}{2R_g} = \frac{10}{10} = \boxed{1 \angle 0^\circ \text{ A}}$

(b) $V_L = Z_L I_L = (5 + j2)(1 \angle 0^\circ) = \boxed{5 + j2 \text{ V}}$

(d) $Q_L = |I_L|^2 X_L = 1 \times 2 = \boxed{2 \text{ Vars}}$

X-17

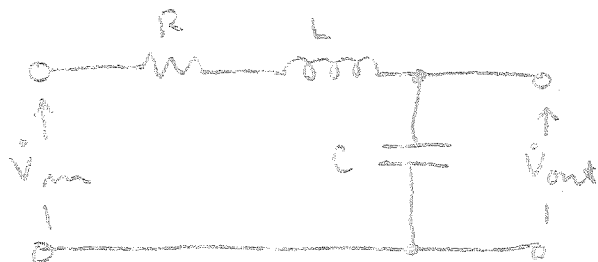

Find $H(\omega) = \frac{V_{out}}{V_{in}}$

$R = 1 \ \Omega$

$L = 1 \ \text{H}$

$C = \frac{1}{2} \ \text{F}$

Find the frequency where ~~the~~ $|H(\omega)|$ is maximum.

Find the frequencies where $|H(\omega)| = 0.707 |H_{max}|$.

Find $|H(\omega)|_{max}$.

X-18


PROBLEM ~~5-12~~ 547.16.12 in SCOTT.

Pp. 510-12

4-7-70


12) a) $10 \angle 0^\circ \Rightarrow 10$

b) $5 \angle 45^\circ$

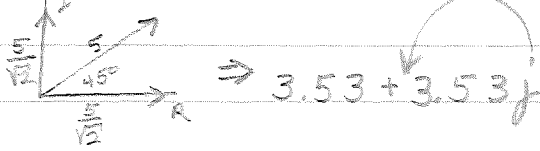

put j operator in from always

e) $10 \angle 135^\circ$

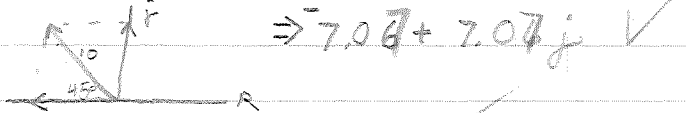

c) $10 \angle -90^\circ \Rightarrow -10j$ ✓

d) $5 \angle 135^\circ \Rightarrow -3.53 + 3.53j$ ✓

use lower case of the final junction

13) a) $P = 10 \cos t$ ✓

b) $Y = 10 \cos(377t + \pi/4)$

c) $Y = 5 \cos(10^3t - 60^\circ)$ ✓

d) $Y = 5 \cos(t + 53^\circ)$


e) $Y = 2.82 \cos(\frac{\pi}{10} + 135^\circ)$ ✓

14) a) $1 + j \Rightarrow \sqrt{2} \cos(\omega t + 45^\circ) = 1.41 \cos(\omega t + 45^\circ)$ ✓

b) $3 - j4$



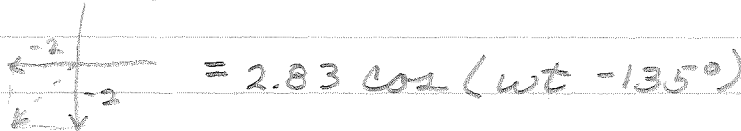
c) $-2 - 2j \Rightarrow 2\sqrt{2} \cos(\omega t - 135^\circ)$ ✓



d) $-3 + j4$



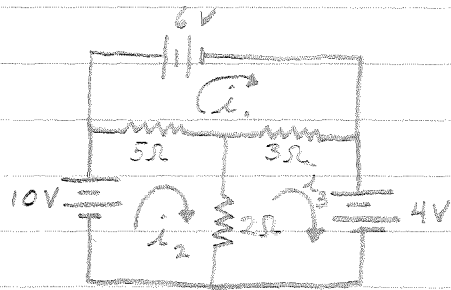e) $j \Rightarrow \cos(\omega t + 90^\circ)$ ✓



$$6 + 8i_1 - 5i_2 - 3i_3 = 0 \Rightarrow i_1 = \frac{-6}{8} + \frac{5}{8}i_2 + \frac{3}{8}i_3$$

$$-10 - 5i_1 + 7i_2 - 2i_3 = 0 \Rightarrow i_1 = \frac{-10}{5} + \frac{7}{5}i_2 - \frac{2}{5}i_3$$

$$4 - 3i_1 - 2i_2 + 5i_3 = 0 \Rightarrow i_1 = \frac{4}{3} - \frac{2}{3}i_2 + \frac{5}{3}i_3$$

$$\frac{-6}{8} + \frac{5}{8}i_2 + \frac{3}{8}i_3 = -2 + \frac{7}{5}i_2 - \frac{2}{5}i_3 = \frac{4}{3} - \frac{2}{3}i_2 + \frac{5}{3}i_3$$


$$\frac{5}{4} + i_2 \left(\frac{5}{8} - \frac{7}{5} \right) + i_3 \left(\frac{3}{8} + \frac{2}{5} \right) = 0 = \frac{10}{3} - i_2 \left(\frac{2}{3} + \frac{7}{5} \right) + i_3 \left(\frac{5}{3} + \frac{2}{5} \right)$$

$$\frac{5}{4} - \frac{31}{40}i_2 + \frac{31}{40}i_3 = 0 = \frac{10}{3} - \frac{31}{15}i_2 + \frac{31}{15}i_3$$

$$50 - 31i_2 + 31i_3 = 0 = 50 - 31i_2 + 31i_3$$

MESH CURRENTS i_1 , i_2 , AND i_3 MAY BE ANY VALUE

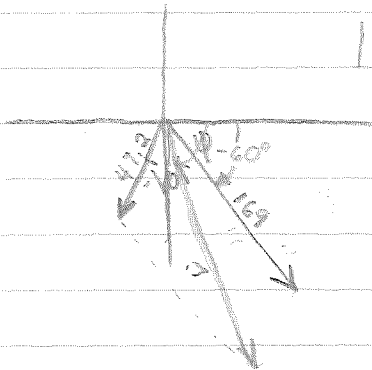2) $V_1(t) = 169 \sin(377t + 30^\circ)$; $V_2(t) = 47.2 \sin(377t - 41^\circ)$
 $V_1(t) = 169 \cos(377t - 60^\circ) \text{ V}$; $V_2(t) = 47.2 \cos(377t - 101^\circ)$
 $\dot{V}_1 = 169 \angle -60^\circ$; $\dot{V}_2 = 47.2 \angle -101^\circ$



$$V = V_1 + V_2$$

$$|\dot{V}| = 169j \sin^{-60^\circ} + 47.2j \sin^{-101^\circ} \text{ v}$$

$$+ 169 \cos^{-60^\circ} + 47.2 \cos^{-101^\circ} \text{ v}$$

$$= j169 \frac{-\sqrt{3}}{2} - 47.2j \sin 79^\circ \text{ v}$$

$$+ 169 \left(\frac{1}{2} \right) - 47.2 \cos 79^\circ \text{ v}$$

$$= -147j - 46.3j + 84.5 - 9.0 \text{ v}$$

$$= -193j + 84.5 \text{ v}$$

$$\psi = \tan^{-1} \frac{193}{84.5} = 2.28$$


$$\cot \psi = .439 \Rightarrow \psi = 64^\circ$$

$$\therefore \dot{V} = \sqrt{3.72 + .714} \times 10^2 \angle -64^\circ = 210 \angle -64^\circ \text{ v}$$

$$v(t) = 210 \cos(377t - 64^\circ) \text{ V}$$

$$\begin{aligned}
 \text{x-27) } Z(s) &= \frac{s+1}{(s+1+j)(s+1-j)} \\
 &= \frac{s+1}{s^2+s-j^2+s+1-j+j^2+j+1} \\
 &= \frac{s+1}{s^2+2s+2}
 \end{aligned}$$

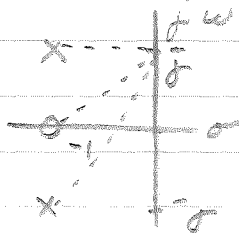
$$\text{b) } Z(s) = \frac{s+1}{(s+1+j)(s+1-j)}$$



$$|Z(s)| = \frac{\sqrt{2}}{1 \cdot \sqrt{5}} = 0.283$$

$$\phi = 0^\circ - 45^\circ - 71.6^\circ = -116.6^\circ$$

X-10)

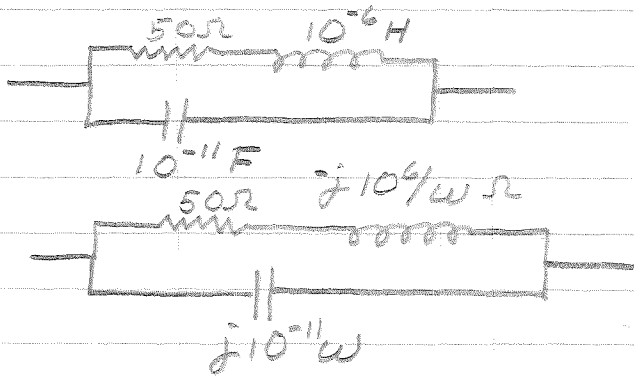

$$Z_{eq} = \frac{j10^{-11}\omega \left(50 - \frac{j10^6}{\omega}\right)}{50 + j \left(10^{-11}\omega - \frac{10^6}{\omega}\right)}$$

$$= \frac{10^{-5} + j50 \times 10^{-11}\omega}{50 + j \left(10^{-11}\omega - \frac{10^6}{\omega}\right)}$$

FOR REAL Z_{eq} :

$$\frac{50 \times 10^{-11}\omega}{10^{-5}} = \frac{10^{-11}\omega - \frac{10^6}{\omega}}{50}$$

$$2.50 \times 10^{-9} = 10^{-16}\omega - \frac{10^6}{\omega}$$

$$2.50 \times 10^{-9}\omega - 10^{-16}\omega^2 + 10 = 0$$


$$10^{-16}\omega^2 - 2.50 \times 10^{-9}\omega - 10 = 0$$

$$\omega = \frac{2.50 \times 10^{-9} \pm \sqrt{6.25 \times 10^{-18} + 4 \times 10^{-15}}}{10^{-32}}$$

$$\sqrt{6.25 \times 10^{-18} + 4000 \times 10^{-18}} \approx 63.2 \times 10^{-9}$$

$$\omega = \frac{65.7 \times 10^{-9}}{10^{-32}} = 65.7 \times 10^{23}$$

X-12)

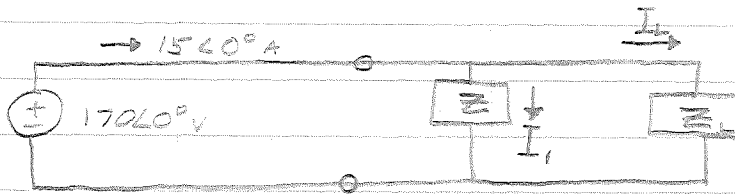

$$P = (15)(85) = 1275$$

$$I_1 = \frac{Z_L}{Z + Z_L} (15)$$

$$P_1 = \left(\frac{Z_L}{Z + Z_L} \right) (15)(85) \cdot 0.8 = 575$$

$$\frac{Z_L}{Z + Z_L} 908 = 575$$

$$I_2 = \frac{Z}{Z_L + Z} 15$$

$$P_2 = \left(\frac{Z}{Z_L + Z} \right) (15)(85)(0.8) = 700$$

$$\frac{Z}{Z_L + Z} 908 = 700$$

$$\frac{Z_L}{Z + Z_L} = .633; \quad \frac{Z}{Z_L + Z} = .771$$

$$Z_L = .663Z + .633Z_L; \quad Z = Z_L \cdot .771 + Z \cdot .771$$

$$.367 Z_L = .663Z$$

$$Z_L = 1.8Z$$

$$Z_L = \frac{.329Z}{.771}$$

$$Z_L = .296Z$$

X 1

E SCI. II
 HOMEWORK

you need to put
 some correct
 answers in
 in a while

X-4



$$L = 1.0 \text{ H}$$


$$R = 5.0 \Omega$$

$$f = 3.0 \text{ Hz}$$

$$\dot{Z} = (5 - j0.6530) \Omega_{\text{net}}$$

$$= \underline{5 \angle -6.1^\circ \Omega} \text{ polar}$$

X-5

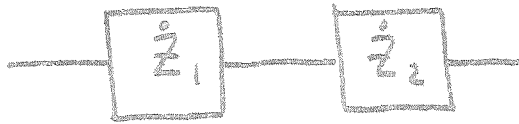

$$Z_1 = 5 - j4 \Omega$$

$$Z_2 = 8 \angle 30^\circ \Omega$$




$$\dot{Z}_{eq} = \underline{11.92 \Omega}$$

X-6

Draw phasors for

$$v(t) = 130 \sin(\omega t + 10^\circ) \text{ V}$$

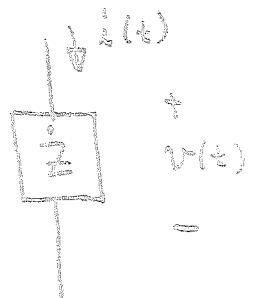
$$i(t) = 65 \cos(\omega t - 50^\circ) \text{ A}$$




$$\dot{Z} = \underline{8430 \angle -130^\circ}$$

EE 202
HOMEWORK

X-7

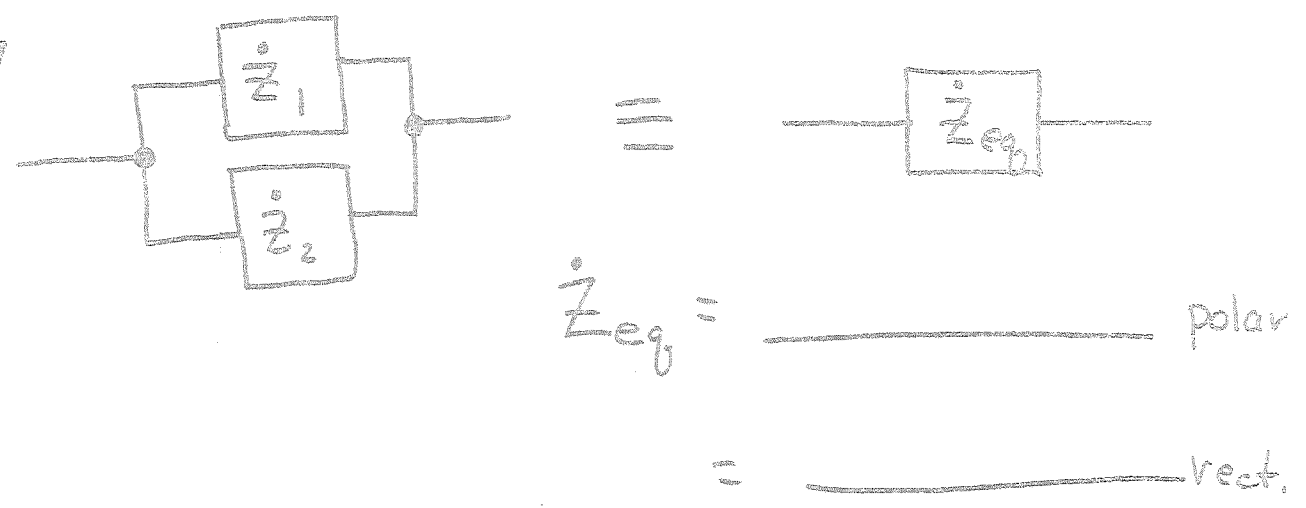


X-8

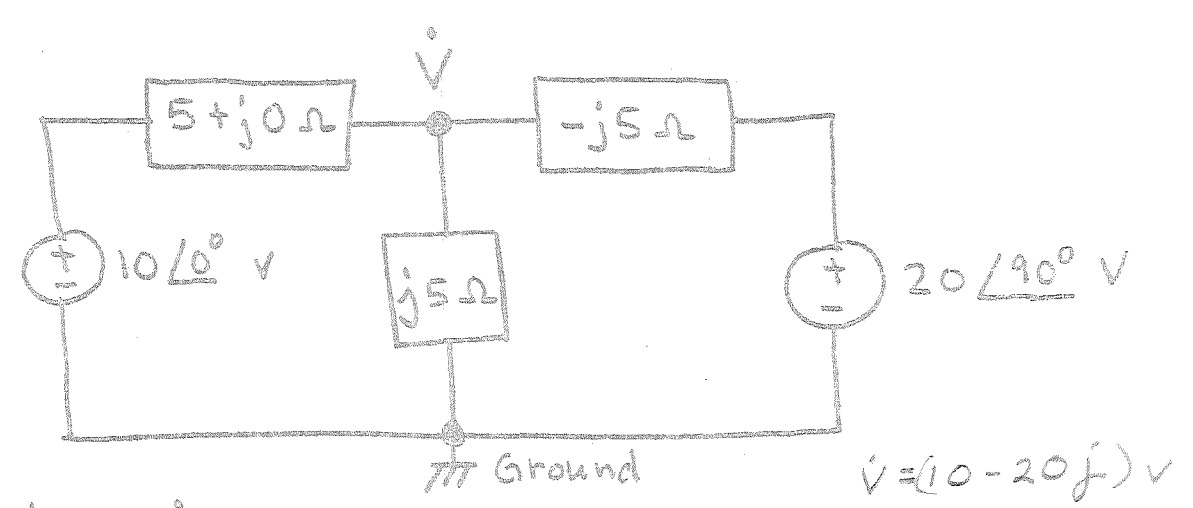

Find \dot{V} , measured against ground.

X-9

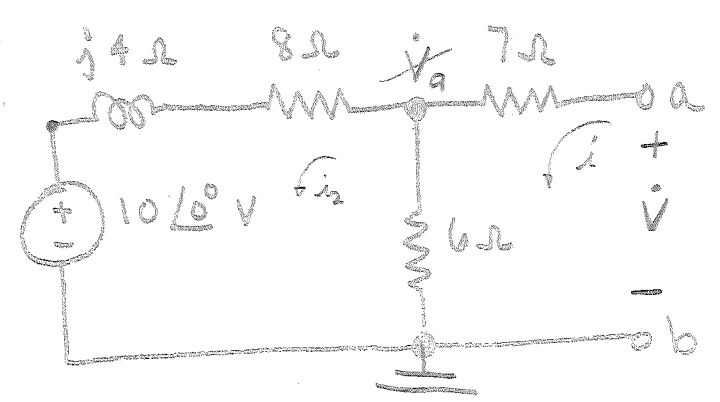

Find Thevenin's equivalent cct. for terminals a, b

x-4) $\omega = 2\pi f = 6\pi$

$$\dot{Z}_L = \frac{1}{j\omega L} = \frac{-j}{(6\pi)(0.1)}$$

$$= -j0.530$$


$$\dot{Z}_{eq} = (5 - j0.530)\Omega$$

$$= 5 \angle -6.1^\circ$$

x-5) $\dot{Z}_2 = 8 \angle 30^\circ = 6.92 + 4j$

$$\dot{Z}_{eq} = 11.92\Omega$$

x-6)

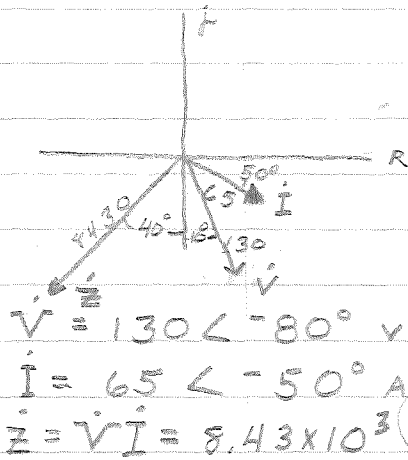

$$\dot{V} = 130 \angle -80^\circ \text{ V}$$

$$\dot{I} = 65 \angle -50^\circ \text{ A}$$

$$\dot{Z} = \dot{V} \dot{I} = 8.43 \times 10^3 \angle -130^\circ \Omega$$

x-7)

$$\frac{1}{\dot{Z}_{eq}} = \frac{1}{\dot{Z}_1} + \frac{1}{\dot{Z}_2} = \frac{\dot{Z}_2 + \dot{Z}_1}{\dot{Z}_1 \dot{Z}_2}$$

$$\dot{Z}_{eq} = \frac{\dot{Z}_1 \dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2}$$

$$\dot{Z}_1 = A_1 \angle \psi_1 = A_1 \cos \psi_1 + j A_1 \sin \psi_1$$

$$\dot{Z}_2 = A_2 \angle \psi_2 = A_2 \cos \psi_2 + j A_2 \sin \psi_2$$

$$\dot{Z}_1 + \dot{Z}_2 = (A_1 \cos \psi_1 + A_2 \cos \psi_2) + j (A_1 \sin \psi_1 + A_2 \sin \psi_2)$$

$$= (A_1 \sin \psi_1 + A_2 \sin \psi_2) / \sin \tan^{-1} \frac{A_1 \sin \psi_1 + A_2 \sin \psi_2}{A_1 \cos \psi_1 + A_2 \cos \psi_2}$$

$$\dot{Z}_1 \dot{Z}_2 = A_1 A_2 \angle \psi_1 + \psi_2$$

$$= A_1 A_2 \cos(\psi_1 + \psi_2) + j A_1 A_2 \sin(\psi_1 + \psi_2)$$

$$\dot{Z}_{eq} = \frac{A_1 A_2 \sin \tan^{-1} \frac{A_1 \sin \psi_1 + A_2 \sin \psi_2}{A_1 \cos \psi_1 + A_2 \cos \psi_2}}{A_1 \sin \psi_1 + A_2 \sin \psi_2} \angle \psi_1 + \psi_2 - \tan^{-1} \frac{A_1 \sin \psi_1 + A_2 \sin \psi_2}{A_1 \cos \psi_1 + A_2 \cos \psi_2}$$

$$\equiv A_3 \angle \psi_3$$

$$= (A_3 \cos \psi_3 + j A_3 \sin \psi_3) \Omega$$

TAIRY ← NO!

x-4) $\omega = 2\pi f = 6\pi$

$$\dot{Z}_L = j\omega L = \frac{-j}{(6\pi)(0.1)}$$

$$= -j0.530$$


$$\dot{Z}_{eq} = (5 - j0.530) \Omega$$

$$= 5 \angle -6.1^\circ$$

x-5) $\dot{Z}_2 = 8 \angle 30^\circ = 6.92 + 4j$

$$\dot{Z}_{eq} = 11.92 \Omega$$

x-6)

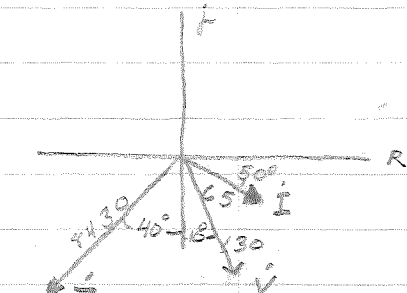

$$\dot{V} = 130 \angle -80^\circ \text{ V}$$

$$\dot{I} = 65 \angle -50^\circ \text{ A}$$

$$\dot{Z} = \dot{V} / \dot{I} = 8.43 \times 10^3 \angle -130^\circ \Omega$$

x-7) $\frac{1}{\dot{Z}_{eq}} = \frac{1}{\dot{Z}_1} + \frac{1}{\dot{Z}_2} = \frac{\dot{Z}_2 + \dot{Z}_1}{\dot{Z}_1 \dot{Z}_2}$

$$\dot{Z}_{eq} = \frac{\dot{Z}_1 \dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2}$$

$$\dot{Z}_1 = A_1 \angle \psi_1 = A_1 \cos \psi_1 + j A_1 \sin \psi_1$$

$$\dot{Z}_2 = A_2 \angle \psi_2 = A_2 \cos \psi_2 + j A_2 \sin \psi_2$$

$$\dot{Z}_1 + \dot{Z}_2 = (A_1 \cos \psi_1 + A_2 \cos \psi_2) + j (A_1 \sin \psi_1 + A_2 \sin \psi_2)$$

$$= (A_1 \sin \psi_1 + A_2 \sin \psi_2) / \sin \tan^{-1} \frac{A_1 \sin \psi_1 + A_2 \sin \psi_2}{A_1 \cos \psi_1 + A_2 \cos \psi_2}$$

$$\dot{Z}_1, \dot{Z}_2 = A_1, A_2 \angle \psi_1 + \psi_2$$

$$= A_1 A_2 \cos(\psi_1 + \psi_2) + j A_1 A_2 \sin(\psi_1 + \psi_2)$$

$$\dot{Z}_{eq} = \frac{A_1 A_2 \sin \tan^{-1} \frac{A_1 \sin \psi_1 + A_2 \sin \psi_2}{A_1 \cos \psi_1 + A_2 \cos \psi_2}}{A_1 \sin \psi_1 + A_2 \sin \psi_2} \angle \psi_1 + \psi_2 = \tan^{-1} \frac{A_1 \sin \psi_1 + A_2 \sin \psi_2}{A_1 \cos \psi_1 + A_2 \cos \psi_2}$$

$$\equiv A_3 \angle \psi_3$$

$$= (A_3 \cos \psi_3 + j A_3 \sin \psi_3) \Omega$$

↑ AIRY ← NO!

EE 202
Answers to homework

X-4

$$\dot{z} = 5 + j 2\pi \cdot 3 \cdot 1 = 5 + j 18.85 \Omega$$

$$= 19.5 \angle 75.15^\circ \Omega$$

X-5

$$z_2 = 8 \cos 30^\circ + j 8 \sin 30^\circ$$

$$= 6.92 + j 4$$

$$\dot{z}_{eq} = 5 - j 4 + 6.92 + j 4 = 11.92 \angle 0^\circ \Omega$$


X-6

$$v(t) = 130 \sin(\omega t + 10^\circ) \text{ V}$$

$$= 130 \cos(\omega t - 80^\circ) \text{ V}$$

$$i(t) = 65 \cos(\omega t - 50^\circ) \text{ V}$$

$$\bar{z} = \frac{130 \angle -80^\circ}{65 \angle -50^\circ} = 2.0 \angle -30^\circ \Omega$$

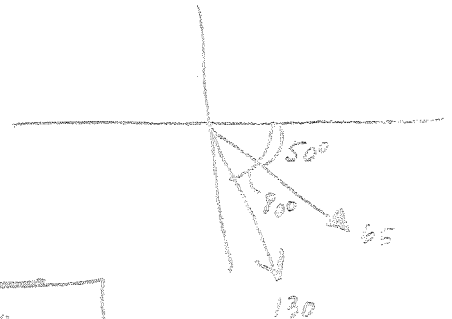

EE 202
Answers

X-7

Using \dot{Z}_1 and \dot{Z}_2 from X-5

$$\dot{Z}_1 = 5 - j4 \Omega$$


$$\dot{Z}_2 = 8 \angle 30^\circ \Omega$$

$$= \frac{5.32}{6.4} \angle -38.7^\circ$$

$$= 6.92 + j4$$

$$\dot{Z}_{eq} = \frac{(5.32 \angle -38.7^\circ)(8 \angle 30^\circ)}{11.92} = \boxed{4.57 \angle -8.7^\circ \Omega}$$

X-8

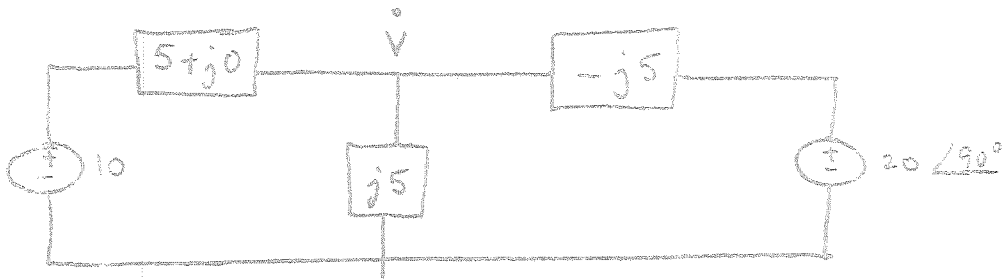

$$\frac{10 - \dot{V}}{5} + \frac{j20 - \dot{V}}{-j5} + \frac{-\dot{V}}{j5} = 0$$

$$2 - 0.2 \dot{V} - 4 - \cancel{j0.2 \dot{V}} + \cancel{j0.2 \dot{V}} = 0$$

$$-0.2 \dot{V} = 2 \Rightarrow \dot{V} = \frac{-2}{.2} = \boxed{-10 \angle 0^\circ \text{ V}}$$

EE 202

Answers

X-9

$$\ddot{V}_T = \frac{6}{14 + j4} 10 \angle 0^\circ$$

$$= \frac{60 \angle 0^\circ}{14.55 \angle 15.95^\circ} = \boxed{4.13 \angle -15.95^\circ \text{ V}}$$


$$\dot{z}_T = 7 + \frac{6(8 + j4)}{14 + j4} = 7 + \frac{48 + j24}{14.55 \angle 15.95^\circ}$$

$$= 7 + \frac{53.6 \angle 26.6^\circ}{14.55 \angle 15.95^\circ} = 7 + 3.68 \angle 10.65^\circ$$

$$= 7 + 3.62 + j0.68 = \boxed{10.62 + j0.68}$$

E.E. 202
ANSWERS TO HOMEWORK

K-10

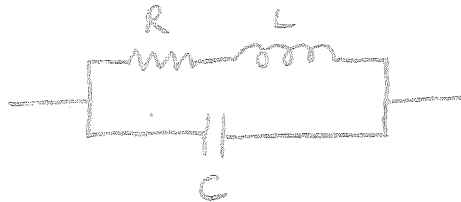

$$R = 50 \Omega$$

$$L = 1 \mu\text{H}$$

$$C = 10 \text{ pF}$$

$$\bar{Z} = \frac{\left(\frac{1}{j\omega C}\right)(R + j\omega L)}{\frac{1}{j\omega C} + R + j\omega L} = \frac{R + j\omega L}{1 - \omega^2 LC + j\omega RC}$$

Impedance is real when angle of numerator = angle of denominator

$$\frac{\omega L}{R} = \frac{\omega RC}{1 - \omega^2 LC}$$

$$R^2 C = L - \omega^2 L^2 C$$

$$\omega^2 L^2 C = -R^2 C + L$$


$$\omega^2 = \frac{-R^2 C + L}{L^2 C} = \frac{-2500 \times 10^{-11} + 10^{-6}}{10^{-12} \cdot 10^{-11}}$$

$$= 10^{-6} \cdot 10^{23} = 10^{17}$$

$$\omega = 10^8 \sqrt{10} = \boxed{3.16 \times 10^8 \frac{\text{rad}}{\text{sec}}}$$

EE 202
ANSWERS

X-11

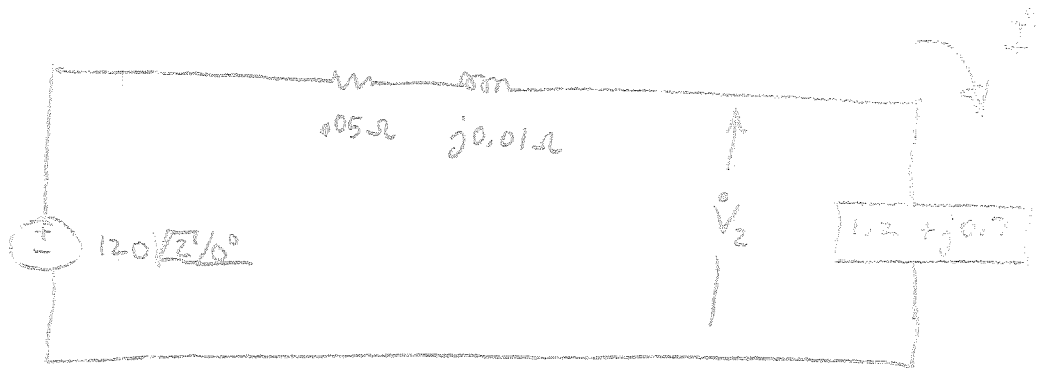

$$\dot{I} = \frac{120\sqrt{2} \angle 0^\circ}{1.25 + j0.71} = \frac{120\sqrt{2} \angle 0^\circ}{1.435 \angle 29.6^\circ}$$

$$= 118.5 \angle -29.6^\circ \text{ A.}$$

$$P_L = \frac{|\dot{I}|^2 R_L}{2} = \frac{118.5^2 \times 1.2}{2} = \boxed{8400 \text{ W}}$$

$$\dot{V}_2 = \dot{I} \dot{Z}_L = \cancel{0.293} (118.5 \angle -29.6^\circ) (1.2 + j0.7)$$


||

$$1.385 \angle 30.3^\circ$$

$$= \boxed{164 \angle 0.7^\circ \text{ V.}}$$

ANSWERS TO HOMEWORK

X-12

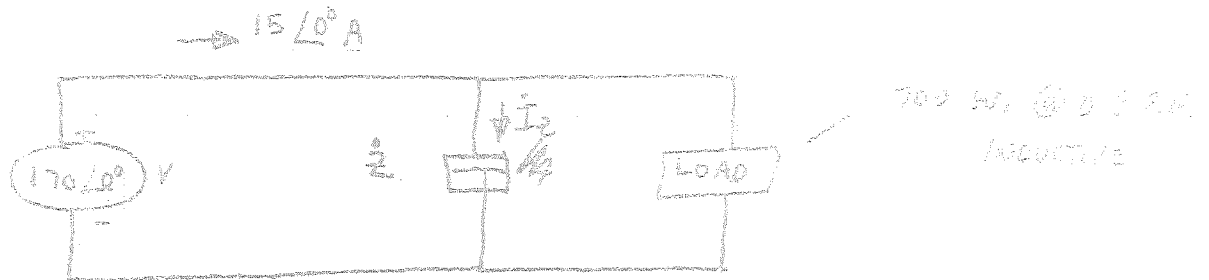

Power transfer for source

$$P_s = 170 \times 15 = 2550 \text{ W}$$

$$Q_s = 0 \text{ VARs}$$

LOAD

$$P_L = 700 \text{ W}, \quad \theta_L = \cos^{-1} 0.8 = 36.9^\circ$$

$$Q_L = 875 \sin 36.9^\circ \quad \overline{VA}_L = 875 \text{ V-A}$$

$$= 525 \text{ VARs}$$


Power Δ for Z

$$P_Z = 2550 - \frac{700}{0.8} = 2550 - 875 = 1675 \text{ watts}$$

$$Q_Z = -525 \text{ VARs}$$

$$\theta_Z = \tan^{-1} \frac{-525}{1675} = -15.85^\circ$$

$$\overline{VA} = 1920 \text{ VA}$$

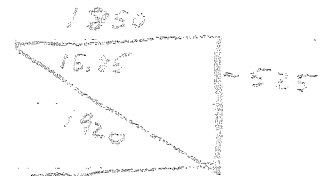

$$|I_Z| = \frac{1920}{170} = 11.3 \text{ A}, \quad |Z| = \frac{170}{11.3} = 15.05 \Omega$$

$$Z = 15.05 \angle -15.85^\circ \Omega$$


-1%
-2%

Department of Electrical Engrg.
Rose Polytechnic Institute
Terre Haute, Indiana
April 28, 1970

GA

EE 202
TEST 1
CLOSED BOOKS - 50 Minutes

1. Find the time equation for $v(t)$.

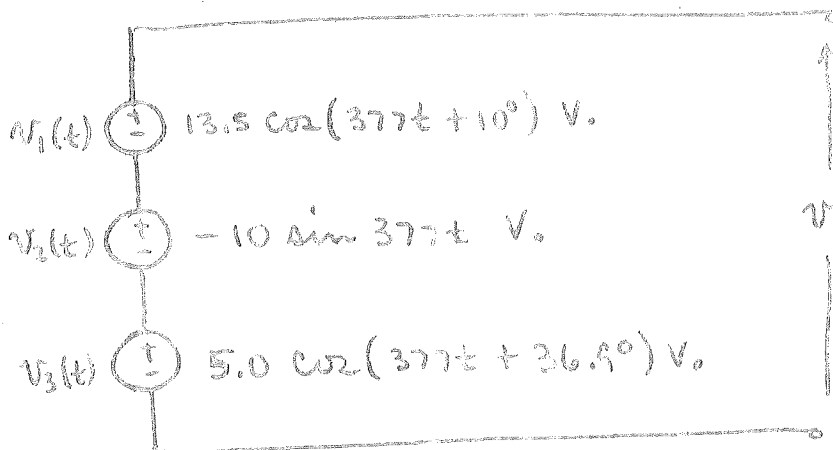

$v_4(t) = 23.1 \cos(377t + 41.6^\circ)$

UNITS



$\omega = 377$

$V_1 = 13.5 \angle 10^\circ = 13.3 + j2.34$
 $V_2 = -10 \angle -90^\circ = j10$
 $V_3 = 5 \angle 36.9^\circ = 4.0 + j3$
 $17.3 + j15.34$

$V_4 = 23.1 \angle 41.6^\circ \text{ V}$

$v_4(t) = 23.1 \cos(377t + 41.6^\circ) \text{ Volts}$

2. Find \dot{I} in the circuit shown.

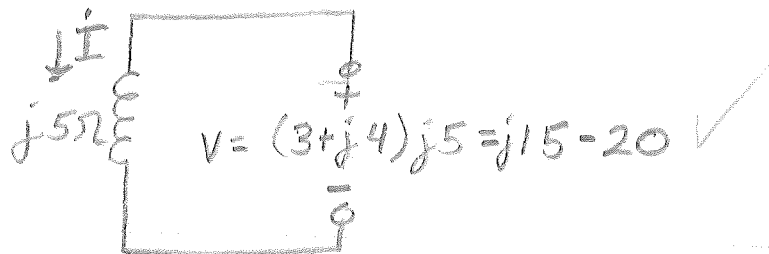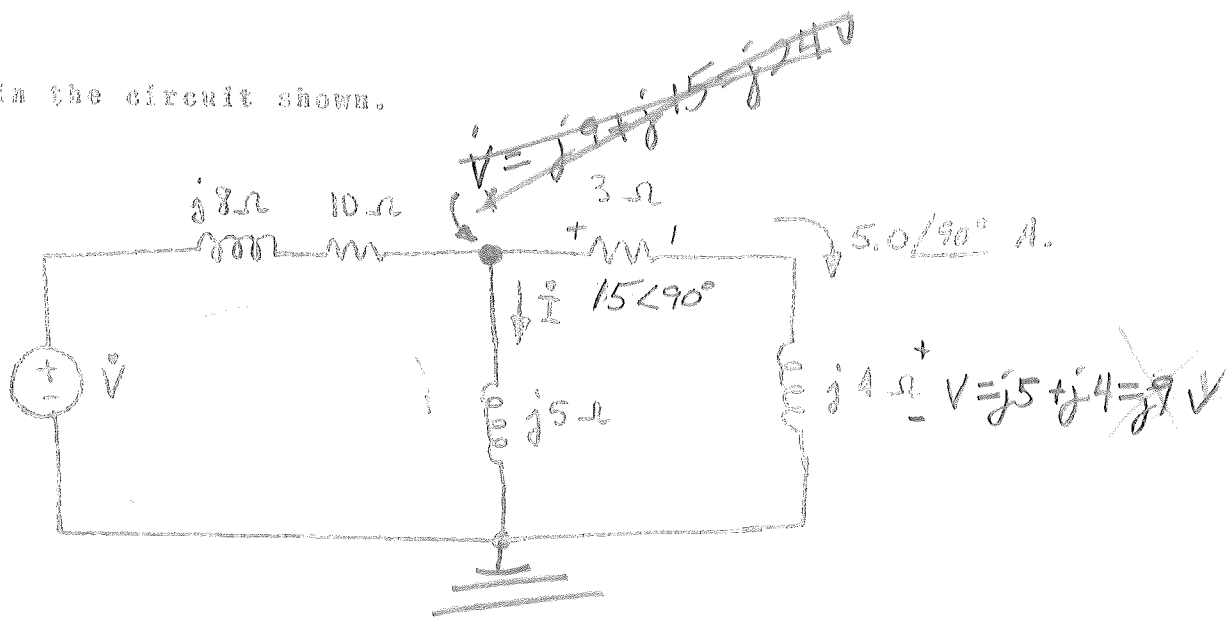

$$\dot{I} = \frac{\dot{V}}{\dot{Z}} = \frac{-20 + j15}{j5}$$

$$= \frac{25 \angle (180^\circ + 36.9^\circ)}{5 \angle 90^\circ}$$


$$= \frac{25 \angle 216.9^\circ}{5 \angle 90.0^\circ}$$

$$\dot{I} = 5 \angle 126.9^\circ \text{ AMPS}$$


quadrant

9

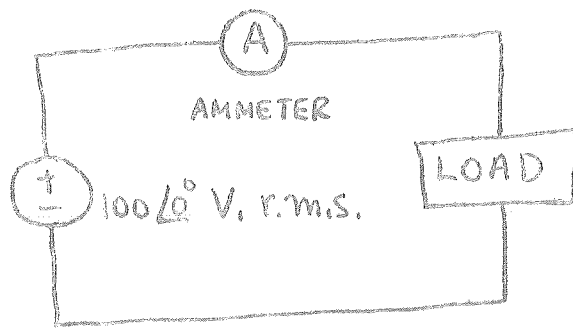3. The power that the load dissipates is 500 watts. Its power factor is 0.707 and known to be inductive. Find the reading of the a-c ammeter and the complex load impedance. The ammeter has zero impedance.



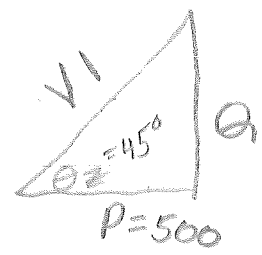500 WATTS
 $\cos\theta_z = 0.707$ INDUCTIVE
 $\theta_z = 45^\circ$



$$P = 500 = VI \cos\theta_z = I(0.707)(100)$$

$$I = \frac{500}{70.7} = 7.07 \angle -\theta_z \checkmark$$


$$\frac{7.07}{\sqrt{2}} = 5$$



→ AMMETER READS ~~5~~ AMPS


$$\dot{Z}_L = \frac{\dot{V}}{I} = \frac{100 \angle 0^\circ}{7.07 \angle -45^\circ} = 14.15 \angle 45^\circ$$

→ $\dot{Z}_L = (10 + j10) \Omega$

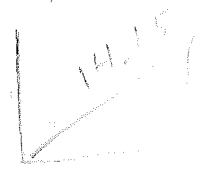

8

4. For the circuit shown find

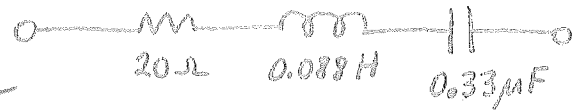

- minimum value of $|z| = 20 \Omega$
- frequency in Hz where minimum value of $|z|$ occurs.
- frequency or frequencies where $|z|$ equals $\sqrt{2}$ (minimum value of $|z|$).
- Q_0 of this resonant circuit
- bandwidth in Hz of this resonant circuit.

a) $|Z|_{\min} = R = 20 \Omega$

~~b) $Z_{eq} = 20 + j8.8 \times 10^{-2} \omega + \frac{1}{j\omega(33 \times 10^{-6})}$~~

~~b) $Z = \sqrt{20^2 + (8.8 \times 10^{-2} \omega - \frac{1}{33 \times 10^{-6} \omega})^2}$~~

~~$= 20 + j(8.8 \times 10^{-2} \omega - 3 \times 10^6 / \omega)$~~

b) $\omega_r = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{8.8 \times 10^{-2} \times 33 \times 10^{-6}}} = \sqrt{\frac{3 \cdot 10^8}{8.8}} = \sqrt{341} \times 10^4$
 $\omega = \sqrt{\frac{3 \times 10^6}{8.8 \times 10^{-2}}} = \sqrt{341} \times 10^2 = 584 \frac{\text{RAD}}{\text{SEC}} = 930 \text{ Hz}$

c) $BW = \frac{R}{L} = \frac{20}{8.8 \times 10^{-2}} = 2.27 \times 10^2 = 227 \text{ MHz}$

$\omega_U = 934 + 113.5 = 1047.5 \frac{\text{RAD}}{\text{SEC}}$

$\omega_L = 934 - 113.5 = 820.5 \frac{\text{RAD}}{\text{SEC}}$


d) $BW = \frac{\omega_r}{Q_0} \Rightarrow Q_0 = \frac{\omega_r}{BW} = \frac{5.87 \times 10^3}{227 \times 10^2} = 25.9 \text{ REL}$

e) $BW = 227 \frac{\text{RAD}}{\text{SEC}} \frac{\text{CYCLE}}{2\pi \text{ RAD}} = 36.1 \text{ Hz}$

10

EE 202
TEST 1
CLOSED BOOKS - 50 Minutes

1. Find the time equation for $v(t)$.

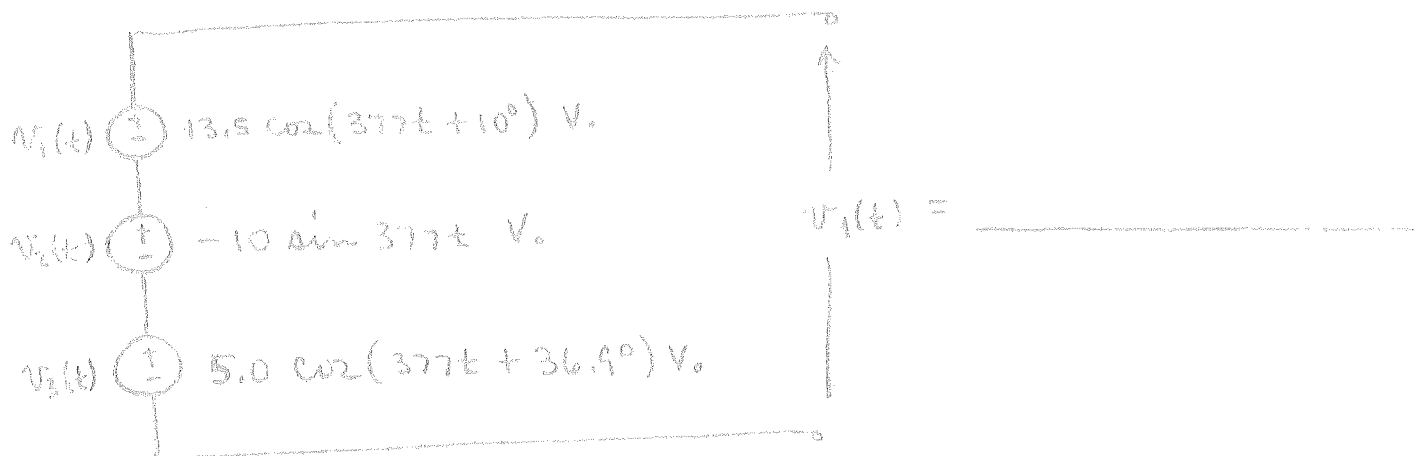

Solution:

$$\dot{V}_1 = 13.5 \angle 10^\circ = 13.3 + j2.26$$


$$\dot{V}_2 = 10 \angle 90^\circ = 0 + j10$$

$$\dot{V}_3 = 5 \angle 36.9^\circ = 4 + j3$$

$$\dot{V}_4 = \dot{V}_1 + \dot{V}_2 + \dot{V}_3 = 17.3 + j15.26 = 23.1 \angle 41.4^\circ \text{ V}$$

$$v_4(t) = \boxed{23.1 \cos(377t + 41.4^\circ) \text{ V}}$$


2. Find \dot{I} in the circuit shown.

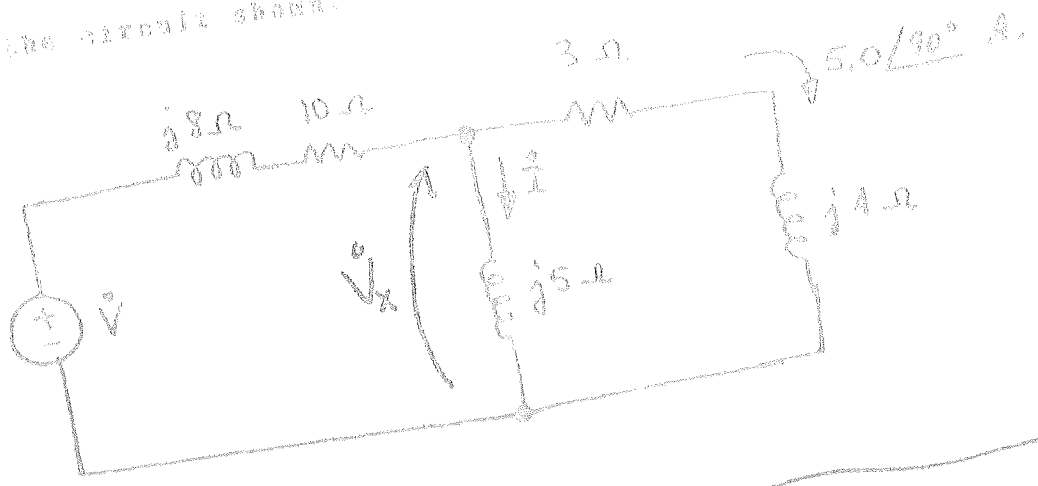

$$\dot{V}_x = (5 \angle 90^\circ)(3 + j4)$$

$$\dot{I} = \frac{\dot{V}_x}{j5} = \frac{(5 \angle 90^\circ)(3 + j4)}{5 \angle 90^\circ} = \boxed{3 + j4 \text{ A}}$$

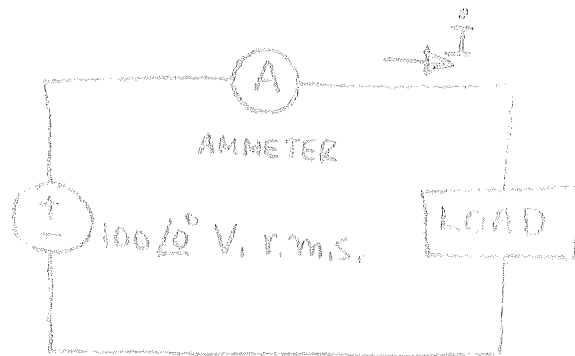The load Z in a 500-watt impedance of $50 \angle 45^\circ \Omega$ and the power factor is 0.707 and known to be inductive. Find the reading of the AC ammeter and the complex load impedance. The ammeter has zero impedance.



$$P = |\dot{V}| |\dot{I}| \cos \theta = 100 \cdot |\dot{I}| \cdot 0.707 = 500$$

$$|\dot{I}| = \frac{500}{100 \cdot 0.707} = \frac{5}{0.707} = \boxed{7.07 \text{ A}}$$

$$|\dot{Z}| = \frac{|\dot{V}|}{|\dot{I}|} = \frac{100}{7.07} = 14.14 \Omega$$

$$\dot{Z} = \boxed{14.14 \angle 45^\circ} = \boxed{10 + j10 \Omega}$$

a) minimum value of $|\dot{z}|$

$$R = 20 \Omega$$

$$L = 0.088 \text{ mH}$$

$$C = 3.3 \mu\text{F}$$

b) frequency in Hz where minimum value of $|\dot{z}|$ occurs,

c) frequency or frequencies where $|\dot{z}|$ equals $\sqrt{2}$ (minimum value of $|\dot{z}|$).

d) Q_0 of this resonant circuit

e) bandwidth in Hz of this resonant circuit.

$$(a) |\dot{z}|_{\min} = R = \boxed{20 \Omega}$$

$$(b) |\dot{z}| = |\dot{z}|_{\min} \text{ when } X_L = -X_C$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{8.8 \times 10^{-2} \cdot 3.3 \times 10^{-7}}}$$

$$= \sqrt{3.44 \times 10^6} = \sqrt{34.4 \times 10^6}$$

$$= 5.87 \times 10^3 = 5870 \frac{\text{rad}}{\text{sec}}$$

$$f_r = \frac{5870}{2\pi} = \boxed{934 \text{ Hz}}$$

$$(c) \pm 20 = 0.088\omega - \frac{1}{3.3 \times 10^{-7} \omega}$$

$$\text{we get } 20 \times 3.3 \times 10^{-7} \omega = 0.088 \times 3.3 \times 10^{-7} \omega^2 - 1$$

$$6.6 \omega = 0.29 \omega^2 - 10^7 \Rightarrow \omega^2 - 228 \omega - 3.45 \times 10^7 = 0$$

$$\omega = \frac{228 \pm \sqrt{228^2 + 4 \times 3.45 \times 10^7}}{2} = 114 \pm \sqrt{114^2 + 3.45 \times 10^7}$$

4 cont

$$\omega = 114 \pm \sqrt{13000 + 3.145 \times 10^7} = 114 \pm \sqrt{34.5 \times 10^6}$$

$$= 114 \pm 5870 = 5984 \frac{\text{rad}}{\text{sec}} = \boxed{953 \text{ Hz}}$$

upper
 $\frac{1}{2}$ power
freq.

Quadratic Sign.

$$\omega^2 + 228\omega - 3.145 \times 10^7 = 0$$

$$\omega = \frac{-228 \pm \sqrt{(\quad)}}{2} = -228 + 5870$$

$$= 5642 \text{ rad/sec} = \boxed{899 \text{ Hz}}$$

lower
 $\frac{1}{2}$ power freq.

$$(d) Q_0 = \frac{\omega_p L}{R} = \frac{5870 \times 0.088}{20} = \boxed{25.8}$$

$$(e) BW = \frac{\omega_p}{Q_0} = \frac{5870}{25.8} = 227 \text{ rad/sec}$$

$$\text{or } \frac{934}{25.8} = \boxed{34.8 \text{ Hz}}$$

EE DEPT RPI
 TERRE HAUTE, IND
 MAY 4, 1970

EE 202
 HOMEWORK

X-20

Draw the Bode diagram for the magnitude of the $H(\omega)$ shown.

$$H(\omega) = \frac{1}{1 + j\omega/5}$$

X-21

Same as above

$$H(\omega) = \frac{(1 + j\omega/10)}{(1 + j\omega/100)}$$


X-22

X-22

Same as above

$$H(s) \Big|_{s=j\omega} = \frac{s+5}{s^2+12s+20}$$

X-23

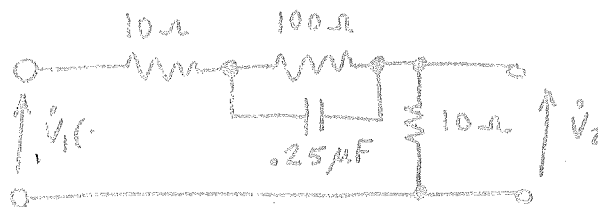

Draw the Bode diagram of $|H(\omega)|$ vs ω on log-log axes for $H(\omega) = v_2/v_1$

EE 202 HOMEWORK
CONTINUED

(X-24)

$$H(s) = \frac{10s(s+40)}{(s+1)(s+200)}$$

Sketch $|H(s)|_{s=j\omega}$ as fct. of ω on log-log axes.

(X-25)

$$H(\omega) = \frac{1 + j \frac{\omega}{10}}{(j\omega)(1 + j \frac{\omega}{10})^2 (1 + j \frac{\omega}{100})}$$

(X-26)


$$H(\omega) = \frac{(1 + j\omega)(1 + j\omega^3)}{(1 + j\frac{\omega}{5})(1 + j10\omega)}$$

Find $|H(100)|$, $|H(1)|$, $|H(3)|$

EE 202 NOTES

Second order response constants, formulas
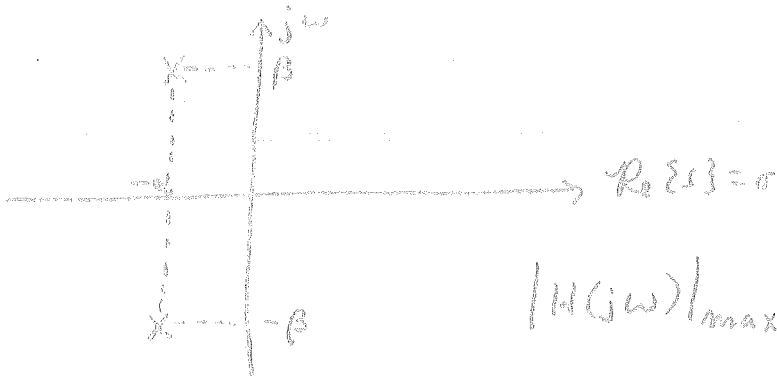
$$\begin{aligned}
 H(s) &= \frac{1}{s^2 + 2\alpha s + \omega_0^2} = \frac{1}{(s^2 + 2\alpha s + \alpha^2) + (\omega_0^2 - \alpha^2)} \\
 &= \frac{1}{(s + \alpha)^2 + \beta^2} \quad \text{assume } \omega_0 > \alpha \\
 &= \frac{1}{(s + \alpha + j\beta)(s + \alpha - j\beta)} \quad \beta = \sqrt{\omega_0^2 - \alpha^2}
 \end{aligned}$$



$$|H(j\omega)|_{\max} = \frac{1}{2\alpha\beta}$$

$$\omega_{\max} = \sqrt{\omega_0^2 - 2\alpha^2} = \omega_0 \sqrt{1 - 2\alpha^2/\omega_0^2}$$

$$\omega_U = \sqrt{\omega_M^2 + 2\alpha\beta}$$

$$\omega_L = \sqrt{\omega_M^2 - 2\alpha\beta}$$

$$BW = \omega_U - \omega_L$$

Approx. formulas; $\omega_0 \gg \alpha$
$\omega_M \doteq \omega_0$
$\omega_U \doteq \omega_0 + \alpha$
$\omega_L \doteq \omega_0 - \alpha$
$A_{\max} = 1/2\alpha\beta$


EE DEPT. IRE
TERRE HAUTE, IND.
MAY 14, 1970

EE 202
MORE HOMEWORK
DUE 5.17.70

X-27 SCOTT'S 633.18.31

X-28 SCOTT'S 634.18.34

X-29 Find $Z(s)$

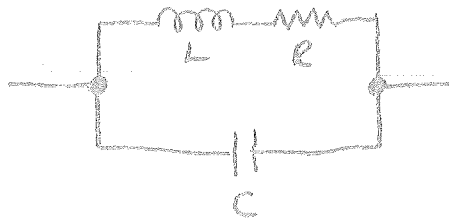

$$L = 88 \text{ mH}$$
$$C = 4 \mu\text{F}$$
$$R = 20 \Omega$$

- Find $Z(s)$
- Find $|Z(j\omega)|_{\max}$
- " ω_{\max} where $|Z(j\omega)|$ is max.

PROB. 16.12

X-17

$$H(s) = \frac{\frac{1}{2} \epsilon}{s^2 + \frac{\epsilon}{2}} = \frac{\omega_0^2}{(s + \alpha + j\beta)(s + \alpha - j\beta)}$$

$$\omega_0^2 = \frac{1}{LC} = 2$$

$$\alpha = \frac{R}{2L} = \frac{0.1}{2} = 0.05 \text{ sec}^{-1}$$

$$\beta = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{2 - 25 \times 10^{-4}} = \sqrt{1.9975} = \sqrt{2 - .0025}$$

$$= \sqrt{2} \cdot \sqrt{1 - .00125} \approx \sqrt{2} (1 - .000625) = \sqrt{2} (.999375)$$

$$\approx 1.4133294 \text{ rad/sec}$$


$$\omega_p = \sqrt{\omega_0^2 - 2\alpha^2} = 1.41244468 \text{ rad/sec}$$

$$\omega_{u1} = \sqrt{\omega_0^2 + 2\alpha\beta} = 1.4633294 \text{ rad/sec}$$

$$\omega_{u2} = \sqrt{\omega_0^2 - 2\alpha\beta} = 1.3633294 \text{ rad/sec}$$

$$|H|_{\text{max}} = \frac{\omega_0^2}{2\alpha\beta} = \frac{2}{2 \times 0.05 \times 1.4133294} = 14.15098$$

X-18 (Prob. 5.47, 16.12) in SCOTT

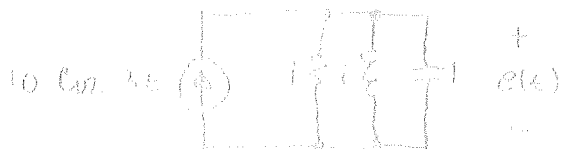

$$I = 10 \angle 0^\circ$$

$$\tilde{Z} = \frac{1}{\frac{1}{1} + \frac{j3}{1} + \frac{1}{3}} = \frac{j3}{1 - 9 + j3} = \frac{j3}{-8 + j3}$$

$$\tilde{Z} = \frac{3 \angle 90^\circ}{8.55 \angle 159.4^\circ} = 0.351 \angle -69.4^\circ$$

$$v(t) = 3.51 \cos(3t - 69.4^\circ) \text{ volts}$$

QUESTION 1

(15)

1.1.1. $\frac{1}{2} \times 1000 = 500$
 1.1.2. $\frac{1}{2} \times 1000 = 500$
 1.1.3. $\frac{1}{2} \times 1000 = 500$

1.2.1. $\frac{1}{2} \times 1000 = 500$
 1.2.2. $\frac{1}{2} \times 1000 = 500$
 1.2.3. $\frac{1}{2} \times 1000 = 500$

1.3.1. $\frac{1}{2} \times 1000 = 500$
 1.3.2. $\frac{1}{2} \times 1000 = 500$
 1.3.3. $\frac{1}{2} \times 1000 = 500$

2.1.1. $\frac{1}{2} \times 1000 = 500$
 2.1.2. $\frac{1}{2} \times 1000 = 500$
 2.1.3. $\frac{1}{2} \times 1000 = 500$

2.2.1. $\frac{1}{2} \times 1000 = 500$
 2.2.2. $\frac{1}{2} \times 1000 = 500$
 2.2.3. $\frac{1}{2} \times 1000 = 500$

2.3.1. $\frac{1}{2} \times 1000 = 500$
 2.3.2. $\frac{1}{2} \times 1000 = 500$
 2.3.3. $\frac{1}{2} \times 1000 = 500$


3.1.1. $\frac{1}{2} \times 1000 = 500$
 3.1.2. $\frac{1}{2} \times 1000 = 500$
 3.1.3. $\frac{1}{2} \times 1000 = 500$

3.2.1. $\frac{1}{2} \times 1000 = 500$
 3.2.2. $\frac{1}{2} \times 1000 = 500$
 3.2.3. $\frac{1}{2} \times 1000 = 500$

3.3.1. $\frac{1}{2} \times 1000 = 500$
 3.3.2. $\frac{1}{2} \times 1000 = 500$
 3.3.3. $\frac{1}{2} \times 1000 = 500$

3.4.1. $\frac{1}{2} \times 1000 = 500$
 3.4.2. $\frac{1}{2} \times 1000 = 500$
 3.4.3. $\frac{1}{2} \times 1000 = 500$

X-14

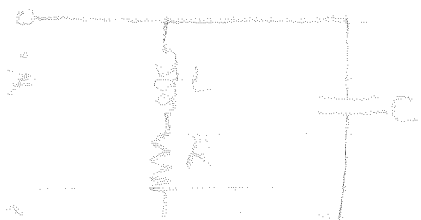

$L = 30 \times 10^{-3} \text{ H}$
 $C = 5 \times 10^{-6} \text{ F}$
 $R = 10 \Omega$

$$Z_{eq} = \frac{j\omega L + R + j\omega C}{j\omega L + R + j\omega C}$$

$$= \frac{R + j\omega C}{R + j(\omega C - \frac{1}{\omega L})}$$

AT DRIVING POINT:

at zero phase
always point

$$\frac{\omega R C}{C} = \frac{\omega C - \frac{1}{\omega L}}{R}$$

$$\omega R^2 L = \omega C - \frac{1}{\omega L}$$


$$\omega^2 R^2 L^2 = \omega^2 LC - 1$$

$$\omega^2 (R^2 L^2 - LC) = 1$$


$$\omega = \sqrt{\frac{1}{R^2 L^2 - LC}}$$

$$= \sqrt{\frac{1}{(10^2 \cdot 9 \cdot 10^{-4}) - (3 \cdot 10^{-2} \cdot 5 \cdot 10^{-7})}}$$
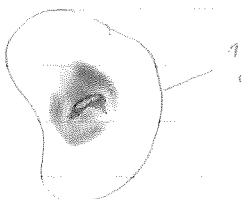
$$= \frac{1}{3} \cdot 10^2 = 33.3 \text{ RAD/SEC}$$



X-18)

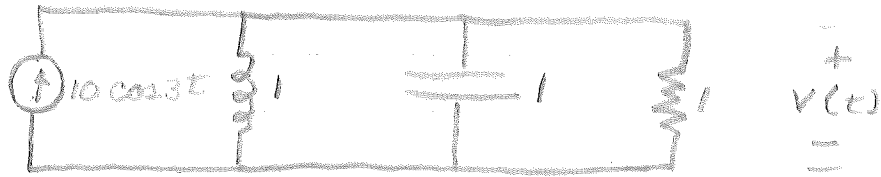

$$V = \frac{\frac{Z_C Z_L}{Z_C + Z_L}}{\frac{Z_C Z_L}{Z_C + Z_L} + Z_R} I$$

$$= \frac{Z_C Z_L I}{Z_C Z_L + Z_R (Z_C + Z_L)}$$

$$= \frac{(j\omega \frac{1}{j\omega}) I}{1 + (j\omega + \frac{1}{j\omega})}$$


$$\dot{I} = 10 \angle 0^\circ ; \omega = 3$$

$$\dot{V} = \frac{10 \angle 0^\circ}{1 + j(3 - .333)} = \frac{10 \angle 0^\circ}{1 + j(2.667)} = \frac{10 \angle 0^\circ}{2.95 \angle 69.45^\circ}$$

$$\dot{V} = 3.51 \angle -69.45^\circ = 3.51 \cos(3t - 69.45^\circ) \text{ volts}$$

✓

X-17)

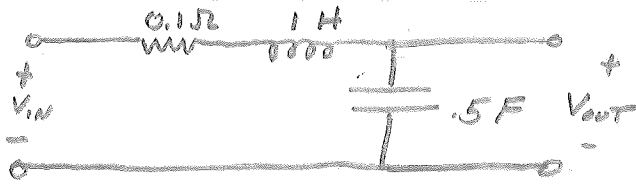

$$\begin{aligned}
 H(\omega) &= \frac{Z_C}{Z_C + Z_L + Z_R} \\
 &= \frac{j.5\omega}{j.5\omega + j\omega + .10} \\
 &= \frac{-.5\omega}{-.5\omega + 1 + .1j\omega} \\
 &= \frac{1}{1 - \frac{1}{.5\omega} - \frac{.1j}{.5}}
 \end{aligned}$$

$$\frac{1}{H(\omega)} = 1 - \frac{1}{.5\omega} - j.2$$

$$\begin{aligned}
 Y &= \left| \frac{1}{H(\omega)} \right| = \sqrt{\left(1 - \frac{1}{.5\omega}\right)^2 + .04} \\
 U &= 1 - \frac{1}{.5\omega} \quad \frac{dU}{d\omega} = \frac{1}{.5\omega^2} \\
 V &= U^2 + .04 \quad \frac{dV}{dU} = 2U = 2 - \frac{4}{\omega} \\
 Y &= V^{\frac{1}{2}} = \frac{1}{2} V^{-\frac{1}{2}} = \frac{1}{2\sqrt{U^2 + .04}} \\
 &= \frac{1}{2\sqrt{\left(1 - \frac{1}{.5\omega}\right)^2 + .04}}
 \end{aligned}$$

$$\frac{dY}{d\omega} = \frac{\frac{1}{.5\omega^2} \left(2 - \frac{4}{\omega}\right)}{2\sqrt{\left(1 - \frac{1}{.5\omega}\right)^2 + .04}} = 0$$

$$\frac{2 - \frac{4}{\omega}}{\omega^2 \sqrt{\left(1 - \frac{1}{.5\omega}\right)^2 + .04}} = 0$$

$$\frac{-2\omega + 4}{\omega^3 \sqrt{\left(1 - \frac{1}{.5\omega}\right)^2 + .04}} = 0$$

$H(\omega)$ MAX AT $\omega = 2$

$$b) \frac{H(\omega)}{H_{\max}(\omega)} = .707 = \frac{|1 - \frac{1}{5\omega} - j.2|}{2}$$

$$1.414 = \sqrt{\left(1 - \frac{1}{5\omega}\right)^2 + .04}$$

$$2 = 1 - \frac{4}{\omega} + \frac{1}{.25\omega^2} + .04$$

$$2\omega = \omega - 4 + \frac{4}{\omega} - .04\omega$$

$$2\omega^2 = \omega^2 - 4\omega + 4 - .04\omega^2$$

$$1.96\omega^2 + 4\omega - 4 = 0$$

$$\omega = \frac{-4 \pm \sqrt{16 + 31.4}}{2.92}$$

$$= \frac{-4 \pm \sqrt{77.4}}{2.92}$$

$$= \frac{-4 + 8.8}{2.92} = 1.64 \frac{\text{RAD}}{\text{SEC}}$$

$$c) P = 1 - \frac{1}{5\omega} - j.2$$


$$\omega = 2$$

$$P = 0 - j.2 = .2 \angle -90^\circ$$


$$H(\omega) = 5 \angle 90^\circ$$

ARG!

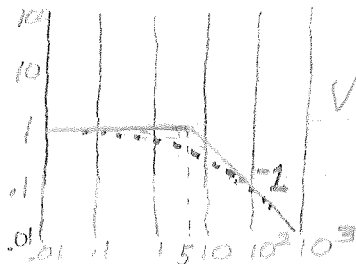
X-20) $H(\omega) = \frac{1}{1+j\frac{\omega}{5}}$



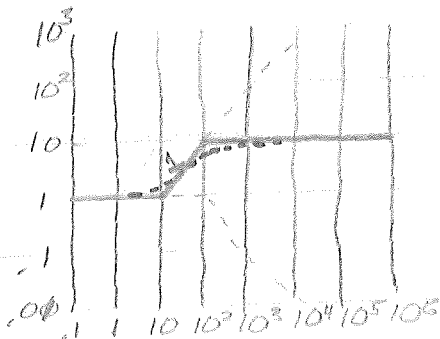X-21) $H(\omega) = \frac{1+j\omega/10}{1+j\omega/100}$



X-22) $H(s) \Big|_{s=j\omega} = \frac{s+5}{(s+10)(s+2)}$
 $H(\omega) = \frac{5+j\omega}{(10+j\omega)(2+j\omega)}$
 $= \frac{5(1+j\frac{\omega}{5})}{10(1+j\frac{\omega}{10}) \cdot 2(1+j\frac{\omega}{2})}$
 $= .25 \frac{(1+j\frac{\omega}{5})}{(1+j\frac{\omega}{10})(1+j\frac{\omega}{2})}$

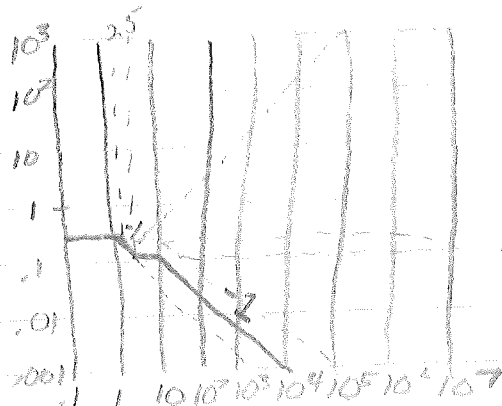


: value

2

X-26)
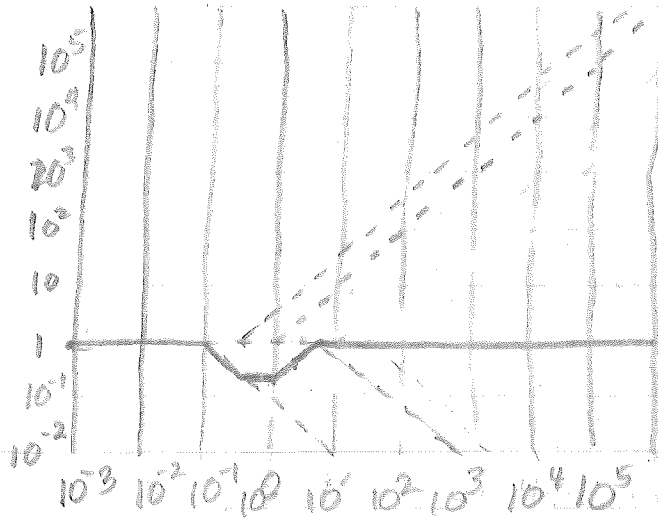
$$H(\omega) = \frac{(1 + j\omega)(1 + j\frac{\omega}{1/3})}{(1 + j\frac{\omega}{5})(1 + j\frac{\omega}{1/10})}$$




a) $H(100) = 0$

b) $5 = \frac{1}{H(1)} \Rightarrow H(1) = \frac{1}{5}$

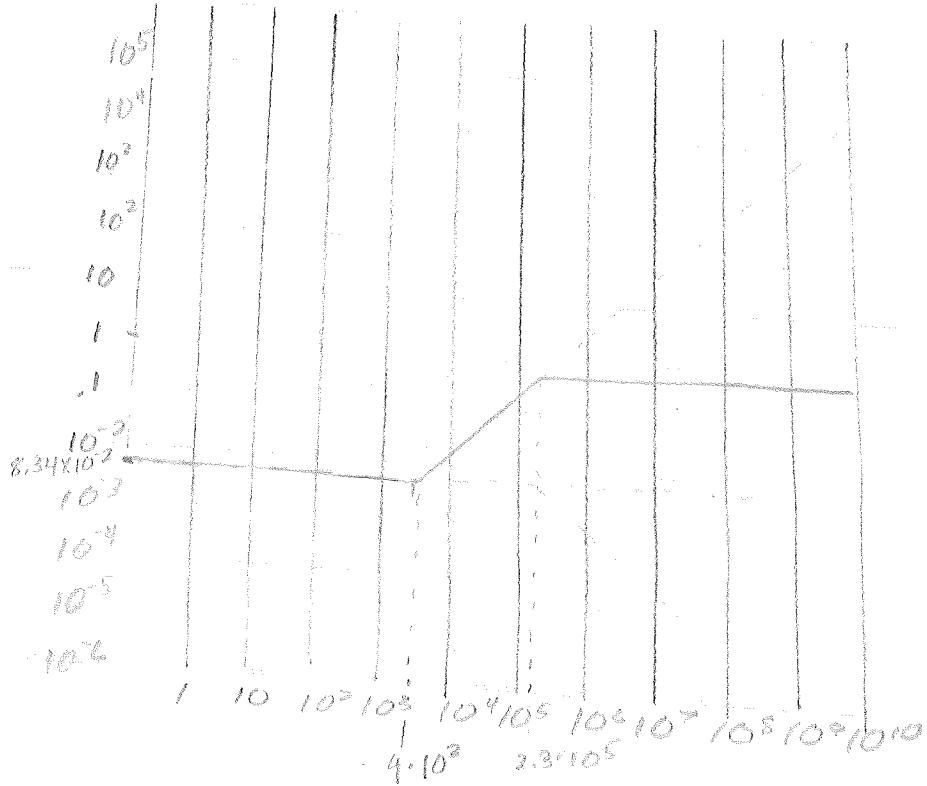c) $\frac{3}{1} = \frac{H(3)}{1/5} \Rightarrow H(3) = \frac{3}{5}$





2 ✓

X-24) $H(s) = \frac{10s(s+40)}{(s+1)(s+200)}$

$$H(\omega) = \frac{10\omega j (\omega j + 40)}{(\omega j + 1)(\omega j + 200)} = \frac{10\omega j \cdot 40 (1 + j \frac{\omega}{40})}{(1 + \omega j) 200 (1 + j \frac{\omega}{200})}$$


$$= \frac{j \frac{\omega}{12} (1 + j \frac{\omega}{40})}{(1 + \omega j) (1 + j \frac{\omega}{200})}$$



100
 10
 1
 0.1

100

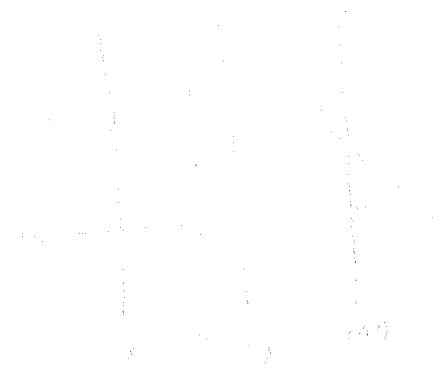
$$H(\omega) = \frac{1}{1 + j \frac{\omega}{10}}$$



100

$$H(\omega) = \frac{1 + j \frac{\omega}{10}}{1 + j \frac{\omega}{100}}$$

100

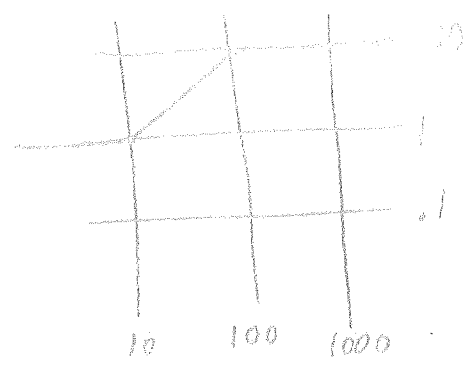


100

$$H(s) = \frac{s+5}{s^2+12s+20} = \frac{s+5}{s^2+12s+36-16}$$

$$\frac{s+5}{(s+6)^2 - 4^2} = \frac{s+5}{(s+6-4)(s+6+4)} = \frac{s+5}{(s+2)(s+10)}$$

100
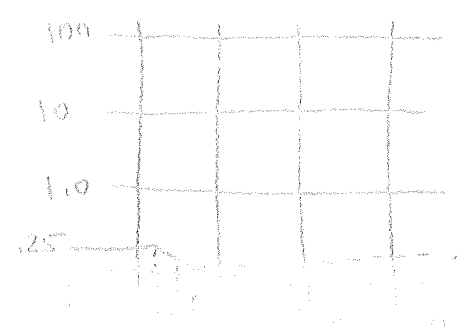
$$H(j\omega) = \frac{j\omega+5}{(j\omega+2)(j\omega+10)} = \frac{5}{2 \times 10} \frac{1 + j \frac{\omega}{5}}{(1 + j \frac{\omega}{2})(1 + j \frac{\omega}{10})}$$



$$\frac{25}{x} = \frac{5}{2}$$

$$x = \frac{5}{2} = 2.5$$

$x = 1 + \frac{1}{2} = 1.5$

EE 202
SOLUTIONS

1.73

$$\frac{V_o}{V_{in}} = H(\omega) = \frac{10}{20 + \frac{100 \left(\frac{10^6}{j\omega + 25} \right)}{100 + \frac{10^6}{j\omega + 25}}}$$

$$\Rightarrow \left(100 + \frac{10^6}{j\omega + 25} \right)$$

$$1000 + \frac{40 \cdot 10^6}{j\omega}$$

$$20 \left(100 + \frac{10^6}{j\omega + 25} \right) + \frac{400}{j\omega}$$

$$2000 + \frac{480 \cdot 10^6}{j\omega}$$


$$\frac{10^6 (30 + j\omega 1000)}{10^6 (20 + \frac{10^6}{j\omega + 25}) + \frac{400}{j\omega}}$$

$$= \frac{1}{12}$$

$$\frac{1 + j\omega (25) \cdot 10^{-6}}{1 + j\omega (4.17) \cdot 10^{-6}}$$

$$\frac{1}{2} \frac{1 + j \frac{\omega}{.04 \times 10^6}}{1 + j \frac{\omega}{0.24 \times 10^6}}$$

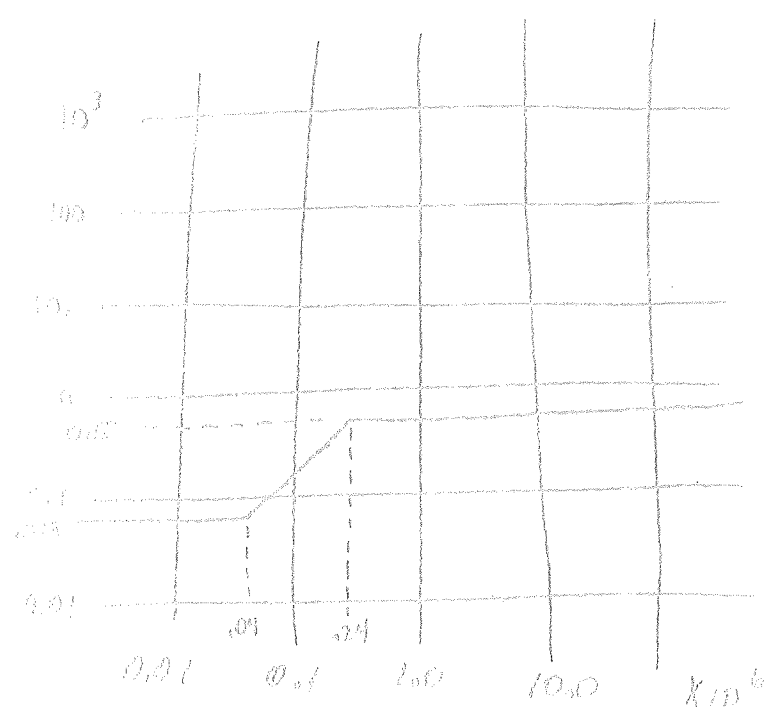1013 $1 + j \frac{\omega}{0.24 \times 10^6}$




$$H(s) =$$

$$\frac{200}{(s+1)(s+200)}$$

$$200(1+s)^{-1}(1+\frac{s}{200})^{-1}$$

$$2(j\omega)(1+j\frac{\omega}{40})$$

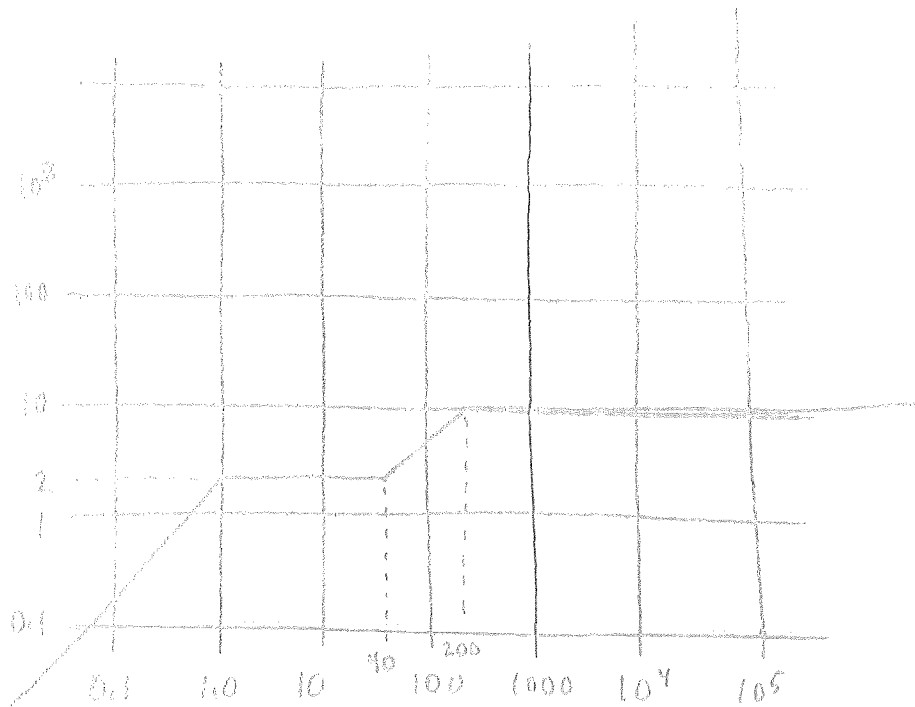
$$\frac{2(j\omega)(1+j\frac{\omega}{40})}{(1+j\frac{\omega}{1})(1+j\frac{\omega}{200})}$$



X 35

$$H(\omega) =$$
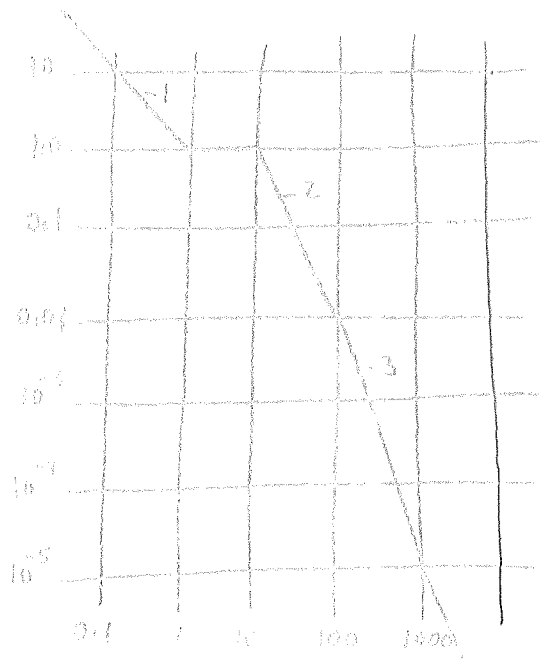
$$\frac{1 + \frac{j\omega}{1}}{j\omega(1 + \frac{j\omega}{10})^2(1 + \frac{j\omega}{100})}$$



$$H(100) = \frac{(1+j20)(1+j20)}{(1+j20)(1+j1000)} \cdot \frac{(100/100) \angle 0^\circ}{(20/89.45^\circ)(1000/45^\circ)}$$

$$= \boxed{1.5 \angle -4^\circ}$$

$$H(1) = \frac{(1+j1)(1+j3)}{(1+j0.2)(1+j10)} = \frac{(3.16 \angle 45^\circ)(3.16 \angle 71.55^\circ)}{(1.02 \angle 11.0^\circ)(10.05 \angle 84.3^\circ)}$$

$$= \frac{4.36}{10.47} \boxed{0.436 \angle 20.95^\circ}$$


$$H(3) = \frac{(1+j3)(1+j9)}{(1+j.6)(1+j60)} = \frac{(3.16 \angle 71.55^\circ)(9.15 \angle 83.65^\circ)}{(1.165 \angle 31^\circ)(60 \angle 89.05^\circ)}$$

$$= \boxed{0.408 \angle 35.15^\circ}$$

EE 202
SOLUTIONS

(a) (continued X-24)

$$H(s) = \frac{s+3}{(s+4)(s+2)}$$

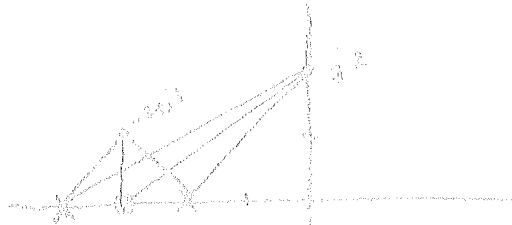

(b)

$$H(-3+j1) = \frac{1}{(\sqrt{2})^2} \angle (90 - 45 - 135) = \boxed{0.5 \angle -90^\circ}$$

$$(c) H(j2) = \frac{\sqrt{3}}{(2\sqrt{2})(\sqrt{20})} \angle \left(\tan^{-1} \frac{2}{3} - \tan^{-1} \frac{2}{2} - \tan^{-1} \frac{1}{2} \right)$$

$$0.285 \angle 34.7 - 45 - 26.6^\circ = \boxed{0.285 \angle -36.9^\circ}$$

Ex 2.2
Answers

(1) $\omega = 2\pi \times 2000$ rad/sec

$$\frac{10^6}{2\pi \times 2000} = \frac{A}{2\pi \times 2000 \times 10^6}$$

$A = 1000$
 $\omega = 10^6$

$$\frac{1000}{20\pi} = \frac{A}{2\pi \times 2000 \times 10^6} = 10^{-7}$$

$$(2) \omega = \sqrt{10^{12} - 25 \times 10^6} = 10^6 \sqrt{1 - \frac{25}{10^6}}$$

$$= 10^6 \left(1 - \frac{12.5}{10^6}\right) = 10^6 - 12.5 = 999987.5 \frac{\text{rad}}{\text{sec}}$$

$$(3) \omega = \sqrt{10^{12} + 20\pi} = 1,000,012.5 \frac{\text{rad}}{\text{sec}}$$

$$(4) \omega = 4,999,974.9 \frac{\text{rad}}{\text{sec}}$$

$$(5) \omega = 1,000,012.5 \frac{\text{rad}}{\text{sec}}$$

$$(6) \frac{\omega_{max}}{\omega_{min}} = 99.996$$

Resonance

1. ω_0 (Resonance frequency) (rad/s)

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 10^{-8}}} = \frac{1}{\sqrt{10^{-11}}} = \frac{1}{10^{-5.5}} = 10^{5.5} = 3.16 \times 10^5 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 10^{-8}}} = \frac{1}{10^{-5.5}} = 10^{5.5} = 3.16 \times 10^5 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 10^{-8}}} = \frac{1}{10^{-5.5}} = 10^{5.5} = 3.16 \times 10^5 \text{ rad/s}$$

$$\omega_0 = 3.16 \times 10^5 \text{ rad/s} \quad \omega_0 = \sqrt{10} \times 10^5 = 3.16 \times 10^5 \text{ rad/s}$$

$$\omega_0 = \sqrt{\omega_0^2 - 2\omega^2} = 2.5 \times 10^5 \sqrt{10^{17} - 2.5 \times 10^6}$$

$$= 3.16 \times 10^5 \sqrt{1 - \frac{2.5}{10^{11}}} = 3.16 \times 10^5 \sqrt{1 - \frac{2.5}{10^{10}}}$$

$$\approx 3.16 \times 10^5 (1 - 1.25 \times 10^{-10}) \approx \omega_0 = 3.16 \times 10^5 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 10^{-8}}} = \frac{1}{10^{-5.5}} = 10^{5.5} = 3.16 \times 10^5 \text{ rad/s}$$

$$\omega_0 = \sqrt{\omega_0^2 - 2\omega^2} = \sqrt{10^{17} - 2 \times 0.25 \times 10^{16}} = \sqrt{10^{17} (1 - 0.05)}$$

$$= \sqrt{10^{17} (1 - 0.05)} = \sqrt{10^{17} (0.95)} = 3.08 \times 10^5 \text{ rad/s}$$

BOB MARKS
EE-202

Department of Electrical Engineering
Rose Polytechnic Institute
Terre Haute, Indiana
May 6, 1970

EE 202

Homework

10


E-1. Plot on log-log graph paper $|H(\omega)|$ for

$$H(\omega) = \frac{(1 + j\omega)(1 + j \frac{\omega}{100})(1 + j \frac{\omega}{10,000})}{(1 + j \frac{\omega}{10})(1 + j \frac{\omega}{1000})(1 + j \frac{\omega}{10^5})}$$

Plot for 10 equally spaced frequencies per decade for a frequency range from 0.1 Hz to 1 MHz. Also plot $\theta_H(\omega)$ for the same frequencies on semi-log.

X-26)
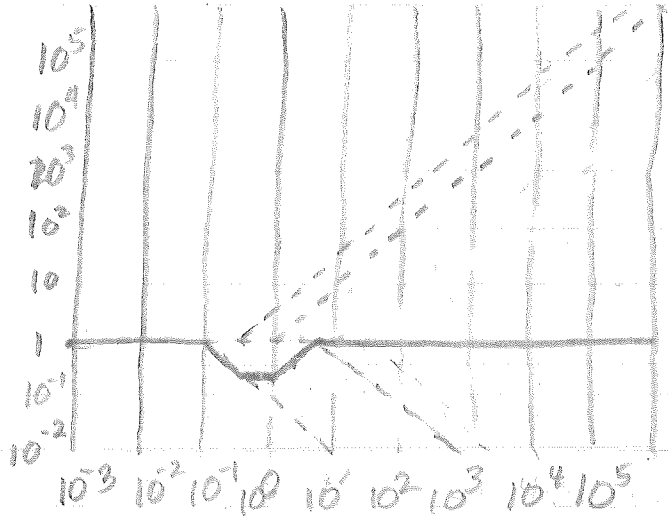
$$H(\omega) = \frac{(1 + j\omega)(1 + j\frac{\omega}{1/3})}{(1 + j\frac{\omega}{5})(1 + j\frac{\omega}{1/10})}$$



a) $H(100) = 0$

b) $5 = \frac{1}{H(1)} \Rightarrow H(1) = \frac{1}{5}$

c) $\frac{3}{1} = \frac{H(3)}{1/5} \Rightarrow H(3) = \frac{3}{5}$




```

// JOB T      08069
// FORTRAN IV
*IOCS(1132 PRINTER,CARD)
* EXTENDED PRECISION
  WRITE(3,30)
30 FORMAT(2X,'BODE DIAGRAM DATA-EE202',/)
  WRITE(3,31)
31 FORMAT(7X,'FREQ',7X,'LOG FREQ',5X,'ANG FREQ',5X,'LOG A FREQ',6X,'H
5(W)',6X,'LOG H(W)', 6X,'AH(W)-RAD',5X,'DEGREES')
  C=ALOG(10.)
  RT=10.** (1./10.)
  F=0.1
  T=10.
  PI=3.1415926535898
  DO 50 J=1,71
  M=J-1
  W=F*2.**PI
  WS=W**2.
  HW=(((1.+WS)*(1.+WS/(T**4.))* (1.+WS/(T**8.)))/((1.+WS/100.)*(1.+WS
2/(T**6.))* (1.+WS/(T**T))))**0.5
  AHW=ATAN(W)+ATAN(W/100.)+ATAN(W/10000.)-ATAN(W/10.)-ATAN(W/1000.)-
2ATAN(W/100000.)
  AID=AHW*180./PI
  TLF=ALOG(F)/C
  TLW=ALOG(W)/C
  TLHW=ALOG(HW)/C
  WRITE(3,20) M,F,TLF,W,TLW,HW,TLHW,AHW,AID
20 FORMAT(13,1X,E12.5,1X,E12.5,1X,E12.5,1X,E12.5,1X,E12.5,1X,E12.5,1X
5,E12.5,1X,E12.5)
  F=F*RT
50 CONTINUE
  STOP
  END
// XEQ

```

// JOB T 08069

// FORTRAN IV
 *IOCS(1132 PRINTER,CARD)
 * EXTENDED PRECISION

FEATURES SUPPORTED
 EXTENDED PRECISION
 IOCS

CORE REQUIREMENTS FOR
 COMMON 0 VARIABLES 78 PROGRAM 430

END OF COMPILATION

// XEQ

BODE DIAGRAM DATA-EE202

	FREQ	LOG FREQ	ANG FREQ	LOG A FREQ	H(W)	LOG H(W)	AH(W)-RAD	DEGREES
0	0.10000E 00	-0.10000E 01	0.62831E 00	-0.20182E 00	0.11787E 01	0.71406E-01	0.50394E 00	0.28873E 02
1	0.12589E 00	-0.90000E 00	0.79100E 00	-0.10182E 00	0.12710E 01	0.10417E 00	0.59748E 00	0.34233E 02
2	0.15848E 00	-0.80000E 00	0.99581E 00	-0.18201E-02	0.14043E 01	0.14748E 00	0.69309E 00	0.39711E 02
3	0.19952E 00	-0.69999E 00	0.12536E 01	0.98179E-01	0.15913E 01	0.20175E 00	0.78416E 00	0.44929E 02
4	0.25118E 00	-0.59999E 00	0.15782E 01	0.19817E 00	0.18457E 01	0.26618E 00	0.86384E 00	0.49494E 02
5	0.31622E 00	-0.49999E 00	0.19869E 01	0.29817E 00	0.21821E 01	0.33888E 00	0.92643E 00	0.53081E 02
6	0.39810E 00	-0.39999E 00	0.25013E 01	0.39817E 00	0.26141E 01	0.41733E 00	0.96810E 00	0.55468E 02
7	0.50118E 00	-0.29999E 00	0.31490E 01	0.49817E 00	0.31529E 01	0.49872E 00	0.98685E 00	0.56542E 02
8	0.63095E 00	-0.19999E 00	0.39644E 01	0.59817E 00	0.38037E 01	0.58021E 00	0.98228E 00	0.56280E 02
9	0.79432E 00	-0.99999E-01	0.49909E 01	0.69817E 00	0.45599E 01	0.65896E 00	0.95545E 00	0.54743E 02
10	0.10000E 01	0.32357E-08	0.62831E 01	0.79817E 00	0.53976E 01	0.73220E 00	0.90901E 00	0.52082E 02
11	0.12589E 01	0.10000E 00	0.79100E 01	0.89817E 00	0.62725E 01	0.79744E 00	0.84754E 00	0.48560E 02
12	0.15848E 01	0.20000E 00	0.99581E 01	0.99817E 00	0.71264E 01	0.85287E 00	0.77760E 00	0.44553E 02
13	0.19952E 01	0.30000E 00	0.12536E 02	0.10981E 01	0.79031E 01	0.89780E 00	0.70702E 00	0.40509E 02
14	0.25118E 01	0.40000E 00	0.15782E 02	0.11981E 01	0.85677E 01	0.93286E 00	0.64366E 00	0.36879E 02
15	0.31622E 01	0.50000E 00	0.19869E 02	0.12981E 01	0.91168E 01	0.95984E 00	0.59405E 00	0.34036E 02
16	0.39810E 01	0.60000E 00	0.25013E 02	0.13981E 01	0.95762E 01	0.98119E 00	0.56271E 00	0.32240E 02
17	0.50118E 01	0.70000E 00	0.31490E 02	0.14981E 01	0.99925E 01	0.99967E 00	0.55216E 00	0.31636E 02
18	0.63095E 01	0.80000E 00	0.39644E 02	0.15981E 01	0.10425E 02	0.10181E 01	0.56325E 00	0.32271E 02
19	0.79432E 01	0.90000E 00	0.49909E 02	0.16981E 01	0.10947E 02	0.10393E 01	0.59525E 00	0.34105E 02
20	0.10000E 02	0.10000E 01	0.62831E 02	0.17981E 01	0.11642E 02	0.10660E 01	0.64580E 00	0.37001E 02
21	0.12589E 02	0.11000E 01	0.79100E 02	0.18981E 01	0.12611E 02	0.11007E 01	0.71052E 00	0.40710E 02
22	0.15848E 02	0.12000E 01	0.99581E 02	0.19981E 01	0.13974E 02	0.11453E 01	0.78305E 00	0.44865E 02
23	0.19952E 02	0.13000E 01	0.12536E 03	0.20981E 01	0.15863E 02	0.12003E 01	0.85566E 00	0.49026E 02
24	0.25118E 02	0.14000E 01	0.15782E 03	0.21981E 01	0.18421E 02	0.12653E 01	0.92063E 00	0.52748E 02
25	0.31622E 02	0.15000E 01	0.19869E 03	0.22981E 01	0.21794E 02	0.13383E 01	0.97151E 00	0.55663E 02
26	0.39810E 02	0.16000E 01	0.25013E 03	0.23981E 01	0.26120E 02	0.14169E 01	0.10038E 01	0.57515E 02
27	0.50118E 02	0.17000E 01	0.31490E 03	0.24981E 01	0.31514E 02	0.14985E 01	0.10151E 01	0.58163E 02
28	0.63095E 02	0.18000E 01	0.39644E 03	0.25981E 01	0.38025E 02	0.15800E 01	0.10046E 01	0.57560E 02
29	0.79432E 02	0.19000E 01	0.49909E 03	0.26981E 01	0.45590E 02	0.16588E 01	0.97303E 00	0.55750E 02
30	0.10000E 03	0.20000E 01	0.62831E 03	0.27981E 01	0.53969E 02	0.17321E 01	0.92277E 00	0.52870E 02
31	0.12589E 03	0.21000E 01	0.79100E 03	0.28981E 01	0.62720E 02	0.17974E 01	0.85821E 00	0.49171E 02
32	0.15848E 03	0.22000E 01	0.99581E 03	0.29981E 01	0.71260E 02	0.18528E 01	0.78574E 00	0.45019E 02
33	0.19952E 03	0.23000E 01	0.12536E 04	0.30981E 01	0.79029E 02	0.18977E 01	0.71307E 00	0.40856E 02
34	0.25118E 03	0.24000E 01	0.15782E 04	0.31981E 01	0.85676E 02	0.19328E 01	0.64794E 00	0.37124E 02
35	0.31622E 03	0.25000E 01	0.19869E 04	0.32981E 01	0.91167E 02	0.19598E 01	0.59679E 00	0.34193E 02
36	0.39810E 03	0.26000E 01	0.25013E 04	0.33981E 01	0.95761E 02	0.19811E 01	0.56405E 00	0.32318E 02
37	0.50118E 03	0.27000E 01	0.31490E 04	0.34981E 01	0.99924E 02	0.19996E 01	0.55219E 00	0.31638E 02

38	0.63095E 03	0.28000E 01	0.39644E 04	0.35981E 01	0.10425E 03	0.20180E 01	0.56195E 00	0.32197E 02
39	0.79432E 03	0.29000E 01	0.49909E 04	0.36981E 01	0.10947E 03	0.20392E 01	0.59256E 00	0.33951E 02
40	0.10000E 04	0.30000E 01	0.62831E 04	0.37981E 01	0.11641E 03	0.20660E 01	0.64158E 00	0.36759E 02
41	0.12589E 04	0.31000E 01	0.79100E 04	0.38981E 01	0.12611E 03	0.21007E 01	0.70454E 00	0.40367E 02
42	0.15848E 04	0.32000E 01	0.99581E 04	0.39981E 01	0.13973E 03	0.21453E 01	0.77499E 00	0.44403E 02
43	0.19952E 04	0.33000E 01	0.12536E 05	0.40981E 01	0.15861E 03	0.22003E 01	0.84510E 00	0.48420E 02
44	0.25118E 04	0.34000E 01	0.15782E 05	0.41981E 01	0.18418E 03	0.22652E 01	0.90700E 00	0.51967E 02
45	0.31622E 04	0.35000E 01	0.19869E 05	0.42981E 01	0.21789E 03	0.23382E 01	0.95408E 00	0.54665E 02
46	0.39810E 04	0.36000E 01	0.25013E 05	0.43981E 01	0.26112E 03	0.24168E 01	0.98169E 00	0.56246E 02
47	0.50118E 04	0.37000E 01	0.31490E 05	0.44981E 01	0.31498E 03	0.24982E 01	0.98709E 00	0.56556E 02
48	0.63095E 04	0.38000E 01	0.39644E 05	0.45981E 01	0.37996E 03	0.25797E 01	0.96919E 00	0.55530E 02
49	0.79432E 04	0.39000E 01	0.49909E 05	0.46981E 01	0.45534E 03	0.26583E 01	0.92834E 00	0.53190E 02
50	0.10000E 05	0.40000E 01	0.62831E 05	0.47981E 01	0.53864E 03	0.27313E 01	0.86644E 00	0.49643E 02
51	0.12589E 05	0.41000E 01	0.79100E 05	0.48981E 01	0.62527E 03	0.27960E 01	0.78730E 00	0.45108E 02
52	0.15848E 05	0.42000E 01	0.99581E 05	0.49981E 01	0.70913E 03	0.28507E 01	0.69653E 00	0.39908E 02
53	0.19952E 05	0.43000E 01	0.12536E 06	0.50981E 01	0.78421E 03	0.28944E 01	0.60096E 00	0.34432E 02
54	0.25118E 05	0.44000E 01	0.15782E 06	0.51981E 01	0.84639E 03	0.29275E 01	0.50724E 00	0.29063E 02
55	0.31622E 05	0.45000E 01	0.19869E 06	0.52981E 01	0.89436E 03	0.29515E 01	0.42056E 00	0.24096E 02
56	0.39810E 05	0.46000E 01	0.25013E 06	0.53981E 01	0.92928E 03	0.29681E 01	0.34399E 00	0.19709E 02
57	0.50118E 05	0.47000E 01	0.31490E 06	0.54981E 01	0.95357E 03	0.29793E 01	0.27862E 00	0.15964E 02
58	0.63095E 05	0.48000E 01	0.39644E 06	0.55981E 01	0.96993E 03	0.29867E 01	0.22416E 00	0.12843E 02
59	0.79432E 05	0.49000E 01	0.49909E 06	0.56981E 01	0.98070E 03	0.29915E 01	0.17953E 00	0.10286E 02
60	0.10000E 06	0.50000E 01	0.62831E 06	0.57981E 01	0.98769E 03	0.29946E 01	0.14336E 00	0.82141E 01
61	0.12589E 06	0.51000E 01	0.79100E 06	0.58981E 01	0.99218E 03	0.29965E 01	0.11426E 00	0.65467E 01
62	0.15848E 06	0.52000E 01	0.99581E 06	0.59981E 01	0.99504E 03	0.29978E 01	0.90955E-01	0.52113E 01
63	0.19952E 06	0.53000E 01	0.12536E 07	0.60981E 01	0.99686E 03	0.29986E 01	0.72346E-01	0.41451E 01
64	0.25118E 06	0.54000E 01	0.15782E 07	0.61981E 01	0.99801E 03	0.29991E 01	0.57516E-01	0.32954E 01
65	0.31622E 06	0.55000E 01	0.19869E 07	0.62981E 01	0.99874E 03	0.29994E 01	0.45711E-01	0.26190E 01
66	0.39810E 06	0.56000E 01	0.25013E 07	0.63981E 01	0.99920E 03	0.29996E 01	0.36322E-01	0.20811E 01
67	0.50118E 06	0.57000E 01	0.31490E 07	0.64981E 01	0.99950E 03	0.29997E 01	0.28858E-01	0.16534E 01
68	0.63095E 06	0.58000E 01	0.39644E 07	0.65981E 01	0.99968E 03	0.29998E 01	0.22925E-01	0.13135E 01
69	0.79432E 06	0.59000E 01	0.49909E 07	0.66981E 01	0.99980E 03	0.29999E 01	0.18212E-01	0.10434E 01
70	0.10000E 07	0.60000E 01	0.62831E 07	0.67981E 01	0.99987E 03	0.29999E 01	0.14467E-01	0.82891E 00


EXECUTION TIME 0047 SEC

Cross Section
10 Squares to the inch

R 2470-10

VERSION 01
DATE 11/11/11

$H(\omega)$

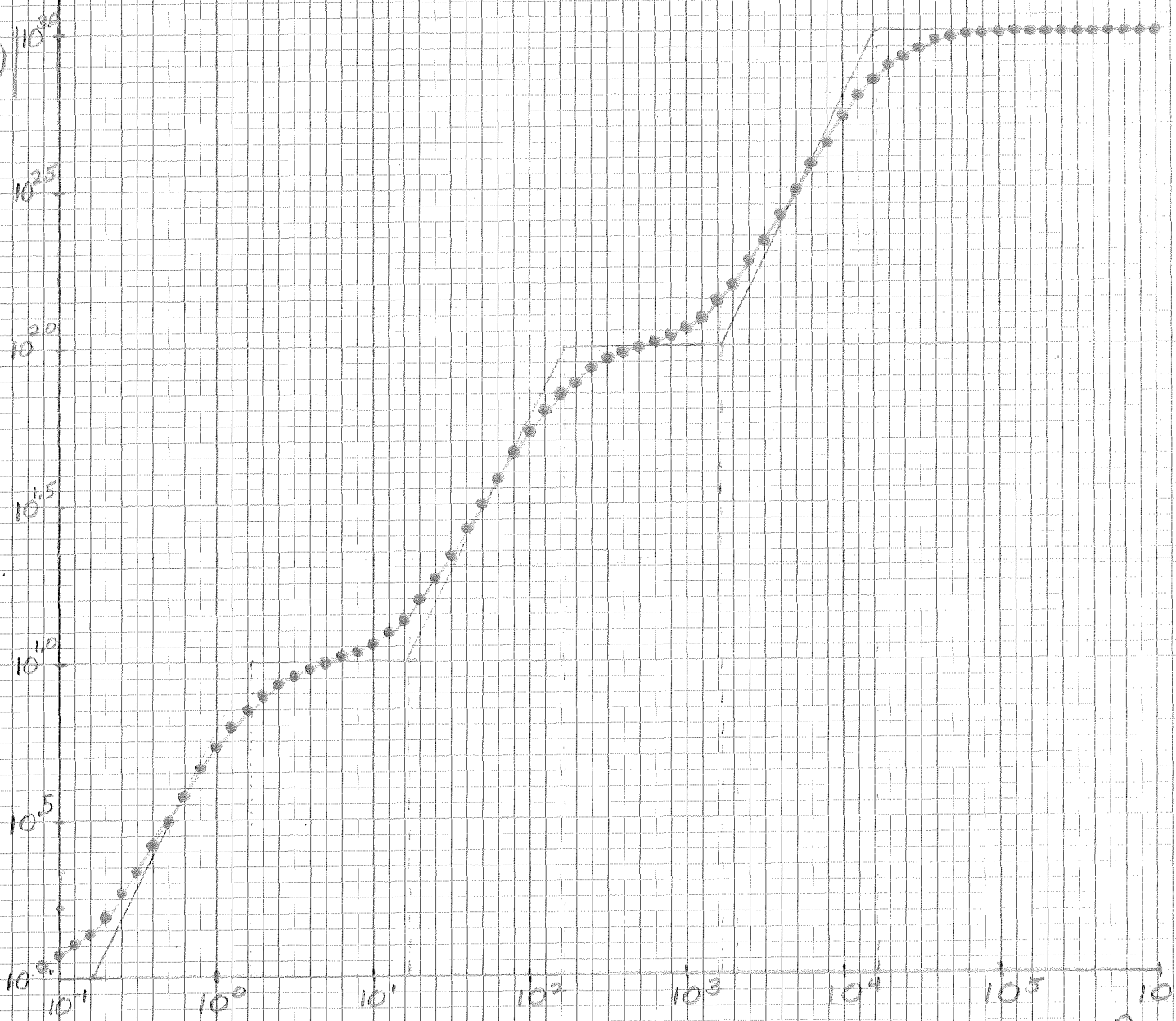


f
(Hz)

VERSION 10 LINE R 2470-10
CROSS SECTION
10 SQUARES TO THE INCH


$\Theta(\omega)$

70
60
50
40
30
20
10

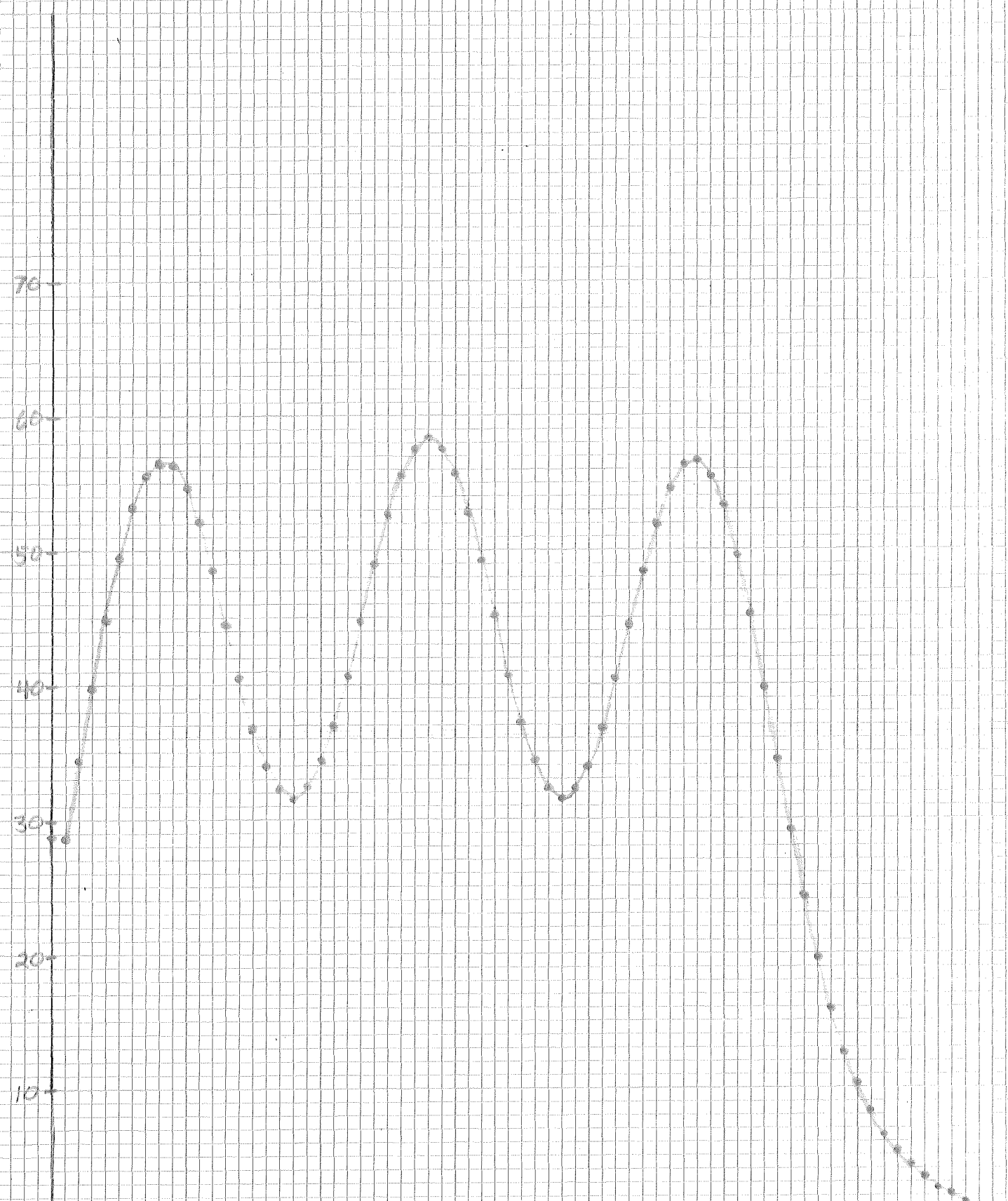10^{-1} 10^0 10^1 10^2 10^3 10^4 10^5 10^6
 f (Hz)



...istance by ...

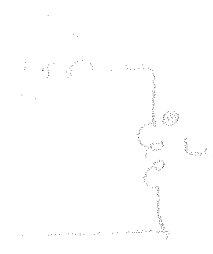

$$L_1 = 2 \text{ H}$$

$$L_2 = 5 \text{ H}$$


$$L_3 = 6 \text{ H}$$

$$L_4 = 3 \text{ H}$$

$$M_{14} = 2 \text{ H}$$

$$M_{23} = 5.2 \text{ H}$$

the circuit shown.

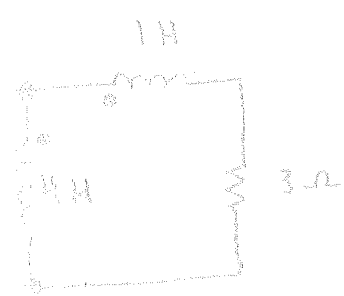


$$\omega = 2 \text{ rad/sec}$$

$$M = 2 \text{ H}$$


2016 6 8-10

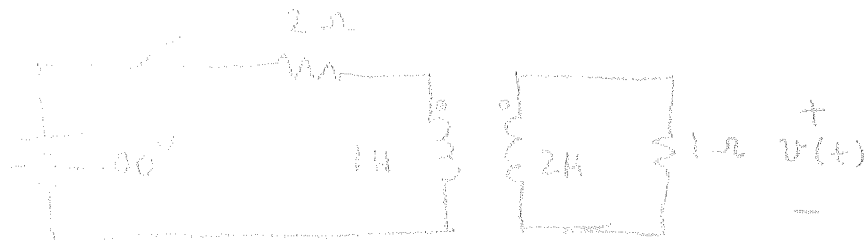X-40] The switch is closed at $t=0$. Solve for $v(t)$



$$M = \sqrt{2} \text{ H}$$

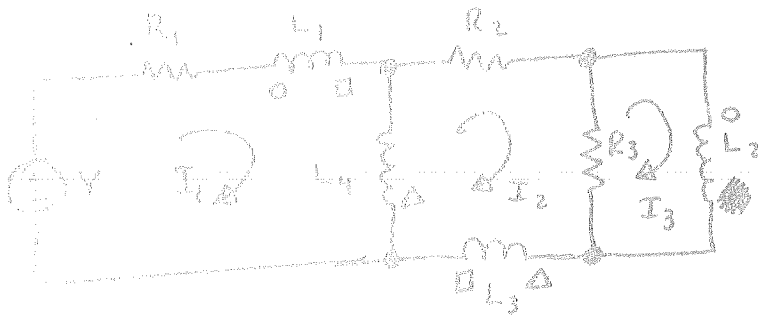X-41] Write the equations for the mesh currents



$$M_{12} \neq 0$$

$$M_{34} \neq 0$$

$$M_{23} \neq 0$$

2.35
 resolution

2.35) f_{max} - class notes

$$A_m = \frac{2A}{T} \frac{\sin \frac{n\pi A}{T}}{\frac{n\pi A}{T}}$$

where $A = 10^{-6}$
 $T = 10^{-3}$

$$A_m = 2 \times 10^{-9} \frac{\sin 10^{-3} n\pi}{10^{-3} n\pi}$$

$\Rightarrow A_0 = 2 \times 10^{-9}$

$$A_m = \frac{2}{n\pi} \sin 10^{-3} n\pi = \frac{.636}{n} \sin n(1.0031415)$$

n	$\frac{.636}{n}$	$\sin n(1.0031415)$	$\sin \theta$	A_m
1	.636	.0031415	← same	1.9999671
2	.318	.006283	0	1.9999868
3	.212	.009423	0	1.9999704
4	.159	.012567	0	1.9999473
5	.127	.0157	0	1.9999177
6	.106	.01885	0	1.999881
7	.091	.022	0	1.999839
8	.079	.0257	0	1.999789
9	.071	.0283	0	1.999783
10	.064	.0314	0	1.999671

NOTE:
 NEEDED
 COMPUTER
 TO FIGURE
 THESE !!

$$= [e^{j2\pi n} - e^0(0+1)]$$

$$= [e^{j2\pi n} - 1]$$

$$(2) \text{ } z = e^{j2\pi n}$$

$$= [e^{j2\pi n} (1 + j2\pi n) - 1]$$

$$= [1 + 2\pi n \sin 2\pi n]$$

$$\left(\frac{\sin 2\pi n}{2\pi n} \right)$$

$$= \left(\frac{1}{2} \right) \cdot 2 = \boxed{1}$$

\Rightarrow odd bet. except for d-c value

inf

$$i_{a1}(t) = \frac{2 \cos 2\pi t}{2\pi t} \quad \text{for } 0 \leq t \leq 1/\pi$$

$$i_{a1}(t) = \frac{2 \cos 2\pi t}{2\pi t} \quad \text{for } 0 \leq t \leq 1/\pi$$

$$i_{a1}(t) = \frac{1}{\pi t}$$

$$i_{a1}(t) = \frac{1}{\pi t}$$

18-31

$\omega_s = 2000$ rad/sec instead of $2\pi/s$ as stated above.
 However this doesn't affect the components

Q.0. Finding average value of filter in d-c + fundamental

$$i_{a1}(t) = \frac{1}{2} - \frac{1}{\pi} \sin 2000t$$